

PRACTICAL

ELECTRONICS

NOVEMBER 1972

20p



Simple

AUDIO SIGNAL GENERATOR

SPECIAL SUPPLEMENT!

Electronic **MUSICAL
INSTRUMENTS**

A SURVEY OF THE COMMERCIAL SCENE



Why take the risk?

of damage to expensive transistors and integrated circuits, when soldering?

Use Antex low-leakage soldering irons



220-240 Volts or
100-120 Volts

Model X25

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with it's truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8".
2 other bits available 3/32" and 3/16".

Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be removed

PRICE: £1.75 (rec. retail)
Suitable for production work and as a general purpose iron

Model CCN 220 volts or 240 volts

The 15 watt miniature model CCN. also has negligible leakage.

Test voltage 4000v. A.C.
Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"

4 other bits available
1/8", 3/16" 1/4" and 1/16"

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8"

PRICE: £1.95 (rec. retail)

A SELECTION OF OTHER SOLDERING EQUIPMENT.



MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24
PRICE: £1.70 (rec. retail)

MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.
PRICE: £1.70 (rec. retail)



MODEL G

18 Watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.
PRICE: £1.83 (rec. retail)

MODEL SK.1 KIT



contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £2.75
(Rec. retail)

MODEL SK.2 KIT

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32",

heat sink, solder and booklet "How to Solder"



PRICE £2.40
(Rec. retail)



MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder."

PRICE £1.95
(Rec. retail)



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from —
ANTEX LTD. FREEPOST
(no stamp required) **Plymouth**
PL1 1BR Tel: 0752 67377

- Please send the ANTEX colour catalogue.
 Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME _____

ADDRESS _____

Connoisseur

B.D.2 Press Button Speed Change Turntable

Now a new development on the well established Connoisseur BD2 belt drive turntable - press button speed change. This new development is exciting news for the enthusiast and comes as part of an integrated turntable and pickup arm assembly which also features a special version of the popular SAU2 arm. This is now fitted with a new lifting device which gives improved lowering characteristics, the headshell allowing for lateral adjustment of the cartridge. The BD2 is supplied as a chassis unit or spring mounted on a wooden plinth with dust cover.

S.A.U.2 Pick-up Arm

Recognised as one of today's most advanced pick-up arms it features

- Auto-bias Compensator
- Hydraulic Lowering Device
- Precision Balance
- New Adjustable Head Shell.



B.D.1 Turntable Kit




The B.D.1, well known for its superb performance and quality two speed working through a flexible belt drive system is now available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.

A.R.SUGDEN & CO.(ENGINEERS) LTD.

Market Street, BRIGHOUSE HD6 1DX. Telephone: Brighouse 2142. Telegrams & Cables: Connoisseur, Brighouse.

FAULT LOCATION

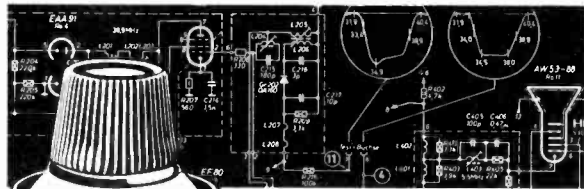

KONTAKT "Cold Spray 75"

For rapid and effective fault location

Non-toxic, non-inflammable, Cold Spray 75 is a chemically inert coolant capable of producing temperatures of down to -42 centigrade. It can also be used to prevent heat damage during soldering processes, for the rapid freezing of small articles for biological and technical purposes and the prompt location of hairline cracks and other faults in temperature dependent components.

Other Kontakt products:


Kontakt 60 and Kontakt 61 for relay contact cleaning; Plastic Spray 70, transparent protective lacquer; Insulating Spray 72; Kontakt WL, Spray Wash; Antistatic Spray 100, Antistatic agent for plastics; Politur 80, Polish and cleaner; Fluid 101, Dehydrating Fluid.

Details from U.K. distributors:

Special Products Distributors Ltd.

81 Piccadilly, London, W.1. Tel. 01-629 9556

Are you alright for Jacks?

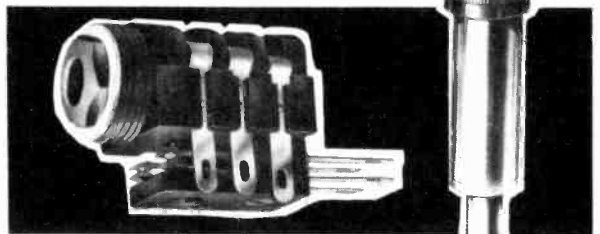

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes... plugs in both screened and unscreened versions... socket bodies in high melting point thermoplastic... several unique features (some protected by UK and US Patents)... Post Office and NATO specifications.


If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!



RENDAR®

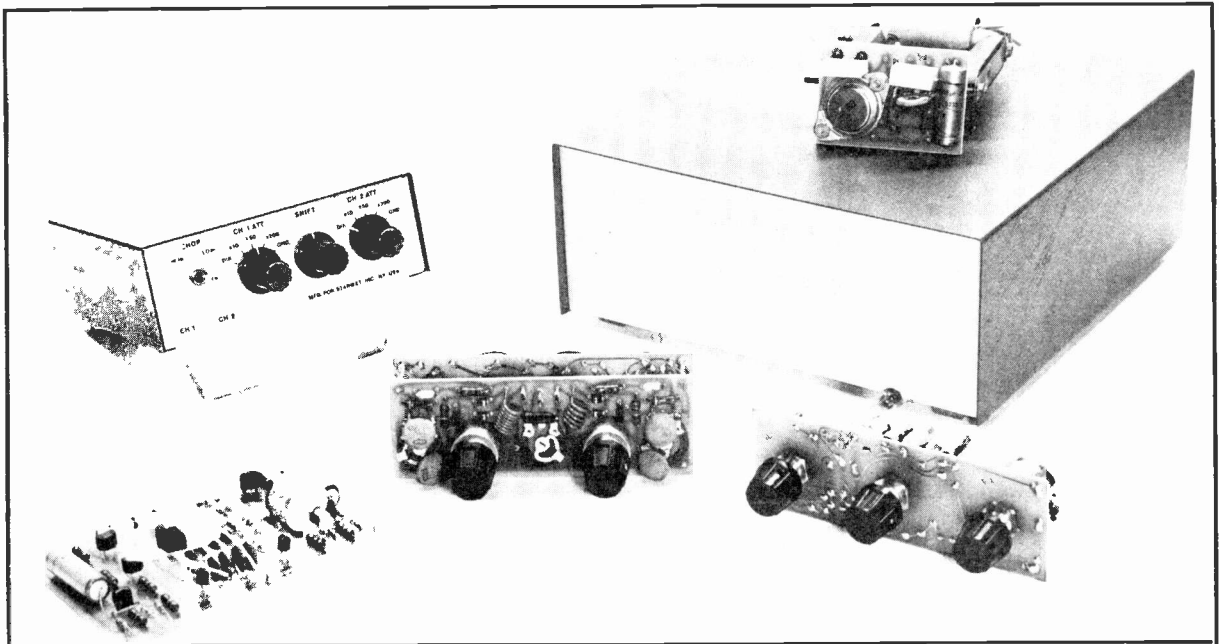Rendar Instruments Ltd., Victoria Road Burgess Hill, Sussex. Tel. Burgess Hill 2642-4 Cables: Rendar, Burgess Hill



2HZ to 20MHZ SOLID STATE BEAM SWITCH

Completely assembled P.C. Board, ready to use on any standard commercial oscilloscope. Size $4\frac{3}{4}$ in \times $3\frac{1}{4}$ in, **£9.25 each.** P & P 25p. Completely encased with attenuators and BNC connectors **£25 each.**

20HZ to 200KHZ SINE WAVE GENERATOR

In four ranges. Wein bridge oscillator, thermistor stabilised, amplitude control, 3V peak to peak. Completely assembled P.C. board, ready to use. 9 to 15V supply required. **£4.85 each.** P & P 25p.

TRANSISTOR INVERTOR

12V to 1.5kV 2 MA AC.
Size $1\frac{1}{2}$ in \times $2\frac{1}{2}$ in \times 4in.
ONLY £2.95 each. P & P 25p.

MODERN INSTRUMENTS CASES

All aluminium construction, etched chassis with removable blue vinyl cover.

Small case

Size $4\frac{1}{2}$ in wide, $1\frac{1}{2}$ in high, $4\frac{1}{4}$ in deep with 2 position tilted hinged rest, **95p each.** P & P 15p.

Large case

Size 8in wide, 3in high, $7\frac{1}{2}$ in deep. Price **£1.87 each.** P & P 25p.

STABILISED POWER UNIT

For BC 221 Frequency meter. Slide-in and connect. **ONLY £3.75 each.** P & P 75p.

The advertised Beam Switch, Square Wave Generator and Sine Wave Generator will fit the smaller case.

**LARGE RANGE OF
OSCILLOSCOPES
ALWAYS AVAILABLE
WRITE FOR LISTS**

WOBBULATOR

For displaying response of 10.7MHZ (FM receiver I.F.'s) and 30-40MHZ (TV I.F. alignment). Requires 6.3V AC and any general purpose oscilloscope. Instructions supplied. Completely assembled P.C. Board, **£9 each.** P & P 25p.

CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College) Tel.: Reading 582605/65916

Come and listen at the year's most exciting exhibition

Join thousands of Hi-Fi enthusiasts in an atmosphere that will set your ears tingling with excitement. Whatever your taste – classics, jazz or pop – there will be something for you. The international giants of the Hi-Fi industry will be there – showing the latest specialist equipment: unit audio; tape recorders, cassette, cartridge and reel-to-reel; loudspeakers; AM/FM tuners, receivers; amplifiers, radios; tapes and discs. There will be continuous demonstrations in over 65 special Audio Studios – plus daily presentations, lectures and discussions in the Hi-Fi Theatre. And the Sunday Mirror is offering concession rates of admission to its readers, plus exciting competitions. Don't miss this great event.

THE 1972 INTERNATIONAL AUDIO FESTIVAL AND FAIR

Sponsored by the Sunday Mirror


OLYMPIA London

Tuesday 24 October to

Saturday 28 October

Daily 10 a.m. to 9 p.m.

Admission 40p

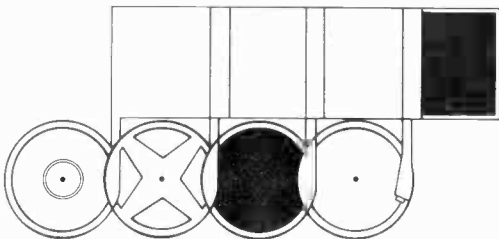

YOU MUST HEAR

**MINIWISE AUDILECT
YOUR
PERSONAL TUTOR**

**THE
No. 1
HIT**

Bring PLEASURE to your CAREER or HOBBY through Integrated LEARNING. ORGANIZED TUITION in your own HOME at your own SPEED—with the TUTOR OF YOUR CHOICE will give you rapid UNDERSTANDING—the key to SUCCESS. ASSURE YOUR FUTURE in RADIO, TV or ELECTRONICS.


**WRITE NOW—RIGHT NOW TO
MINIWISE PRODUCTS
FREEPOST, BLETCHLEY, BUCKS**

FOR FREE DETAILS OF THIS UNIQUE sensible method just send us your name and address quoting PE11, no one will call. Or include only 90p to own a trial LESSON* on either a C90 cassette in Lib. case or L.P. Tape (state which).

*Your money INSTANTLY REFUNDABLE if not 100% convinced that this can be the turning point in your hobby or career.

THE NATURAL WAY TO LEARN

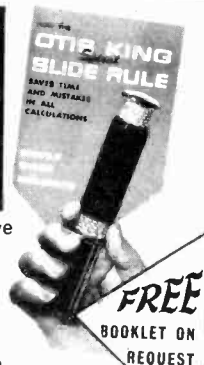*The most accurate
pocket size
CALCULATOR
in the world*



The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send £4.50 for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

CARBIC LTD. (Dept. PE43)
54 Dundonald Road, London SW19 3PH

SANWA MULTI TESTERS

P2B	2,000Ω/V	£4.85	360 YTR	10,000Ω/V	£7.95
JR-5D	2,000Ω/V	£5.80	A303 TRD	20,000Ω/V	£10.35
U50-DX	20,000Ω/V	£8.35	N401	200,000Ω/V	£32.85

RECORDING TAPE

S.P.	5in 600ft	50p	5 1/2in 900ft	65p	7in 1200ft	78p
L.P.	5in 900ft	65p	5 1/2in 1200ft	83p	7in 1800ft	98p
D.P.	5in 1200ft	92p	5 1/2in 1800ft	£1.18	7in 2400ft	£1.44

MAGNETIC CARTRIDGES

Goldring	G800 Super E	£18.25	M55-E	£8.85
G800	G850	£4.95	M75-G Slim	£8.85
G800H	Shure		M75-E(2)	£12.70
G800E	M44-7	£6.95	M75-E(2)	£13.75

TRANSISTORS

AC107	28p	AD161	75p pr	BC147	20p	OC71	14p
AC126	27p	AD162		BD112	44p	OC81D	19p
AC127	23p	BC107	12p	BFY51	23p	OCP71	45p
AC132	19p	BC108	12p	OC26	40p	2N2926	13p
AD149	47p	BC109	12p	OC28	52p	2N3055	65p

R.S. COMPONENTS, TUNERS, AMPLIFIERS, DISCO, VERO BOARD
S.A.E. for FREE leaflets. CATALOGUE 25p POST FREE
All prices POST FREE. Minimum order 50p.

MAIL ORDER ONLY FROM

CELETRON-E

P.O. BOX No. 1, LLANTWIT MAJOR, GLAMORGAN CF6 9YN

ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £80 radios! *Test 7 days, we'll refund instantly if you are not astounded! Elegant black & chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth 24 hours a day including all normal transmissions. VHF, AM, FM, MW, LW, USW, plus local & new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With WRITTEN GUARANTEE manual with simple operating instructions & circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra). **BOX, POST, ETC. 50p.** *BUT WAIT, for only 55p extra you get the sensational "COMPUTERISED" WORLD TUNING GUIDE (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. NO GUESSING! NO MESSING!) PLUS Standard 'longlife' batteries PLUS ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) HURRY! Send today or call at either store.

JUST ARRIVED! THIS YEAR'S NEW * COMPUTERISED? RUSSIAN MIRACLE!

BRAND NEW SPACE AGE model - SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!

THE FABULOUS ASTRAD 17

PORTABLE RADIO & COMMUNICATIONS RECEIVER

THE OFFER ONLY FROM US!

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!



28 TRANSISTORS AND DIODES!

WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

***COMPARE ITS PERFORMANCE with £80 RADIOS!**

BATTERY MODEL £20.75 **BOX POST ETC. 50p**

MAINS/BATTERY ELIMINATOR £1.48 extra

FIRST TIME EVER!

***NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE!**

NO MORE GUESSWORK - INSTANT DATA at your fingertips - enables you to TUNE IN A FLASH to transmissions the world over!

ANOTHER EAST EUROPEAN MIRACLE!

FANTASTIC 2-in-1 PERSONAL PORTABLE and CAR RADIO

NOW WORLD WIDE RECEPTION

IN YOUR CAR TOO! (RUNS OFF 12v. CAR BATTERY)

4 WAVEBAND VHF AM FM / LONG & SHORT WAVEBANDS

FANTASTIC PRICE £9.95

Box, Post ETC. 45p.

TRY AND MATCH IT FOR UNDER £35!

Position it for CAR RADIO, results will justify! OR detach & use carry handle for PORTABLE with its own batteries!

FANTASTIC! Brand spanking new from East Europe—we bring you this incredible 2-in-1 Radio! First class makers—because of our crazy price, contract stipulates we must NOT mention name! Beautifully made, 9 x 4 x 2 1/2 inches overall approx. Every up-to-date technological improvement. 15 SEMI-CONDUCTORS, 9 Transistors, 5 Diodes and Stabiliser! **FOUR WAVEBANDS!** Yes, VHF model with AM/FM Long and Short wavebands! Will get stations around the world, including Standard Long, Medium and Short Wave, also local and new stations not yet operational! Built-in internal ferrite aerial plus 5 section 26in. swivel telescopic aerial—on/off volume and tone controls. Clear Station Selector Dial. Waveband selector! Equally wonderful in CAR or HOME! **TWO Tuning Dials** for flat or upright use as illustrated. **RUNS OFF 12 VOLT BATTERY!** (ASA PORTABLE it runs on standard batteries.) **PLUG IN 12 VOLT ADAPTOR JACK PROVIDED** and automatically cut out internal batteries, using car battery only! Don't you think it's miraculous! Span the Oceans and pull in hundreds of transmissions 5 day and night, including short wave—even in car! **BUT WAIT—** simply remove Radio from car, "snap on" optional carry handle **AND YOU HAVE A DE-LUXE PORTABLE**, with additional upright tuning dial. **WRITTEN GUARANTEE.** Only £9.95 box, post 45p. *Sprung all metal matching detachable carry handle (as illus.) & batteries only 25p ex. if required. Match with sets costing £35 or more. Test 7 days—refund if not delighted. Order by post to Uxbridge Road address, or call at either store.



THIS FANTASTIC OFFER ONLY FROM US! SAVE £20.25 NOW!

FABULOUS BRAND NEW SOLID STATE

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE

OUR PRICE £23.75 **CARR ETC. 35p**

RECOMMENDED RETAIL PRICE £44

This equipment's got EVERYTHING!



Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!) We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240v. AC line cord.) Record and play back anything, anywhere! Even tape direct from the Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: * Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL! * "MAGIC EYE" Visual Battery check/monitoring level indicator or built-in automatic Leveller! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in approx.!) Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. **AND the amazing built-in full circuit VHF, AM/FM Radio** gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £ £ £'s more for a Car Radio or Car Cassette player ALONE! £23.75, CARR. ETC. 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send today or call at either store. Test 7 days, refund if not delighted. **BONUS OFFER:** Batteries and Cassette Tape 25p extra if required.

Dept. PE/22, 164 UXBRIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) **BOTH STORES OPEN FROM MONDAY TO SATURDAY FROM 9 A.M. UNTIL 6 P.M.**

SHOPERTUNITIES LTD.

RTVC THE

THE FABULOUSLY SUCCESSFUL VISCOUNT III AUDIO £52 complete

14 + 14 watts r.m.s. 40Hz to 40kHz \pm 3dB. Total distortion at 10 watts at 1kHz — 0.1%.

This is real value for money! We have designed 2 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For both systems we have chosen the famous Garrard SP25 Mk. III deck which comes complete with simulated teak plinth and dust cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

SPEAKERS

Duo Type II Size approx. 17in. \times 10 $\frac{1}{2}$ in. \times 6 $\frac{1}{2}$ in. Drive unit 13in. \times 8in. with parasitic tweeter. Max power 10 watts, ohms. Simulated Teak cabinet. £14 pair + £3 p & p.

Duo Type III Size approx. 23 $\frac{1}{2}$ in. \times 11 $\frac{1}{2}$ in. \times 9 $\frac{1}{2}$ in. Drive unit 13 $\frac{1}{2}$ in. \times 8 $\frac{1}{2}$ in. with H.F. speaker. Max power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p & p.

SPECIFICATION R101

14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms). Total distortion @ 10W @ 1kHz 0.1%. P.U.1. (for ceramic cartridges) 150mV into 3 Meg. P.U.2. (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within \pm 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal-to-noise ratio: (all controls at max) — P.U.1. and radio — 65dB, P.U.2 — 58dB. Cross talk better than — 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ in. \times 9in. \times 3 $\frac{1}{2}$ in. Send S.A.E. for fully illustrated brochure.
12 MONTH'S WRITTEN GUARANTEE.

PRICES: SYSTEM 1

Viscount III R 101 amplifier	£22.00 + 90p p&p
2 \times Duo Type II speakers	£14.00 + £2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
Total	£59.00

Available complete for only **£52** + £3.50 p & p

PRICES: SYSTEM 2

Viscount R 101 amplifier	£22.00 + 90p p&p
2 \times Duo Type III speakers	£32.00 + £3 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
Total	£77.00

Available complete for **£69** + £4 p & p

— ONLY FROM US



MUSIC MAKERS

UNISOUND FOR THE NEW SOUND

AT £25

The whole system is complete including superb cabinets in simulated teak—just simply screw together the components and you save pounds!

Amplifier is based on the famous Mullard Unilex system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13in. x 8in. EMI Twin-cone speakers ready for mounting in their elegant cabinets, which simply need screwing and glueing together. All glue and screws supplied. Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound.


£25 complete plus £2.80 p. & p. Diamond Stylus £1.25 extra.

Power output: 4 watts per channel into 8 ohms. Inputs: 120 mV (for ceramic cartridges). Stereo headphones with adaptor £4.00.

UNISOUND MODULES ONLY £6.95

If you prefer, you can buy the three modules—pre-amplifier power supply/dual power amplifier, and control panel—by themselves for only £6.95. P. & P. 50p extra.

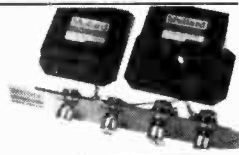No soldering, just simply screw together with screwdriver supplied. Their overall specification is the same as shown for the complete Unisound console, using the high efficient I.C. monolithic power chips to ensure very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum.



AN **R T V C** EXCLUSIVE DESIGN

A 'NATURAL' ONLY FROM **R T V C** THE TOURIST PB CAR RADIO KIT

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components, this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. Four push-buttons for medium wave, one for long wave. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohm speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms. Power consumption is less than 1 amp.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale for easy reading at night. Chassis size is: 7in wide, 2in. high and 4 1/2 in. deep (excluding front panel, etc.).

★ Circuit diagram and comprehensive instructions 50p, free with parts.


★ Fully retractable lockable car aerial £1.25 post paid.

PRICE ONLY £7 + p & p 50p

8 ohm speaker with baffle and fixing strips £1.50 + 25p p & p, post free if brought with the kit.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

ONLY
£7.00

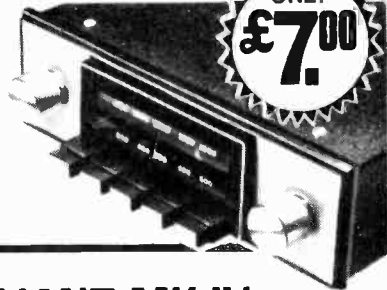

RELIANT MK.IV

★ 5 Electronically Mixed Inputs. ★ 3 Individual Mixing Controls. ★ Separate bass and treble controls common to all 5 inputs. ★ Mixer employing F.E.T. (Field Effect Transistor). ★ Solid State Circuitry. ★ Attractive Styling. ★ Sides finished in solid teak.

INPUTS:—1. Crystal Mic. or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram., Tuner, Monitor, Organ, etc.). All 250mV sensitivity.

CONTROLS:—3 Volume controls. Bass control range: 13dB @ 60Hz. Treble control range: ±12dB @ 15KHz. Separate ON/OFF Switch. Neon indicator. **POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker. **SIGNAL NOISE:**—Better than -60dB on inputs 3, 4 and 5 & -50dB on 1 & 2. **SUPPLY:**—220-250 A.C. Mains. **SIZE:**—12 1/2 in. x 6 in. x 3 1/2 in.

£10.50

plus p & p 60p

VISIT OUR SHOWROOM

R T V C

Radio and TV Components (Acton) Ltd.
21D High St., Acton, London W3 6NG
323 Edgware Road, London, W.2

Mail orders to Acton · Terms C.W.O. · All enquiries S.A.E.
Goods not dispatched outside U.K.

TRANSFORMERS

MAINS ISOLATING SERIES
 Primary 200-250 Volts Secondary 240 Volts Centre
 Tapped (120V) and Earth Shielded
 ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P
107	20	1 11	7.0 × 6.0 × 6.5	£ 1.61 30p
100	60	3 8	8.9 × 8.0 × 7.7	2.39 36
61	100	5 12	10.2 × 8.9 × 8.3	2.62 52
30	200	9 8	12.0 × 10.3 × 10.0	4.39 52
62	250	12 4	9.5 × 12.7 × 11.4	5.80 67
55	350	15 0	14.0 × 10.8 × 12.4	7.77 82
63	500	27 0	17.1 × 11.4 × 15.9	11.20 *
92	1000	40 0	17.8 × 17.1 × 21.6	20.63 *
128	2000	63 0	24.1 × 21.6 × 15.2	34.10 *

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P
113	20	1 11	7.3 × 4.3 × 4.4	0-115-210-240	0.85 22
64	75	1 14	7.0 × 6.4 × 6.0	0-115-210-240	1.66 30
4	150	3 0	8.9 × 6.4 × 7.6	0-115-200-220-240	2.00 36
66	300	6 0	10.2 × 10.2 × 9.5	3.89 52
67	500	12 8	14.0 × 10.2 × 11.4	5.78 67
84	1000	16 0	11.4 × 14.0 × 14.0	10.49 82
93	1500	28 9	13.5 × 14.9 × 16.5	15.20 *
95	2000	40 0	17.8 × 16.5 × 21.6	19.84 *
73	3000	45 8	17.4 × 18.1 × 21.3	26.99 *

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
 115V 500 Watt totally enclosed auto transformer, complete with
 mains lead and two 115V outlet sockets, £7.87. P & P 67p.
 Also available a 20 Watt version, £1.67. P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Windings	P & P
110	0.25	1 2	7.6 × 5.7 × 4.4	0-12V at 0.25A × 2	0.85 22
213	0.5	1 0	8.3 × 5.1 × 5.1	0-12V at 0.5A × 2	1.01 22
71	2	1 0	7.0 × 6.4 × 5.7	0-12V at 1A × 2	1.33 22
18	4	2 2	8.3 × 7.0 × 7.0	0-12V at 2A × 2	1.86 36
70	6	3 12	10.2 × 7.6 × 8.6	0-12V at 3A × 2	2.24 42
108	8	4 5	10.0 × 8.3 × 8.2	0-12V at 4A × 2	2.48 52
72	10	5 8	7.9 × 10.8 × 10.2	0-12V at 5A × 2	2.94 52
17	16	8 7	12.1 × 9.5 × 10.2	0-12V at 8A × 2	4.54 52
115	20	10 13	12.1 × 11.4 × 10.2	0-12V at 10A × 2	5.78 67
187	30	15 12	13.3 × 12.1 × 12.1	0-12V at 15A × 2	10.67 82
226	60	30 34	17.0 × 14.5 × 12.5	0-12V at 30A × 2	19.61 *

30 VOLT RANGE

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P
112	0.5	1 4	8.3 × 3.7 × 4.9	0-12-15-20-24-30V	1.01 22
79	1	2 0	7.0 × 6.4 × 6.0	1.35 36
3	2	3 2	8.9 × 7.0 × 7.6	2.01 36
20	3	4 6	10.2 × 8.9 × 8.6	2.48 42
21	4	6 0	10.2 × 10.0 × 8.6	2.94 52
51	5	6 8	12.1 × 10.0 × 8.6	3.66 52
117	6	7 8	12.1 × 10.0 × 10.2	4.36 52
88	8	10 0	14.0 × 11.7 × 10.0	5.64 67
89	10	12 2	14.0 × 10.2 × 11.4	7.14 67

50 VOLT RANGE

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P
102	0.5	1 11	7.0 × 7.0 × 5.7	0-19-25-33-40-50V	1.33 30
103	1	2 10	8.3 × 7.3 × 7.0	1.94 36
104	2	5 0	10.2 × 8.9 × 8.6	2.69 42
105	3	6 0	10.2 × 10.2 × 8.3	3.65 52
106	4	9 4	12.1 × 11.4 × 10.2	4.83 52
107	6	12 4	12.1 × 11.1 × 13.3	7.14 67
118	8	18 9	13.3 × 13.3 × 12.1	9.32 97
119	10	19 12	16.5 × 11.4 × 15.9	11.68 97

60 VOLT RANGE

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P
124	0.5	2 4	8.3 × 9.5 × 6.7	0-24-30-40-48-60V	1.35 36
126	1	3 0	8.9 × 7.6 × 7.6	1.88 36
127	2	5 6	10.2 × 8.9 × 8.6	2.94 42
125	3	8 8	11.9 × 9.5 × 10.0	4.48 52
123	4	10 6	11.4 × 9.5 × 11.4	5.78 67
120	6	16 12	13.3 × 12.1 × 12.1	8.37 82
122	10	23 2	16.5 × 12.7 × 16.5	13.85 *

LEAD ACID BATTERY CHARGER TYPES

Ref. No.	Ampls.	Weight lb oz	Size cm.	P & P
45	1.5	1 9	7.0 × 6.0 × 6.0	£ 1.34 30p
5	4.0	5 11	10.2 × 7.0 × 8.3	2.03 42
86	6.0	5 12	10.2 × 8.9 × 8.3	3.07 52
146	8.0	6 4	8.9 × 10.2 × 10.2	3.49 52
50	12.5	11 14	13.3 × 10.8 × 12.1	5.20 67

All ratings are continuous. Standard construction: open with solder
 tags and wax impregnation. Enclosed styles to order.
FULL SPEC. TRANSISTORS
 BC107/108/109 9.0p each 2N 3055 68p each AD 161/162 60p pair
 25+ 7p + mica and bushes 25+ 35p + mica and bushes
 100+ 65p 25+ 55p
 500+ 6p 100+ 45p 100+ 50p
 Minimum order 10 500+ 40p 500+ 45p
 pieces this range. 1000+ 40p

**AVOMETERS · MAINS KEYNECTOR
 ELECTROSIL RESISTORS**

*CARRIAGE VIA BRB

BARRIE electronics

11 MOSCOW ROAD, QUEENSWAY

LONDON W2 4AH Tel: 01-229 6681/2

NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY

SOUND BARGAINS



GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER
 WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE £10-50
 +40p P. & P.

THIS NEW 1972 RADIO. No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHERBAND. Frequency ranges: MW340-1600KHz, FM88-108MHz, Airband 108-145 MHz, VHF 145-175 MHz, 23 semiconductor, 12 transistors, 11 diodes and thermistors. Automatic frequency control. 31in telescopic aerial. Runs off mains a.c. 230/250V or off 4 U2 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10 1/2" x 8 1/2" x 3 1/2". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries free. HURRY! Limited quantity only from Marktype.

VHF, FM, AM, A.F.C. AIR BAND, PUBLIC SERVICE AND WEATHER BANDS

OUR PRICE £28-95
 +50p P. & P.



Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks: leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 230-240V domestic mains supply. 14 transistors; 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350 kHz. Medium 353-1605 kHz. Marine 1.6-4.5 MHz. Short Wave 12-24 MHz. FM/VHF 88-108 MHz. Aircraft 108-135 MHz. PUBLIC SERVICE BANDS 135-174 MHz. Fully guaranteed.

MARKTYME (Dept. PE6), 372 EDGWARE ROAD, LONDON, W.2. Tel. 01-723 0094
 Callers welcome Mon. to Sat. 9 a.m.-6 p.m.

N.B. The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

TESL (ELECTRONICS)

37 TALGARTH ROAD, LONDON, W.14

MAIL ORDER ONLY

THE ONLY "SPEC" OF DIFFERENCE IS THE LOWER PRICE
 BRAND NEW FULLY GUARANTEED

RESISTORS
 Full range of ISKRA carbon film resistors. All 5% (except values over 47MΩ)—high stability—very low noise—E12 values.
 1/4W, 1/2W 1p; 1W 2p.

POTENTIOMETERS
 Carbon track 5KΩ to 2MΩ log or linear. Single 11p; Dual gang (stereo) 38p; Single D.P. switch 23p.

SLIDER POTENTIOMETERS
 Overall length 86.6mm. Fixing centres 80mm. Single 10K, 25K, 50K, 100K. 35p each. Dual gang dual values as above, 50p each. Knob for above, 10p each.

TRANSISTORS					
AC125	12p	AF114	14p	BC147	9-5p
AC126	12p	AF115	14p	BC148	9-5p
AC127	11p	AF116	14p	BC149	9-5p
AC128	11p	AF117	14p	2N2218A	13p
AC132	12p	BC107	7p	2N2222	13p
AC187	14p	BC108	7p	2N2222A	13p
AC188	14p	BC109	7p	2N3014	13p

Any one type
 25+ 100+ 1,000+
 Discounts 10% 20% 40%
 Wholesale enquiries welcome

DIODES

LINEAR ICs TO99	
ZENER—400mW 5% 3-3V to 30V, 12p each	709C, 25p each
SIGNAL—OA90, 4p; OA91, 4p	723, 51p each
RECTIFIER—IN4001, 4p; IN4004, 7p	741C, 30p each

Terms: C.W.O. please. P. & P. please add 10p for orders below £2. Discount 7 1/2% for orders above £10. Full Catalogue on request. S.A.E. appreciated.

NEW! FROM ADCOLA

THE BEST IN SOLDERING KITS

Styrene packed with see-through top
Makes the perfect gift!





- Contents**
BOX OF SOLDER
TWO SPARE BITS
HINTS ON SOLDERING
686 SOLDERING STAND
646 INVADER SOLDERING TOOL

Built to world safety standards

The Adcola Invader Soldering Kit comes to you in a presentation pack!
 The 'READY TO USE KIT' offers maximum versatility of a 23 watt soldering instrument.

only £3.99

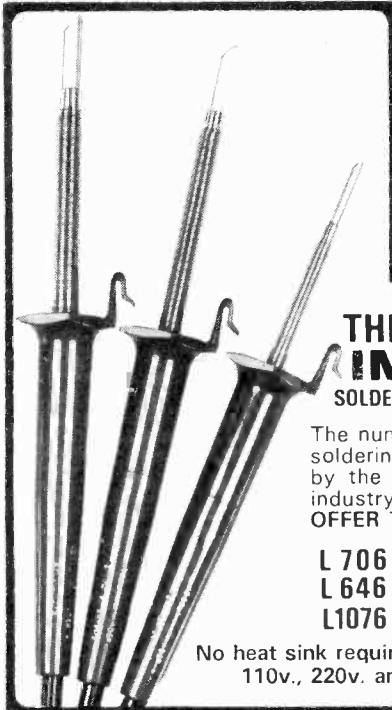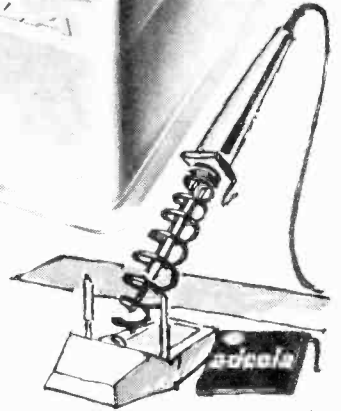

THE FABULOUS INVADERS

SOLDERING INSTRUMENTS

The number one accepted soldering instrument used by the professional in industry. IS NOW ON OFFER TO YOU.

- L 706 19watts £1.96
- L 646 23watts £2.12
- L1076 27watts £2.18

No heat sink required. Stock voltages 110v., 220v. and 230/250v.


L686 SOLDERING INSTRUMENT STAND



The perfect instrument stand for your 'Invader'.

£1.71

MULTI-CHANNELLED SOLDER

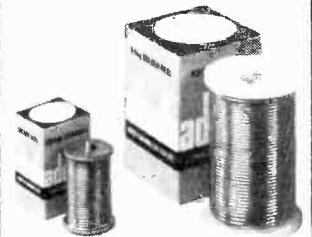

Pre fluxed solder 'READY TO USE' produced to B.S.I. 441 IN HANDY SIZES. £0.41 and £1.16

PLEASE SEND ME THE FOLLOWING ITEMS

NAME & ADDRESS _____

INVADER SOLDERING KIT

1076 'INVADER' _____

646 'INVADER' _____

706 'INVADER' _____

686 SOLDERING STATION _____

1/2 kg SOLDER REEL _____

SMALL SOLDER REEL _____

Postage & packing add 10p free over £2


Enclosing P/O and cheque



ADCOLA PRODUCTS LTD. ADCOLA HOUSE
 GAUDEN ROAD LONDON, SW4 6LH
 TELEPHONE. 01-622-0291/3

PE

LINDAIR (ELECTRO-TECH) LTD

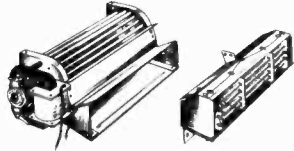

TANGENTIAL HEATER

Silently driven by a shaded pole Mylexal motor. Compact, powerful and quiet running with aluminium impeller (outlet $5\frac{1}{2} \times 1\frac{1}{2}$). Mains voltage. PLUS matching heater unit with spiral element. May be switched for 500 or 1,000 watts. **PRICE ONLY £1.60** P. & P. 40p

SYNCHRONOUS AUTO-RESET PROCESS TIMER



By LONDEX LIMITED

Type **IMP Mk. 2**. Brand New and Boxed. These well known timers are already in world-wide use and are perfect for Industrial Electronic Timing. Research and for all machine control timing problems. Repetitive accuracy better than 0.5% of full scale setting. Two or more can be inter-connected to give control of a series of processes. 230/250v. 50Hz. also available 60Hz. 15 minutes full scale, 15 secs. per division. Driven by self-starting sync. motor. Contact rating 5 amp at 250v. a.c. Incorporates solenoid operated clutch. Also, lever actuated micro switches. Normal price probably in excess of £18. Complete with multi-pin connector as illustrated.

OUR PRICE ONLY

£6.50

SEEN THIS ?

This is the only way way we could illustrate this fabulous item.

NORPLEX the famous American fibre-glass copper-clad laminate. Finest quality with Woven Glass base of Epoxy-resin. Excellent mech. and elec., conductive properties. Heat Resistant. Ideal for P.C.s., etc. **THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST.** Sizes: 12" x 12", 24" x 12", 24" x 24". **FULL SHEET** 43" x 37" (11 sq. ft.). Single sided copper with thicknesses of $\frac{1}{32}$ ", $\frac{3}{64}$ ", $\frac{1}{16}$ " $\frac{3}{32}$ ". also Double sided $\frac{1}{32}$ ", $\frac{1}{16}$ ", $\frac{3}{32}$ ".

PRICE ONLY £1 per sq. ft. £8 per full sheet. P. & P. 25p up to 4 sq. ft. Over 4 sq. ft. (cut sizes only) Post FREE. Full sheets post by rail G.B. only £1 one or more sheets.

MICRO-LITES

Wonderful engineering—micro miniature incandescent lamp small enough to pass through the eye of a needle! 1,000's of uses. Will operate from the output of a transistor. Rating: 1.5v, 10-15ma. Size: 4.4 x 1.4mm. dia. Leads: 22mm. These fantastic lamps have a life expectancy of 1,000 hrs. **OUR PRICE**



£3.25

per doz. Free p. & p.

NEW AND UNUSED

Postal or carriage charges are for Great Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50, cash with order please.


FURTHER BULK PURCHASE SILVANA MAGNETIC SWITCH



NOW COMPLETE WITH REFERENCE MAGNET! A magnificently activated switch. Vacuum sealed in a glass envelope. Silver contacts normally closed, rated 3 amp at 120v. 15 amp at 240v. Size (approx.) $1\frac{1}{16}$ " long $1\frac{1}{16}$ " dia. Ideal for Burglar Alarms, Security systems, etc., and wherever non-mechanical switching is required. **Now Lower Price. Only £2.10** for 12. £8 for 50 or £15 for 100 complete with magnet.

£2.10

PROGRAMMER TIMER BY HONEYWELL

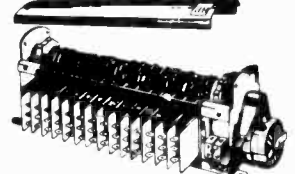


A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Designed originally for vending machines at a cost of £15.00 plus. Many applications where continuous sequence programmes are required, such as lighting effects etc. New in original makers cartons. First class value at £5.75 plus 25p P. & P.

£5.75

315 EDGWARE ROAD, LONDON W2. Tel. 01-262 2251. Open 9 a.m.-6 p.m. MON to SAT

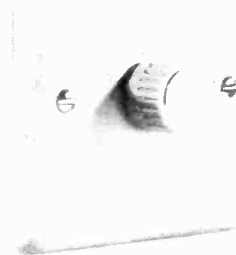Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt—£3.20. Kit Form £2.70
300 Watt—£2.70. Kit Form £2.20

All plus 10p post and packing. Please send C.W.O. to:—

DEXTER & COMPANY


1 ULVER HOUSE, 19 KING STREET
CHESTER CH1 2AH Tel. 0244-25883

As supplied to H.M. Government Departments

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

DISCOUNT PRICES

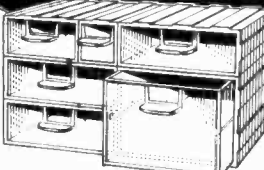

5 SIZES ALL INTERLOCK

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins) £1.35 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins) £2.25 DOZEN.

TREBLE (3D) £2.35 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £3.65 for 8, EXTRA LARGE SIZE (6D1) £3.30 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £5 and over DEDUCT 5% in the £
Orders £10 and over DEDUCT 7½% in the £
Orders £20 and over DEDUCT 10% in the £
PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £5. Orders £5 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID

IVORVET LIMITED

(Dept. PE11) 124 Cricklewood
Broadway, London, N.W.2
Tel. 01-450 4844



TONE TESTER

The Tone Tester is a solid-state dual impedance continuity tester with tone injection.

Applications: Wiring. Cable installation. Production line testing. Damage free testing of solid-state assemblies.

Power supply: integral 1.5v battery. Continuity test: impedance—low 0—10 ohms high 0—50k ohms.

Tone injection: 1.4 Vp—p up to 300 ohms D.C. loop. *Tone injection on HTD only.*

HTD dual impedance with tone injection £5.80. HTL low impedance only £4.84.

HTH high impedance only £4.96.

Highams Electronic Communications Ltd
Dept E 58-60 Redchurch St London E2

BI-PRE-PAK

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 50p

POST & PACKING 15p

TESTED AND GUARANTEED PAKS

- B2 4 Photo Cells, Sun Batteries, 0.3 to 0.5V, 0.5 to 2mA. **50p**
- B79 4 IN4007 Sil. Rec. diodes, 1,000 PIV 1 amp. plastic **50p**
- B81 10 Reed Switches, mixed types large and small. **50p**
- B99 200 Mixed Capacitors. Approx. quantity, counted by weight **50p**
- H4 250 Mixed Resistors. Approx. quantity counted by weight **50p**
- H7 40 Wirewound Resistors. Mixed types and values **50p**
- H8 4 BY127 Sil. Recs. 1000 PIV 1 amp. plastic **50p**
- H9 2 OC771 Light Sensitive Photo Transistor **50p**
- H28 20 OC200/1/2/3 PNP Silicon uncodded TO-5 can **50p**
- H30 20 1 Watt Zener Diodes, Mixed Voltages 6.8-43V **50p**
- H35 100 Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked **50p**
- H38 30 Short lead Transistors, NPN Silicon Planar types **50p**
- H39 10 Integrated circuits 6 gates BMC 962, 4 flip flops BMC 945 **50p**

UNMARKED UNTESTED PAKS

- B1 50 Germanium Transistors PNP, AF and RF **50p**
- B66 150 Germanium Diodes Min. glass type **50p**
- B83 200 Trans. manufacturers' rejects all types PNP, PNP, Sil. and Germ. **50p**
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202 **50p**
- B86 50 Sil. Diodes sub. min. IN1914 and IN1916 types **50p**
- B88 50 Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc. **50p**
- H6 40 250mW. Zener Diodes DO-7 Min. Glass Type **50p**
- H15 30 Top Hat Silicon Rectifiers, 750mA. Mixed volts **50p**
- H16 15 Experimenters' Pak of Integrated Circuits. Data supplied **50p**
- H17 20 3 amp. Silicon Stud Rectifiers, mixed volts **50p**
- H20 20 BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts **50p**
- H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can **50p**

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		4p	
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-15	2N1502-3	0-15
ACY17	0-20	2N1304-5	0-17
AF239	0-30	2N1306-7	0-20
AF186	0-20	2N1308-9	0-22
BC148	0-10	2N3819FET	0-40
BC154	0-10	2N4416FET	0-35
BC107	0-20		
BC108	0-10	Power Transistors	
BC109	0-10	OC20	0-40
BC169	0-12	OC21	0-25
BF194	0-15	OC23	0-25
BF274	0-20	OC25	0-25
BFY50	0-15	OC26	0-25
BSY25	0-13	OC28	0-30
BSY26	0-13	OC35	0-25
BSY27	0-13	OC36	0-37
BSY28	0-13	AD149	0-35
BSY29	0-13	AU710	0-75
BSY95A	0-10	25034	0-25
OC41	0-15	2N3055	0-40
OC44	0-13		
OC45	0-10	Diodes	
OC71	0-10	AY42	0-10
OC72	0-10	OA95	0-07
OC81	0-13	OA79	0-07
OC81D	0-13	OA81	0-07
OC83	0-13	OA95	0-07
OC139	0-18	OA95	0-07
OC140	0-15	IN914	0-06

POWER TRANSISTOR PRICE BREAKTHROUGH!

Plastic Cased Silicon Power Transistors of latest design. 40 watts and 90 watts. PNP and NPN types. All types available at the most shatteringly low prices of all time. All are fully tested, marked and guaranteed!

	1-12	13-25	26-50
40W NPN	20p	18p	16p
40W PNP	21p	19p	17p
90W NPN	24p	22p	20p
90W PNP	25p	23p	21p

PAKS of matched pairs:
MP40 40W + 40W 50p 48p 46p
MP90 90W + 90W 60p 58p 56p



A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS



8 RELAYS FOR VARIOUS TYPES P. & P. 25p £1

INTEGRATED CIRCUITS

- Clocked Flip Flop, BMC931 1-12 13-25 26-50 20p 18p 16p
- Ex. 2/4-input Buffer, BMC932 12p 11p 10p
- 2/4-input Expander, BMC933 12p 11p 10p
- Hex. Inverter, BMC934 12p 11p 10p
- Hex. Inverter, BMC935 12p 11p 10p
- Hex. Inverter, BMC936 12p 11p 10p
- Hex. Inverter, BMC937 12p 11p 10p
- Decade Counter, BMC938 25p 23p 21p
- Div. by 16 Counter, BMC939 25p 23p 21p
- Hex. Inverter, BMC940 12p 11p 10p
- Hex. Inverter, BMC941 12p 11p 10p
- Type D Flip Flop, BMC942 20p 18p 16p
- Ex. 2/4-input Power, BMC944 12p 11p 10p
- Clocked Flip Flop, BMC945 20p 18p 16p
- Quad Inverter, BMC946 11p 10p 9p
- Clocked Flip Flop, BMC948 20p 18p 16p
- Quad Inverter, BMC949 12p 11p 10p
- Pulsed Trig. Binary, BMC950 20p 18p 16p
- Monostable Multivib., BMC951 25p 23p 21p
- Dual J/K Flip Flop, BMC952 20p 18p 16p
- Dual J/K Flip Flop, BMC955 20p 18p 16p
- Dual J/K Flip Flop, BMC956 20p 18p 16p
- Quad. 2-input Power, BMC958 12p 11p 10p
- 2/4-input Gate, BMC961 12p 11p 10p
- 3/3-input NAND Gate, BMC962 11p 10p 9p
- 3/3-input NAND Gate, BMC963 12p 11p 10p
- Audio Amp. 3-watts. £1 50 £1 40 £1 36
- SL403D
- Linear Op. Amp. 709C 25p 20p 15p
- Decade Counter, SM7490 65p 60p 55p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low
16 pin type at 16p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes: 40p
This includes many thousands of British U.S.A., European and C.V. equivalents.
The IIRa Radio Valve & Transistor Data Book 9th Edition: 75p
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

DISCOUNTS UP TO

60%* ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

SPECIAL OFFER
Garrard SP25 Mk. III £17.75
Goldring G800
Teak plinth and tinted cover.
All leads supplied.
Please add £1.25 for P. & P.

TURNTABLES

Please add 75p post & packing

Garrard SP25 Mk. III £10.25
Garrard AP76 £17.75
Garrard SL65B £12.65
Garrard 1025T + cart. £5.97
Garrard 2025TC, Sonotone 9TAHC cart. £8.75
Garrard 401 £26.90
Garrard Zero 100 (Auto) £38.75
Garrard Zero 100 (Single) £36.55
BSR MP60 £9.65
Goldring GL72 £22.00
Goldring GL72/P £28.75
Goldring GL75 £29.50
Goldring GL75/P £42.75
Goldring GL85/P £55.50
Goldring 101/P.C. £22.00
Leak Delta £54.00
Wharfedale Linton + cart. £27.25
Thorens TD125 £57.50
Thorens TD125AB £92.00
Thorens TD150 Mk. II £27.50
Thorens TD150A Mk. II £33.50

AMPLIFIERS

Please add 75p post & packing

Amstrad 8000 Mk. II £16.25
Amstrad IC2000 £27.50
Amstrad Integra 4000 £21.95
Armstrong 521 (Teak cased) £43.95
Alpha Highgate 212 £24.95
Alpha Highgate FA300 £30.95
Alpha Highgate FA400 £34.50
Leak Delta 30 £47.65
Leak Delta 70 £56.50
Metrosound ST20E £43.45
Metrosound ST60 £45.95
Pioneer SA900 £92.00
Pioneer SA1000 £94.00
Rogers R/brook (Chassis) £35.00
Rogers R/brook (Cased) £37.00
Rogers R/bourne (Chassis) £41.95
Rogers R/bourne (Cased) £47.50
Rotel RA210 £24.50
Rotel RA310 £33.00
Rotel RA610 £49.95
Scanetra HT58 £29.75
Sinclair PR060 2 x Z30/PZ5 £14.95
Sinclair PR060 2 x Z30/PZ6 £17.00
Sinclair PR060 2 x Z50/PZ8 £17.00
Trans £21.25
Sinclair AFU (Filter Unit) £4.40
Sinclair 605 £18.50
Sinclair 2000 Mk. II £21.50
Sinclair 3000 Mk. II £29.25
Wharfedale Linton £37.50
Goodmans Max Amp £37.95
Eagle TSA149 £24.95
Eagle TSA151 £34.50
Teleton SAQ 206B £20.50
Teleton SAQ 307 £22.50

TUNERS

Please add 75p post & packing

Amstrad Multiplex 3000 £27.95
Armstrong 523 £39.50
Armstrong 524 £30.95
Rogers R/brook FET4 (Chassis) £31.00
Rogers R/brook FET4 (Cased) £35.00
Rogers R/bourne FET4 (Chassis) £43.00
Rogers R/bourne FET4 (Cased) £48.00
Sinclair PR060 (Module) £16.50
Sinclair 2000/3000 Tuner £31.95
Philips RH690 £33.00
Leak Delta FM (Cased) £54.75
Leak Delta AM/FM (Cased) £64.50

TUNER/AMPLIFIERS

Please add 75p post & packing

Armstrong 525 (Teak cased) £67.95
Armstrong 526 AM/FM £77.75
Leak Delta 75 £124.75
Philips RH781 £50.00
Philips RH702 £82.50
Teleton 2100 £29.95
Goodmans One Ten £99.50
Rogers Ravensbrook (Teak cased) £78.50
Rogers R/brook (Chassis) £72.75
Scanetra 1515 AM/FM £102.50
Scanetra 3030 FMG £110.50
Scanetra 1515 FM £74.50

SPEAKERS

Please add £1.25 for post & packing

Amstrad 138 £15.95
Wharfedale Denton 2 £28.30
Wharfedale Linton 2 £35.90
Wharfedale Melton 2 £47.25
Wharfedale Dovedale 3 £59.50
Celestion Ditton 120 £37.45
Celestion Ditton 15 £52.00
Celestion Ditton 25 £87.00
Celestion County (new prod.) £55.95
Goodmans Double Maxim £48.25
Goodmans Mezzo 3 £44.95
Goodmans Magister £74.00
Sinclair Q16 £112.50

CARTRIDGES

Please add 10p post & packing


Goldring G850 £3.25
Goldring G800 £5.75
Goldring G900E £8.50
Goldring G800 Super E £14.35
Shure M3D £3.85
Shure M44E £5.65
Shure M55E £5.85
Shure M75E Type 2 £10.35
Sonotone 9TAHC £1.75

£3.20*

Plus 35p P. & P.
Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25, 2025TC, 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR, McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B; £4.20 plus 35p P. & P. Also finished in walnut to match Japanese equipment—at no extra.

PHOTOELECTRIC KIT

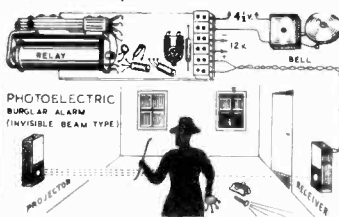CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a steady-light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT £2-60

Postage and Pack. 15p (U.K.)
Commonwealth:
SURFACE MAIL 25p
AIR MAIL £1.40
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price £1.25. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 30p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Large Lenses, Filter, etc. Price £1.85. Postage and Pack. 15p (U.K.). Commonwealth: Surface Mail 20p; Air Mail £1-10.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.
CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price £1.25. Postage and Pack. 10p (U.K.). Commonwealth 20p; Airmail 50p.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit. Price 75p. Post and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 30p.

YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

IDEAL FOR HOME CONSTRUCTORS



Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges.

EASY-TO-USE DISPENSERS



Size 5 (Savbit) 18swg, 18p (illustrated)
Size 19A (60/40 alloy) 18swg. 18p
Size 15 (60/40 alloy) 22swg. 22p

BIB WIRE STRIPPER AND CUTTER



Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings, 4&6 BASpanner ends, ground cutting edges Price 32p. Also available, de luxe Model 8. Price 58p.

NEW!

From Electrical and Hardware Shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE15) 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. **LATE NIGHT FRIDAY 7 p.m.**

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

E.M.I. WOOFER AND TWEETER KIT

£5.75 POST 25p

Comprising a fine example of a Woofer 10 1/2" dia. with a massive Ceramic Magnet, 44oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2" square has a special lightweight paper cone and magnet flux 10,000 lines. With Crossover condenser. Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in. £9 Pos 25p
MODERN TEAK DESIGN



8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts, 10in. 12 watts music power. **£3.75**

TEAK HI-FI SPEAKER CABINETS

Fluted Wood Fronts

MODEL "A". 20 x 13 x 9in. For 12in. dia. or 10in. speaker. **£9** Post 25p

MODEL "B". 18 x 10 x 9in. For 13 x 8in. or 8in. speaker **£5** Post 25p

MODEL "C". 18 x 8 x 6in. For 10 x 6in. or 6in. speaker. **£4** Post 25p

LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

BARGAIN AM TUNER. Medium Wave. Transistor Superhet **£4.50** Ferrite aerial. 9 volt.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. battery operated. **£3.50**

STEREO VERSION OF ABOVE £4.50.

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4in. **£12.50**

BARGAIN FM TUNER £8.85 as above less cabinet

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Full Ready built, with volume control. 9 volt battery operated. **£3.50**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£2.35** Post 15p

WAFER HEATING ELEMENTS


THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopiers and print drying. Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seedraising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series or parallel.

ONLY 40p EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

BAKER 12in MAJOR £9

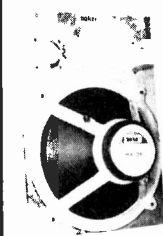

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11.50**

BAKER "BIG-SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" 12in. 25 watt **£8** Post Free 3, 8 or 15 ohms.

GROUP "35" 12in. 35 watt **£9** Post Free 3, 8 or 15 ohms.

GROUP "50" 15in. 50 watt **£20** Post Free 3, 8 or 15 ohms.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. **£49** Post Free




CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. Limited number! **£55**

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

1/2 in. Round 68p	1 1/2 in. Round 98p	Key "B" for above 8p
1 in. Round 75p	1 in. Round 98p	2 in. Round £2.05
Key "T" for above 5p	1 1/2 in. Round 98p	2 1/2 in. Round £2.30
1/2 in. Round 83p	1 1/2 in. Round £1.05	Key "C" for above 12p
1 in. Round 83p	1 1/2 in. Round £1.05	Flux Density 15,000gauss
1 in. Round 88p	1 1/2 in. Round £1.10	Useful response 20-17,000cps
1 in. Round 88p	1 1/2 in. Round £1.10	8 or 15 ohms models
1 in. Round 90p	1 1/2 in. Round £1.25	Key "E" for above 18p
Key "A" for above 5p	1 1/2 in. Round £1.43	1 in. Square with key £1.93

SLIDER VOLUME CONTROLS

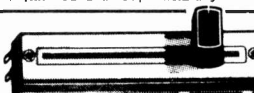

Available in both LOG and LINEAR type. Size 3 1/2 x 1 1/2 x 1/2 in. with knobs. 5K, 10K, 25K, 50K, 100K, 250K, 500K, 1 MEG, 2 MEG. **65p EACH**

E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 - 0.75in. Size 3 1/2 x 2 1/2 in. (Illustrated). Post 15p. **£1.25**

BALFOUR GRAM. MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 - 3/20. Size 2 1/2 x 2 1/2 in. Post 15p. **85p**

E.M.I. GRAM MOTORS. 120V or 240V a.c. 2,400 r.p.m. 2-pole 70mA. Spindle 1/2 x 1/4 in. Size 2 1/2 x 2 1/2 x 3/8 in. **75p** Post 15p

BAKER HI-FI SPEAKERS

HIGH QUALITY — BRITISH MADE

REGENT

12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver. Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps 3 or 8 or 15 ohm models

£8 Post Free

DE-LUXE Mk II

12in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone. Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-16,000cps 8 or 15 ohms models

£10 Post Free

SUPERB

12in. 20 watts

A high quality loudspeaker. its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps 8 or 15 ohms models

£15 Post Free

AUDITORIUM

12in. 25 watts

A full range reproducer for high power. Electronic Guitars, public address, multi-speaker systems, electronic organs. Ideal for Hi-Fi and Discos. Bass Resonance 12cps
Flux Density 15,000gauss
Useful response 25-16,000cps 8 or 15 ohms models

£14 Post Free

AUDITORIUM

15in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discos, Electronic instruments and the home. Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps 8 or 15 ohms models

£20 Post Free

Hi-Fi Enclosure Manual containing 20 plans, crossover data and cubic tables. 42p. Post Free.

CALLERS WELCOME • CUSTOMERS FREE CAR PARK

SPECIALISTS

(Export: Remit cash and extra postage.)

337 WHITEHORSE ROAD • CROYDON


OPEN 9-6 p.m. (WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

The *Litesold* CONQUEROR

An outstandingly simple and efficient new soldering tool, featuring a fully enclosed element and slip-on bits which can't seize. Five tip sizes available, $\frac{1}{16}$ in to $\frac{1}{4}$ in, covering most work with one iron only. Lighter and slimmer than comparable irons, and with better performance. A pleasure to use and excellent value. Mains or low voltages. Conqueror spring stand gives complete safety and convenience, and holds spare bits.

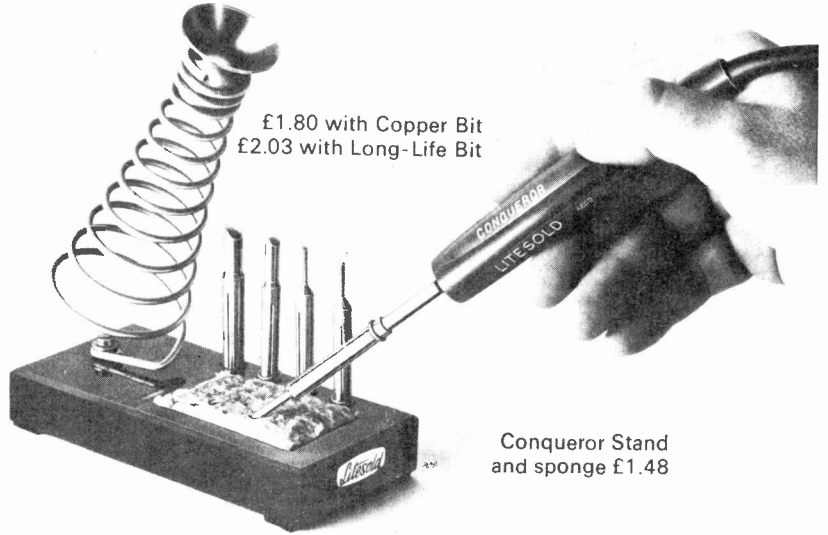

£1.80 with Copper Bit
£2.03 with Long-Life Bit

Conqueror Stand
and sponge £1.48

Note that we are now supplying a range of small pliers, cutters, soldering aids and other small tools for use in Electronics. Please ask for leaflet.

Please ask for leaflet 37/1016.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road · Croydon CR9 2LL

01-688 8589/4559

B.H. COMPONENT FACTORS LIMITED

POLYESTER CAPACITORS MULLARD C280 250V
 μ F: 0-01, 0-015, 0-022, 0-033, 0-047, 3p each; 0-068, 0-1, 0-15, 4p each; 0-22, 5p; 0-33, 7p; 0-47, 8p; 0-68, 10p; 1-0, 13p; 1-5, 20p; 2-2, 23p.

MULLARD POLYESTER CAPACITORS C296 SERIES
 160V: (μ F) 0-01, 0-015, 0-022, 2p; 0-047, 0-068, 3p; 0-15, 0-22, 4p; 0-33, 5p; 0-47, 6p; 0-68, 1-0, 10p.
 400V: (μ F) 0-001, 0-0015, 0-0022, 0-0033, 0-01, 2p; 0-015, 0-033, 3p; 0-068, 4p.

MINIATURE ELECTROLYTIC MULLARD C426 SERIES (5p each)
 (μ F/V) 0-64/64, 1-6/25, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/6-4, 125/16, 200/6-4, 200/10, 320/6-4.
MULLARD C437: (μ F/V) 64/64, 9p; 160/25, 9p; 160/40, 11p; 640/6-4, 9p; 1600/6-4, 14p.

ELECTROLYTIC CAPACITORS, Tubular and large can
 (μ F/V) 2-5/50, 3p; 4/10, 6-4/50, 16/15, 20/25, 25/15, 25/25, 40/6, 64/10, 200/6, 250/10, 4p; 10/6, 10/50, 25/50, 32/50, 50/10, 64/25, 100/25, 5p; 50/50, 64/40, 250/15, 1,000/3, 6p; 100/50, 250/25, 400/10, 500/10, 500/12, 640/10, 1,000/6, 8p; 500/25, 10p; 500/50, 12p; 1,000/12, 10p; 1,000/25, 2,000/12, 2,500/12, 15p; 1,000/50, 35p; 2,000/25, 25p; 2,500/25, 30p; 3,000/50, 65p; 5,000/50, 85p.

CERAMIC PLATE CAPACITORS
 750V: (pF) 5, 10, 25, 40, 70, 100, 220, 22p; 22pF 50V, 21p. (μ F/V) 0-001/50, 0-0047/30, 0-01/50, 0-01/350, 2p; 0-022/50, 21p; 0-047/30, 3p; 0-1/30, 4p; 0-1/100, 5p.

CARBON FILM RESISTORS $\frac{1}{2}$ W 5%, 10 ohms—1M, 1p each, or 100 for 55p.

SPECIAL RESISTOR KITS ($\frac{1}{2}$ W 5% CARBON FILM)
 10E12 Kit: 10 of each E12 value, 10 ohms—1M, a total of 610, £2-80 net
 25E12 Kit: 25 of each E12 value, 10 ohms—1M, a total of 1,525, £6-50 net

VEROBOARD							
24 × 5in	25p	IN4001	6p	2N706	10p	AC127	15p
24 × 3in	23p	IN4002	7p	2N708	13p	AC128	20p
32 × 5in	17p	IN4003	8p	2N1303	17p	BC108	11p
32 × 3in	23p	IN4004	9p	2N3055	60p	BFY51	20p
24 × 3in	25p	IN4014	6p	2N3866	80p	OC71	12p
24 × 1in 2 for 12p	12p	7400N	15p	7440N	25p	OC75	15p
24 × 5in (plain)	12p	7401N	15p	7470N	30p	OC83	18p
24 × 3in (plain)	11p	7401N	15p	7483N	120p	OC84	18p
5 × 3in (plain)	20p	7430N	15p	7493N	80p	μ L914	30p
Insertion tool	54p	Tunnel Diodes: IN3717 £1; TD715, TD716 50p					
Track cutter	40p						
Pins, pkt. 25	8p						

2 pin DIN Plug, 12p;	Panel Neon 240V, Red	15p
Socket, 10p;	RF Chokes (μ H) 0-22, 2-2, 12, 22	8p
3 pin DIN Plug, 13p;	PVC wire 7/0076, 5 · 10yd	30p
Socket, 10p;	PVC wire 14/0076, 5 · 10yd	30p
5 pin DIN Plug, 180 · 15p;	Neon bulb 80V wire ended	5 for 20p
Socket, 12p;	Min. push button, push to make	50p
Transistor Book, 40p	Mains transformer 32-0-32 at 150mA	10p

C.W.O. only. P. & P. 10p on orders below £5.
 Discount: £10—10%, £20—15%

Dept. P.E. 61, CHEDDINGTON ROAD, PITSTONE
 Near LEIGHTON BUZZARD, BEDS LU7 9AQ
 Tel.: Cheddington 668446
 Inquiries—S.A.E. List 5p. Callers by appointment only.

GUNTON ELECTRONIC IGNITION KIT £7.95 + 35p P. & P.

★ ALL HIGH QUALITY COMPONENTS ★
 Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- Continual Peak Performance
 - Up to 20% reduced fuel consumption
 - Easier All-weather Starting
 - Increased Acceleration and Top Speed
 - Longer Spark Plug Life
 - Increased Battery Life
 - Elimination of Contact Breaker Burn
 - Purer Exhaust Gas Emission
- 12 volt only—state pos. or neg. earth. Supplied with illustrated assembly and fitting instructions, with details for fitting all types of tachometers. Can be built in an evening and fitted in 15 minutes. Spare snap-on connectors for coil, etc. Call in for a demonstration. S.A.E. all enquiries please. Ready built unit, guaranteed 5 years—£9 95 + 35p P. & P.




"SCORPIO" COMPONENTS: Transformer £1-85 + 25p P. & P. Fibreglass printed circuit board 65p + 10p P. & P. Silver-grey stove enamelled steel and aluminium case with heat sink 75p + 20p P. & P.

ELECTRONICS DESIGN ASSOCIATES
 82 BATH STREET, WALSALL WS1 3DE

NEW LIGHT SENSITIVE SWITCHES

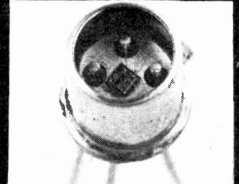TWO NEW LITE-IC'S—
 COMPLETE LIGHT SWITCHES
 CONSISTING OF
 PHOTODETECTOR + AMPLIFIER
 + TRIGGER + DRIVER—all in a
 single 4mm. dia. can.



NEW FEATURES: WIDER
 VOLTAGE SUPPLY RANGE—
 LITE-IC 2 11V to 20V
 LITE-IC 3 20V to 30V
 HIGHER OUTPUT CURRENT
 DRIVE—to 40mA.

APPLICATIONS INCLUDE: Relay, Triac or Logic Drive. Automatic Light Switching and Door Control, Beam/Break Detection—Burglar Alarm, Batch Counting and Code Reading.
PRICE ONLY 95p each with full operating instructions. 10 off for 80p each. Postage free in the U.K. P.O./CHEQUES made payable to ELBON and crossed (with order).
LITE-IC, ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated telescopic aerial, for peak short wave and VHF listening. Push-pull output using 600mW transistors, Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced gauged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS


£8.50

P.P. & INS. 50p
(OVERSEAS P. & P. £1)



ROAMER EIGHT Mk. I


NOW WITH VARIABLE TONE CONTROL

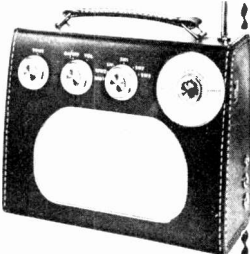

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced gauged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6.98** P.P. & INS. 45p
(OVERSEAS P. & P. £1)


ROAMER SEVEN Mk. IV

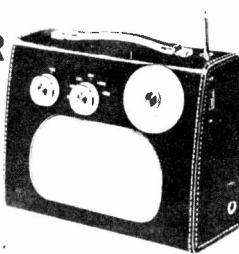

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced gauged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 10p (FREE with parts).

TOTAL BUILDING COSTS **£5.98** P.P. & INS. 45p
(OVERSEAS P. & P. £1)


ROAMER SIX

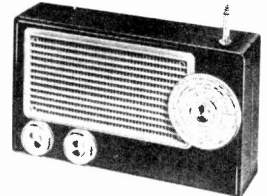

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages 6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Easy build plans and parts price list 15p (FREE with parts).

TOTAL BUILDING COSTS **£3.98** P.P. & INS. 30p
(OVERSEAS P. & P. £1)


POCKET FIVE

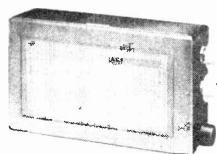

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages-5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2in x 1 1/2in x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2.29** P.P. & INS. 21p
(OVERSEAS P. & P. 63p)


TRANSONA FIVE

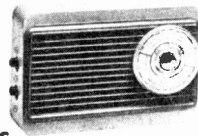

5 TRANSISTORS AND 2 DIODES
3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/2in x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts).


TOTAL BUILDING COSTS **£2.50** P.P. & INS. 24p
(OVERSEAS P. & P. 63p)

TRANS EIGHT

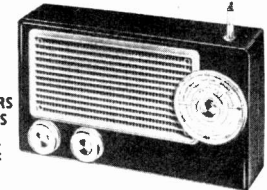

8 TRANSISTORS AND 3 DIODES
6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

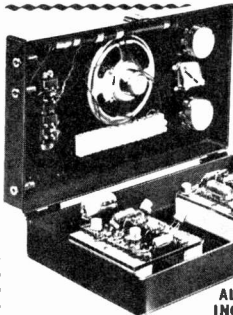TOTAL BUILDING COSTS **£4.48** P.P. & INS. 32p
(OVERSEAS P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 slider switches: 3 Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 4in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

ALL PARTS INCLUDING CASE AND PLANS **£5.50** P.P. & INS. 32p
(OVERSEAS P. & P. £1)

FULL AFTER SALES SERVICE

★ Callers side entrance Barratts Shoe Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday

RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £ please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for

Name

Address

P.E. 47

S.C.S. COMPONENTS

P.O. BOX No. 26 • WEMBLEY • MIDDLESEX HA0 1YY

the "PROFESSIONAL" amateur supplier

NEW
SIGNETICS DATA BOOK £1 each
postage and packing 10p.
Book one digital bipolar circuits—
contains full Data Sheets and
Application notes on complete
Signetics range of Digital devices.
596 pages.
Book two covers full range signetics
linear devices including Audio
Amplifiers and preamplifiers.
240 pages.

SPECIAL OFFERS

MEL12	50p	LM301A	90p
EM401	8p	2N5459	49p
TT3643	30p	BC108	10p
MA741	34p	2N3643	25p
2N3648	£1.10	BC178	22p
IN914	6p	2N2646	77p
BC107	10p	EP404	80p
CI06Y1	50p	CI0601	55p
UA709	31p	UA748	34p
1MΩ Trimpots			11p

Texas 20 + 20 watt Stereo.
Complete kit of Semiconductor £6.30

*** 2N3055 Si NPN power
TX 115 watt 35p ***
send S.A.E. for priced list of
all parts for any E.T.I. constructional
project.

SIGNETICS NE555V Timer
first time offered to constructors.
Features

- Timing from microseconds through 1Hr.
- Can either free run or hatch.
- Adjustable duty cycle.
- Time delays can be reset.
- Temperature stability 0.005% per C.
- Operates from 4 to 15 volts for 1% change in timing.
- Timing can be changed 10-1 with control voltage.
- Output can source or sink 100 M.A.
- 8 pin plastic D.I.L. package plus Data and Application Notes 90p

SEMICONDUCTORS

AA119 9p	BC137 20p	BF179 30p	OA91 7p
AA119 10p	BC139 25p	BF180 35p	OA95 7p
AA130 10p	BC142 21p	BF184 20p	OA200 7p
AA133 10p	BC143 23p	BF185 20p	OA202 10p
AC107 34p	BC147 12p	BF194 15p	OA2223 45p
AC126 25p	BC148 10p	BF195 15p	OA2230 45p
AC127 25p	BC149 12p	BF196 15p	OC28 65p
AC128 25p	BC152 20p	BF197 15p	OC35 50p
AC141K 25p	BC153 20p	BF200 35p	OC36 65p
AC142K 18p	BC157 15p	BF222 30p	OC44 15p
AC153 25p	BC158 12p	BF224J 15p	OC45 15p
AC153K 22p	BC159 15p	BF256L 30p	OC70 15p
AC175K 36p	BC170 15p	BF256LC 34p	OC71 11p
AC176 25p	BC171 15p	BF36A 37p	OC74 25p
AC176K 25p	BC171A 17p	BF717A £1.22	OC75 23p
AC187 25p	BC177 20p	BFX37 30p	OC170 23p
AC187K 25p	BC177B 23p	BFX84 23p	R2008 £3.5
AC188K 25p	BC178B 16p	BFX85 25p	R2009 £2.5
AC193K 25p	BC179 20p	BFY50 20p	R2010 £2.5
AC194K 27p	BC182L 10p	BFY51 20p	SP8385 £1.0
ACY20 20p	BC182LB 10p	BFY52 20p	TA7000 £2.4
ACY21 20p	BC183 10p	BFY90 59p	TA7100 £1.3
ACY22 12p	BC183L 10p	BSX20 15p	TBA500 £2.0
AD143 45p	BC183LB 10p	BSX60 50p	TBA510 £2.0
AD161 35p	BC184LC 12p	BSX61 35p	TBA520 £2.5
AD162 35p	BC186 25p	BT106 85p	TBA520Q £2.5
AF115 25p	BC187 25p	BU105/102 £2	TBA530 £1.8
AF117 20p	BC208A 14p	EY126 15p	TBA530Q £1.8
AF112 30p	BC212 10p	EY127 15p	TBA540 £2.0
AF124 25p	BC212L 12p	EY147 £1.04	TBA550 £3.0
AF126 20p	BC212LA 13p	EY164 35p	TBA550Q £3.0
AF127 20p	BC213L 12p	BZY88 ser 9.5p	TBA570Q £1.2
AF139 30p	BC214 15p	BZY94 ser 9.5p	TBA750 £1.4
AF179 25p	BC214L 15p	BR100 15p	TBA750Q £1.4
AF178 35p	BC250B 14p	BRC4443 90p	TIC46 40p
AF170 60p	BC261 16p	BRY39 30p	TIP29A 50p
AF239 40p	BC268 11p	E1222 40p	TIS60M/61M 37p
ASZ17 50p	BC308A 17p	E5024 40p	TIS61 20p
BA102 30p	BC317 20p	GET102 39p	TIS91 17p
BA145 15p	BCY21 96p	GET103 25p	2N404 15p
BA148 15p	BCY31 40p	IS921 25p	2N697 12p
BA154 9p	BCY42 30p	IS923 12p	2N706 9p
BA155 10p	BCY70 15p	ME0404 11p	2N708 12p
BA163 90p	BCY71 20p	ME0412 15p	2N753 10p
BAX12 12p	BCY72 15p	ME0413 12p	2N919 45p
BAW63 36p	BCY89 97p	ME0462 19p	2N920 42p
BAW65 36p	BD115 75p	ME2002 8p	2N1302 17p
BAW67 35p	BD124 80p	ME4003 12p	2N1304 21p
EB105 37p	BD131 75p	ME4102 10p	2N1306 24p
BBY20 37p	BD132 80p	ME4104 8p	2N1307 24p
BC107 10p	BD135 75p	ME6002 12p	2N1308 24p
BC107B 12p	BD175 44p	ME6101 12p	2N1309 24p
BC108 10p	BD181 90p	ME6102 13p	2N3053 20p
BC108A 10p	BD184 61p	ME8001 12p	2N3054 50p
BC108C 15p	BF121 25p	ME8003 13p	2N3055 55p
BC109 12p	BF123 30p	MEF104 34p	IN914 6p
BC113 15p	BF125 25p	MEL11 30p	IN916 10p
BC116 20p	BF127 30p	MPB112 34p	IN4148 6p
BC117 20p	BF153 20p	MPB113 40p	
BC119 30p	BF154 20p	OA47 10p	
BC121 25p	BF160 25p	OAB1 10p	
BC125B 25p	BF171 45p	OA85 12p	
BC136 20p	BF178 25p	OA90 8p	

TERMS. Retail mail order subject to £1 minimum order. Cash with order only. Trade and educational establishments M/AC on application (minimum £5). Postage 10p inland, 25p Europe. GUARANTEE. All goods carry full manufacturer's warranty. Special Enquiries, etc. Please enclose stamped addressed envelope.

ELECTROKIT

Now available from one company are complete kits for many of the articles published in the Electronics, Radio and TV Journals. Examples of our range are:

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), £10.50, including P. & P. This kit includes all the parts for the assembly of this popular and reliable system. The hardware and instruction data are included.

ELECTRONIC PIANO (P.E. Sept. 1972), price £41, including P. & P. This kit consists of all the resistors, capacitors, presets and semiconductors to complete this project. The hardware and keyboard are not included in the kit.

DRILL SPEED CONTROLLER (E.E. Aug. 1972). Kit consists of resistors, rectifiers, thyristor and tag board as specified in the article, price £1.05, including P. & P. Kit with M.K. box, plate and switch, price £2.05, including P. & P. We shall also be offering kits for most articles published in the P.E. and other popular electronics magazines and will be pleased to quote prices.

Send for details of Light Dimmer and Windscreen Wiper Delay Kits (please enclose S.A.E.). At present we can only accept orders by post but if you have any inquiries please phone 01-286 5282.

ELECTROKIT

126 Headstone Road • Harrow • Middlesex

NOT JUST A RADIO BUT A COMPLETE COMMUNICATIONS RECEIVER

BATTERY/MAINS PORTABLE RECEIVER

WHAT RADIO PRICED AT UNDER £120 GIVES YOU SUCH A VARIED CHOICE OF TRANSMISSIONS?

CASH PRICE £49.50 + 50p P. & P. or £14.50 dep. + 50p P. & P. and 6 months at £7 (£56.50)

8 WAVEBANDS
The most exciting radio ever!

Picks up ALL THE USUAL BBC Programmes ★ All the new local radio stations ★ Continental ★ World-wide transmissions ★ Pop Pirates ★ Radio Hams ★ Aircraft ★ Shipping ★ Police ★ Taxi ★ RAC ★ AA ★ Fire Brigade ★ TV Sound ★ Ambulances and 1,000s more.

THE BEST PORTABLE RADIO EVER MADE! We think so. What radio priced at under £120 gives you such a varied choice of transmissions? As well as the standard long and medium wavebands it has three short wave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE VHF BANDS, truly a complete WORLD-WIDE communications Receiver. JUST THINK! one minute you can be listening to your favourite BBC programme and then—at the flick of a switch—you can tune into the control tower and hear a "crippled airliner" being talked down to safety. Or listen to the trawlers and ocean-going liners—Eavesdrop on the taxi-cabs, fire brigades, ambulances, AA, RAC and 100s of other RT mobiles—even your local police! Extensive shortwave coverage can give you Australia, Pakistan, Luxembourg, North America, Far East, etc., you name it—it gets it! Manufactured by one of the world's leading specialists in communications and TV equipment, each set carries a **FULL 3-YEAR WRITTEN GUARANTEE.** Beautifully finished in Teak Wood and Stainless Steel—will add distinction to any living-room. Completely portable 12in x 9in x 4in, using standard batteries—or can be plugged directly into mains—14 transistors, 6 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external-teleopic antenna—with sockets for additional aeriels. Complete with beat frequency oscillator for the real enthusiast or car aeriels. Automatic Drift-Free Reception. Tone control. Fine squelch control. Hi-Fidelity earphone for private listening, local DX switch. **FREQUENCIES:** Long W 150-350 Kcs. Medium W 540-1605 Kcs. Marine 1.6-4 Mcs. Short W 1.7-9 Mcs. Short W/2 9-22 Mcs. FM (VHF) 88-108 Mcs. Aircraft (VHF) 108-136 Mcs. Public Service (VHF) 148-174 Mcs. **THE ULTIMATE** in communications receivers—used by professionals and amateur enthusiasts all over the world. **INSTANT CASH REFUND** if not overwhelmed by the superb tone clarity and performance range.

SCIENTIFIC AND TECHNICAL (PEI1)
507-511 LONDON ROAD, WESTCLIFF, ESSEX

FERRANTI

PROFESSIONAL
GRADE
SEMICONDUCTORS

New Low Prices!

All devices Top grade, Brand new, Fully guaranteed

BFS59 13p	ZTX304 19p	ZTX503 12p	ZS142 30p	KSO36A 17p
BFS60 18p	ZTX310 8p	ZTX504 39p	ZS170 9p	KSO39A 17p
BFS61 18p	ZTX311 9p	ZTX510 15p	ZS171 11p	KSO43A 17p
BFS96 13p	ZTX312 9p	ZTX530 19p	ZS172 14p	KSO47A 17p
BFS97 21p	ZTX313 10p	ZTX531 20p	ZS174 15p	KSO51A 17p
BFS98 18p	ZTX314 11p	ZTX550 15p	ZS176 21p	KSO56A 17p
ZTX107 8p	ZTX320 28p	ZTX551 20p	ZS178 34p	KSO62A 17p
ZTX108 7p	ZTX330 13p	2N3055 65p	ZS270 10p	KSO68A 17p
ZTX109 10p	ZTX331 14p		ZS271 14p	KSO75A 17p
ZTX114 20p	ZTX382 11p	*DIODES*	ZS272 16p	KSO82A 17p
ZTX212 12p	ZTX383 13p	ZS120 7p	ZS274 17p	KSO91A 17p
ZTX213 12p	ZTX384 16p	ZS121 9p	ZS276 23p	KS100A 17p
ZTX214 13p	ZTX450 15p	ZS122 11p	ZS278 33p	KS110A 17p
ZTX300 10p	ZTX451 15p	ZS123 14p		KS120A 17p
ZTX301 11p	ZTX500 10p	ZS124 16p	*ZENERS*	KS130A 17p
ZTX302 15p	ZTX501 11p	ZS140 22p	KSO30A 17p	KS150A 17p
ZTX303 12p	ZTX502 15p	ZS141 39p	KSO33A 17p	KS180A 17p

GEMINI AMPLIFIER

Set of Main Amp. semiconductors (stereo)	£5-60
Set of Pre-amp. semiconductors (stereo)	£1-55
Set of Power Supply semiconductors	£2-15
Main amp. printed circuit board	£1-45
Pre-amp. printed circuit board	£1-95
Power Supply printed circuit board	£0-60
(P.C.B.'s are glass fibre and are roller tinned and drilled)	
Set of GEMINI TUNER semiconductors	£6-60

P. E. ELECTRONIC PIANO

350 ZS170	£20-00	110 ZTX300	£9-50
24 ZN7474E	£14-40	14 KSO47A	£2-30

Postage & packing 10p. Free over £2. Send SAE for Ferranti data.

WE CAN SUPPLY ANY FERRANTI DEVICE. Send SAE for quotation.

DAVIAN ELECTRONICS, P O BOX 38, OLDHAM, LANCs

UHF-AERIALS

Suitable for colour and monochrome reception.
PLANAR folded dipoles + MESH reflectors



ILLUSTRATED UHF.50

Aerial Arrays designed for fringe area reception

UHF.50	£3-90
UHF.18	£2-60

Without alochrome process for loft/window sill mounting	UHF.10	£1-95
chm Bkt & 5° angled mast	C.5	£1-50
wall Bkt & 5° angled mast	W.5	£1-00

(Available by mail order only when ordering UHF.50-UHF.18 or FM Aerials)

VHF/FM AERIALS

Aerial Array single-dipole	B.21	£1-30
Aerial Array dipole-reflector	B.22	£1-65

CAR-AERIALS

Wing mounting spring Aerial 3-section extends to 48 1/2"	A.6	£1-60
Motorised electric Aerial complete with details & switch. 12V poss or neg. 5-section extends to 40"	A.7	£6-00

PRE-AMPLIFIERS

Suitable for colour and monochrome. freq coverage 40-860 MHZ-14dB Gain

Weather proof Pre-Amplifier	T1	£5-25
240V.A.C. Power Unit	T1/PU	£4-25

Low-Loss co-axial cable sold in multiples of 5 meters at 40p, nylon cable clips per 100 at 30p. Aerial switches at 90p Co-axial plugs at 8p.

P & P. UHF & VHF/FM Aerials 50p, Car Aerials-Amps & cable etc., 25p.

When ordering UHF Aerials, please state channel combination or transmitter location. S.A.E. with enquiries please.

Terms P.O./Cheque with order. U.K. Mainland only.

AVEE (COMMUNICATIONS) LTD

Dept P.E.1. 96a Plains Avenue, Maidstone, Kent
Telephone Maidstone 56962

BUILD YOUR OWN

LIQUID OIL WHEEL PROJECTOR

SUITABLE FOR DISCO OR HOME ENJOYMENT

TOP QUALITY

6 inch dia. MULTICOLOURED OIL WHEEL
PLUS

1 R.P.M. MINIATURE GEARED MOTOR

Complete Kit £6-50 inc. postage

C.T. ELECTRONICS

267 ACTON LANE, LONDON, W.4 01-994 6275

SURPLUS ELECTRONICS WAREHOUSE NOW OPEN AT

20-24 BEAUMONT ROAD, LONDON, W.4

Thousands of component and equipment bargains

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72)
MOTOROLA MC1310P

EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz—15kHz. Distortion: 0.3%. I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8-12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB

(Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. & Instructions. Only £3-50 post free.

LIGHT EMITTING DIODE (Red)

Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only 35p + p.p.

MC1310P only £2-77 + p.p. 6p

SPECIAL OFFER

IN4001 50V 1A RECT. DIODES. Full Specification Devices. ONLY 5p each
709° DIL 14 PIN OP AMPS. Full Specification Devices. ONLY 34p each

Fi-Comp Electronics

BURTON ROAD, EGGINTON, DERBY DE6 6GY

JUST PUBLISHED '73 AUDIO-TRONICS

The great new 1973 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 48 newspaper size pages—many in full colour—are packed with 1,000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communication's Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio Accessories, see the great new Lasky's Credit Plan Scheme—enabling you to buy your ideal choice of equipment on easy terms. Send your name and address and 15p for post and inclusion on our regular mailing list.

LEAK TEAK CASES

Teak or Walnut case for Stereofetic tuner only.

LIST PRICE **LASKY'S PRICE** £2.50 C & P 25p

Double case to hold Stereo 30 or Stereo 70 and Stereofetic tuner in Teak or Walnut.

LIST PRICE **LASKY'S PRICE** £4.95 C & P 35p

LEAK TRUSPEED

2-speed 45 and 33 $\frac{1}{2}$ rpm belt drive turntable complete with plinth, cover and Shure cartridge.

LIST PRICE £69.50

LASKY'S PRICE £47.50 C & P £1.50


SINCLAIR PHASE LOCK LOOP STEREO FM TUNER

Incorporates varicap diodes, printed circuit, coils, squelch circuit I.C. Decoder, etc., supplied completely built and tested and ready to

be mounted into any cabinet you choose. It may be used with any High Fidelity Amplifier. Power requirements 25/30V DC.

LIST PRICE **LASKY'S PRICE** £15.75 C & P £25.00

BSR TAPE DECK SCOOP

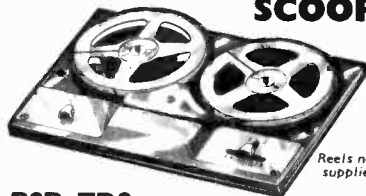

Reels not supplied

BSR TD2

FANTASTIC VALUE, ONLY Lasky's can offer you a tape deck at such an amazing price. The BSR TD2 tape deck operates by a simple reliable mechanism using the minimum of controls.

With $\frac{1}{2}$ track mono heads. Incorporates fast wind and fast rewind, records at 3 $\frac{1}{2}$ ips, giving up to 3 hrs playing time, takes up to 5 $\frac{1}{2}$ in. spools. Size 13in. 8 $\frac{1}{2}$ in. front to rear, 2 $\frac{1}{2}$ in. below plate, 1 $\frac{1}{2}$ in. above plate.

ALSO SUITABLE FOR USE AS A TAPE TRANSPORTER

LASKY'S PRICE £8.95 C & P 35p


BELTEK C5700 8 TRACK

Stereo car Player

Accepts all standard pre-recorded 8 track stereo cartridges. Features include automatic head cleaner, channel select and channel repeat push buttons, slider type volume and tone controls, channel balance. Output 5 watts per channel, frequency response 50Hz-10KHz. Output imp. 4 ohms, size 4 $\frac{1}{2}$ (W) x 1 $\frac{1}{2}$ (H) x 6 $\frac{1}{2}$ (D) in. Operates on 12V DC negative earth. Beautifully styled with black ivory and chrome trim.

BELTEK C5700 complete with mounting brackets and 8 track pre-recorded demonstration cartridge.

£19.75 C & P 30p

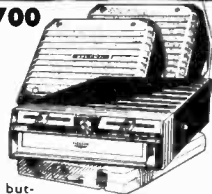

BELTEK R5310 FM TUNING ADAPTOR

Matches the C5700, the ideal car stereo system.

LASKY'S PRICE £18.95 C & P 25p

Add £3.75 to any BELTEK car player for pair of FANTAVOX KS701 car soakers.

AKAI TAPE RECORDER SCOOP!

(C & P 75p on all Tape Decks.)

AKAI 4000D illustrated

List Price £93.65

Lasky's Price £61.50

AKAI I720L

List Price £87.36

Lasky's Price £58.95

AKAI X1800SD

List Price £162.79

Lasky's Price £111.50

AKAI X200D

List Price £157.93

Lasky's Price £106.50

2 CSS-8 Speakers

List Price £25.00 (pair)

Lasky's Price £15.95


C & P 50p

2 ADM 11/8 mics.

Suitable for use on all Akai tape recorders. List Price £11.90.

Lasky's Price (pair) £7.50. C & P 15p.

NEW WELER MINI WORKSHOP KIT MODEL 600K

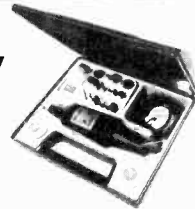

Powered by a 25,000 rpm, 115V, 75A Universal motor. This small versatile, easy to handle, power tool is ideal for handymen, hobbyists and professionals. The wide selection of bits helps you grind, sharpen, drill, rout, cut, etc. Perfect for delicate work and hard to reach places. The complete MINI-WORKSHOP is housed in a strong plastic carrying case. For 240V a.c. mains operation.

MODEL 600K place Kit contains: ● Model 600 Power Unit ● Accessory Caddy ● 8 Grinding/Sharpening Bits ● 3 polishing Wheels ● 4 Cleaning Bits ● 8 Abrasive Discs ● 3 Abrasive Bands ● Expanding Drum ● Drill Bit ● Mandrell ● Chuck Wrench ● Dressing Stone ● Plastic polish ● Jewellers Rouge ● Complete with owners' manual ● Size of power unit only 7 $\frac{1}{2}$ in.

LEAK SPEAKERS

150 Speakers (pair)	£38.95	C & P
250	£48.95	£2.50
600	£68.75	

DIGITAL CLOCK

EXCLUSIVELY FROM LASKY'S

The clock measures 5 $\frac{1}{2}$ " (W) x 2 $\frac{1}{2}$ " (H) x 3" (D) (over-all from front of drum to back of switch). SPEC: 210/240V a.c. 50Hz operation; switch rating 250V, 3A. Complete with instructions. NOW WITH ILLUMINATED DIAL COMPLETE WITH KNOBS FEATURES: ● MAINS OPERATION ● 12-HOUR ALARM ● AUTO "SLEEP" SWITCH ● HOURS, MINUTES AND SECONDS READ-OFF ● FORWARD AND BACKWARD TIME ADJUSTMENT ● SILENT OPERATION ● SHOCK AND VIBRATION PROOF ● BUILT IN ALARM BUZZER

SPECIAL QUOTES **LASKY'S PRICE** £6.75 C & P 25p



BSR TD8S

8 TRACK STEREO CARTRIDGE PLAYER

The TD8S is suitable for use with most modern stereo amplifiers and delivers a pre-amp output of 125mW. Power requirements: 210/250V AC, 50Hz. Frequency response: 50Hz-10KHz. 4 pole dynamically balanced synchronous motor. Black and woodgrain plastic cabinet. Size: 8 $\frac{1}{2}$ (W) 3 $\frac{1}{2}$ (H) 10 $\frac{1}{2}$ (D) in.

List Price £24.20

LASKY'S PRICE £17.95



Garrard Record Players

SP25 Mk. III Deck Only



SP25 Mk III	£10.85
AP76	£18.75
SL95B	£32.50
SL95B on base with 9TA cart.	£44.00
SL72B	£23.95
401	£28.95
40B	£9.50
2025TC with stereo 9TA cart.	£7.95
Zero 100	£39.95
Zero 100S	£37.50

NEW RECORD PLAYER MODULES

These new "Module" systems from Garrard and Lasky's enable you to buy your record player complete with attractive wood plinth, tinted acrylic dust cover and high quality compatible stereo magnetic cartridge together offering optimum performance and appearance.

GARRARD MODULES

Garrard SP25 Mk. III turntable with Shure M75/6 cartridge	£23.95
Garrard AP76 turntable with Shure M75/6 cartridge	£33.95
Garrard AP96 turntable (single play version of SL95B)	£38.75
Garrard Zero 100S turntable with Shure M93/E cartridge	£52.75
C. & P. 75p.	

LASKY MODULES

Lasky's (Garrard) SP25 Mk. III turntable with Goldring G800 cartridge	£20.50
Lasky's (Garrard) AP76 turntable with Goldring G800 cartridge	£30.50
Lasky's (Goldring) GL75 turntable with Goldring G800 cartridge	£45.00
Lasky's (Goldring) GL75 turntable with Goldring G800/E cartridge	£49.50
C. & P. 75p.	

Lasky's

MAIL ORDERS AND CORRESPONDENCE
3-15 CAVELL STREET
LONDON E1 2BN 01-790 4821

West End and City Branches

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01- 636 0845

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1. Tel: 01-636 2605

Open all day 9a.m. - 6p.m. Monday to Saturday.

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1p.m. Saturday

gspk (sales)

quite simply — the best

RESISTORS

FULL RANGE OF CARBON FILM RESISTORS

½W (range 4.7 ohms to 470K) 1p each
 ¼W and ⅓W (range 4.7 ohms to 10 Megs) 1p each
 1W (range 4.7 ohms to 10 Meg) 2p each
 2W (range 4.7 ohms to 10 Meg) 3p each

These Miniature High Stability carbon Film Resistors have negligible noise factor.
 All Resistors ±5 per cent (except values over 4.7 Megs). These Resistors are even lower in price than most 10 per cent and older carbon composition types.

PRE-SET POTENTIOMETERS

Standard values of pre-sets from 100 ohms to 5 Meg—
 Standard/miniature 7p each Sub-miniature 5p each

SIEMENS PROFESSIONAL CAPACITORS

POLYCARBONATE AND POLYESTER

Voltage	Capacitance	Price
100V	0.1µF	6p
100V	0.15µF	6p
100V	0.22µF	6p
100V	0.33µF	9p
100V	0.47µF	10p
100V	0.68µF	15p
250V	0.01µF	5p
250V	0.015µF	5p
250V	0.022µF	5p
250V	0.033µF	6p
250V	0.047µF	6p
250V	0.068µF	6p
250V	0.1µF	6p

ELECTROLYTIC

Voltage	Capacitance	Price
10V	22µF	7p
10V	47µF	11p
16V	47µF	7p
25V	10µF	7p
25V	100µF	9p
25V	220µF	11p
25V	470µF	14p
25V	1,000µF	12p
25V	2,200µF	42p
35V	4.7µF	7p
35V	220µF	14p
100V	10µF	8p
100V	22µF	9p
100V	47µF	14p

SPECIAL OFFER

Bumper Bundle of power transistors, capacitors and diodes. Retail value £5. Yours for only **£1.50**. Offer valid for limited period only.

SEMICONDUCTORS

Here are just a few examples of our **LOW** Semiconductor prices. Many more semiconductors available all at equally sensational prices. **NOV**

1+	25+	BZY88C Series	1+	25+	1+	25+
AC127	24p	E12 (2.7V-30.0V)	OC76	21p	OC170	21p
AC128	19p	---	IN4001	6p	IN4002	6p
AC176	15p	---	IN4003	7p	IN4004	8p
ACY18	18p	NKT210	IN4005	10p	IN4006	12p
AD161	27p	NKT211	IN4007	18p	IN4148	4p
AD162	27p	NKT212	2N1302	16p	2N1304	21p
AF139	28p	NKT213	2N1613	14p	2N1711	15p
BC107	9p	NKT214	2N2904	29p	2N2905	24p
BC108	8p	NKT218	2N2906	19p	2N2907	22p
BC109	9p	NKT219	2N3053	17p	2N3054	49p
BC147	8p	NKT223	2N3055	57p	2N3055	57p
BC148	8p	NKT224	(BD130)			
BC149	8p	NKT242				
BCV70	14p	NKT243				
BCV71	20p	NKT401				
BCV72	14p	NKT402				
BDY20	91p	NKT403				
BFY29	24p	NKT453				
BFX30	24p	OA47				
BFY50	19p	OA79				
BFY51	18p	OA90				
BFY52	19p	OC70				

NUMEROUS OTHER ITEMS AVAILABLE INCLUDE:

Switches. Comprehensive range of N.S.F. Toggle switches and Rotary Wafer switch kits (to enable you to make your own switch to your own specification).
 Copper laminate and all materials available to make your own printed circuit boards.
 Lamps and lampholders for every requirement. **Ready Built Circuits and Modules.**
 Freezer and Cleaner aerosol sprays.
 Jack plugs and sockets.
 Variety of speciality products.
 Recording Tape.

All orders value £2 or over post free. Other orders please add 10p P. & P. We only sell new products—do not confuse with "seconds" or surplus stock. Because of our keen prices we regret the prices apply to U.K. and B.F.P.O. addresses only.

To **GSPK (Sales) Limited**

Dept. P.E., Head Office, Hookstone Park, Harrogate, Yorkshire HG2 7BU

ALL CALLERS WELCOME

Please fill in the coupon and send with 10p (refundable on ordering) for catalogue

Name

Address

..... P.E.

MON. TO FRI. 9-5.00

PCB's and KITS

For Designs Published in P.E.

All PCB's Fibreglass, Drilled, Roller-Tinned (Circuit and assembly notes free with each PCB)

AURORA—Multichannel Sound Controlled Light Designer Approved PCB's and Kits. Semiconductors (SCR's excl.), 8 Ch., £7.65; 4 Ch. £4.50 R's, C's, Pots (erratic Cores, 8 Ch., £10.00; 4 Ch., £5.50 Power supply (will supply 8 Channels), £2.85 PCB (4½in × 11in) holds Pre-amp and 4 chans., incl. pots, £2.35 PCB (4½in × 6½in) holds PSU, Sync Gen., 8 cores, 8 SCR's, £1.35

CALLERCORD—Automatic Answering Machine Designer Approved PCB and Kit. 5/C's, R's, C's, Pots, Switches, Relays, T/Former, £12 PCB (4in × 7½in) also holds edge-cons. and relays, £1.50 Parrot tape recorder, £6.95

DIGI-CAL—Details of PCB's on request

DOOR BELL YODELLER 5/C's, R's, C's, Pots, £4.45; PCB (3in × 3½in), 75p

ELECTRONIC PIANO—Details of PCB's on request.

GEMINI PRE-AMP Semiconductor set (stereo), £1.90 R's, C's, Rotary pots and Sw's to fit PCB (Stereo), £8.85 PCB (3½in × 10½in) Stereo. Also hold pots and Switches, £2.10

GEMINI MAIN AMPLIFIER (30W per channel) PCB (3½in × 5½in) Stereo, £1.40; R's, C's, Pots (stereo), £4.30

GEMINI POWER SUPPLY PCB (2in × 4in), 75p, R's, C's, Pot, £3.70

GEMINI STEREO TUNER PCB (4½in × 10in) as published, £1.80

LOGICAL RADIO CONTROL—All PCB's—details on request.

MICROPHONE MIXER—APRIL 1969 5/C's, R's, C's, pots, £2.90. PCB (3½in × 4½in) also holds pots, £1.20

MODEL SERVO CONTROL—All PCB's—details on request.

PHOTOPRINT PROCESS UNIT 5/C's, SCR, LDR, R's, C's, Pots, Relay, Sw, T/Former, £1.90 PCB (3½in × 5½in) also hold pots, relay, keyswitch, £1.20

TAPE NOISE LIMITER 5/C's, R's, C's, Pot, PCB (1½in × 3in), £2.20

VERSATILE LIGHT EFFECTS UNIT—Single Channel Sound Controlled Light 5/C's (excl. SCR) R's, C's, Pots, T/Formers, Keyswitch, £8.85 PCB (5½in × 5½in) also hold pots, Sw, T/Former (T/77), £1.50

Orders 10p P. & P. Other Designs Available. S.A.E. for list.

PHONOSONICS

DEPT. P.E.II, 25 KENTISH ROAD, BELVEDERE, KENT
 MAIL ORDER ONLY

Introduction to Field Effect Transistors

by J. Watson Ph.D.,
 University of Wales

128 pages about the theory and applications of field effect transistors: • Introduction to the field effect transistor • Characteristics, parameters and tolerances of the field effect transistor • Biasing and audiofrequency amplification • Voltage-controlled resistors, current limiters and d.c. amplifiers • High-frequency amplifiers and mixers • FET switches, choppers and analogue gates • Integrated circuits • Miscellaneous devices and applications.

SILICONIX LTD.
 Sketty, Swansea, SA2 8BA
 Tel: Swansea (0792) 21221



Please send copy copies of "an Introduction to Field Effect Transistors" for which I enclose cheque/P.O. No to the value of £

Name _____
 Company _____
 Address _____

£1 U.K.
 £1.25
 OUTSIDE
 U.K.



SEMI-CONDUCTORS/VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	2N3416	2N3417	2N3499	2N3500
2N3415	2N3416	2N3417	2N3500	

Integrated Circuits	FH1101	FH1111	FH1121	FH1991	FH2001
FH1101	FH1111	FH1121	FH2001	

VALVES	6X4	6X5	6X6	6X7	6X8	6X9	6X10	6X11	6X12	6X13	6X14	6X15	6X16	6X17	6X18	6X19	6X20	6X21	6X22	6X23	6X24	6X25	6X26	6X27	6X28	6X29	6X30	6X31	6X32	6X33	6X34	6X35	6X36	6X37	6X38	6X39	6X40	6X41	6X42	6X43	6X44	6X45	6X46	6X47	6X48	6X49	6X50	6X51	6X52	6X53	6X54	6X55	6X56	6X57	6X58	6X59	6X60	6X61	6X62	6X63	6X64	6X65	6X66	6X67	6X68	6X69	6X70	6X71	6X72	6X73	6X74	6X75	6X76	6X77	6X78	6X79	6X80	6X81	6X82	6X83	6X84	6X85	6X86	6X87	6X88	6X89	6X90	6X91	6X92	6X93	6X94	6X95	6X96	6X97	6X98	6X99	6X100
6X4	6X5	6X6	6X7	6X8	6X9	6X10	6X11	6X12	6X13	6X14	6X15	6X16	6X17	6X18	6X19	6X20	6X21	6X22	6X23	6X24	6X25	6X26	6X27	6X28	6X29	6X30	6X31	6X32	6X33	6X34	6X35	6X36	6X37	6X38	6X39	6X40	6X41	6X42	6X43	6X44	6X45	6X46	6X47	6X48	6X49	6X50	6X51	6X52	6X53	6X54	6X55	6X56	6X57	6X58	6X59	6X60	6X61	6X62	6X63	6X64	6X65	6X66	6X67	6X68	6X69	6X70	6X71	6X72	6X73	6X74	6X75	6X76	6X77	6X78	6X79	6X80	6X81	6X82	6X83	6X84	6X85	6X86	6X87	6X88	6X89	6X90	6X91	6X92	6X93	6X94	6X95	6X96	6X97	6X98	6X99	6X100	

HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE
SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



RECORD DECKS


B.S.R. UA50 Mono:	£4-97
C129:	£6-50
MP60	£10-40
G10	£14-07
G10	£11-50
G10	£9-40
G10	£23-45
MP60/G800*	£12-90
MP60/TPD1	£17-12
MP60/TPD1	£19-50
G800*	£15-40
MP60 TPD2	£10-40
G10	£20-35
G10 TPD1	£18-20
210 Package*	£9-55
HT70	£14-99
HT70/G800*	£17-25
HT70 Package*	£21-60
HT70/G800*	£23-95



GOLDRING


GL689/2	£18-97
GL692/2/P	£24-20
GL72	£23-50
GL72/P	£30-55
GL75	£31-35
GL75/P	£38-65
LID75	£3-95
LID72	£3-55
G99	£22-20
GL85/P/C	£65-25
LID85	£5-25
G101	£22-20

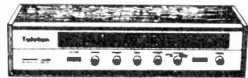TELETON F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/ Amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/ Cer. phono inputs. AFC/Built-in MPX. **OUR PRICE £28.25** Carr. 50p.

★ TRANSISTORED FM TUNER ★

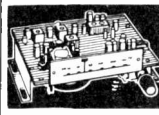

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2 in. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 MHz. Ready built ready for use. Fantastic value for money. £8.97. P. & P. 12p.

Stereo multiplex adaptors £4.97.

GARRARD 2025TC*	£8-50	THORENS TD125 II	£69-95
40B*	£9-25	TD125AB II	£105-00
SP25 III	£10-25	1X25	£7-40
SL65B	£13-45	TD160C	£58-95
AP76	£18-85	TD150	£29-50
SL72B	£22-95	TD150A II	£38-95
SL95B	£22-50	TD150AB II	£38-95
401	£28-50	TD150 Plinth	£3-90
ZERO 100A	£38-95	TX11	£3-80
ZERO 100S	£37-50		

*Mono cart. *Stereo cart. All others less cartridge. Carriage 50p extra any model.
RECORD DECK PACKAGES
 Decks supplied with cartridge ready wired in leak veneered plinth with cover.



Garrard 2025TC/STAHCD	£12-95
Garrard SP25 III/PTAHCD	£18-95
Garrard SP25 III/MS75-6	£18-50
Garrard SP25 III/M44-7	£19-75
Garrard SP25 III/M44-E	£20-40
Garrard SP25 III/M65E	£22-95
Garrard SP25 III/G800 (Play on Flinth and Cover)	£18-75
Garrard AP76/M55E	£22-95
Garrard AP76/M75-6	£20-25
Garrard AP76/M55E	£32-25
Garrard AP76/M75EJ	£34-25
Garrard AP76/G800E	£30-75
Garrard AP76/M44E	£31-15
Garrard AP76/M75EJ	£32-95
BSR McDonald MP60/G800	£19-95
BSR McDonald MP60/M44-7	£20-95
BSR McDonald MP60/M44-E	£21-50
Goldring GL72/G800	£34-50
Goldring GL75/G800	£41-95
Goldring GL75/G800E	£44-95

Carriage 50p any item.

SINCLAIR EQUIPMENT




Project 60. Package offers. 2 x 230 amplifier, stereo 60 pre-amp. P25 power supply, £15.95. Carr. 37p. Or with P26 power supply, £18.00. Carr. 37p. 2 x 750 amplifier, stereo 60 pre-amp. P28 power supply, £20.25 Carr. 37p. Transformer for P28, £2.97 extra. Add to any of the above £4.45 for active filter unit and £13.80 for pair of Q16 speakers. Project 60 FM Tuner £15.75. Carr. 37p. New Project 60S £20.97. Carr. 37p. All Sinclair products in stock. £12.80. P. & P. 10p. 2,000 amplifier, £21.95. Carr. 37p. 3,000 Amplifier, £28.50. Carr. 37p. Neoteric amplifier, £43.95. Carr. 37p.

LATEST CATALOGUE

Our 7th edition gives full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 320 pages, fully illustrated and detailing thousands of items at bargain prices.

SEND NOW— ONLY 40p P. & P. 10p

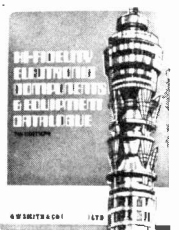

WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5" dia. Impedance 4/8 ohms. High flux ceramic magnet. 20 watts rms. Brand new. £1.50. Carr. 37p.



MCA. 220 AUTOMATIC VOLTAGE STABILISER

Output 88-125 V.A.C. Output 120 V.A.C. or 175-250V input Output 240 V.A.C. 200 VA rating. £11.97. Carr. 50p.




BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18-200,000Hz; Square 18-50,000Hz. Output max +10dB (10kΩ). Operation internal batteries. Attractive two-tone case 7 1/2 x 5 1/2 x 2 1/2 in. Price £17.50. Carr. 17p.




TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

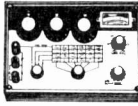A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ. 6 Ranges +1%. L. 1μH - 1 H. HENRYS 6 Ranges -2%. C. 10pF - 1110 mF d.c. 6 Ranges -2%. TURNS RATIO 1:1/1000-1:1/100. 6 Ranges -1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100mA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2 in. £20. P. & P. 25p.



230/240V SMITHS SYNCHRONOUS MOTORS

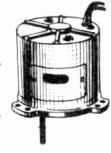Built in gearbox. All brand new and boxed. 60RPM (CW; 30RPM CW; 15/HR ACW; 2R/HR CW; NR/DAY CW; 10RPM CW; 20R/HR ACW; 50p each. Post 12p.



240° WIDE ANGLE

1mA METERS MW1-6 60mm square £3.97. MW1-8 80mm square £4.97. P. & P. extra.



HELICAL POTENTIOMETERS

1TT MCPM15 19 turn 2W. Available 500ohm, 1K, 5K ohm. £1.25 ea. P/P 15p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. 4in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1,000/1,500 or 5,000 ohms. 80p. P. & P. 7p. 50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms. £1.15. P. & P. 7p. 100 WATT. 15/10/25/50/100/250/500/1,000 or 2,500 ohms. £1.65. P. & P. 7p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery


S-260 General Purpose Bench Mounting		S-260B Panel Mounting	
1A	£7.00	1A	£7.00
2.5A	£8.05	2.5A	£8.05
5A	£11.75	Please add postage	
8A	£15.90	ALL MODELS	
10A	£22.50	INPUT 230 VOLTS. 50/60 CYCLES.	
12A	£23.80	OUTPUT VARIABLE 0-260 VOLTS	
20A	£49.00	Special discounts for quantity	

G.W. SMITH & CO. (RADIO) LTD

10 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-637 2232
 27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
 257/258 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-580 0670
 3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
 34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
 311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

CALLERS WELCOME MONDAY TO SATURDAY 9AM-6PM
 All Mail Orders to— 11-12, Paddington Green, London, W.2 Tel: 01-262 6562

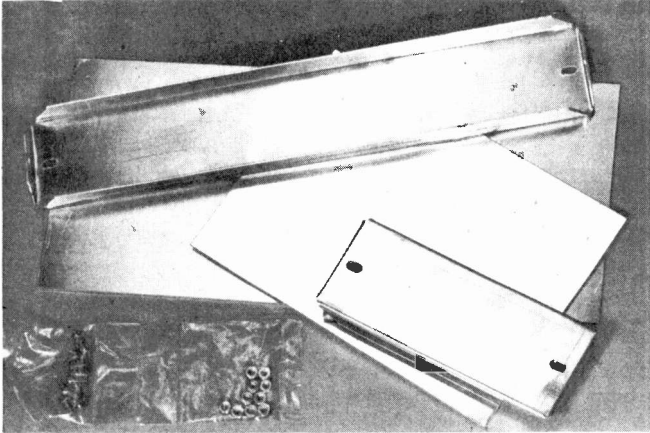From a recent copy of "Everyday Electronics"...



The advantages of this unique chassis are:

1. From stock, we can offer you a choice of 188 sizes, ranging from 3 x 3 x 1in. to 14 x 14 x 4in.
2. All parts are sold separately, so that a spoiled plate can be quickly and cheaply replaced. This is invaluable to the experimenter, who can use the same sides over and over again.
3. By fitting a plate to the bottom, a whole range of small metal cabinets, complete with handles if required, can be assembled.


This unique UNIVERSAL CHASSIS is obtainable ONLY from Home Radio (Components) Ltd.

A full list of plate sizes, together with reference numbers for ordering, is given in our Components Catalogue. *This famous "Constructor's Bible" lists over 8,000 components, over 1,500 of them illustrated.* It provides the quick, simple means of ordering all your component needs. Every catalogue contains 10 vouchers, each worth 5p when used as instructed. The Catalogue costs 70p, including postage and packing. Drop us a line or use this coupon.

Ring 01-648 8422

Ask for details of our Credit Account Service

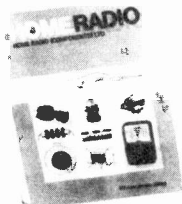The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.




Problems

Now to try and deal with some of the problems. We have had a number of reader's asking where the universal chassis parts that we have specified for some projects are available, the answer is Home Radio Components Ltd., who advertise their catalogue in our pages regularly.

Editorial extract reproduced by kind permission of the Editor of "Everyday Electronics"

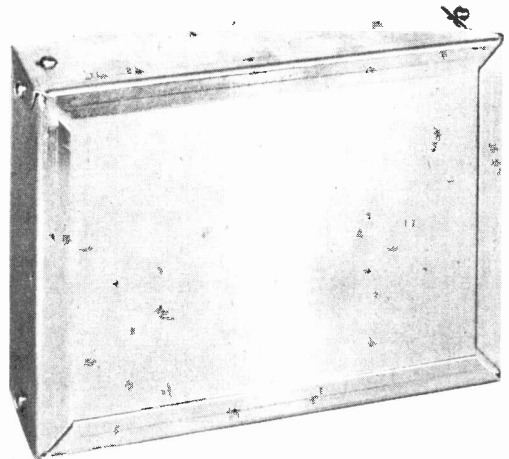Our famous Universal Chassis, which for many years has formed the basis of thousands of radio and electronic projects, consists of a top and four separate sides. The five parts, which are made of 18 S.W.G. aluminium, can be quickly assembled with the screws provided to form a chassis even more rigid than the standard type.



POST THIS COUPON with your cheque or postal order for 70 pence



It would help us considerably if we knew whether this was your first Home Radio Components Catalogue. If it is please place a tick in the box.

This is my first H.R. Components Catalogue

Name.....

Address.....



HOME RADIO (Components) LTD.
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial D. BARRINGTON G. GODBOLD S. R. LEWIS B.Sc. (Eng.)
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY R. J. GOODMAN
Advertisement Manager D. W. B. TILLEARD

OUR BUSINESS

THIS magazine has its own established editorial conventions relating to constructional projects. These have remained unaltered since we started business and we have no plans to depart from these well proven conventions in the future. Perhaps these conventions should be clarified for the benefit of our readers.

Firstly, let us deal with the "exceptional". From time to time a constructional project appears with the prefix "PRACTICAL ELECTRONICS" incorporated in its title. This distinction is not awarded haphazardly. Our name is attached to selected projects only when the following conditions are fulfilled: the project is unique, in that it offers the home constructor something not previously available in a detailed comprehensive form, and it represents a significant or important new application of electronic circuitry. The original concept for the project may have come from the staff of this magazine; or may be the result of consultation with an outside designer. In either case, the actual development and production of the first model is put in the hands of a specialist contributor.

Apart from such commissioned designs, there are examples where a completed project has been offered to us in the normal way (without prior collaboration in the initial planning stage) and upon examination the project proves to "qualify" in the terms stated above. In such an event it may be decided to "adopt" this design to bring it into a special, close relationship with this magazine. This is subject to the agreement of the contributor naturally—but none so far has raised any objections to an adoption proposal!

We are certain that every one of the selected designs published under the P.E. insignia has been a credit to the designer concerned; furthermore we believe these designs stand out as notable landmarks in the eventful story of home constructed electronics, an activity which has progressed and expanded so dramatically over the recent years.

This special singling out of certain projects in no way diminishes the merit of the other projects published in these pages. All designs are rigorously vetted before acceptance and many of these do indeed indicate a very high degree of technical inventiveness and skilful workmanship on the part of the individuals responsible for their conception and subsequent execution.

Constructional projects are obviously the life blood of this magazine. Only projects designed and built expressly for the home constructor (the designer may himself be either a professional or an amateur in the electronics sense) are considered for inclusion under this

continued on page 922

THIS MONTH

CONSTRUCTIONAL PROJECTS

A.F. SIGNAL GENERATOR	918
P.E. ELECTRONIC PIANO—3	924
SIMPLE C-R BRIDGE	934
P.E. DIGI-CAL—5	940

SPECIAL SERIES

DESIGNING WITH I.C.s—2	961
------------------------	-----

GENERAL FEATURES

INGENUITY UNLIMITED	953
---------------------	-----

NEWS AND COMMENT

EDITORIAL	917
POINTS ARISING	922
SPACEWATCH	923
P.E. AT THE AUDIO FAIR	933
INDUSTRY NOTEBOOK	938
NEWS BRIEFS	948
PATENTS REVIEW	949
ON THE FRINGE	950
READOUT	954

SPECIAL SUPPLEMENT


ELECTRONIC MUSICAL
INSTRUMENTS

*Our December issue will be published on
Friday, November 10*

© IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.65.

Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202

Simple A.F. SIGNAL GENERATOR

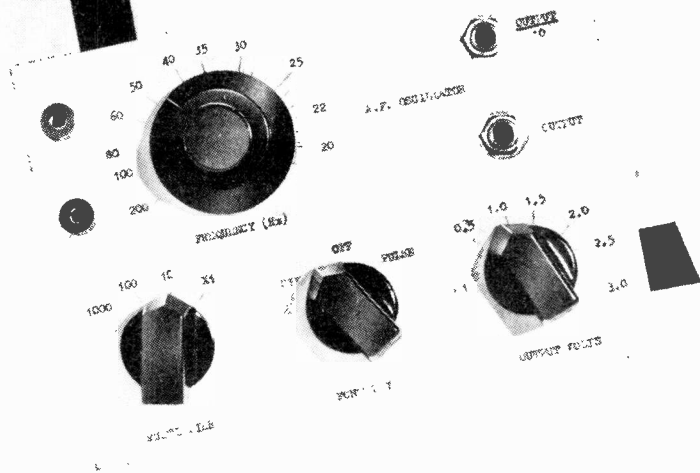

By D. W. Easterling

THE audio frequency signal generator to be described here produces sine waves or pulses over the frequency range 19Hz to 200kHz in four bands. The amplitude of the sine waves is sensibly constant over the entire range, and the waveform good. The pulses are square in shape, with 1:1 mark/space ratio over the lower three bands, that is from 19Hz to 20kHz. Above this frequency the waveform and level progressively deteriorates.

The maximum output level, both for sine and square waves is 3V peak-to-peak, just over one volt r.m.s. A constantly variable output control enables this to be reduced to zero, and is calibrated down to 100mV.

There is also a second output socket permanently attenuated by 20dB, thus permitting accurate setting of the output level to 10mV.

The complete unit operates from a self-contained 9V dry battery, and is housed in a case measuring 7in x 5in x 2½in. Costing less than £4 to build from new components, this test set will be of value to the radio experimenter and hi fi enthusiast.

WIEN BRIDGE

The circuit is illustrated in Fig. 1. Transistors TR1 and TR2 are connected as an inverted Wien bridge oscillator. To sustain oscillation positive feedback is arranged between the two emitters via network LP1 and R5.

At the same time, considerable negative feedback from TR2 emitter to TR1 base prevents the circuit from oscillating at any frequency except that selected by the Wien bridge network. This consists of VR1a, R1, VR2, R2, and VR1b; a pair of capacitors selected by the range switch S1a ganged to S1b completes the network. The variable resistors VR1a and VR1b are in fact one double-gang control which is used to provide continuous tuning over each range.

The series resistors R1 and R2 are chosen to provide a 10:1 frequency swing without permitting the minimum resistance of the network to reach such a low value that it seriously loads the emitter circuit of TR2.

The potentiometer VR2 enables both arms of the network to be balanced, particularly at the high

frequency (low resistance) end of each range, otherwise there is a tendency for the output level to dip beyond the auto-control circuit. VR2 can be omitted and the values of R1 and R2 set by trial. For example, in the prototype the values of R1 and R2 were 4.7 and 5.1 kilohms respectively.

The capacitors C1 to C8 determine the frequency ranges as follows:

Capacitors	Nominal Value	Frequency Range
C1, C2	120pF	19kHz to 200kHz
C3, C4	1,500pF	1.9kHz to 20kHz
C5, C6	0.015 μ F	190Hz to 2kHz
C7, C8	0.15 μ F	19Hz to 200Hz

It will be noticed that C1 and C2 are made less than the expected 150pF, due to the effect of stray capacitances. To ensure accurate range multiplication each of these capacitors may consist of a 100pF silver mica fixed capacitor in parallel with a 30pF air spaced trimmer which is adjusted during calibration. In the prototype it was found that single fixed 120pF capacitors of close tolerance provided sufficient accuracy.

POSITIVE FEEDBACK

The amount of positive feedback in the oscillator is critical. It must be sufficient to sustain oscillation without being so large that it drives the transistors off the linear part of their characteristic and produces unwanted harmonic distortion.

Unfortunately the changing characteristics of the load, power supply, and frequency selective network, tend to cause large variations in signal level which can only be overcome by using some form of automatic level control. Changes in level due to range

switching can be countered by switching in different series resistors (VR3 to VR6), but this is insufficient when, as in this case, the frequency swing on each range is in the order of 10:1, consequently a more sophisticated arrangement is employed.

The usual method of solving this problem is to use sensitive thermistors which are both fragile, and costly. The circuit in Fig. 1 achieves the same result by using a 6 volt 40 mA lamp. The lamp in series with a 150 Ω resistor is connected across the oscillator output.

As the output voltage increases, so does the current through the lamp, heating the filament and causing the lamp resistance to rise. This has the effect of reducing the voltage appearing at the junction of the lamp with the resistor, and thus the positive feedback. With careful design, the circuit becomes self balancing, and the output level stable.

It will be noticed that the lamp normally runs just below the level where it produces light, although under certain conditions a glow can just be seen. The nominal current through the lamp is in the order of 20mA.

The output of the oscillator is taken direct from the emitter of TR2 as a sine wave, or via TR3 and TR4 as a pulse or square wave. TR3 is a grounded emitter amplifier with a high value collector load resistor. Squaring occurs because the input signal is sufficient to bottom the base and collector characteristics on alternate half cycles.

Resistor R8 isolates the input circuit of TR3 from the output of TR2, thus preserving the sine wave output, and with R9, regulates the input to TR3 to ensure a square wave mark space ratio of 1:1. Adjustment of these resistors provides a convenient

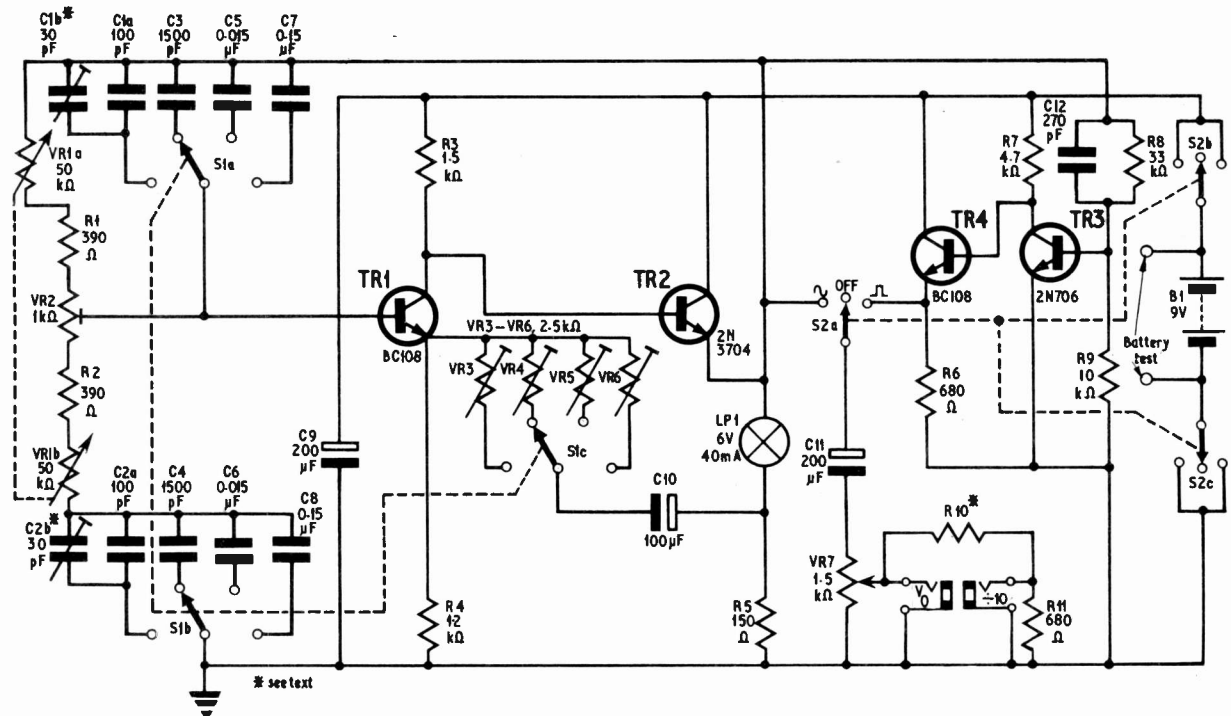


Fig. 1. The circuit diagram of the complete a.f. signal generator

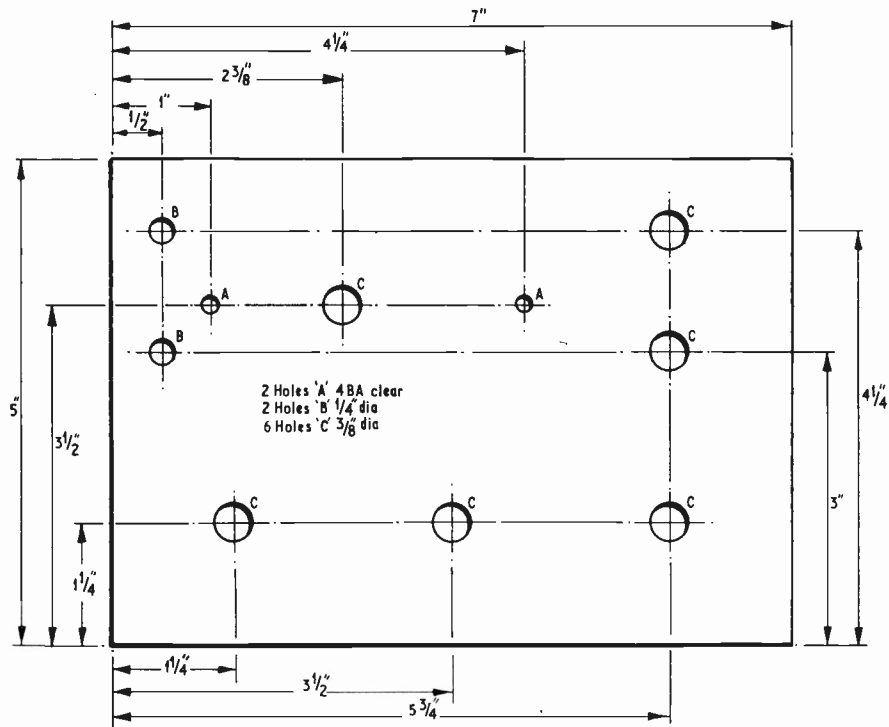


Fig. 2. The front panel drilling details to take the controls and sockets. The component board is bolted to this panel before the panel is covered with adhesive plastics sheet

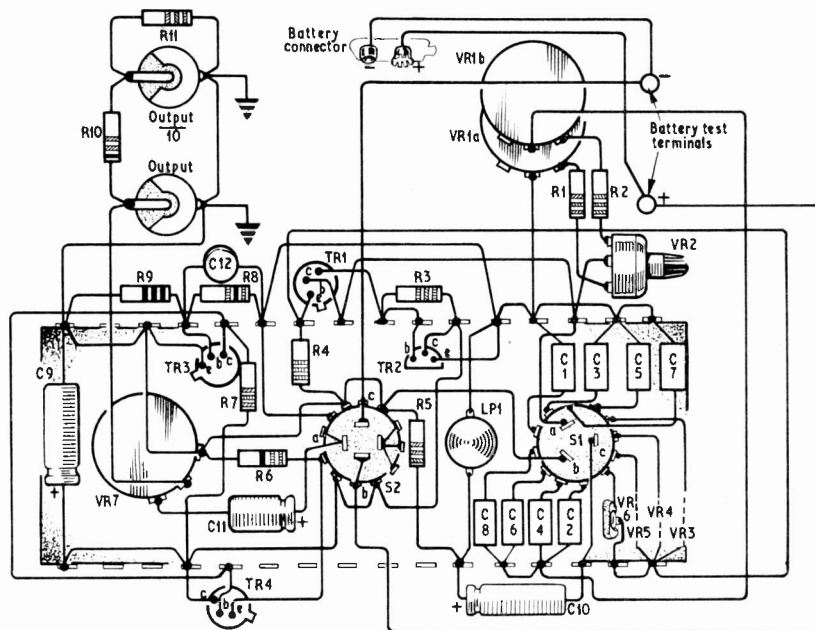


Fig. 3. The components are assembled on a tag board attached to the front panel

COMPONENTS . . .

Resistors

R1	390 Ω	R6	680 Ω
R2	390 Ω	R7	4.7k Ω
R3	1.5k Ω	R8	33k Ω
R4	1.2k Ω	R9	10k Ω
R5	150 Ω	R10	(see text)
		R11	680 Ω

All $\pm 5\%$ $\frac{1}{4}$ W carbon

Potentiometers

VR1	50k Ω linear, twin-gang
VR2	1k Ω linear preset
VR3, VR4, VR5, VR6	2.5k Ω linear preset (4 off)
VR7	1.5k Ω linear

Capacitors

C1, C2	100pF silver mica in parallel with a 30pF air spaced trimmer or single 120pF silver mica (see text)
C3, C4	1,500pF 400V
C5, C6	15,000pF 400V
C7, C8	0.15 μ F 250V
C9	200 μ F elect. 16V
C10	100 μ F 400V
C11	200 μ F 400V
C12	270pF ceramic disc

Transistors

TR1	BC108
TR2	2N3704
TR3	2N706
TR4	BC108

Switches

S1	3-pole, 4-way switch
S2	3-pole, 3-way switch

Battery

B1	9V dry battery
----	----------------

Lamp

LP1	6V 40mA lamp
-----	--------------

Miscellaneous

Aluminium case	7in \times 5in \times 2 $\frac{1}{2}$ in
Jack sockets	(2 off)
Wander sockets	(2 off)
Battery connector	
Pointer knobs	
Lamp holder, m.e.s.	
Component assembly board	

method of tailoring the mark space ratio to individual requirements.

Capacitor C12 provides a degree of high frequency compensation. Transistor TR4 matches the high load resistance of TR3 to the comparatively low impedance output circuit.

OUTPUT TERMINALS

Selection of sine wave or pulse is by switch S2a, which is ganged to S2b and S2c in series with the battery to put the unit to "off" in the centre switch position.

The standing d.c. potentials at the emitters of TR2 and TR4 are blocked from the output by capacitor C11, which must be of sufficiently large capacitance to pass the lowest frequency without significant attenuation.

The output control VR7 can be reliably calibrated down to 100mV, but for many applications, such

as testing pre-amplifiers, this is too high; hence the alternative output attenuated by network R10 and R11 which enables an output level of 10mV to be selected. Separate output sockets are preferred to a switched attenuator, as they facilitate simultaneous connection to two circuits, e.g. a test load and a monitor.

Terminals connected across the battery and brought out to the front panel facilitate battery checking, and may perhaps be useful in providing a power source for some other item of equipment but should not be allowed to interfere with the oscillator stability. The normal voltage across these terminals will be from 7.8 to 9 volts depending on the state of the battery. The battery should be replaced when the voltage falls below 7.8V on load.

CONSTRUCTION

The aluminium case was purchased ready made and consists of two "chassis" type box trays with butting corners. The shallow tray acts as a lid and becomes the front panel. All of the components are mounted on it including the battery, as shown in the photograph.

The frequency control VR1 dominates the front panel with sufficient space around it to accommodate a large pointer knob and associated calibration. It is positioned off-centre in order to provide accommodation for the battery which is mounted alongside VR1, and retained by spring curtain wire stretched between two 4B.A. bolts.

Switches S1 and S2, and the output control VR7, are mounted in line across the lower part of the panel. Their fixing also retains the tagboard on which all the other components including the transistors and preset controls are mounted. This arrangement facilitates wiring, which is kept as short as possible to minimise stray capacitance effects.

The holder for lamp LP1 is also wired on to the tagboard between S1 and S2. The output jacks and battery test terminals are fitted at opposite ends of the front panel in line with VR1.

In order to provide a suitable background for the calibration marking and switch legends the front panel is covered in self adhesive plastics sheet. The same material is used on the underside to insulate the tagboard. The panel is covered after it has been drilled and before the components were finally mounted.

A single sheet covered the whole panel including the holes, and unwanted parts were removed with a half round file. The covering will take instant lettering transfers, typewriter ink, or ball pen markings, which are then made permanent by a coating of clear varnish. Fingernail varnish is ideal. Without this protection the marks are easily removed using a clean cloth.

All the required words and figures can be typed on to a single sheet of plastics which is then varnished. It is a simple matter to cut out the appropriate word or figure as a label and attach it in the required position on the panel during the test and calibration process.

TESTING

After carefully checking the wiring, and correctly connecting the battery, switch the unit on to sine waves. For this first test a current meter was inserted in series with the battery to monitor the

current, which should not exceed 25mA. With the output connected to an oscilloscope, the appropriate positive feedback preset potentiometers VR3 to VR6 were adjusted for each range so that the level at the output remained sensibly constant over the entire sweep of the frequency control without there being any apparent distortion. The aim is to produce a clean sine wave with minimum harmonic content.

Due to the thermal lag of the lamp LPI, the level tends to "bounce" if the frequency control is adjusted too rapidly. A tendency for the change in level between the low and high frequency ends of the frequency control to be outside the control circuit was corrected by adjustment of VR2.

Having established that the sine wave generator was operating satisfactorily, the unit is switched to square waves, which should be good up to 20kHz, but thereafter deteriorate as the frequency is increased.

As an alternative to an oscilloscope, headphones or an amplifier and loudspeaker could be used for audible testing of the unit over the three lower ranges. The higher frequencies are of course outside audibility. The positive feedback preset potentiometers should be adjusted to the point where oscillation is sustained over the entire range. Remember that too much feedback will produce a distorted waveform. On sine waves the tone is clear and pure. On square waves the harmonics become noticeable, the tone harsh, and apparently louder.

CALIBRATION

Frequency calibration is most easily done using a counter. The writer used an oscilloscope to compare the low frequency end of the output against the 50Hz mains supply (via a suitable low voltage isolating transformer), and the high frequency end against a separate 100kHz oscillator beating against the carrier frequency of the transmission (BBC Radio-2 Long Wave 200kHz 1.500 metres) for the high frequencies.

An alternative method would be to compare the note heard through headphones with that from a well tuned piano. Piano keyboard frequencies based on orchestral pitch (A = 440Hz) are given in various reference books and cover the range 27.5Hz (bottom A) to 4,186Hz (top C).

The output control was calibrated in volts peak to peak because this value is meaningful for square waves as well as sine waves. Again an oscilloscope was used. An uncalibrated oscilloscope could be used for this purpose with reasonable accuracy by setting it up against the a.c. voltage range of a multimeter fed by the unit switched to sine waves at about 50 to 100Hz. One volt r.m.s. on the meter is $1 \times 2\sqrt{2} \approx 2.8$ volts peak to peak.

Suppose that the oscilloscope is adjusted so that 2.8V peak to peak produces a deflection of 5.6cm, then the oscilloscope sensitivity is $5.6/2.8 = 2\text{cm/volt}$, and so 500mV peak to peak would produce a 1cm deflection. Lower values can be measured by expanding the trace. For example, with 500mV peak to peak producing a deflection of 5cm, 100mV peak to peak would produce a 1cm deflection.

The values of the fixed attenuator network R10 and R11 are nominal preferred values and were selected on test to reduce the output to one-tenth using the methods of measurement just described. ★

OUR BUSINESS *continued from page 917*

heading. We do *not* include commercial kits in this category. Not that we have anything against kits. Some of our best advertisers are in this business, and for the man in a hurry, there's a lot to be said in their favour. But we feel it would be a mis-use of our editorial pages to describe in detail how to assemble some such kit. Provision of this kind of information is the business of the kit suppliers.

We know *our* business: encouraging genuine enthusiasts to build and learn; and encouraging individual circuit designers and application innovators to produce novel and practical projects to sustain this absorbing hobby. The steady expansion of our wide ranging readership at home and overseas convinces us that this policy is the right one. The almost insatiable demand for original designs is a challenge, but one our contributors and ourselves eagerly and willingly accept.

As stated in the opening paragraph, no changes are contemplated. (Why interfere with a successful formula?) PRACTICAL ELECTRONICS will continue as an unrivalled source of original design and construction information—conceived and planned throughout with the private constructor first and foremost in mind.

F.E.B.

POINTS ARISING

NOUGHTS AND CROSSES GAME (*Oct. 1972*)

In Fig. 6 p. 834 (caption omitted), all contacts on wafer S1e should be blank except for a "1" against position 5 instead of position 6 as shown.

The 10-pole 10-way switch can be made from "Maka-switch" components but if a ready made switch is purchased, all wafers being make-before-break, then one wafer can be converted to break-before-make as required by carefully trimming the wiper contact until it does not short two contacts as the position is changed.

COMBINATION LOCK (*Ingenuity Unlimited Oct. 1972*)

The transistors can be almost any low power pnp switching types or general purpose types, so long as they are all the same.

TTL EQUIVALENCE GATE (*Ingenuity Unlimited Oct. 1972*)

In the diagram the last gate before the output has two inputs. These inputs are connected to the outputs of the preceding pair of gates respectively; they should not be joined together.

In the truth table, both "difference" conditions should have a "1" output.

TRANSECTOR (*July 1972*)

The value of R6 is 2.2 k Ω .

WHO'S WHO

I.C. INTERCOM in the October 1972 issue has been accredited to the wrong author. The author of this article is **J. LEWIS**, to whom we offer our sincerest apologies. We regret any inconvenience which may have occurred to Mr Lewis and to Mr R. A. Penfold, who is the real author of the *CR Bridge* in this issue.



BY FRANK W. HYDE

ORBITING OBSERVATORY

The largest telescope that has ever been put into space is carried aboard the newest orbiting observatory *OAO-C*. It is to be named *Copernicus* in a tribute to Nicklaus Copernicus as the father of modern astronomy. This forms a fitting part of the celebration of the 500th anniversary of his birth.

The observatory weighs some 4,900lb and orbits at 460 miles altitude. The spacecraft is about ten feet long and the 32-inch reflecting telescope occupies the centre of the vehicle.

In an effort to save weight the mirror is made of fused quartz and has been reduced in thickness to save 250lb. The actual weight is 105lb as against a normal reflecting mirror which would amount to about 350/360lb.

To achieve the necessary rigidity and constant figure the thin main disc is supported by quartz ribs and since gravity is reduced there is a further safeguard by carrying the telescope in space. This type of construction has been put into operation before by amateurs in an effort to reduce costs using the normal glass.

The 32-inch primary mirror collects the light rays and directs them to a smaller mirror 3.9 inches in diameter and thence to a spectrometer. The received data is then telemetered to earth.

This telescope is designed for the observation of ultra-violet light which is absorbed in the atmosphere. By working at a level where the atmospheric effects are minimal very valuable observations can be made. This type of work has been continuing for some time but with much smaller telescopes.

In addition to the large telescope there are three smaller telescopes on board the main purpose of which

is the X-ray observations that are to be made. These telescopes are part of the equipment provided by University College, London.

Work on the detection of X-ray sources has been going on for some time and to date some 200 sources have been identified.

In the early days X-ray studies were made with the sounding rockets and later with the famous *Explorer 42* perhaps better known as *UHURU* which was launched in December 1970. The observations confirmed that there were X-radiations from distant sources very much greater in amount than those from the sun. It is believed that these may come from the far distant parts of the universe.

The record of these orbiting observatories has been an extremely good one. Apart from the unfortunate accidents during the early stages of the series, with the first one failing three days after launch in April 1966, and the third one failing to attain orbit because of the malfunction of the shroud jettison mechanism, the programme for the four observatories in this project has had its rewards. Some 10,000 observations of celestial objects have been made including major observations of comets and in May 1972 the event of a supernova.

On board the *OAO-C* observatory will be a computer capable of storing about 1,024 commands from the ground. This gives comprehensive and fully automatic operation while within range of the ground station at Rosman, North Carolina.

Any information obtained by the *Copernicus* observatory will be freely available to researchers all over the world.

LAST OF THE APOLLO'S

The *Apollo 17* spacecraft left its berth at vehicle assembly Cape Kennedy, Florida on August 28, 1972. This spacecraft, the last of the *Apollo* series will carry the sixth team to a landing on the moon.

This last mission for this period will commence on Wednesday, December 6 at 21.53 EST (02.53 GMT Thursday) for the 12-day round trip to the moon. Three days will be spent on the surface of the moon.

Making his first space flight will be 37-year-old Harrison H. Schmitt, Ph.D., who is the first geologist to take part in an *Apollo* mission. His companion on the lunar surface will be 40-year-old Eugene A. Cernan, a veteran of some 264 hours of space flight and one of which took him to within 8 miles of the moon. Cernan will also undertake specially selected tasks during the mission.

The two astronauts will set up the fifth automatic station on the moon. The instruments to be set

up are varied and one of these is the tidal gravimeter or lunar surface gravimeter. This instrument has been under development since 1964 and will be used to test the theory of gravity waves. This is at the moment a most important point in understanding the nature of the forces which celestial objects exert on each other.

Another type of gravimeter named the traverse gravimeter will be carried on the lunar rover. With this instrument the astronauts will record the changes in the gravity that take place over the lunar terrain. Thus, the anomalies will enable comparisons to be made with earth gravity changes.

Explosive measurements with seismic instruments will show the profile which will help determine the physical structure of the moon. Also operating will be instruments to check the cosmic dust and meteoritic fall-out, to see what are the effects of erosion on the moon.

The spacecraft will be launched on a *Saturn V* rocket and will be the first to be launched after dusk.


THE EXPLODED PLANET

Many people have explained the asteroid belt, the multitude of small bodies from less than egg size to chunks large enough for a space probe to land on, by the theory that there was a planet which was disrupted by the tremendous forces that exist in the solar system. This belt which lies between the orbits of Mars and Jupiter is being traversed by the Jupiter probe which may take photographs of some of them. In terms of proximity, of course, there is not likely to be many of these fragments near each other.

The problem of this debris is highlighted by the recent work of Michael Ovenden. Formerly of London and Edinburgh, Professor Ovenden is now at the University of British Columbia. He has been seeking a solution to certain celestial problems and his latest theory seems to be a satisfactory way of explaining the asteroid belt.

The various bodies which all interact with each other tend to settle to a minimum attraction position. Ovenden has checked this on such systems as Barnard's star which has planets. He has been able to get to an accuracy of 99 per cent with his theory.

To get the sums right for the earth and the rest of the solar system a planet 90 times heavier than the earth would be needed. It seems that the asteroid belt formed into a planet would be needed. It seems that the asteroid belt formed into a planet would satisfy this criterion. So he has called this planet *Aztec*. Though its real existence cannot yet be proved it is a good point from which to proceed.

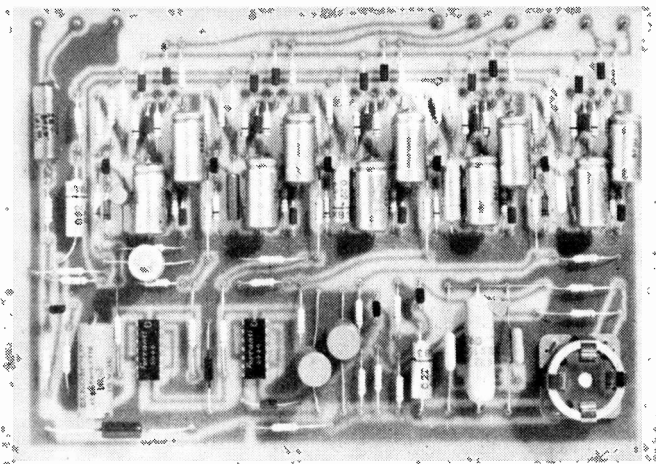

ELECTRONIC PIANO

Part 3

By A. J. Boothman B.Sc.

THIS part of the series is devoted solely to the main circuit boards of which there are 13 containing 90 per cent of the electronic components involved in the project. For convenient reference this board has been called the pitch board.

The function of the board, as described previously, is to generate a basic pitch and sub-harmonics of the same, followed by attack, decay, mixing, and tone circuits.

PITCH OSCILLATOR

The important requirements of the pitch oscillator is that it should have good long term frequency stability, good stability under varying ambient temperatures, and that it should present a suitable waveform which will reliably drive the frequency divider circuits. The circuit used is given in Fig. 3.1 which shows the various circuit elements that go to make up a complete pitch board.

The frequency of operation is determined by the tank circuit components C48 and L1. The inductance L1 is variable and is wound on a bobbin set in a ferrite core. After initial setting up C48 is fixed and comprises a number of capacitors in parallel dependent on the pitch concerned.

The oscillator transistor (TR16) is followed by a high gain buffer stage (TR17) which squares the waveform to give sufficiently fast edges at the collector to drive the first divider IC2. The cathode of diode D34 is returned to the divider supply rail in order to limit the positive excursion of the output waveform from TR17 ensuring that the maximum voltage presented to the divider input is approximately 5.3 volts.

PITCH DIVIDERS

In order to produce sufficient tones to cover the five octaves the fundamental frequency from the

buffer transistor is used for the top octave, whilst the other notes are produced at the outputs of four integrated circuit dividers which are packaged in pairs.

With the increase in availability of certain integrated circuits, the cost of these devices has dropped considerably, and to such an extent that in addition to circuit board area saving and ease of assembly, the incorporation of integrated circuits results in a significant cost reduction when compared with equivalent discrete circuitry.

The divider circuits (IC2, IC3) are dual-in-line 14 lead packages each containing two flip-flops. The type of element used is described as a D-type edge triggered JK flip-flop. From its description it follows that the input waveform must have clean fast edges for reliable operation. For second, third and fourth stages this is provided by the previous flip-flop, but for the first stage it is important that the output from TR17 should have fast edges. To ensure that this condition is met R119 is kept deliberately low.

FLIP-FLOP ACTION

The D-type flip-flop element (Fig. 3.1) operates in such a way that when a leading (positive going) edge appears at the clock input (CP) then the output at Q takes up the same state as that present at the D input immediately prior to the appearance of the clock pulse. Thus, if D was at a high voltage before the input signal rises then Q will take up the high voltage state and remain there after the input voltage falls again. If the input at D is then changed to a low voltage then Q will change to a low voltage as soon as the input waveform rises.

The state of the D input is controlled by externally connecting the \bar{Q} output to the D input. By definition \bar{Q} is the complement of Q and so it can be seen that when the clock input is low D is always

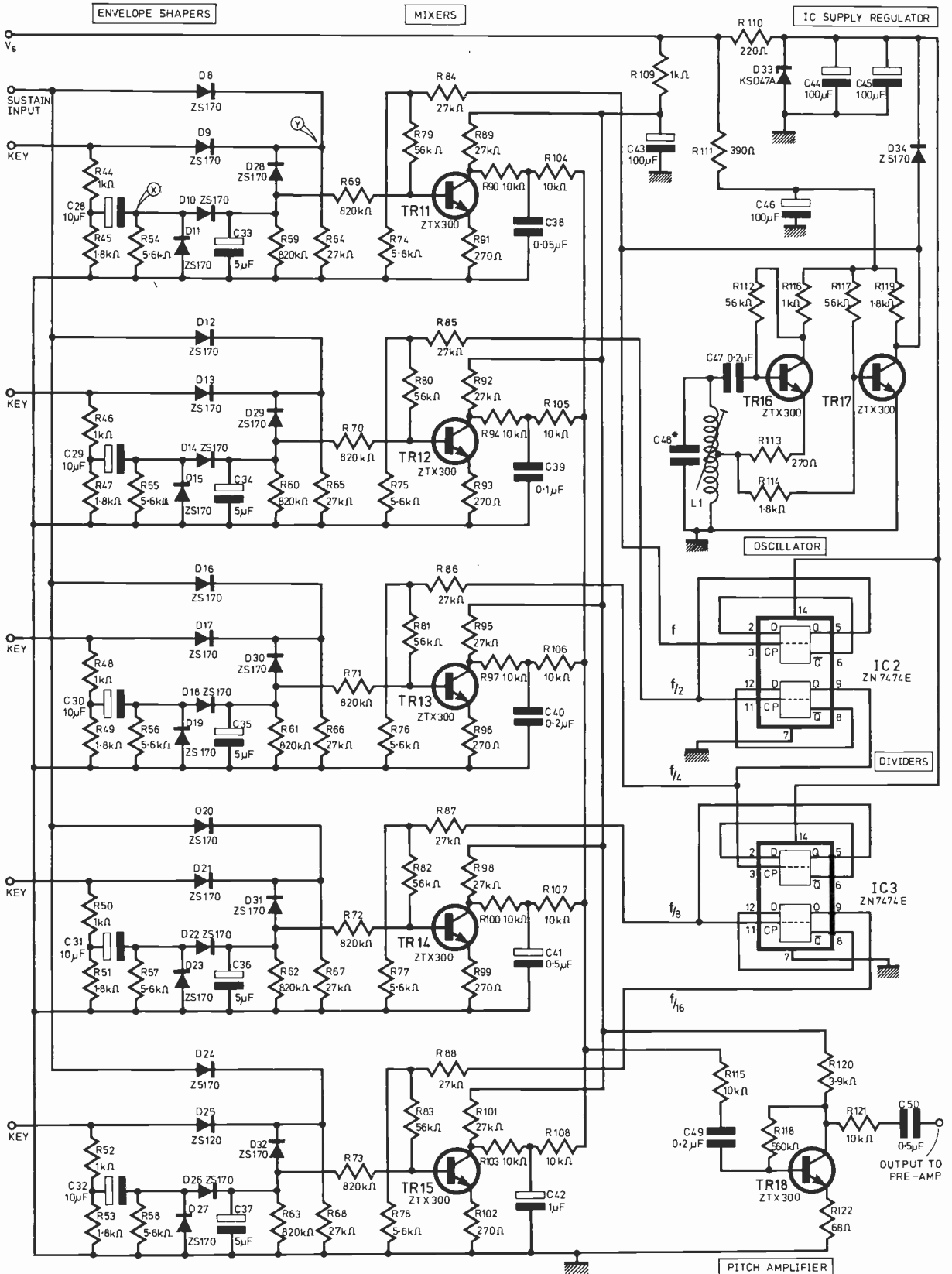


Fig. 3.1. Circuit diagram of a pitch p.c.b.

the opposite to Q, such that when the clock input rises Q will always change state, and remain in the new state until the clock has both fallen and risen again, at which point Q will again change state.

Since the clock input signal from the pitch generator is a square wave signal f, the Q output from the first flip-flop will be another square wave signal at half the frequency, $f/2$.

The other sub-harmonics are similarly generated by routing appropriate Q outputs to succeeding flip-flops.

ATTACK AND DECAY ENVELOPE

The most important area in determining the character of this instrument is that concerned with the envelope, or attack and decay characteristic.

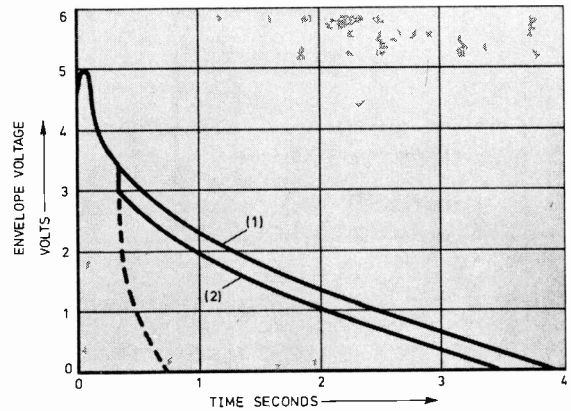
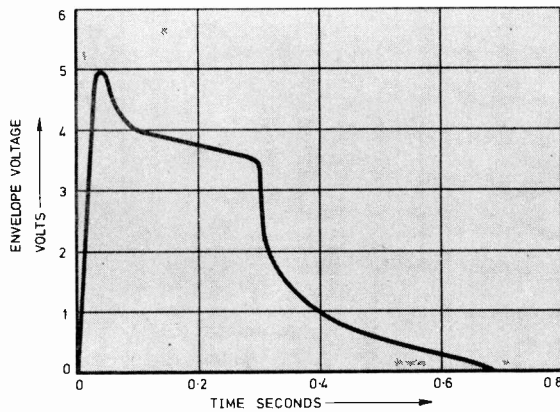


Fig. 3.2(a). Envelope circuit output characteristic in the non sustain mode with key released after 0.3 seconds. (b) Envelope circuit output characteristic with (1) key held depressed in the system or non sustain mode; (2) key released after 0.3 seconds in the sustain mode

The influencing factors involved are listed as follows:

- The rate of rise of the leading edge of the envelope (attack).
- The height of the leading edge.
- The amount of rapid fall following the attack.
- The length of decay when a key remains depressed.
- The length of decay after the key is released (non-sustained).
- The length of decay after the key is released with the sustain pedal on.

It is of course possible to display the output waveform of a string piano on an oscilloscope, and this could be followed by a point by point attempt at electronically simulating the envelope. In experimenting in this way, combined with straight-forward comparative ear tests, the author noted certain features of the electronic equivalent which made it desirable to depart from an identical copy of the string piano envelope.

SLOW DECAY ENVELOPE

The curve shown in Fig. 3.2a indicates the envelope required under non-sustaining conditions, i.e. when a key is depressed and released fairly quickly without use of the sustain pedal.

In order to obtain a percussive effect a fast rate of rise is required on the leading edge, followed by a rapid decay to a medium level of sound, and further followed by a relatively slow decay. On releasing the key the decay of sound should be fast but in the case of a piano this does take a finite time.

A string piano is activated by a hammer system where the level of attack is determined by the impact velocity of the hammer on the string, which is proportional to the rate of acceleration of the finger placed on the key. In the case of the electronic piano, in addition to a simulation of the hammer velocity action on each key, the maximum level of attack is determined by a five position touch switch which presets the key voltage supply.

The level of initial attack on a string piano, when compared with the mean level of sound output, is very high, and a similar ratio is difficult to reproduce electronically if economical amplifier and loudspeaker capacities are to be used. This is the first point of compromise which has to be considered. Having recognised the need for a clear pip at the commencement of the envelope it is then necessary to consider the rate of decay in the medium level of sound region mentioned above. This is clearly coupled with the full decay period and again due to peak/mean power considerations it is somewhat slower than on a string piano.


Finally, when the key is released on a string piano a damper comes into operation immediately and quickly kills the vibration of the string. This action is reproduced realistically by an analogous electronic circuit.

LONG DECAY ENVELOPE

The curve shown in Fig. 3.2b indicates the other two possible conditions.

- When the key is held depressed for a considerable time.
- When the key is released quickly, but the sustain pedal is depressed.

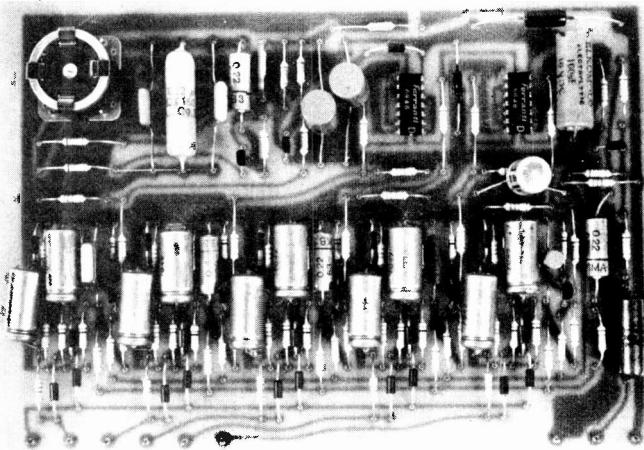In both cases the first part of the envelope is



A completely assembled pitch p.c.b.

required to be exactly the same as in Fig. 3.2a. If the key remains depressed then the output decays slowly to zero in a time that is easily varied by the suitable choice of one resistor value in each envelope circuit. In the prototype this provides a decay of approximately 3.5 seconds, which is somewhat larger than for a string piano.

In the key released, sustain pedal on condition, it is more important to have a large amount of rapid fall following the attack in order to retain the percussive characteristic of the instrument when repeatedly playing the same note at a fast rate. As mentioned earlier a string piano has a very high peak capability and a fast initial decay. This allows fast repetition of one note whilst, even under sustain conditions, maintaining the discrete identity of each input via its attack characteristic.

The attack characteristic of the first curve in Fig. 3.2a is insufficient to reveal differentiation between consecutive notes in the sustain condition, and a second characteristic is therefore introduced whereby a second fall in level occurs as the key is released, followed by a shorter decay time of approximately 3 seconds.

THE ENVELOPE CIRCUIT

Each of the d.c. key inputs in Fig. 3.1 are shaped by envelope circuits. As can be seen there are five duplicated circuits that precede the mixers to fulfil this function. To understand the action of these let us look at the topmost shaper of Fig. 3.1.

A note is initiated when a d.c. level of between 11 and 18 volts, depending on the touch setting, is applied to the input of the circuit via the keyboard. Capacitor C33 is charged via R44 and C28, with R44 providing some slight slowing of the rise time in order to protect against key noise, and also being a factor in determining the height of the attack pip.

Following the relatively quick charging of C33, C28 is charged which means that point "X" falls towards ground potential. The presence of D10 isolates the input circuitry from C33 and there is no further interaction between the two circuits. Removal of the key voltage results in the discharge of C28 via the diode D11 and resistor R45.

It is important that R54 should be sufficiently low to provide fairly rapid charging of C28, and

that R45 should be sufficiently low to allow complete discharge of C28 before the next key voltage is applied. However, both resistors are involved in determining the voltage applied to C33 during attack (voltage sharing with R44), and all values are therefore both important and interrelated.

TOUCH SENSITIVITY

In order to give touch sensitivity R45 can be replaced by a grounded switch contact in the key-switch action which becomes a double throw switch between a zero volt potential and the supply voltage on the second pole.

During the interval when the switch is changing over, C28 is charged by a bleed resistor between rail voltage and the centre contact of the change-over switch. This reduces the attack voltage excursion at the point when the changeover is complete, by an amount dependent on the time taken over the movement between the two poles. Further details on this will be given later.

SUSTAIN AND DAMPING

Now, ignoring the input circuit, we can consider the sustain and damper portion of the envelope. The keying operation had charged C33 to approximately 5 volts, and whilst the key remains depressed point "Y" is held at approximately 14 volts, thus isolated from the output line by diode D28.

In this condition C33 is slowly discharged by the combined effect of R59 and the load placed across the output. If at any point during this decay the key should be released then D28 and R64 would appear across the output, and since R64 is made very low compared to R59 this provides the damper action.

When the sustain pedal is in operation D8 is held at approximately 4.5 volts which causes a quick drop in the output voltage on release of the key, but then holds off the action of R64 during the remaining part of the sustain period.

TONE FORMING

Tone forming in the system is very simple and consists only of a low pass capacitive filter after each transistor. The complete circuit of the combined envelope and tone forming section is shown in Fig. 3.1.

As stated in the first article the prime purpose of the project is to provide a reliable portable keyboard instrument with a percussive characteristic similar to that of the piano. The tone of a piano is of course extremely variable from one instrument to another, and whilst it is possible to incorporate involved tone circuits to match one particular piano colouring, the author decided that the simple filter above produced a sound which is completely acceptable for both the home and band applications.

TONAL CHARACTERISTICS

It is difficult for the author to give an objective description of the sound produced by the instrument, but generally the piano type characteristics are most noticeable above middle C, and the attack becomes less apparent in the lower registers, where a fuller more organ like sound is evident.

When driving an external amplifier of course, using the appropriate output socket, the tonal

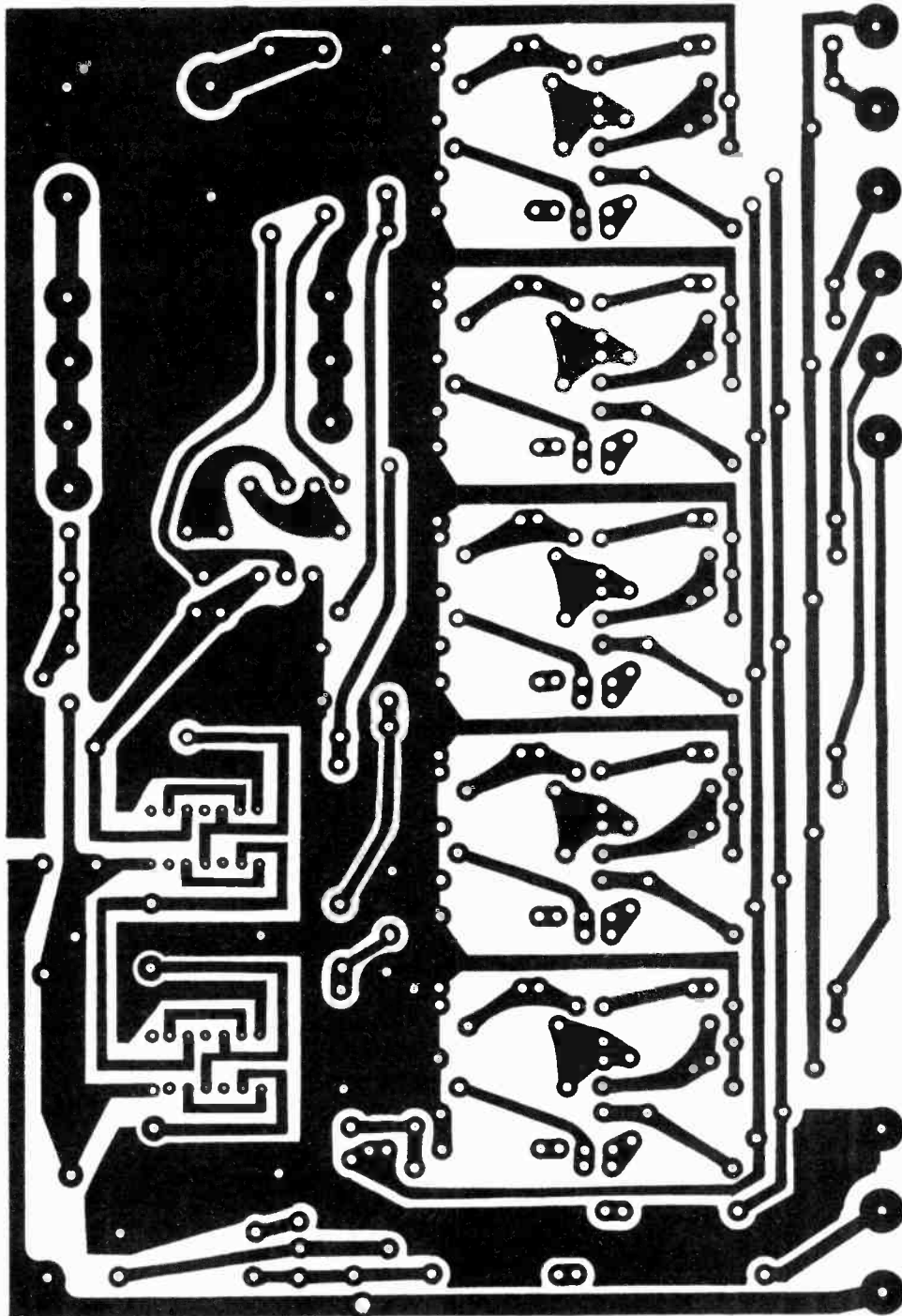


Fig. 3.3. Etching details for pitch p.c.b. This is full size

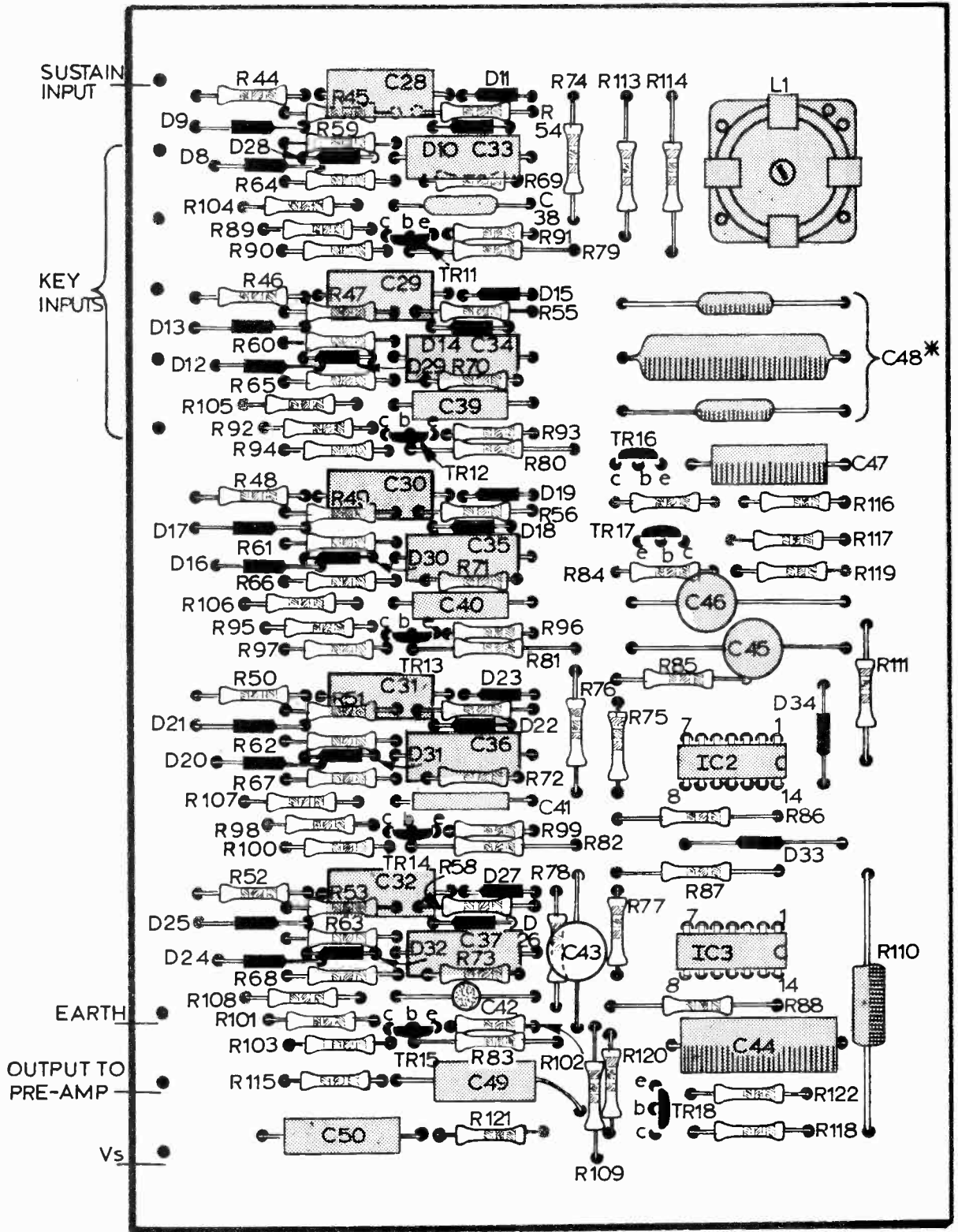


Fig. 3.4. Component layout for pitch p.c.b.

characteristics can be varied over a wide range by variation of the tone control settings on the external amplifiers.

The piano has been used in this manner on a number of occasions and exhibits the characteristics of piano, vibraphone and electric guitar depending on the chosen bass and treble positions, and the way in which it is played.

PITCH AMPLIFIER

Each printed circuit board contains five envelope circuits which are then fed into a pitch amplifier which in turn is followed by the pre-amplifier described last month.

The values of C49, R121 and C50 are important, as up to this point all coupling has been direct, and

it is necessary in the amplifier to filter out the large very low frequency excursions due to the keying action.

ETCHING DETAILS OF PITCH P.C.B.

The 8in × 5½in printed circuit board is etched according to the pattern of Fig. 3.3. Thirteen such boards are required. Fig. 3.4 shows the component layout for the boards.

COMPONENTS

All transistors specified are Ferranti type ZTX300. It is of course possible that other equivalent transistors could perform the same functions, but no work has been carried out to prove this. The diodes contained in the prototype were a mixed batch of

COMPONENTS . . .

PITCH BOARD

(12 are required with a full component complement as listed.
The thirteenth requires components as shown asterisked)

Resistors

R44*	1kΩ
R45*	1.8kΩ
R46	1kΩ
R47	1.8kΩ
R48	1kΩ
R49	1.8kΩ
R50	1kΩ
R51	1.8kΩ
R52	1kΩ
R53	1.8kΩ
R54*-R58	5.6kΩ (5 off)
R59*-R63	820kΩ (5 off)
R64*-R68	27kΩ (5 off)
R69*-R73	820kΩ (5 off)
R74*-R78	5.6kΩ (5 off)
R79*-R83	56kΩ (5 off)
R84*-R88	27kΩ (5 off)
R89*	27kΩ
R90*	10kΩ
R91*	270Ω
R92	27kΩ
R93	270Ω
R94	10kΩ
R95	27kΩ
R96	10kΩ
R97	270Ω
R98	27kΩ
R99	270Ω
R100	10kΩ
R101	27kΩ
R102	270Ω
R103	10kΩ
R104*-R108	10kΩ (5 off)
R109*	1kΩ
R110	220Ω 3W
R111*	390Ω
R112*	56kΩ
R113*	270Ω
R114*	1.8kΩ
R115*	10kΩ
R116*	1kΩ
R117*	56kΩ

R118*	560kΩ
R119*	1.8kΩ
R120*	3.9kΩ
R121*	10kΩ
R122*	68Ω

All resistors ±5% ¼W carbon except where otherwise stated

Capacitors

C28*-C32	10μF elect. 15V (5 off)
C33*-C37	5μF elect. 15V (5 off)
C38*	0.05μF
C39	0.1μF
C40	0.2μF
C41	0.5μF elect. 15V
C42	1μF elect. 15V
C43*	100μF elect. 15V
C44	100μF elect. 15V
C45	100μF elect. 15V
C46*	100μF elect. 15V
C47*	0.2μF
C48*	See text
C49*	0.2μF
C50*	0.5μF

Transistors

TR11-TR18 ZTX300 (8 off)
(4 required for p.c.b. 13)

Diodes

D8-D32 ZS170 (25 off) (see text)
(6 required for p.c.b. 13)
D33-KS047A 4.7V 400mW Zener (or equivalent)

Integrated Circuits

IC2-IC3 Z7474E (2 off)

Inductor

L1—260 ± 260 turns of 36 s.w.g. enamelled copper wire. S.E.I. pot core assembly for this can be obtained from Clef Products (Electronics Division), Yew Tree Lane, Poynton, Stockport, Cheshire

FREE

*Information on our sophisticated but low-cost kits . . .

*New 1214 Audio Range. Build your system in a few evenings.

*New loudspeaker range.

*Unbeatable quality and specifications.

*Incredibly good value for your money.

*New continuous credit and no-deposit terms. Even includes instruments.

*Over 30 new models.

*Over 130 models in range.

*Packed full of invaluable information about the world's finest electronics . . .

It's New. It's the biggest Audio/Instrument kit catalogue in the U.K. And it's absolutely FREE.

Our new jumbo size Heathkit catalogue is full of good things: low-cost Testers and Instruments, Metal Detectors, Electronic Calculator, Intercoms., Amplifiers, Tuner/Amplifiers, Tuners and Loudspeakers - there's even a Battery Charger.

You name it, Heathkit can supply. What's more, you can build everything yourself. Heathkit help you each step of the way. Simply follow the Heathkit step-by-step construction manual. It's like painting by numbers but with something unique at the end of it. Fantastically satisfying, and less expensive than buying readymade. Our products are advanced in specification and performance. And they're regularly reviewed by leading journals. You have to be good to merit that sort of treatment.


We guarantee that by using the Heathkit step-by-step construction method you can build a piece of electronic equipment without needing to know the first thing about electronics.

Mail the coupon today for your copy of the free Heathkit catalogue. The kits shown take just one or two evenings, and we promise that whichever kit you choose it'll be more rewarding than washing the car or watching television.



Want to know more?

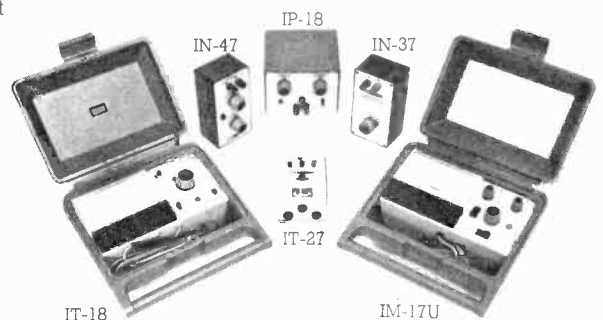Mail the coupon for a FREE CATALOGUE. Don't forget . . . This includes Instruments and low-cost Testers.



Why not visit your Heathkit Electronics Centres . . . and see our Instruments and Testers.

London 233 Tottenham Court Road. Telephone: 01 636 7349
Open hours: Monday - Saturday 9-6.00 p.m.

Birmingham 17-18 St. Martin's House, Bull Ring
Telephone 021 643 4386 Open hours: Friday - Saturday 10-5.30 p.m.

Gloucester Cole Avenue Roundabout, Bristol Road.
Telephone 045229451 Open hours: Monday - Friday 9-5.00 p.m.
Saturday 9-12.30 p.m.

Please send me the FREE New 1972 Heathkit catalogue

Name

Address

.....

HEATHKIT
Schlumberger

HEATH (Gloucester) Ltd.,
Dept. PE 11/72
Gloucester GL2 6EE

HENRY'S - Your complete Semi-Conductor Store!

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIR-CHILD



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
8N7400	0.20	0.18	0.16	8N7450	0.20	0.18	0.16	8N74145	1.50	1.40	1.30
8N7401	0.20	0.18	0.16	8N7451	0.20	0.18	0.16	8N74150	3.35	2.95	2.15
8N7402	0.20	0.18	0.16	8N7453	0.20	0.18	0.16	8N74151	1.10	0.95	0.80
8N7403	0.20	0.18	0.16	8N7454	0.20	0.18	0.16	8N74153	1.35	1.27	1.20
8N7404	0.20	0.18	0.16	8N7460	0.20	0.18	0.16	8N74154	2.00	1.75	1.55
8N7405	0.20	0.18	0.16	8N7470	0.30	0.27	0.25	8N74155	1.55	1.47	1.35
8N7406	0.30	0.27	0.25	8N7472	0.30	0.27	0.25	8N74156	1.55	1.47	1.35
8N7407	0.30	0.27	0.25	8N7473	0.40	0.37	0.35	8N74157	1.80	1.70	1.50
8N7408	0.20	0.18	0.16	8N7474	0.40	0.37	0.35	8N74160	2.80	2.40	2.25
8N7409	0.45	0.42	0.35	8N7475	0.55	0.52	0.50	8N74161	2.80	2.40	2.25
8N7410	0.20	0.18	0.16	8N7476	0.45	0.42	0.39	8N74162	4.40	3.95	3.70
8N7411	0.23	0.22	0.20	8N7480	0.80	0.75	0.67	8N74163	3.40	3.25	3.00
8N7412	0.42	0.40	0.35	8N7481	1.25	1.15	1.10	8N74164	2.75	2.50	2.10
8N7413	0.30	0.27	0.25	8N7482	0.87	0.80	0.70	8N74165	4.00	3.50	3.00
8N7416	0.30	0.27	0.25	8N7483	1.00	0.90	0.85	8N74166	4.00	3.50	3.00
8N7417	0.30	0.27	0.25	8N7484	0.90	0.85	0.80	8N74167	6.25	5.60	5.10
8N7420	0.20	0.18	0.16	8N7486	0.45	0.41	0.38	8N74170	1.10	0.95	0.85
8N7422	0.48	0.44	0.40	8N7490	0.45	0.42	0.39	8N74172	2.00	1.75	1.60
8N7423	0.48	0.44	0.40	8N7491AN	1.00	0.95	0.90	8N74173	1.50	1.40	1.35
8N7425	0.48	0.40	0.35	8N7492	0.75	0.70	0.65	8N74176	1.80	1.65	1.50
8N7427	0.42	0.39	0.35	8N7493	0.75	0.70	0.65	8N74177	1.60	1.45	1.25
8N7428	0.50	0.45	0.42	8N7494	0.80	0.75	0.70	8N74180	1.55	1.30	1.20
8N7430	0.20	0.18	0.16	8N7495	0.80	0.75	0.70	8N74181	7.00	6.00	5.50
8N7432	0.42	0.39	0.35	8N7496	1.00	0.97	0.95	8N74182	2.00	1.80	1.60
8N7438	0.65	0.60	0.50	8N7497	1.00	0.95	0.90	8N74184	2.40	2.20	2.00
8N7437	0.65	0.60	0.50	8N74100	2.50	2.30	2.00	8N74185A	2.40	2.00	1.90
8N7438	0.65	0.60	0.50	8N74104	1.45	1.35	1.20	8N74190	1.95	1.85	1.75
8N7440	0.20	0.18	0.16	8N74105	1.45	1.35	1.20	8N74191	1.95	1.85	1.75
8N7441AN	0.75	0.72	0.70	8N74107	0.50	0.45	0.40	8N74192	2.00	1.90	1.80
8N7442	0.75	0.72	0.70	8N74110	0.80	0.70	0.60	8N74193	2.00	1.90	1.80
8N7443	1.00	0.95	0.90	8N74118	1.00	0.95	0.90	8N74194	2.00	2.25	1.90
8N7445	2.00	1.75	1.60	8N7415	1.90	1.75	1.65	8N74195	1.55	1.70	1.60
8N7446	2.00	1.75	1.60	8N74121	0.80	0.55	0.50	8N74196	1.55	1.40	1.30
8N7447	1.75	1.60	1.45	8N74122	1.25	1.25	1.10	8N74197	1.80	1.70	1.60
8N7448	1.75	1.60	1.45	8N74123	2.70	2.55	2.47	8N74198	4.80	3.70	3.35
				8N74141	1.00	0.95	0.90	8N74199	4.60	3.70	3.35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
 LARGER QUANTITY PRICES PHONE (01) 402 4891
 TEXAS HANDBOOK NO. 2, I.C. 700 PAGES DATA 60p. POST 20p.
 HIGH POWER SM 74 HOO Now in stock—send
 LOW POWER SM 74 LOO for list No. 36

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AAY30 10p	BC147 12p	HU105 2.25	OC44 15p	T1843 25p	2N3055 55p
AAV42 15p	BC169C 12p	BY100 15p	OC45 15p	V405A 25p	2N3440 75p
AAZ13 10p	BC182 10p	BY126 15p	OC57 50p	ZTX108 12p	2N3442 1.25
AC107 35p	BC214 15p	BY127 15p	OC71 15p	ZTX300 12p	2N3525 75p
AC126 25p	BCY32 75p	BYZ13 85p	OC72 25p	ZTX301 15p	2N3614 55p
AC127 25p	BCY34 45p	CI06D 10p	OC77 40p	ZTX302 18p	2N3615 75p
AC128 25p	BCY39 1.00	CI08H 55p	OC81 25p	ZTX341 20p	2N3702 10p
AC176 25p	BCY43 30p	CI08S 25p	OC82 30p	ZTX300 15p	2N3704 10p
AC187 25p	BCY43 25p	CI08S 25p	OC140 55p	ZTX503 17p	2N3705 10p
AC188 25p	BCY55 2.50	LM309K	OC170 25p	ZG301 30p	2N3714 1.80
ACY17 30p	BCY70 15p	(T03) 1.87	OC171 30p	2N404 20p	2N3771 1.75
ACY20 20p	BCY71 20p	MAT121 25p	OC200 45p	2N527 35p	2N3773 2.00
ACY21 20p	BCY72 10p	MJE340 50p	OC201 75p	2N596 15p	2N3790 2.25
ACY39 55p	BCY87 2.98	MJE370 70p	OC202 80p	2N597 15p	2N3820 50p
AD140 50p	BCZ11 50p	MJE390 75p	OC203 50p	2N706 75p	2N3820 50p
AD149 50p	BD124 80p	MJE2955	OCPT1 1.25	2N930 20p	2N3866 85p
AD161 35p	BD131 75p	1.10	ORP12 50p	2N987 45p	2N3903 15p
AD162 35p	BD132 80p	MJE3055	ORP60 40p	2N1131 25p	2N3906 12p
AF117 20p	BF115 25p	75p	P346A 20p	2N1132 25p	2N4061 12p
AF118 50p	BF107 25p	MPF105 40p	RA8310AF	2N1302 18p	2N4062 12p
AF124 25p	BF173 25p	NKT214 20p	45p	2N1304 22p	2N4126 15p
AF139 30p	BF179 30p	NKT216 40p	RA8508A1P	2N1305 22p	2N4871 35p
AF186 40p	BF180 30p	NKT217 40p	55p	2N1307 25p	2N5457 30p
AF239 40p	BF194 15p	NKT403 70p	TAA263 75p	2N1308 25p	2N5777 55p
ASV27 30p	BF195 15p	NKT404 50p	TAL209 38p	2N1613 20p	28001 1.00
ASV28 25p	BF891 25p	OA5 50p	TIP29A 50p	2N1671 1.00	28012 10.00
BA102 30p	BF898 25p	OA10 35p	TIP30A 50p	2N1247 75p	28018 6.25
BA115 7p	BFX25 25p	OA81 10p	TIP31A 80p	2N190 80p	28026 9.90
BA145 15p	BFX34 75p	OA91 7p	TIP32A 70p	2N2217 25p	28301 50p
BAX13 5p	BFX37 30p	OA200 7p	TIP33A	2N2219 20p	28303 65p
BAX16 7p	BFX88 20p	OA202 10p	1.00	2N2221 25p	28324 95p
BC107 10p	BFY50 20p	OC16 75p	TIP34A	2N2222 50p	40250 50p
BC108 10p	BFY51 20p	OC20 85p	1.50	2N2369A	40360 40p
BC109 10p	BFY52 20p	OC23 65p	1.50	2N1302 15p	40361 40p
BC109C 12p	BFY84 50p	OC25 40p	1.50	2N2906 20p	40362 60p
BC113 15p	BFY90 80p	OC28 65p	1.50	2N2926 (all	40408 50p
BC117 20p	BSX20 15p	OC35 50p	3.00	coils) 10p	40486 75p
BC143 35p	BSY27 15p	OC36 65p	85p	2N3053 20p	40636 1.10
		OC42 40p	TIP42A 75p	2N3054 50p	40430 1.00

INTEGRATED CIRCUIT SOCKETS LOW PROFILE PLATED PINS



(16 Lead
 D.I.L.)
 17p

(14 Lead
 D.I.L.)
 15p

(8 Lead
 D.I.L.)
 15p

QUANTITY DISCOUNTS

10% 12+ : 15% 25+ : ANY ONE
 20% 100+ : 25% 250+ TYPE

From above sections except Integrated Circuits and Special Offers where discounts are included.
 Minimum order value £1 please.
 Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	1000 MC/S	59p
25 +	20p	
100	+ 15p	
500 +	15p	

AFI17 Mullard 25p

25 +	17p
100 +	15p
500 +	12p

OC170 Mullard 25p

25 +	20p
500 +	18p
1000 +	13p

BY127 Mullard 15p

25 +	12p
100 +	10p
500 +	9p
1000 +	8p

OA202 10p

25 +	8p
100 +	7p
500 +	6p
1000 +	5p

OC35 Mullard 50p

25 +	45p
100 +	40p
500 +	35p
1000 +	30p

ZENER DIODES

400 M/W 5%
 Miniature
 BZY 88 Range
 All voltages
 3.3 - 53 Volt
 10p each

25 +	9p
100 +	8p
500 +	6.5p
1000 +	5p

Any one type.

1 1/2 Watt 5%
 Wire Ends
 Metal Case
 All voltages
 6.8 - 100 Volts
 20p each

25 +	60p
100 +	18p
500 +	12p
1000 +	10p

Any one type.

3 Watt Plastic
 Wire Ends 5%
 3EZ Range
 All voltages
 6.8 - 100 Volts
 30p each

SILICON RECTIFIERS WIRE ENDED PLASTIC

Type P.I.V. 1-11
 1 amp miniature
 1N4001 50 8
 1N4002 100 7
 1N4003 200 8
 1N4004 400 8
 1N4005 600 10
 1N4006 800 12
 1N4007 1000 15
 1 1/2 amp miniature
 PL4001 50 8
 PL4002 100 9
 PL4003 200 10
 PL4004 400 10
 PL4005 600 12
 PL4006 800 15
 PL4007 1000 15


2N2926	10p
All Colours	
25 +	9p
100 +	8p
500 +	6p
1000 +	5p

2N3819 Texas 35p

25 +	30p
100 +	25p
500 +	20p
1000 +	15p

BC107, BC108, BC109 10p each

All Makes	
25 +	8p
100 +	7p
500 +	6

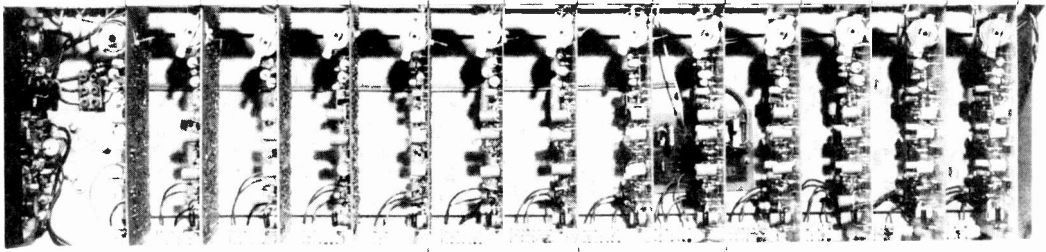

The thirteen pitch boards mounted in a wooden sub-frame

rejects from the Ferranti ZS170 and ZS100 series production lines. *Reject devices are not available from the manufacturer*, but similar diodes are available from a number of suppliers.

The specification required is that all diodes should have a breakdown in excess of 20 volts, and be reasonable low leakage, which should be adequately covered by the use of silicon types.

The 4.7 volt Zener diodes were Ferranti type KSO47A, but again a number of equivalents should also be available.

PITCH BOARD LAYOUT

In arranging a component layout for the pitch board an attempt was made to match the physical to the circuit arrangement. This can be seen by comparing Figs. 3.1 and 3.4.

Thirteen boards are required in total. Of these 12 are required containing the full circuitry and they cover bottom F to top E.

It must be obvious, however, that in a five octave 61 key system a single note generator is required to produce top F. In general the only requirements for the thirteenth board are an oscillator, single envelope circuit, mixer and pre-amplifier. No divider circuitry is required.

The components required for this particular board are marked with an asterisk in the components list.

WINDING THE TUNING COIL

To make up the tuning inductors for the oscillators, simply pile wind 260 turns of 36 s.w.g. enamelled copper wire onto the bobbin. With even layers this works out at about 33 turns/layer. When this is done bring the wire end out through one of the slots on the bobbin on the same face as entry. Doubling the wire back, continue to wind on an additional 260 turns. The point where the wire is doubled is, of course, the centre tap and this and the two ends should be cleaned prior to tag soldering.

To hold the coil in place on the bobbin, wrap round a piece of insulation tape. With the pot core clamped round the bobbin and lead outs soldered to the tag board the inductor can be assembled to the p.c.b.

Details on the tuning process and choice of capacitor will be provided later.

Note: All enquiries for Kimber-Allen keyboard should be directed to Alan Douglas, 4 Lees Barn Road, Radcliffe-on-Trent, Notts.

AUDIO FESTIVAL AND FAIR

FOR the fourth consecutive year PRACTICAL ELECTRONICS is exhibiting at the International Audio Festival and Fair, held at Olympia, London from October 24 to 28, 1972. Equipment on display on **Stand 19** includes the P.E. Electronic Piano (currently being described in the magazine) and a number of other exciting projects to be published in the coming months; these are:

Sound Synthesiser

The P.E. Music Synthesiser is a completely self-contained sound effects unit whose composition possibilities extend as far as the user's imagination. The modular construction of the various electronic sub-assemblies means that the synthesiser can provide a limited facility for sound source production and treatments even in early stages of construction. This, of course, offsets the total production cost and enables the constructor to build, test and play with the separate modules according to his effects requirement.

A fascinating feature is that the synthesiser can be programmed to play by itself for as long as the listener wishes. (See *Lecture-Demonstration below*.)

Rhythm Generator

This variable-tempo rhythm generator can be programmed to any required rhythm to accompany a piano, organ or other musical instruments.

The percussive effects available are bass drum, high and low bongos, blocks, snare drum, cymbals and long and short brushes. Besides the programmed facility a selector switch provides a choice of a number of popular rhythms.

High Quality Tape Link

Forthcoming articles will describe how to build new stereophonic electronics for an existing tape transport deck or for a complete recorder.

The Tape Link employs separate record and replay amplifiers, the latter being driven via an extremely low current bias f.e.t. stage from a low impedance head; consequently noise and distortion figures are kept to a very low level. Replay equalisation is achieved with an integrated circuit operational amplifier, which also provides frequency compensation for circuit stability and output short circuit protection. Power amplifiers are not included. Tape speeds catered for are $1\frac{7}{8}$, $3\frac{3}{4}$, $7\frac{1}{2}$ inches per second.

Lecture-Demonstration

Visitors to the Audio Fair should note the P.E. Sound Synthesiser is being demonstrated during a special lecture entitled "Sound Synthesis for the Amateur", presented in the exhibition lecture theatre on Tuesday, October 24 and again on Saturday, October 28, at 2 p.m.

We welcome all readers in London in October to see our exclusive designs in the flesh. Only at Olympia, October 24 to 28, 1972.

SINCE few component manufacturers use really identifiable identification markings on their components, it is inevitable that sooner or later the home constructor will require a piece of equipment, which will enable him to measure the value of a component from which these markings have been erased. Such a unit is also extremely useful when trying to locate a faulty component, or when trying to identify one with an unfamiliar colour coding. The bridge described in this article will fulfil all these functions.

CIRCUIT DESCRIPTION

An extremely simple circuit with only three transistors is used. Ranges of the bridge cover capacitance from 100pF to 10μF and resistance up to 100 kilohms, in five ranges of capacitance, and five ranges of resistance.

These ranges are as follows:

Range	Capacitance	Resistance
1	100pf-1000pf	0-10Ω
2	1000pf-0.01μF	0-100Ω
3	0.01μF-0.1μF	0-1kΩ
4	0.1μF-1μF	0-10kΩ
5	1μF-10μF	0-100kΩ

THE WHEATSTONE BRIDGE

The circuit is based on the Wheatstone Bridge, and a short explanation of the operation of this will be given.

The circuit of a basic Wheatstone Bridge is given in Fig. 1. It will be seen that the bridge consists of four resistors and a meter. There will be no indication on the meter when the circuit is balanced, that

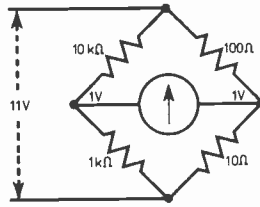


Fig. 1. The basic Wheatstone Bridge circuit (left)

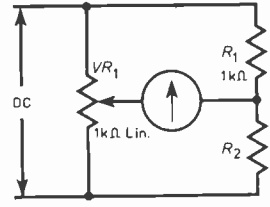


Fig. 2. A modification of the Wheatstone Bridge circuit normally used for resistance measurement (right)

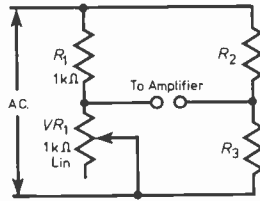


Fig. 3. An improvement of the previous circuit which produces a linear scale (left)


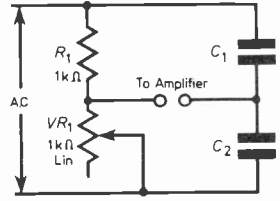


Fig. 4. A modification of the basic bridge circuit used to measure capacitance. This system does not produce a linear scale (right)

Simple C-R BRIDGE

By R. A. PENFOLD

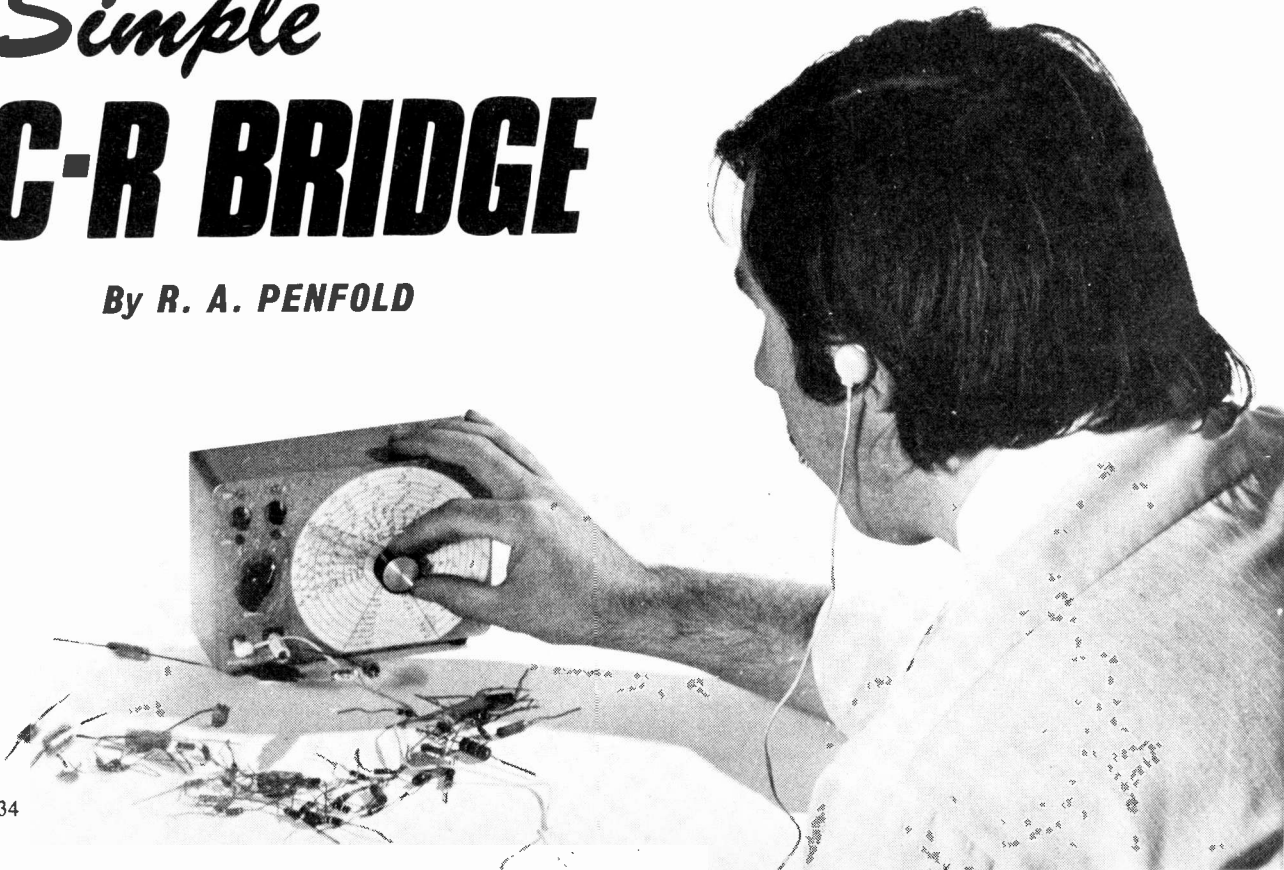

is, when there is the same voltage at the junction of the 1 kilohm and the 10 kilohm resistors as there is at the junction of the 10 ohm and 100 ohm resistors.

The meter will read the difference between the two potentials at these points. As there is one volt across both points, there is no difference in potential, and there can be no deflection on the meter.

Should one of these resistors be altered in value, even very slightly, then there would be an indication on the meter. If R_1 and R_2 were replaced by a potentiometer, as in Fig. 2, then it would be possible to adjust this component so that the circuit was once again balanced.

The voltage on the slider of the potentiometer would be variable from zero to the supply voltage, and could therefore be adjusted for zero reading on the meter, whatever the ratio of R_1 to R_2 .

If the variable resistor is fitted with a suitable scale, then when this component is adjusted for a null on the meter, the value of the resistor under test may then be read off the scale.

This is of course only possible if R_1 is a fixed, and known value, or a series of resistors of known value. Whatever the value given to R_1 , the same value will appear at the centre of the scale of $\sqrt{R_1}$.

IMPROVED METHOD

Theoretically the circuit is capable of measuring any resistance from zero to infinity, but in practise, the scale would become so cramped at the ends, that it would be impossible to use.

Therefore if R_1 is made of several switchable resistors, then the resistor to be tested can be measured near the centre of the scale, where it is less cramped.

An improved arrangement is shown in Fig. 3. This will measure resistance from zero to the value of R_3 with a linear scale. There is no cramping of the

scale, which covers a far smaller range than the arrangement of Fig. 2.

This arrangement is also different in that the d.c. source has been replaced by an a.c. source, and the meter has been replaced by an audio amplifier, which would be connected to an earpiece.

Using an a.c. source enables capacitance to be measured by changing the resistor, R_2 , for a capacitor. Fig. 4 shows the arrangement for the measurement of capacitance.

Unfortunately, when measuring capacitance a linear scale is not obtained. This is due to reactance (resistance to an a.c. flow) decreasing as capacitance increases.

This means that the bridge will measure from the value of C_1 to infinity, with a centre scale of double the value of C_1 . The scale does become rather cramped at the high value end, but this is far less so than the arrangement of Fig. 2.

THE PRACTICAL CIRCUIT

A circuit diagram of the complete C-R Bridge is given in Fig. 5.

A multivibrator using two BSY95A transistors is used to provide the a.c. source. The audio amplifier uses a single type 2N2926 transistor, which feeds into a high impedance crystal or magnetic earpiece.

The range switch is a two-pole five-way wafer switch which selects one of five resistors from 10 ohms to 100 kilohms and one of five capacitors from 100pF to 1 μ F. A second switch is used to select either resistance or capacitance.

Separate power supplies have to be used for the amplifier and the multivibrator, to prevent the amplifier from picking up the output from the multivibrator through the supply lines. This also makes the coupling between the bridge, and the oscillator and amplifier much simpler.

Two torch batteries are used to supply the power.

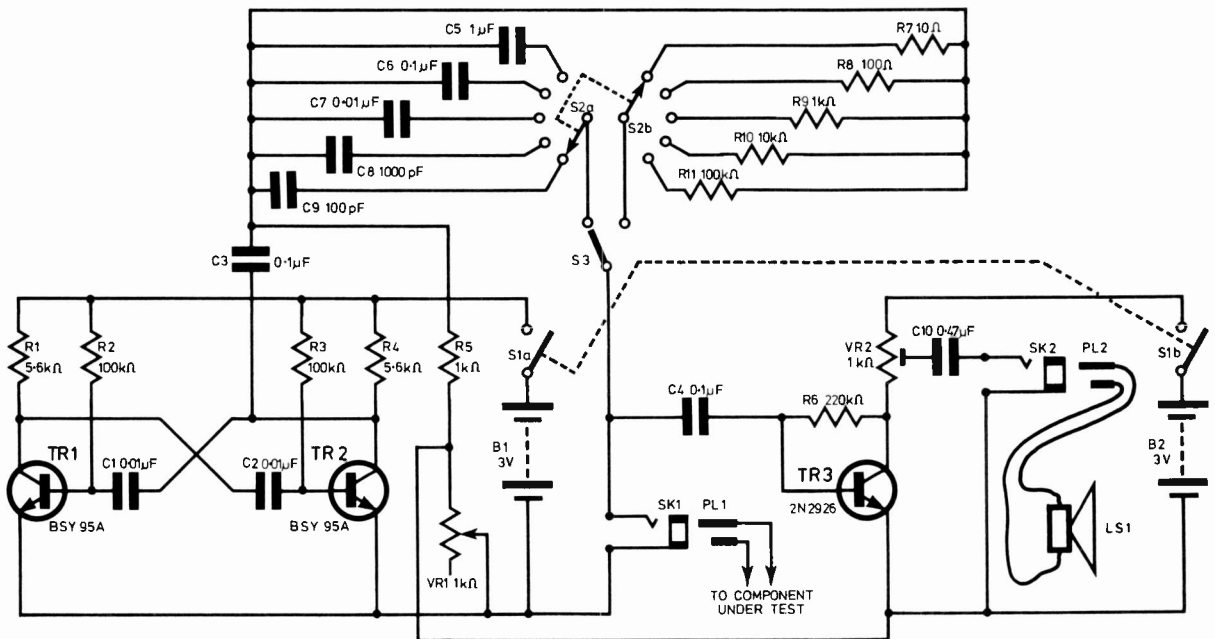


Fig. 5. Circuit diagram of the complete unit with the oscillator, bridge and amplifier

COMPONENTS . . .

Resistors

R1	5.6k Ω
R2	100k Ω
R3	100k Ω
R4	5.6k Ω
R5	1k Ω 2%
R6	220k Ω
R7	10 Ω
R8	100 Ω
R9	1k Ω
R10	10k Ω
R11	100k Ω

} 2%

All $\pm 10\%$ $\frac{1}{2}$ W unless otherwise stated

Potentiometers

VR1	1k Ω linear wirewound
VR2	1k Ω miniature skeleton preset

Capacitors

C1, C2	0.01 μ F ceramic (2 off)
C3, C4	0.1 μ F ceramic (2 off)
C5	1 μ F
C6	0.1 μ F
C7	0.01 μ F
C8	1000pF
C9	100pF
C10	0.47 μ F

} 5% or better

Transistors

TR1, TR2	BSY95A or similar (2 off)
TR3	2N2926

Switches

S1	2 pole on/off slide
S2	2 pole 5-way rotary
S3	1 pole changeover slide

Miscellaneous

PL1, PL2 and SK1, SK2	Miniature jack plugs and sockets (2 off)
LS1	High impedance earpiece
B1, B2	3V torch batteries (2 off)
$3\frac{1}{2}$ in \times $1\frac{1}{2}$ in	0.15in matrix Veroboard
	Aluminium case, battery clips, crocodile clips

COMPONENTS

As the sensitivity of the earpiece may vary according to which particular type is used, a one kilohm preset potentiometer is incorporated, so that the output may be reduced, should it be found to be excessive. The circuit is unsuitable for use with a low impedance earphone.

Although adequate results may be obtained using a carbon potentiometer for VR1, better results will almost certainly be obtained using a wirewound type. Other components for the bridge should preferably be one or two per cent tolerance types, with a high stability, if a reasonable accuracy is to be attained.

Transistors other than the types specified have been found to work in the circuit, and it would operate using almost any transistors.

CONSTRUCTION

The prototype was built in an aluminium case, measuring $6\frac{1}{2}$ in \times $4\frac{1}{2}$ in \times $2\frac{1}{2}$ in, but almost any case of about these dimensions could be used, although the unit could not easily be made much smaller than this.

If a metal case is used, neither the oscillator or the amplifier should be earthed to it as this would encourage oscillator breakthrough.

A small piece of Veroboard (0.15in matrix) 21×7 holes, was used as a basis on which to construct the main circuit. A wiring diagram for this is given in Fig. 6.

The best method for connecting the component under test into circuit was found to be a lead with a jack plug one end, and a couple of crocodile clips the other end.

The jack plug may be plugged into the bridge, while the crocodile clips connect to the leads of the component under test.

INTERWIRING

All wiring associated with VR1, switches S1 and S2, and the two crocodile clip leads, should be as short as possible otherwise breakthrough of oscillations may make it impossible to locate a proper null point on some ranges, and capacitance in the wiring could make capacitance Range 1 wildly inaccurate.


Both the earphone socket and the test lead socket have to be insulated from the front panel to prevent them from being electrically connected, and to prevent breakthrough. This may be achieved by drilling the mounting holes slightly too large, and then fitting bakelite washers either side of the panel.

Capacitor C10 is only required if the bridge is to be used with a magnetic earpiece. If a crystal type is used, C10 may be omitted, and the earpiece connected directly to the slider of VR2.

CALIBRATION ACCURACY

Although both the resistance and the capacitance scales can be calculated mathematically this is unnecessarily complicated, and is unlikely to be as accurate as the following method. This method is to calibrate the scale against a number of close tolerance components of suitable values.

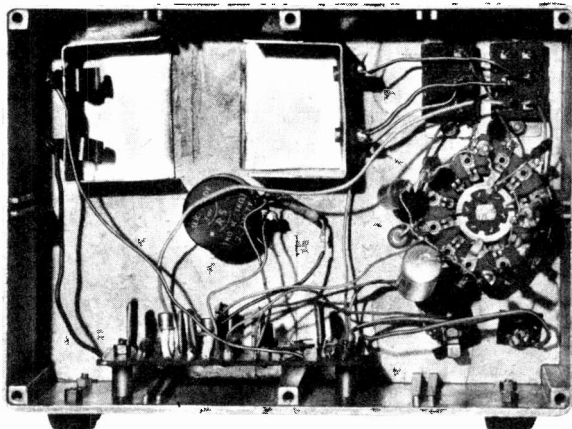
An individual scale is required for each range. The resistance scales will read in the opposite direction to the capacitance scales. They should be marked in preferred values, from 10 to 100. At the end of each scale there should be added a multiplier. For example. On Range 4 resistance $\times 100$ should be added at the end of the scale, so that if



Rear view of the unit showing the disposition of the batteries, component board and switches

ELECTRONIC MUSICAL INSTRUMENTS

...A SURVEY OF THE COMMERCIAL SCENE



If one goes back far enough, and includes isolated private experiments, it is difficult to know just when electrical music started. It is certainly more than 100 years ago. But practical instruments have only been in existence for some 40 years, so it is a comparatively new art, now rapidly expanding with the semiconductor and its offshoots.

Electronics is linked to music in two ways: either the sound is produced by a conventional instrument which uses electrical means to process it in some way (e.g. amplification or change in tonal quality), but where the sound could still be heard if there were no electronics; or, the "sound" is generated by electronic circuits, originating as electrical oscillations or waveforms and therefore inaudible without further electronic processing.

Electronics is a science; music is an art. They do not speak the same language for one is based on provable parameters, whilst the other relies entirely on personal

appraisal. For this reason we cannot comment on the aesthetic appeal (or otherwise) of electronic music. But to the technically inclined, there are other appeals; the future is pregnant with unlimited scope for generating new sounds, modifying existing ones, simplifying playing techniques and many other facets of the art.

Electronics and music have grown into a formidable combination, and so we take this opportunity of bringing together some of the many examples of this association. But fully to appreciate these great advances, which so many people take for granted, one should know something of the long and fascinating history of electronic musical instrument development; the more so as this is a hobbies journal, and some of the ideas which were not suitable for commercial development make interesting propositions for "one-off" projects.

ELECTRONIC ORGANS

We begin with electronic organs, because these instruments represent the most ingenious combination of mechanics and electronics, can often be built at home, and are capable of endless development. All such instruments are played from keyboards and the controls follow internationally recognised methods to a great extent, but certainly not exclusively. The whole concept of organs has changed in the last 20 years. There is now no resemblance (in the popular mind) to the conventional organ with pipes. Yet, incredibly, the same conventional names for the sounds appear on the stops!

Harking back to the days when valve circuits tended to be unstable, mechanical systems with transducers seemed the best answer; of these, two survive today, Hammond and Compton. Such organs are permanently in tune but require complex circuitry and switching devices. With the increasing cost of manufacture it seems probable that they will disappear in time. Already solid state circuitry is taking the place of mechanical switching in pipe organs, although slowly, but for other kinds of electronic organ, semiconductors are paramount.

It is easier to start from the top and work downwards, so we give an example of an imitative organ by Conn as representing the "real thing". Fig. 1 illustrates a church or concert organ having tonal and control properties exactly corresponding with pipes.

This instrument has independently tuned oscillators for each note and these can give at least three different waveforms for tonal synthesis. As the sound in a pipe organ comes from a widely dispersed source, so this class of electronic organ requires many channels of amplification and many loudspeakers—a minimum of perhaps 25.

Multiple oscillators are never exactly in tune, but perhaps more important is the fact that there are trifling differences in the harmonic content of each oscillator. This gives a close resemblance to organ pipes, which have the same properties. The sound is full and rich, excellent for a real organ, but quite useless for pop or jazz.

Nine out of ten organs of the popular domestic type which can be seen in any music shop use a quite different generating system. The 12 top notes are produced by tuned master oscillators, but all

other pitches downwards are obtained by frequency division. Since the octave is an exact doubling or halving of any frequency, 2:1 bistables or flip-flop circuits serve admirably. Readers will recall that this was the method used in the P.E. organ. It lends itself to mass production especially now that i.c.s are becoming so cheap; and with diode or transistor keying, cheap single contacts per key suffice.

If properly designed, this kind of organ can be very satisfying more especially at the low output levels demanded in the home. Unfortunately it is commonly found in forms which have neither the proper playing facilities of imitative organs, or the "new" sounds associated with rhythmic organs. Excessive amplification makes these organs lose what character they possess, and underlines the old saying that you can't get a quart out of a pint pot.

However, the prompt attack and the easy application of rhythm units to this kind of instrument makes them eminently suitable for pop groups and this has led to a form of tonal synthesis which contrasts well with guitar or voice. To a great extent they must be treated

Fig. 1. The three manual Conn Custom organ has independently tuned oscillators for each note. These can provide at least three different waveforms for tonal synthesis of a church or concert pipe organ.



The Kentucky Challenger with string, flute and woodwind voicing available via the 4-octave solo and accompaniment manuals.

The effects include solo manual and pedal sustain, variable attack, reverberation, vibrato and Hawaiian glide.



Disco

SOUND & LIGHTING EQUIPMENT

from 4 SPECIALISED DISCO STUDIOS

HIGH POWER SPEAKER SYSTEMS

Strong leather cloth finish 1" board, fully lagged. Fitted high efficiency 8 or 16 ohm speakers.

- PRINCE.** 50 watt rms. 12". Size 24" x 16" x 12".
CONSORT. 100 watt rms. 2-12" speakers. Size 30" x 18" x 12".
MAJESTIC. 100 watt rms. 15" Crescendo. Size 38" x 24" x 15".
SOVEREIGN. 100 watt rms. 18" Bass. 12" Full range. Size 50" x 26" x 14".

FULL RANGE OF MICROPHONES, STANDS, ETC. ALWAYS IN STOCK



SOUND CONTROLLED AND SOUND TO LIGHT UNITS

Mid, Treble and Bass Channels, up to 1kw of lamps per channel plus override switching.

- DJ80L.** Sound to light. Takes output from most amplifiers. Adjustable levels.
DJ40L. Sound controlled version. Built in microphone, no connections required.

ASSEMBLED DISCOTHEQUES

DISCO-PLINTH. Consists of 2 turntables fitted with high quality ceramic cartridges. The unit has a built in cross-fade rotary control for transferring the sound from left to right decks. The unit has no amplification built in and must be used with amplifiers such as the D.J. 105S or D.J. 70S. Size 32" x 14" x 7" (incl. lid). **£55-00**

DISCO-IMP. The latest addition to the Discosound range of discotques. Even smaller and more compact than the Disco-Mini, it contains all the necessary features for the smooth running of a mobile unit. Size 29" x 18" x 7". **£79-00**


DISCO-MINI. Complete portable Disco with built-in full function preamplifier/mixer. For use with any power amplifier such as "Discmaster". Size 30" x 20" x 8". **£98-50**

DISCO-STANDARD. Has all the facilities of the Disco-Mini with the addition of a built-in 100 watt power amplifier making it a completely self contained disco unit. A V.U. meter gives visual indication of output levels. Size 32" x 27" x 7". **£180-00**


DISCO-SUPER. A slightly larger version of the Disco-Standard. Fitted individual controls for both mic. and deck inputs plus a cross-fade for deck to deck transfer. A built in P.F.L. cueing system, mic. over-ride, also a V.U. meter gives visual indication of output levels. DJ. 30L (3000w) 3-channel psychedelic light unit is a standard fitting. Deck cut out switches are also featured for ease of cueing. Size 38" x 27" x 10". **£224-00**

DISCO-SUPREME. All facilities of the Disco-Super plus a third turntable which can be used for Jingles or other effects without using the main deck system. Flexi lights are also fitted. Size 60" x 27" x 10". **£261-00**

PA-DISCO AMPLIFIERS

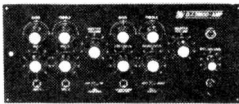

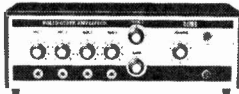DISCO-AMP. 100 watt rms. output for 8-16 ohms, 4 channel inputs, 2-mic, 2 decks. Separate volume control plus masters. Response 30Hz -30KHz, distortion less than 1%. Treble/Bass/PFL/Mic over-ride etc. Panel size 16 1/2" x 7".



DJ.70S MIXER/AMPLIFIER. 70 watt rms. output for 8-16 ohms. 2-mic, 2-aux/decks. Master volume/Bass/Treble. Size 15 1/2" x 5" x 6".

DJ.105S. 30 watt rms. version. Size 11 1/2" x 5" x 6".
DISCMASTER SLAVE AMPLIFIER. 100 watt rms. for 8-16 ohms. **£59-50**

NEW D.J. 500 SERIES P.A. AMPLIFIERS 50 WATT, 70 WATT & 100 WATT MODELS


This new range incorporates many features that make them ideal for the professional user, clubs, discotheques, factories etc. Fibre glass P.C. Boards are used throughout with low noise silicon transistors, high stability resistors, generously rated components and hand-welded assembly to ensure reliability and quality.

★ Exclusive "Fail Safe" Electronic Protection circuit.

★ Fault Condition warning lamp.

★ Built in bass boost below 30 Hz.

★ 4 channel mixer with slider control.

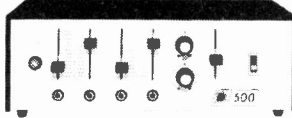

All three amplifiers have a built in emitter follower output socket for connecting a slave amplifier to enable the power output to be increased up to 1000 watts or more if required. A matching range of slave power amplifiers and a separate matching 100V line transformer is available

SPECIFICATION

Frequency Response	50-20,000 Hz ± 3db (10dB Bass Boost at 10 Hz)
Signal/Noise Ratio	better than =50db.
Harmonic Distortion	less than 1%
Speaker Impedance	8-16 ohms.
Inputs: Mic 1 & 2	5mV at 50K ohms (50 or 600 ohm to order)
Aux 3 & 4	100mV at 1 meg ohm.
Size (all models)	15 1/2" x 5" x 6".
Power Output:	Model D.J.500 — 50 watts R.M.S. £56-25
(at 8 ohms)	Model D.J.700 — 70 watts R.M.S. £67-50
	Model D.J.1000 — 100 watts R.M.S. £79-00

DISCO MINI


Hardly larger than a suitcase yet contains all the necessary features for a high quality mobile unit. The pre-amp has separate tone controls for both mic. and decks, and each input has its own individual volume controls and inputs.

plus the addition of a cross fade for deck to deck sound transfer. A built in P.F.L. system for cueing, together with mic-over-ride facility are standard on all units. Response 20-20,000 Hz. Mic. input 5mV. 50K. Output 1 volt.

McDonald M.P.60 Turntables are used with high quality ceramic cartridges, and each deck has its own individual cut out switch fitted. This unit is suitable for Discos or Clubs having a power amplifier, or for use with the "Discmaster" 100 watt power amplifier as above. Size 32" x 20" x 8". **£98-50**



EFFECTS PROJECTORS

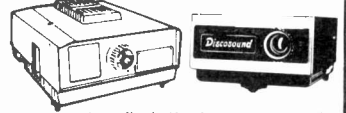

A small selection from our vast stock and Group use.

- DISCO COLT.** 150 watt.
LIQUIMATIC MINI. 50 watt Q1 with 6" wheel.
DISCOWHEEL. 50 watt Q1 with quick change Cassette.
GNOME 150. 150 watt Q1 with Cassette.
LIQUIMATIC. 150 watt Q1 with 6" wheel.
PLUTO TUTOR-2. 250 watt Q1 with Cassette and 6" wheel.
TUTOR-2. with Liquidspole Tank.
KALEIDOSCOPE LENS (for Tutor-2) 8" Liquid Wheel and Crystal Wheel Liquid Cassette and Moire (24 different types to choose from). Portable Hi-Power Strobes.


YOU WILL BE SURPRISED BY THE LOW PRICES & PERFORMANCE

SDL POWER SPEAKERS

High efficiency 12" speakers. Ferrite magnets. Heavy duty voice coils and cones for Disco and Group use.

- 12" 50 watt rms. 8 ohm Full range.
 12" 25 watt rms. 15 ohm Mid-Treble.
 15" 50 watt rms. 15 ohm. Full range.
 15" 100 watt rms. 15 ohm. Bass.
 18" 100 watt rms. 15 ohm. Bass.

DISCO SPOT BANK

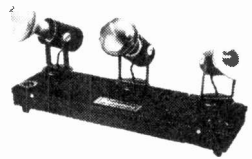

Designed to take three E/S Type spot or colour bulbs up to 150 watts each. The unit is of all metal construction and has one 3-pin mains input socket plus one 3-pin main-outlet socket for connecting more than one bank together if required. The unit can be left free-standing or wall mounted if needed. Black crackle finish gives the unit a very professional appearance.

Size 18" x 6" x 7" (excluding bulbs)

Also in stock: Ultra Violet Spot Lamps and Fluorescent Lamps, Standard and Colour Spot Lamps and Fittings. Rotating Colour Displays. Flexilights, Fibre Optics, Dimmers, Flashers Effects Foils, etc. Your enquiries invited.

MIXER UNITS

DJ.101. Battery powered, 6-channel, variable levels, 3 x 50k mic., 1 x 100mV. aux., 2 x 100mV p.u. Output 250mV.

DJ.102. Mains operated, 4-channel, variable levels. 2 x 50k mic., 2 x 100mV p.u. PFL control, master volume, mic. over-ride, output variable 0-500mV.

DISCO 40. Pre amp part of Disco amp (see above). All facilities. Output will drive up to ten 100 watt amplifiers.

Discoscene

536, Sutton Road,
Southend, Essex.
(0702) 611577

Discosound

122, Balls Pond Road,
London, N.1.
(01) 254 5779

Discosound

(Birmingham) Ltd.
494, Bristol Road,
Selly Oak, B'ham 29.
(021) 472 1141

Henry's Disco

309, Edgware Road,
London, W.2.
(01) 723 6963

CHECK WITH YOUR NEAREST STUDIO FOR LATEST PRICES AND DETAILS (TRADE AND RETAIL SUPPLIED)

Go Hi-Fi yourself!

**New Goodmans Din 20
loudspeaker kit—specially
designed to give the D.I.Y.
enthusiast excellent hi-fi
reproduction at moderate
cost.**

This system has been thoroughly tested to Goodmans high standards. It will provide extremely satisfactory listening levels from amplifiers rated at 10 watts (per channel, in the case of stereo equipment) but it may also be operated from amplifiers of higher power.

The kit contains all parts needed to complete the system (except timber and other material for the cabinet itself) and has detailed, illustrated assembly instructions.

Contents

1. Bass unit 204mm (8in) diameter
 1. Dome HF radiator 25.4mm (1in) diameter
 1. Port tube
 1. Crossover panel with colour coded leads
 1. Terminal board
 1. Foam gasket
 1. Input lead complete with DIN plug and spade terminals
- Acoustic wadding foam pad
Fixing screws and hardware
Cabinet template (on bottom of box)

Specification:

20 watts DIN, 4 ohms impedance, 8in bass unit, dome HF radiator, crossover frequency 4,000 Hz

**For further details
and the name of
your Goodmans
dealer, send the
coupon now**



Goodmans
Sound reasoning.

THORN A member of The Thorn Group

Name _____

Address _____

PE3

To: Goodmans Loudspeakers
Ltd., Downley Road, Havant,
Hampshire

Please send me free leaflets on
Constructors' equipment and
the name of my Goodmans
dealer

audio ICs from Ferranti..

See us at the Audio Festival and Fair

STAND 6

Ferranti Limited, IC Marketing,
Electronic Components Division,
Gem Mill, Chadderton, Oldham,
Lancs. OL9 8NP
Telephone: 061-624 6661

FERRANTI

FE420 

as new sound devices and we show one of the most modern and effective examples in Fig. 2. This is made by Jennings Electronic Instruments, and bristles with ingenious features.

In this organ, the emphasis is on facilities for rhythmic playing rather than on simulation of conventional organ tonecolours; a special training and a special mentality is required to conform to the needs of a purely rhythmic group, and this is an excellent example of an instrument specially designed to this end.

The foregoing organs have all had tuned oscillators for each primary function and once these are adjusted, it is not possible to alter them easily. But now, it is possible to design and make an organ having only one master oscillator from which all pitches are derived. One great advantage is clearly that transposing is easily carried out—i.e., if one presses just one key, the pitch can be changed by a single adjustment so

that one passes through a succession of keys. The player who can only use the white keys can now accompany say, a B flat clarinet whilst still using his white keys.

There are several ways of doing all this, mostly very complex, and all a tribute to microminiature circuits; for without these it would be quite impossible to build such an organ within any console or case. Modern i.c. component density can reach 2,000 elements in a chip only $\frac{1}{4}$ in square and so the very complex circuitry required to steer and smooth the pulses of such a system can be made quite small. Two of the present methods for generating the frequency spectrum from a single source have been described in *Practical Electronics* for July 1972 but in the picture of the Philips generator the actual size was not obvious; in Fig. 3 you can see the relative size of this unit.

An organ built from half a dozen of these units would have amazing powers of synthesis.




Fig. 3. Demonstrating the small size of the N.V. Philips' digital organ generator.

Fig. 2. The three manual, portable, Jennings J.71 with drawbar control of harmonics from 16' to 1' pitch and percussive attack. This, with the provision of dual waveforms, enables the organist to reproduce any mixture of sound required.

Other features include separate by-pass tabs for Theatre and Baroque organ. The top manual covers three octave providing 16'-8'- and 2' pitch with controls for tonal effects which include vibraharp, piano, string, percussion and sustain.



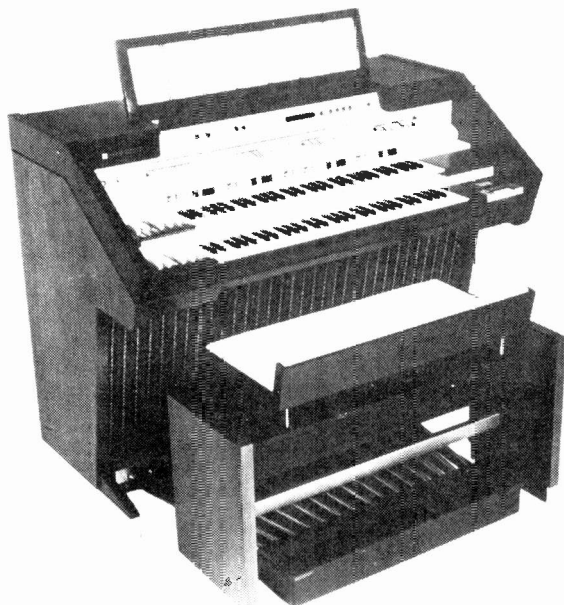One of Hammond's new models, the Concorde, incorporates custom built LSI packages. This harmonic tone-bar organ has two 61 note keyboards and such features as polysyntoesis percussion, manual and pedal sustain, automatic accompaniment and automatic rhythm, lower manual to pedal couples and cassette recorder.



Talking about synthesis, we find small keyboard controlled devices mounted in the Wurlitzer organs on which many effects not obtainable with any ordinary organ circuits can be produced. For instance, gliding tones, wah-wah, touch sensitive vibrato, extended pitch range and other effects are some of the attributes of the Orbit synthesisers on this organ. Certainly it is time that double touch was more used on organs, especially since it was an integral fitment of all cinema organs since the 1920s. So many things can be done with a second touch.

Now we have seen three kinds of tone generating systems for organs of a more or less conventional kind. But for the beginner, or one who does not wish to lay out much money on a single-purpose instrument, there are other ways of making musical sounds. Perhaps the simplest device is the

stylophone, shown in Fig. 4. This is a simple multivibrator, played by using a metallic stylus to make the connection for changing the pitch. It is a continuously re-tuned system, capable of only one note at a time, but having a vibrato circuit which relieves the monotony. Constructional articles for something of this kind have appeared in various journals and it is a nice project for the beginner.

A more sophisticated device is the Pianomate. This assumes ownership of a piano, although it could be energised by a separate keyboard. It can be seen in Fig. 5 lying over the keys of a piano. Again, it is a simple generator, but chords can be played with care. The system uses one generator for every three notes, but if played with the piano, which of course is fully polyphonic, it appears that the organesque sounds from the generator are also fully polyphonic.


A small mains unit which stands on the floor contains all the electronics and allows changes of tone-colour; a volume control pedal is also available. Incidentally, as the contact unit for the four octaves of keys only rests on the back of the piano keyboard, it can be removed or placed on another make of piano in a moment and cannot damage the woodwork.

We find many people interested in playing music who are not satisfied with synthetic tone colours; certainly many organs become very trying to listen to for long and rely heavily on vibrato to break up the lifeless sounds. Many attempts have been made to bring the actual sounds from organ pipes or orchestral instruments to the keyboard, culminating in the Mellotron. Originally this instrument was much more complex but the present version is easily portable and just as accurate tonally.

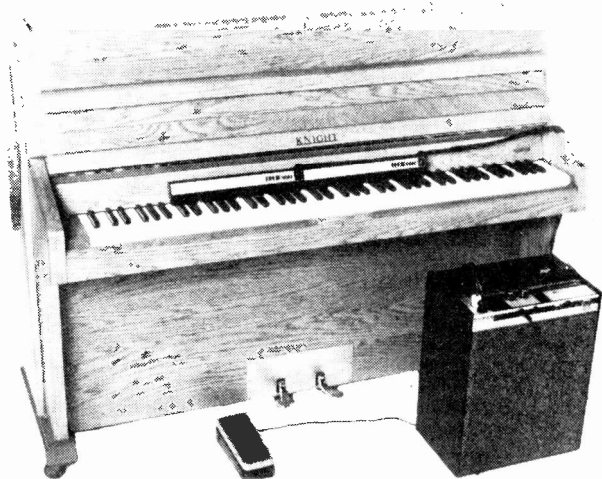Fig. 4. The Dubreq Stylophone has a reedy voice, derived from a multivibrator circuit. To this vibrato can be added if desired. This instrument is only capable of producing one note at a time, each being selected with a metal stylus which constitutes part of the electronic circuit. In concert the sound produced can be very pleasant.

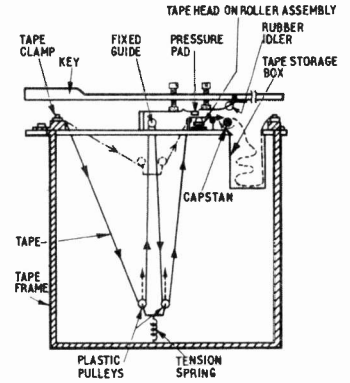


Fig. 5. The Dubreq Pianomate in position on a conventional pianoforte keyboard. This consists of two double octave unit whose contacts move with the piano key to augment the piano sounds with organesque tone colours. A tone selector switch provides three different colours: flute, church organ and jazz buzz. A two speed vibrato is also included. The Pianomate is completely tuneable via a single control for pianos which may be out of pitch by as much as a semitone



The system uses pre-recorded tapes but these are not in the form of loops as might be thought; the ingenious mechanism is too complex to describe here, but in essence when a key is pressed, a tape head is brought into contact with a record of the selected sound and continues to sound (so long as the key is held down) for up to 8 seconds. The tape then rewinds at once and is ready again. All the sounds provided are of course as authentic as the fidelity of the reproducer, all can be mixed, and many effects sounds can be brought in on other tapes; indeed, the Mellotron is popular as a pure effects machine, from which every conceivable noise can be obtained at will. Fig. 6 illustrates the action of this instrument.

Fig. 6 A pure effects machine, the Mellotron is a source for every conceivable noise. The system uses prerecorded tapes of other instrumental sounds or special effects which can be mixed at will by the performer making him, in effect, a one man band. The action of the Mellotron can be understood by referring to the profile drawing of the key and tape transport system; when the key is depressed the idler engages with the capstan pulling the tape into the storage box; the tape is kept in tension by the rising pulleys; with the key released the tape is made ready for replay as the tension spring returns to its original position pulling the stored tape with it.



The RIHA Largo, besides having the normal footages in the upper and lower manual, has fractional number stops to provide more colourful registration. Playing features include a two-speed Leslie tremulant (a spatial effect achieved by feeding the loudspeaker output into a rotatable drum), vibrato delay, which provides a much more natural vibrato sound and solo percussion which gives the choice of many effects such as banjo and Hawaiian guitar.

The sustain feature on the pedals provides a string-bass effect on the pedal 8' stops so giving rhythmic support to melody on the manuals. The sustain can also be used to play legato on the 13 note pedalboard.

The Harmonics Solette organ with a specification designed to cover all aspects of organ music from the classics to pop. It has a full size 61 note keyboard and a total of 19 registers.



Now that you've got

Audio

You've never heard it so good!



It had to happen . . . and it has. **Audio** is the new-style magazine that brings excitement and vitality to the interests of music and hi-fi.

Written and designed by an expert editorial team, **Audio** is about the latest advances in equipment, its installation, its operation. Radio and television in the home . . . tape or disc . . . film or video . . . car stereo, slot or cassette. **Audio** takes it all in; reports on all important developments.

Audio is about the music made . . . the places where the making is done . . . the reason it's done the way it is . . . the artists and composers you most enjoy. Performance test on the latest Nivico Tape Recorder

David Burnett James writes on the new Wharfedale Isodynamic Headphones.

Christopher Headington writes about a notable anniversary in Solti is Sixty . . .

Other contributors include: **Katie Boyle** **Colin Wilson** . . . **Richard Williams** . . .

Top-name contributors . . . outstanding features and illustrations special technical and record reviews.

FREE! unique 7" flexible record
Audio past present and future

with commentary spoken by **RICHARD BAKER** 33 $\frac{1}{3}$ rpm Mono Stereo

Audio

for your greater enjoyment of leisure listening - Monthly 20p

ISSUE ONE (NOVEMBER) OUT OCT 19

INSTRUMENT TRANSDUCERS

Electric guitar pick ups have been with us for a long time; more recently the use of transducers has spread to other instruments such as clarinets, saxophones, violins and accordions. The aim of these methods is twofold; to amplify the original sound, and to be able to alter the waveform of the sound by electronic means, e.g. to remove harmonics or to add extra octaves by frequency division; or to modify the steady tone in some other way. But firstly let us look at how the guitar operates.

The diameter of a string is so small compared with the wavelength of any frequency within the range of that string that the back wave from the vibration would at once neutralise the front wave and nothing would be heard; the string produces no sound, it drives the belly or resonating body of the guitar and this couples with sufficient air to make the resultant vibrations audible as sound. However, it is costly to make a good acoustic guitar and the resulting sound is not loud enough to compete with other sounds in a modern group; the acoustic guitar is therefore reserved for the classical player, since it is many times more sensitive to fingering than its electrical counterpart, and the tone is not coloured by amplifiers or loudspeakers.

For the pop scene, it is desirable to convert all sounds into electrical waveforms and hence have complete control over them. So all we need is the vibrating string with suitable pick-ups. This means a simpler instrument in theory, but by the time that electronic controls and perhaps multiple pick-ups are fitted, it may well be more complex. Constructional data for pick-ups has been published and it is very easy to amplify this sound; one can then add simple tone controls and so alter the effect. If, therefore, it is possible to use steel strings or strings wrapped with steel wire over the pick-up location, magnetic pick ups are easily applied to any stringed instrument.

Note that the string pick-up is to be preferred to any form of microphone attachment; because the latter is sensitive to air pressure waves as well, and can pick up breathing and scratching noises from fingering the string. But when one comes to other instruments, in which the same amount of energy is not required of the player (or in a different form, such as blowing a clarinet), then it is possible to use noise cancelling types of microphone to amplify the tone. Certainly this has advantages if only because the waveform of the generated sound can be changed

and one may get the effect of several different kinds of instrument from the one. An excellent example of this is the electric mouth organ or harmonica.

There are examples of amplified accordions and a number of purely electronic ones, using the circuitry of a miniature organ and connected to external amplifiers and loudspeakers. Then again, it is possible to obtain an electronic string bass unit, buttons producing all the effects from normal bowing to pizzicato or col legno (playing with the back of the bow). This is made by Hohner.


Many of these existing tone qualities can be completely transformed by, say, a percussion unit; this enables some sound which would normally be smooth and sonorous to be made aggressive and staccato. This kind of percussion unit can be wired in anywhere between a pick-up and its amplifier. It is not to be confused with a rhythm unit, which is a quite independent source of percussive sounds acting as rhythm markers and non-musical in effect. Many such rhythm boxes are on the market now, nearly every large domestic organ has one as an integral part and many can be bought to add to whatever sound source would benefit.




Hornby-Skewes accordion microphone is connected to the side of the accordion and picks up sound for feeding to an amplifier



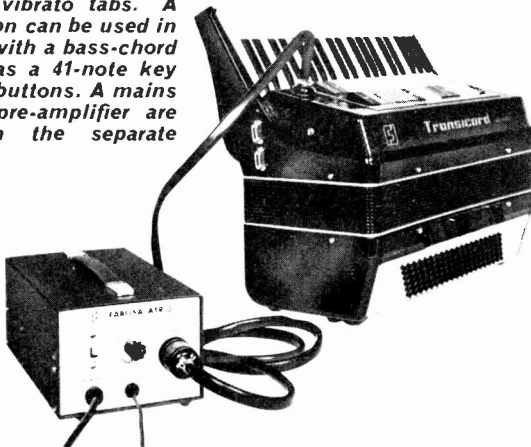Farfisa Transicord electric accordion with seven voices, sustain and vibrato tabs. A rhythm section can be used in conjunction with a bass-chord facility. It has a 41-note key and 120 bass buttons. A mains supply and pre-amplifier are contained in the separate module



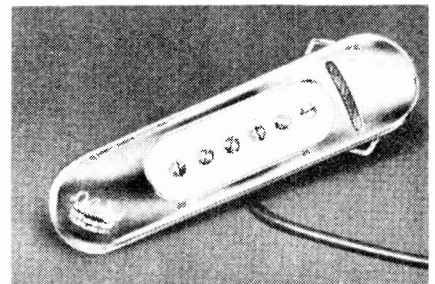Magnetic type contact pick-up with fingertip control. Suitable for nylon string guitar.




Six magnet pick-up for flat top guitars.



The Farfisa Super Piano with keyboard and decay as on the conventional piano. The effects which can be obtained on the first 24 notes are, for the bass: bass, string bass and bass guitar. For the chords: piano-forte, guitar and banjo. Also available is automatic bass and chord rhythms. Output available is 25 watts.

A Yamaha electric guitar.

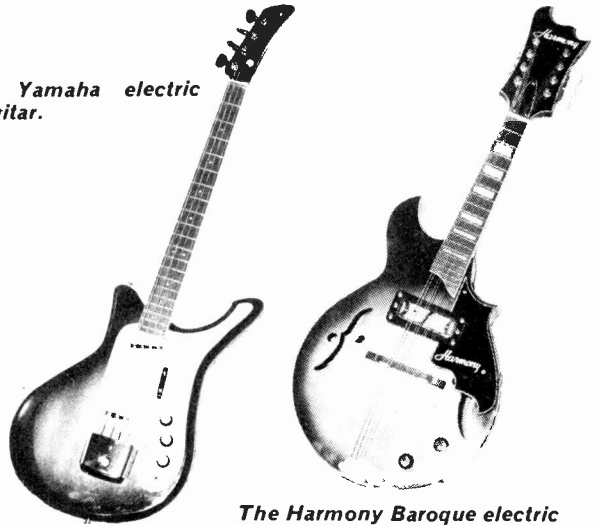

The Harmony Baroque electric mandoline with a body shape that departs from the classical for ease of playing.



Maestro ring modulator.



The Jennings Winchester "Rifle" guitar with a body which is constructed entirely of metal providing a crisp, pure tone. Apart from the normal guitar sound this instrument has internal electronics to provide bass, treble, fuzz, presence and repeat.



Soundimension: a device for providing echo and reverberation affects when used with an amplifying system.



Typical reverberation unit from the Laney Sound Supergroup Series.



A "Cry-baby" wah-wah pedal.



"Fuzz-face" distortion unit with separate volume and fuzz controls.

SPECIAL EFFECTS

The continual search for new effects has led to the electronic controls known as wah-wah, growl, glide, etc. All of these do something not normally expected from the instrument to which they are attached. Once associated solely with the guitar, they are now found on electronic organs and other complex devices. Readers will be familiar with the effects on the tone, and constructional details for most have been described in the press.

The wah-wah is a tuned circuit, the resonance of which can be altered at will; some band of frequencies is then accentuated and moves progressively to another band by the manipulation of a foot control. The growl is almost identical, but operates at lower frequencies. A glide circuit is found on some organs, usually it provides a limited frequency shift by altering the base biasing of a transistor oscillator through a voltage control; again the foot is used to move a variable resistor of some form.

Since some of these effects may be needed at short notice, it is possible to combine the controls on a single foot pedestal where the toe selects the function, whilst the heel operates a rotary volume or similar control. A commercial

multiple control unit is shown in Fig. 7. There is clearly a limit to the number of controls which can be used by someone who is usually playing an instrument at the same time.

The vibrato produced by a violinist, which is an important part of his technique, may be imparted by a mechanism which alters the tension of the guitar strings by a lever; but it can also be done by an electronic circuit—commonly a form of adjustable speed multivibrator. This again can be inserted between the pick-up and the amplifier but naturally it is not so expressive or controllable as manipulation of the strings. However, playing finesse is not so important with groups.

Since power is such an essential ingredient with today's performers, we find large amplifiers which are now sophisticated in that they have mixing and vibrato circuits incorporated; however, we shall not discuss these or loudspeakers at this time. Suffice it to say that many groups prefer valves, since they stand such overloads and misuse.


There is room for improvement in the means for connecting units together, there still are casualties from time to time and it is diffi-

cult to understand why Ministry of Defence or Home Office approved connectors are not compulsory.

One final piece of apparatus which has effects uses is the ring modulator. This is a circuit artifice whereby two applied signals are combined to form sum and difference frequencies, one of which is extracted and used as a final signal. For this reason the device should be fed from sine waves, but since these do not exist outside the laboratory, some very peculiar sounds result—always discordant.

The ring modulator is often fed from a musical source, a singing voice via a microphone, a pick-up from a saxophone, etc. Many intriguing effects are possible with care, certainly all are novel and often incapable of analysis by the hearing system yet of too short a duration to give rise to irritation. It is in fact interesting to note that distortion is deliberately sought, so intense is the search for novelty. The clipping amplifier or fuzz box is a good example of such techniques. Of course, as the ambient noise level around us increases, discomfort arising from other noises has less effect and we come to accept it.

Fig. 7. The Jennings Scrambler is a complete remote foot control of effects associated with amplification. Besides the quadrant of foot switches the Scrambler has two rotary turntable controls for intensity volume and wah-wah.

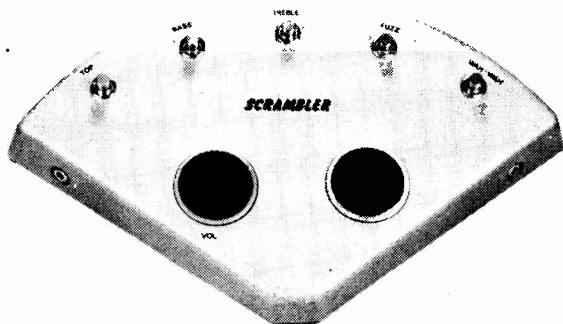

A quartet of effects units that can be used with almost any kind of electronic musical instrument.



SYNTHESISERS

The idea of compounding sounds from their bare ingredients is far from new; indeed, one of the most successful synthesisers was built 20 years ago; but, it occupies a whole room! So for a more general acceptance of these devices, we had once again to wait for the semiconductor.

Now a synthesiser is nothing more than a number of units which represent the basic parameters of sounds, so organised that they are easily controlled by the operator and of such a nature that the absolute values of these parameters can be set up again and again with accuracy; in other words, so far as is possible, the elements are calibrated.

One can compose music with a range of tonal qualities, but can-

not write this down in conventional musical notation, although it can be written in terms of instrument settings. It was never possible to write the composition of, say, a trumpet sound on a conventional music score, but one can write this electronically in terms of the values of the constituents; so in this way, the actual nature of a sound can be put in black and white so that someone else can recreate the same sound and this has never before been possible.


Clearly the facilities of a synthesiser relate to its use. An amateur experimenter may not need the many duplicated oscillators, noise sources, amplifiers and treatments which are called for by a professional musician or composer. So it is useful that simple modules can

be made or bought and added to as required. One must have at least one good tape recorder for the weakness of all synthesisers of low cost is that they have no storage facilities; all work involves short-term events and constant re-recording.

Most if not all modern synthesisers are voltage controlled; that is, the conduction properties of the transistors are set by applied d.c. voltages; in this way, several advantages follow at once, the principal ones being linearity of signal with applied voltage change; low impedance of control circuits; and complete absence of hum pick up because one does not trail base (or grid) circuits out from the main apparatus. Hundreds of feet of signal control cable can in this way be run out.

Voltage control is also convenient for a keyboard, since at no time would the voltage across any part of the system exceed about 30V. By controlling the frequency

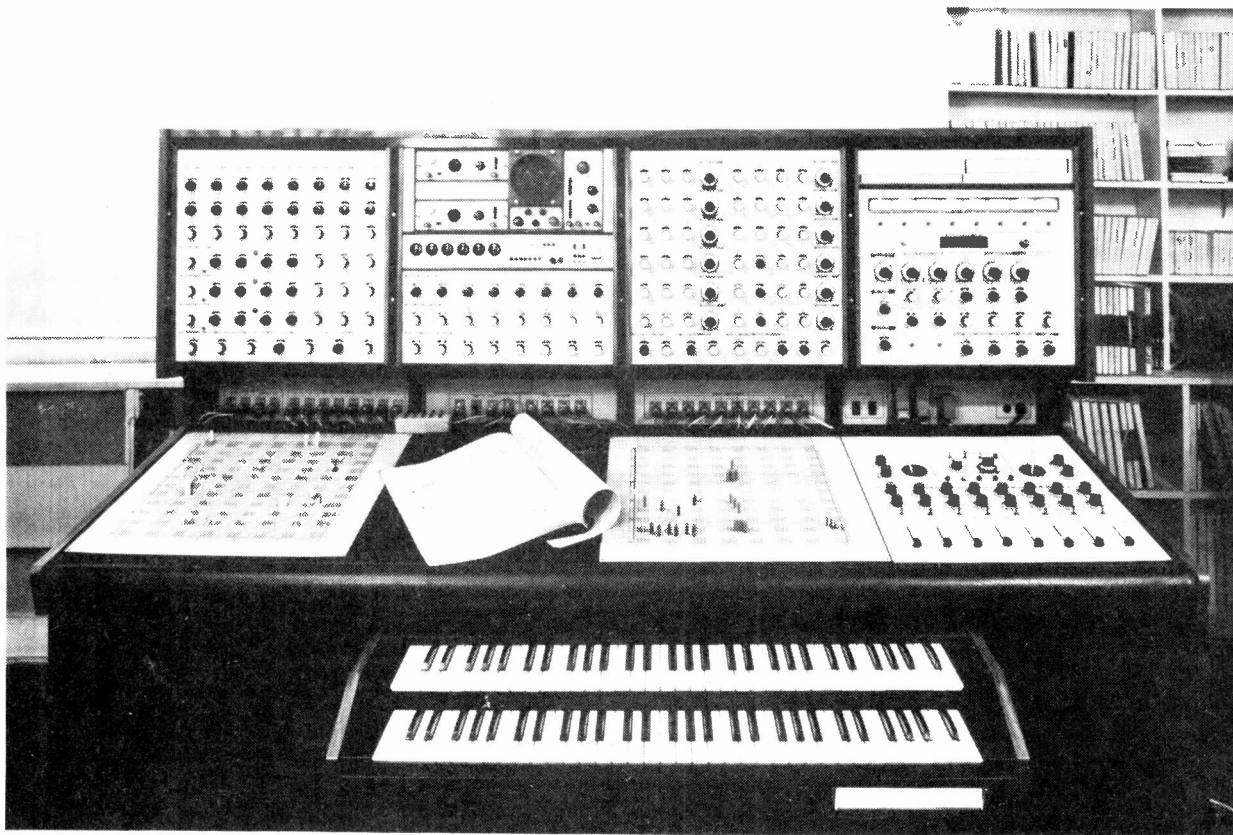The Synthi 100 synthesiser made by EMS of London has almost unlimited facilities for sound synthesis and serious composition. It has provision for storage and immediate recall of sounds devised. Compare the elaborate patch panels with that of the VCS3 synthesiser.




SAXON ENTERTAINMENTS

STANDARD and CUSTOM-BUILT AUDIO and ELECTRONIC EQUIPMENT
NEW and SECONDHAND MUSICAL INSTRUMENTS. MAIN DISTRIBUTORS
FOR A.G.K. HIGH QUALITY MICROPHONES

SA25-SA35-SA100

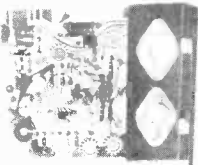LOW-PRICED AUDIO MODULES FOR
DOMESTIC and COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UN-
PARALLELED SUCCESS DURING THE FIRST FEW
MONTHS OF THEIR BEING MADE AVAILABLE TO
THE GENERAL PUBLIC. WE ARE PLEASED TO
ANNOUNCE THAT WE CAN NOW OFFER FAST
DISPATCH ON MOST OF OUR ADVERTISED ITEMS,
INCLUDING THESE THREE MODULES.

SA25 £2-95 carr. free

25 WATTS R.M.S. 7 transistors, 7 diodes.

SA35 £4-45 carr. free

35 WATTS R.M.S. 7 transistors, 7 diodes

SA100 £10-90 carr. free

100 WATTS R.M.S. 11 transistors, 6 diodes

ALL THREE MODULES HAVE OPEN AND SHORT
CIRCUIT PROTECTION, AND THE SA100 IS PROOF
AGAINST OVER-DISSIPATION AND FAULTY IN-
DUCTIVE LOADS.

ONLY ADVANCED DESIGN TECHNIQUES MAKE
THESE EXTRAORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz ± 1dB
Distortion	0.2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15mA
Noise	Better than -75dB
Supply voltage	25-45V, SA25/35 40-70V, SA100
Size	4½in × 4in × 1in (SA100) 4in × 3in × 1in (SA25, SA35)

Circuits, connecting instructions and application data
are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 and SA100 AUDIO MODULES

PS45	Stabilised module for 2 SA25's or two SA35's, £35-0, carr. free
MT45	Transformer for above, heavy duty, £2-85, carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted, £3-50, carr. 20p
PU70	Unstabilised supply for one or two SA100, £6-75, carr. 40p
PS70	Stabilised supply module for one or two SA100's, £4-90, carr. free
MT70	Transformer for PS70, £4-90, carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C.
BOARD

CALLERS AND MAIL
ORDER:
327-331 Whitehorse Rd.,
West Croydon, Surrey
CRO 2HS Tel. 01-684 6385

CALLERS ONLY:
6a Delco Rd., Rochester,
Kent. Tel. Medway 404199

BUSINESS
HOURS:
9.30 a.m. to
5.30 p.m.

TERMS OF BUSINESS: C.W.O. or
C.O.D. (35p extra). All cash in regd.
envelopes please! Telephone orders to
our CROYDON BRANCH. TRADE
AND EXPORT ENQUIRIES
INVITED

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE

Featuring a rugged class A driver stage, this module will run from all our mixers etc., and most other makes of mixer. It delivers 120W into an eight ohm load and employs 4 TO 3 can (115W) output transistors.

SPECIFICATION

Power output	120W into 8 ohms
Freq. response	30-30,000Hz ± 2dB
Input sensitivity	200mV into 10K
Construction	Fibreglass board
Size	8in × 4in × 4in (5in with supply)
Low distortion parallel push-pull output stage.	


£13-90 + 20p carr. or with
supply £18-95 + 40p carr.



SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100W. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

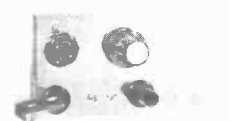Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



£8-90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3,000W (3kW) this unit is unique for its price in that not only bass middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue televite hooded cover. Fully guaranteed.

£19-75 carr. 30p

SAXON STEREO CONTROL UNIT



£15-80 carr. 30p
MONO VERSION
£6-50, carr. 20p


(As illustrated left. S.A.E. details. 9V operation)

OUTPUTS UP TO 1V RMS

Two decks, and full headphone monitoring. The unit is mains operated and measures 17½in × 3in × 4in deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, headphone selector and volume, microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCO-THEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.

COMPLETE AMPLIFIERS

THE CS 100. £34-90 carr. free

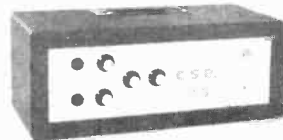

This versatile unit is now available in a black vynidie case and so represents even better value than ever, delivering speech and music powers of up to 100W R.M.S. and continuous sine wave outputs of 70W.

Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups. D.J.'s, etc.

The SAXON 100. £48-50, carr. free.



With an R.M.S. output of 120W speech and music, 100W continuous power, four individually controlled F.E.T. input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains ! ! !

12in 25W 8/15 ohms £5-95, carr. 30p. 15in 50W 8/15 ohm, £14-50, carr. 50p.

12in 40W 15,000 gauss magnet system 8/15 ohm, £11-50, carr. 40p.

A.K.G. microphones suitable for disco, group or general P.A. use

D11DHL r.r.p. £11, our price £9-45 post free.

D190C High Z r.r.p. £21-50, our price £17-45 post free.

D1000C 24 ct. gold plate r.r.p. £37, our price £32 post free.

SEND S.A.E. FOR
OUR A.K.G. PRICE
LIST. DISCOUNTS
ON ALL MICS.



ORGAN KITS

Build your own Electronic Organ, if you want the best value for your money. Yes you really save over 50% and get the best and up-to-date designs. There are four models to choose from.

- ★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, at £103-00, P/P £1-50.
- ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato built in amplifier and 50 watt 12" Goodmans speaker at £167-00, P/P £5-00.
- ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, Wah Wah, etc. at £404-00. Carr. paid on complete kit U.K. only.
- ★ Console—2 x 5 octave keyboards and 32 note pedal boards, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at £572-55 carr. paid on complete kit U.K. only.

We regret H.P. facilities are not available, but components can be bought separately. Trade and overseas enquiries welcomed. Send 25p for latest catalogue.

Please call in for demonstration. Business hours: 10 a.m. to 7 p.m. Monday to Saturday. Thursday closed.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE RD., LONDON
S.W.18 TEL: 01-870 4949

Bus numbers 37, 220, 225, 168 pass the door. Nearest stations: Wandsworth Town, East Putney, Putney, Putney Bridge.

BUILD A Voltage-Controlled SYNTHESIZER

using
Dewtron

NEW TRADE MARK

Professional Modules

These modules are as used in our synthesiser which was recently on demonstration at the British Musical Instrument Trade Fair.

For details see our PROJECT X advert. on page 982 of this issue Practical Electronics.

D.E.W. LTD.

254 Ringwood Road
Ferndown
Dorset



For all your
ELECTRONIC MUSIC
PARTS
contact

Harmonics*

(BROMLEY) LTD.

CLARION WORKS
NAPIER ROAD
BROMLEY, KENT
Tel. 01-460 2122

WILSIC SOUND EFFECTS KITS

WAH-WAH PEDAL KIT (Illustrated)



Kit comprises a SELECTIVE AMPLIFIER MODULE KIT to convert the FOOT VOLUME CONTROL PEDAL (as photo) to Wah-Wah operation. Amplifier module £1-75, pedal unit £5-13, COMPLETE KIT £6-50 add 30p for assembly of module, but please note we cannot supply kits fully built.

REVERBERATION UNIT KIT. For dimension effect. Connects between sound source, mic., etc., and amplifier. Battery powered. COMPLETE KIT £9-50 (excluding case £7-50). Assembled and tested £12-50.

VIBRATO UNIT KIT. Foot pedal unit with variable speed and depth controls. COMPLETE KIT £5-25.

SEND 15p for the WILSIC PLANS BOOK, with full details of these kits; circuits, drawings and price lists.

LATEST CATALOGUE 5p (stamps)

WILSIC ELECTRONICS LTD.
6 COPLEY ROAD, DONCASTER, YORKS.

of an oscillator by adjustment of the base voltage from a resistor chain contacted by playing keys, intervals other than those of the equally tempered scale can be produced. This is very useful for exploring the possibilities of the quarter or tenth tone scale—or other subdivisions. This is an approach to the continuous or gliding scale, available on certain instruments like the violin or trombone, but only to a very limited extent; there is no limit to electronic glissando.

Synthesisers have envelope controls; the overall shape of a waveform is called its envelope. By altering the rate at which the wave starts, or stops, or both, profound changes in the character of the sound emerge. One could thus determine, for instance, if it would be a good thing to make the attack of a 'cello longer or shorter, by simply feeding the pick up on the

'cello into the envelope shaper circuit. These methods have been used on the continent to try to improve the properties and characteristics of some instruments of the orchestra.


Then there are noise generators. Electronic noise is very controllable and can be useful to augment the impact of certain musical effects. It is also valuable to imitate storm, rain or wind and for this latter purpose can be coloured by a tone superimposed, rather like the sound of wind in telegraph wires. In short, if the synthesiser has enough parameters, almost any musical or abstract array of waveforms can be achieved and recorded; and there are commercial examples of disc records based on purely electronic sound.

Today there are many synthesisers on the market; most have similar parameter facilities, but some are much easier to patch or

cross-connect than others. As experience was gained in their use, controls became simpler and more accurate. The one time room full of gear became a table-top unit as we can see in the illustration of the EMS portable synthesiser.

The ultimate in versatility is the Synthi 100, as used by the BBC and other broadcasting authorities, and made by EMS of London. It has storage facilities and quite elaborate compositions can be realised and performed on it. There is provision to call up anything previously recorded, erase or add to it, and play it at any time. In short, it has all the facilities one could reasonably demand.

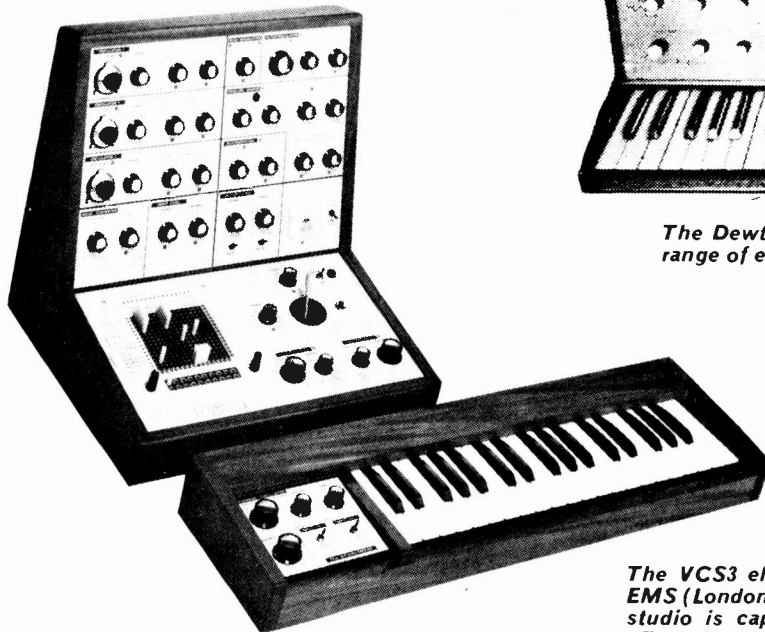Supplement cover picture by courtesy of St. Giles Music Centre.




The Dewtron synthesiser which combines a whole range of effects in a simplified unit.

The VCS3 electronic music synthesiser produced by EMS (London) Ltd. This small scale voltage controlled studio is capable of producing a great many sound effects by treatment of three oscillatory sources. Signal sources and treatments are labelled down the left-hand side of the patch board. These may be connected in any permutation to the signal input and control input listed along the top by simple jack plugs. Effects produced can then be applied to the keyboard if required.



THE HY41

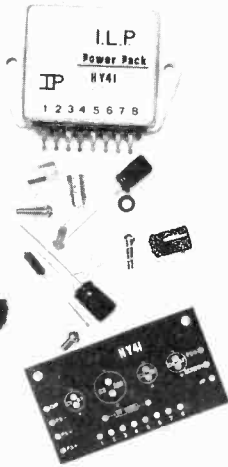

The HY41 supersedes the popular HY40 introduced by I.L.P. last year. This highly improved module achieves true High Fidelity with a dramatic reduction in distortion (typically 0.05% at 1KHz into 8 ohms!) and is electronically and mechanically compatible with the HY40.

With this important improvement the HY41 retains all of the quality characteristics found in the earlier version and P.C. board, Resistor, Capacitors, Hardware Mountings and comprehensive manual are included in the basic kit. No further components are required to construct a complete power amplifier of extremely high performance sufficiently versatile to provide power not merely for Hi-Fi but also for public address systems and industry.

The free manual gives a full circuit diagram of the HY41 and its various applications including a complete stereo amplifier.

Like its predecessor the HY41 is based on conventional and proven circuit techniques developed over recent years.

OUTPUT POWER: British Rating 40 WATTS PEAK, 20 watts

R.M.S. continuous.

LOAD IMPEDANCE: 4-16 ohms.

INPUT IMPEDANCE: 30K ohms at 1KHz.

VOLTAGE GAIN: 30db at 1KHz

TOTAL HARMONIC DISTORTION: less than 0.15% (typical 0.05%) at 1KHz.

FREQUENCY RESPONSE: 5Hz-50KHz \pm 1db.

SUPPLY VOLTAGE: + 22.5volts D.C.

SUPPLY CURRENT: 0.8 amps maximum.

PRICE: inc. comprehensive manual, P.C. board, five extra components and P. & P.—

MONO: £4.90

STEREO: £9.80

UNIQUE HYBRID PRE-AMPLIFIER

The HY5 has rapidly established a position in the WORLD as the sole hybrid pre-amplifier to contain all feedback and equalization networks within an integrated pre-amplifier circuit.

Supplied with the HY5 are two stabilizing capacitors and by the addition of volume, treble and bass potentiometers it is ready for use.

Internally the HY5 provides equalization for almost every conceivable input, the desired function is achieved by use of a multi-way switch or by direct interconnection.

Two distinctive features of the HY5 are its inbuilt stabilization circuit, allowing it to be run off any unregulated power supply from 16-25 Volts and a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo pre-amplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY41 and PSU45 forms a completely intergrated system.

INPUTS

Magnetic Pick-up (within \pm 1db RIAA curve)

2mV 47K Ω

Tape Replay (external components to suit

head), 4mV, 47K Ω

Microphone (flat) 10mV, 47K Ω

Ceramic Pick-up (equalized and compensatable) 20-2000mV, variable.

Tuner (flat) 250mV, 100K Ω

Auxiliary 1 250mV, 47K Ω

Auxiliary 2 2-20mV, 100K Ω

OUTPUTS

Main Pre-amp output 500mV.

Direct tape output 120mV.

ACTIVE TONE CONTROLS (Bexendall)

Treble + 12db.

Bass + 12db.

INTERNAL STABILIZATION


Enables the HY5 to share an unregulated supply with the Power Amplifier.

SUPPLY VOLTAGE

16-25 volts

PRICE: MONO: £3.60

STEREO: £7.20

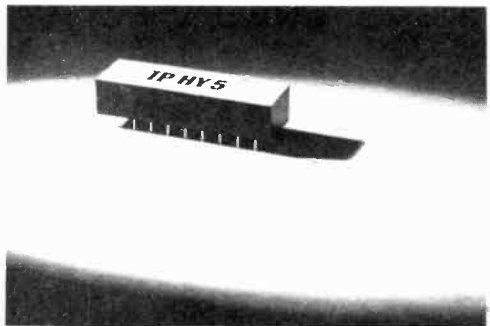

SUPPLY CURRENT

6mA approx.

OVERLOAD CAPABILITY

better than 26db on most sensitive input infinite on tuner and auxl.

OUTPUT NOISE VOLTAGE: 0.5mV.

POWER SUPPLY PSU45

The versatile P.S.U.45 is designed to supply your HY41's +HY5's in stereo or mono format.


Specification

Input: 200-240 Volts

Output: + 22.5 Volts at 2amps.

Overall Dimensions: L. 7"; D. 3.8"; H. 3.1"


PRICE: £4.50 inc. P. & P.

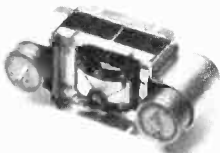

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Fig. 6. Layout of the components on the Veroboard

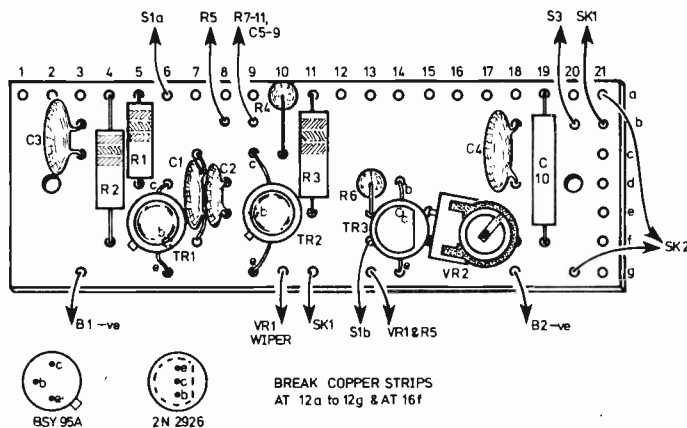

82 is read off the scale, this multiplied by 100 to give 8200, which is the value in ohms of the resistor under test.

MARKING THE SCALE

The procedure for calibrating the unit is as follows. With the unit switched to resistance, a resistor of the same value as that switched in by S2 should be connected across the test leads. The control knob of VR1 should be swung towards the high value of the scale until the bridge balances, and then the scale should be marked 100 at this point.

A resistor one tenth of the value of that switched in by S2 should then be connected across the test leads. The knob of VR1 should then be swung to the low value end of the scale until the bridge balances, and the scale marked 10 at this point.

A full range of components should then be used to fill in all the numbers of preferred values between these two points. The same procedure should be used for all five resistance ranges.

CAPACITANCE RANGES

Suitable scales for the capacitance ranges may then be marked by the same method, except the

components required to mark the ends of the scales will have to be ten times the value, and the same value as that switched in by S2.

The accuracy of the unit will depend almost entirely on the tolerance of the components used in its calibration. The only other factors affecting this, being, the stability of the components used in the bridge, and the care taken when marking the scales.

Most potentiometers have fairly large tolerances, and it is possible that this could cause the unit to be unable to cover the full ranges quoted. If this should occur, it may be corrected by reducing the value of R5 to 910 ohms, or if full coverage is still not obtained, 820 ohms.

USING THE BRIDGE

Adjustment of VR2 has to be made before the unit may be used. The range switch should be switched to resistance Range 1, and the earphone plugged in. VR1 should then be adjusted for maximum output in the earphone. VR2 is then adjusted so that the volume is fairly loud, but not excessively so.

To measure the value of a component it is merely connected to the two crocodile clips, and then the bridge switched to read resistance or capacitance as appropriate. If the component under test is wired into a circuit, one of its leads must be disconnected, to prevent other components in the circuit from affecting the reading.


If the value of the component is known, and it is merely to be checked, then the bridge should be switched to the appropriate range, and then balanced (VR1 set for minimum output in the earphone).

COMPONENTS OF UNKNOWN VALUE

If a component of an unknown value is to be measured, then the bridge should be switched to a middle range such as Range 3, and then balanced if possible.

Should the bridge balance with the pointer of VR1 on the scale, then a reading may be taken. If the bridge will not balance and it is a capacitor under test, then a lower range should be tried.

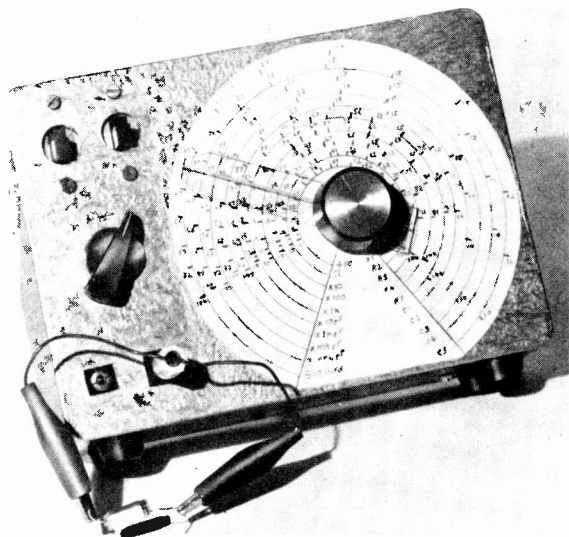Should this occur when a resistor is under test, then a higher range should be tried. If the bridge balances, but is off the scale, then either a higher range of capacitance, or a lower range of resistance is required. ★



The completed C-R Bridge showing the scale fixed to the front panel and calibrated

THE BIG INDUSTRIAL "TRANSFER" MARKET

THE past few weeks have seen a spate of activity in takeovers and mergers.

As forecast in this column in the July issue, Racal were in fact in negotiation at the time and the result was the acquisition of the communications division of S. G. Brown Ltd. from the Hawker Siddeley Group for a reported cash sum of about £1 million.

Unitech Group have acquired APT Electronics from the Bonochord Group. APT's range of

Then there was the merger of Gresham Recording Heads with Information Magnetics Corporation of California, a company little known in the U.K. but well-esteemed in the U.S.A. even though it has been in business only since 1969 manufacturing disc recording heads in competition with IBM and other U.S. giants.

All this flurry of activity (and the examples I have given are by no means all) shows a general trend towards re-grouping in the face of increasing competition and the need to decide which market sector is appropriate to the business you think you are in.

CALCULATED RISK

Advance Electronics has gone the whole hog in the competitive electronic calculator market by following up the Executive 8, announced at this year's I.E.A. exhibition, with a further five models including a pocket machine which sells at £52.50 for which Advance expect sales of at least 25,000.

It has been generally thought that the Japanese had the bulk of the world market for electronic calculators nicely sewn up. Not so. See what has happened in the United States when some of the more enterprising manufacturers decided to take the plunge in the low-price consumer field. They are choc-a-bloc with orders. So much so that they are now in trouble.

Computer Design Corporation, one of the entrepreneurs, has been complaining that the semiconductor manufacturers have let them down on the supply of the LSI MOS chips which are the heart of the machines. Computer Design has been reported as having over 4,000 machines on the shelf waiting for components. Computer Design has three suppliers of LSI memory circuits to be on the safe side but delivery dates have been seriously under-estimated, in some cases it is reported the delay is six months.

Another U.S. manufacturer of calculators is complaining not only of late delivery of circuits but also that rejects were as high as 70 per cent although the figure has now improved to 10 per cent.

Nobody has extolled the virtues of LSI more than the semiconductor manufacturers. Now they find they can't cope with the demand. The supply of LSI chips is in the hands of a very few multinational manufacturers who can dictate where available supplies should go. Such is their power that they could make or break a calculator manufacturer if they so wished.

ELECTRO-OPTICS

In our September issue I wrote that nobody has yet made a fortune out of lasers, but they could

become big business. I now record that the enterprising Munich Trade Fair Company is promoting a Laser '73 exhibition in their city next September with the forecast that this no-longer novel technology (the laser was first demonstrated in 1960 by Theodore H. Maiman in Hughes Research Laboratories) will have a civil market alone worth billions of dollars. Be that as it may, the exhibition should itself prove a profitable affair because despite its title it will cover the whole field of electro-optics which is about the fastest growing sector of electronics.

... AND MICROWAVES

If electro-optics is a booming industry so is microwaves judging from the response to the Microwave '73 international exhibition and conference scheduled to be held at Brighton next June. Stand area has just been increased by 40 per cent to cope with the demand for space. So far, nearly 80 companies from U.S.A. and Europe have booked space as exhibitors and the accompanying conference, I understand, will be heavily slanted towards applications of microwave technology rather than theory.


"FAX" MARKET OPENS UP

Facsimile transmission was first demonstrated—at least in principle—by Alexander Bain, a Scottish clockmaker, way back in 1842. Now, 130 years later it is really beginning to be big business and the high-powered companies are already moving in.

Plessey is one of the recent entrants with an American designed machine built in Japan. Plessey did a test marketing operation last year before deciding to go ahead. The operation is already swinging and Plessey expect to be selling over 5,000 a year by 1976.

Most unusual use for the Plessey "Remotecopier" was in "British Steel" during the recent single-handed transatlantic yacht race when skipper Brian Cooke had one aboard for reception of weather charts from which he was able to predict wind changes several hours ahead of his competitors. But the big market is in offices where it is being promoted as "business tool".

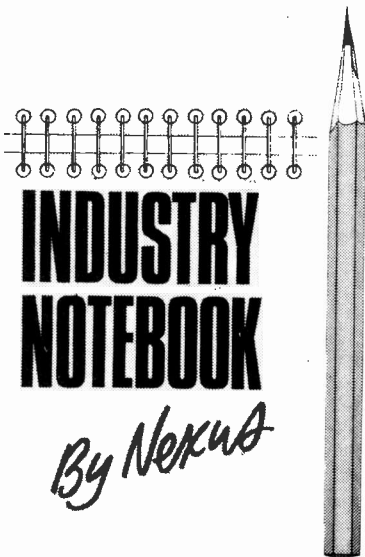But, as the market opens up, so the competition increases. There are seven major manufacturers in the field. In the U.K., latest entry is EMI who is marketing EMIfax machines through its subsidiary company SE Computer Peripherals. The machine is produced by the German company Rudolph Hell which happens to be a subsidiary of Siemens.




power supplies will now complement those already manufactured by the Unitech subsidiary, Coutant, although I understand that APT and Coutant will continue to operate as separate companies. Having hived off APT, the Bonochord Group then acquired Livingston Hire and its subsidiary companies for a sum in excess of £1 million.

RATIONALISATION

The old-established Dubilier, itself only acquired a few months ago by a consortium headed by Hambro's Bank and Slater Walker Securities, has now acquired Greenpar Engineering and Kenneth E. Beswick. Greenpar was acquired by Thorn Group not all that number of years back—was it two or three?—and Beswick, who has been in the fuse business for fifty years was a subsidiary of Tremletts.

TWO SPECIAL CONSTRUCTIONAL PROJECTS FOR THE PARTY SEASON

RALLY DRIVING GAME

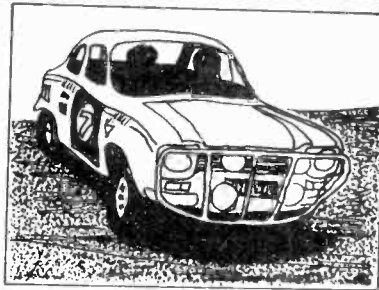

Five different "cars" participate in a competition of "driving" skill. Which driver can keep his car on the road, under optimum acceleration and braking conditions, depends on the acquired skill of simulating his driving conditions on a control panel, bearing in mind the type of car he is driving.



HOOTING OWL

Leave the hooting owl in a conspicuous place in your lounge and someone is bound to pick it up to take a closer look.


He arouses curiosity, he is a pet for the children; he just likes to sit and gaze into space. He feeds on small batteries (about twice a year when contented). But if he is frequently handled, his appetite goes up to help him hoot.

PRACTICAL

ELECTRONICS

DECEMBER ISSUE ON SALE NOVEMBER 10

PE

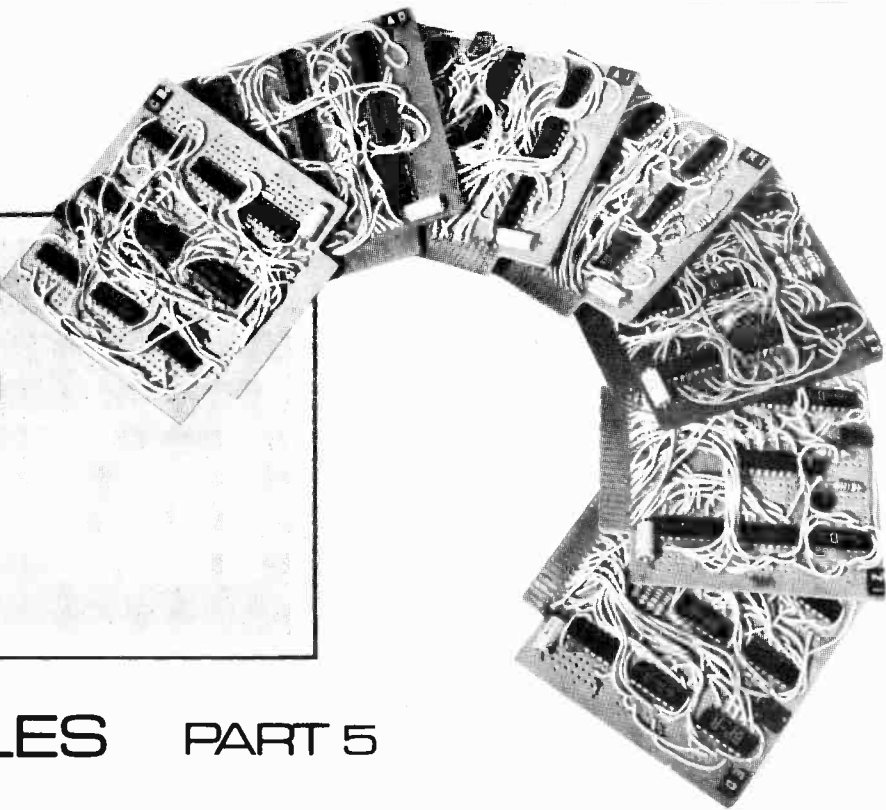

By R.W. COLES PART 5

ENTRY REGISTER LOGIC AND HARDWARE

LAST month we dealt with the construction of the keyboard logic panel which has the function of converting each key depression into suitable logic signals for entry and control of data.

As stated in the first part, entries of up to six digits can be made. The subject of this month's part is the Entry register and associated logic which has the function of storing these six entered digits in their correct order for use in calculation to come. A six digit number can also be placed in a memory for use at any number of times during the calculation.

This part also discusses the possibility of a "fixed constant" key whereby a single depression of an extra key causes a chosen number (such as π) to be entered into the entry register.

ENTRY REGISTER LOGIC

A block diagram of the ENTRY register complex is shown in Fig. 5.1, which is an expansion of the ENTRY register section of the overall arithmetic section block diagram from Part 1 (Fig. 1.3).

The operation of the ENTRY register and its associated constant store and display multiplexer is relatively straightforward, each of the possible six decimal entry figures being stored as a four-bit parallel B.C.D. code, requiring a total of 6×4 (= 24) separate storage bistables.

The 24 bistables or flip-flops are arranged as a shift register six decimal digits long and four B.C.D. digits wide, so that with each clock pulse a complete B.C.D. group (i.e. one decimal digit) is shifted into, or down, the register.

Each time a number key is pressed, the keyboard circuits (which were described last month) staticise the corresponding B.C.D. code and generate a single

clock pulse, which is used to clock the four bit code into the ENTRY register.

Pressing a second or subsequent number key causes the first group to shift down the register to the "left," its place being taken by the new entry. This process can continue until the first entered number ends up in the extreme left-hand location of the register, after which any further entries will cause that first number to be destroyed by being shifted out of the end of the register.

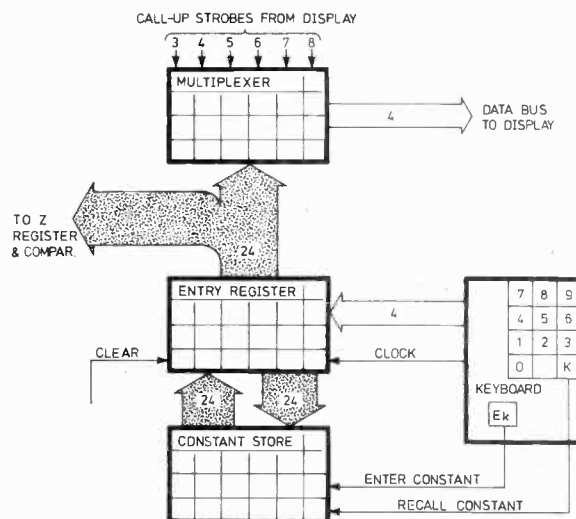


Fig. 5.1. Block diagram of the Entry Register complex showing the inputs and outputs

Note that the ENTRY register accepts the most significant digit of the complete figure entry *first*, just as we write figures ourselves. This makes the ENTRY register a "left-shift" register and distinguishes it from the other registers which normally accept the least significant digit (L.S.D.) first, and are thus termed "right-shift" registers.

CIRCUIT PARTITIONING

The ENTRY register and associated constant store and multiplexer, are built on three separate plug-in cards. The way in which the circuit is divided among the four cards is shown in Fig. 5.2., where it is immediately apparent that three of the cards are identical.

In effect partitioning the circuit in this way results in three independent shift-registers, each two decimal digits long and four B.C.D. digits wide, and each having a proportionate amount of constant storage.

In use these small units are connected in series, via the edge connector wiring, but because each card is identical they can be freely interchanged and this is a great help in tracing any faults which may occur.

The display multiplexer is built on a separate card with a 44-way edge contact instead of the 22-way type used for the other three cards, and although not shown on the block diagram, this card also houses two SN7440 buffer gate packages used to drive the CLOCK and CLEAR lines of the register.

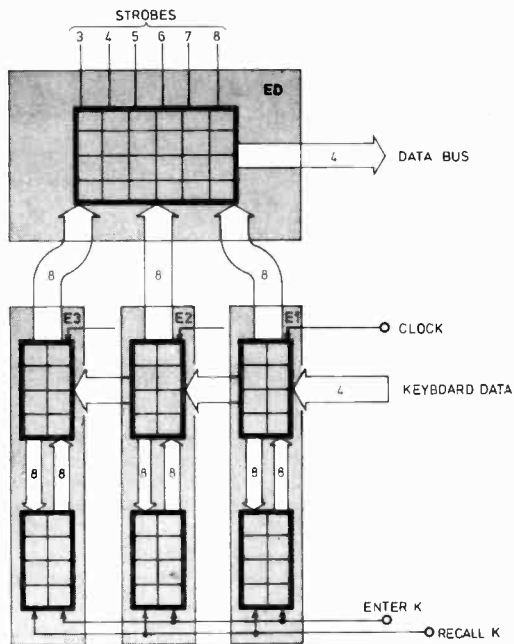


Fig. 5.2. Partitioning of the entry Register into the four boards. Boards E1, E2, E3 are identical and each contain two digits of the entry and two digits of the stored constant. Board ED contains the multiplexer

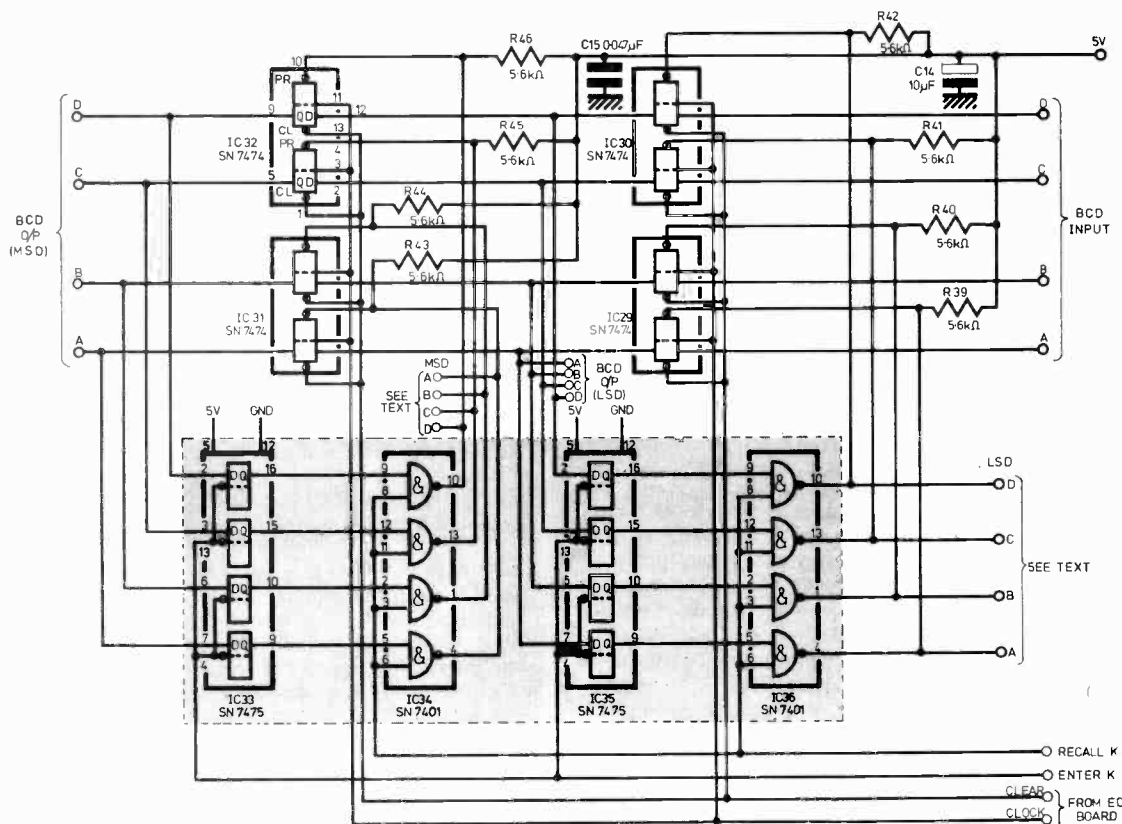


Fig. 5.3. Circuit of the Entry Register board E1. Boards E2 and E3 are identical to this. The dotted line encloses the constant store which may be omitted if not needed

REGISTER CIRCUIT

The full circuit diagram of an individual register board is shown in Fig. 5.3, three of these sections being required to form the complete register.

The circuit splits horizontally into two logical sections, the upper four i.c.s forming the shift register proper, and the lower four forming the constant store.

The components forming the constant store are enclosed in a dotted box for easy identification, and it is these i.c.s which may be left out if required, along with their associated wiring.

The eight bistables which comprise the shift register itself are SN7474 dual D-type elements, chosen because of their flexibility and low power dissipation.

Both of the two bistables in each package have independent clock, data, preset and clear inputs, together with true and inverted outputs. D-type flip-flops are more suitable than the J-K types for shift register application because they only require a single data (D) input which has the effect of reducing wire interconnections and leaving pins available for the independent preset function without recourse to the more expensive 16-pin package.

To form the register the flip-flops are connected in series pairs, there being four such pairs on each board to cater for the four separate digits (A, B, C, D) of the B.C.D. code.

Each vertical group will contain four binary digits which, taken together, represent one of the decimal numbers zero to nine.

The clock input to the register has to drive all of the flip-flop clock inputs in parallel so that after each pulse the data in a particular four bit group move one place to the left, and are themselves replaced by new data.

It is necessary to clear all the data from the ENTRY register simultaneously when required by the programme, and to this end all the CLEAR inputs are connected together to a common input, a low level, or "ground" condition on this input will set the Q outputs of all the flip-flops to zero, and the \bar{Q} outputs to one.

CLEARING OPERATION

The contents of the ENTRY register are transferred in parallel to the Z register early in the arithmetic programme, except during MULTIPLY, when they remain to be compared with the contents of the counter.

When the register contents are finished with the ENTRY register is cleared by a signal from the programme, ready for subsequent entries to be made by the operator.

Any errors made during figure entry (e.g. pressing "8" instead of "6") can be corrected by pressing the CLEAR ENTRY key which also has the effect of clearing the contents of the register ready for new data.

CONSTANT STORE

The constant store is shown beneath the ENTRY register, and is of the same 24 position capacity, so that any entry made can be stored for further use in a calculation.

This store is not essential to the correct operation of Digi-Cal and can be left out permanently or temporarily if desired, without the need for any modification to the rest of the circuit.

In operation, with the desired constant entered in the usual way into the ENTRY register, the ENTER K (EK) key is pressed, which duplicates the contents of the ENTRY register in the constant store by means of a single, parallel, 24 bit transfer.

Constants stored in this way remain available until they are either replaced by a new number or the machine is switched off, there being no requirement or provision for clearing this store, other than by entering a constant which consists of all zeros.

Constant recall is carried out by pressing the K key in the numeral section of the keyboard whereupon a reverse transfer occurs, in parallel, from the constant store to the ENTRY register. This operation does not destroy the contents of the store so that any constant can be used as many times as required in a calculation.

The constant store need not be used simply for storing constants in the accepted sense, since it will act as a memory of any result or intermediate answer if required, provided these numbers are entered through the keyboard in the usual way.

This mode of operation really acts as a substitute for pencil and paper, and can be most useful at times in long calculations.

DISPLAY MULTIPLEXER

The display board, described in Part 3, will display either entries or answers depending on a signal from the programme, entry and answer data being routed to the display via two four-line "buses."

Timing signals, in the shape of "character call-up" strobes are produced by the display board to enable the four line buses to carry all the data in their associated register to the display in a time-shared sequence, the sequence being produced in a multiplexer circuit.

There are two multiplexers in Digi-Cal, one for the eight digit answer and the other, which we are interested in here, to handle the six digit entries.

Only strobes three to eight inclusive are used by the ENTRY multiplexer, each of these allowing only one four-bit B.C.D. digit on to the bus at any instant in time, the strobe direction being from most to least significant digit (M.S.D. to L.S.D.).

CONSTANT CIRCUIT

Simpler storage elements can be used for the constant store since there is no requirement for PRESET or CLEAR inputs, and the devices chosen to fulfil this function are the SN7475 four bit latches.

Like the SN7474s these quad latches require only single "D" inputs, the data to be stored being of course the outputs from the shift register flip-flops.

Clocking is controlled by the ENTER K key, via a buffer gate mounted off the board. There is no need to "debounce" the output of this switch because of the simple "gated latch" operation of the SN7475 flip-flops and the static nature of the inputs during the entry operation.

Stored constants are returned to the shift register via the SN7474 PRESET inputs, transfer being controlled by the SN7401 quad NAND gates, which have a common input enabled by the RECALL K key, via a buffer gate. The PRESET inputs of the SN7474s are "active low," i.e. they set the Q output to "1" when an "0" input is present, and so require inverted data from the constant store. This inversion is provided by the SN7401 gates.

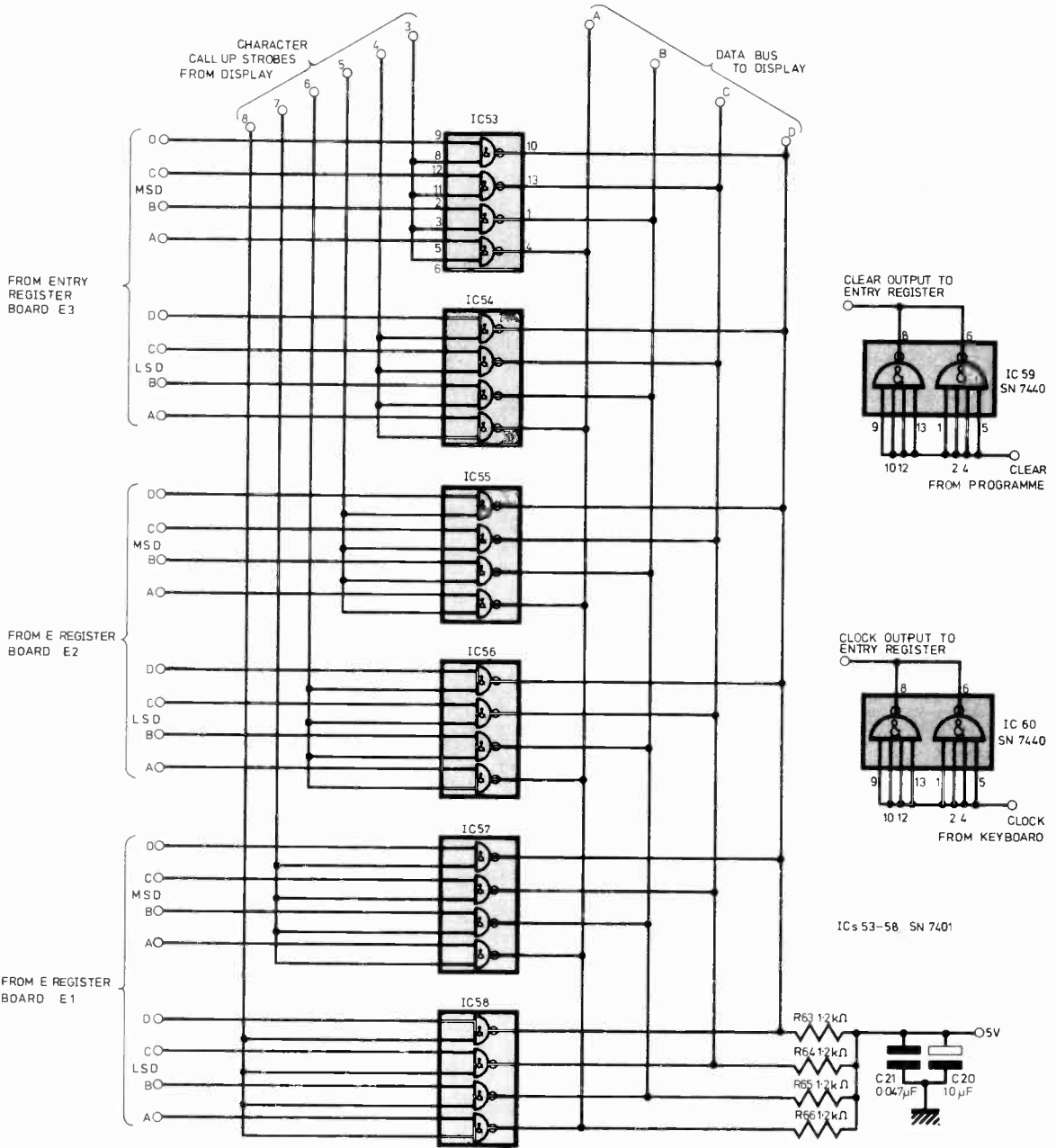


Fig. 5.4. Circuit of the Entry Register Board ED. The two SN7440 i.c.s are simply buffers and only placed on this board for convenience

MULTIPLEXER CIRCUIT

The circuit of the display multiplexer, Fig. 5.4, is quite straightforward, it being formed only from gates and resistors. Each SN7401 gate package has its four inputs wired to the corresponding four B.C.D. output pins on the appropriate register board, there being a separate gate i.c. for each decimal digit.

The common input to the four gates in each i.c. is driven by the "character call-up" strobe appropriate to that digit.

All the "A" outputs from the gate packages are wired together, as are the B, C, and D outputs, to form the four line display bus, which is referenced to the 5V line by the four 1.2 kilohm resistors.

Note that SN7401 open collector gates are essential for this circuit, SN7400 gates being unsuitable due to the fact that several gate outputs are connected directly together to provide the "Wired OR" function.

Interconnection of outputs is not permitted with the basic TTL gate because of the "active pull-up"

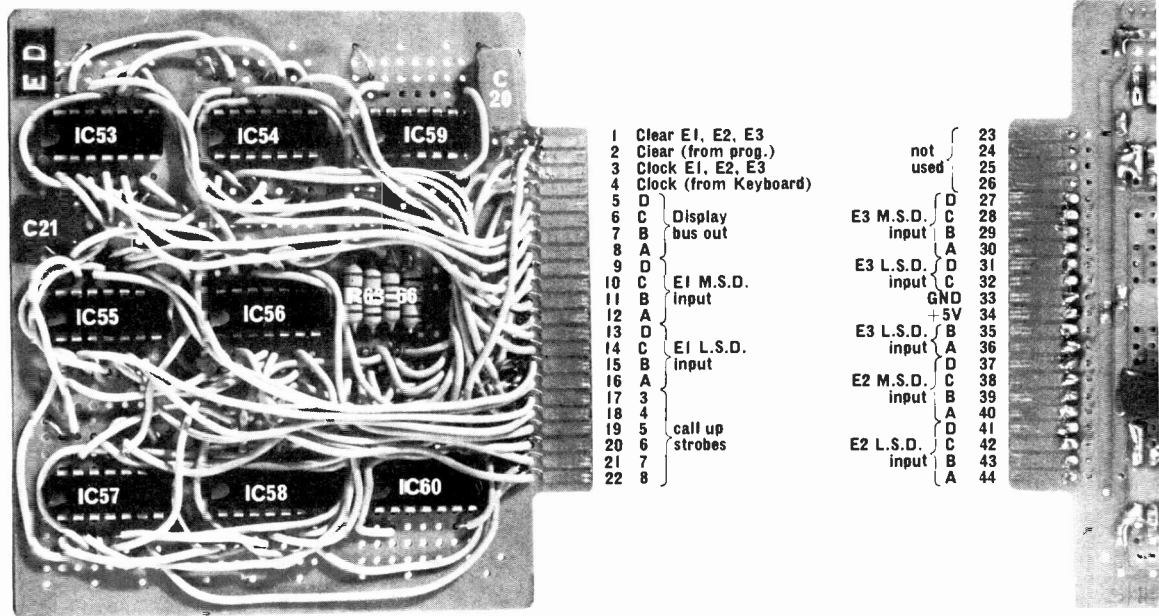


Fig. 5.5. Layouts of the components on the register board ED and functions of edge contacts


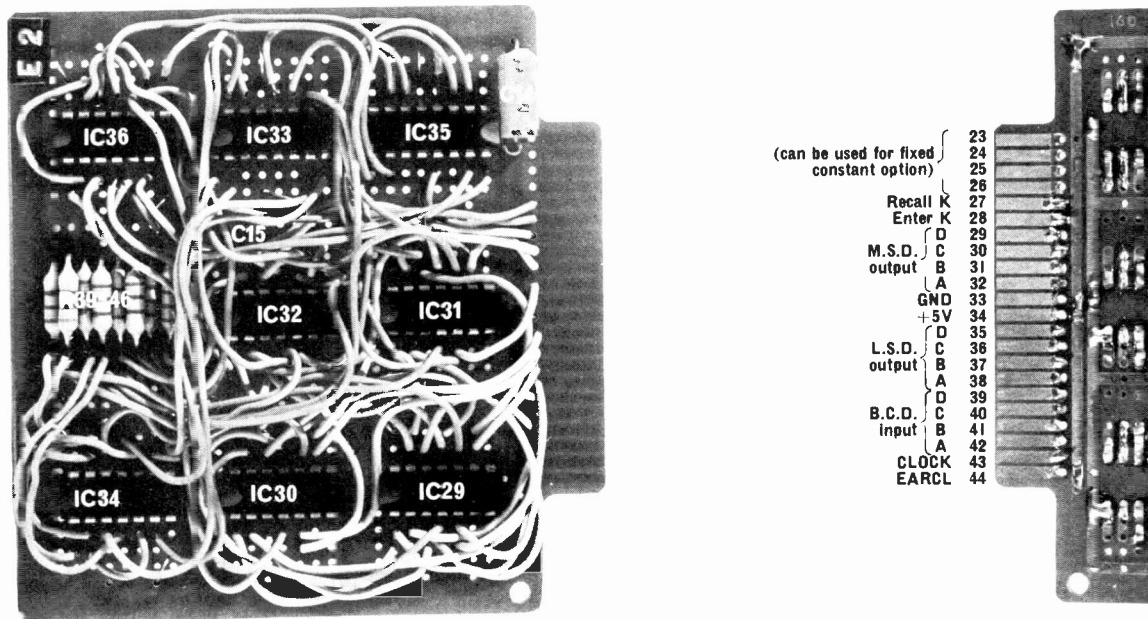


Fig. 5.6. Layout of the components on the Entry Register Boards E1, E2, and E3 and functions of edge contacts which only appear on the underside

look! electronics really mastered

...practical
...visual
...exciting!

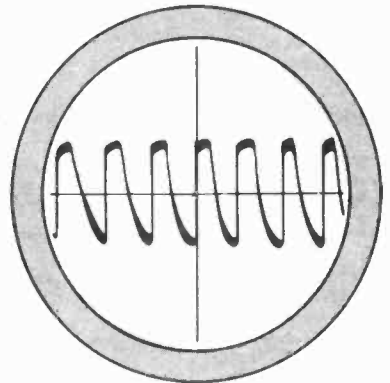no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

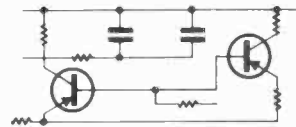2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL102

special free gift also to all our students

COMPONENTS . . .

REGISTER BOARDS E1, E2, E3

Resistors

R39-R62 5.6kΩ ±10% ¼W carbon (24 off)

Capacitors

C14, C16, C18 10µF 15V elect. (3 off)
C15, C17, C19 0.047µF (3 off)

Integrated Circuits

IC29-IC32, IC37-IC40, IC45-IC48 SN7474 (12 off)
IC33, 35, 41, 43, 49, 51 SN7475 (6 off)
IC34, 36, 42, 44, 50, 52 SN7401 (6 off)

Printed circuit boards and sockets

Type DL109/22 (3 off) (Available from Shirehall Electronics Ltd., Station Yd., Borough Gn., Sevenoaks, Kent)
SK2-4 DPK165 edge connectors (Shirehall) (3 off)

(Note that the three boards are identical, each board taking one third of each group of components shown above)

REGISTER BOARD ED

Resistors

R63-R66 1.2kΩ ±10% ¼W carbon (4 off)

Capacitors

C20 10µF 15V elect.
C21 0.047µF

Integrated Circuits

IC53-IC58 SN7401 (6 off)
IC59, IC60 SN7440 (2 off)

Printed circuit board and socket

Type DL109/44 (Shirehall)
SK1 DPK165 edge connector (Shirehall)

output stage. The SN7401 is a gate specially produced to allow "Wired or" function in TTL systems, and has no pull-up device incorporated.

The two SN7440 buffer gates are positioned on the multiplexer board but have no direct connection with the multiplexer circuit. The two buffers in each package are wired in parallel to give sufficient drive capability (or "fan-out") to handle the large load represented by the ENTRY register CLOCK and CLEAR lines (48 loads and 72 loads respectively).

CONSTRUCTION

Wiring up is carried out in the same fashion as the display board described last month, though the plug-in cards are much easier to work with because of the pre-tinned finish and the ready formed i.c. pads which obviate the need for "spot face" cuts.

By referring to the appropriate circuit diagram and the i.c. layouts shown in Fig. 5.5 and Fig. 5.6 wiring is quite straightforward, the only points to remember being the need for links from the power buses to each i.c. and from these power buses to the appropriate edge contacts, along with the need to orientate the i.c.s correctly before soldering into circuit.

All wiring up is carried out on the blank side of the boards, using single core wire.

The best order to complete the construction of the boards is as follows: ED board (display multiplexer) including the buffer gates, on a Shirehall DL109/44; then the register section (SN7474s) of boards E1, 2, 3, on Shirehall DL109/22 cards; and finally when the above sections are operating correctly, the constant store and if required, the fixed constant option, may be added.

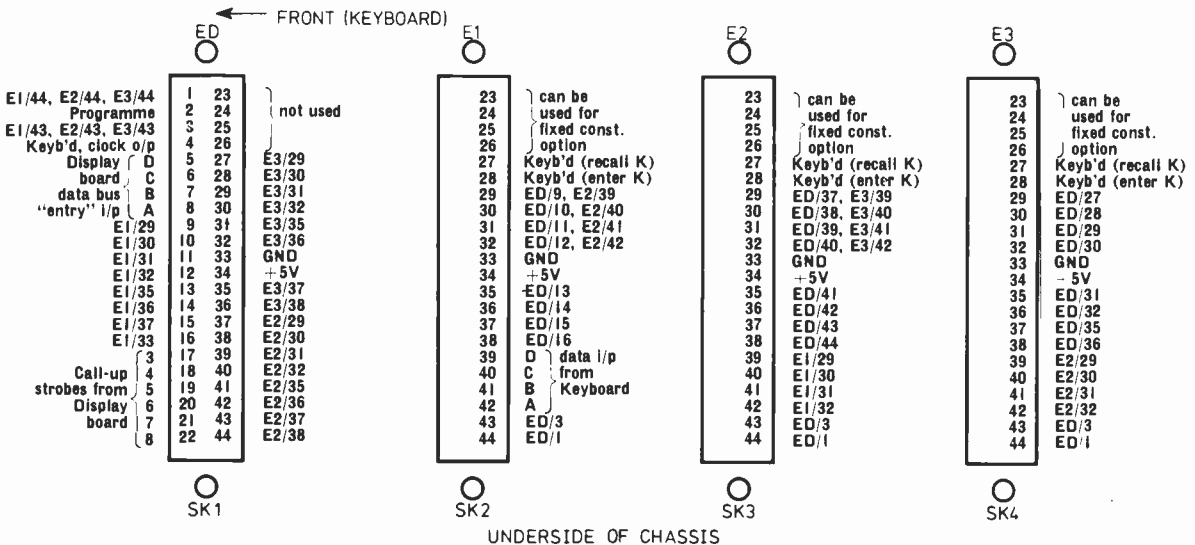


Fig. 5.7. Interwiring of the four entry register boards is carried out using the edge connectors fitted in the large hole cut in the chassis plate. The edge connectors are fitted so that the boards plug in from above. Destinations of wires are shown next to each contact (e.g. contact 30 on socket E1 should be wired to contact 10, board ED, and contact 40, board E2)

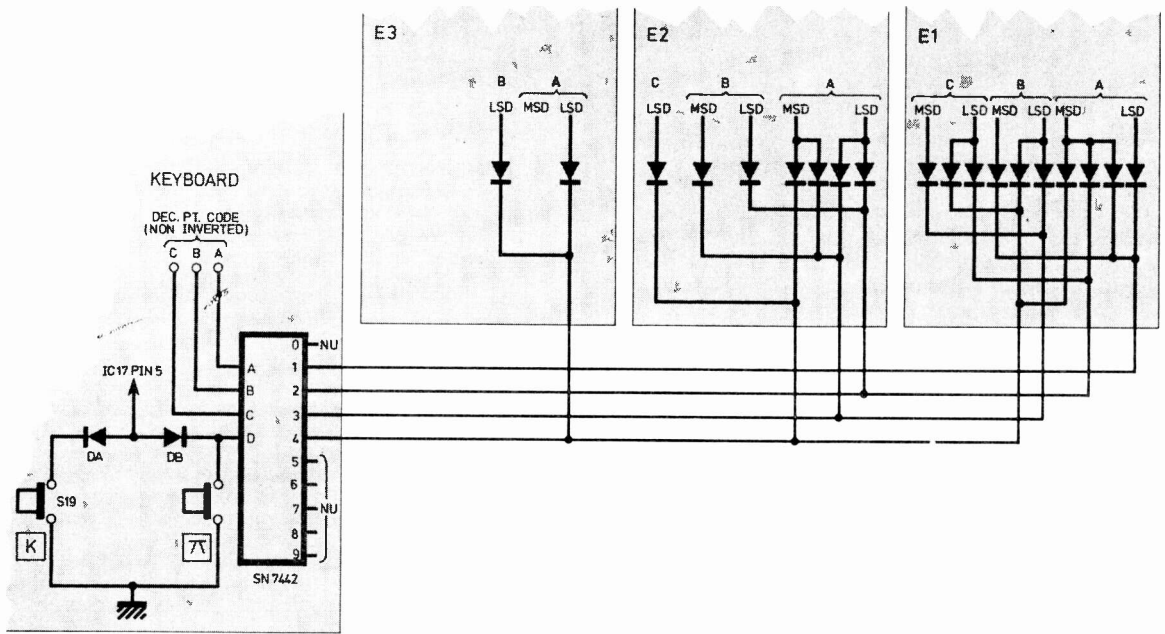


Fig. 5.8. Extra wiring to allow for a fixed constant key in addition to the K key. The diodes shown allow for the number π or a close approximation, to be placed in the entry register when a single key is depressed. The SN7442 is an extra i.c., space for which can be found on the Keyboard panel

INTERCONNECTION AND TESTING

Under chassis edge connector wiring can be started early in the construction sequence to allow operational testing to be carried out as necessary, and this task can be readily completed by referring to the edge connector layout and wiring tables (Fig. 5.7).

The tables are easier to use than wiring diagrams

their instructions being implemented by simply wiring the edge connector pin required to all (or any part as required) of the destination listed.

When the register section of one or more of the boards is completed, keyboard entries should be possible by pressing a sequence of number keys, provided of course that the display and keyboard are already functioning, and that the required CLOCK, CLEAR, and data interconnections have been made.

Table 5.1 EXAMPLE OF FIXED CONSTANT KEY DIODE PLACING

Dec. pt setting	Required " π " value	Decimal digit identification						B.C.D. digit
		Board E3		Board E2		Board E3		
		M.S.D.	L.S.D.	M.S.D.	L.S.D.	M.S.D.	L.S.D.	
1	3-1					x	x	D C B A
2	3-14				x		x	D C B A
3	3-142			x	x	x	x	D C B A
4	3-1416		x	x	x		x	D C B A

NEWS BRIEFS

The only temporary test connection required to render the circuit operational is a ground connection to the CLEAR buffer gate input to prevent a permanent CLEAR signal being produced.

FIXED CONSTANT OPTION

SN7401 open collector gates are used in the RECALL K path in preference to SN7400 gates because they can be used to perform the "Wired OR" function at their outputs. In practical terms this means that it is possible to "get at" the SN7474 PRESET inputs for use with other data sources than the constant register without altering existing logic.

This possibility opens the door to all sorts of custom modifications to enhance the usefulness of Digi-Cal, and to show how simple some improvements can be, let us consider a scheme for entering a constant which is very commonly used, without taking up space in the constant store itself.

The constant is the ubiquitous Pi (π), but in fact any constant which is likely to be often used is suitable for our purposes, the object being to have the chosen constant always available at the press of its own *separate* key, without interfering with the operation of the constant store which remains available for routine use.

This modification requires only the incorporation of a number of diodes into the ENTRY register boards and the addition of an extra "pi" key on the keyboard with a single extra i.c. The circuit for such a scheme is shown in Fig. 5.8.

An extra diode must be connected to the keyboard logic panel (Fig. 4.2), between the top of the "K" switch S19 and pin 5 on IC17, the previous direct connection being broken. This diode, marked DA in Fig. 5.8, together with diode DB forms an OR gate so that pressing either key "K" or " π " causes the automatic normalisation to be inhibited.

OPERATION OF CONSTANT FACILITY

The principle of operation is that when the "pi" key is pressed one of the outputs of the SN7442 decoder will go low, depending on the setting of the decimal point switch.

The energised output is used to PRESET a number into the ENTRY register via diodes wired in wherever a "1" is required. The diodes are connected to the PRESET inputs at the points marked in Fig. 5.3, and perform the "Wired OR" function with the SN7401 outputs.

The whole circuit acts as a diode "Read Only Memory," where the contents of the memory are programmed at the construction stage by wiring in diodes where required.

The memory contains four separate numbers to allow for the four possible decimal place selections. Table 5.1 shows how the placing of the diodes is determined, a cross marking the position of each.

This circuit can be very useful if Digi-Cal is to be used for calculations containing an often used constant, and can be substituted for the constant store or used to complement it. If this option is never likely to be taken up it would be possible to use SN7400 gates in the RECALL path instead of the SN7401s and resistors, but note that the pin connections for the SN7400s are different.

Next month: Logic and construction of A and Z registers.

New Data Transmission Technique

A NEW technique of data transmission is to be tested in a forthcoming experiment involving the Post Office and computer manufacturers and users. The system is known as "packet switching" and is basically the transmission of computer data in self-contained, addressed blocks like a series of high speed telegrams.

The user of such a system sends out the data together with the address of its destination and the data is automatically routed to that destination by the system. The need to set up a direct link between sender and receiver before transmission is thus eliminated.

Circuits connecting packet switching exchanges can be used for carrying packets sent by other customers in the time intervals between packets in a series making up a complete message. Because many signals travel on the same wire a large number of low capacity connections to a multi-access computer can be replaced by a single high capacity connection.

The system has the advantage of lower error rates than conventional systems and enables two terminals with different data transmission rates to be connected.

New Range of Calculators

A RANGE of five new electronic calculators has just been announced by the British firm Advance Electronics Ltd.

Because of large scale integration whereby all the electronics can be placed in a handful of discrete packages, assembly costs of complex instruments have been reduced drastically. The features which Advance are promoting are reliability and value for money rather than such dubious advantages as extreme miniaturisation.

The new range consists of four desk-top calculators known as the Executive 16 range and a pocket-sized calculator known as the Executive.

The Executive 16 range all feature 16 digit capability and a keyboard specially designed for high speed work. The keyboard allows a key to be pressed even when another has already been pressed providing that they are released in the correct order.

The basic model (retailing at £95) has the four basic arithmetic operations as well as a " $\%$ " key.


The 16 + 1 (at £115) has a versatile memory with full 16 digit capacity which can also function as an accumulator for automatic list totalling.

The 16 + 2 (at £145) is specially suitable for V.A.T. calculations featuring two memories.

The 16R (at £175) has all the features of the 16 + 2 but also includes a square root key.

The fifth member of the range is an eight-digit portable (at £52.50) with a plinth for desk use and mains power supply option extras.

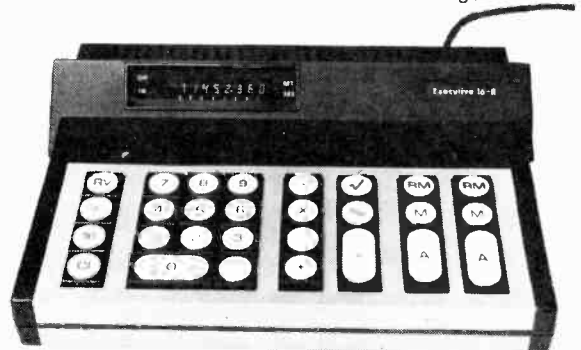Shown here is the Executive 16R which is the most versatile of the Executive 16 range



PATENTS REVIEW...

AUDIO FREQUENCY ANALYSIS

THE analysis of audio frequencies by separating a selected frequency component from a complex signal can be useful for any number of purposes. In BP 1 282 487 The Standard-Triumph Motor Company Limited describe an analysis system which they have found particularly suitable for checking the audible noise from a gear box to isolate gears which are unduly noisy.

Past practice, directed at separating the noise of the gear in question from the overall gear noise, has been to compute the main frequency of sound produced by any two gear wheels by considering their teeth number and speed. With the main frequency

component thus known it is isolated by applying a reference signal (from a tone wheel) to "beat" with the selected frequency.

A simple bridge and capacitor arrangement is used to measure the amplitude. But the snag has been poor low frequency response and confusion due to ripple in the output waveform due to the presence of rectified a.c.

In the new invention a tone wheel produces an audio frequency signal which is fed to the tone input. The noise signal to be analysed is applied to the noise input and the tone and noise signals are respectively amplified and applied to three transformers which constitute a balanced modulator.

The secondary of one transformer is applied to the primary of another via a ring modulator. The secondary of the latter is fed

to a 100Hz low-pass filter which passes the beat signal only and blocks all other residual signals (reference and noise).

The filter output is amplified, rectified and fed to a voltage comparator. Two gate drive transistors control a gate, which is opened once every half cycle, allowing a storage capacitor to sample the smoothed beat signal voltage available when the gate is open.

The criterion of the invention is the feature whereby the storage capacitor mentioned above is connected after the gate so that it can only sample the smoothed voltage available when the gate is open. Previously the storage capacitor would have been connected across the output of the rectifier and so responded to a low frequency ripple. This will of course confuse the true response.

ELECTRONIC CONTROL OF SORTING

IN BP 1 279 134 Gunson's Sortex Limited of London E3, describe a fairly simple method of detecting the difference between mixed objects to be sorted, e.g. between scrap polyethylene and scrap copper. They claim that if modified their device can also be used to sort objects made from different types of plastics material.

The basic feature is that the mixed objects falling down a chute pass through a coil (in Fig. 1) with a small number of turns. This coil is part of a tuned circuit connected into an oscillator circuit.

The output of the oscillator is used to control a sorting deflector which pneumatically deflects objects of one type.

The circuit (Fig. 2) shows the coil together with the tuning capacitors and transistor functioning as a Colpitts oscillator. The frequency produced is usually within the range 200 to 300 MHz.

When an object passes through the coil a positive going change occurs in the output signal from the oscillator. The change in output signal is amplified and fed to a magnitude detector stage. This transistor amplifies and inverts to provide a negative-going signal which can be used to drive a power amplifier for controlling the deflector mechanism.

To distinguish between different objects of similar material, the detector transistor switches according to the signal rate of change. Fig. 3 shows an arrangement whereby an "object presence" sensor makes sure that the deflector operates only when required by one object.

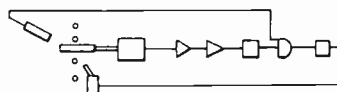


Fig. 3. Gating for one object at a time.

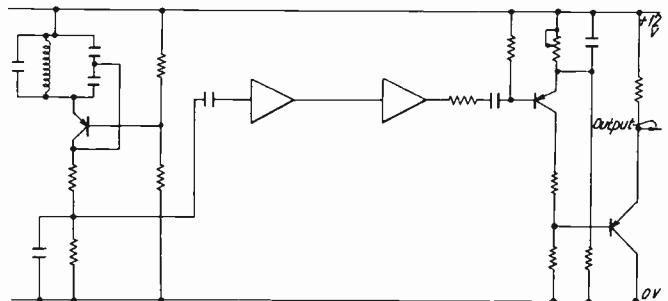


Fig. 2. Basic amplifier and switching circuit

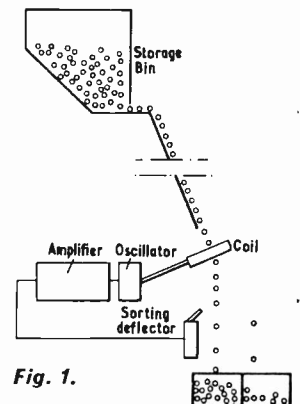


Fig. 1.

Gerry Brown ON THE FRINGE



CHARGE

Back in Queen Anne's time, the superstitious held that "air electricity" could have a profound influence on both behaviour and on general disposition. Indeed, such expressions as, "he has the wind in his tail" probably originated this long ago, since it was common practice in European courts to treat felonies with more tolerance whenever the Ides of March were blowing.

In common with many old beliefs which have subsequently become contemporary facts, air electricity is no exception. Apparently it is ions which are responsible for this effect on people. Ions are atoms (more likely, in this case, molecules) which have either lost or gained a number of electrons; those with extra electrons become negative ions, and those losing electrons, positive ions. For some obscure reason the positive ions make us feel tired and lower our capacity for work, while negative ions produce just the reverse; as when, for example, a thunderstorm has just passed.

Prior to a storm it has been noticed, though, that the air charge is predominantly positive so if the theory is right this would correlate with feeling "lifeless" and "head-achey" at such times.


Thunder and lightning aside, in spite of our technical enlightenment we probably do more to make our lives uncomfortable than the "superstitious" people of yesterday.

Consider what we wear. Nearly all our clothing is prepared from synthetic material; shirts and dresses are made from nylon, rayon, or similar fibre, while the soles of our shoes are generally fashioned from some form of man-made "leather", all of which cause us to acquire a relatively permanent high-voltage charge.

This charge is positive and, what's more, according to some researchers causes most of the fatigue and general debility experienced these days. The question is, should we drag around discharging chains in order to maintain equilibrium, or would we be better off minimising "droop" under a d.c. version of the National Grid?

FIRE WITHOUT SMOKE

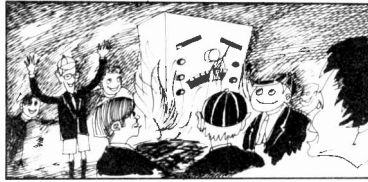Since we have had every opportunity to become fully hyper-conscious about pollution and its effects, it is staggering to think that most of us are quite uncritical of the quantity of such belched into the atmosphere during that evening



on November the 5th. This is particularly hard to bear when one considers that fireworks have advanced little, technically, for the thousand or so years since the Chinese began using them; albeit, the bangers were likely better then!

So, since this burning sense of fun remains with us to relive the next year, and generally costs more per shower of sparks than it did the year previously, a nagging feeling is left that perhaps the time has now come to rethink the Guy Fawkes night phenomenon. And who could be more fortunate than us to enjoy a relatively luxurious imagination in this respect. While there's still a little time left before this year's "big burn", and before Dad sets light to the poplars again, let's see how realistic a smokeless 5th might be.

For starters, we could do-away with the conventional Catherine wheel and substitute it for a spinning frame of lights, faded electronically in sequence from the centre, and fed via slip rings on the drive shaft. Then add a bit of novelty to roman candles by employing solenoid-released, spring-ejected, miniature mercury cell

powered micro-lamps. Or what about capacitor discharge "canon crashers" with extra large xenon flash tubes for realistic back-up?

Occasional bursts of envelope shaped white noise would not come amiss, particularly in synchronism with periodically operated, brightly lit water fountains. Realistic smoke would be produced with solid CO₂.

With a philosophy like this fireworks could be arranged to have a virtually indefinite "burning time", and would hardly ever wear out. Honestly, when you consider just how much electrical power is available for the really enthusiastic, it's a wonder someone hasn't done a back-garden Son et Lumière already!

EYE-AYE!

Sensory deprivation still remains a bit of an enigma; indeed, the discovery of every new effect has raised an even greater number of questions about its possible mechanism.


Many of the problems associated with experiments up until now could well have been attributed to the rather general nature of the experiments, and further complicated by interaction (or lack of it) between large numbers of unstimulated areas in the brain.

Although the days are not yet past when experimental volunteers need be suspended in tanks of warm water for hours at a time, there does appear to be a modest break-away toward more systematic examination by limited deprivation of inputs to individual senses.

Employing this technique, two workers at the University of Manitoba have recently discovered an effect very similar to that which occurs following actual severance of sensory nerves. For their experiment each of 15 students were asked to wear a light-blocking patch over one eye during a working day on the campus. The uncovered eye was checked periodically for sensitivity to flickering, rather than continuous light.

On aggregate, uncovered eyes were initially less sensitive, but, given several hours, subsequently began to increase in sensitivity, eventually exceeding even the normal level. In some instances students reported that this hypersensitivity lasted for days afterwards.

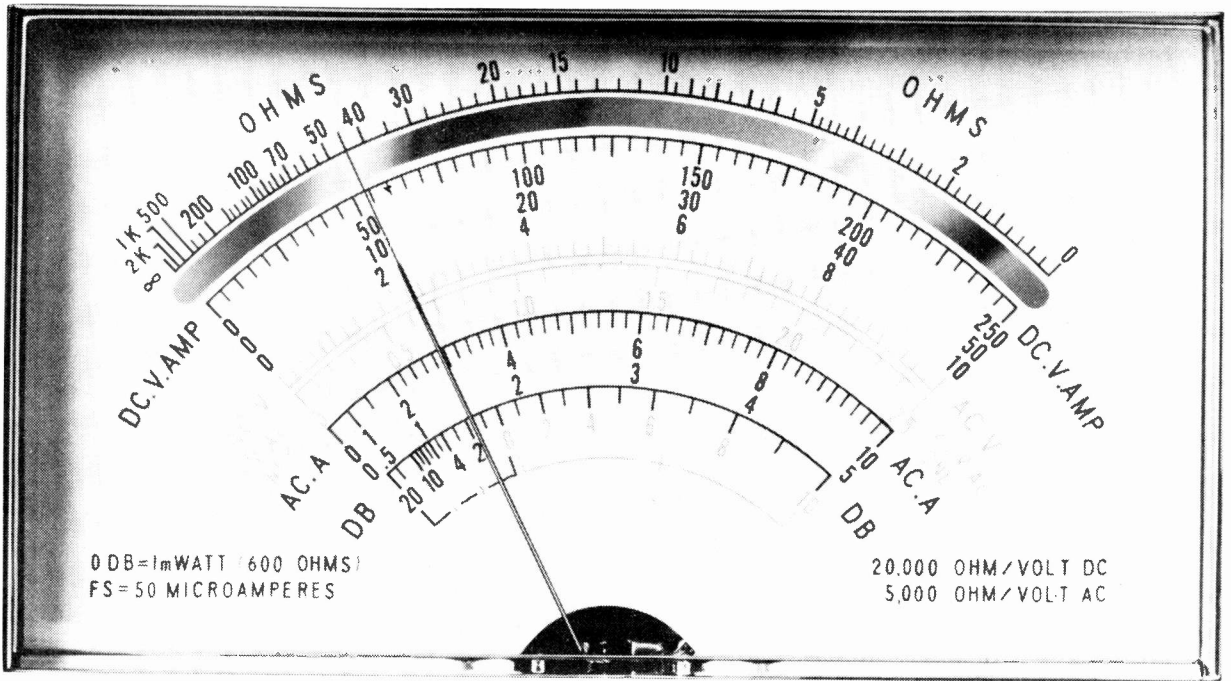These odd happenings could, by implication, be no mere trifle, especially in the context of stimulus withdrawal for any great length of time. Paradoxically, though, an additional effect was that the covered eye maintained normal sensitivity throughout the tests. Perhaps Nelson, bless his heart, really didn't see any ships after all!



You can see why we sell a lot of multimeters.

Ours are so much easier to read.

The Eagle K1400, for instance, has a big open face and a beautifully laid-out mirror scale.

Decibels and AC Voltage are picked out in red, and the others in black. Which makes it all crystal clear.

The K1400 is easier to use, too. There are two knobs: the left for functions, the right for range limits.

Again, you can't go wrong. Everything's clearly marked, including the 'Off' position which protects the meter movement against knocks and bangs.

And, of course, Eagle's exclusive overload protection circuit is built in.

All Eagle test equipment is like this. Simple to use. Reliable. Backed by a full two year guarantee.

And like H. W. Hellyer, one of the country's leading technical experts said, "Not by any means expensive: it is well worth what it costs".

If you send us the coupon, we'll send you our catalogue.

*RER - September, 1971

SPECIFICATION Ranges - K1400

D.C. Volts: 0-0.25, 1, 2.5, 10, 50, 250, 1,000 and 5,000 volts.

Input resistance: 20,000 ohms/volt.

Accuracy: better than $\pm 3\%$ full scale.

A.C. Volts: 0-5,000 volts in six ranges, steps similar to above.

Input resistance: 5,000 ohms/volt.

Accuracy: better than $\pm 4\%$ full scale.

D.C. Amps: 0-50 microamps, 1mA, 10, 100, 500mA and 10 amps.

Accuracy: better than $\pm 3\%$ full scale.

A.C. Amps: 0-10A in 4 ranges, steps as before.

Accuracy: better than $\pm 4\%$ full scale.

Resistance: 0-20M ohms in 3 ranges.

Accuracy: better than $\pm 3\%$ of scale length.


Decibel scale: -20 to +50dB.

Standard level: 0dB = 1mW, 600 ohms load.

Frequency Response: 10-100,000 Hz for 2.5V, 10V and 50V ± 0.5 dB.

Size: 6 $\frac{3}{8}$ x 8 x 3 $\frac{3}{8}$ in. **Weight:** 3 $\frac{1}{2}$ lb.

Rec. Retail Price: £28.00

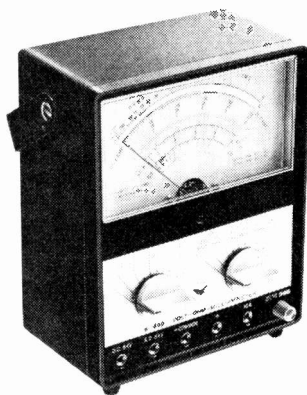

Eagle International

Eagle International Precision Centre Heather Park Drive
Wembley HA0 1SU Telephone 01-903 0144

Please send me your catalogue with full details of Eagle multimeters and other test equipment.

Name _____

Address _____

**PRACTICAL ELECTRONICS
"SCORPIO"
ELECTRONIC IGNITION
SYSTEM**




This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.

Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.

Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7 1/2 in x 4 1/2 in x 2 in. approx. Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P.

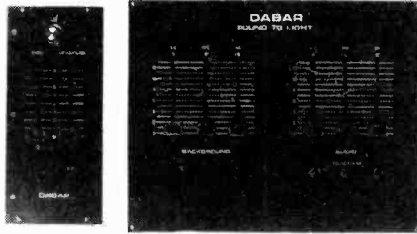DABAR LIGHTING EFFECTS
NEW! NEW! NEW! NEW! NEW! NEW!



**SINGLE CHANNEL
SOUND TO
LIGHT UNIT
STL/1**

Single channel "Sound to Light" unit with slider fader controls for audio trigger level and background load dimmer. Switchable for response to High, Mid and Low frequency audio input signals, selected by fascia control. D.J. Pulse-Flash push button fitted to fascia for manual flashing of lamp load. Neon load indicator fitted. Constructed on glassfibre printed circuit material with attractive black anodised fascia panel. Input and load connections via Cinch printed circuit connector. Maximum Load 1kW at 250V 50HZ. R.F.I. filtered. Price: £13 each post free U.K.

**THREE CHANNEL
SOUND TO
LIGHT UNIT
STL/3**

Three channel "Sound to Light" unit with slider fader controls for audio trigger level and background load dimmer. An attractive unit with independent control of High, Mid and Low frequency audio trigger levels. Slider fader background or dimmer controls on each channel. D.J. Pulse-Flash push buttons on each channel together with neon load indicators. Constructed on glassfibre printed circuit material with attractive black anodised fascia panel. Input and load connections at rear so unit is ideally suited for mounting into disco-console. Maximum Load 1.5kW per channel at 250V 50HZ. R.F.I. filters incorporated. Price: £38.50 each post free U.K.

S.A.E. All Enquiries please

Trade enquiries Welcome

**PSYCHEDELIC LIGHTING
UNIT Mk. 3**



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 carr. paid.

DABARELECTRONICPRODUCTS
98a Lichfield Street, Walsall
Staffs. WSI 1UZ
TELEPHONE: WALSALL 34365
TELEGRAMS: DABELEC Walsall Staffs.

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG
Tel.: Bristol 421196. STD Code 0272
Your West Country shop for electronic components and solid state devices

2 METRE CONVERTER KIT

9V Neg. earth feeding 28-30 MHz. Consisting of: RF BF180. Fet. mixer, crystal osc. BF180 and multiplier BF180. Complete with all components, instructions and aluminium box.

Not for beginners. £5, post paid.

2 METRE PRE-AMPLIFIER

Single F.E.T. Pre-amp. neg. earth. Gain app. 12 dB. Circuit, Instructions and Components. All you need is a tobacco tin. £1.20, post paid.

AIRCRAFT BAND CONVERTER

Circuit, Instructions and Components. All you need is a tobacco tin. £1.27, p.p.

TAPE RECORDER LEVEL METERS

500uA, size 1in x 1in x 3/4in. 55p, p.p.

LINEAR I.C.'S

uA 709 Op. amp. T05 or DIL. 42p, P. & P. 5p.

Transistor Equivalent Book

44p, post paid.

Coil Design and Construction Manual

34p, post paid.

Tested Transistor Circuits (1972)

44p, post paid.

World's Short Wave, Medium Wave, FM and TV Listing. 40p, p.p.

NUMERICATORS

GNP-7AH, similar XN3, side reading clear. Send 5p for data. With data, 75p plus 10p P. & P., 4 post free.

WE STOCK "Weco" Television Tubes. 1972 CATALOGUE, 5p, Post Free

BASIC TELEVISION

3 Vols. combined edition

£3.50. Postage 25p.

A NEW PICTURE BOOK MANUAL
IN THE COMMON CORE SERIES

PRACTICAL TRANSISTOR NOVELTY CIRCUITS, by H. Ness. 40p. Postage 5p.

ELECTRONICS EXPERIMENTERS CIRCUIT MANUAL, by General Electric. £1. Postage 10p.

DIGITAL LOGIC BASIC THEORY AND PRACTICE, by J. H. Smith. £1.50. Postage 10p.

FOUNDATIONS OF WIRELESS AND ELECTRONICS, by M. G. Scroggie. £1.80. Postage 20p.

THE MAZDA BOOK OF PAL RECEIVER SERVICING, by D. J. Seal. £3.50. Postage 20p.

TRANSISTOR POCKET BOOK, by R. G. Hibberd. £1.40. Postage 10p.

MAKING AND REPAIRING TRANSISTOR RADIOS, by W. Oliver. £1. Postage 10p.

RADIO VALVE AND TRANSISTOR DATA, by A. M. Ball. 75p. Postage 10p.

THE MODERN BOOK CO.


BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 1 p.m.

**6 WATT
STEREO AMPLIFIERS**

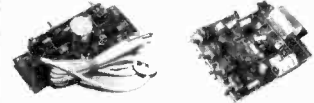

High quality amplifiers giving 3W/channel RMS. With low distortion (0.2%). The circuit is designed around the Plessey Integrated Circuit Type SL403D. There is a single and a two-tone control model each designed to accept a crystal pick up. Giving a frequency response from 50 to 15kHz with a load of 8 ohm impedance 3W/channel.

Transformers for above amplifiers	98p
Single Tone Controls	£4.95 each
Dual Tone Controls	£7.46 each

LOUDSPEAKER ENCLOSURE



Incorporating 6 x 4in Fane speaker 10,000 Gauss. Voice coil impedance 8 ohm. With 6ft of lead. Teak Vinyl covered enclosure with slotted Scandinavian type front. Size 12 1/2 x 7 1/2 x 3 1/2in. Ideal for extension speakers. Price, £3.60 each.

Plessey I.C.'s Type SL403D complete with circuit diagram. £1.25 each.

Trade enquiries invited. Post and packing 20p for speakers and amplifiers.

CIRTEC PRINTED CIRCUITS LTD
HIXON INDUSTRIAL ESTATE, HIXON
STAFFORD

SINGLE SHOT FOR OSCILLOSCOPES

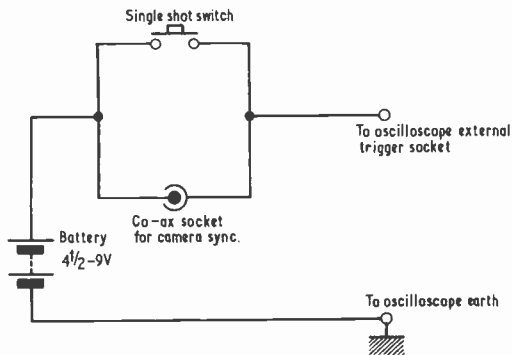


Fig. 1. Final circuit for adding a one shot facility to an oscilloscope

HAVING a double beam oscilloscope which does not have an integral single shot facility, it was felt that single shot operation would be useful in photographing traces. Inspection of the circuit diagram of the 'scope had shown that with a judicious choice in the setting of the trigger level and stability controls together with the application of external trigger pulses, a very simple system could be used to initiate single sweeps.

The external input to the trigger circuit of my 'scope (D51) can be a positive or negative going waveform of amplitude greater than three volts. The current required was small, so an old PP3 battery could be used until corrosion rendered it useless.

All that was thus required was a battery and a push on/release off switch connected in series with the external trigger socket of the 'scope.

It was realised that the switch could be replaced by the flash contacts of a camera. Use of a slow shutter speed and X (or electronic flash) synchronisation allows the trace to be recorded on film even under fairly high levels of ambient illumination.

The final circuit is shown in Fig. 1, the flash contacts being wired in parallel with the push on/release off switch to allow setting up and single shot operation without unnecessary wastage of film.

To set the equipment up, turn the trigger selector to external. Next turn the stability control from the free-run portion of its range until the trace just disappears. Turning the trigger level control from "auto" through the set level area of its range should at some point produce one trace. With the control in this position apply the external trigger pulses and optimise the settings of the stability and trigger level controls for reliable single shot triggering. The 'scope is then set up.

R. A. Shackelford,
Glasgow.

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

SENSITIVE LIGHT SWITCH

ENCLOSE a circuit diagram, Fig. 1, of a very sensitive light operated switch which may be of interest to readers.

When the light dependent resistor PCC1 is illuminated its resistance is low making the inverting input of the i.c. positive with respect to the non-inverting (the potentiometer VR1 is adjusted to ensure this) so the output will be at 0V and the transistor TR1 will be cut off. As the light level falls the l.d.r.'s resistance increases until the inverting input is more negative than the non-inverting. This causes the amplifier to saturate and the output rises to +12V, which switches on TR1 and operates the relay.

The point at which the relay operates is controlled by VR1, and is really stable as supply voltage variations have small effect because both voltages vary together (l.d.r. junction and VR1 wiper).

If the reverse operation is required (i.e. relay operates as light increases) connect the l.d.r. to 0V and resistor R1 to +12V.

R. S. Girdwood,
Norwich.

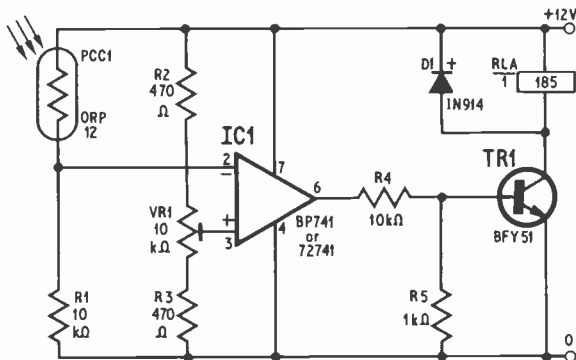


Fig. 1. Circuit diagram for a very sensitive light switch

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

True values

Sir—Messrs. Bobker, Harrison, and Barrett have a rather strange sense of values (*Readout*—Oct. 1972). They seem to have been caught by the general malaise that is creeping over many sections of society that if you cannot make something for a "profit" then its not worth bothering. They seem to have blinded themselves with the financial matters of the subject and have forgotten that your magazine is not designed with commercial interests in mind but to offer amateur enthusiasts a source of up-to-date knowledge on all aspects of electronics coupled with instructions on how to make equipment.

You cater for amateur hobby interests and the value of a hobby is beyond price if you are sufficiently interested in the subject. The price it costs to make something and learn from it is irrelevant—provided one can actually afford the expenditure. If one cannot afford the price of making something then one can still get a high degree of satisfaction out of reading and understanding, in a very practical sense, the workings of a sophisticated piece of equipment.

Digi-Cal is the first publicly issued inside story of the workings of a desk calculator and as such is a long waited for event on the amateur front; the three correspondents named above should be thankful that at last someone has gone to the trouble of designing such a piece of equipment and is also capable of explaining its workings in a clear and straightforward manner.

Your correspondents have got the wrong end of the stick. If they want something cheap then they should buy it. If they want real value for money then they should make an effort to scrape together the money to do something worthwhile. Just for a moment let's consider whether they have their commercial facts right. Let's assume they have bought their cheap commercial instrument; something goes wrong with it that is outside the guarantee. What do they do (assuming no inside information regarding *Digi-Cal*)?

Of course they have to lay out more money to get the equipment repaired. If they had dropped or crushed their pocket sized instrument it is quite likely that they will have cracked the single i.c. element. How much does this cost to replace?—probably in the order of £24 to £40 depending on the type. How much would it cost if a similar thing happened to *Digi-Cal*? Certainly a lot of time sorting out the fault—but in material costs probably not more than a few pence!

I'm afraid I do not agree with the last paragraph of your editorial. *Digi-Cal* is NOT "priced out"—if anything it is absurdly cheap. An annual subscription to P.E. costs £2.65; the electronics, mathematical knowledge, and logic experience that can be gained from a series such as this is far beyond the learning one can gain in a whole year of university work in the same field.

My interest is in the field of digital electronics, but I know very little about calculators. This hole in my knowledge is now being filled. I would like to congratulate Mr. Coles for making such an effort in designing a topical, useful and educative project, and I measure that most enthusiastic readers would agree with me.

Michael J. Hughes,
Westerham, Kent.

Raudive voices

Sir—Mr Morton (September, '72) would appear not to have read "Breakthrough" as well as he might have. I quote, "Scientific tests have shown (in a Faraday cage, for example) that these voices originate outside the experimenter and are not subject to auto-suggestion or telepathy." Also, "They are twice the speed of human speech and of a peculiar rhythm which is identical in the 72,000 examples so far examined." Would different experimenters all have the same style of modulation?

There is the possibility that the tape irregularities themselves, when

passed through a high-gain amplifier, might sound like words to anyone who expected (however unconsciously) words to be there. However it sounds unlikely, but, until we know more, it must be an open question.

Michael Fleming,
Solihull, Warwicks.

Michael Fleming raises three issues: one trivial and two worth a closer look. I will try to deal with them in turn.

First, the "tape irregularity" explanation, which is in fact a politer way of saying "imagination" or even "fraud". Can we doubt that a phenomenon so seemingly preposterous as the Raudive voices would have been examined by reputable technicians well used to the vagaries of magnetic tape? If we are going to accuse Raudive of trickery then let's do so openly—and be ready to say how it is done—without invoking explanations which don't explain.

Secondly, the two quotations Mr Fleming gives certainly do not deal a deathblow to the psychic/electronic interaction hypothesis I proposed. Admittedly we have little real knowledge of the laws behind parapsychological activity; but all the evidence says that neither telepathy nor telekinesis are electromagnetic radiation; do not obey the known principles of propagation; and cannot be blocked by any shielding. Therefore the fact that Raudive voices appear on recordings made inside a Faraday cage is quite irrelevant to the present argument.

I will not try to answer the point about the "identical peculiar rhythm" of the recordings because I believe little sense can be said without more facts to go on. But I would point out that brains are not so dissimilar in some of their manifestations as Mr Fleming suggests; for example the alpha rhythms in most normal brains are too alike for it to be possible to distinguish between them by these traces alone; and one of the important things about psychical research is that its evidence suggests all minds are linked "under the surface" in a way we don't understand. Therefore it's not too surprising if all brains react with electronic circuitry in much the same way; or at least seem to with our relatively crude equipment. In any case, if Raudive is to be believed, the voices are quite distinctive in pitch and timbre. This is not to say that because the voices are recognised, they may therefore be taken to be those of dead people: I hate to think of any of my dead relatives being forced to utter the kind of imbecilities we have immortalised in "Breakthrough". We do know from research into mediums and their activities that



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 85p. Postage 20p for first one then 10p for each one ordered.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way
3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 20p each, £1.80 for ten, your assortment.


SPARTAN Portable RADIO

£1.99 Only. Six transistor medium wave pocket loud-speaker radio. Loud and with good tone will make wonderful Christmas presents. Buy while stocks last. Full money back guarantee. Renowned for wave only, 7 transistors—£1.95.



ELECTRIC CLOCK WITH 20AMP SWITCH

These units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another time or alarm—this may be set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price, less than the value of the clock alone—post and ins. 15p.

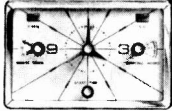

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

RESETTABLE FUSE

How long does it take you to renew a fuse? Then next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1 each or £11 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.



FLUORESCENT CONTROL KIT

Each kit comprises seven tubes—Choke, 2 tube ends, starter, holder and 2 table clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. £1. Kit B—30-40 w. £1. Kit C—80 w. £1.20. Kit E—65 w. £1.20. Kit F for 8ft. 125 w. tube £1.75. Kit MF1 is for 6in., 9in. and 12in. miniature tubes £1. Kit MF2 for 21in. 13 w. miniature tube £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23p on first kit then 18p for each kit ordered. Kit F 33p then 23p for each kit ordered. Kit MF1 18p on first kit then 15p on each two kits ordered.



DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master intercom. Simply plugs together. Originally sold at £10. Special snip price £5.50 plus 20p postage.



SOLDER GUN

A must for every busy man, gives almost instant heat also illuminated job. 100 watt £2.25 plus post and ins. 20p. BIG JOB 250 watt model £4.75 plus post and ins. 40p.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor condensers and instructions. Real snip at only 85p, plus 20p postage.


MULLARD AUDIO AMPLIFIERS. All in module form, each ready to mount complete with heat sinks and connection tags, data supplied.
Model 1153 500m watt power output 75p.
Model 1172 750m watt power output 85p.
Model EP9000 4 watt power output £1.45p.
10% discount if 10 or more ordered.

MULLARD

4 + 4

STEREO AMPLIFIER

We demonstrate these daily and almost always a sale results; it really is a cracking amplifier. Only Mullard with their know how could have made it possible at this low price. SPEC:—Mains operated, 4 watts music or speech per channel. Double wired power supply eliminates cross talk. Harmonic distortion less than 2%. Frequency response 50Hz-16KHz. Input suitable for pick-up tuner or microphone. 6 month guarantee. Only £8.95p + 30p postage and insurance.

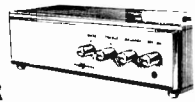


COMPUTER TAPE

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in. wide £1.00 plus 33p post and insurance, with cassette. 3/4in. wide £1.00 plus 30p post and insurance with cassette, 3/4in. wide 85p plus 25p post and insurance with cassette. Spare spools and cassettes—1in. 75p, 3/4in. 75p each plus 20p post and insurance.




TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £3.50, 3kW. Model as above except 2 kilowatts £2.50. Don't miss this. Control Switch 35p, P. & P. 40p.

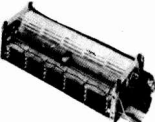

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £2.75 plus 25p post and insurance. Don't miss this terrific bargain.

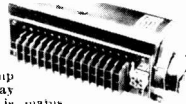

THIS MONTH'S SNIP

TIMAC 94 hour 15 amp Clock Switch. Self-contained unit for flex connection to the mains. Clock switches 2 on/off's per 24 hours. Operates a 15 amp switch. All neatly made up in an ivory moulded case with outlet socket. The only snag is that the outlet socket is the continental type. Plugs for these can be brought in this country alternatively you could fit a connector strip in place of the outlet socket. Overall size of this unit is approx. 4" x 2 1/2" x 3" and the clock has a clear perspex cover which is easily removable for reprogramming. Ideal for blanket controller, etc. Price £2.75 each.



THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95, plus 20p post and insurance.



DIGITAL COUNTER TIMER

Very stable and reliable crystal controlled circuit. Capable of work in excess of 15 MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case £39.50 or construction data and price list 50p.

MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into 8 ohms speakers. Input suitable for crystal mic, or pick-up. 9V battery operated. Size 2 1/2in long x 1 1/2in wide x 1in high. SPECIAL SNIP PRICE 60p each. 10 for £5.40, 100 for £50.



3 STAGE PERMEABILITY TUNER

Made originally for Radiomobile car radios. This is a medium wave tuner with a frequency coverage 16Kc-25Kc. Aerial, RF and oscillator sections (long wave coil available) small size, only 2 1/2" x 1 1/2". Can be used with our IF module and AF module and a few inter connection components to make a complete compact receiver. Circuit supplied. Price 85p less 10% for 10.



IMMERSION HEATERS BY REMPOY

Standard fitting for domestic water tanks, made by the famous Remploy Company. Complete with sealing washers suitable for 200-240 volts A.C. Depth into tank 1 1/2". 2 1/2 kw or 3 kw. £2 plus 40p each post and insurance.



13 AMP TWIN GANG SOCKETS

Offered at less than wholesale price your opportunity to replace those dangerous adaptors brown bakelite flush mounting—standard fitting. Unswitched 20p each, separately switched 30p each. Separately switched and with neon on/off indicators 45p each. Less 10% ten or more + 20p postage if order under £5.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

POCKET CIRCUIT TESTER

Test continuity of any low resistance circuit, house wiring, car electric. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied). 30p or 2 for 50p post paid.



AMPLIFIER IN CASE WITH SPEAKER

Marketed by British Relay under the name Luxistor. This is a very neat looking cabinet and is ideal around the home or in the workshop for trouble shooting or for testing out a quick lash up. Size approx. 9 1/2" x 6 1/2" x 3 1/2" deep. Input is via a matching transformer and volume control and amplifier may be powered by an internal 9V battery or an external 110v source. Speaker is an R-A elliptical 6" x 3 1/2" 10,000 Gauss. The amplifier proper is a Newmarket model ref. P.C.4. Price £3.50 each, 10 for £31.50. Post and insurance 20p.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and aerial rigs, etc. Price 45p each.



TELEPHONES

Complete as illustrated. Save your legs, time and temper, simply by putting in some telephones. Ex-G.P.O., not new but guaranteed in good condition and serviceable. Supplied with diagram and instructions showing how to connect. Price 75p each + 50p post or 2 for £2 post paid. Also available separately, dials and handsets 50p each + 20p post.



ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1" 6p each, 10 for 54p.



SLIDE SWITCHES

Slide Switch. 2-pole changeover panel mounting by two 6BA screws. Size approx. 1in. x 1/2in. rated 250V lamp. 6p each, 10 for 54p. 100 for £5-10. 500 for £24. Ditto as above but for printed circuit 5p each, 10 for 46p. 100 for £4-25. Sub Miniature Slide Switch, DPT 19mm (1in. approx.), between fixing centres. 18p each or 10 for £1.05.



EDUCATIONAL KITS—all with pictorial instructions

THIS BALANCE KIT FREE. Educational kits, Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 40p each post paid. Special price for all 8 kits £3 with free balance kit.

KA2 Lens Kit. Eleven parts, including candle, one concave lens, one convex lens, stage and slit frame, etc. Watch light rays bend as they pass through different lenses.
KA3 Water Pump Kit. Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily whilst working. Three types of pump may be made: Lift pump, Force Pump and Force Pump with reservoir and nozzle.
KA4 Burner Kit. Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer.
KA5 2-Pole Motor Kit. Twenty-four parts including enamel wire, armature and pole piece, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor.
SP Change over spring return 250v 1 amp 10p.
KA7 Electro-Magnet Kit. Fifteen parts, includes compass. Makes two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.
KA8 Current and Resistance Kit. Twenty-nine parts, including bench and light bulb. Conduct interesting and educational projects to learn the application of "OHMS LAW" and see the difference in current and resistance with different types and lengths of wire.
KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.
KA10 Morse Key trigger and bell kit. 25 part kit easy to construct, simple to operate.



J. BULL (ELECTRICAL) LTD.

(Dept. P.E.) 7 Park Street, Croydon CRO 1YD
Callers to 102/3 Tamworth Road, Croydon.

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.
2% ELECTROSIL TRS

Power watts	Tolerance	Range	Values available	Price 1-99	100+
↓	5%	4.7Ω-2.2MΩ	E24	1p	0-8p
↓	10%	3.3MΩ-10MΩ	E12	1p	0-8p
↓	2%	10Ω-1MΩ	E24	3.5p	3p
↓	10%	1Ω-3.9Ω	E12	1p	0-8p
↓	5%	4.7Ω-1MΩ	E12	1p	0-8p
↓	10%	1Ω-10Ω	E12	6p	5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0-1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

TRANSISTORS

AC107 15p	BC108 10p	BFY51 22p	OCF71 40p	2N3703 12p
AC126 12p	BC109 10p	BFY52 22p	ORP12 50p	2N3704 13p
AC127 12p	BC147 10p	BSY 56 32p	2N2369 16p	2N3705 12p
AC128 12p	BC148 13p	OC26 45p	2N2646 60p	2N3706 11p
AC131 12p	BC149 13p	OC28 45p	2N2926R 9p	2N3707 12p
AC132 12p	BC157 13p	OC35 45p	2N2926O 9p	2N3708 10p
AD140 50p	BC158 13p	OC42 12p	2N2926V 9p	2N3709 11p
AD161 33p	BC159 13p	OC44 12p	2N2926G	2N3710 11p
AD162 36p	BD131 75p	OC45 12p		2N3711 11p
AF114 20p	BD132 75p	OC70 12p	2N3054 58p	2N4062 12p
AF115 20p	BF179 32p	OC71 12p	2N3055 60p	ZTX302 15p
AF116 20p	BF181 25p	OC72 12p	2N3442	ZTX500 16p
AF117 20p	BF194 15p	OC81 12p	2N3472	ZTX503 16p
AF118 38p	BF195 13p	OC82 12p	2N3702 13p	40362 58p
BC107 10p	BFY50 22p			

ZENER DIODES

400mW 5% 3.3V to 30V, 15p. DIL Socket 14 and 16 pin. 16p

LINEAR I.C.'s (D.I.L.)
709 50p 741, 50p
710 50p 748, 50p

DIODES

DIODES RECTIFIER			SIGNAL	
BY127 1250V	1A	12p	OA85	7p
BZV10 800V	6A	25p	OA90	5p
BZY13 200V	6A	20p	OA91	5p
IN4001 50V	1A	7p	OA202	7p
IN4004 400V	1A	8p	IN4148	5p
IN4007 1000V	1A	12p	BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2in = 10p; 9in x 2in = 7p.

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of crack 59mm
SINGLE 10kΩ, 25kΩ, 50kΩ, 100kΩ, log or lin
DUAL GANG 10kΩ + 10kΩ, etc, log or lin
Knob for above
FRONT PANEL
20 gauge panel 12in x 4in with slots cut for use with slider pots.
Grey or matt black finish, complete with fixings for 4 pots.

40p
60p
12p
65p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V P.C. mounting: 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 7p. 0.33μF, 11p. 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF 3 1/2p. 0.15μF 4 1/2p. 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7 1/2p. 0.68μF, 11p. 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 4p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 8 1/2p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF, 20p. 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 2p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

100/40, 160/25, 40/2.5, 80/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6/4, 6/4, 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1-6/25, 6-4/25, 12.5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.64/64, 2.5/64, 5/64, 10/64, 20/64, 32/64.

MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6.4, 800/4, 1000/2.5, 9p. 100/64, 160/40, 250/25, 400/16, 640/10, 1250/4, 1000/6.4, 1600/2.5, 12p. 160/64, 250/40, 400/2.5, 640/16, 2000/4, 1000/10, 1600/6.4, 2500/2.5, 15p. 250/64, 400/40, 640/25, 3200/4, 1000/16, 1600/10, 2500/6.4, 4000/2.5, 18p.

ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25. 5p each.

VEROBOARD

0-1	0-15		
2 1/2 x 3 1/2	22p	16p	
2 1/2 x 5	24p	24p	
3 1/2 x 5	24p	24p	
3 1/2 x 5	27p	27p	
1 1/2 x 2 1/2	75p	57 1/2p	
17 x 3 1/2	100p	78p	
17 x 5 (plain)	—	82p	
17 x 3 1/2 (plain)	—	60p	
17 x 2 1/2 (plain)	—	42p	
2 1/2 x 5 (plain)	—	12p	
2 1/2 x 3 1/2 (plain)	—	11p	
Pin insertion tool	52p	52p	
Spot face cutter	42p	42p	
Pkt. 50 pins	20p	20p	

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
		3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable 22p/metre.

BATTERY ELIMINATOR

£1.90
9V mains power supply. Same size as PP9 battery.

THERMISTORS

VA10555 15p; VA10665 15p; VA1077 15p; R53 £1.35.

COMPACT CASSETTES—IN PLASTIC LIBRARY BOX

C90 65p C120 85p.

LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	3200μF 16V	50p
2500μF 40V	74p	4500μF 16V	50p
2500μF 50V	58p	4500μF 25V	£1.68
2500μF 64V	80p	5000μF 50V	£1.10
2800μF 100V	£3.00		

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p	0.047μF 13p	0.22μF 20p
0.022μF 12p	0.1μF 13p	0.47μF 22p

POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values 4p each.

SOKSOL DE-SOLDER KIT: Here is a kit that is a must for every service engineer and electronic project constructor. You make it up to your own exacting requirements. It desolders transistors, I.C.s, those wrap-round solder joints on switches, potentiometers, transformers, etc., etc. Simple to use—you just drop special brand in the supplied chemical solution, pull out and allow to dry. When ready to use just simply place braid on device to be desoldered, apply soldering iron to braid and the rest is sheer magic as all solder is soaked up in seconds. The kit includes 20ft. of special braid, chemical solution and full instructions, £1, post 15p. Money back guarantee if dissatisfied.

Bargain component parcels include resistors, silver mica, polystyrene and electrolytic capacitors. Valve holders, rotary switches, transistor panels plus a generous selection of other components. Guaranteed to be the best mixed parcel on offer or your money back. 4 lb. nett weight, £1, post 40p.

Assorted computer panels contain I.C.s, thyristors, transistors, diodes, trim pots, etc., etc. Don't miss this bargain, 5 assorted panels, £1, post 20p.

Assorted silver mica, polystyrene and ceramic capacitors, extra good selection, 100 for 50p, post 10p.

ELEKON ENTERPRISES

224A ST. PAUL'S ROAD, Highbury Corner
LONDON, N.1

FERRANTI

SEMICONDUCTORS ... COMPARE OUR PRICES

Transistors	ZTX320	28p	BFS61	19p	ZS176	21p	
ZTX107	10p	ZTX330	13p	BFS96	16p	ZS178	34p
ZTX108	9p	ZTX331	14p	BFS97	21p	ZS200	17p
ZTX109	10p	ZTX500	10p	BFS98	21p	ZS271	14p
ZTX114	20p	ZTX502	15p			ZS272	17p
ZTX300	10p	ZTX504	39p	DIODES		ZS274	17p
ZTX302	15p	ZTX510	15p	ZS140	22p	ZS276	23p
ZTX304	19p	ZTX530	19p	ZS141	39p	ZS278	33p
ZTX310	7p	ZTX531	20p	ZS142	30p		
ZTX311	9p	ZTX550	15p	ZS170	9p	P.E. PIANO	
ZTX312	9p	BFS59	15p	ZS171	11p	Special Offer	
ZTX313	10p	BFS60	19p	ZS172	14p	Send S.A.E.	
ZTX314	11p	BFS61	19p	ZS174	15p	for Price List	

Postage and Packing 10p. Free above £2. S.A.E. for full list

VALENCIA ELECTRONICS

134 UNION STREET, ASHTON-U-LYNE, LANCs.

Readout —

A SELECTION FROM OUR POSTBAG

the subconscious mind is capable of generating all kinds of personas (synthetic personalities) to give substance to its longings, hopes, hatreds, etc. That these figments should then escape into the "mental ether" and come to react with electronic equipment I find quite plausible, especially when supported by other experimental evidence.

And there is experimental evidence. If any readers are ready to jib at the notion of mere thoughts directly affecting electronic circuitry I would direct them to the work of Helmut Schmidt, a physicist of international repute. He has devised an apparatus on which trained subjects can both predict and control random events at the sub-atomic level (the decay of Strontium-90 nuclei) at a high level of probability by willing alone. There is a good summary of his work in Arthur Koestler's "The Roots of Coincidence", 1972.

— Peter R. Morton

Amongst the white noise

Sir—After reading Mr Peter Moreton's letter in the September edition of P.E. on "Psi-Tronics". I wondered if your readers would be interested in similar experiences of my own?

I have a temperamental (!) v.h.f. receiver which I use in a radiotelescope aerial system, and during tuning up of this receiver and its associated preamp to the required band, it was left switched on for long periods producing nothing but what has become to be known as "white noise". The preamp being very difficult to align, I was often switching the signal generator off and on, making adjustments, and trying again. On many occasions, during range testing of my aerial, I am sure I heard the signal generator whilst it was switched off, i.e. all the radio was receiving was the usual v.h.f. spurious noise. This happened so frequently that I had to keep checking that the signal generator was switched off, before I tried to properly "tune in" this figment of my imagination!

I put it to Mr Brown and Mr Morton that the mind has some mechanism whereby it hears amongst the white noise what it wants or expects to hear, and that

this explains the phenomena, since in my case, the familiar note of my signal generator is unmistakable, and I certainly was fully conscious of the fact I was hearing something that *couldn't* be there!

I must confess to being still sceptical about such things as the "Raudive Voices", but when it happens to you personally, it's something quite different!

L. M. Newell,
Woodbridge, Suffolk.

Road choir !

Sir—In connection with the recent interest shown in "Raudive voices" I should like to give an example of my own subjective interpretation of white noise.

Some years ago, while riding on the cab of a noisy long-distance lorry I was enveloped by the sound of the engine, the sound of other cars on the road and the various vibrations and rattles from parts of the lorry, i.e. a broad band frequency spectrum somewhat resembling white noise. I hummed a pop tune to myself and to my surprise I heard the pop song coming from somewhere inside the cab sung, as it seemed to me, by a choir of out-of-tune voices. There was no radio in the cab and it seems that the voices were a purely subjective interpretation of the random noise spectrum reaching my ears. With practice it was possible to hear the voices "sing" any tune at will, there being a period of some seconds between conceiving a tune and actually "hearing" it. Since that time I have met one or two people who have had the same experience. The moral seems to be that if it is possible for some people to hear pop songs in white noise, then it is equally possible for others to hear voices from the dead if they so wish.

An explanation may be as follows. When a memory comes to mind the brain cells that correspond to the sensual experience of that memory become active. If (when the memory is of a noise) the ears perceive white noise simultaneously, then the same mechanism that allows concentration on one conversation when several may be going on will come into effect, only allowing the memory of the noise to come into consciousness. This memory will, however, appear to come directly from the senses since the white noise components corresponding to the noise will be allowed to pass by the brain's "filters".

It may be interesting for psychologists to carry out experiments

in this area, and perhaps with other senses. (Is there any capacity to project visual images when in an environment of completely white light for example) perhaps even ending up with "White taste" and "White smell".

I would, of course, be interested to hear other people's interpretations and experiences in this area.

K. Willson, B.Sc.,
London S.W.16.

Unconvinced

Sir—I was interested to read in the September issue that the phenomenon of "Raudive Voices" had cropped up again under the general heading of Psitronics. The hypothesis on the origin of this phenomenon suggested by your correspondent, Peter Morton, is most ingenious but is open to criticism on one simple count.

It is now generally recognised that the operation of the brain is related to a measurable form of electrical activity. Thus it is reasonable to assume that telepathic communication is, ipso facto, electrical in origin also. If this assumption is accepted as being substantially correct it becomes increasingly difficult to explain the positive results from experiments into the phenomenon which were conducted with the recording apparatus sealed within a Faraday Cage.

If we accept that the phenomenon exists, and there appears to be plenty of evidence that it does, then it seems that we must resort to the explanation tendered by one of Raudive's original witnesses—"that it transcended the known laws of Physics". All of which leaves a wide open field for future experimenters.

Having read "Breakthrough" shortly after its publication a friend and I decided to carry out a number of experiments to prove the existence of the phenomenon for ourselves. My colleague in this, besides being a highly qualified electronics engineer, has had a genuine "feel" for what might be termed supernatural phenomena all his life, and thus felt that everything was on our side.

We built two forms of each type of detector described in the book and combined these, in turn, with six types/models of tape recorder. In addition we tried the microphone and radio methods of recording, but after many hours and several miles of tape had recorded only one voice which could not be directly attributable to spurious "E" propagation or something similar. Our prize voice resisted all attempts of filtration and re-amplification to

Readout—

A SELECTION FROM OUR POSTBAG

become intelligible so we decided to retire unconvincd.

I too would be interested to learn of the experiences of others in this field.

Douglas Shaw,
Eaton Socon, Hunts.

Authoritative opinion appears to be opposed to the view that telepathy is a form of electromagnetic radiation. Dr Grey Walter in his book, "The Living Brain" (1961) states: "if we consider the largest rhythms of the brain as casual radio signals, we can calculate that they would fall below noise level within a few millimetres from the surface of the head".

There is evidently much general interest in this topic. Many readers have written describing their own experiences and experiments, but no one has reported a success in recording "Raudive voices".

Retort from Australia

Sir—I read with great interest the article *Report from Australia* and I am sure that the article was written with the best of intentions in the world. However, the Australians in general tend to gloss over many things, and literally hate comparisons when it comes down to earth, i.e. hard cash! This particularly so in the radio field.

I go green with envy when I read the cost of components, transistors and integrated circuits in the U.K. and I compare them with those available here. For example,

take the BC108 listed in P.E. at 10p or 20 cents Australian, the BC108 here is 45 cents and on top of that there is up to 27% sales tax, depending on the State in which you live. This tax is very crippling when you come to build any of the available projects. So my advice to any intending migrant is to do two things: forget most of what the brochures from Australia House tell you, and if you still intend to come, take things as they are and you'll make out. The second thing is to bring out as much gear as you possibly can.

This is a mighty big country, so its a little unfair to classify most radio sets as made for local station reception. There are areas (fewer now than they used to be) of poor reception in the U.K. Well England from top to bottom is approx. 560 miles. Folks here often drive this distance, and more, just to visit friends at a weekend. It has to be a really good quality radio set to pull in inter-state radio stations during the day. At night of course it's not so bad. In the more thickly populated areas this situation may not arise as transmitters are closer together, but it is certainly true of South Australia.

It's all very well to say that Australia is as technically advanced as its contemporaries, but I have found that when dealing with i.c.'s the manufacturers' applications notes are so technical that they are for boffins only—and I include all American manufacturers — so I am indebted to your magazine for *Making The Most Of Logic* and subsequent articles on i.c.'s and most important the way these articles have been presented.

Talking of f.m. I bought a German radiogram in Singapore in 1959. I arrived in this country in 1966. F.M. was, as it is now, being

talked about but I'll believe it when I see it! I am told they had a few f.m. stations in the Sydney area of N.S.W., but they died through lack of interest as far back as 1966.

Well, this letter was prompted for two reasons, my personal dislike of half truths, and the fact that I'm in the radio field and I did migrate to Australia. So if this does anything to put the record straight I'll be happy.

P. Hickman,
Greenacres, South Australia.

Musician's ambition

Sir—As another of your younger readers I fully agree with Neville Powell's letter in your September issue. It would be nice to see designs for transistorised sound effects apart from the more common tremolo and fuzz, etc. These things are fairly easy for the average constructor to design whereas more complicated effects such as echo, reverb, and waa-waa are harder to design and build.

It is every musician's ambition (I am no exception!) to own a synthesiser, but the prices of commercially made instruments are out of this world! I am sure it would be possible to make a synthesiser using cheap and easily obtained i.c.'s.

Hoping to see something of this kind in the future issues of PRACTICAL ELECTRONICS.

Andrew Copesey,
Gildersome, Nr. Leeds.

You will! The P.E. Synthesiser will be on display at the Audio Fair, Olympia, London, October 24-28.

All of the sound effects mentioned in your first paragraph have been covered as constructional projects in past issues of this magazine.

BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

Any Back Numbers

Mr. E. N. Elia, P.O. Box 297,
Baghdad, Iraq.

December 1968

Mr. D. W. Jones, Hefindre,
Llangefni, Anglesey.

March, April, June 1972

Mr. G. A. Herd, 4, Graig Lwyd,
Radyr, Cardiff.

October 1971

Mr. T. Svenell, Östra Farmvägen
40B, S-21441 Malmö, Sweden.

February 1969

Mr. G. Paine, 21, Estridge Way,
Tonbridge, Kent.

March 1966

Mr. B. L. Codd, 46, Woodrows,
Woodside, Telford, Shropshire.

April 1970

Mr. M. Dowding, 89, Beresford
Road, Lowestoft, Suffolk.

February 1971

Mr. B. Whiting, Fellands Gate,
Old Leake, Boston, Lincs.

November 1964 to March 1965; October to December 1970, February and March 1972

Mr. P. U. Sukhadia, 1-16,
Shantinath Bhuvan, 427, Sion
Road, Matunga, C.Rly. Bombay-
19, India.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

May 1969 to March 1970

Mr. V. T. Brown, 242, Little
Waking Road, Woking,
Southend SS3 0JN.

March 1968, January 1971,

April 1971, June and July 1972
Urs Bachofner, Wulfingerstrasse
92, CH-8400 Winterthur,
Switzerland.

August 1969

Mr. M. Latter, 45, Wortley Road,
W. Croydon, Surrey.

April-May 1972

Mr. G. Slack, 87, Upham Road,
Swindon, Wiltshire.

ATTRACTIVE DISCOUNTS

ON VERY MANY ITEMS WHEN YOU BUY FROM US

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS

Wide range. Up to date. Brand new — no 'seconds' or surplus. Highest quality and reliability.

	5p		5p
IN4148	0-04	AF139	0-38
IN5309	0-24	AF239	0-36
2N2848	0-37	BC107	0-13
2N3055	0-65	BC108	0-12
2N3702	0-10	BC109	0-14
2N3703	0-10	BC177	0-09
2N3704	0-10	BC177	0-11
2N3819	0-25	BC184L	0-11
2N4286	0-15	BC212L	0-14
2N4289	0-15	BD130	0-65
2N4443	0-88	BD131	0-77
2N5062	0-42	BD132	0-81
2N5088	0-46	BD135	0-25
2N5192	0-77	BD136	0-27
2N5195	0-90	BDY20	0-97
2N5457	0-30	BFY51	0-20
40361	0-45	BRV39	0-30
40362	0-45	BY164	0-45
40432	1-80	MJ481	1-20
40512	1-70	MJ491	1-86
40669	1-20	MJE3055	0-68
AC128	0-28	OA91	0-06
AD142	0-50	OCS5	0-63
AD149	0-68	S2CN1	0-12
AD161	0-42	SD4	0-09
AD162	0-40	TO3 Transistor covers, ea.	7p

RESISTORS 10%—5%—2%

Code	Power	Tolerance	Range in ohms	Values 1 to 9	10 to 99	100 up
C	1/20W	5%	82-220K	E12	9	8
C	1/8W	5%	4.7-470K	E24	1	0.8
C	1/4W	10%	4.7-10M	E12	1	0.8
C	1/2W	5%	4.7-10M	E24	1-2	1
C	1W	5%	4.7-10M	E12	2-5	2
MO	1/2W	2%	10-1M	E24	4	3
WW	1W	10%	0.22-3.9	E12	7	7
WW	3W	5%	1-10K	E12	7	7
WW	7W	5%	1-10K	E12	9	8

Codes: C = carbon film high stability low noise
MO = metal oxide ElectroSil TR5 ultra low noise
WW = wire wound Plessey

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 72, 91 and their decades. Prices are in pence each for same ohmic value and power rating, 50T sized values. (Ignore fractions of 1p on total value of resistor order.)

Minitron DIGITAL INDICATOR



TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 0-9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V d.c. per segment. A limited number of alphabetical symbols also available. In 16 lead DIL case


Suitable BCD decoder driver type FLL121T net £1-36

DIL Socket: 16 lead 30p. No. 3015G showing + or - and fig. 1 and decimal point 22.

PRECISION COMPONENTS

Resistors by Rivlin, 0.1% to 0.01%, £1 to £2. Capacitors by MFD, 0.1 µF to 22 µF, 70p to £3-50. Prices and delivery times on request.

SLIDE POTENTIOMETERS

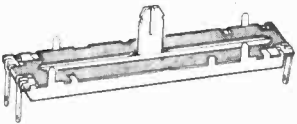

Robust construction, smooth silent action. In values from 4kΩ to 1MΩ, linear or log. 25p each. Escutcheon, light grey. 10p. Knobs, flat, grip type, in black/red/green/white/blue/light grey/dark grey or white. 5p each.

SOLDERSTAT SOLDER IRONS

As appointed distributors for well-known Eimco-Wolf "Solderstat" irons, we offer this model H38 in 16 or 24 watt, a.c. mains, net £1-87

INFINITELY VARIABLE TEMPERATURE CONTROLLED SOLDER IRON £9-20

DE-SOLDER BRAID

Per 6ft length, net 50p.

NIPPBOARDS

A useful board for circuit building. Type 1A. Single basic pattern 2"2" 1.7, 15p. Type 2A. Two pins, side by side, 28p. Type 3A. Dual channel, 28p. Type 3A. 3 pins, side by side, 36p. Type 4AS. Dual channel, 2 above 2, 44p. Many others in stock up to 10 patterns.

PUBLICATIONS

Handbook of Transistor Equivalents, 40p. Handbook of Tested Transistor Circuits (H. News), Radio & Electronics. Colour codes & data wall chart, 15p. Engineers Reference Handbook & Tables, 20p. (Add 3p for postage on each of above if bought separately.)

SIEMENS TTL

INTEGRATED CIRCUITS

These prices are nett.

FLH101 (7400)	20p	FLJ121 (7473)	45p
FLH201 (7401)	20p	FLJ141 (7474)	45p
FLH191 (7402)	20p	FLJ151 (7475)	45p
FLH291 (7403)	20p	FLJ131 (7476)	45p
FLH211 (7404)	25p	FLH221 (7480)	68p
FLH271 (7405)	25p	FLH231 (7482)	87p
FLH381 (7408)	25p	FLH241 (7483)	1-38
FLH391 (7409)	25p	FLH341 (7486)	33p
FLH111 (7410)	20p	FLJ161 (7490)	80p
FLH351 (7413)	35p	FLJ221 (7491A)	1-28
FLH121 (7420)	20p	FLJ171 (7492)	85p
FLH181 (7430)	20p	FLJ181 (7493)	80p
FLH141 (7440)	24p	FLJ231 (7494)	1-13
FLH101 (7414)	1-22	FLJ191 (7495)	87p
FLH281 (7442)	1-16	FLJ261 (7496)	1-48
FLH361 (7443)	1-45	FLJ301 (74100)	1-64
FLH371 (7444)	1-45	FLJ271 (74104)	48p
FLH151 (7450)	20p	FLK101 (74121)	52p
FLH161 (7451)	20p	FLK111 (74122)	48p
FLH171 (7453)	20p	FLJ201 (74190)	1-80
FLH181 (7454)	20p	FLJ211 (74191)	1-80
FLY101 (7466)	20p	FLJ241 (74192)	1-74
FLJ101 (7470)	45p	FLJ251 (74193)	1-74
FLJ111 (7472)	32p		

BAXANDALL SPEAKER

As designed by P. J. Baxandall and originally described in "Wireless World". Complete kit inc. spkr., equaliser and special cabinet kit (18in x 12in x 10in) cut to size. 10 watt RMS/15Ω loading. Part cost carr. in U.K. 60p. Net £13-81

Speaker unit and equaliser kit, net. Post free £4-81. Pack flat cabinet assembly (all cut to shape), natural teak finish with instructions, 22p net. Part cost carr. in U.K. 60p.

SIEMENS THYRISTORS
0-8A-400V, 56p. 600V, 70p.
3A-400V, 60p. 600V, 86p.

CARBON SKELETON PRE-SETS
Small high quality, type PR linear only: 100Ω, 220Ω, 470Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

ZENER DIODES 5% full range. E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.3V to 82V, 27p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

MINIATURE TOGGLE SWITCHES
2A/250V. DP/DT, 48p.

MAINLINE AMPLIFIER KITS
70 watt power amp module kit, £12-60 net. Power supply kit, £6-50 net.

Q.E.D. HIGH QUALITY AMPLIFIER SYSTEMS. Built to your personal specifications. Enquiries invited. Please quote PE.7.

SIEMENS CAPACITORS

POLYCARBONATE - 5% TOLERANCE
250V up to 0.1µF; 100V/0.1µF and above.
0.01, 0.012, 0.015, 0.018, 0.022, 0.027, 0.033, 0.047, 0.056, 4p each.
0.068, 0.082, 0.1, 0.12, 0.15, 4p each.
0.18, 0.22, 5p each.
0.27, 0.33, 6p; 0.39, 7p; 0.47, 8p; 0.56, 10p; 0.68, 11p; 1µF, 13p.

ELECTROLYTIC CAPACITORS
(Values in µF/V)
0.47/100, 1/100, 2.2/63, 4.7/35, 10/25, 22/16, 47/10, 47/25, 100/10, 220/3, 7p each.
10/63, 22/35, 47/35, 100/16, 100/25, 220/6, 220/16, 470/3, 7p each.
47/50, 47/63, 100/35, 220/16, 8p each; 100/50, 220/35, 10p each; 100/63, 470/25, 1000/10, 12p each; 220/63, 470/35, 1000/16, 17p each; 1000/25, 20p each; 470/63, 1000/35, 22p each; 2200/25, 36p each; 1000/63, 2200/35, 4700/16, 40p each.

Tantalum and other capacitors, etc., see latest 1972 catalogue—issue No. 6.

1972 ELECTROVALUE CATALOGUE (No. 6)

Third printing with latest price and information details. Contains 96 pages plus cover. More items, more information, more diagrams than ever. Post free in U.K. 10p.

NEWMARKET LINEAR I.C.s

LIC 709C/14 dual in line, 34p. L709C/5, TO5 38p.
LIC 741C/14 dual in line, 40p. 741C/5, TO5 42p.

CARBON TRACK POTENTIOMETERS

CARBON TRACK POTENTIOMETERS, long spindles. Double wipers.
SINGLE GANG linear 100Ω to 2.2MΩ, 12p; Single gang log, 4.7kΩ to 2.2MΩ, 12p; Dual gang linear 4.7kΩ to 2.2MΩ, 42p; Dual gang log, 4.7kΩ to 2.2MΩ, 42p; Log/antilog, 10kΩ, 22kΩ, 47kΩ, 1MΩ only 42p; Dual antilog, 10kΩ only, 42p. Any type with 2A D.P. mains switch, 12p extra. Only decades of 10, 22 and 47 available in ranges quoted.
DUAL CONCENTRIC in any combination of P.20 values, 60p; with switch, 72p. Knobs, pair 24p.

DISCOUNTS

10% on orders £5 to £15. 15% on orders over £15. No discount on items marked N.C. Prices subject to alteration without notice.

POSTAGE AND PACKING

FREE, unless otherwise stated. Handling surcharge 10p on mail orders under £2. Overseas orders: carr. and insurance charged at cost. U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

ENQUIRIES FROM TRADE AND OTHER LARGE QUANTITY BUYERS INVITED.

ELECTROVALUE

(Dept. PE 11), 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Hours: 9—5.30, Sat. 1 p.m. Tel.: Egham 3603 (STD 0784-3). Telex 264475
ELECTROVALUE LTD.—AN INDEPENDENT COMPANY SINCE ITS ESTABLISHMENT IN 1965

JAMES SCOTT

SALE OF SURPLUS ELECTRONIC EQUIPMENT

The following items are available for immediate delivery at very competitive prices—

SCANNING ALARM INDICATOR

Can be used for Automatic Monitoring of All Types of Test Points (Up to 25)


Incorporates Auto and Manual Facilities
Illuminated Digital Input Identification
Double Pole Gold Plated Contacts on Uni-selectors

Units Supplied Untested Less Indicating Meter. Price £25 00
Carriage and Insurance (U.K. only) £1 50



DOSIMETER CHARGING UNIT TYPE 200

PORTABLE INSTRUMENTS USED TO CHARGE QUARTZ FIBRE TUBE POCKET DOSIMETER TO ZERO. SUITABLE FOR USE WITH ALL STANDARD TYPES OF QUARTZ FIBRE DOSIMETERS HAVING A MAXIMUM OUTSIDE CHARGING END DIAMETER OF 0.805mm TELEPHONE TYPE A.C. AND GENERATOR. THE OUTPUT OF WHICH IS RECTIFIED AND CHARGES UP A RESERVOIR CAPACITOR TO A MAXIMUM POTENTIAL OF ABOUT 300 VOLTS D.C. SUPPLIED LESS GENERATOR HANDLES. PRICE £15 00. P & P 20p

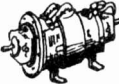


SEALED RELAYS (NATO APPROVED)

GEC 4 pole c/o 24V 870 ohm. GEC 2 pole on/off 24V 870 ohm. GEC 2 pole c/o 65V 5,000 ohm. STC 2 pole c/o 12V 170 ohm

Price each 75p. P & P 10p

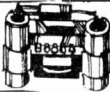PC162 Supply voltage 220-250V a.c. Output voltages 21 Volts d.c. at 330MA 21 Volts a.c. at 540MA



NEWMARKET TRANSISTORS

NKT351	73p	NKT12329	27p	2N2222	18p	NKT218	23p
NKT352	23p	NKT12429	27p	NKT12	30p	NKT221	30p
NKT406	80p	NKT13329	27p	NKT72	25p	NKT222	18p
NKT420	£1 80	NKT13429	27p	NKT73	22p	NKT223	25p
NKT450	30p	NKT16229	27p	NKT121	21p	NKT224	22p
NKT803	22p	NKT20329	29p	NKT124	28p	NKT227	25p
NKT813F	28p	NKT80111	85p	NKT125	36p	NKT237	29p
NKT874	30p	NKT80113	88p	NKT126	35p	NKT238	16p
NKT877	18p	NKT80125	80p	NKT127	23p	NKT249	29p
NKT713	27p	BC107	8p	NKT128	18p	NKT281	18p
NKT734	24p	BC108	8p	NKT129	22p	NKT270	18p
NKT736	26p	NKT80770	13p	NKT135	24p	NKT271	16p
NKT773	23p	BFY51	17p	NKT137	30p	NKT272	15p
NKT0216	20p	BSY95A	10p	NKT142	48p	NKT273	18p
NKT3055	23p	2N887	13p	NKT143	48p	NKT274	16p
NKT6817	27p	2N706	8p	NKT212	23p	NKT275	21p
NKT10339	23p	2N914	15p	NKT213	23p	NKT278	18p
NKT10419	17p	2N918	28p	NKT214	21p	NKT301	70p
NKT10439	25p	2N930	22p	NKT215	19p	NKT302	85p
NKT10519	20p	2N1990	22p	NKT217	48p	NKT303	70p
						NKT304	78p

S.T.C. RELAYS—BRAND NEW

TYPE	CONTACT FORM	NOMINAL COIL VOLTAGE	COIL RESISTANCE (OHMS)	PRICE EACH
250 ARO	4 CHANGE/OVER	6V d.c.	52	£0 68
250 ABO	4 CHANGE/OVER	48V d.c.	2,500	£0 68


TYPE	CONTACT FORM	COIL VOLTAGE	SWITCHING CURRENT	PRICE EACH
SL722212	3 Pole on/off	12V a.c.	10A at 440V a.c.	£1 00
SL7622715	2 Pole C/O	220V a.c.	10A at 440V a.c.	£0 87

TYPE	CONTACT FORM	COIL VOLTAGE	COIL RESISTANCE	PRICE EACH
SP13372	Single Pole C/O	6V d.c.	140 ohm	£0 40
SP13366	Single Pole C/O	12V d.c.	350 ohm	£0 40
11301D	Single Pole C/O	18V d.c.	875 ohm	£0 40

UNISELECTOR SWITCHES

6 bank 25 way 75 coil 50V d.c. operation. Mounted on Modular Type Chassis with front panel containing 20 illuminated Push Button Switches Completely wired for operation.

Price £15 P & P £0 55

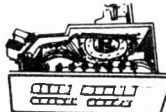

AUTOMATIC CYCLER UNIT

This unit generates stepping pulses (50V d.c.) at intervals of 6 pulses per min to 120 pulses per min—continuously variable. Can be used for Automatic Stepping of one or more uniselector switches shown above.

Price £12 50 P & P £0 45

NEWMARKET PACKAGED AUDIO AMPLIFIER

PC1 150mW Audio Amplifier Price £1 00 each. P & P £0 10
PC10 Magnetic replay head amplifier supply voltage 9V d.c. Input impedance 150. Price £0 90 each. P & P £0 10

WE HAVE A LARGE RANGE OF CAPACITORS AND RESISTORS. PLEASE SEND STAMPED AND ADDRESSED FOOLSCAP ENVELOPE FOR YOUR CATALOGUE

POST & PACKING OVER £2—FREE. OVER £1 AND UNDER £2—15p. UNDER £1—10p UNLESS SPECIFICALLY MENTIONED. P. & P. U.K. ONLY

JAMES SCOTT (ELECTRONIC ENGINEERING) LIMITED
CARNTYNE INDUSTRIAL ESTATE, GLASGOW G32 6AB
TEL: 041-778 4206

COMPARE OUR PRICES

Speaker Bargains

E.M.I. 13in x 8in 3, 8 & 15 ohms plain 2-00
with tweeter 2-25
twin tweeter 3-50

8in x 6in 3, 8 & 15 ohms 1-30
7in x 4in 3 & 8 ohms 1-05
FANE 8in 8 ohm, dual cone 2-30
CELESTION 8in 15 ohm 1-50
GOODMANS 10in x 6in 3 ohm 1-60
BAKER GROUP 25 12in 25W 8 or 15 ohm 5-75

Postage 25p per speaker
2 1/2in or 64 ohm P.P. 10p 50
Kit-torm cabinets, leak (17in x 10in x 6in) 2-75
with a 13in x 8in or 8in cut out (12in x 12in x 6in) with a 9in 5in or 8in cut out. 2-25
(please specify cut out)
Add 35p per cabinet for post & packing

Microphone Bargains 2p
MIC45 "ACOS" metal case, crystal hand 95
CM 20 Crystal Hand 45
DX166 Dynamic Stick 90
DX143 Dynamic, cassette-type stick 1-00

MIC60 "ACOS" stick crystal 1-00
CM70 SWANET stick metal, switch crystal 1-45
DM160 Dynamic uni-dir, ball metal 3-75
UD180 50K/600 ohm uni-dir, ball metal 4-50
TW200 Leason dual imp ball metal uni-dir 5-75
Guitar mike 45
Lapel type, crystal 40
Postage 17p each

THIS MONTH'S SPECIAL OFFER
Solid state stereo amplifier tt-200, 10 watts/channel r.m.s. 8 ohm output imp. Delux Walnut Cabinet, brushed aluminium front. Switches for tape, tuner, crystal/magn. cartridge. Stereo reverse

left and right channel. Source and monitor, independent bass and treble control for each channel. Headphone socket. ONLY £21 Whilst stocks last. P. & P. 21.

Cartridges—with standard fittings & styli 8p
ACOS GP91/29C or GP91/35C stereo compatible 1-05
ACOS GP94 stereo ceramic 1-90
ACOS GP95 stereo crystal 1-85
9TH AC Sonotone stereo ceramic (diamond) 2-00
ACOS GP67/2C mono crystal 85
ACOS GP101 compatible crystal 75
19-T Sonotone stereo crystal 80p
Postage 9p per cartridge

Multitesters 8p
1,000 ohms/volts £2-50
2,000 ohms/volts £2-75
10,000 ohms/volts £5-00
50,000 ohms/volts £10-00
100,000 ohms/volts with transistor tester £15-00
Postage 17p each

Panel Meters 2in sq. 0-500mA, 0-1mA, 0-10mA, 0-100mA 0-500mA, "S" METER £1-50 Postage 17p each

Tapes—"MYLAR" base finest quality British made. 8p
5in 600ft 45p
5in 900ft 45p
5in 1200ft 60p
5 1/2in 900ft 49p
5 1/2in 1200ft 58p
5 1/2in 1800ft 85p
7in 1800ft 85p
7in 2400ft 90p
Postage 7p each

RIVERSDALE ELECTRONICS

ALL OUR MERCHANDISE IS FULLY GUARANTEED

Mail Order Dept. E11/72,
P.O. Box 470,
Manchester M60 4BU
SEND 25p FOR
COMPLETE CATALOGUE

REED COILS

3, 6, 9, 12, 24V Miniature 27p
Small 27p
Standard 34p

P. & P. 7p on all orders.

REED SWITCHES

Large range of many sizes, types and manufacture
Popular types:
E Small n/o 10 for 50p
A Miniature n/o 24p each
B Standard c/o 40p each

REED PUSH BUTTON SWITCHES

Momentary Action
1 contact £1-00
2 contacts £1-25
Illuminated 1 contact £1-30
Illuminated 2 contacts £1-55

REED RELAYS

Many versions available, popular types: 3, 6, 9, 12, 24V
Miniature 1/A normally open 56p
Small 2/E 1 contact 36p
2/EE 2 contacts 44p
2/EE 3 contacts 52p
STD 3/B change over 87p

REELS OF ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g. 50, 100 & 200 grams, Send for prices

C.B.M. ELECTRONIC COMPONENTS LTD.

26 Avon Trading Estate, Avonmore Road, London, W 14

P.E. 'GEMINI' STEREO AMPLIFIER

30 watts (R.M.S.) per Channel into 8 ohms!
Total Harmonic Distortion 0.02%!
Frequency Response (—3 dB) 20Hz—100kHz!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but is well within the capabilities of the ambitious constructor.

WE CAN NOW SUPPLY A REPRINT OF THE ARTICLES IN BOOKLET FORM, PRICE 55p, PLUS 4p POSTAGE, WITH FREE COMPLETE COMPONENT PRICE LIST.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.

ALL PARTS AVAILABLE SEPARATELY



ELECTRO SPARES
21 BROOKSIDE BAR
CHESTERFIELD, DERBYSHIRE

QUALITY • SERVICE • VALUE

Designing with

Integrated circuits

BY A. FOORD

A new series designed to help the experimenter to use I.C.s in practical applications. The circuits provided are not intended as definitive designs, but rather as a basis on which to experiment further.

2

Digital I.C. Gates

A BINARY information signal in logic i.c.s has only two possible states: a logic level 1 of about 4 volts and a logic level 0 of about 0 volts. Each logic circuit produces an output logic level that is a logical function of the input logic levels. These levels are not critical provided that they are clearly recognised as 0 or 1, and small changes in levels cannot accumulate to cause loss of accuracy.

Simple logic functions are achieved by using gates while more complex functions use specifically designed circuits, which may include gates but not necessarily so.

TTL SERIES

Several classes of integrated circuit logic are available, including RTL, DTL, TTL and ECL. However, now that TTL logic is available in a variety of speeds and a considerable range of functions, no other type need be considered for general use in this series of articles.

The Series 74 integrated circuits available from many sources are designed and characterised for general purpose high speed digital applications where a high d.c. noise margin and medium power dissipation are important. The series includes gates, bistables, complex logic functions, and many other circuits.

Four compatible TTL families are available to allow switching speed (and hence power dissipation) to be chosen according to the system requirements. The largest and most widely used family is the SN7400 series which has a 10ns propagation delay per gate. (Alternative types are made by various manufacturers and details of equivalents were given in the P.E. I.C. Identichart last month.)

The 74H00 or 74S00 series can be used for minimal propagation delay times, with the 74L00 series reserved for low speeds. A comparison between these families is shown in Table 2.1.

The speed differences over the range are not a matter of selection as the circuits differ, although the logic

Table 2.1

Series Code	Power Dissipation	Propagation Delay	Approx. Relative Price Factor
SN74L00	1mW per gate	33ns delay	1.8
SN7400	10mW per gate	10ns delay	1.0
SN74H00	23mW per gate	6ns delay	2.4
SN74S00	19mW per gate	3ns delay	6.7

functions and levels are compatible. The SN74S00 series, for example, have Schottky barrier-diode clamping to achieve ultra high speeds with the best speed-power product of any high speed logic family.

The Schottky barrier-diode clamping prevents the transistors from going into saturation and eliminates the effect of excess charge storage and subsequent recovery times. These recovery times contribute significantly to the overall propagation delays obtained with conventional saturated TTL circuits.

GUIDELINES WHEN USING TTL

Power Supplies. Ripple and spikes should be kept to 5 per cent or less and regulation should be maintained to better than 5 per cent. Every five to ten packages should be bypassed to r.f. with ceramic capacitors of 0.1 to 0.01 μ F.

A ground plane is desirable especially in large systems, or make the earth line as wide as possible on a printed circuit board and return both ends of long ground wires to a common point.

Gates. Gates should preferably be driven from a low impedance source. If the source impedance is greater than 100 ohms (for example, non TTL circuits) then the input rise and fall times should be less than 1 μ s to avoid instability and oscillation occurring when the gate goes through its active region of operation. Data pulse widths should be 30ns or more.

The unused inputs of AND and NAND gates and unused presets and clears of bistables can be treated as follows:

- They can be tied directly to $+V_{cc}$ where V_{cc} is guaranteed to be *always* equal to or less than 5.5V.
- Connected to $+V_{cc}$ through a resistor of 1 kilohm which protects the input if the supply exceeds 5.5V. Up to 25 unused inputs can be connected to one resistor.
- Connected to an independent supply of between 2.4 and 3.5V.
- Connected in parallel with a used input of the same gate if the maximum fan-out of the driving output will not be exceeded. Each input presents a full load in the logical 1 state to the driving stage.

Completely unused gates can be taken to ground for the lowest power dissipation, or left floating (unconnected).

Unused inputs of NOR gates can be tied to the used input of the same gate (if the maximum fan-out of the driving gate is not required) or returned to ground.

Bistables. If a clock pulse is present maintain the preset or clear pulse until the clock goes low. Rise and fall times of the clock pulse should be less than 150ns to aid noise immunity.

In general the input data of a master/slave JK bistable should not be changed while the clock pulse is high, but exceptions are given in manufacturers' data sheets.

BASIC GATES

Five logic functions are summarised in Table 2.2. Their interrelationship can be seen by comparing the

GLOSSARY

BUFFER An integrated circuit with a higher fan-out than usual, for driving heavy loads.

CHARGE STORAGE Energy stored in a transistor when it is heavily saturated.

DTL A logic circuit using diodes for the input coupling to a common emitter amplifier.

ECL A logic circuit consisting of an *npn* current mode switch.

FAN-OUT The number of inputs which can be driven by the output of a logic gate.

NOISE IMMUNITY A measure of the ability of a logic gate to reject noise pulses. It is the smallest 1 level output voltage minus the minimum effective 1 level input voltage, or the minimum effective 1 level input voltage minus the maximum 0 level output, whichever is the smaller.

PROPAGATION DELAY A measure of the time taken for a change in logic level to be transmitted through an element.

RTL A logic circuit using resistors for the input coupling to a common emitter amplifier.

TTL A logic circuit having all inputs connected to the multiple emitters of a single, common base connected transistor.

Table 2.2: The basic logic functions

IN-PUTS		OUTPUTS				
A	B	AND A.B	NAND $\overline{A.B}$	OR A + B	NOR $\overline{A + B}$	EXCLUSIVE-OR A \oplus B
0	0	0	1	0	1	0
0	1	0	1	1	0	1
1	0	0	1	1	0	1
1	1	1	0	1	0	0

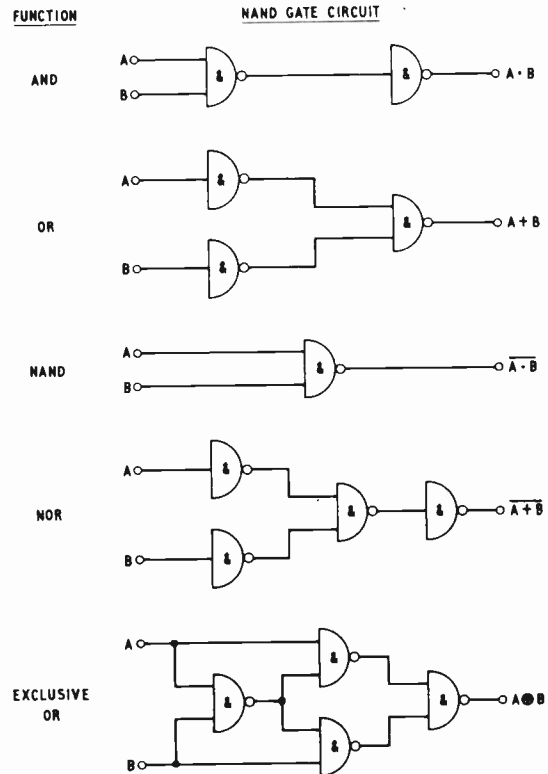


Fig. 2.1. Some logic functions obtained by using only NAND gates

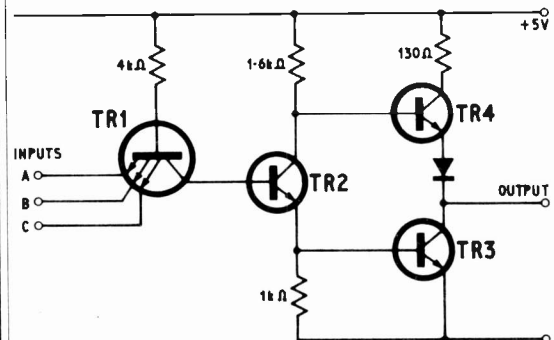


Fig. 2.2. The circuit for a 3 input NAND gate

Table 2.3: Some of the available NAND gate i.c.s

SN7400	Quadruple 2-input NAND gates
SN7401	Quadruple 2-input NAND gates with open collector output
SN7410	Triple 3-input NAND gates
SN7420	Dual 4-input NAND gates
SN7430	8-input NAND gate
SN7437	Quadruple 2-input NAND buffer
SN7440	Dual 4-input NAND buffer

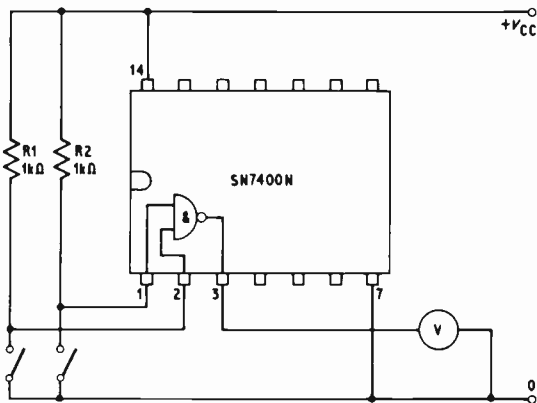


Fig. 2.3. Static tests on a 2 input NAND gate


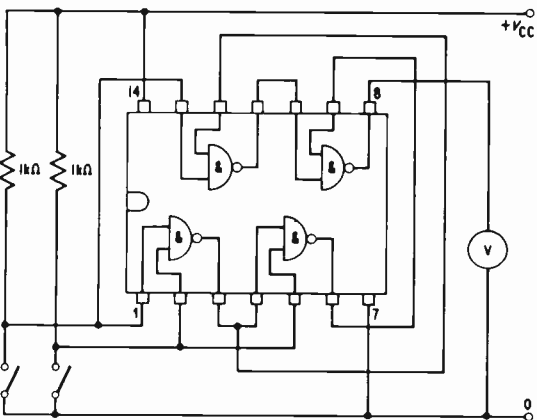


Fig. 2.4. An EXCLUSIVE-OR circuit realised with NAND gates. $V_{cc} = +5V$

Table 2.4:

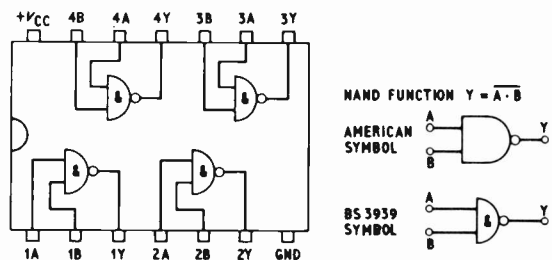Package details and parameters for the SN7400N



PACKAGE DETAILS FOR SN7400N (TOP VIEW)

Supply Voltage V_{cc}	5V	0.25V
Fan-out from each output	10	
Logical 1 input voltage required	2V min.	
Logical 0 input voltage required	0.8V max.	
Logical 1 output voltage	3.3V typical	
Logical 0 output voltage	0.4V max.	
Propagation delay time to logical 0 level	7ns typical	
Propagation delay time to logical 1 level	11ns typical	

output columns. The NAND is obtained by inverting the AND output, while the OR function is the NAND column upside down and can be obtained by inverting the A and B inputs.

It can be seen that the AND function gives a 1 when both A and B are at 1, and so on. The EXCLUSIVE-OR function has a symmetry of its own and is sometimes considered as a separate basic logic function.

Most of the logic functions can be achieved by using only NAND or only NOR gates at the expense of speed and package count, so that for experimental work it is not necessary to maintain a complete stock of all types. This is shown in Fig. 2.1.

NAND GATES

The internal circuit for a three-input TTL NAND gate is shown in Fig. 2.2. TR1 is a multiple emitter transistor. If one or more emitters are grounded the transistor is forward biased, the collector is at a low potential, and TR2 is turned off. This allows TR3 to turn off and TR4 to conduct, resulting in a logic 1 output level.

If, however, all inputs are high the base-collector junction of TR1 will conduct, forward biasing TR2. This turns TR4 off and TR3 on, giving a logic 0 at the output.

The standard TTL gate has a 10ns propagation delay time, a fan-out of about 10 and a noise immunity of at least 1V, making it suitable for most applications. Table 2.3 lists some of the common NAND gates available.

The SN7400 is a quadruple two-input positive NAND gate, package details and parameters are shown in Table 2.4. Although the logic functions can be worked out from the circuit in this case, for more complex packages the corresponding truth table would have to be used.

EXPERIMENT TO VERIFY THE NAND FUNCTION

For experimental work it is convenient to wire several dual-in-line type i.c. holders to pins on a patch board or experimental wiring board; six holders would be enough for many applications and facilitates replacing i.c. packages for other purposes.

The circuit in Fig. 2.3 could be made up to confirm the truth table, the meter indicating go or no-go conditions (or 1 and 0).

EXPERIMENT TO VERIFY THE EXCLUSIVE-OR FUNCTION

The circuit is shown in Fig. 2.4. This function gives an output when A and B are not equal. If one input is inverted the overall function will give an output when A and B are equal. Both arrangements are similar to the upstairs-downstairs light switching found in many homes where a lamp can be switched on or off from either of two places.

Although in this case an EXCLUSIVE-OR package is available (the SN7486) the circuit shows how a simple logic function can be obtained using NAND gates when a suitable package is not to hand.

This article has concluded with two experiments illustrating the static characteristics of the NAND gates. Future articles will deal with further applications of the TTL logic families.

Next month: Basic operational amplifiers

**THE MIDLAND
NATIONAL
AMATEUR RADIO
&
ELECTRONICS EXHIBITION
AT THE
GRANBY HALLS, LEICESTER
OCTOBER
26th to 28th, 1972**

**SPONSORED BY
THE AMATEUR RADIO RETAILERS' ASSOCIATION**

**COME AND SEE THE LATEST DEVELOPMENTS IN
RADIO COMMUNICATIONS AND ELECTRONICS
WORLD-WIDE CONTACTS FROM THE EXHIBITION**

LARGE CAR PARKS

EASY ACCESS FROM M1 MOTORWAY

ADMISSION 20p

**THIS INCLUDES A CHANCE TO WIN A PIECE OF THE
BEST IN RADIO EQUIPMENT**

OPENING TIMES:

THURSDAY 26th and FRIDAY 27th — 12 noon to 9 p.m.

SATURDAY 28th — 10 a.m. to 7 p.m.


OVERSEAS VISITORS FROM PARIS

FRANKFURT, AMSTERDAM AND BRUSSELS

PLEASE CONTACT:

**MIDAWAY LTD., 40a HILLSIDE, CASTLE DONNINGTON, nr. DERBY,
FOR INFORMATION REGARDING INCLUSIVE AIR CHARTER
FLIGHTS TO AND FROM THE SHOW**

SUPERSOUND 13 HI-FI MONO AMPLIFIER

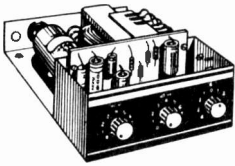


A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with 1/2 ohm stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, eicteon panel, input and output plugs. Overall size 3in high x 6in wide x 7 1/2in deep. A.C. 200/250V.

PRICE £10.50 P. & P. 25p.

DE LUXE STEREO AMPLIFIER

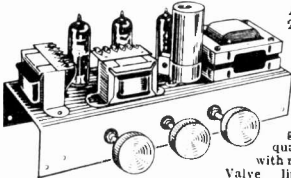

A.C. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:-2x ECL86 Triode Pentodes.

Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. x 4in. x 4in. Overall height including valves 5in. Ready built and tested to a high standard. **Price £8.92.** P. & P. 45p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7 1/2V and 9V and 12V at 1 amp continuous (1 1/2 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 7" x 4" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £4.50 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2in x 3in approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS

8in x 6in x 1/4in. FIVE for 50p. P. & P. 13p.

LIMITED NUMBER! COILED SPRING BACK TELEPHONE CABLE. Closed approx. 10', extends to 36'. 4 core or 6 core. 25p each. P. & P. 5p. 5 or more post free.

SPECIAL OFFER! MAINS TRANSFORMER. 200/240V A.C. input. 35V at 1 amp output. Overall size 2 1/2" x 2 1/2" x 3" approx. Suitable for drop through or vertical mounting. 75p. P. & P. 30p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL x 3 1/2inW x 3inD. Price £1.75. P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 88p. P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.38. P. & P. 30p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.C. Tape, MKE, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/4 x 1/2in. Brand new - complete with instructions. Price 88p. P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS and SUBSTITUTES A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. **ONLY 40p.** Post 5p.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £8.97. Carr. 50p. With stereo cartridge £7.97. Carr. 50p.
LATEST GARRARD MODELS. S.A.E. for Latest Prices!

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, EL165B, AT60, etc., or B.S.R. C109, C129, A21, etc. Choice of black leatherette or teak grain finish. Size 12 1/2in x 14 1/2in x 3 1/2in (approx). 7 1/2in high, including rigid smoked acrylic cover. Price **£5.50** P. & P. 60p.

LATEST ACOS GP91/18C Mono Compatible Cartridge with 1/2 ohm stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.

SOROTONE STEREO COMPATIBLE STEREO CARTRIDGE
T/O stylus. Diamond Stereo LP and Sapphire 78. **ONLY £2.50.** P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1.63. P. & P. 10p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. £1.50. P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in x 9 1/2in. Ready built and tested. **PRICE £3.75.** P. & P. 40p. **ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit cabinet below. **PRICE £4.88.** P. & P. 50p.

DE LUXE QUALITY PORTABLE R/P CABINET MK II
Uncut motor board size 14 1/2in. clearance 2in. below. 6 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE £4.75.** P. & P. 60p.

SPECIAL OFFER!! HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2in high x 10 1/2in wide x 5 1/2in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8.40 Carr. 65p.
CABINET AVAILABLE SEPARATELY £4.50. Carr. 60p.

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £6.50. Carr. 65p.

LOUDSPEAKER BARGAINS

5in 3 ohm £1.05. P. & P. 15p. 7 x 4in 3 ohm £1.15. P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1.62. P. & P. 20p. E.M.I. 13 1/2 x 8in with high flux ceramic magnet 3, 8, or 15 ohm £3.20. P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two built-in tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

BRAND NEW. 12in 15W Hi-Fi Speakers, or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly £6.75. Guitar models: 25w £6.75. 35w £8.50. P. & P. 38p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticised cone surround. **£3.75.** P. & P. 25p.

12in "RA" TWIN CONE LOUSPEAKER
10 watts peak handling. 3, 8 or 15 ohm. £2.20. P. & P. 30p. 35 ohm SPEAKERS 3". **ONLY 65p.** P. & P. 13p.
"POLY PLANAR" WAFER-TYPE. WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 1 1/2in x 1 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. **Only £5.75 each.** P. & P. 25p.

VYNAR & REXINE SPEAKERS & CABINET FABRICS
app. 5 1/2in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.


HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexiform ear-muffs. Wired and fitted with standard stereo jin jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £2.95.** P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. 0.1uF **PRICE £1.05.** P. & P. 8p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100uA for balance or tuning. Approx. size 1in x 1in x 1/2in. Limited number 75p. P. & P. 10p.

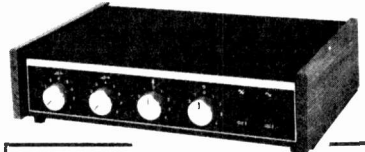HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONNECTION


A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 10W per channel into 8 ohms. Frequency response \pm 3dB 12-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1-0 amp. Overall size 12" wide 8" deep x 2 1/2" high.

Fully detailed 7-page construction manual and parts list free with kit or sent 18p plus large S.A.E.

PRICES AMPLIFIER KIT. **£10.50** P. & P. 15p. (Magnetic input component* 30p extra)
POWER PA'K KIT. £3 P. & P. 30p.
CABINET. £3 P. & P. 30p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested. **£20.50.** Post Free.

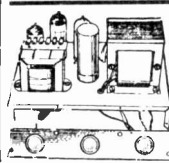Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.



3-VALVE AUDIO AMPLIFIER H434 MK II
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in w. x 4in. d. x 4 1/2in h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4.75.** P. & P. 35p.

HBL "FOUR" AMPLIFIER KIT. Similar in appearance to H434 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.88. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx 3 1/2 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

OUR ROCK BOTTOM BARGAIN PRICE **£2.75** P. & P. 35p

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speakers and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. **ONLY £7.97.** P. & P. 55p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.


Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Sinclair Project 60

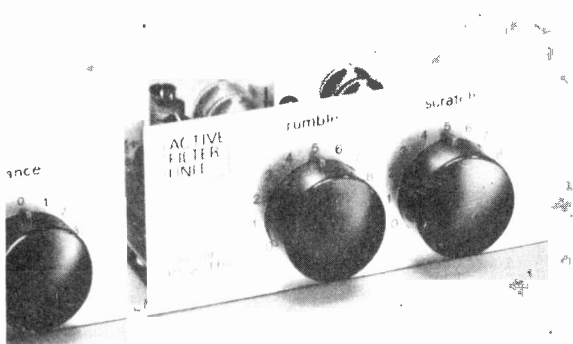

Active Filter Unit (A.F.U.)

Built and tested
post free
£5.98

The value of an efficient filtering system cannot be over emphasized in these days of very high quality reproduction since there are so often occasions where its use can mean the difference between comfortable and uncomfortable listening. On the low pass side the Sinclair A.F.U. will effectively reduce hiss from radio or tape, cut out heterodyne whistles on A.M. reception, greatly reduce record surface noise and other imperfections; on the high-pass side it will cut out motor rumble and other spurious low frequency intrusion. The unit is for use between pre-amp (including tape pre-amps) and power amplifiers, and operates in two sections, both stereo. The cut-off frequencies are continuously variable, and since attenuation in the rejection band is rapid (12dB/octave) there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is as easy to mount as the stereo 60 pre-amp/control unit which it matches in styling, along with the Stereo FM Tuner.

SPECIFICATIONS

The A.F.U. employs two Sallen and Key type active filter stages, one rumble (high pass) and one scratch (low pass). The two stages use complementary transistors to minimise distortion.

Supply voltage: 15 to 35 volts. Current 3mA maximum


Gain at 1kHz: Filters flat 0.98 (—0.2 dB)

HF cut off: (—3dB) variable from 28 kHz to 5 kHz at 12 dB/octave.

LF cut off: (—3dB) variable from 25Hz to 100Hz at 12dB/octave.

Distortion: at 1kHz (35 volt supply) 0.02% at rated output.

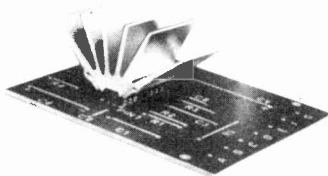Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC, make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak), 6—8Ω. **Frequency Response:** 5Hz to 100KHz ±1dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.
£2.98 Post free

Project 605



The easy way to buy and build Project 60

Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

Everything you need to assemble a superb 30 watt high fidelity stereo amplifier without having to solder.

sinclair

Sinclair Radionics Ltd, London Road, St. Ives, Huntingdonshire PE17 4HJ. Tel: St. Ives 64311


the world's most advanced high fidelity modules

Z.30 & Z.50 power amplifiers

Built, tested and guaranteed with circuits and instructions manual **z.30 £4.48 z.50 £5.48**

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to provide unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and are intended for use principally with other units in the Project 60 range. Their performance and design are such, however, that Z.50s and Z.30 may be used in a far wider range of applications.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).— Power Outputs: Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts. **Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts. **Frequency response:** 30 to 300,000Hz ± 1dB. **Distortion:** 0.02% into 8 ohms. **Signal to noise ratio:** better than 70dB unweighted. **Input sensitivity:** 250mV into 100 Kohms (for 15w into 8Ω). For speakers from 3 to 15 ohms impedance **Size:** 14 x 80 x 57mm

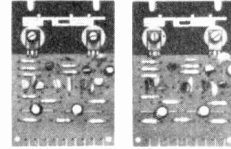


Stereo 60 Pre-amp/control unit

Built, tested and guaranteed. **£9.98**

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio — up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve ±1dB 20 to 25,000 Hz. Ceramic p.u. — up to 3mV. Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to -12dB at 10KHz; BASS +12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

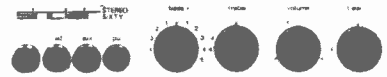

Project 60 Stereo F.M. Tuner

Built and tested. Post free. **£25**

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.


SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7µV for lock-in over full deviation. **Squelch level:** Typically 20µV. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz — 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2µV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on, tuning. **Size:** 93 x 40 x 207mm.



Power Supply Units

Designed specifically for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 or PZ.8 where a stabilised supply is essential.

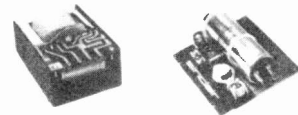PZ.5 30 volts un stabilised £4.98
PZ.6 35 volts stabilised £7.98
PZ.8 45 volts stabilised £7.98
(less mains transformer)
PZ.8 mains transformer £5.98



Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de RMS stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic, guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

SINCLAIR RADIONICS, ST IVES, HUNTINGDONSHIRE PE17 4HJ

Please send _____

I enclose cash/cheque/money order.

Name _____

Address _____

PE1172

sinclair

NOW YOU CAN CATCH SHOALS OF BIG FISH with new electronic miracle

First time marketed in England, this exciting electronic instrument (the "Decoytron") is the one responsible for starting the electronic fish-lure rage in the U.S.A. just recently. Uses ingenious double-action method of attracting all kinds of fish from hundreds and hundreds of feet away... saltwater or freshwater. Why this device is so fantastically successful is because it *actually imitates the sound of wet insects milling about the surface.* These sound waves spread out hundreds of feet in all directions. Although this peculiar sound frequency won't sound like much to you—to all the fish in the area it's their dinner bell! But that's not all... *electroluminescence neon tubes cunningly flicker intermittently,* penetrating the area for hundreds of feet around, at a frequency fish are unable to resist. The fish mistake this flickering glimmer for the soft phosphorescence glow given off by Plankton... a favourite delicacy of most fish! All you do is switch on, lower into the water (it's completely water resistant) allow around 5 minutes—then start reeling 'em in. We'll bet you won't be able to reel 'em in fast enough. Self-contained batteries last ages—cost pence. Kit of all parts including special easy as a, b, c. directions only **£2-50 + 25p P. & P.** (Parts available separately.)

BUILD 5 RADIO AND ELECTRONIC PROJECTS



ONLY £2-45

Amazing Radio Construction set! Become a radio expert for **£2-45.** A complete Home Radio Course. No experience needed.

Part 1 including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation box **45p** extra as illus. (if required) (parts available separately) no soldering necessary. Send **£2-45 + 20p p. & p.**

SOOTHE YOUR NERVES RELAX WITH THIS AMAZING RELAXATRON



ONLY £2-75

CUTS OUT NOISE POLLUTION—SOOTHE YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON—is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainforest mystery relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, components, nuts, screws, wire, etc., no soldering. **£2-75 + 25p P. & P.** (Parts available separately.)

AMAZING MAGIC MUSIC BOX

make electronic music waving your hands about

ONLY £2-75

Everyone's heard the weird, wonderful, but beautiful music used in Science Fiction Films, Horror Films, etc. also on Radio & Television. This unearthly, eerie music is almost always produced by a little known electronic device measuring only a few inches... called a Theremin. All you have to do is switch on your radio (almost any type will do) and place the Theremin close by. Switch on the Theremin and proceed to wave your hands mysteriously in the air like a magician. The most fantastic musical sounds are then produced, and with a little practice people can learn to play all the well known tunes. Apart from its musical value, its small size allows it to be used to best advantage at parties, gatherings of friends, etc., where it attracts tremendous interest. Provides hours and hours of pleasure to young and old. Uses standard PP3 battery which lasts ages. The 3 Transistor circuit, though fairly advanced is simple to build with our pictorial step-by-step plans. No soldering necessary. Easily built in an hour or so using our special terminal board (Pat. applied for). All parts including nuts, bolts, case, etc., **ONLY £2-75 + 25p P. & P.** (Parts available separately.)



INGENIOUS ELECTRONIC SINGING & WARBLING CANARY!

ONLY £4-50

Actually whistles and warbles like a real live Canary! Amazing circuitry faithfully reproduces the Canary's magnificent song. Just switch on and leave it whistling down scale for some seconds, suddenly breaking into a delightful warble, then several seconds later shifting to a second or two only to start automatically again in a few seconds. People listen to the delightful song all day and never get bored! Relax, as the sweetest nerve-soothing birdsong takes you to leafy woods and glades. Provides countless hours of joy to young and old alike. Standard self-contained battery lasts ages. Easily built in an hour or so with special pictorial step-by-step plans. No soldering necessary. All parts including terminal board (Pat. applied for), transformers, loudspeaker, transistors, nuts, screws, wire, etc., plus case (which fits under cage—case and toy bird not supplied). **ONLY £4-50 + 25p P. & P.** (Parts available separately.)

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD. (PEI), 8 Westborough Grove, London, W.2. (Calls welcome. 9 a.m.-5.30 p.m.)



The amazing "Phototron" SOUND OPERATED FLASH

Take flash pictures at the exact instant of the bursting of a balloon. A champagne cork leaving the bottle. The split second a hammer strikes a light bulb. The mind boggles at the possibilities of the "Phototron"... *the only limit is your imagination.* Now that inexpensive flash guns are on the market in quantity, it has made possible, with strictly limited funds, the production of a wide variety of exciting photography effects, once extremely brief and normally measured in Milliseconds. Now, providing the camera shutter is left open in a dark or subdued light, it is the timing of the flash that determines what is imprinted on the film—not necessarily anything done by the camera. As electronic flash guns are fired by making a switched connection then it becomes obvious that one of the latest Silicon Controlled Relay's can be used. If we make this S.C.R. operate by sound (with variable sensitivity control for soft/light sounds) some real "eyes out" photography effects can be captured forever on film. Easily built in a couple of hours or so, the "Phototron" is fully solid state, uses self-contained PP3 battery. No soldering necessary using our special terminal board (Pat. applied for). All parts including special pictorial step-by-step plans, transistors, microphone, S.C.R., potentiometers, switches, test lamp, case, nuts, screws, etc., **ONLY £4-50 + 25p P. & P.** Made up must be worth at least £10. (Parts available separately.)

Eavesdrop on the exciting world of Aircraft Communications—

V.H.F. AIRCRAFT BAND CONVERTER ONLY £2-85



Listen in to AIRLINES, PRIVATE PLANES, JET-PLANES. Eavesdrop on exciting cross talk between pilots, ground crew control, airport tower. Hear for yourself the disciplined voices hiding themselves on talk-downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAX, PRESTWICK, ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend lead aerial, plug close to any ordinary medium wave radio (even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. SEND **ONLY £2-85 + 20p p. & p.** for kit including case, nuts, screws, wire, etc. etc. (Parts available separately.)

FIND BURIED TREASURE!

Transistorised Treasure Locator




This fully portable transistorised metal locator detects and tracks down buried metal objects in signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES, ETC. ETC. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards. With the clear, easy-to-follow, step-by-step, fully illustrated instructions, uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2-85 + 25p p. & p.** (Sectional handle as illustrated **95p** extra.) Parts available separately. Made up looks worth £15!

TREASURE LOCATOR MODULE

ONLY £4-50

FULLY TRANSDUCED METAL DETECTOR MODULE. Uses PP3 battery and phones. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN. **£4-50 + 30p** carr. for kit. (High quality Danish Stethoscope headphones **£2-75** extra if required.)

SHORTWAVE TRANSISTOR RADIO

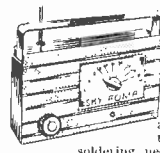

ONLY £2-75
Anyone from 9 years old can follow the step-by-step, easy as ABC, fully illustrated instructions. No soldering necessary. 76 stations logged on top aerial in 30 mins—Russia, Africa, USA, Switzerland, etc. Experience thrill of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3in x 4 1/2in x 1 1/2in. **ONLY £2-75 + 20p p. & p.** Kit includes cabinet, screws, instructions, etc. (Parts available separately.)

UNIQUE RADIO FOR BEDROOM OR OFFICE

No batteries, no electricity. **ONLY £1-70** never wears out



Tune in your favourite programmes of the news, or sports in the Office or in your bedroom. Uses sensitive, germanium diode originally evolved from wartime radar. Never buys a battery. Never use electricity. Never replace. Covers all medium waves. Clear beautiful tone. Size 4 1/2in x 2 1/2in x 1 1/2in in beautiful case. **ONLY SEVEN CONNECTIONS AND IT'S WORKING.** No soldering necessary. CAN BE BUILT ALMOST BLINDFOLD IN UNDER 15 MINUTES! Ideal for absolute beginner from 8 years of age upwards. SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS, **ONLY £1-70 + 20p P. & P.** for all parts including beautiful case. Germanium semi-conductor, tuning condenser, personal phone, wire, nuts, screws, SIMPLE AS ABC INSTRUCTIONS (Parts available separately.)

"READ PEOPLE'S MINDS"—TEST THEIR NERVES—BEAT THEM AT CARDS, ETC. WITH THIS ASTONISHING

ELECTRONIC BRAIN BOX Only £2-87


With this "Brain-box" you will be able to perform mind-boggling feats. THE MIND READING GAME will make people swear you can "telepathic" thoughts. THE AMAZING CARD TRICK UNIT completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. THE ELECTRONICS NERVES TESTER puts your friends to a very lively test. It gives out fail and flush signals (the winner is the person with lowest number of fail signals). Can be adjusted from the person. THE ELECTRONIC MAZE tests the mental ability of the player because it uses psychology with an electronic twist on it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof. Size 1 1/2in x 1 1/2in x 6in (max.). You can play all these games and more besides after building the "Brain-box". No soldering, you get pictorial, easy as ABC step-by-step simple instructions. **ONLY £2-87 + 35p P. & P.** for all parts including chassis, switches, stylus, signalling lights, wire, nuts, screws, etc. Uses standard battery. Presentation box 35p extra as illus. (if reqd.). (PARTS AVAILABLE SEPARATELY) FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.



Have fun with electronics...



Radionic Construction Kits

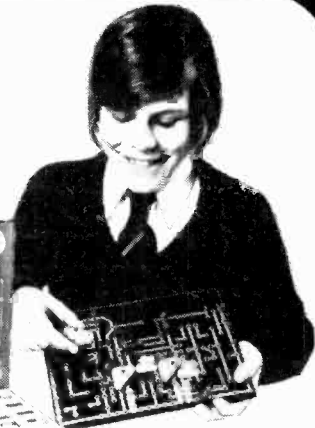

NO SOLDERING BATTERY OPERATED

Build your own radio receiver and many exciting experiments with the unique printed circuit board and mounted components. Easy to build, no soldering, battery operated, plus a fully illustrated instruction manual giving precise directions for each experiment. Ideally suitable for both the experimenter and beginner.

Radionic Products Limited

St Lawrence House, Broad Street, Bristol BS1 2HF
Tel. 0272 25351

A member of the ESL BRISTOL Group of Companies

PHILIPS

Please send me literature on Radionic radio and electronics construction kits.

NAME _____

ADDRESS _____

VALVES

SAME DAY SERVICE
NEW! TESTED! GUARANTEED!

SETS 1R5, 1R6, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for £1-12. DAF96, DF96, DK96, DL96. 4 for £1-55.

1R5	-28	30C17	-78	8B91	-10	EM80	-38	PCF806	-66	U329	-66
1R6	-22	30C18	-58	EBC33	-40	EM81	-38	PCF808	-68	U301	-80
1T4	-18	30F5	-84	EBC41	-54	EM84	-32	PCL82	-30	UABC80	-32
3R4	-26	30FL1	-65	EBC81	-30	EM87	-50	PCL83	-57	UAF42	-50
3V4	-47	30FL12	-89	EBC90	-22	EY51	-36	PCL84	-34	UBC41	-46
6U4G	-31	30FL14	-88	EBF80	-32	EY86	-29	PCL86	-38	UBF80	-34
6V40	-85	30L1	-29	EBF83	-39	EY87	-29	PCL86	-38	UBF89	-32
6Y3GT	-34	30L15	-70	EBF89	-29	EZ40	-43	PCL88	-68	UC84	-32
6Z4G	-38	30L17	-67	ECC81	-17	EZ41	-43	PCL90	-89	UC85	-35
6/30L2	-54	30P4	-65	ECC82	-20	EZ80	-22	PCL905	-38	UCF80	-32
6AL5	-11	30P12	-69	ECC83	-35	EZ81	-23	PENA4	-77	UCH42	-58
6AM6	-13	30P19	-65	ECC85	-34	EZ90	-25	PEN36C	-70	UCH81	-32
6AQ5	-22	30PL1	-60	ECC804	-54	GZ30	-34	PFL200	-52	UCL82	-32
6AT6	-20	30PL13	-89	ECF80	-31	GZ32	-40	PL36	-49	UCL83	-55
6AT6	-20	30PL14	-68	ECF82	-26	KT41	-77	PL81	-44	UF41	-52
6BA6	-20	35L6GT	-45	ECH33	-55	KT61	-55	PL81A	-47	UR89	-30
6BE6	-21	35W4	-25	ECH42	-59	KT66	-78	PL82	-31	UL41	-53
6BJ6	-41	35Z4GT	-25	ECH81	-29	LN319	-63	PL83	-33	UL84	-30
6BW7	-52	50CD6G	-68	ECH83	-40	LN329	-72	PL84	-30	UM84	-22
6F14	-40	807	-48	ECH84	-36	LN339	-65	PL500	-63	UY41	-39
6F53	-68	AC/AP2	-77	ECL80	-35	N78	-87	PL504	-83	UY85	-25
6FZ5	-53	B49	-65	ECL82	-31	P61	-40	PM84	-33	VF4B	-77
6J7G	-24	B729	-62	ECL86	-35	PABC80	-34	P255	-95	W77	-43
6K7G	-12	CCH35	-67	EP39	-38	PC86	-47	PY32	-52	Z77	-22
6K8G	-17	CY31	-30	EF41	-60	PC88	-47	PY33	-52	Transistors	
6Q7G	-35	DAF91	-22	EF80	-23	PC96	-42	PY81	-25	AC107	-17
6SL7GT	-30	DAF96	-38	EF85	-28	PC97	-38	PY82	-25	AC127	-18
6SN7GT	-30	DF91	-16	EF86	-30	PC900	-29	PY83	-26	AD140	-37
6V6G	-28	DF96	-38	EF89	-26	PC984	-29	PY88	-73	AF15	-20
6V6GT	-28	DH77	-20	EP91	-13	PC85	-23	PY800	-34	AF116	-20
6X4	-28	DK32	-33	EP92	-27	PC88	-38	PY801	-34	AF117	-20
6X5GT	-28	DK91	-28	EP98	-65	PC89	-45	R19	-30	AF125	-17
10P13	-53	DK92	-50	EF183	-28	PCC189	-48	R20	-70	AF127	-17
12AT7	-17	DK96	-45	EF184	-31	PC805	-70	U25	-73	OC26	-25
12AU7	-20	DF95	-19	EF90	-34	PC806	-28	U26	-70	OC44	-12
12AX7	-22	DL92	-28	EL33	-55	PCF80	-28	U27	-47	OC82	-12
19BG6G	-80	DL94	-47	EL34	-45	PCF82	-33	U49	-70	OC71	-12
20F2	-67	DL96	-38	EL41	-54	PCF86	-46	U52	-31	OC72	-12
20P3	-75	DY86	-24	EL84	-23	PCF800	-58	U78	-24	OC75	-12
25L6GT	-19	DY87	-24	EL90	-26	PCF801	-28	U191	-68	OC81	-12
25Y4GT	-57	DY802	-33	EL95	-33	PCF802	-40	U193	-42	OC81D	-12
30C1	-28	EAF180	-32	EL95	-33	PCF802	-40	U251	-64	OC82	-12
30C16	-58	EAF42	-50	EL500	-62	PCF805	-58	U301	-38	OC82D	-12
										OC170	-28

READERS RADIO


85 TORQUAY GARDENS, REDBRIDGE, ILFORD
ESSEX Tel. 01-550 7441

Minimum post/packing on 1 valve 7p, on each additional valve
(3p per valve extra)

Any parcel insured against damage in transit 3p extra.

A.M.C. ELECTRONICS LTD.

"GEMINI" FM STEREO TUNER

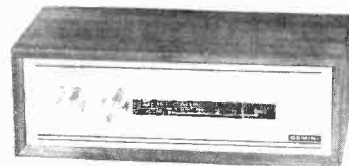

All components to build this outstanding phase lock easily aligned tuner as described in April/May/June P.E. We are offering an optional chassis and solid wood sleeve in ready to assemble form. S.A.E. for details and itemised prices. Complete kit £33.90.

SCORPIO ELECTRONIC IGNITION

Complete kit with comprehensive construction and fault finding data. £11. Post paid. Data 10p. Itemised prices, S.A.E. please.

AMCEL, MAIL ORDER, 160 DRAKE ST.,
ROCHDALE Tel. 0706-46234

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the **practical way**.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Built Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.


You LEARN—but it’s as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

Specialist Booklet

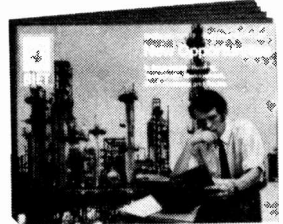If you wish to make a career in Electronics, send for your FREE copy of “NEW OPPORTUNITIES”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

B12

NAME (BLOCK CAPITALS) _____ AGE _____

ADDRESS _____

SUBJECT OF INTEREST _____

MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES LARGEST RANGE
BRAND NEW FULLY GUARANTEED

MOTOROLA			1-24 95-99		1-25 95-99	
We can now offer a vast range of Motorola IC's at industrial distributor prices.			\$p	\$p	\$p	\$p
Examples	\$p	Data Sheets				
MC724P	86		8N7416	0-45 0-40	8N7496	0-87 0-77
MC780P	1-94	\$0.12j	8N7417	0-30 0-25	8N7497	0-25 5-25
MC1303L	8-70	extra	8N7420	0-20 0-18	8N74100	1-64 1-44
			8N7421	0-22 0-20	8N74104	1-52 1-23
			8N7422	0-48 0-42	8N74105	1-58 1-23
			8N7423	0-40 0-41	8N74107	0-43 0-38
			8N7425	0-48 0-42	8N74109	1-08 0-98
			8N7426	0-32 0-28	8N74113	0-90 0-70
			8N7427	0-48 0-42	8N74111	1-57 1-28
			8N7428	0-50 0-41	8N74118	1-00 0-78
			8N7430	0-14 0-12	8N74119	1-92 1-68
			8N7432	0-42 0-36	8N74120	1-06 0-89
			8N7433	0-71 0-62	8N74121	0-43 0-38
			8N7437	0-52 0-45	8N74122	0-52 0-47
			8N7438	0-52 0-45	8N74123	0-90 0-89
			8N7439	0-52 0-45	8N74128	0-90 0-70
			8N7440	0-20 0-18	8N74141	0-90 0-80
			8N7441AN		8N74145	0-90 0-80
					8N74150	1-19 1-08
					8N74151	1-10 0-92
					8N7442	0-79 0-63
					8N7443	1-04 0-88
					8N7444	1-04 0-88
					8N7445	1-85 1-70
					8N7446	1-00 0-90
					8N7447	1-30 1-20
					8N7448	1-04 0-92
					8N7449	Price to be announced
					8N7450	0-20 0-18
					8N7451	0-20 0-18
					8N7452	0-20 0-18
					8N7453	0-20 0-18
					8N7454	0-20 0-18
					8N7455	0-20 0-18
					8N7456	0-20 0-18
					8N7457	0-20 0-18
					8N7458	0-20 0-18
					8N7459	0-20 0-18
					8N7460	0-20 0-18
					8N7470	0-20 0-22
					8N7472	0-30 0-25
					8N7473	0-40 0-34
					8N7474	0-40 0-34
					8N7475	0-45 0-35
					8N7476	0-44 0-39
					8N7480	0-70 0-65
					8N7481	1-25 1-07
					8N7482	0-87 0-81
					8N7483	0-96 0-71
					8N7484	0-95 0-85
					8N7485	2-60 2-30
					8N7486	0-33 0-28
					8N7487	12-40 11-80
					8N7488	0-97 0-80
					8N7489	0-75 0-70
					8N7491	1-00 0-80
					8N7492	0-75 0-70
					8N7493	0-75 0-70
					8N7494	0-80 0-74
					8N7495	0-80 0-75
					8N74167	14-08 12-88
					8N74170	4-18 3-55
					8N74174	2-00 1-74
					8N74175	1-35 1-17
					8N74176	1-30 1-10
					8N74178	1-80 1-58
					8N74179	1-70 1-58
					8N74180	1-37 1-20
					8N74181	5-50 4-75
					8N74182	1-48 1-34
					8N74183	1-95 1-75
					8N74184	2-26 2-04
					8N74185	1-70 1-50
					8N74186	2-00 1-80
					8N74187	2-00 1-80
					8N74188	2-00 1-80
					8N74189	2-00 1-80
					8N74190	1-80 1-68
					8N74191	1-80 1-68
					8N74192	1-80 1-68
					8N74193	1-80 1-68
					8N74194	2-00 1-78
					8N74195	2-00 1-78
					8N74196	2-00 1-78
					8N74286	2-00 1-78
					8N74287	

LARGEST STOCKS WIDEST RANGE SEMICONDUCTORS & COMPONENTS BRAND NEW GUARANTEED

TRANSISTORS

2G301	15p	2N2923	12p	2N4930	£2-20	AF115	24p	BC301	34p	BF250	15p
2G302	15p	2N2924	12p	2N4931	£2-20	AF116	23p	BC302	27p	BF257	15p
2G303	20p	2N2925	12p	2N5172	8p	AF117	20p	BC303	60p	BF258	46p
2G306	30p	2N2926	12p	2N5173	8p	AF118	50p	BC304	43p	BF259	46p
2G309	30p	" Green	10p	2N5174	25p	AF119	12p	BC307	9p	BF261	23p
2G344A	25p	" Yellow	10p	2N5176	25p	AF124	45p	BC307A	9p	BF264	23p
2G345B	25p	" Orange	10p	2N5245	45p	AF125	20p	BC307V1	14p	BF270	25p
2G371	15p	2N3053	15p	2N5190	92p	AF126	18p	BC308	8p	BF271	21p
2G374	15p	2N3054	45p	2N5191	92p	AF127	20p	BC308A	8p	BF272	21p
2G381	22p	2N3055	50p	2N5192	£1-24	AF130	30p	BC308B	8p	BF273	25p
2G417	20p	2N3080	20p	2N5193	£1-24	AF139	25p	BC309	9p	BF274	25p
2N109	40p	2N3391	20p	2N5194	£1-10	AF172	25p	BC309A	9p	BF457	46p
2N174	£1-40	2N3391A	22p	2N5195	£1-40	AF175	42p	BC309B	9p	BF458	57p
2N176	75p	2N3392	13p	2N5245	43p	AF179	45p	BC313	30p	BF459	57p
2N274	75p	2N3393	13p	2N5457	30p	AF180	50p	BC327	21p	BF821	£2-10
2N335	75p	2N3394	12p	2N5458	33p	AF186	40p	BC328	18p	BFS21A	£2-30
2N351	90p	2N3402	17p	2N5459	33p	AF200	35p	BC337	17p	BFS28	22p
2N376	75p	2N3403	17p	3N128	63p	AF239	38p	BC338	17p	BF861	27p
2N384	93p	2N3407	15p	3N136	£1-37	AF240	63p	BC339	27p	BF898	81p
2N388A	40p	2N3405	27p	3N139	£1-46	AF279	47p	BCY31	30p	BFW10	61p
2N404	40p	2N3414	10p	3N140	76p	AF280	47p	BCY32	50p	BFW11	61p
2N456	75p	2N3415	10p	3N141	69p	AFY42	65p	BCY33	25p	BFW15	75p
2N466A	75p	2N3416	15p	3N142	54p	AFY211	55p	BCY34	20p	BFX13	23p
2N467A	80p	2N3417	21p	3N143	64p	AL102	75p	BCY38	40p	BFX29	25p
2N491	£2-80	2N3370	£1-26	3N152	79p	AL103	70p	BCY39	60p	BFX30	25p
2N584	26p	2N3407	15p	3N136	£1-37	AF240	63p	BCY42	50p	BFX37	30p
2N591	34p	2N3472	97p	3N154	74p	ASV27	80p	BCY42	50p	BFX44	30p
2N696	15p	2N3702	10p	3N159	£1-45	ASV28	25p	BCY43	15p	BFX63	23p
2N697	15p	2N3703	10p	3N187	£1-30	ASV29	27p	BCY66	18p	BFX68	30p
2N698	20p	2N3704	10p	3N200	£2-07	ASV20	20p	BCY69	19p	BFX84	24p
2N699	20p	2N3705	10p	3N201	£1-05	ASV55	35p	BCY66	62p	BFX85	24p
2N706	20p	2N3706	90p			AS221	51p	BCY67	58p	BFX86	24p
2N706A	20p	2N3707	90p			BCY29	£1-35	BCY70	13p	BFX87	25p
2N708	18p	2N3708	70p			BC107	10p	BCY71	15p	BFX88	25p
2N709	38p	2N3709	90p			BC108	10p	BCY72	13p	BFX89	25p
2N711	20p	2N3710	90p	40050	50p	BC109	10p	BCY87	£3-47	BFY10	35p
2N718A	21p	2N3711	90p	40051	55p	BC113	10p	BCY88	£2-40	BFY11	35p
2N720	30p	2N3712	90p	40399	90p	BC114	12p	BCY89	80p	BFY17	90p
2N721	30p	2N3713	£1-08	40310	37p	BC115	15p	BCZ10	27p	BFY18	25p
2N722	50p	2N3714	£1-18	40360	35p	BC116	15p	BCZ11	40p	BFY19	25p
2N914	15p	2N3715	£1-23	40361	37p	BC118A	18p	BD115	75p	BFY22	60p
2N916	17p	2N3716	£1-30	40362	40p	BC117	20p	BD116	75p	BFY29	60p
2N918	30p	2N3773	£2-35	40363	61p	BC118	11p	BD121	65p	BFY37	20p
2N919	20p	2N3774	£2-33	40389	37p	BC119	27p	BD123	80p	BFY41	43p
2N929	14p	2N3775	£2-19	40394	59p	BC121	20p	BD124	60p	BFY43	62p
2N930	25p	2N3776	£2-95	40395	55p	BC123	25p	BD130	50p	BFY50	16p
2N1090	25p	2N3777	£2-84	40406	40p	BD131	15p	BD131	75p	BFY51	16p
2N1091	24p	2N3778	£2-25	40407	31p	BC126	20p	BD132	75p	BFY52	16p
2N1131	20p	2N3779	£2-15	40408	31p	BC132	30p	BD135	38p	BFY53	15p
2N1132	20p	2N3780	£2-50	40409	49p	BC134	11p	BD136	44p	BFY56	34p
2N1184	£1-27	2N3781	£2-67	40410	53p	BC135	11p	BD137	47p	BFY64	41p
2N1302	16p	2N3782	£2-37	40411	£1-40	BC136	15p	BD138	52p	BFY75	40p
2N1303	15p	2N3783	£1-76	40467A	57p	BC137	15p	BD139	66p	BFY76	22p
2N1304	20p	2N3790	£1-60	40468A	57p	BC138	20p	BD140	75p	BFY77	24p
2N1305	20p	2N3791	£2-06	40600	57p	BC140	30p	BDY10	£1-25	BFY78	24p
2N1306	22p	2N3792	£2-20	40601	55p	BC141	34p	BDY11	£1-50	BFY90	55p
2N1307	22p	2N3794	10p	40602	40p	BC142	18p	BDY17	£1-50	ERY39	30p
2N1308	25p	2N3819	20p	40603	49p	BC143	21p	BDY18	£1-75	BSX19	13p
2N1309	25p	2N3820	47p	40604	45p	BC144	24p	BDY19	£1-97	BSX20	14p
2N1483	90p	2N3823	50p	40636	33p	BC145	21p	BDY20	75p	BSX21	20p
2N1507	24p	2N3824	75p	40673	60p	BC146	15p	BDY28	55p	BSX22	20p
2N1613	20p	2N3826	23p	AC107	30p	BC148	9p	BDY60	90p	BSX26	34p
2N1631	35p	2N3854	10p	AC113	10p	BC149	10p	BDY61	95p	BSX27	34p
2N1637	30p	2N3854A	10p	AC115	10p	BC153	10p	BDY62	75p	BSX28	25p
2N1638	87p	2N3855	10p	AC117	20p	BC154	10p	BF115	23p	BSX29	47p
2N1671	15p	2N3856A	10p	AC121	11p	BC157	9p	BD117	43p	BSX30	88p
2N1701	£1-10	2N3856	18p	AC126	20p	BC158	10p	BF119	55p	BSX35	54p
2N1702	£2-15	2N3856A	18p	AC127	20p	BC159	10p	BF121	25p	BSX60	60p
2N1711	17p	2N3858	18p	AC128	20p	BC160	11p	BF123	27p	BSX61	61p
2N1893	34p	2N3858A	10p	AC141K	30p	BC167B	11p	BF125	25p	BSX76	15p
2N2102	10p	2N3859	16p	AC142K	26p	BC168B	10p	BF127	27p	BSX77	20p
2N2147	70p	2N3859A	15p	AC151V	12p	BC169C	10p	BF152	20p	BSX78	25p
2N2148	60p	2N3860	15p	AC152V	11p	BC169B	10p	BF153	28p	BSW70	28p
2N2192	40p	2N3866	70p	AC153	18p	BC169C	10p	BF154	20p	BSY24	20p
2N2192A	40p	2N3877	25p	AC153K	22p	BC170	11p	BF158	15p	BSY25	15p
2N2193	40p	2N3877A	20p	AC154	20p	BC171	13p	BF159	27p	BSY26	15p
2N2193A	42p	2N3878	£1-22	AC176	16p	BC172	11p	BF160	28p	BSY27	15p
2N2194	27p	2N3879	£1-91	AC176K	17p	BC182	10p	BF161	35p	BSY28	15p
2N2194A	30p	2N3880	20p	AC182V	15p	BC183K	9p	BF163	30p	BSY38	15p
2N2195	37p	2N3900A	21p	AC188K	23p	BC183	13p	BF166	15p	BSY39	15p
2N2195A	18p	2N3901	32p	ACY17	25p	BC183L	9p	BF167	18p	BSY51	25p
2N2218A	18p	2N3903	20p	ACY18	16p	BC184	11p	BF173	10p	BSY62	25p
2N2219	80p	2N3904	17p	ACY19	20p	BC184L	11p	BF177	25p	BSY63	25p
2N2219A	80p	2N3905	21p	ACY20	20p	BC186	25p	BF178	25p	HSY64	30p
2N2220	80p	2N3906	20p	ACY21	18p	BC187	25p	BF179	30p	BSY66	79p
2N2221	80p	2N4036	40p	ACY22	10p	BC204	11p	BF180	35p	BSY65	15p
2N2221A	25p	2N4037	85p	ACY28	17p	BC205	10p	BF181	32p	BSY78	61p
2N2222	20p	2N4058	12p	ACY30	42p	BC206	11p	BF182	30p	BSY79	40p
2N2222A	25p	2N4059	90p	ACY39	47p	BC207	10p	BF183	40p	BSY790	45p
2N2368	11p	2N4060	11p	ACY40	17p	BC208	9p	BF184	17p	BSY95A	9p
2N2369	12p	2N4061	11p	ACY41	15p	BC209	10p	BF185	17p	BU104	£1-42
2N2369A	13p	2N4062	11p	ACY44	25p	BC219	80p	BF194	14p	BU105	36p
2N2646	41p	2N4302	25p	AD135V	84p	BC212K	10p	BF195	15p	C407	18p
2N2647	£1-20	2N4303	35p	AD140	49p	BC212L	18p	BF196	15p	C424	18p
2N2711	12p	2N4913	80p	AD142	50p	BC214L	14p	BF197	15p	C425	18p
2N2712	12p	2N4914	87p	AD143	45p	BC236	10p	BF198	15p	C426	25p
2N2713	17p	2N4915	96p	AD149V	50p	BC237	8p	BF199	18p	C428	25p
2N2714	17p	2N4917	17p	AD150	£1-23	BC238	9p	BF200	35p	C444	25p
2N2904	18p	2N4918	60p	AD161	35p	BC251	20p	BF224J	14p	D40N1	55p
2N2904A	25p	2N4919	58p	AD162	35p	BC252	18p	BF225J	19p	D40N3	62p
2N2905	25p	2N4920	60p	AD161 PR	BC253	23p	BF237	22p	GET111	45p	
2N2905A	23p	2N4921	50p	AD162 J	60p	BC257	8p	BF238	22p	GET113	40p
2N2906	18p	2N4922	55p	ADZ11	£1-50	BC258	11p	BF244	14p	GET114	20p
2N2906A	23p	2N4923	60p	ADZ12	£1-75	BC259	11p	BF245	33p	GET115	20p
2N2907	18p	2N4927	£1	AF106	24p	BC262	18p	BF246	43p	GET119	35p
2N2907A	25p	2N4928	£1-80	AF109R	35p	BC263	23p	BF247	49p	GET120	25p
2N2913	75p	2N4929	£2-23	AF114	25p	BC300	24p	BF254	14p	GET536	20p

D.C. PANEL METERS

MR38 SERIES—FACE SIZE 42 x 42mm. ALL PRICES FOR 1-9 PIECES.
 50µA, £2.00; 100µA, £1.87;

FREE VEROBOARD INSIDE
RADIO & ELECTRONICS
CONSTRUCTOR 20p
 Vol. 26 No 3
 OCTOBER 1972



FREE VEROBOARD
IN OCTOBER ISSUE
LOOK FOR THIS COVER
ON SALE NOW

PROJECT 1
 SIGNAL INJECTOR

Very suitable for beginners—consists of a wide-band signal injector which is capable of injecting an amplitude modulated signal into any medium and long wave receiver having a ferrite rod aerial—a useful and inexpensive item of test equipment.

PROJECT 2
 RADIO 2 TUNER

A fairly complex assembly making full use of the connection points on the Veroboard. A pre-tuned Radio 2 Tuner incorporating two transistors. Current consumption from the 9 volt battery is of the order of 2mA only.

PROJECT 3
 INTEGRATED
 CIRCUIT
 AMPLIFIER

Designed around the readily available R.C.A. CA3020 i.c., this a.f. amplifier offers a high level of performance and relatively few components are needed—output in excess of 300mW, input impedance 50k Ω .

Copies may also be obtained direct from the Publishers, 26p, including postage. Published by Data Publications Ltd. 57 Maida Vale, London W.9.

Buy NOW and be sure of your copy—PRICE 20p

introducing

ARROW ELECTRONICS LTD. 

“Service the way it ought to be!”

an associate Company of LST ELECTRONIC COMPONENTS LTD

When it comes to retail distribution we're head and shoulders above the rest!

We're a new Company but our experience and ability in electronic components goes back a long way

Here at Arrow Electronics fast, reliable service is law!

We offer a rapid, same day turn round on all mail received up to 3 pm on any given weekday.

What's more, when we promise to clear all orders on receipt, we really mean it!

Our no fuss, no bother ordering system is a joy to behold. We'll give you all the forms and envelopes you could possibly need. Combine them with our simple Catalogue Coding and hey presto, you can order and order, time and time again without the slightest error or mistake.

You'll always be up to date with us—we're continually adding to our high quality stock range and always up dating our catalogue.

Get to know us and you'll soon raise your hat to our customer discount—it's tops with a total order value discount of 10% on orders exceeding £4.00.

Now's your chance to get to know us better. Our brand new Catalogue is now awaiting you, hot from the presses!

The New Arrow catalogue features the following:-

- Extended Ranges of Bridge Rectifiers
 - Capacitors
 - Interference Suppression Kits
 - Low Cost Integrated Circuit Mounting Pins
 - Knobs
 - Light Emitting Diodes
 - A Novel Logic Testing Instrument giving immediate visual indication
 - Magneto Resistors
 - Optically Coupled Isolators
 - Extended Range of Potentiometers
 - Medium current and High current Rectifiers
 - Temperature controlled Soldering Irons
 - Extended Range of Thyristors
- and many other items of great interest to the home constructor.

Arrow Electronics Limited
 Dept. PE3,
 7 Coptfold Road
 Brentwood Essex
 Tel: Brentwood 219435


Shoot me your catalogue

I enclose PO/Cheque for 10p.
 Name
 Address
PE3.



"Where can I get exclusive units at lowest prices?..."

ROC ELECTRONICS!

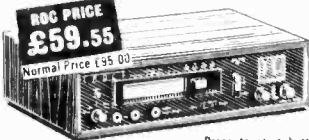

ROC PRICE
£59.55
Normal Price £85.00

8-TRACK STEREO CARTRIDGE TAPE DECK MODEL RP-1000ST
The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual override.

Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in pre-amp. Tape speed 3 1/2 ips (9.5 cms). Frequency response, playback 30-10,000 Hz; recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect on a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 9" deep. Cabinet in walnut. Including connecting leads.

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls - magnetic phono (high/low) tuner, aux, mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz ± 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA, tuner/aux 250mV. Hum and noise: phono - 50db, tuner/aux - 65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.



As reviewed in "POPULAR HI-FI" February 1972

ROC PRICE
£35.20
Normal Price £55.50



ROC PRICE
£31.20
Normal Price £50.00

OLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as its good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz, AM: 525-1605 kHz. FM Sensitivity: FM, 3µV, AM, 250µV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size 11 1/2" wide, 4" high, 7 1/2" deep.



ROC PRICE
£12.45
Normal Price £21.00

REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide x 3" high x 5 1/2" deep. And yet it has separate gated volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/headphone and power on/off slide switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz ± 3 db. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.



EAGLE LC.05 STEREO MAGNETIC CARTRIDGE

For fabulous reproduction at a very low price, you'll find it hard to beat. 0.7 mil diamond stylus. Output: 6mV per channel. Frequency range: 30-18,000 Hz. Channel balance: ± 1.5 db. Channel separation: 20dB. Recommended stylus pressure: 2-4 grams. Compliance: 9 x 10⁻⁶ cm/dyne. **ROC PRICE** £4.75



EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE

Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: ± 1 db. Channel separation: 28dB. Compliance: 12 x 10⁻⁶ cm/dyne. **ROC PRICE** £6.37



ROC PRICE
£24.10
Normal Price £39.80

OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3 db. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3mV RIAA, crystal phono 100mV, tape 160mV, tuner 160mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well - sounds even better!



ROC PRICE
£28.00
Normal Price £30.70

A-3000 36-WATT SOLID STATE STEREO AMPLIFIER

The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (± 2 db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux. Tape Play. Size: 345mm x 300mm x 130mm.



ROC PRICE
£10.50
Normal Price £15.70

OLSON AM-3574-WATT STEREO AMPLIFIER

Here's a marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for tuntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3 db. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV, tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.

25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-56



ROC PRICE
£27.25
Normal Price £39.95 each.

This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units an 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s. into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.

CONSTRUCTORS' KITS

CRYSTAL RADIO KIT
Complete with earpiece
£1.50

TWO TRANSISTOR RADIO KIT
Complete with solar cell
£2.50

10 PROJECT INTEGRATED CIRCUIT KIT
Build a radio, Morse key, etc.
£3.50

SOLAR ELECTRONIC KIT
20 ways of harnessing the sun's energy
£4.50

TWO OCTAVE ELECTRONIC ORGAN KIT
Make your own music. Complete with speaker
£4.50

LIMITED STOCKS BUY NOW FOR XMAS!



ROC PRICE
£27.55
Normal Price £42.00

PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-18

This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to 'Stereo'! The SSA-18 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz, AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3 db. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.



ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317

This exclusive ROC Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 6 1/2" deep. It contains its own mains power supply and has a gated volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz ± 3 db; output 3.5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise ratio better than 45dB.


ROC PRICE
£5.50
Normal Price £7.75



R.446 3-WAY MATCHED SPEAKERS

These will do justice to your amplifier - and to your pocket. At only £16.40 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.

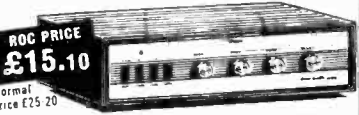ROC PRICE
£17.80
Normal Price £25.00 per pair.



ROC PRICE
£15.10
Normal Price £25.20

OLSON AM-372 18-WATT STEREO AMPLIFIER

Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3 db. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

ROC ELECTRONICS LTD


N. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211

CALLERS WELCOME 9-6 MON. TO SAT.

ALSO AT 87 TOTTENHAM COURT RD. LONDON W1

TEL: 01-580 3739 OPEN 9-6 MON.-FRI. SAT. 9-1

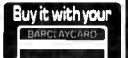Return-of-post mail order service. Orders over £10 post free (UK only). Add 25p for postage to orders under £10. HP terms available for callers



VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50 60 OUTPUT VARIABLE 0-260V

All Types from 1 to 50 amp from stock.

SHROUDED TYPE

1 amp, £7.00	20 amp, £49.00
2.5 amp, £8.05	25 amp, £58.00
5 amp, £11.75	37.5 amp, £82.00
10 amp, £22.50	50 amp, £98.00
15 amp, £25.00	

(Panel Mounting) 1 amp, £4.75, 2.5 amp, £4.75, 5 amp, £7.00, 10 amp, £11.75, 15 amp, £15.00. All carriage paid.



L.T. TRANSFORMERS

All primaries 220-240V	Type No.	Sec. Taps	Price	Car.
1 30, 32, 34, 36V at 5A	44-68	45p		
2 30, 40, 50V at 5A	46-88	45p		
3 10, 17, 18V at 10A	44-95	45p		
4 6, 12V at 20A	46-43	45p		
5 17, 18, 20V at 20A	47-28	55p		
6 6, 12, 20V at 20A	46-88	55p		
7 24V at 10A	45-23	45p		
8 4, 6, 24, 32V at 12A	47-15	45p		
9, 6 and 12V at 10A	43-75	45p		

DOUBLE ENDED BLOWER UNIT

Powerful, continuously rated, 2-speed. Blades easily removable. Either 6 or 12 volt D.C. operation. PRICE £1.75. P. & P. 25p.



12 VOLT D.C. MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train (removable) giving approx. final speed of either 125 r.p.m. or 240 r.p.m. Size: 4 1/2 x 2 1/2 in. dia. Either type price 95p incl. post.




CONSTANT SPEED. PRECISION MADE 6 VOLT D.C. GOVERNED MOTOR

Seven pole armature, ballrace bearing. 2,750 r.p.m. Length 2 1/2 in. Dia. 1 1/2 in. Shaft length 1 1/2 in. Shaft dia. 5/64 in. No load 40 mA. Normal load 350 mA. Ideal for portable recorders, etc., etc. PRICE £1.25 P. & P. 10p.



PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

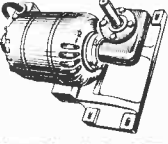30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of maker's price. £6.30. P. & P. 50p.



PARVALUX Type: SD1.S/86896/OJ

230/250V A.C. 50 r.p.m. 7 lb. ins. Continuously rated. Less base. £6. P. & P. 30p.
TYPE: SD1.S/89400/OM
230/250V A.C. 50 r.p.m. 22 lb. ins. Continuously rated. Incl. base. £7. P. & P. 30p.
The above motors are new and unused.



PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £1.75. P. & P. 25p.



600 WATT DIMMER SWITCH.

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3 incl. P. & P.

24-HOUR TIMER

Can be adjusted to give a switching delay of between 1/2 hr. to 24 hrs. Driven by 200/250V A.C. synchronous motor. 15 amp c/o contacts. Mfg. Crater Controls Ltd. Supplied with scale calibrated 0-10 (2 hrs. per division). Brand New. £1.75. P. & P. 25p.



LIGHT SENSITIVE SWITCHES

Kit includes ORP.12 Photocell, Relay Transistor Circuit. For 6 or 12V D.C. operation. Price £1.50 plus 12p P. & P. ORP. 12 and Circuit 63p post paid. 220/240V A.C. MAINS MODEL
Mains transformer, rectifier, relay, 1 make H.D. contacts. price incl. circuit £2.65. P. & P. 20p.



230V A.C. SOLENOID

Extremely powerful with approx. 14lb pull, 1in travel. Fitted with mounting feet. Size: 4in long, 2 1/2in wide, 3in high. £2.00 incl. P. & P.



230-250 VOLT A.C. SOLENOID

Manufactured by Westool Ltd. (similar in appearance to above illustration). Approx. 1 1/2lb pull. Feet size 1 1/2 in. Price 85p incl. P. & P.

18-24 VOLT D.C. SOLENOID

Size: O.A.L. 3 1/2 in. 1 1/2 in. Max. push 3 1/2 lb. incl. approx. PRICE: 75p incl. P. & P.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.30, plus 25p P. & P.

NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Roller in printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.

HY-LYGT STROBE MK III
Designed and produced for use in large rooms, halls and the photographic field and utilises a silica tube, printed circuit also a special trigger coil. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12.00. P. & P. 50p. **SPECIALY DESIGNED. THE 'SUPER' HY-LYGT KIT**

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:
● Heavy duty power supply
● Variable speed from 1-23 flash per sec.
● Reactor control circuit producing an intense white light.

Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P. **ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE** specially designed for the Super Hy-Lyght Kit including reflector. £7.00. P. & P. 45p.

For Hy-Lyght Kit including reflector. £4.00. **7-INCH POLISHED REFLECTOR**
Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

6 INCH COLOUR WHEEL

As used for disco lighting effects, etc. £5.75 incl. P. & P. can be operated from our one r.p.m. synchronous motor price 75p incl. P. & P. Motor available with wheel.


INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8in, W. 4in, H. 6in, weight 6lb. 1,000V, 1,000 megohms, £34.00 carriage paid.
500V, 500 megohms, £28 incl. P. & P.



UNISELECTOR SWITCHES

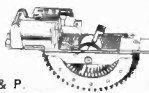NEW 4 Bank 25 Way
24V d.c. operation. £5.88. P. & P. 25p. **6 Bank 25 Way**
24V d.c. £6.50. P. & P. 25p.
8 Bank 25 Way, 24V d.c. operation. £7.62 plus 25p. P. & P.



VENNER ELECTRIC TIME SWITCH

200/250V Ex. GPO
Tested. Manually set on, 2 off every 24h. Override switch: 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk. OFF dawn. Price as above.



PROGRAMME TIMERS

240V A.C. 5 r.p.m. motor. 2 models available with either 10 cams or 15 cams. Each cam operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. **NEW 10 cam £4.75 P. & P. 25p. 15 cam £5.75 P. & P. 25p.**

2 CAM PROGRAMMER
Crouzet 15 r.p.m. 240V. A.C. motor, drives 2 individually adjustable cams. Each cam operates 2 c/o micro switches. Mfg. Honeywell. £1.75 P. & P. 20p.

MOTOROLA MAC II/6 PLASTIC TRIAC 400 PIV. 10 AMP
Now available **EX STOCK**. Supplied with full data and applications sheets. Price £1.05. P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

Superior Quality Precision Made

NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230 mA; 2.5 kΩ, 2A; 3.5 kΩ, 140 mA. Diameter 3 1/2 in. Shaft length 3/4 in. dia. 1/8 in. All at £1.65 each. P. & P. 75p.
50 WATT. 1/5/10/25/50/100/250/500/1/1 1/2-5/3/5kΩ. All at £1.15 each. P. & P. 75p.
25 WATT. 10/25/50/100/250/300/500/1/1 1/2-5/3/5/5kΩ. All at 90p each. P. & P. 75p.
Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia brass bush. Ideal for above Rheostats. 18p ea.

RELAYS SIEMENS, PLESSEY, Etc.

MINIATURE RELAYS

Col. (1)	1	2	3	4
Coil ohms				
Col. (2)	52	3-6	2 c/o	63p*
Working d.c. volts	67	4-8	3 c/o HD	78p*
	410	10-18	4 c/o	73p*
	600	12-24	4 c/o	73p*
	700	16-24	4M 2B	63p*
Col. 3	700	16-24	4 c/o	78p*
Contracts	700	15-35	2 c/o HD	73p*
	700	16-24	6M	65p*
Col. (4)	700	6-12	1 c/o HD	50p*
Price	700	20-30	6 c/o	75p*
	1,250	24-36	4 c/o	63p*
HD =	2,500	36-45	6M	63p*
Heavy duty	1,250	30-48	4 c/o	50p*
Incl. Base	9,000	40-70	2 c/o	50p
Post paid.	15k	85-110	6M	50p*

12 VOLT D.C. RELAY 140 ohm coil

Type 1: Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)
Type 2: One set of c/o contacts. 60p incl. P. & P.

'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. PRICE: 50p. P. & P. 10p. (100 lots £40 including P. & P.)



230 VOLT A.C. RELAYS MFG. KEY SWITCH

One set c/o contacts rated at 7.5 amps. PRICE: 40p. P. & P. 5p. (100 lots £32 incl. P. & P.)

MINIATURE LATCHING RELAY

Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size 1/2 high, 3/4 wide, 3/4 thick. Complete with 3 leads. New 73p, incl. P. & P.

ELECTRONIC ORGAN KIT


Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1.5V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3. P. & P. 22p.

50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

36V 30 AMP. A.C. or D.C. VARIABLE L.T. SUPPLY UNIT

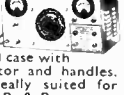INPUT 220/240V a.c. OUTPUT CONTINUOUSLY VARIABLE 0-36V
Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter, Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £68 plus £2 P. & P.



'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V A.C. Black knob 1in. Fixing hole; in. ONE bank 30p; TWO bank 40p; THREE bank 55p; incl. P. & P. Quot. for quantity.



'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. Types N39, N95, N100, N101. NEW in maker's carton. PRICE: 10p for £1.90 incl. P. & P.



Very special offer MICRO SWITCH

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 incl. post. (Min. order 20.)

D.C. AMMETERS NEW!

1A, 5A, 15A, 20A. £1.75, incl. P. & P. 0-300V a.c., £1.90, incl. P. & P.



All Mail Orders—Callers—Ample Parking
Dept. PE11, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.40. P. & P. 55p extra.

INTERCOM/BABY ALARM



£3.35

Same as 4-station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. 25p.

Transistor TELEPHONE AMPLIFIER



£2.99

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephonic messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE 1)
169 KENSINGTON HIGH STREET, LONDON, W.8

AN EXCITING MAGAZINE BRINGING A FASCINATING HOBBY TO EVERYONE

Projects easy to construct
Theory simply explained

EVERYDAY ELECTRONICS

Yes, this exciting magazine will give you all the know how needed to make electronic gadgets for your home, car and other hobby applications. Just follow the easy, step-by-step illustrated constructional details and articles on techniques and theory!

ONLY 15p MONTHLY Place a regular order now!

EX COMPUTER PRINTED CIRCUIT PANELS
2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4-OC28) 50p. P. & P. 6p.

9 OAS, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded-on panels 13in x 4in. 4 for £1. P. & P. 25p.

709C OPERATIONAL AMPLIFIER T05
8 lead I.C. 1 off 50p. 50 off 35p. 100 off 20p.

250 MIXED RESISTORS 62p
i & j watt.

150 MIXED HI STABS 62p
i, j & k watt 5% or better.

QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

GPO EXTENSION TELEPHONES
with dial but without bell. 95p each. P. & P. 30p. £1.76 for 2. P. & P. 30p.

BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2.5kΩ coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
44 EARLS COURT ROAD
LONDON, W.8 01-478 8499

OSMABET LTD. We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS

Prim. 200/240V a.c., 6.3V, 1.5A, 85p; 3A, £1.18; 6A CT, £1.80; 12V, 1.5A £1.13; 3A CT, £1.80; 6A CT, £2.70; 18V, 1.5A, £1.60; 24V 1.5A CT, £1.80; 3A CT, £2.70; 5A, £3.75; 8A, £6; 12A, £9; 40V 3A CT, £3.45; 50V 6A CT, £9.75.

MIDGET RECTIFIER TRANSFORMERS

For FW rec.; Prim. 200/240V a.c. Output, 9-0-9V, 0.3A; 12-0-12V, 0.25A; 20-0-20V, 0.15A; £1.20 each. 9-0-9V, 1A, 98p; 12-0-12V, 1A; 20-0-20V, 0.75A, £1.20 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS

P.P. sec. tapped, 3-7.5-15 ohms, A-A 6.8kΩ, 30W (KT66, etc.), £4.05; A-A 3kΩ, 50W, £6.75; A-A, K Q (EL34, KT88, etc.) 100W, £11.40.

MAINS TRANSFORMERS FOR POWER AMPLIFIERS

Prim. 200/240V a.c. TX6, sec. 425-0-425V 500mA, 6.3V 6A CT, 6.3V 6A CT, 0-5-6.3V 3A, £12.76; TX1 sec. 425-0-425V 2500mA, 6.3V 4A CT, 6.3V 4A CT, 0-5-6.3V 3A, £7.50.

Full transformer lists S.A.E.

LOUDSPEAKERS FOR POWER AMPLIFIERS

FANE 15W with tweeter, £4.99; 50W, £10.90; 60W, £12.90; 100W, £22.50. Baker 25W, £6.40; 35W, £7.20; 50W, £16.20; E.M.I. 13j x 8in, £2.25.

LOUDSPEAKERS

5in 3-15 or 25Ω, 5 - 3in 3, 8, 15 or 25Ω, £1.05; 6 x 4in 8 or 25Ω, 7 - 4in or 15Ω, 6in 3Ω, £1.25; 8 x 5in 3, 8, 15 or 25Ω, £1.50; 10 - 6in 2Ω, £2.

SPEAKER AUTO MATCHING TRANSFORMERS

12W 3 to 8 or 15Ω, up or down, 75p. P. & P. 15p.

G.E.C. MANUAL OF POWER AMPLIFIERS

Covering valve amplifiers of 30 to 400 watts, with price list of transformers and chokes specified, 30p. Bernard's Amplifier Manual, 5 to 1,000 watts, 75p. Practical Stereo Handbook, 30p. Transistor Audio Designs, tables, data, etc., etc., 40p. Sound and Loudspeaker Manual, 93 pp, a must for all P.A. workers. Speaker grouping, networks, etc., 50p.

BULK TAPE ERASERS

Instant erasure, tape spools and cassettes, demagnetizes tape heads, 200/240V a.c., £2.40 plus 25p post.

MAINS SIGNAL LAMPHOLDER

Bulgin, new, Type D20 for SBC lamp. 1in dia. lens clear glass, 20p, 10 for £1.

S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8TG
Carriage extra all orders. Tel.: 01-958 9314

MULTI MINI VICE AND STAND

£5.90
26p P. & P.



This unique all purpose vice is just like a 'third hand' countless uses for the electronics enthusiast—assembly, soldering, gluing, wiring, drilling, etc. Firm base, positive grip for all shapes of work, with independently adjustable twin jaws.

Truly a precision made bargain.

Also single jaw model £3.37 (22p P. & P.)

FREEBORN LTD. (Dept. PE11)
Beechfield House • West Bar
Banbury • Oxon

Eliminators



9 volt @ 20mA (PP3)	£1.25
6 volt @ 50mA	£1.50
9 volt @ 50mA	£1.50
6 + 6 volt, 50mA	£2.50
9 + 9 volt, 50mA	£2.50
7½ volt for cassette recorders	£2.00
6, 7½ or 9 volt	£3.00
3, 4½, 6, 7½, 9, 12 @ 500mA	£3.99
Car Battery Converter fully stabilised to provide 6, 7½ or 9 volts (rated)	£4.99
(p. & p. 15p. on all types)	

DIL Sockets




14 and 16 pin

16p

(including ZIG-ZAG)

THE TEXAN

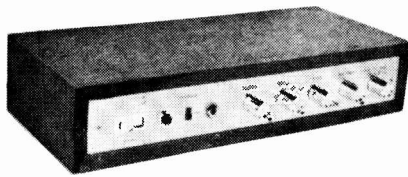

Complete Kit (inc. Test Case) **£28.50** 66p 45p

20 Watts per channel integrated stereo amplifier developed by engineers of Texas Instruments Ltd. This designer approved kit, has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 Hz - 3dB. The semiconductor complement of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistors, 4 rectifiers and 2 zeners. Controls include: bass; treble; volume; balance; on/off; 'on' indicator; headphone sockets, scratch filter; rumble filter; inputs for magnetic phono; tuner; aux or tape; tape head etc. input, selector; mono/stereo switch. The construction of this kit was featured in 'Practical Wireless' May - Aug. 1972

Veroboard

	Copperclad	Plain
	0.1"	0.15"
2½" x 1"	6p	6p
2½" x 3½"	20p	16p (9)
2½" x 5"	24p	21p (7)
3½" x 3½"	24p	21p (8)
3½" x 5"	27p	27p (10)
17" x 2½"	67p	50p
17" x 3½"	90p	70p
17" x 5"	-	75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2½"	5½"	1½"	35p	8p
(8)	4"	4"	1½"	35p	8p
(9)	4"	2½"	1½"	35p	8p
(10)	4"	5½"	1½"	40p	8p
11	4"	2½"	2"	35p	8p
12	3"	2"	1"	32p	9p
13	6"	4"	2"	50p	10p
14	7"	5"	2½"	58p	12p
15	8"	6"	3"	75p	18p
16	10"	7"	3"	85p	20p

Resistors

½ watt 5% Carbon Film - low noise Hi-Stabs All E24 values 1p. each plus p. & p. 7p. for up to 50 Resistors and a further 2p for each additional 50. Deduct 33 1/3% for 100 of one type or 25% for mixed orders over £1 in value.

1 watt	10% Carbon Composition	3p. each
2 watt	10% Carbon Composition	6p. each
2½ w	5% Wire wound	9p. each
5 W	Wire wound	9p. each
10 W	Wire wound	10p. each

plus p. & p. 7p. for up to 25 resistors plus 1p. for each additional 25.

Semiconductors


AC107	25p	AF239	30p	BF197	15p	2N1304	22p	AA120	9p
AC126	17p	BC107	10p	BU105	£2	2N1893	30p	AA129	9p
AC127	15p	BC108	10p	MPE102	40p	2N2926	10p	BA100	15p
AC128	15p	BC109	10p	MPE103	37p	2N3053	23p	BA154	13p
AC176	20p	BC147	10p	MPE104	37p	2N3055	49p	BA155	14p
AC187	25p	BC148	10p	MPE105	40p	2N3702	12p	BA156	15p
AC187K	25p	BC149	10p	MPE106	45p	2N3704	17p	OA47	10p
AC188	25p	BC157	12p	OC28	40p	2N3819	35p	OA79	9p
AC188K	25p	BC158	10p	OC35	40p	IN914	6p	OA81	7p
AD140	40p	BC159	12p	OC44	15p	IN4148	6p	OA90	7p
AD149	40p	BC169	15p	OC45	15p	IN4001	6p	OA91	7p
AD161	60p	BF180	25p	OC71	11p	IN4002	7p	OA200	10p
AD162	60p	BF181	30p	OC72	17p	IN4003	8p	OA202	10p
AF114	18p	BF184	25p	OC170	23p	IN4004	8p	SL403D	£1.50
AF115	18p	BF185	25p	OC171	30p	IN4005	10p	µA709C	45p
AF116	18p	BF194	15p	2N697	18p	IN4006	12p	µA710	45p
AF117	18p	BF195	15p	2N706	12p	IN4007	15p	µA741C	50p
AF119	28p	BF196	15p	2N708	15p	AA119	9p	µA723C	£1.05

Thermistors



RS3	£1.32
VA1005	15p
VA1026	13p
VA1033	13p
CZ1	15p
CZ4	13p
CZ13A	13p
GL16	£1.00
GL23	£1.00
A15B	75p

Heat Sinks

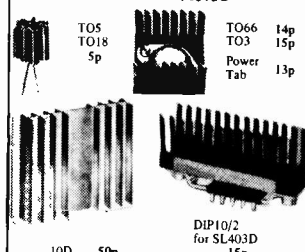

CHROMASONIC electronics

Capacitors

Mylar

- 100V

1000pf	2p	0.04µF	3p
2000pf	2p	0.05µF	3p
5000pf	2p	0.068µF	4p
0.01µF	3p	0.1µF	4p
0.02µF	3p	0.2µF	5p

Polystyrene - 160V

10pf to 10,000pf all 3p. each in multiples of 10, 15, 22, 33, 47 & 68.

Mullard C280 - 250V

0.01µF	3p	0.22µF	5p
0.015µF	3p	0.33µF	6p
0.022µF	3p	0.47µF	8p
0.033µF	3p	0.68µF	11p
0.047µF	3p	1µF	13p
0.068µF	3p	1.5µF	20p
0.1µF	4p	2.2µF	24p
0.15µF	4p		

Mullard C281 - 400V

0.01µF	4½p	0.1µF	7p
0.015µF	4½p	0.15µF	8p
0.022µF	4½p	0.22µF	10p
0.033µF	5½p	0.33µF	14p
0.047µF	6p	0.47µF	15p
0.068µF	6p		


Mullard C426, 015

£016 all 6p each

Voltage	10	16	25	40	63		
2.5	4	6.4	10	16	25	40	64
Capacity µF	22	15	10	6.8	1		
	47	68	22	47	2.2		
	100	150	47	100	4.7		
	220	100	10	4.7			
		150					
10	8	6.4	4	2.5	1.6	1	0.64
40	32	25	16	10	6.4	4	2.5
80	64	50	32	20	12.5	8	5
160	125	100	64	40	25	16	10
320	250	200	125	80	50	32	20
500	400	320	200	125	80	50	32

Mullard C437 & 017

2.5	4	6.4	10	16	25	40	64
1000	800	640	400	250	160	100	64
1600	1250	1000	640	400	250	160	100
2500	2000	1600	1000	640	400	250	160
4000	3200	2500	1600	1000	640	400	250
			470				10p
			470				10p
			1500				18p

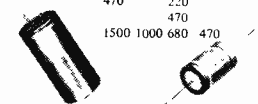

We also hold:
Mullard C333 ceramics 1.8pf - 330pf 63V. 5p
Silvered Mica 1%, 500V, 2.2pf - 820pf 7p
Feedthrough ceramic 1000pf; 350V 5p
Disc ceramics, monolithic ceramic, high voltage types; tantalums etc.

Mullard C431

10	16	25	40	64
2000	1250	800	500	320
3200	2000	1250	800	500
5000	3200	2000	1250	800
10000	6400	4000	2500	1600
16000	10000	6400	4000	2500

HT Electrolytics

1: 2; 4; 8µF	450V	14p
16µF	450V	15p
32µF	450V	20p
50µF	350V	20p

TV & Radio Types

8 + 8µF; 450 V.W	18p	32 + 32µF; 350 V.W	25p
8 + 16µF; 450 V.W	20p	32 + 32µF; 450 V.W	43p
16 + 16µF; 450 V.W	25p	50 + 50µF; 350 V.W	35p
16 + 100 + 100 + 300µF; 275 V.W	£1.23		
32 + 100 + 125 + 200µF; 275 V.W	£1.23		
32 + 100 + 200 + 200µF; 300 V.W	£1.23		
100 + 100 + 100 + 150 + 150µF; 320 V.W	£1.66		
100 + 100 + 200 + 300µF; 275 V.W	£1.23		
60 + 100 + 200µF; 300 V.W	93p		
100 + 200 + 200µF; 300 V.W	£1		
100 + 200µF; 275 V.W	75p		
100 + 400µF; 275 V.W	£1.15		
200µF; 275 V.W	50p	300 + 300µF; 300 V.W	£1.90

Potentiometers



5K Ω	50K Ω	500K Ω
10K Ω	100K Ω	1M Ω
25K Ω	250K Ω	2M Ω
log or lin less switch		12p
log or lin with switch		24p
dual less switch		40p
dual with switch 10K, 100K & 1M log only		52p
10K log + 10K antilog less switch		40p

Slider Pots

Single	Dual		
10K	10 + 10K		
25K	25 + 25K		
50K	50 + 50K		
100K	100 + 100K		
30p	50p		
Knobs	10p.		

Presets

Vertical or Horizontal					
0.1 watt	5p	0.25 watt	7p		
100	1K	10K	100K	1M	
250	2.5K	25K	250K	2.5M	
500	5K	50K	500K	5M	

MAIL ORDERS: Where no p. & p. charge is shown, a minimum of 7p. applies. P. & P. on overseas orders is charged at cost.
ADDRESS TO: Mail Order Dept.,
56, Fortis Green Road, London, N10 3HN.
TELEPHONE: 01-883 3705

Practical Electronics Classified Advertisements

RATES: 8p per word (minimum 12 words). Box No. 10p extra. Semi-Display £6 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

BOOKS AND PUBLICATIONS



THE PICTURE BOOK METHOD OF LEARNING

BASIC ELECTRICITY 5pts £4.50. BASIC ELECTRONICS 6pts £5.40. BASIC TELEVISION 3pts £3.50

The quickest and soundest method of gaining mastery over these subjects. The clear and concise illustrations make study a real pleasure. P. & P. included. Your Money Back Guaranteed. Free Illustrated Prospectus on request. SELRAY BOOK CO., 60, HAYES HILL, BROMLEY BR2 7HP.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

CATALOGUE NO. 18. Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

MORSE MADE EASY!!
FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed. Beginner's Section only £3.30, complete course £4.50 (Overseas £1 extra) details only, 4p stamp. 01-060 2896 GHSOC (Box 19), 45 GREEN LANE, PURLEY, SURREY

COMPLETE SET P.E. For Sale. Offers Please. R. Kerr, 4 Lothian Street, Bonnyrigg, Midlothian, Scotland.

TRANSISTOR SALE. Tested PNP Transistors, 20 for 50p, 45 for £1. Free 3 pieces of 10' 5 heat sink with each £1 order. P. & P. 15p extra. B. HYAMS, 10 Westcott Place, Swindon, Wilts.

SMALL QUANTITIES. Components at large quantity prices. 87 Oakington Manor Drive, Wembley, 01-902 3390.

QUAD 303 stereo amplifier, excellent condition. £30 o.n.o., 17 The Avenue, Hailsham BN27 3HT. Telephone, Hailsham 842456.

SITUATIONS VACANT

ELECTRIC SALESMAN needed in N.W.1. £22 p/w plus commission and Profit Sharing to the right man. Age over 22 years, with driving licence. Phone anytime 485 5322 or 272 1231.

£2500 career Yours in 6 weeks?

Yes. That's all the time it takes ACT to turn a person with the aptitude into a qualified Computer Programmer. Able to hold down a responsible, well-paid job in the world of computers. And our own exclusive appointments agency will introduce you to all the right connections. FREE. We've already trained vast numbers of people; pointed them in the direction of success and life-long security. Write or phone TODAY for FREE details without obligation. **ACADEMY OF COMPUTER TRAINING.** E81, Oxford House 9-15, Oxford Street, W.1. Telephone: 01-734 2874

127, The Piazza, Dept. E81, Piccadilly Plaza, Manchester 1. Telephone: 061-236 2935

SERVICE SHEETS

★ SERVICE SHEETS • MANUALS • BOOKS ★

SERVICE SHEETS OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK ON RADIOS, TV's, R.PLAYERS AND T.RECORDERS, ETC... **SERVICE SHEET** 30p + Postage PLEASE ENCLOSE S.A.E. WITH ENQUIRIES... Catalogue 20p.

NEW BOOKS & PUBLICATIONS	PRICE + P. & P.
79. QUESTIONS & ANSWERS ON COLOUR TELEVISION. by J.A. Reddihough. 108 pages	£0.60 10p
80. QUESTIONS & ANSWERS ON AUDIO by Clement Brown. Assoc. Brit. IRE	£0.60 10p
81. QUESTIONS & ANSWERS ON COMPUTERS by Clement Brown Assoc. Brit. IRE	£0.60 10p
82. QUESTIONS & ANSWERS ON ELECTRIC MOTORS by A.J. Coker.	£0.60 10p
83. QUESTIONS & ANSWERS ON ELECTRICITY by K.G. Jackson	£0.60 10p
84. QUESTIONS & ANSWERS ON ELECTRONICS by Clement Brown. Assoc. Brit. IRE.	£0.60 10p
85. MANUAL OF SOUND RECORDING. 2nd Edition by J. Aldred. 289 pages.	£3.50 15p
86. SEMICONDUCTOR PHOTOELECTRIC DEVICES by Dr. Ins. A. Ambrosiak. 344 pages. 242 illus.	£3.75 20p
87. PICKUPS & LOUDSPEAKERS by John Earl. 203 pages. 156 Illustrations	£3.00 15p
88. PUBLIC ADDRESS HANDBOOK. A Manual of Sound Reinforcement by V. Capel	£3.00 15p
89. RADIO & TELEVISION YEAR BOOK by IPC Ltd. Lists latest Models with Illustrations	£1.00 15p
90. HI-FI, PA & DISCOTHEQUE AMPLIFIER DESIGN HANDBOOK (5 to 1,000 Watts) 122 pages	£0.75 10p
91. BEGINNERS GUIDE TO HI-FI. by J.R. Hey. ASERT. An introduction to HI-FI Equipment	£0.35 7p
92. GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Data on Trans/Receivers Etc	£2.80 20p
93. COLOUR TELEVISION WITH PARTICULAR REFERENCE TO THE PAL SYSTEM by G.N. Patchett	£3.00 20p
94. PAL-D COLOUR RECEIVER: QUESTIONS & ANSWERS by K.J. Bohlman. AM.Inst.E.	£0.60 10p
95. TELEVISION SERVICING by G.N. Patchett. Vol.1. Principles. Video & Sound, IFS, Tuners etc.	£0.75 10p
96. TELEVISION SERVICING by G.N. Patchett. Vol.2. C.R.T. Sync.Seps. Time-Bases etc.	£0.85 10p
97. TELEVISION SERVICING by G.N. Patchett. Vol.3. Limiters, A.G.C. Flywheel Sync. etc.	£0.55 10p
98. TELEVISION SERVICING by G.N. Patchett. Vol.4. Practical Servicing & Fault-Finding	£0.75 10p
99. RADIO SERVICING by G.N. Patchett. Vol.1. Basic Electrotechnology.	£0.60 10p
100. RADIO SERVICING by G.N. Patchett. Vol.2. Intermediate Radio Theory.	£0.90 10p
101. RADIO SERVICING by B. Foxard, B.Sc.Eng.C.Eng-MIEE. Vol.3. Final Radio Theory	£0.75 10p
102. RADIO SERVICING by G.N. Patchett. Vol.4. Fault-Finding	£0.85 10p
119. MECHANICS COURSE IN RADIO, TELEVISION & ELECTRONICS (433) by B. Foxard	£0.50 10p
120. PART 1. Electronic Systems	£0.60 10p
121. PART 2. Second Year. Electronic Systems	£0.95 10p
122. PART 2. Third Year. Electronic Systems	£2.00 15p
123. AUDIO TECHNICIANS BENCH MANUAL by John Earl. 182 pages. 114 Illustrations	£3.00 15p
124. TUNERS & AMPLIFIERS by John Earl. 187 pages. 127 Illustrations.	£2.10 15p
125. WORLD RADIO-T.V. HANDBOOK 1972. Immense amount of tabulated matter	£2.80 25p
126. VIDEO RECORDING: RECORD & REPLAY SYSTEMS by G.White. 216 pages	£3.25 20p

Send S.A.E. for Free LISTS of Practical and Technical Books on Radio & Television now available to **BELL'S TELEVISION SERVICES** Albert Place, Harrogate, Yorks. Tel. 0423-86844

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/inquiries. Catalogue 15p. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

WANTED

CASH PAID for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hamwell, London, W.7. 01-567 5400/2971.

TOP PRICES PAID
for new valves and components
Popular T.V. and Radio types
KENSINGTON SUPPLIES
(B) 367 Kensington Street
Bradford 8, Yorks.

LADDERS

LADDERS. 20ft. £7-80. Callers Welcome. Carr. 80p. Leaflet (Dept. PEE), HOME SALES, Baldwin Road, Stourport, Worcs. Phone 02-993 2574/5222. Ansafone installed 5222. Open Sunday 8-12 noon.

MUSICAL INSTRUMENTS

ELECTRONIC PIANO

Touch Sensitive Pedal Sustain
Adjustable Decay

Plug-in units for constructing 2, 4, 6 octave ELECTRONIC PIANO. Also, Touch Sensitive Percussion Units for Keyboard Bass or add Piano Sound to existing organ. S.A.E. details of these and other units.

To: **DIGICHORD**
Duffryn Glywd House
Elm Road, Tokers Green
Reading, Berks.

HI-FI EQUIPMENT

DISCOTHEQUE AND THEATRE EQUIPMENT. Custom built to 1,000W audio and 100kW lighting control. Made to measure design service. Inquiries to Box No. 44.

Peerless

HI-FI LOUDSPEAKERS
... Acclaimed by the Experts
MULTI-UNIT SYSTEMS
IN KIT FORM
MATCHING CABINET KITS
ALSO AVAILABLE

Full details & address of your local dealer from:

P.F. & A.R. Helme Ltd. (Dept. PE11)
 Summerbridge: Harrogate G63 4DR
 Yorks. Tel. Darley 279 (STD 0423-72)

RECEIVERS AND COMPONENTS

MINI MAINS TRANSFORMER MT7, 30 x 30 x 37mm, 7-0-7V rms, 120mA, for 9V rectified d.c. Top quality component with really comprehensive data. **70p**, U.K. post 5p. Mail order only. **AMATRONIX LTD.**, 396 Selston Road, South Croydon, Surrey, CR2 0DE.

POLYSTYRENE CAPACITORS, 125V-100, 120, 150, 180, 220, 270, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 15p doz., post 10p. 0-015, 0-018, 0-022, 0-027, 0-033, 24p doz., post 10p.

COMPUTER PANELS, 5-BC108, diodes, etc., 4-50p, post 10p. American panels, 4-55p, post 12p. Panel type 773B, 8 silicon transistors, 40 diodes, 20p; 701B, 6 silicon transistors, 16 diodes, 12p, post 5p each. For lists of other types and components send large S.A.E.

UNIT WITH 4LA2 POT-CORES + CAPS, 50p, post 15p. LA2 ex. equip., 20p, new and boxed, 30p. C.P. ORP12 ON PANEL EX. EQUIPT., 35p. C.P. M.C. METERS 2 and 3in, three ass., £1-05, post 25p. **WIRE ENDED NEONS**, 10-45p, 20-75p, post 5p. **BANK OF FIVE WITH FIVE C407 DRIVER TRANSISTORS**, 45p. C.P. Bank of 30 with 30 transistors, £2-15. C.P. **NEW 48 WAY STEPPING SWITCH WITH RESET** for mains operation, £1-25, post 25p. **CROUZET GEARED SYN. MOTOR**, mains operation 15 r.p.m. a.c. wire, 75p, post 15p. **VELODYNE UNIT** 7 min. valves, v.w. res. caps, etc., 35p, post 10p. **IC 7400 SERIES** on panels, 10-75p, post 10p. **NEW COIL PACK LMSW**, 8 piano keys, no dope, 50p, post 20p. **COPPER CLAD PAXOLIN**, single sided, 5 1/2 x 3 1/2in. 6 for 30p, post 10p.

ASSORTED COMPONENTS, 7in, £1-30, C.P.
ASSORTED COMPUTER PANELS, 2in, £1-30, C.P.
MIXED POLYSTYRENE, S/MICA CAPS, 100-40p, C.P.

MIXED TRANSISTOR AND I.C. FALL OUTS, 100 approx., 18p., C.P.

J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCs.
 Mail Order only

AARVAK ELECTRONICS. Soundlight. Converters. 3 channel 1-2kW £17, 3kW £25. Strobes, 1 Joule £16, 4 Joule £25. Mail or call, 74 Bedford Avenue, Barnet, Herts. Tel. 01-449 1268.

METERS, Motors, Relays, Valves, Electronics. At **ROGERS FASCINATING ESTABLISHMENT**, 31 Nelson Street, Southampton.

Arbour Electronics Ltd.

EAST HANNINGFIELD INDUSTRIAL ESTATE, Near CHELMSFORD, ESSEX
 Telephone: Hanningfield 700

EX COMPUTER COMPONENTS

5 multi contact relays 2-5K ohm coil, 50p. P. & P. 10p. 8 micro switches, mixed, 50p. P. & P. 10p. 240V motor with governor and slipping clutch 90p each. P. & P. 20p. 2-5A meters 3in x 3 1/2in, 75p each P. & P. 10p. 5 printed circuits 4in x 4in approx. 100 semiconductor, 50p. P. & P. 10p. Memory core stores ferrite cores 25 x 50 £1-50 each, 30 x 30 £1-00 each. P. & P. 30p.

300 mixed resistors/capacitors as new, 65p. P. & P. 5p. Cable 14/0076 600V. 100 yds, 65p. P. & P. 10p. Instrument cases, 8in x 6in x 6in, blue with white front panel, £1-60. P. & P. 25p.

SPECIAL OFFER. 100 mixed resistors. Preferred Values 1W and 1/2W £1-25, including postage. 2-2mF 250V WKG 10p each, including P/P. **ALEXANDERS**, 16 Inverness Street, London, N.W.1. Tel. 485 5322.

100 WATT AMPLIFIER

Fully protected, transformerless, 9 transistor circuit. Input 500 mV. Output into 8 ohms. 0-1% distortion.
 Printed circuit board and full instructions. £1-45p + 10p P. & P. S.a.e. for list of component bargains.

EDMUNDS COMPONENTS, 134 NORTH END ROAD, LONDON, W14. (Mail order only)

SURPLUS STOCK AT REDUCED PRICES

Cs · Rs · TRANSISTORS · SMALL 3 V ELECTRIC MOTORS
 RELAYS · TRANSFORMERS
 PLUGS · SOCKETS, ETC., ETC.

SEND S.A.E. FOR LIST

W.E.C. LTD.

High Street · Ripley · Surrey

5-N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.
 Send 5p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LTD.

45 Station Road, Gerrards Cross, Bucks.
 MAIL ORDER ONLY

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15V or 25V. 1, 2, 2, 4, 7, 10 mfd., 3p. 22, 47, 4p. 100, 5p. 50V, 1p extra. Subminiature bead-type tantalums, 0-1/35V 0-22/35V, 0-47/35V, 1/35V, 2-2/35V, 10/16V. 8p. Mylar Film 100V, 0-001, 0-002, 0-005 0-01, 0-02. 2p. 0-04, 0-05. 2 1/2p. 0-068, 0-1 3p. Polystyrene 63V, 10pf. 10-1000pf., E12 series. 2p. Mullard miniature: Carbon Film Resistors, E12 series, third watt 1Ω - 10 MΩ, 8 for 5p. Insured postage, Sp. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield S8.

Modern Computer Panels with TO5 and plastic transistors, 6 for £1, 15p p. & p.

P/C Board S/S 5 1/2in x 5 1/2in. 10 for 50p + 15p p. & p. Panel with 8 OC43 + 24 OA81, 35p. p.p.

Transformers, 7-5 + 7-5V app. 1/2A, 60p, p.p. 18-0-18V 200mA - 24V 40mA 70p, p.p.

Brand New Min Jones Plugs and Sockets, 6W, 30p; 8W, 40p; 12W, 50p; 18W, 60p; 24W, 75p. All pairs p.p. 700 m/watt amp, 9V, 8Ω output, £1, p.p., with connections.

Transformers, 52-0-52V 1A + 22-0-22V 0-2A, £2, p.p. 34-0-34V 2A + 22-0-22V-2A, £2, p.p.


3EG1 Scope Tube, new, £1-75, p.p. **UHF Tuners**, transistorised, £1-50, p.p.

Veroboard 0-1 4in x 2 1/2in. 10 for £1 + 15p p. & p.

R.T. SERVICES (Mail order only)
 77 Hayfield Road, Salford 6

Trampus electronic

All Brand New. Money Back Guaranteed. Fast Service.
5V DIGITAL INDICATOR 0-91P, with socket and red filter. £1-55. 7447 £1-49.
IC GAS DETECTOR. Smoke. Butane. Vapour, etc., £2-19.
data 9p. ULTRASONIC TRANS-DUCER. Transmit or receive. £2.
42. LIGHT EMIT DIODES. Visible red/panel clip/data, 39p.
INFRA RED (invisible beam), £1-10.
IC CALCULATOR CHIP-TMS1802NC. 4 function, 8 digit, 3 register storage. ROM and RAM memory. 28 25 DIL, £28, data 85p. **LED DISPLAYS** to suit. DIL/HT £4-49 each. 5 1/16"ITS with magnifier. DIL case, £17-49. **KEYBOARD**. 12 way reed switch, £14-97.
INTEGRATED CIRCUITS: with data.
 741 op. amp. TO5 or DIL, 31p; 709 TO5, 23p; 709 DIL, 29p; 710, 38p; 723, 59p; 748, 39p.
PHOTO DETECTOR & AMPLIFIER, lens case, 44p.
AUDIO AMP, 3-3V H-Fi, etc., £1-24. Stereo: Dual Pre-amp, £1-49. FM MPX Decoder, £1-49. 74M Data Booklet, 12p; gates 7400, etc., 15p; 7470/72; 7492; 7478, 39p; 7490, 63p; 7499, 73p. **DIL SOCKETS** low profile 11 or 16 pin, 13p.

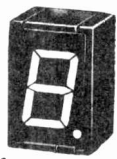

TRANSISTORS:
 2N3055, 39p. BC107, 8p. BC108, 7p. BC109, 8p. AC125/6/7/8, 125/7, AC187/8, AF117, 18p. AD161/2, 35p. BC167/8/9, 12p. BC177/8/9, 15p. BC182/3/4, 11p. BC212/3/4, 3p. BCY70, 16p. BFY50/51/52, 17p. T1843 UJT, 89p. 2N3068, 12p. FET 2N3819, 28p; 2N2926 0, Y, 9p. 2N3063, 17p; 2N3702/3/4/5/6/7, 11p; 2N3708/9/10/11, 9p.
DIODES:
 1N914/6, 5p. 0A81/91, 7p. 0A200/202, 10p. 1A RECTS: 50V, 4p; 400V, 8p. Bridge, 20p.
ZENERS: BZY88 400mW, 12p. BZY100, 29p. MINI SCR 4A/400V, 55p. TRIAC 6A/400V, 87p.
CAPACITORS: 25/30V Electrolytic, 10p/50/100µF, 5p; 200/500µF, 8p; 1,000µF, 15p. **DISC**: 22pF thro' to 0.047µF, 3p; 0.01 to 0.6p. **RESISTORS** 1W 5%, 1p. PRESETS 0-25W, 5p. **ELED** 16p/23p, etc., DIN plugs, 13p; sockets, 9p. Stereo Amp kit case, £14. 5 pin, 11pin, 14pin. **ELECTRONIC CAR IGNITION KIT**, £6-87. **FREE**. CATALOGUE, S.A.E., DATA SHEETS, 6p each. C.W.O. P. & P. 7p. Overseas 35p. Discount 10 + 10%.

P.O. BOX 29, BRACKNELL, BERKS.

Professional quality at budget prices!
 using Range 500 mixer modules.
 m.510 Microphone amplifier (600Ω), £4;
 m.511 Equaliser (Bass & Treble), £4; m.512
 Ceramic amplifier, £3-80; m.513 Line amplifier,
 £3-80; m.514 Buffer amplifier, £3-60; E.400
 Phase amplifier, £3-30; B.30 Booklet on mixing
 circuits, 30p.
 12p P. & P. Above 5 units free, above 10 units
 15% discount.
 Mixers and Effects equipment built to order.
CRAIG AUDIO EQUIPMENT
 54 Charles Street, Herne Bay, Kent

NEW FULL SPEC. DEVICES BY RETURN MONEY BACK GUARANTEE

MICROCIRCUITS: 709 30p; 710 38p; 723 71p; 741 32p; 748 37p; 78N6013 £1-24. 74 SERIES TTL: 00 16p; 01 18p; 02 18; 04 18p; 10 16p; 11 21p; 20 16p; 30 19p; 40 16p; 47 £1-35; 118p; 72 30p; 73 41p; 74 33p; 75 44p; 81 £1-26; 86 41p; 92 72p; 01 £1-21. **TRANSISTORS**: 2N3054 38p; 2N3055 42p; BC107 12p; BC108 7p; BC109 8p. **ME SERIES**: 42p; BC177 12p; BC178 12p; BC179 12p. **DIODES**: 1N914 3p; 1N916 4p; 1N4148 4p; OA5 17p; OA47 7p; OA50 6p; OA91 5p; OA200 7p; OA202 8p. **SCR**: 600V 1A 75p; 400V 5A £1-14; **LED PANEL LAMP** 45p. **SOLDERCON** 12 PIN SOCKETS 0-7p per pin any length. **PC RESIST PEN** 80p. 14 PIN DIL SOCKETS 14p. **MICROHM** Resistors 4p.

JEF ELECTRONICS (P.E.II)

YORK HOUSE, 12 YORK DRIVE, GRAPPENHALL, WARRINGTON, WA4 2EJ. Mail Order Only. C.W.O. P. & P. 9p per order. Overseas 65p. Discounts start at 10% for 10+.

SOUND SUPPLIES (Electronics) Co. Ltd.
 P.A. EQUIPMENT, Marshall amps, instruments and guitars, etc. TOA and Eagle amps and accessories, Reslo mics, etc.
 COMPONENTS, Resistors, capacitors, plugs, sockets, cables, audio leads, semiconductors, valves, vero board, etc., for the constructor.
 Power packs and car droppers for the cassette recorder or radio.
 S.A.E. for list and enquiries. P.A. list 15p.
 12 Smarts Lane, Loughton, Essex
 Tel. 01-508 2715 Closed all day Thursday

TAPE AMPLIFIERS

2 • ECC83, EL84, EZ80, 20μV/I/P sensitivity, 2 watts O/P into 7" 4" 3 ohm speaker. All contained in polished cabinet with non-standard single motor deck. Supplied complete with circuit. £3 + £1 carr.

GREENWELD ELECTRONICS (PE2)

24 Goodhart Way, W. Wickham, Kent
S.a.e. circuit and details

PRECISION POLYCARBONATE CAPACITORS

Fresh Stock — Fully tested

Close tolerance. High stability. All 63V d.c.

0.47μF:	±5%	30p:	±2%	40p:	±1%	50p
1.0μF:	±5%	40p:	±2%	50p:	±1%	60p
2.2μF:	±5%	50p:	±2%	60p:	±1%	75p
4.7μF:	±5%	70p:	±2%	90p:	±1%	£1.15
6.8μF:	±5%	95p:	±2%	£1.15:	±1%	£1.50
10μF:	±5%	£1.10:	±2%	£1.40:	±1%	£1.80
15μF:	±5%	£1.60:	±2%	£2.10:	±1%	£2.70

TANTALUM BEAD CAPACITORS. Values available 0.22, 0.47, 1.0, 2.2, 4.7, 6.8μF at 35V, 10μF 25V, 15μF 20V, 22μF 15V, 33μF 10V, 47μF 6V, 100μF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (72 capacitors) £5.

NEW TRANSISTORS. BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices.

POPULAR DIODES. IN914, 7p each; 8 for 50p; 18 for £1. IN916, 9p each; 6 for 50p; 14 for £1. 1S44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE — 400 mW Zeners. Values available 4.7, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 10p each; 6 for 50p; 14 for £1.

RESISTORS. Carbon film 1/4W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS. 0.1μF, size 1 1/2in × 1/2in, 25p; 0.25μF, size 1 1/2in × 3/4in, 30p; 0.47 and 0.8μF, size 1 1/2in × 1in, 35p; 1.0μF, size 2in × 1in, 45p; 2.0μF, size 2in × 1 1/2in 75p.

SILICON PLASTIC RECTIFIERS 1SA— Brand new wide-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

V. ATTWOOD, DEPT. B6, P.O. BOX 8, ALRESFORD, HANTS

TV Line out-put Transformers

Replacement types ex-stock.

For "By-return" service, contact London 01-948 3707

Tidman Mail Order Ltd., Dept. PE,
236 Sandycombe Road,
Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-put Transformers also stocked. Callers welcome.

COMPUTER PANELS

Panel contains 2 x Mullard OC23 Transistors and 5 other Transistors, etc. 2 panels 50p p.p. 15p. Panel contains 2 x Mullard OC28 Transistors 2XBCY34, etc. 2 panels 30p p.p. 15p. Assorted Computer Panels contain many useful Transistors, Diodes, Trim Pots, etc. 4 Panels for £1 post free.

Assorted Panels contain minimum of 10 integrated circuits, also Transistors, Diodes, etc. £1 p.p. 15p.

Electrolytic Capacitors UF/V. 2,000/35, 10,000/15, 10,000/25, 12,500/35. All at 30p each p.p. 6p. 2,000/50, 2,500/50, 5,000/50, 10,000/50, 12,500/50, 50,000/15 all at 40p each p.p. 10p.

Also available wide range motor start capacitors also block paper, etc. Send your exact requirements.

Assorted miniature and subminiature Electrolytic Capacitors, 100 for £1.20 p.p. 15p.

Mail Order only

XEROZA RADIO

1 East Street, Bishop's Tawton, Devon

KITS! KITS! KITS!

A new range of audio kits for discotheques, groups, musicians, etc. All parts guaranteed and full assembly instructions supplied.

REVERBERATION UNIT KIT
4 input 2 channel mix plus reverberation level control, etc. Battery operated. £10.50 + 50p P. & P.

100 WATT SLAVE AMPLIFIER KIT
A mains operated solid-state power amplifier for P.A. applications. Delivers 110 watts into 6 ohm load. £20 + £1 P. & P.

100 WATT INSTRUMENT/P.A. AMPLIFIER KIT
A professional amplifier using plug-in printed circuit boards. 4 input 2 channel mix with high-lift treble and bass controls on each channel. Separate master volume, etc. £30 + £1 P. & P.

FUZZ BOX KIT
A compact battery operated unit with pre-set fuzz/volume level controls and changeover switch. £3.50 + 25p P. & P.

SOUND-TO-LIGHT KIT
An effects lighting control unit featuring built-in amplifier and microphone. Modulates up to 1500 watts of lamps. Sensitivity fully variable. £8.50 + 50p P. & P.

The above kits are also available fully built and tested. S.A.E. for full details. Mail order to:

REID ELECTRONICS

43 Heaton Grove, Newcastle upon Tyne NE6 5NP

MISCELLANEOUS

CIRCUIT BOARD ETCHING KITS, full instructions, £1.25, c.w.o. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

SURPLUS ELECTRIC CABLE. 3-core rubber covered 28/0076 (100yd coils), 24 per roll, 50p postage. 3-core rubber covered 28/0076 (500yd coils), £15.50 per roll. Free, 3-core PVC Black 14/0076 (100yd coils), £3.50 per roll 25p. Single core PVC flat. 14/0076 (100yd coils), 60p per roll, 10p. 3-core PVC Black flat 28/0076 (100yd coils), £3.50 per roll, 25p. Single core PVC Black 14/3B (100yd coils), 50p per roll, 10p. Instrument (Case Strap), 3/8in wide nylon black (100yd coils), 50p per roll, 10p. New 1/20 H.P. Fraemo £4.50. BROXBORNE ENG. CO., Salisbury Road, Hoddesdon, Herts. Telephone, Hoddesdon 63666.

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to METER REPAIRS, 39 Chesholm Road, London, N16 0DS.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London, N10 3HN. 40-page illustrated catalogue 20p post free.

FIBRE OPTICS

FLEXIBLE LIGHT PIPE used to convey light to inaccessible positions for inspection, panel indicators, photo-electric and other applications. FIBROFLEX Type 1 glass fibre flexible light conduit 1.14 mm active dia bundle sheathed in P.V.C. Prices per metre (U.K. post free): 1-4, 70p; 5-9, 55p; 10+, 40p. 25 metres £6 per reel. CROFON (Trade mark of Du Pont) Type 1610 plastic flexible light conduit now available. 64 filaments. Active dia. 1.80 mm. Prices per metre: 1-4, £1.20; 5-9, £1; 10+, 80p. 25 metres £16 per reel.

Send S.A.E. for full range of products, price list and literature.

FIBRE OPTIC SUPPLIERS
P.O. BOX 702, LONDON W10 6SL

RUN YOUR TAPE RECORDER OFF

A.C. MAINS
Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.) P. & P. 15p. Also available for single outputs 6V, 9V, 12V, 18V, £2. P. & P. 15p.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E17

YOUNG SCIENTISTS

and not-so-young, whether beginner or advanced—we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW! (S.A.E. for details).

TO: BOFFIN PROJECTS

4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

COME INTO SPACE NOW!

38 STAMPS



ONLY 10p

ASK FOR LOT PE 2

BROADWAY APPROVALS
50 DENMARK HILL, LONDON, S.E.5.

CONSTRUCTION AIDS. Fascia panels, dials, nameplates in etched aluminium to individual specification. Sheet aluminium, printed circuits—drafting tapes, negatives supplied, boards manufactured, singles or small runs. Copper clad laminate supplied. Hardware for constructors. S.A.E. details. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

FOR ALL your Electronic Component requirements. Send for free list to B.C. ELECTRONIC SUPPLIES, 7 Regent Road, Huddersfield, HD1 4NR.

PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN.

TRIAL KIT £1.30 Carr. Paid
No. 1 KIT £1.88 Carr. Paid
No. 2 KIT £2.39 Carr. Paid

M.P.E. Ltd., BRIDGE ST., CLAY CROSS, DERBYS.

DIMMIT

range of light dimmers

standard wall mounting models

Rotary: 400W £3.10 1KW £3.95

module only: 400W £2.80 1KW £3.60

Slider: 400W £4.35 1KW £4.95

module only: 400W £3.50 1KW £4.05

2 kW Slider module now available

Send 10p for complete catalogue of Dimmits. Orders: add 10p P. & P. for each dimmer.

YOUNG ELECTRONICS

54 Lawford Rd., London NWS 2LN 01-267 0201

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5 50 NOW (S.A.E. for details)
TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

P.E. GEMINI. Etched aluminium fascia panels as detailed in latest publication. Printed circuit boards and other items. S.A.E. details. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warwicks.

CALCULATOR CHIP


TEXAS 1802 One-Chip Calculator Circuit. Build yourself a low-power pocket calculator with 8 digit display (7-Segment) and all professional functions.

Calculator Chip TMS 1802NC	£30.00
RAPIDMAN 800 Calculator	£39.50
LED Displays	One digit £4.50
	Four digits £17.00
	5 x 7 Dot Matrix £12.50

All displays 14 pin D.I.L. packages. CWO to:

BYWOOD ELECTRONICS

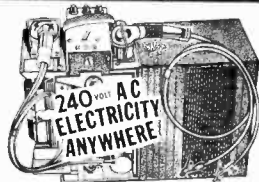181 EBBERS ROAD, HEMEL HEMPSTEAD, HERTS.
0442 62757



BEST EVER—INTERNATIONAL 230 VOLT A.C. "MAINS" PERFORMANCE from 12 volt car battery. **R.C.A. INTERNATIONAL 230 volt A.C. POWER UNIT.** Wonderful 230 volt a.c. performance with low battery drain. Marvellous for A.C. **FLUORESCENT LIGHTING** and hundreds of makes and types of 200/240 volt A.C. and **UNIVERSAL A.C./D.C. APPLIANCES.** Can be used for re-charging battery by using an ordinary motorist's 4 amp battery charger. Total weight of unit 21 lbs. Price **ONLY £4.90**, plus £1 delivery. Money back if not delighted. C.O.D. with pleasure.

Dept. PE, BROADWAY DISTRIBUTORS, The Generator Centre, House of Time, 273 Broadway, Rossall, Fylde, Lancs.

YUKAN SELF-SPRAY 50 PROFESSIONAL THE YUKAN AEROSOL WAY—
Get these NOW! OR **BLACK WRINKLE** (CRACKLE) finishes

Yukan Aerosol spray contains 45% fine quality durable stainless steel spheres. No stove burning required. Finishes available in Grey and Black. 25p tin of Modern Eggshell Black Wrinkle (Crackle) producing a 3D textured finish. 45p tin of all at 87p per pint. Includes self-sealing car air capacitor. Also durable heat and water resistant Black Matt Tough (32p) and water proof only (72p) and

SPECIAL OFFER One tin plus optional interchangeable strap on trigger handle (value 25p) for 80p per tin. Choice of 13 per quart paint colours. Please enclose cheque or money P.O. for cash orders direct to:

DEPT. PE: YUKAN, 307A EDGWARE ROAD, LONDON W2 1BN

We supply main Government Departments, Municipal Authorities, Hospitals and leading Industrial Organisations. We can assist you too. Write to the Secretary, Street Thursday afternoons. *Now British made better.*

CLOSED ALL DECEMBER FOR ANNUAL HOLIDAY

ELECTRONIC MUSIC

CIRCUIT ASSEMBLIES for all your music projects, ready-to-use modules ideal for Synthesizers, Sound Effects, Organs, Instrument modifiers.

CHOOSE from over 25 circuits, including our new range of I-C designs for Synthesiser work. **OUR CATALOGUE** contains full technical details, explanations and definitions, suggestions for projects, and discount price details.

OUR PRICES are the lowest in this field and represent unbeatable value for money. Send only 20p for our latest catalogue.

TAYLOR ELECTRONIC MUSIC DEVICES
GREYFRIARS HOUSE • CHESTER

EDUCATIONAL

GET INTO Electronics—opportunities for trained men. Learn at home. Postal courses in RTEB, City & Guilds, Radio, TV, Telecoms, etc. **FREE** informative guide: **CHAMBERS COLLEGE** (Dept. R.103), Aldermaston Court, Reading, RG7 4PE.

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Building, etc. **FREE** book from: **BLET** (Dept. H.4), Aldermaston Court, Reading, RG7 4PE. *Accredited by C.A.C.C.*

STANDARDISED PRINTED CIRCUIT SYSTEM for I.C.s and discrete Transistors

Sample packs with three different board sizes and full details
S.B.P. undrilled 95p. Drilled £1-84 with **FREE** mounting
Glass Fibre undrilled £1-09, Drilled £2-15 with **FREE** mounting
Please state whether for I.C.s or transistors, pillars
Starter packs of mixed undrilled small boards 50p & 70p
Gold plated Edge Connectors, 14 way 35p, 30 way 68p
Mounting pillars from 3p, Card handles 5p

NIP-E-BOARD

MAKE YOUR P.E. PROJECTS ON NIP-E-BOARD
I.C. Intergrain Amalgams on ardp drilled 82p (2 boards), undrilled 95p. *Aglassa drilled 95p, undrilled 95p.*
Resistor Plate Generator on ardp drilled 80p, undrilled 90p, *Aglassa drilled 80p, undrilled 90p.*
Logic Demonstrator on ardp drilled 80p, undrilled 90p, *Aglassa drilled 80p, undrilled 90p.*

LAYOUT PLANNING CHART PROVIDED

Quantily discounts. We supply retail trade, industry, export

NIP ELECTRONICS
DEPT. NE/E, P.O. BOX 11, ST ALBANS, HERTS.

HONS. DEGREE IN ELECTRONIC ENGINEERING

Two academic years in college, one year in industry and a final academic year in college.

HONS. DEGREE IN ELECTRICAL ENGINEERING

Three years on a six-monthly Polytechnic/Industry sandwich pattern followed by a final academic year in college.

H.N.D. IN ELECTRICAL and ELECTRONIC ENGINEERING

Three year thin-sandwich course. For full details apply to Head of Department of Electrical and Electronic Engineering, North Staffordshire Polytechnic, Beauside, Stafford or telephone him at Stafford 52331. Please quote reference 1546/PE on both envelope and letter.

TELEVISION TRAINING (MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commences January 1st. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. B/11, 20 Pennywell Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**

RECORD T.V. SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included. **£1** post free. **CROWBOROUGH ELECTRONICS (P.E.)**, Eridge Road, Crowborough, SUSSEX.

Versatile
10 in ONE



MINI-LAB

Comprising:
• AC and DC Voltmeter • Audio Generator • Ohm Meter • Resistance Substitution • Capacitance Substitution • DC Ammeter • Battery Supply • RF Signal Generator • RF Field Strength Indicator.


This new, unique instrument combines all you need for testing. Guaranteed, money back if not satisfied. Cash with order or write for illustrated data sheet to:

R.S.L. COMPONENTS (Dept. PE)
Cricklefield Lane, Bishop's Stortford, Herts

£11.25

plus 25p.p.&p.

BUILD A PROJECT 'X' SYNTHESISER

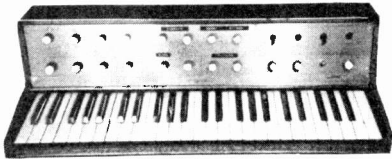

Typical Simplified Synthesiser

MAN-SIZED ROBUST PATCHBOARD

MAKE A "PATCH" AS IF YOU MEAN IT. "K-L-O-N-K" and it's MADE!

No fiddling with fragile patch pins. No cables. Countless possible combinations giving **FULL RANGE EFFECTS**. Keyboards available for versatile "live" use.

NEW BREAKTHROUGH

VCO-2 gives SINE, TRIANGULAR and SQUARE outputs, and is stable! 1 volt/octave control. Single £20 each. Matched and tracked £23 each.

SHE-1 SAMPLE, HOLD and ENVELOPE module gives sustain and variable env. to VCO signal. £11.50.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to a leading group. Our modules are used in professional equipment! Send s.a.e. for synthesiser details or send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES

CASH SAVINGS

by buying modules and parts in bulk! All modules are available separately: Ring Modulator RM2, £7. Voltage-controlled Oscillator VC01, £9.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £12.50. White noise type WN1, £6. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £12. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £9. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £4.50.

TRANSFORMERS

DOUGLAS GUARANTEED
12 or 24 Volts

Output V. & Amps.	Ref. No.	Price P. & P.
12V x 2 250 mA x 2	MT111 CS*†	£0.91 8p
12V x 2 500 mA x 2	MT213 CT*†	£0.97 13p
12V x 2 1A x 2	MT 71 AT†	£1.48 24p
12V x 2 2A x 2	MT 18 AT	£2.04 30p
12V x 2 3A x 2	MT 70 AT	£2.50 32p
12V x 2 4A x 2	MT 108 AT	£2.92 33p
12V x 2 5A x 2	MT 72 AT	£3.38 34p

30 volts. All tapped at 0-12-15-20-24-30V

Out-put Amps.	Ref. No.	Price P.P.	Out-put Amps.	Ref. No.	Price P.P.
1A	MT 79 AT	£1.55 29p	4A	MT 21 AT	£3-10 40p
2A	MT 3 AT	£2.28 30p	5A	MT 51 AT	£4-81 42p

500 mA	Ref. No.	Price P. & P.			
MT 112 CT†	1-18 15p	3A MT 20 AT	£2.64 32p		
1A	MT 79 AT	£1.55 29p	4A	MT 21 AT	£3-10 40p
2A	MT 3 AT	£2.28 30p	5A	MT 51 AT	£4-81 42p

500 mA	Ref. No.	Price P. & P.			
MT 102 AT†	1-46 24p	3A MT 105 AT	£3.91 41p		
1A	MT 103 AT	£2.00 32p	4A	MT 106 AT	£5.06 41p
2A	MT 104 AT	£3-10 32p	6A	MT 107 AT	£7-47 50p

500 mA	Ref. No.	Price P. & P.			
MT 124 AT†	1-46 21p	2A	MT 127 AT	£3-16 41p	
1A	MT 126 AT	£2-24 28p	3A	MT 125 AT	£4-69 41p

Power output	Winding tapped at	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 113 CT	£0.89 15p
75 VA	MT 64 AT	£1.72 30p
150 VA	0-115-200-220-240	MT 4 AT	£2.15 31p
200 VA	MT 65 AT	£2.80 32p
400 V. Output at 60 HZ.	Ref. IT3 AT	Price P. & P.	
C-D Ignition system by R. M. Marston	Eq.	£2.95 29p	

Sec. Output (r.m.s.)	Ref. No.	Price P. & P.
3-0-3 V.	200 mA MT 209 CS*†	£0.89 8p
9-0-9 V.	100 mA MT 13 CS*†	£0.91 8p
12-0-12	50 mA MT 210 CS*†	£0.91 8p
20-0-20	30 mA MT 211 CS*†	£0.91 8p
0-20 x 2	300 mA MT 214 CT*†	£1.21 14p
0-8-8 x 2	500 mA x 2 MT 207 CT*†	£1.46 20p
0-15-20 x 2	500 mA x 2 MT 205 AT*†	£2.12 29p
0-15-27 x 2	500 mA x 2 MT 203 AT*†	£2.45 29p
0-15-27 x 2	1A x 2 MT 204 AT*†	£2.42 30p
10-12-0-12-20	700 mA (d.c.) MT 221 AT*†	£1.11 25p

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; *with interwinding screen; †untapped 240V Primary; ‡ Primary tapped at 210-240V; other Primaries tapped at 200-220-240V. Over 200 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD.
(Dept. MO. 58), Thames Street, LOUTH, Lincs.

MINIATURE PUSH-BUTTON SWITCHES

4 pole changeover, 250V. Switching 0-1A and carrying 3A. 12-7mm pitch. Total depth 64mm. Available in banks of 1, 3 or 5. Actions available: independent, normal interlock, or momentary. Price per switch unit 40p.

Mains switch 250V amp can be fitted separately or on same frame as above: 1 pole changeover, 70p; 2 pole changeover, £1-10. Illumination for above (12V lamp, holder button) 70p. The Main Switch above with 12mm threaded bush and nut for panel mounting: 1 pole changeover, 90p; 2 pole changeover, £1-30.

NEON in amber lens and holder with resistance for 250V operation, 15p.

MINIATURE SLIDER SWITCH 2 pole changeover. Outside sizes 25mm x 8mm switching 0-3A and carrying 1A 15p.

MINI MOTOR BOOSTER (P.E. July 1972). Complete kit of parts excepting motor, £2-25, or built and tested, £3. Using 2N3054 and OC202.

All components supplied separately.

2N3054	50p	BC107	9p	BC169	12p
2N3055	70p	BC108	10p	OA200	9p
OC202	95p	BC109	10p	IN4001	07p

P. & P. up to £3-10p. Over £3-free-Post only.

BORDER ELECTRONICS

(Supplies and Manufacture)
8 Broompark, KELSO, Roxburghshire
Tel.: Kelso 2864 TDS 75N

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250v D.C. Gold clad contacts. 62p per doz.; £3.75 per 100; £27.50 per 1,000; £150 per 10,000. All carriage paid.
G.W.M. RADIO, LTD.
40/42 Portland Road, Worthing, Sussex BN93 3ABP

U.H.F. TV AERIALS

SUITABLE FOR COLOUR & MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS
7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75.

WALL MOUNTING c/w WALL ARM AND BRACKET. 7 element £3-25. 11 element £3-75. 14 element £4-25. 18 element £4-75.

CHIMNEY MOUNTING ARRAYS c/w MAST AND LASHING KIT. 7 element £4. 11 element £4-50. 14 element £4-75. 18 element £5-25.

MAST MOUNTING arrays only 7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd.

KING TELEBOOSTERS from £3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps £7-50. State clearly channel number required on all orders. P. & P. on all aerials 50p accs. 15p. C.W.O. min. C.O.D. charge 25p.

BBC-ITV-FM AERIALS

BBC (band 1) Wall S/D £2. LOFT inverted 'T' £1-25. EXTERNAL 'H' array only £3. ITV (band 3) 5 element loft array £2-50. 7 element £3. COMBINED BBC-ITV left 1+5 £2-75. 1+7 £3-50. WALL AND CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from £3-75.

COMBINED U.H.F.-V.H.F. aerials 1+5+9 £4. 1+5+14 £4-50. 1+7+14 £5. F.M. RADIO loft S/D £1. 3 element £3-25. 4 element £3-50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P. & P. all aerials 50p, accs. 30p. C.W.O. min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY
K.V.A. ELECTRONICS
40-41 Monarch Parade, London Rd.
Mitcham, Surrey
Telephone 01-648 4884

ELECTRONIC COMPONENTS

Wholesale/Retail:

369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

INDUSTRIAL USERS!

We have access to some of the largest stocks of transistors and I.C.s in Europe. Some sample prices are given below. Regret that it is not possible to supply less than 100 of any one type at these prices. All marked and to full specification. Please phone or write for immediate quote should types you require not be listed.

AD 149 .. 34p each	BD 137/138 .. 46p pair	2N 3055 .. 31p each	741C (T05 or DIL) .. 27p
AD 161/162 .. 35p pair	2N 1613 .. 8p each	2N 3053/4037 .. 34p pair	723C (T05 or DIL) .. 40p
AF 124 .. 9p each	2N 1711 .. 9p each	2N 5179 .. 38p each	
BC 141/161 .. 38p pair	2N 3053 .. 11p each	709C (T05 or DIL) 25p	

RECTIFIERS
IN4007 1200
peak volts, 30
amps peak
current, 1 amp
mean current
100 for £7.50
1,000 for £50

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light-sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.

Light-sensitive aerosol spray £1 plus
Developer and Etchant 50p postage

NEWER THAN NEW!!!!

Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.

75mm x 100mm .. 33p
150mm x 100mm .. 66p
150mm x 200mm .. £1.32

Epoxy-Resin

75mm x 100mm .. 22p
100mm x 150mm .. 44p
150mm x 200mm .. 88p

Plain Fibre Glass Board

290mm x 175mm .. 45p

Bakelite Laminate Board, 1.57mm thick

1 sq. foot .. 50p

Special Offer Pack consisting of 5 2 1/2in x 1in boards and a Spot Face Cutter—50p. "ODDS & ENDS"—1p sq. in.

VEROBOARD

2 1/2in x 1in x 0.15in	6p
3 1/2in x 2 1/2in x 0.15in	16p
3 1/2in x 3 1/2in x 0.15in	20p
5in x 2 1/2in x 0.15in	20p
5in x 3 1/2in x 0.15in	28p
17in x 2 1/2in x 0.15in	55p
17in x 3 1/2in x 0.15in	74p
3 1/2in x 2 1/2in x 0.1in	21p
3 1/2in x 3 1/2in x 0.1in	24p
5in x 2 1/2in x 0.1in	23p
5in x 3 1/2in x 0.1in	28p

Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0.1 or 0.15) 36 for 18p.

TANTALUM CAPACITORS

Special offer to clear!— 5p each; 50p dozen; £3.50 per 100.

0.47µf 20V	0.22µf 50V	2.7µf 50V	6.8µf 60V	47µf 50V
0.056µf 50V	0.33µf 50V	3.0µf 12V	12µf 50V	56µf 16V
0.033µf 20V	0.39µf 35V	3.3µf 15V	12µf 35V	56µf 20V
0.056µf 50V	0.47µf 50V	4.7µf 35V	15µf 20V	82µf 20V
0.068µf 35V	0.68µf 35V	5.6µf 6V	22µf 15V	150µf 6V
0.068µf 50V	0.68µf 50V	5.6µf 35V	22µf 75V	180µf 10V
0.07µf 20V	1.5µf 20V	5.6µf 50V	18µf 35V	270µf 6V
0.12µf 35V	2.7µf 15V	6.8µf 20V	27µf 20V	
0.15µf 35V	2.7µf 35V	6.8µf 50V	27µf 35V	

ELECTROLYTIC CAPACITORS

2,000µF 25V Rev.	25p
1,000µF 70V	35p
10,000µF 35V	50p
10,000µF 25V	35p
60µf + 200µf 300V	30p
10µf 6V	2p
10µf 25V	4p
16µf 250V	8p
32µf 275V	8p

Miniature type. Both wires same end.
5µf 10V .. 3p each
30µf 10V ..
50µf 10V ..
220µf 25V ..

AXIAL LEADS

250µf 25V	10p
500µf 25V	13p
1,000µf 25V	16p
1,000µf 25V	25p
2,500µf 50V	30p
400µf 40V	20p
125µf 4V	} 3p each
400µf 6.4V	
320µf 10V	
16µf 16V	
320µf 2.5V	
125µf 4V	

RECORD PLAYER CARTRIDGES. Well below normal prices!
GOLDRING G850 Magnetic Stereo Cartridges, Diamond Needle, £4.75.
ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 9/3 (Compatible, Crystal) £1.
ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1.25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1.63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1.50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1.88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1.25.

ERIE MONOLITHIC CERAMIC CAPACITORS

3p each; 20p dozen; £1.75 per 100	
10pf	330pf
15pf	470pf
22pf	560pf
33pf	620pf
39pf	680pf
47pf	1,000pf
68pf	1,500pf
100pf	2,200pf
150pf	2,700pf
220pf	3,300pf

MULLARD POLYESTER CAPACITORS

500,000 IN STOCK!!!

0.01µf	0.018µf	0.056µf	0.15µf
0.012µf	0.022µf	0.1µf	0.33µf
0.015µf	0.027µf	0.12µf	0.82µf
20p dozen; 75p-100; £5-1,000; £40-10,000			
15µf	22µf	39µf	82µf
18µf	27µf	68µf	1µf
20p dozen; £1-100; £6.50-1,000; £50-10,000			

TRANSISTORS AND INTEGRATED CIRCUITS

FJH231/7401N	Quadruple 2-input positive NAND gate with wired-OR capability	12p			
FJH111/7420N	Dual 4-input NAND gate	12p			
FJH141/7440N	Dual 4-input NAND buffer gate	12p			
FJH171/7453N	8-input AND/OR/NOT 2-level logic circuit	12p			
FJJ101/7470N	Edge-triggered JK flip-flop with two J, K and one J, K input	24p			
FJJ111/7472N	Master-slave JK flip-flop with triple J and K inputs	24p			
FJJ131/7474N	Edge-triggered dual D-type flip-flop with direct, clear and preset inputs, complementary Q and Q outputs	32p			
FJH201/7482N	2-bit binary full adder with summation outputs provided for each bit and the resultant carry obtained from the second bit	88p			
FJJ151/7491AN and FJJ271	8-bit shift register consisting of eight R-S master-slave flip-flops with input gating and clock driver	78p			
FJJ251/7492N	4-bit binary counter consisting of four master-slave flip-flops internally connected to provide a divide-by-two and divide-by-six counters	58p			
FJJ211/7493N	4-bit binary counter consisting of four master-slave flip-flops internally connected to provide a divide-by-two and divide-by-five counters	58p			
FEQ101	64-bit read/write random access memory. Supply voltage—27V. Stand-by dissipation per bit—2.0mW. Cycle time—750ns. Read access time—250ns. 16-lead dual-in-line package	£1			
709	Operational amplifier with high-impedance differential inputs and low impedance output, for use as inverting, non-inverting and differential amplifiers with bandwidths from 0-500kHz. Available in moulded 14 lead dual-in-line package or T05 encapsulation	27p			
741	A development of 709-OPA offering circuit simplification by employing internal frequency compensation. Mounted in a miniature 8-lead moulded dual-in-line package, or T05 encapsulation	35p			
BZY95/C82	20p	LD270	25p	LDA450	25p
LDA400	25p	CV7700	£1	LDA452	25p
GET113	5p	(BZ 791C IOR)	£1	CV7747(BCY40)	25p
CL8390	£10	CL8380	£10	CL8370	£10
CL8450	£10	CL7331	£20	CL8470	£40
CAY10	£5	OA2236 (22V, 10W)	25p	AZ292 (9-IV, 7W)	25p
2N697	15p	1N4885	25p	1N4885	£2
BF1804	25p	2N1307	15p	AEY162	£10
AEY173	£4	AEY131	£5	BXY28	£1
BXY28C	£1	BXY27	£1	BXY36C	£1
BXY41E	£1	BXY35A	£1	BFS19	10p
BFS18R	10p	BCY71	10p	BTY99/100R	£4
BTY99/200R	£5	BFX86	5p	BTY99/500R	£6
BTY34/400	£1	BTY99/300R	£5.50	BTY95/100R	£3
BTX37/500R	£4	BTX34/400R	£1	BTX50/1100R	£5
BTX66/500R	£5	BTX37/700	£5	BTX66/700R	£7
BTX75/100R	50p	BTX66/600R	£5	BLY36G	£3.50
BLY89A	£5	BTX83/600R	£2.50	BFY53	5p
BFR64	£1	BLY93A	£9	BCI09	7p
BF194	7p	BCI08	7p	OCP70	50p
OC41	3p	OC4	4p	OC43	3p
OC46	3p	OC42	3p	DW7662(BC115)	5p
BZ788/C7V5	5p	BD112	25p		

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p

CRESCENT RADIO LTD.

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

**COMPONENTS AND HI FI
FOR THE HOME CONSTRUCTOR**
OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc. amplifier.



£1.75
plus 13p P. & P.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2½in x 2½in x 3½in. Our Price **£2.75** plus 10p P. & P. Same model suitably wired for the Philips Cassette **£3** plus 10p P. & P.

DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components **£32.50** + 50p P. & P. Please send B.A.E. If you require more information.

IB40K05
Bridge Rectifier (Texas)
Plastic encapsulated 50V
at 4A. Approx. size 1½in. x 1½in. x ½in. Our Price **60p** each.

MINI LOUSPEAKERS
2½in 8 ohm **50p**
2½in 80 ohm **50p**
2½in 40 ohm **50p**
Please include 5p P. & P. on each L.S.

EA1000 3 WATT AUDIO AMPLIFIER
An Audio Amplifier designed around the TAA621 Linear I.C. —
Supply Voltage 9-24V
Speaker Imp. 8-16 ohm
Frequency 50Hz-25kHz
Overall Size 2in x 3in x 1½in
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at **£2.63** + 5p P. & P.

BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price **£2.75** plus 8p P. & P. each



TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. x 3½in. x 1½in. This suitably wired for the Philips Cassette **£3** plus 10p P. & P. and is transistor regulated. A real money saving device for **£2.50** plus 10p P. & P.

MINIATURE RELAY
6 volt 70 ohm.
Single Pole Changeover — **40p** plus 5p P. & P.
Approx. size = 1½in. x 1in. x ½in.

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL
Spec: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and plus 25p
Control Switch. **£5.75** P. & P.

PRINTED CIRCUIT KIT

BARGAIN S.O.R.
Treated Thyristor.
400V, 3amp.
45p each. 50p for £2.
5p P. & P.

Everything for producing your own Printed Circuits. **£1.40** plus 10p P. & P.

CRESCENT CASSETTES
Top quality cassettes at unbeatable prices (complete with standard storage case): C60 **28p**, C90 **38p**, C120 **48p** plus 5p P. & P.

PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18.50** plus 38p P. & P.

If you require more information please send S.A.E.

S. G. BROWN HEADPHONES

Used! But in good working condition. These Type "P" phones are 4,000 Ω imp. **50p** P. & P. per pair and a bargain at

CRESCENT 100W STEREO

A new style 100 watt per channel stereo amplifier. All loudspeaker systems, 8-15 ohm are suitable. This amplifier is designed for the D.J. and group who must have good looking and reliable equipment. A bargain at **£60**. We also have a mono 100 watt at **£42**. Please include 11 P. & P. and insurance. If you require more information please send B.A.E.

EMI LOUSPEAKER 450

10W 13in x 8in = two 2½in tweeters and cross over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. **£3.50** plus 38p P. & P. each.

7" x 4" LOUSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in. x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: **£1.00**. Free postage on this item.

BEDFORD ELECTRONICS

2 GROVE PLACE, BEDFORD
(continuation of Lurke Street)

MULLARD C296 POLYESTER FILM CAPACITORS
400V: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 2½p, 0.0068, 0.01, 0.015, 0.022, 0.033, 3p, 0.047, 0.068, 0.1, 4p, 0.15, 5½p, 0.22, 7p, 0.33, 10½p, 0.47, 12p, 160V: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 3p, 0.1, 3½p, 0.15, 4p, 0.22, 4½p, 0.33, 5½p, 0.47, 7p, 0.68, 10p, 1.0, 12p.

MULLARD C280 METALLISED FILM CAPACITORS 250V
0.01, 0.015, 0.022, 3p, 0.033, 0.047, 0.068, 3½p, 0.1, 4p, 0.15, 0.22, 4½p, 0.33, 6p, 0.47, 7½p, 0.68, 10p, 1.0, 12p, 1.5, 18p, 2.2, 2½p.

CERAMIC CAPACITORS 50V (Square plaquette body)
E12 Series 22pF-1,000pF, 1½p, 0.0015-0.01, 2p, 0.015-0.047, 2½p.

HIGH VOLTAGE CAPACITORS 1000V d.c. (300V a.c.)
0.001, 0.0022, 0.0033, 0.0047, 7p, 0.0068, 0.01, 0.022, 10p, 0.047, 0.1, 12p, 0.22, 20p, 0.47, 22p.

ISKRA POLYSTYRENE CAPACITORS 160V, 2½%
Values in pF: 5, 10, 15, 22, 33, 47, 56, 68, 100, 150, 220, 330, 470, 560, 680, 820, 1000, 3½p.

SOLID TANTALUM RESIN DIPPED BEAD CAPACITORS
MF/V: 0.1/35, 0.22/35, 0.47/35, 1.0/35, 2.2/35, 4.7/35, 10/63, 10/16, 10/25, 12/25, 47/63, 100/63, 150/63, 15p.

MULLARD 015/016/017 ELECTROLYTICS (Replaces C426/C437)
MF/V: 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/63, 10/63, 15/10, 15/10, 15/63, 22/25, 22/63, 33/16, 33/40, 47/10, 56/16, 100/4, 100/10, 100/25, 150/16, 220/16, 5p, 47/63, 470/63, 5½p, 68/63, 330/16, 9p, 100/63, 150/63, 680/16, 1500/63, 11p, 220/63, 470/40, 1000/16, 15p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/63, 18p.

RESISTORS	Type	Tolerance	Range	Values	Price each
ISKRA 1/2W		5%	4R7-2M2	E24	1p
ISKRA 1/2W		10%	3M3-10M1	E12	1p
MULLARD 1/3W		5%	1R-3R9	E12	1p
ISKRA 1/5W		5%	4R7-1M	E24	1p
WIREWOUND 2.5W		10%	R22-R47	E12	9p
WIREWOUND 2.5W		5%	1R-270R	E12	7p
PRESETS 100R, 250R, 500R and Decades to 5M, 0.1W, 5p, 0.25W, 6p.					

Post and packing 10p on orders under £2.
FULL CATALOGUE ON REQUEST.

COLOUR T.V.

19" Tube £125 — 25" Tube £160
COMPLETELY OVERHAULED — SIX MONTHS' GUARANTEE
— VARIETY OF MAKES AND MODELS

FABULOUS WINTER VIEWING:
MONOCHROME
UHF — SINGLE STANDARD — PUSH BUTTON TUNER
20" Tube £34.95 — 24" Tube £44.95

Carr. + ins. £2.50. Famous make D/5 chassis—Thoroughly overhauled—Fitted with "Square Screen" tube—Transistorised "Push Button" tuner—Fitted in an attractive cabinet, refinished in a choice of teak, walnut, or mahogany veneers (state 1st and 2nd choice)

12 month written guarantee with every set—Leaflet and copy guarantee sent on receipt of your stamped, self addressed envelope.

The above models can be seen working in our Langley showroom.

Working and overhauled BBC 2 TV'S (Ferguson 900 and similar sets) £20 carr. £2

SUMIKS (P.E.), 7 HIGH STREET LANGLEY, WARLEY, WORCS.

BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power	35 watts
Bass Resonance	35 c.p.s.
Flux Density	15,000 gauss
Voice coil impedance	8 or 15 ohms models
Useful response	20-14,000 c.p.s.
GUITAR MODEL "GROUP 50"	50 watt £20
15 in. Heavy Duty.	

£20

POST FREE



Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.


Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.J.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.
 "My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

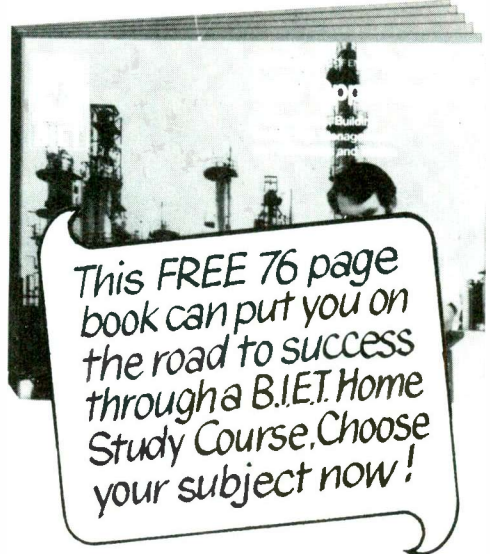These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. B38, Aldermaston Court, Reading RG7 4PF



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

- | | | |
|--|--|---|
| <p>MECHANICAL
 A.M.S.E. (Mech.)
 Boiler Inspection & Operation
 C & G Eng. Crafts
 C & G Fabrication
 Diesel Eng.
 Eng. Inspection
 Eng. Metallurgy
 Inst. Eng. & Tech.
 Inst. Motor Ind.
 Maintenance Eng.
 Mechanical Eng.
 Sheet Metal Work
 Welding</p> | <p>Man. Prod.—cont.
 Salesmanship
 Storekeeping
 Work Study
 Management</p> <p>DRAUGHTSMANSHIP
 A.M.I.E.D.
 Design of Elec. Machines
 Die & Press Tool Design
 Electrical Draughtsmanship
 Gen. Draughtsmanship
 Jig & Tool Design
 Technical Drawing</p> <p>RADIO & TELE-COMMUNICATIONS
 Colour TV
 C & G Radio/TV/ Electronics
 C & G Telecomm. Tech.
 Frac. Radio & Elec. (with kit)
 Radio Amateurs Exam.
 Radio Servicing & Repairs
 Radio & TV Eng.
 Transistor Course
 TV Main. & Serv.</p> <p>AUTO & AERO
 Aero Eng.
 A.M.I.M.I.
 A.R.B. Cert.
 Auto Engineering
 Auto Repair
 C & G Auto. Eng.
 Garage Management
 MAA/IMI Diploma
 Motor Vehicle Mechanics</p> <p>CONSTRUCTIONAL
 A.M.S.E. (Civil)
 Architecture
 Building</p> <p><i>Coaching for many major exams, including HNC, ONC, C & G, etc.</i></p> | <p>Constructional-cont.
 Building Drawing
 Building Foreman
 Carpentry & Join.
 Civil & Municipal Engineering
 Constructional Engineering
 Construction
 Surveyors
 Institute Clerk of Works
 Council Eng.
 Geology
 Health Eng.
 Heat & Vent.
 Hydraulics
 Inst. of Builders
 Inst. Clerk of Works
 Inst. Works & Highway Supers.
 Painting & Dec.
 Public Hygiene
 Road Engineering
 Structural Eng.
 Surveying</p> <p>GENERAL
 Agricultural Eng.
 Council of Eng. Inst.
 Farm Science
 General Education
 Gen. Plastics
 Pract. Maths
 Pract. Slide Rule
 Pure & Applied Maths
 Refrigeration
 Rubber Technology
 Sales Engineers
 Tech. Report Writing
 Timber Trade University Ent.</p> <p>G.C.E.
 58 'O' & 'A' LEVELS SUBJECTS
 Over 10,000 group passes</p> |
|--|--|---|

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. B38, Aldermaston Court, Reading RG7 4PF B38

NAME _____
 Block Capitals Please
 ADDRESS _____

SUBJECT OF INTEREST _____ AGE _____
Accredited by the Council for the Accreditation of Correspondence Colleges.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



Published approximately on the 15th of each month by I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand: Gordon & Gotch (A.Sia) Ltd.; South Africa: Central News Agency Ltd.; Rhodesia and Zambia: Kingstons Ltd. East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.95 (22.13.0.). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

U.K.'s LARGEST ELECTRONICS CENTRES!

HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381
 354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736
 309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963
 303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1BW

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

BUILD THE TEXAN


20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

★ FREE TEAK CASE with complete kits!

FEATURES: New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 Zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

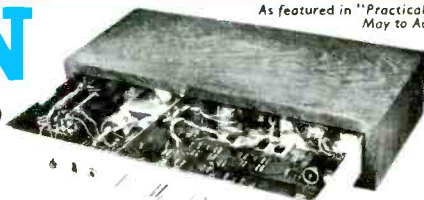FACILITIES: On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Plug, P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape head etc. (Parts list Ref. Low on request). Constructional Details Ref. No. 21. 30p.



As featured in "Practical Wireless" May to August 1972

SPECIAL KIT PRICE
£28.50 P. & P. 45p

SLIM DESIGN WITH SILVER TRIM

Overall chassis size 1 1/4 in. x 6 in. x 2 in. high

COMPLETE WITH FREE TEAK CABINET

Designer approved kits distributed by Henry's!

LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2 in x 8 1/2 in and Ceramic Magnet
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150TC Twin cone version £2.75. Post 22p.
TYPE 450 1 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.



POLISHED CABINETS 150, 150TC, 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 OHM)
SERIES 6 (Assembled 150TC) per pair £16.50. Post 70p.
SERIES 8 (Assembled 450) per pair £18.95. Post 70p.

ML3 MW/LW TUNER TO BUILD



Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7 in x 2 1/4 in x 3 1/4 in. **TOTAL COST TO BUILD £4.85.** Post 15p. All parts sold separately—Leaflet No. 6.

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit anti transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. **TOTAL COST TO BUILD £7.98,** p.p. 32p (Batt. 22p). All parts sold separately—Leaflet No. 2.

CATALOGUE


Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information.

10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post paid (40p FOR CALLERS)

PLUS! FIVE 10p VOUCHERS

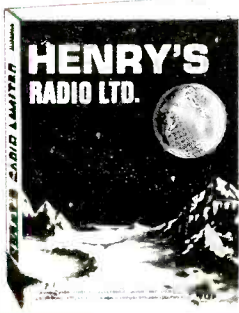
Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.



TEST EQUIPMENT

Just a selection

- SE250B Pocket Pencil Signal Injector, £1.90
- SE500 Pocket Pencil Signal Tracer, £1.50
- THL32D Robust 2 K/Volt, £4.55; with case £4.95
- TE15 Grid Dip Meter 440 KHz—280 MHz, £13.45
- 500 30 K/Volt Multimeter, £9.25; with leather case, £10.50
- 200H/20K/Volt Multimeter, £4.20; with case £4.95
- AF105 50K/V Multimeter, £8.50; with case, £9.50
- U431 AC/DC Multimeter with transistor tester with steel case, £10.50
- TE20D RF Generator 120KHz—500MHz, £15.95. Carr. 35p
- TE22D Audio Generator 20Hz—200KHz, £17.50. Carr. 35p
- CI-5 3in Pulse Scope 10Hz—10MHz, £39.00. Carr. 50p
- TE65 Valve Voltmeter 28 ranges, £17.50. Carr. 40p

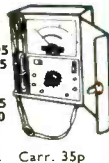

ALL NOMBREX MODELS IN STOCK

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound.

All parts sold separately. Free Leaflet No. 3 & 7. **TOTAL £6.97,** p.p. 20p.
 Decoder Kit £5.97. Tuning meter unit £1.75.
 Mains unit (optional) Model PS900 £2.47. Post 20p.
 Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p.



PA—DISCO—LIGHTING

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

- DJ30L 3 Channel sound to light unit, 3kW, £39.75
- DJ40L 3 Channel Mic (Built-in) to light, 3kW, £38.75
- DJ70S 70 watt Disco amp/mixer, £49.95
- DISCOAMP 100 watt Disco amp/mixer, £67.95
- DJ105S 30 watt Disco amp/mixer, £32.75
- Anti-Feedback Quality Mic, £11.50
- DJ300 50 watt PA amplifier, £56.25
- DJ300 150 watt rms Group Valve amplifier, £99.50



FIBRE OPTICS
 LIGHTING—MICS
 EFFECTS—PROJECTORS—SPOTS
 DIMMERS
 STANDS MIXERS
 SPEAKERS
 Everything for PA—Disco—Lighting. FREE Stock List Ref. No. 18.

SINCLAIR PROJECT 60 MODULES

—SAVE POUNDS

- Z30 £3.57 Z50 £4.37
- STEREO 60 £7.97 PZ5 £3.97
- PZ6 £6.37 PZ8 £4.77
- Transformer for PZ8 £2.95.
- Active Filter Unit £4.45.
- Stereo FM Tuner £16.95.
- IC12 £1.80 Q16's £15 pair.



Post, etc. 20p per item.
PACKAGE DEALS Post 25p
 2 x Z30, Stereo 60, PZ5 £15.95
 2 x Z30, Stereo 60, PZ6 £18.00
 2 x Z50, Stereo 60, PZ8 £20.25
 Transformer for PZ8 £2.95
 PROJECT 60S KIT £19.95

RECORD DECKS

- CHASSIS (Post 50p)
- SP25/3, £11.25 HT70, £15.95
- MP60, £11.25 MP610, £14.75
- AP76, £19.50 GL75, £29.20
- PLINTH/COVERS (State Model)
- SP25/MP60/610 £3.65 (Post 40p)
- AP76 £4.50 (Post 40p)
- CART/PLINTH/COVER (Post 70p)
- (HL) MP60/G800H/PC £18.95
- MP610/SC5MD/TPD2/PC £19.95
- AP76/M756SM/PC £32.50
- AP96/M756SM/PC £39.95
- (HL) AP76/G800/PC £29.95
- (HL) SP25/G800H/PC £19.95
- HT70/G800/TPD1/PC £27.00
- (HL) Z025/9TAHCD/PC £14.95
- MP60/SC5MD/PC £17.25
- (HL) GL75/G800E/PC £44.50
- (HL) GL75/G800/PC £39.95

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits. **PRICE PER PAIR £5.90.** Post 10p.

MARRIOT TAPE HEADS

- 4 TRACK MONO or 2 TRACK STEREO
- "17" High Impedance £2.00
- "18" Med. Impedance £2.00
- "36" Med.-Low Imp. £3.50
- Erase Heads for above 75p
- "63" 2 track mono — High Impedance £1.75
- "43" Erase Head for above 75p

POWER INTEGRATED CIRCUITS

Plessey SL403D—3 watt with 8-page data, layouts and circuits £1.50. P.C. Board 60p; Heat Sink 14p. Sinclair IC12—6 watt with data and circuits £1.80. TH9013P—20 watt Power Amp Module £4.57. TH9014P—IC Pre-amplifier £1.50. Data/Circuits (No. 42) for above 10p.

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
 XN3, XN13, GN6 0-9 side view with data, 85p.
 GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
 3015F 7 seg. £2 each, £7 per 4 with data.
 12 and 24 hour clock circuits. Ref. No. 31 15p.

MINIATURE AMPLIFIER

5 transistor. 300mW o/p. Fitted volume and sensitivity control 9 volt operated. £1.75 each, p.p. 15p.

QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ, 1 meg. Log and Lin. 45p each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, Log and Lin. ganged. 75p each.

HI-FI AND TAPE EQUIPMENT

Acknowledged as U.K.'s Largest Stockist with Lowest Prices Plus 12 Months Guarantee. Write or call for FREE 16 page lists (Ref. No. 17)



MORE OF EVERYTHING ALWAYS AT HENRY'S

All the parts you need plus Data and Circuits. Get a Catalogue—it's all in there! Prices subject to change without notice. E. & O.E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H