

PRACTICAL

ELECTRONICS

APRIL 1976

35p


SPECIAL 8 PAGE

**SOUNDS
EXTRAORDINARY
ELECTRONIC EFFECTS IN MUSIC
SUPPLEMENT**

PE

DIGI-PROBE

a useful
easy to use
instrument

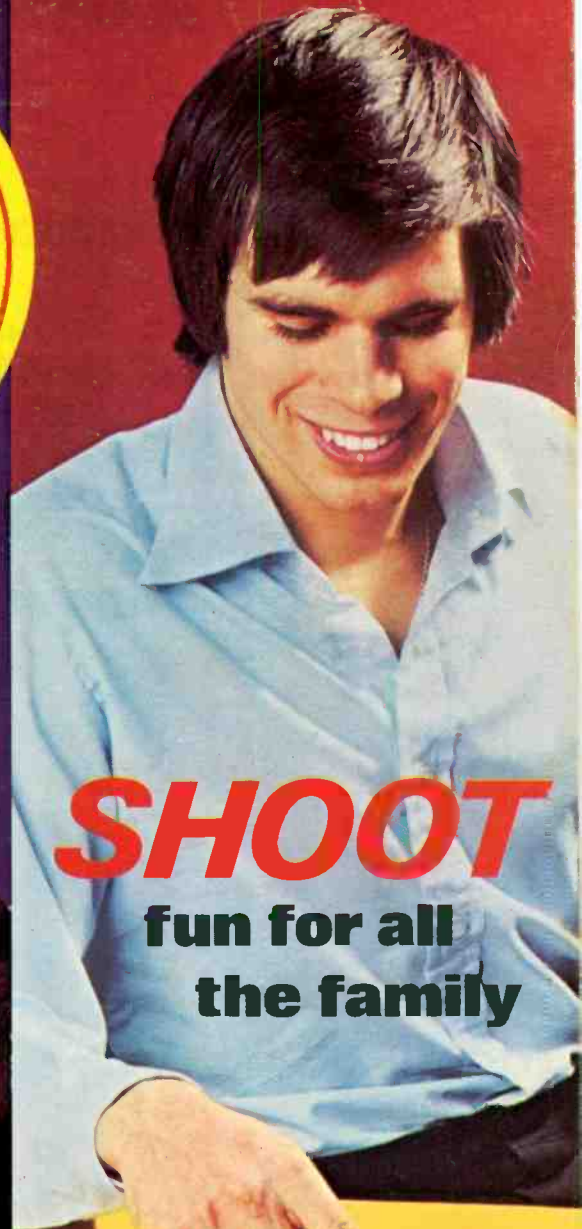

SHOOT

fun for all
the family

PRACTICAL ELECTRONICS

VOLUME 12 No. 4 APRIL 1976

CONSTRUCTIONAL PROJECTS

- P.E. DIGI-PROBE** *by B. Cullen & R. W. Coles*
A logic state monitor with 3-state indication 288
- ADSR ENVELOPE SHAPER** *by P. R. Williams*
An ADSR design which includes a VCA 293
- D.C. MILLIVOLTMETER** *by H. T. Kitchen*
Uses operational amplifier techniques to achieve good sensitivity and high input impedance 305
- SHOOT** *by P. Adams*
Challenge your reaction time with this ingenious game 318

GENERAL FEATURES

- USING CMOS DIGITAL I.C.s—4** *by D. B. Johnson-Davies & A. M. Marshall* 300
Linear applications and circuits for a tachometer and an oscilloscope trace doubler
- TIME CONSTANTS** *by D. Maynard* 309
A look into this sometimes confusing subject
- INGENUITY UNLIMITED**
Electronic Flasher—Patch Board—Transistor Tester—Electronic Dice—Car Battery Condition Indicator—Frequency Changer—Relay Operation—BCD to 7-Segment Decoder—Tuning Indicator—Car Alarm—Sound to Light Modulator—7-Segment to BCD Encoder—Auxiliary Power Supply—Thyristor Windscreen Wiper Delay 324

NEWS AND COMMENT


- EDITORIAL—Order In The Ranks** 287
- SPACEWATCH** *by Frank W. Hyde* 296
Helios 2—Target Saturn—The Sun—China
- HOW INVENTIVE WERE YOU?** 299
A report from the judges of the Plessey/P.E. competition
- SEMICONDUCTOR UPDATE** *by R. W. Coles* 313
A look at some recently released devices
- NEWS BRIEFS** 314
Digital Watches—IBA Handbook—BS9000
- MARKET PLACE** 322
Interesting new products
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith* 323
Electronic music matters
- PATENTS REVIEW** 335
Thought provoking ideas on file at the British Patents Office
- INDUSTRY NOTEBOOK** *by Nexus* 336
What's happening inside industry

SPECIAL 8-PAGE SUPPLEMENT


- SOUNDS EXTRAORDINARY** 1-8
An account of the many different electronic effects used in music today

Our May issue will be published on Friday, April 9, 1976
(for details of special free piece of Veroboard and other contents, see page 315)

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

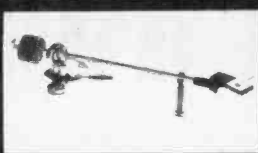

New from Connoisseur - BD3 Transcription Unit
 With a studio style rising turntable giving accurate cueing. Run up time is only a fraction of a second.
 Other important features include an external power source and consequently no hum field. A belt driven turntable with neon illuminated stroboscopic disc with 3 speeds, 33, 45 and 78 - all featuring variable control.
 The BD3 arm is lightweight and incorporates a unique method of magnetic stabilisation with an interchangeable head shell tracking cartridges down to 0.6 grams.

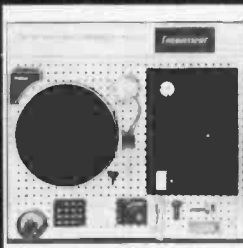

*Connoisseur
 Sound
 Design*



The unit features brushed aluminium trim and is mounted on a matched wooden plinth complete with acrylic dust cover.
BD2 Turntable Assembly
 The famous BD2 belt drive turntable features push button speed change, an SAU2 pick up arm with damped lowering device, brushed aluminium trim, and specially designed turntable mat.
 It is available in chassis form, or as illustrated mounted on a slimline wooden plinth, with acrylic cover which features an easy hinged on hinged off movement.



BD1 Turntable Kit
 The BD1, well known for its excellent performance and superb quality is available in kit form, which allows greater freedom of choice for the practical enthusiast with regard to mounting, selection of arm etc. Construction is simplicity itself with no soldering required. Now it's easy to own the best.


Top left: The BD1 Turntable Kit.
 Top: The SAU2 pick up arm.
 Top right: The BD2 Turntable Assembly.
 Right: The BD3 Transcription Unit.

SAU2 Pick Up Arm
 Recognised as one of today's most advanced pick up arms. Among its star features is an Auto Bias compensator, hydraulic lowering device, precision balance and an adjustable head shell which can be matched to a wide variety of decks and pick up cartridges, ideal for the demanding practical audiophile.
 For further details of all Connoisseur products, the BD3 or BD2, the BD1 kit or SAU2 arm, to the still popular SCUI cartridge and our precision stylus balance, please contact your dealer or send a stamp for brochure.

Connoisseur Manufactured by:
A. R. Sugden & CO. (Engineers) Ltd. Atlas Mill Rd, Brighouse, Yorks, HD61ES
 Tel: Brighouse (04847) 2142. Telegrams & Cables: Connoisseur, Brighouse.

Dimmit
 range of light
 dimmers and lighting
 control systems

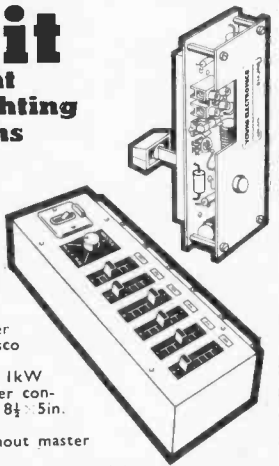Illustrated is the popular PMSD1000 module. A 1kW slider control dimmer, interference suppressed, 60mm slider range size 4½ x 2 x 1½ in. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £8-60 inc. VAT and postage and packing.



Complete compact light dimmer systems for stage, club and disco lighting, etc.

DD61M (illustrated). Six 1kW channels, six outlet sockets, master control, mains on/off switch, size 23 x 8½ x 5in. Price £108-00 inc. VAT.

DD61. As DD61M but without master control. Price £86-40 inc. VAT.

DD61-B. Six 1kW channels, using module PMSD1000, lowest cost system. Size 16½ x 8 x 5in. Price £54-00 inc. VAT.

DD62M. As DD61M but with six 2kW channels, size 25 x 10½ x 6in. Price £156-60 inc. VAT.

DD62. As DD62M but without master control. Price £129-60 inc. VAT.

Add £2-20 postage and packing for all systems.

The Dimmit range includes rotary and slider control dimmers and sound to light converters for home, entertainment and professional applications. Ratings 1kW, 2kW, 3kW.

All products are guaranteed and are supplied with full instructions and applications. Full after-sales service. Technical advice given.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Callers welcome, visit our showroom for a demonstration of any of the modules or systems. Mon.-Fri. 9.30 to 6.0 p.m. Sat. by arrangement.

YOUNG ELECTRONICS LTD.
 184 Royal College Street, London NW1 9NN Tel. 01-267 0201

FREE
 YOURSELF FOR A
BETTER JOB WITH **MORE PAY!**



Do you want promotion, a better job, higher pay? New Opportunities shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.
 This helpful guide to success should be read by every ambitious engineer. Send for this helpful 44 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!
 Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Practical Radio and Electronics (Technatron)	<input type="checkbox"/> C & G Radio TV & Electronics, Mechanics Radio Amateurs	<input type="checkbox"/> C. & G. LI Installations and Wiring
<input type="checkbox"/> Electronic Engineering	<input type="checkbox"/> Practical TV Colour Television	<input type="checkbox"/> General Electrical
<input type="checkbox"/> Television Maintenance and Servicing	<input type="checkbox"/> Servicing Computer Electronics	<input type="checkbox"/> Engineering
<input type="checkbox"/> General Radio and TV Engineering	<input type="checkbox"/> C & G LI Radio TV Servicing cert.	<input type="checkbox"/> Society of Engineers (Electrical Engineering)
<input type="checkbox"/> Radio Servicing, Maintenance and Repairs	<input type="checkbox"/> Post Master General 1st & 2nd class certs.	<input type="checkbox"/> Electrical Installations and Wiring
	<input type="checkbox"/> C. & G. Electrical Engineering Practise	<input type="checkbox"/> C. & G. Electrical Technicians (Primary)
		<input type="checkbox"/> C. & G. Telecommunications

To **ALDERMASTON COLLEGE** Dept. EPE 16
 Reading RG7 4PF
 Also at our London Advisory Office, 4 Fore St. Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-428 2721.
 NAME (Block Capitals Please) _____
 ADDRESS _____
 POSTCODE _____ Age _____
 Other subjects _____
 Accredited by C.A.C.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

RETURN OF POST MAIL ORDER SERVICE

R.C.S. 10 WATT AMPLIFIER KIT



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. A mono kit or a stereo kit. The mono kit uses 13 semiconductor. The stereo kit uses 22 semiconductor with printed front panel and volume, bass and treble controls. Spec. - 10 watts output into 8 ohm, 7 watts into 15 ohms. Response 20 CPS to 30 K/C.S. Input 100 M.V. high imp. Size 9 1/2 in. x 3 in. x 2 in.

Mono kit **£12-50** Stereo kit **£20** post 45p
Easy to build. Full instructions supplied.



ELAC 10 inch

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts **£5-50**

TEAK VENEER HI-FI SPEAKER CABINETS

Fluted Wood Fronts

MODEL "A". 20 x 13 x 12 in. For 12 in. dia. **£12-50** Post Baker speaker. 75p

MODEL "B". 16 x 10 x 9 in. For 13 x 8 in. **£6-95** Post EMI speaker. 45p

LOUDSPEAKER CABINET WADDING 18 in. wide, 20p ft.

BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft. HI-FI CABINET £21-50. Carr. £2 each. Few only. Size 30 x 20 x 12 in. Teak Finished Fluted Front.


TEAKWOOD LOUDSPEAKER FRONT GRILL
Modernise your cabinets with the Grooved look. 10 1/2" x 7 1/2" 45p.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER

Will mix Microphone, records, tape and tuner with separate controls into single output 9 volt battery operated. **£5-20**

STEREO VERSION OF ABOVE £6-85.

R.C.S. STEREO FM TUNER

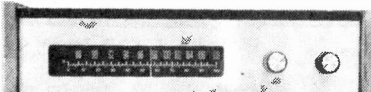

This completely cased mains powered Hi-Fi Tuner with brushed aluminium face is British made using the latest circuitry. Bargain **£30** Post 45p.

BARGAIN 8 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£3-95**

WAFER HEATING ELEMENTS

THIN

Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V. a.c. 250 watts approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos.

ONLY **40p EACH** (FOUR FOR £1-50)
ALL POST PAID—Discounts for quantity.


E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With flared tweeter cone and ceramic magnet, 10 watt, 8 ohm. **£3-45**
Bass res. 45-60 cps. Flux 10,000 gauss. Post 45p

With tweeter. **£5-25**
And crossover. 10 watt. Size 3 or 8 ohm. As illustrated. Post 45p
15 watt model 8 or 15 ohm £8.



BAKER MAJOR 12" £11-50

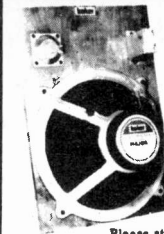

Post 50p
80-14,500 c/s. 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c/s. Rated 25 watts. NOTE: 8 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14-50**
As illustrated. Post 50p
Please state 8 or 8 or 15 ohms. Post 80p

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£8-95**
12 in. 30 watt
3, 8 or 15 ohms. Post 40p

GROUP "35" **£10-50**
12 in. 40 watt
3, 8 or 15 ohms. Post 40p

GROUP 50/12 in. **£14-50**
80 watt 8 or 15 ohms Post 80p

GROUP "50" **£19-50**
15 in. 75 watt
8 or 15 ohms. Post 80p

Group + PA Cabinets in stock Send for Leaflet.



BAKER 50 WATT ALL PURPOSE TRANSISTOR AMPLIFIER



All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 2 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. **£49** Carr. £1-00


NEW 'DISCO 100 WATT' **£55**
ALL PURPOSE AMPLIFIER CHASSIS Carr. £1
2 inputs. 4 outputs separate volume treble and bass controls. Ideal disco or slave amplifier chassis.

PW SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three 1000 watt channels. As featured in December Practical Wireless. **£12-50** CABINET extra £3.

GOODMANS CONE TWEETER
18,000 cps. 25 watts 8 ohm. Price **£3-60**

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS

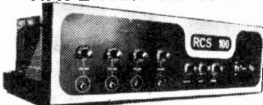

Professional model. Four inputs. Treble, Bass, Master, Volume Controls. Ideal disco, P.A. or groups. S.A.E. for details. 5 speaker **£85** plus £1-50 carr. outputs, very robust job. Suitable carrying case £18-50

E.M.I. GRAM MOTOR **£1-25**
120v. or 240v. A.C. 2,400 rpm. 2-pole Post 20p
70mA. Size 2 1/2 x 2 1/2 in.

E.M.I. TAPE MOTOR **£2-00**
4 pole, 140 v. 185 mA. Post 30p
1400 rpm Spindle 1/4 in. diameter. 120v version £1. (Illustrated). Size 3 1/2 x 2 1/2 in.



NEW BSR HI-FI AUTOCHANGER STEREO AND MONO

Plays 12", 10" or 7" records Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 18 1/2 x 11 in. Above motor board 3 in. Below motor board 2 in. With STEREO/MONO CARTRIDGE **£10-95**
Tubular Arm & Cueing device Post 75p



PORTABLE PLAYER CABINET £4-50

Modern design. Size 16 1/2 x 15 1/2 x 7" casing Post 50p. Covered. Large front grille. Hinged Lid. Chrome fitting. Motor board cut for Garrard or BSR deck. Few only. in red and black

HEAVY METAL PLINTHS

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Model "A". Size 12 1/2 x 14 1/2 x 7 in. **£5-95**
Model "B". Size 16 x 13 1/2 x 7 in. £6-50 Post 75p



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/comp. cartridge. Base-plate. Size 11 in x 8 in. Turntable. Size 7 in diameter. A/C mains. 220/250V.

3 speeds plays all size records. **£6-95** Post 45p
Two for £13. Post 75p

TINTED PLASTIC COVERS

Sizes: 'A'—14 1/2" x 12 1/2" x 4 1/2", £2-50. 'B'—20 1/2" x 12 1/2" x 4 1/2", £3. 'C'—17 1/2" x 13 1/2" x 3 1/2", £3-25. 'D'—19 1/2" x 14 1/2" x 4 1/2", £3-50. Ideal for record decks, tape decks, etc. Post 45p.


BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

SUPERB

12 in. 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps Flux Density 16,500gauss Useful response 20-17,000cps 8 or 15 ohms models.


£17-00 Post 80p

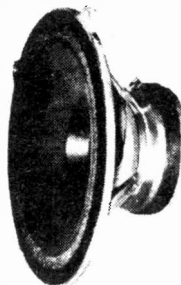

AUDITORIUM 12 in. 35 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Disco-theques. Bass Resonance 35cps Flux Density 15,000gauss Useful response 25-16,000cps 8 or 15 ohms models.

£15-50 Post 80p

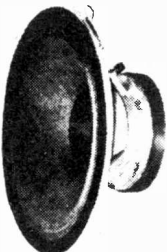

AUDITORIUM 15 in. 45 watts

£19-50 Post 80p
Bass Resonance 35cps Flux Density 15,000 gauss Useful response 20-14,000 cps 8 or 15 ohms models.

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)
Rail Selhurst. Tel. 01-684 1665

Minimum post 30p. Access and Barclaycard Welcome. Radio Books & Components Lists 10p.

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation. . .

Each of the 6 volumes of this self-instruction course measures 11½" x 8½" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers. Design of Digital Systems.



£5.95

plus 50p packing and surface post anywhere in the world.

Payments may be made in foreign currencies.

Quantity discounts available on request.

VAT zero rated.

Also available—a more elementary course assuming no prior knowledge except simple arithmetic. Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£3.95

plus 50p P. & P.

Offer Order both courses for the bargain price £9.25, plus 50p P. & P.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises (Dept. ENG)
FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR

*Please send me . . . set(s) of Design of Digital Systems at £6.45 each, p & p included

*or . . . set(s) of Digital Computer Logic and Electronics at £4.45 each, p & p included

*or . . . combined set(s) at £9.75 each, p & p included

Name

Address

*delete as applicable
No need to use a stamp—just print FREEPOST on the envelope. PE4

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4J5
Phone: 888-4474

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)

£18.50 plus 75p. P. & P. + 8%.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

- ★ Completely portable.
- ★ Solders up to 150 joints per charge.
- ★ Recharges in its own stand.
- ★ Fine tip for all types of soldering.
- ★ Only 8in long and weighs just 6 ozs.

OUR PRICE £9.75 + 8%.
(Spare bits are available)

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or chassis panels with metal front plate fitted with four screws (all supplied). An ideal box to give a small project a professional finish. SIZE (internal) 81mm x 51mm x 25mm.

OUR PRICE 40p. + 8%.



U.K. CARRIAGE 50p UNLESS OTHERWISE STATED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD. IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ **THE POWER AMP MODULE**
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ **THE PRE-AMP MODULE**
Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ **THE POWER SUPPLY**
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. £27.50, carr. £1.20. Send S.A.E. for further details on this or our ready built amplifiers. + 8%.

12-0-12V 500M/A

240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price £1.80. + 8%.

TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket. Fully extended 43". Fully closed 7". Our Price 50p + P/P + VAT @ 25%.

Low Voltage Stereo Amplifier

8 transistor stereo amplifier with volume, bass, balance and tone controls. Approx. 3W into 8 ohm per channel. Needs a 9/12V d.c. supply and is complete on a 2½in x 7½in P/C board. Ideal for domestic record players, etc.

A BARGAIN AT £5 + 25% VAT

12in. LONG PERSISTENCE CRT. Full spec. Price £8.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £8.25, P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £8.75, P. & P. 35p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8.85 each. SINE WAVE only £8.85 each. P. & P. 35p. (Not cased, not calibrated.) GRATICULES 12cm x 14cm high quality plastic 15p each, P. & P. 8p.

*Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of ELECTRONIC GOODIES for £1.78. Post paid.

*METER PACK—3 different meters for £2. P. & P. 55p.

MIN TRANSFORMER. 240V input, 3V 1A output. Brand new 85p each, P. & P. 20p.

P.C.B. PACKS. S. & D. Quantity 2 sq. ft.—no tiny pieces. 50p, P. & P. 37p.

*CAPACITOR PACK—50 brand new components, only 50p, P. & P. 37p.

SOME OSCILLOSCOPES ALWAYS AVAILABLE. S.A.E. stating specification and price range.

*TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/80pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 15p.

*PHOTOCELL equ. OCP71, 13p each.

*MULLARD OCP70, 10p each.

LISTS OF EQUIPMENT, etc., now available. S.A.E. please. Callers always welcome.

*MODERN TELEPHONES. Type 708: two tone grey or black, £3.75 each. Style similar to Type 748: grey, or black, £3 each. As above but discoloured, grey only, £2 each. P. & P. all types 45p each.

*HANDBETS. Complete with 2 inserts and lead. £1.25 each, P. & P. 37p.

*DIALS. ONLY 50p each, P. & P. 25p.

*HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1.75, post paid.

*CRYSTALS. 4 43MHz. Brand new. £1.25 each. P. & P. 15p.

RESETTABLE COUNTERS—4 digit by Sodeco/Stonebridge. 1,000 ohm coll. £2 each. P. & P. 35p.

*BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each, P. & P. 15p; 10-99 10p each, P. & P. 25p; 100-999 7p each, P. & P. free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each. Carr. £2.

*1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p, P. & P. 15p.

VAT NOT INCLUDED IN PRICE
Goods marked * 25% VAT, otherwise 8%
OPEN 9 a.m. to 5.30 p.m. ANY DAY



CHILTMead LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel. Reading 582805





WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£8-64
Baker Group 35, 3, 8 or 15 ohm	£10-25
Baker Group 50/12 8 or 15 ohm	£14-00
Baker Group 50/15 8 or 15 ohm	£18-62
Baker Deluxe 124 8 or 15 ohm	£13-75
Baker Major 3, 8 or 15 ohm	£11-87
Baker Super 8 or 15 ohm	£18-12
Baker Regent 12in 8 or 15 ohm	£10-00
Baker Auditorium 12in 8 or 15 ohm	£16-25
Baker Auditorium 15in 8 or 15 ohm	£21-56
Celestion G12M 8 or 15 ohm	£12-95
Celestion G12H 8 or 15 ohm	£15-95
Celestion G12/50 8 or 15 ohm	£16-50
Celestion G12/50TC 8 or 15 ohm	£18-00
Celestion G15C 8 or 15 ohm	£26-95
Celestion G18C 8 or 15 ohm	£34-50
Celestion HF1300 8 or 15 ohm	£7-75
Celestion HF2000 8 ohm	£9-50
Celestion MH1000 8 or 15 ohm	£13-50
Celestion CO3K	£4-95
Decca London ribbon horn	£32-00
Decca London CO/1000/8 crossover	£7-50
Decca DK30 ribbon horn	£19-06
Decca CO/1/8 crossover (DK30)	£5-00
EMI 150 13 x 8in d/cone 8 ohm	£2-94
EMI 13 x 8in 20W bass 8 ohm	£9-00
EMI 14 x 9in bass 8 ohms, 14A770	£13-25
EMI 8 x 5in, 10W, d/cone, roll surr.	£3-95
EMI 6 1/2in d/cone, roll surr., 8 ohm	£4-37
EMI 8in roll surr. bass	£8-37
EMI 5in mid range	£3-50
Eiac 59RM109 (15 ohm), 59RM114 (8 ohm)	£3-44
Eiac 6 1/2in d/cone, roll surr., 8 ohm	£4-06
Eiac 10in 10RM239, 8 ohm	£3-95
Eagle Crossover 3000Hz 3, 8 or 15 ohm	£1-75
Eagle FR4	£8-12
Eagle FR65	£9-62
Eagle FR8	£12-31
Eagle FR10	£15-62
Eagle HT15	£4-40
Eagle HT21	£6-61
Eagle MHT10	£4-44
Eagle FF28 Multicell. horn	£9-00
Fane Pop 15, 8 or 16 ohm	£5-25
Fane Pop 25T, 8 or 16 ohm	£7-50
Fane Pop 33T, 8 or 18 ohm	£8-75
Fane Pop 50, 8 or 16 ohm	£12-00
Fane Pop 55, 8 or 16 ohm	£15-50
Fane Pop 60, 8 or 16 ohm	£17-25
Fane Pop 70, 8 or 16 ohm	£18-75
Fane Pop 100, 8 or 16 ohm	£25-95
Fane Crescendo 12A, 8 or 16 ohm	£34-50
Fane Crescendo 12BL, 8 or 16 ohm	£36-50
Fane Crescendo 15/100A, 8 or 16 ohm	£47-50
Fane Crescendo 15/125, 8 or 16 ohm	£57-95

SPEAKERS

Fane Crescendo 18, 8 or 16 ohm	£62-95
Fane 910 MK II horn	£14-95
Fane 920 MK II horn	£33-95
Fane HPX1 crossover 200W	£2-50
Fane 13 x 8in, 15W dual cone	£5-50
Fane 801T 8in d/c, roll surr.	£9-95
Gauss 12in 200W	£73-00
Gauss 15in 200W	£83-00
Gauss 18in 200W	£110-00
Goodmans Axent 100	£8-44
Goodmans Audiom 100 15 ohm	£13-90
Goodmans Audiom 200 8 ohm	£13-90
Goodmans Axiom 402 8 or 15 ohm	£20-00
Goodmans Twinaxiom 8, 8 or 15 ohm	£10-55
Goodmans Twinaxiom 10, 8 or 15 ohm	£10-95
Goodmans 8P 8 or 15 ohm	£5-95
Goodmans 10P 8 or 15 ohm	£8-25
Goodmans 12P 8 or 15 ohm	£13-95
Goodmans 12PG 8 or 15 ohm	£15-95
Goodmans 12PD 8 or 15 ohm	£16-95
Goodmans 12AX 8 or 15 ohm	£36-50
Goodmans 15AX 8 or 15 ohm	£45-00
Goodmans 15P 8 or 15 ohm	£22-50
Goodmans 18P 8 or 15 ohm	£39-00
Goodmans Hifax 750P	£16-00
Goodmans 5in midrange 8 ohm	£4-50
Jordan Watts Module, 4, 8 or 15 ohm	£17-06
Kef T27	£6-06
Kef T15	£5-94
Kef B110	£8-37
Kef B200	£9-50
Kef B139	£16-95
Kef DN8	£2-31
Kef DN12	£5-99
Kef DN13 SP1015 or SP1017	£4-50
Lowther PM6	£27-50
Lowther PM6 Mk I	£29-95
Lowther Pm7	£48-00
Peerless KO10DT 4 or 8 ohm	£8-06
Peerless DT10HFC 8 ohm	£9-18
Peerless KO40MRF 8 ohm	£10-31
Peerless MT225HFC 8 ohm	£3-12
Richard Allan CA12 12in bass	£22-00
Richard Allan HP8B	£13-25
Richard Allan LP8B	£9-25
Richard Allan DT20	£8-75
Richard Allan CN8280	£15-00
Richard Allan CN820	£3-50
Richard Allan Super Disco 60W 12in	£16-95
Richard Allen CG15 15in bass	£27-95
Richard Allen Super Disco 12in 60 watt	£15-95
Richard Allen Super Disco 10in 50 watt	£9-95
Richard Allen Super Disco 8in 50 watt	£11-95
Radford BD25	£18-44
Radford MD9	£11-50

Radford MD6	£12-50
Radford TD3	£8-06
Radford Cross Over Network	£14-25

STC 4001G	£6-56
Tannoy 10in HPD	£75-00
Tannoy 12in HPD	£81-95
Tannoy 15in HPD	£97-95
Wharfedale Super 10 RS/DD 8 ohm	£15-00

SPEAKER KITS

Baker Major Module 3, 8 or 15 ohm	each	£14-75
Goodmans DIN 20 4 or 8 ohm	each	£14-75
Goodmans Mezzo Twin kit	pair	£47-19
Helme XLK 30	pair	£10-00
Helme XLK 35	pair	£24-00
Helme XLK 40	pair	£35-00
Helme XLK 50	pair	£58-00
Kefkit 1	pair	£53-00
Kefkit III	each	£48-00
Peerless 20-2	each	£17-44
Peerless 30-28	each	£24-38
Peerless 20-3	each	£26-56
Peerless 50-4	each	£40-50
Peerless 3-15	each	£17-19
Peerless 1060	pair	£56-00
Peerless 1070	each	£48-00
Peerless 1120	each	£50-00
Richard Allan Twin assembly	each	£14-95
Richard Allan Triple 8	each	£22-50
Richard Allan Triple 12	each	£27-95
Richard Allan Super Triple	each	£32-50
Richard Allan RA8 Kit	pair	£42-00
Richard Allan RA82 Kit	pair	£66-00
Richard Allan RA82L Kit	pair	£73-00
Wharfedale Linton II kit	pair	£23-12
Wharfedale Glendale 3XP kit	pair	£56-00
Wharfedale Dovedale III kit	pair	£63-12

HI-FI ON DEMONSTRATION in our showrooms:

Akal, Armstrong, Bowers & Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc.—ask for our Hi-Fi price list!

Complete RADFORD range in stock: amplifiers, preamps, power amps, low distortion oscillator, distortion measuring set, etc.

All items guaranteed new and perfect

Prompt despatch
PRICES INCLUDE VAT AND ARE CORRECT AT
8/2/78

Carriage: 50p per speaker (12in and over 75p each), Tweeters, crossovers 30p each. Kits 80p each (£1-60 pair).

Send stamp for free booklet "Choosing a Speaker"

WILMSLOW AUDIO

Dept P.E.

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire.

P.A., Hi-Fi, etc.: 10 Swan Street, Wilmslow, Hi-Fi, Radio, etc.: Swift of Wilmslow, 5 Swan Street, Wilmslow.

Telephone Wilmslow 29599 (speakers); 26213 (hi-fi, etc.).

Complete kits in stock for Radford Studio 90, Monitor 180, Studio 270, Studio 360, Hi-Fi Answers Monitor, Hi-Fi News No-compromise, Wireless World Transmission Line, Practical Hi-Fi and Audio (Giles) Monitor, etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, etc., free on request.

P.A. amplifiers, microphones, etc., by Linear, Shure, Eagle, Beyer, AKG, etc.

FREE with orders over £10—"Hi-Fi Loudspeakers Enclosures" book.

It's here!

The Minisonic Mk. 2 has arrived—available **NOW** for the first time in kit form, the Minisonic 2 probably represents the best value for money in electronic music today.

Kits are available for complete instruments or individual sections, or for the conversion of Mk. 1 Minisonics to Mk. 2 specification. (Conversion details apply to Eaton Audio P.C.B.s, but may be adapted to suit others.)

In order to ensure that the appearance of the complete instrument enhances its performance, a complete cabinet kit is available, incorporating a **fully finished** black enamelled, silk-screened front panel, with matching back and base, and solid Afrosmosia end-cheeks. This kit also includes all switches, knobs, sockets, screws and panel indicators. Suitable keyboards and contact assemblies are also in stock.

Cabinet Kit Inc. and cheeks, panels, switches, knobs, sockets, LED indicators, etc.
 Kit MS2-1
 Keyboard Kit—3 octave inc. GB contacts
 Kit MS2-2
 Combined Kit—MS2-1 and MS2-2 £192.84
 Keyboard Controller—incorporating long duration "Hold" circuit
 Kit MS2-3 £8.87
 Voltage Controlled Oscillator (including temperature stabilization)
 Kit MS2-4 £16.96
 Note: 2 off MS2-4 are required.
 Envelope Shaper/VCA
 Kit MS2/5 £6.88
 Note: 2 off MS2/5 are required.
 H.F. Oscillator/Detector
 Kit MS2/6 £1.94

Hold Isolator (including relay)
 Kit MS2/7 £3.24
 Voltage Controlled Filter
 Kit MS2/8 £7.54
 Ring Modulator
 Kit MS2/9 £3.75
 Noise Generator
 Kit MS2/10 £2.00
 Output Amplifiers (including panning, mixer and headphone amplifiers—2 channels)
 Kit MS2/11 £6.93
 Control Envelope Inverter
 Kit MS2/12 91p
 Stabilised Power Supply (includes reference supply and the transformer)
 Kit MS2/13 £9.00
 Send large S.A.E. for further details or contents of kits. Some items are contained in two kits, thus a refund will be made when two such kits are ordered together.

Conversion Kits
Ancillary Functions Kit—for conversion of kbd. control, H.F. osc., detector, envelope shapers, V.C. filter, ring modulator, inverter, power supply, reference rails, output stages.
 Kit MS2/14C £11.67
Oscillator Conversion Kit (for one V.C.O. only)
 Kit MS2-15C £11.04

SEPARATE ITEMS
P.C. Boards—Main Board (all modules except power supply, hold isolator, reference supply).
 Board EA014 £3.80
Power Supply Board
 Board EA015 £1.80
 MD 8001 Dual Transistor £1.20
 LM318N high speed op. amp £2.14
 2N5459 Field Effect Transistor 48p
 Multiturn Preset Pots—1k, 10k or 20k (Cormet) 95p



READY-MADE
INSTRUMENTS
AVAILABLE

EATON AUDIO

DEPT. PE, P.O. BOX 3
ST. NEOTS, CAMBS.
PE19 3JB

TERMS: MAIL ORDER ONLY C.W.O. MINIMUM ORDER £1. VAT Please add 25% to value of order inc. P & P unless otherwise stated. Cheques or P.O.s payable to Eaton Audio. Orders over £5 free of P & P otherwise please add 10p in the £1.

New sloping cases from OLSON

Type	Panel Dim	Depth	Height	Price
1	150mm x 100mm	95mm	95mm	£1.55
2	200mm x 100mm	95mm	95mm	£1.75
3	250mm x 100mm	95mm	95mm	£1.95

PLEASE ADD 40p P. & P. and VAT

New range of cases at 45° sloping panels. Attractively designed, of robust construction, and finished in two tone colour. supplied complete with four rubber feet. Available from stock in three different widths.

MATERIALS

Cases made from 20g steel. Front panels made from 20g aluminium.

COLOURS

Cases sprayed in light brown hammer finish. Front panels sprayed in light grey semi gloss enamel.



PORTABLE POWER DISTRIBUTION
 Complete with 6ft cable and 13A plug.
 4 sockets 13A £8.00
 6 sockets 13A £9.50
 4 sockets 13A + 5W £9.15
 6 sockets 13A + 5W £10.10

Please add VAT and 50p post and packaging. Trade counter is open for personal callers from 9 a.m.-5 p.m., Monday-Friday

OLSON ELECTRONICS LTD.
 5-7 LONG STREET, LONDON E2
 Tel. 01-739 2343

P.E. CAR CLOCK with Journey Timer

6-digit clock for use in any car with 12V battery, with an independent journey timer incorporated. Bright Jumbo LED display comes on with ignition—automatic intensity control. Complete kit of all parts needed to build this clock, including case, PCBs and all components. Full instructions, £39.50.

Easy to Build DIGITAL CLOCK (as in Jan E.E.). Kit of all components, including case, etc., for this attractive 4-digit clock with 12mm green display. Full instructions, £16.20.

A complete kit of parts to build this month's P.E. **Main Alarm Clock** will also be available—send large s.a.e. for details and prices or phone for immediate dispatch, £26.80.

50Hz CRYSTAL TIMEBASE KIT for clocks: all parts incl. PCB £6.28.

CMOS ICs	CD4031	1.82	CD4062	7.33	CD4518	1.03	Display Int	
RCA—Mot only	CD4032	0.88	CD4063	0.90	CD4520	1.03	SN75491	0.81
	CD4000	0.17	CD4033	1.16	CD4066	0.58	CD4527	1.30
	CD4001	0.17	CD4034	1.56	CD4067	2.95	CD4532	1.16
	CD4002	0.17	CD4035	0.97	CD4068	0.18	CD4555	0.74
	CD4006	0.97	CD4036	1.82	CD4069	0.18	CD4566	0.74
	CD4007	0.17	CD4037	0.78	CD4070	0.18	MC14508	2.37
	CD4008	0.79	CD4038	0.88	CD4071	0.18	MC14528	0.86
	CD4009	0.46	CD4039	2.86	CD4072	0.18	MC14534	6.04
	CD4010	0.46	CD4040	0.88	CD4073	0.18	MC14553	4.07
	CD4011	0.17	CD4041	0.69	CD4075	0.18	MC14566	1.21
	CD4012	0.17	CD4042	0.69	CD4076	1.27	MCM14552	8.05
	CD4013	0.46	CD4043	0.83	CD4077	0.18		
	CD4014	0.83	CD4044	0.77	CD4078	0.18	Clock Chips	IC Socket
	CD4015	0.83	CD4045	1.15	CD4081	0.18	MK50253	3.60
	CD4016	0.46	CD4046	1.10	CD4082	0.18	MM5314	4.44
	CD4017	0.83	CD4047	0.74	CD4085	0.59	AY51224	3.66
	CD4018	0.83	CD4048	0.46	CD4086	0.59	AY51202	4.78
	CD4019	0.46	CD4049	0.46	CD4089	1.27	MK50250	5.00
	CD4020	0.92	CD4050	0.46	CD4093	0.68		
	CD4021	0.83	CD4051	0.77	CD4094	1.53	CMOS Books	Supports
	CD4022	0.79	CD4052	0.77	CD4095	0.86	No VAT or	24 PIN
	CD4023	0.17	CD4053	0.77	CD4096	0.86	P & P	28 PIN
	CD4024	0.64	CD4054	0.85	CD4099	1.50	RC14975	2.87
	CD4025	0.17	CD4055	1.08	CD4502	0.98	MCM05	2.77
	CD4026	1.42	CD4056	1.08	CD4510	1.12		
	CD4027	0.46	CD4057	20.35	CD4511	1.28	Displays	Verocases
	CD4028	0.74	CD4058	10.64	CD4514	2.56	SLT-01	5.80
	CD4029	0.94	CD4060	0.92	CD4515	2.56	DL704E	0.85
	CD4030	0.46	CD4061	16.43	CD4516	1.12	FND500	1.50
							751410J	2.64
							751411D	3.04
							751412K	4.00

ADD VAT at 8% (higher rate does not apply to any of above). 15p P. & P. on orders under £3 (despatch is by 1st Class Post). Price list and data sent FREE with an order, or on request (an S.A.E. helps). Official orders welcomed (written or phoned). Universities, Polytechnics, Government, Companies, etc. Export orders (no VAT): add 35p (Europe), £1 (overseas) for airmail P. & P.

SINTEL 53b ASTON STREET, OXFORD
 TEL. 0865 49791

ADCOLA

Special offer

A FABULOUS DE-SOLDERING GUN
PLUS THE RENOWN INVADER
SOLDERING IRON


De-Soldering is no longer a problem when you use the de-soldering gun and Adcola Invader soldering iron.

NORMAL PRICE £10.38 **SPECIAL OFFER PRICE £7.25**

If you order the L646 Soldering Iron and de-soldering gun, this offer saves you 30% off the manufacturer's recommended list price for these top quality tools.

DESOLDERING MADE SIMPLE

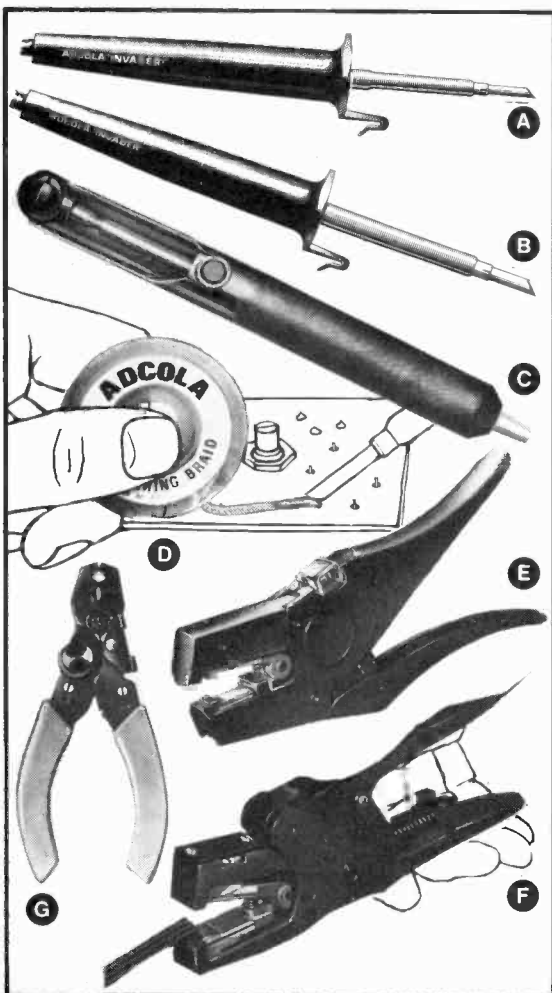- ONE HAND OPERATION
- NO ELECTRICS
- NO CABLES
- TROUBLE FREE




- A L706.** One of the most famous soldering irons in the world, 17 watt, $\frac{1}{8}$ " diameter bit. The best iron for small electronic work priced at £3.76.
- B L646.** As the above described tool but 23 watt, $\frac{3}{16}$ " diameter bit. Efficient, reliable and above all, trouble free. The general purpose soldering tool at only £3.91.
- C FM22.** Easy to use de-soldering gun. Simply press the plunger and place the nozzle over the molten solder as illustrated above. Solder is drawn up into the gun by pressing the release button. Pellets of hardened solder are ejected by depressing the plunger for further use, price £6.47.
- D DE-SOLDERING BRAID.** Used in conjunction with a soldering iron and operates by capillary action. Supplied in 5½ft reels at 98p per reel.
- E FM28.** Lightweight self-adjusting Wire Stripper. Fitted with the famous flexi-jaw consisting of a large number of independent leaf blades enabling the cutting edge when under pressure to surround each conductor. The blades therefore self adjust to wire diameter and cannot damage conductors. Also fitted with a wire cutter. Capacity 0.2mm – 2.75mm. Weight 127gms. The tool for the discerning user at £14.97.
- F FM27.** A slightly heavier version of the FM28 stripper but without wire cutter. Capacity 0.2mm – 3.75mm. Weight 243gms. Price £14.97.
- G FM29.** Wire Stripper/Cutter. An inexpensive quality tool for cutting and stripping wires. The tool has moulded handles, high grade steel blades and a capacity up to 6mm². Priced at £1.96.

All prices include 8% V.A.T.

Please add 30p to all orders for postage and packing.

**BUY AT THESE PRICES
-NOW!**

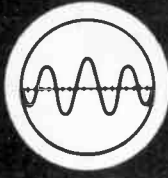
SEND CHEQUE OR POSTAL ORDER NOW TO: ADCOLA PRODUCTS LIMITED, GAUDEN ROAD, LONDON S.W.4. 6LH



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137 9080


MONO DISCO MIXER WITH AUTO FADE

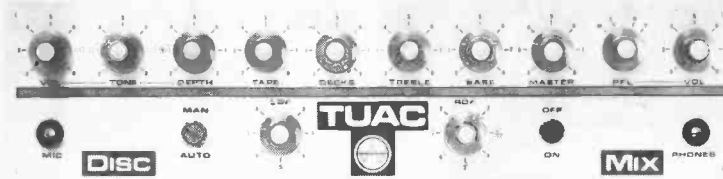

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth, auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.
Specification: Deck Inputs—50mV into 1M Ω ; Deck Tone Controls—treble +20 -10dB at 12kHz, Bass +22 -15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10k Ω ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47k Ω ; Power Requirements—30-50 volts at 50mA.

£31.50
PANEL SIZE
18 x 4½ in
DEPTH 3 in

PRE AMPLIFIERS

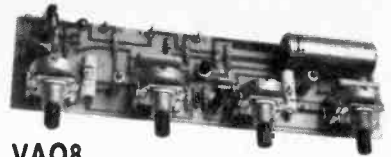

VA08

Designed for use with TUAC power amplifier modules. Extensive research has gone into various wide range tone control circuits to produce superb sound quality. Thousands are already in use in high quality professional amplification systems.

VA08 Vol, Treb, Mid and Bass controls. HI. IMP. FET. I/P suitable Mid. Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 1kHz Bass x20 -10dB at 40Hz.

£6.50

VA06 Vol, Treb, and Bass controls. Sensitivity 8mV. Treb +28 -15dB at 12kHz, Bass \pm 18dB at 40 Hz.


£5.50

SVA08 STEREO PRE AMP Vol, Treb, Mid and Bass controls, I/P suitable, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 4kHz. Bass +20 -10dB at 40Hz Plus Full Balance Control. Full I/C operation supply voltage \pm 15VDC.

£12.50

★ TUAC AMPLIFIER MODULES ★ POWER AND QUALITY ★

- 125 watts R.M.S. continuous sine wave output

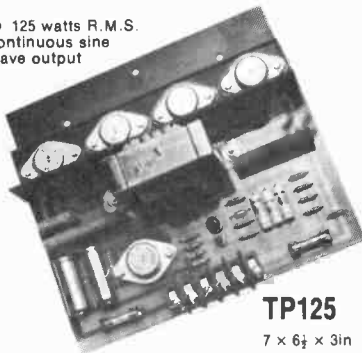


TP125

7 x 6½ x 3 in


£19.50

- 4 R.C.A. 150 watt 15 amp output transistors
- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 6 connections

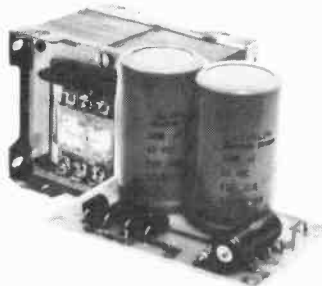Power supplies vacuum impregnated. Transformers with supply board incorporating pre-amp supply:



PS 250 for supplying 2 TP125s	£22.00
PS 60/60 for supplying 2 TL60s	£19.50
PS 125 \pm 45 volts for TP125	£13.75
PS 100 \pm 43 volts for TL100	£12.00
PS 60 \pm 38 volts for TL60	£11.50
PS 30 \pm 25 volts for TL30	£7.50
PSU 2 for supplying disco mixer	£5.50

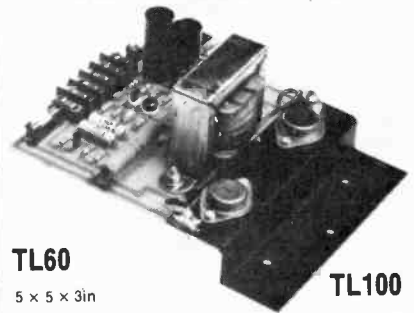

TL60

5 x 5 x 3 in

- 60 watts R.M.S. continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

£13.50

TL100

5 x 5 x 3 in


- 100 watts R.M.S. continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors

£16.25

Specification on all power modules: All output power ratings \pm 0.5dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10k Ω ; Frequency response 20Hz-20kHz \pm 2dB; Hum and noise better than -70dB.

STOCKISTS—CALLERS ONLY

Geo Mathews. 85/87 Hurst Street, Birmingham (Tel. 021-622 1941)
Arthur Sallis Ltd., 28 Gardner, Street (Tel. Brighton 65806)
Bristol Disco Centre, 26 The Promenade, Gloucester Road (Tel. Bristol 41666)
Socodi, 9 The Friars (Tel. Canterbury 60948)
Cookies, 132 West Street (Tel. Crewe 4739)
A1 Music Centre 88 Oxford Street, Manchester (Tel. 061-236 0340)
Damon Electronics, 99 Carrington Street (Tel. Nottingham 53880)
Electra Centre, 58 Lancaster Road (Tel. Preston 58488)
Mitchell Electronics, 64 Winchester Street (Tel. Salisbury 23689)
Mitchell Electronics for Southampton area

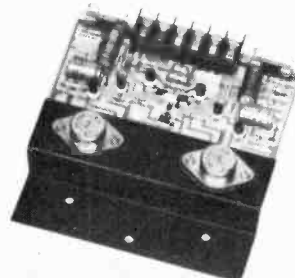

5 x 5 x 1½ in

TL30

NEW FROM TUAC TL30 D.C. COUPLED POWER AMPLIFIER MODULE.

- Output power 30 watts R.M.S. continuous sine wave
- Output impedance 8-15 ohms
- T.H.D. at full power 0.5%
- Signal to noise ratio -85dB
- Input sensitivity 60mV into 50k ohms
- Frequency response 25Hz-50kHz
- 8 transistors
- 4 diodes
- Only six connections

£9.75

Send large stamped addressed envelope with all enquiries or send £1 (refundable against purchase) for fully illustrated 20 page catalogue.

FUZZ LIGHT




**RED GREEN
BLUE AMBER**

240V a.c. Long Life Candle Bulb, Revolving Reflector, adds a new dimension to disco lighting effects.


£19.50

TUAC

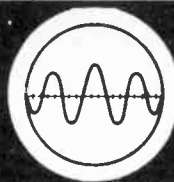

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
PERSONAL SHOPPERS MON, TUES, THURS, FRI and SAT
9 a.m. - 6 p.m. WED 9 a.m. - 1 p.m.

TUAC STEREO DISCO MIXER

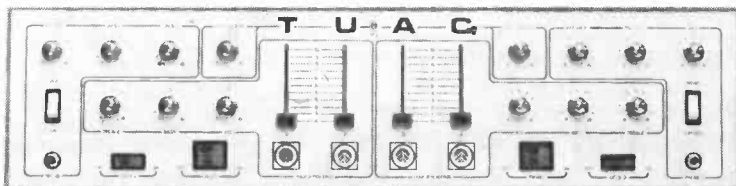


INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble, and bass controls for each pair of sliders. Sensitivity mag., 3mV (R.I.A.A. comp.). Flat 50mV at 1kHz. Bass controls $\pm 18\text{dB}$ at 60Hz. Treble controls $\pm 18\text{dB}$ at 15kHz.

OUTPUT: Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz-25kHz $\pm 1\text{dB}$. P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switch. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.

£75

Size: 25in long x 6in high x 3in deep

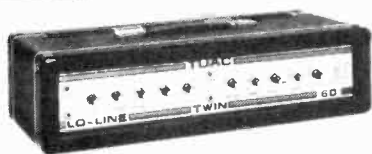

**TWIN
60**

- ★ Lo-Line Twin 125 (125 watts version) **£98.00**
- ★ Lo-Line 60 (single pre-amp version) **£65.00**
- ★ Lo-Line 125 (single pre-amp version) **£81.00**
- ★ Lo-Line 125 slave output power 125 watts R.M.S. **£70.00**

£80.00


Output power 60 watts R.M.S. Four inputs, two channels each with volume, treble, middle and bass controls. Variable wave form control.

▲ All Lo-Line Amplifiers are 25in long x 11in high x 6in deep ▲

NEW TUAC LO-LINE STEREO 250 125 WATTS PER CHANNEL—£130

3 CHANNEL LIGHT MODULATOR

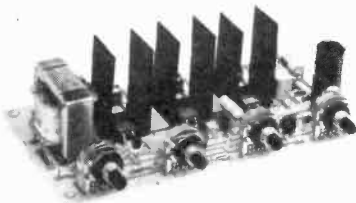
- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections



£15.50 (Single Channel Version 1500 Watts £7.25)


4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER—4LSMI

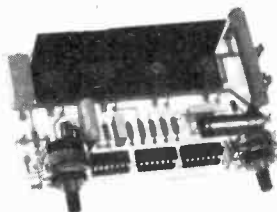- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections



Patents applied for **£17.25**

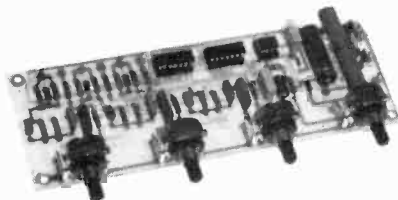ADD SEQUENCE CHASING AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel
- 9 easy connections

SEQUENCE DIMMER MODULE—3SDMI

£11.75

HOW TO ORDER BY POST

Make cheques/P.O.s payable to
TUAC LTD (PE4)
or quote Access/Barclaycard No.
and post to TUAC LTD (PE4)
163 Mitcham Road, London, SW17 9PG
We accept phone orders against
Access/Barclaycard holders
Phone: 01-672 3137/9080


ALL PRICES INCLUDE V.A.T. POSTAGE AND PACKING FREE

ACCESS AND BARCLAYCARD ACCEPTED—JUST SEND OR PHONE US YOUR NUMBER

HP ENQUIRIES INVITED

SENSATIONAL — WORLDBEATING DIGITAL ALARM KIT

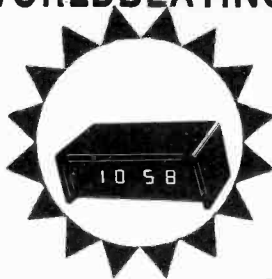- BUILT IN ALARM
- PHOTOCCELL CONTROLLED BRIGHTNESS
- AM/PM INDICATOR
- GIANT 0.5in LED DISPLAY
- POWER FAILURE INDICATION
- SNOOZE FACILITY



£15

ONLY

NB. STANDARD NON-ALARM NOW ONLY £12 IN KIT FORM

CLOCK READY BUILT £21.50

TEAK Case £15.70

INC. VAT & P & P etc.

BARGIN BITS

ALL ITEMS CARRY FULL MFG GUARANTEE. VAT INCLUSIVE
ORDERS UNDER £2 ADD 25p FOR HANDLING CHARGE

- MM5314 Clock Chip 4-6 Digit £2.95
 Gl. AY51202 Clock Chip 4 Digit £4.76
 DS8865N Seg. Driver Chip £0.50
 Futaba 4 Digit Display plus AM/PM £5.94
 Resistors ½W 5% carbon film, most values. £0.10
 Packs of 10 only per pack
 Resistors ½W 5% carbon film, most values. £0.10
 Packs of 10 only per pack
 Resistors 1W 5% carbon film, most values. £0.15
 Packs of 5 only per pack
 Triac 400V 15A isolated tab TO220 £1.98
 Transistors Plastic BC183/213/307 £0.10

- 12V Relays min. IP c/o 330Ω coil £1.80
 LM3900 quad op amp £0.60
 LM309H 200mA 5V reg. £1.15
 741 mini DIP 8 pin £0.31
 IN4001 50V 1A diode £0.04
 IN4148 Small signal diode £0.03
 Fuse holders 20 x 5mm £0.20
 Slide Switch 4 pos. £0.20
 Mains Transformer 110/240V IN £2.00
 0-16.5 at 100mA OUT
 Slide Pot 5K ohm LIN 45mm £0.55
 5-pin DIN plug £0.14
 5-pin DIN Socket Chassis Mount £0.08

- CAPACITORS
 Pack of 5
 0.001 400V 20p
 0.01 400V 20p
 0.022 100V 20p
 0.033 100V 20p
 0.022 250V 35p
 0.01 630V 55p
 0.1 250V 30p
 0.22 250V £1.10
 1µF 250AC
 Mains £0.41 each



CWO
S.A.E. for complete list.

PULSE ELECTRONICS

Dept. P.E.11, 202 SHEFFORD ROAD,
CLIFTON, SHEFFORD, BEDS.

NO HIDDEN EXTRAS!

ALL PRICES INCLUDE VAT. POST FREE IN U.K.
A small selection from our comprehensive range



Transistors	C-mos	THYRISTORS	TTL	LINEAR IC's	BUNDLES	ARROW for ● OVERSEAS ● EDUCATIONAL ● GOVERNMENT
AC128 22p	CD4000AE 19p	CR1/051C 1 amp 50V 68p	7400 11p	741/BDIL 33p	11 x 741/8 DIL £3.00	<p>* ULTRASONICS *</p> <p>40kHz TRANSDUCERS AT LOW PRICE AS USED IN MANY MAGAZINE ARTICLES. PRICE INCLUDES SUGGESTED CIRCUITS. TYPE RL400PP PER PAIR £4.58.</p> <hr/> <p>ARROW SERVICE PLUS TOP QUALITY PRODUCTS BY RETURN. FURTHER DETAILS → VAT Reg. 246 0626 72</p>
AC176 26p	CD4001AE 19p	CR1/401C 1 amp 400V 89p	7402 11p	747/14DIL £1.10	25 x 741/8 DIL £6.50	
AD161 51p	CD4002AE 19p	BTY79/400R 6 amp 400V £2.49	7404 11p	748/TOS 53p	100 x 741/8 DIL £25.00	
AD162 51p	CD4007AE 19p	BT106 1 amp 700V £1.42	7405 11p	CA3018 94p	8 x Red LEDs £1.00	
BC107 12p	CD4008AE 52p	IRC20 1.3 amp 200V 78p	7408 20p	CA3018A £1.08	25 x Red LEDs £2.80	
BC108 12p	CD4010AE 52p	2N3228 5 amp 200V 99p	7410 11p	CA3028A £1.03	100 x Red LEDs £10.00	
BC109 12p	CD4011AE 19p	2N3525 5 amp 400V £1.18	7413 27p	CA3035 £1.78	100 x IN4148 £3.00	
BC109C 21p	CD4012AE 19p	2N4441 5 amp 50V 79p	7417 96p	CA3046 91p	500 x IN4148 £12.00	
BC148 14p	CD4013AE 52p	2N4444 5 amp 600V £2.49	7472 24p	CA3048 £2.74		
BC149 15p	CD4014AE 94p		7473 31p	CA3052 £2.11		
BC158 16p	CD4015AE 94p		7474 31p	CA3080 £0.61		
BC169 16p	CD4016AE 52p	T27000 6 amp 400V £1.14	7475 31p	CA3088 £1.61		
BC169C 17p	CD4017AE 94p	T4700B 15 amp 200V £1.28	7476 40p	CA3089 £2.52		
BC177 23p	CD4018AE 94p	T4700D 15 amp 400V £1.48	7490 55p	CA3123E £1.82		
BC178 26p	CD4019AE 52p	T2800D 7 amp 400V £1.01	7492 68p	MC1303L £2.07		
BC179 26p	CD4020AE £1.04	T2800M 8 amp 600V £1.50	7493 68p	MC1307P £1.79		
BD241A 57p	CD4022AE 89p	2N5756 2.5 amp 400V £1.02	7495 53p	MC1310P £2.86		
BD242A 73p	CD4023AE 19p		74121 40p	MC1330P £1.04		
BD243A 81p	CD4024AE 72p		74122 40p	MFC4000B 92p		
BD244A 88p	CD4025AE 19p		74154 £1.46	MFC6040 £1.49		
BFY51 26p	CD4026AE £1.60	FET's	74196 £1.29	NE555V 63p		
OC45 17p	CD4027AE 52p	MPF102 46p				
OC71 26p	CD4028AE 83p	MPF103 42p				
OC72 26p	CD4029AE £1.06	MPF104 64p				
OC81 36p	CD4030AE 52p	MPF105 42p				
ZTX300 15p	CD4035AE £1.00	MPF119 32p				
ZTX500 15p	CD4040AE 99p	2N3819 55p				
2N706 16p	CD4042AE 78p	2N5245 88p				
2N1711 17p	CD4043AE 94p	2N5457 42p				
2N2926 12p	CD4044AE 87p	2N5458 64p				
2N3053 21p	CD4046AE £1.24	2N5459 42p				
2N3055 15p	CD4048AE 52p	3N128 83p				
2N3702 15p	CD4050AE 52p	3N140 93p				
2N3704 15p	CD4051AE 87p	4048A 50p				
2N3707 9p	CD4056AE £1.22	40673 58p				
2N5777 51p	CD4060AE £2.50					
		UJT's				
		2N2646 64p				
		2N4871 54p				
		2N6027 85p				
		BRY39 75p				
		IR2160 93p				
		TIS43 41p				
		Diacs, etc.				
		S-Dec £2.24				
		T-Dec £4.10				
		µ-Dec 'A' £4.51				
		µ-Dec 'B' £7.75				
		16 DIL				
		Adaptor* £2.07				
		10 TOS				
		Adaptor £1.94				
		*For T-Dec and				
		µ-Dec 'A'				
		OTHER POPULAR ITEMS				
		De-soldering tool £4.66				
		I.C. Test Clip £2.54				
		TBA810S 7 watt I.C. £1.29				
		I.C. Pin Sockets (1000) £7.00				
		I.C. Pin Sockets (100) £1.00				
		CA3401E Quad Op. Amp 84p				
		1 watt Zeners 7.5 to 30V 16p				
		BZY88 Zeners 3.3 to 30V 11p				
		Red LEDs 14p				
		Metal Oxide Resistors 5p				
		½W and ¼W Carbon Resistors 1p				

ARROW ELECTRONICS LTD.

DEPT. PE14, 7 COPTFOLD ROAD
BRENTWOOD, ESSEX CM14 4BN
Tel. 0277 219435 Telex 99443

Co. Reg. No. 1062424

NAME _____
ADDRESS _____

I enclose PO/Cheque for 10p
ARROW ELECTRONICS LTD
DEPT. PE14
7 COPTFOLD ROAD
BRENTWOOD
ESSEX



FROM BI-PRE-PAK

Stirling Sound Products


BECAUSE OF DEMAND AND RE-ORGANISED PRODUCTION THE SUPERB

SS125 HIGH FIDELITY POWER AMP

NOW COSTS **£6.50** INC. POSTAGE AND VAT

- **OUTPUT**—25W R.M.S. into 8Ω using 50V; 22W R.M.S. into 4Ω using 33V (low imp. not less than 4Ω).
- **DISTORTION**—Less than 0.05% at all power levels (from 10Hz to 10kHz).
- **FREQUENCY RESPONSE**—±1dB 15Hz to 30kHz (4Ω); ±1dB 10Hz to 30kHz (8Ω).
- **HIGH Z INPUT**—100kΩ (40dB gain/100×).
- **INPUT SENSITIVITY**—150mV for 25W R.M.D out.
- **SIZE** (inc. heat-sink type mounting bracket)—4½in × 3in × ½in high.


Not only is this Stirling Sound's best audio amplifier yet; it rightfully qualifies as one of the best of its kind yet made available to constructors. Intended above all for high-fidelity, the characteristics of the SS125 are such that it can be used in many other applications where dependability is the prime consideration. The SS125 integrates well with other SS units as well as those of other manufacturers. Incorporates new circuitry using a complimentary long-tailed pair input and full complementary output circuits to give lab. standards of performance.

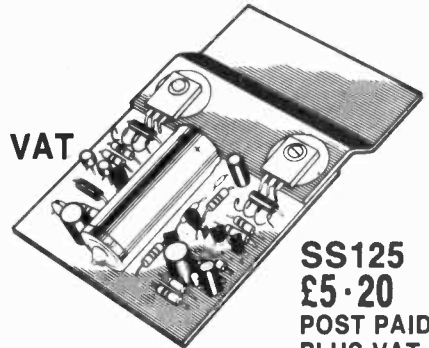

SS125
£5.20
POST PAID
PLUS VAT =
£6.50

... AND 5 NEW STIRLING SOUND POWER SUPPLY UNITS

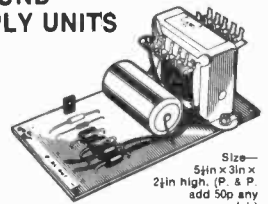Robustly designed units on each of which is a stabilised take-off point to provide power for tuner, pre-amp and control stages, etc.



Size—
5½in × 3in ×
2½in high. (P. & P.
add 50p any
model.)


... FOR CONSTRUCTORS WHO UNDERSTAND QUALITY!

MORE STIRLING SOUND MODULES

With easy to follow instructions

F.M. TUNER UNITS

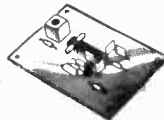- SS201** Tuner front end. Ganged, geared variable tuning, 88-108MHz. A.F.C. **£5.00**
- SS202** I.F. amp. A meter and/or A.F.C. can be connected (size 3in × 2in) **£2.65**
- SS203** Stereo decoder for use with SS201 and SS202 or any good F.M. tuner. A L.E.D. beacon may be attached (3in × 2in) **£3.85**



AUDIO MODULES

- SS105** 5 watt amplifier to run from 12V (3½ × 2in × ½in) **£2.25**
- SS110** Similar to SS105 but more powerful giving 10W into 4 ohms **£2.75**
- SS120** 20 watt module when used with 34 volts into 4 ohms **£3.00**
- SS140** Delivers 40 watts R.M.S. into 4 ohms using a 45V/2A supply such as our SS345. The power and quality of this unit are superb—two in bridge formation will give 80 watts R.M.S. into 8 ohms. Size 4in × 3in × ½in **£3.75**
- SS100** Active tone control, stereo ±15dB lift/cut bass-treble **£1.60**
- SS102** Pre-amp (stereo) inc. line feed back and RIAA correction **£2.25**
- SS101** Pre-amp for ceramic, etc. **£1.60**



- SS312** 12V/1A **£3.75***
- SS318** 18V/1A **£4.15***
- SS324** 24V/1A **£4.60***
- SS334** 34V/2A **£5.20***
- SS345** 45V/4A **£6.25***

(All above are at 8% V.A.T.)

A new Stirling Sound Capacity Discharge Ignition Unit for your car

Even better than the original B-P-P version, thousands of which are in use saving motorists appreciable time and money for petrol. Very easy to instal. The Stirling Sound model incorporates switch for instant change to conventional ignition; immediate adaption to pos. or neg. earth return; anti-burglar immobilising switch, pre-set control for rev. limitation. There are no exposed parts, the unit, on p.c.b., being housed in strong enclosed metal box. With instructions and leads. Size 7½in × 4½in × 2½in ex. switches.

KIT £7.95* **BUILT AND TESTED £10.05***

A USEFUL CATALOGUE—FREE

Send us a large S.A.E. with 10p stamp and we will send you back the latest Bi-Pre-Pak catalogue free by return. Packed with useful lines, it's a real money saver.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 25p for UK orders unless marked otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

Order your Stirling Sound products from

BI-PRE-PAK LTD

Co Reg No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9QF.
TELEPHONE: SOUTHEND (0702) 46344

Make cheques/money orders payable to Bi-Pre-Pak Ltd

TO STIRLING SOUND (BI-PRE-PAK LTD), 220/222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9QF

Please send

..... for which I enclose £.....
Inc. V.A.T.

NAME

ADDRESS

PE2B

AT LAST! THE GREAT RADIO OFFER WE HAVE BEEN WAITING FOR! Think of the year 1984 and what might be produced then—now get the **ASTRAD SOLAR MK 11** and SEE for yourself that the Russians have done it all NOW! It's a radio enthusiast's dream come true! This Brand New, space-age model is so far ahead of its time it will probably make your present radio seem like a "crystal set"! Compare its performance with other radios costing up to £80 or more—we'll refund your money in full if you're not absolutely thrilled! Fantastic specification! Latest advanced solid state, multi-transistor **INTEGRATED CIRCUITS** for maximum selectivity, reliability and interference rejection. Instant **PUSH BUTTON** multi-waveband and function selection. Wider band spread with latest automatic electronic "lock-in" prismatic colour change visual indicator for pin-point tuning, plus "switch-in" automatic frequency control for ultra perfect tuning sensitivity. **EVERY WAVEBAND** instantly at your fingertips including VHF, standard long, medium and a host of short waves to cover the four corners of the earth 24 hours of the day, including all normal stations, local city and regional broadcasts, commercial, pop and continental stations plus an incredible variety of specialised transmissions, short mobile, experimental transmissions and messages from all over the world! Separate Treble and Bass plus ON/OFF, HI/LO volume controls for utter perfection of reproduction and tone. Large single rotary station tuning control. Electronically controlled dial illumination (for use in dark) with energy saving feature. DIN input/output socket for tape recorders, record players, etc. TV style co-axial and additional sockets for short-wave and car aerials, personal earphone, external power supply, etc. **Completely portable**—runs economically on standard batteries obtainable everywhere, or direct through battery eliminator from 220/250V A.C. Mains supply. Also fabulous as a **CAR RADIO!** Beautiful teak effect finish cabinet, size 13½in. x 9½in. x 3½in. overall approx. Incorporating "fold-away" carry handle. Internal ferrite rod aerial plus 31in. telescopic swivel antenna. Complete with full operating instructions and **WRITTEN GUARANTEE** (full U.K. service facilities and spares). **ONLY £28.95** box, post etc. 75p ***BUT WAIT**, for only 85p extra you can also get the sensational **"COMPUTERISED" WORLD TUNING GUIDE** (enables you to zone and time in a flash for transmissions the world over—even lets you know when to tune into the U.K. when abroad—No guessing. No messing!) plus standard long life batteries (send total £30.55). Send quickly. 7 days' mail order approval from receipt of goods. Refund if not delighted. Or call at either store. Access & Barclaycards welcome—Please state number when ordering by post.

HUGE £150,000 CONTRACT secures us **ADVANCE RELEASE** OF BRAND NEW 1976 MODEL specially flown over from **RUSSIA** for us!



RUSSIAN EARTH SHRINKER!
SHRINKS the WORLD to 13½x9½x3½ inches overall!
YEARS AHEAD IN SPACE-AGE TECHNOLOGY, QUALITY, PERFORMANCE, RELIABILITY AND VALUE!

The **1976 ASTRAD SOLAR MK II** PORTABLE RADIO & COMMUNICATIONS RECEIVER

WITH LATEST **AUTOMATIC ELECTRONIC PIN-POINT VISUAL TUNING INDICATOR** with **AUTO-STATION COLOUR CHANGE**

THIS MODEL'S GOT EVERYTHING! 6 INTEGRATED CIRCUIT SETS EQUIVALENT TO

45 TRANSISTORS AND DIODES

WAVEBANDS:

V.H.F. AM/FM PLUS STANDARD LONG, AND MEDIUM **5 SHORT WAVE BANDS TO COVER THE WORLD!** PLUS **AUTOMATIC FREQUENCY CONTROL**

GREAT SALE! OUR EARTH SHATTERING PRICE **£28.95** BOX, POST ETC. 75p (INCLUDES SH. V. A.C.T. NO MORE TO PAY!)

COMPARE PERFORMANCE WITH OTHER RADIOS COSTING UP TO £80!

A THOUSAND in ONE! **GIANT SPEAKER MODEL** with **WORLD WIDE RECEPTION** THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!



* **AVAILABLE WITH FABULOUS "COMPUTERISED" WORLD TUNING GUIDE** No more guesswork—instant data at your fingertips enables you to zone and time in a flash for transmissions the world over!

Dept. PE/45, 164 UXBRIDGE ROAD, LONDON W12 8AQ (Thur. 1, Fri. 7) (facing Shepherds Bush Green). Also 37/39 High Holborn (opposite Chancery Lane), London, W.C.1. (Thur. 7). Both Stores open Monday to Saturday from 9 to 6.

SHOPERTUNITIES LTD.

FREE Brochure on New KITS

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.

Send 15p S.A.E. (10in x 12in) to cover postage
PLEASE NOTE OUR NEW ADDRESS



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits—

- ★ Mullard CCTV Camera
- ★ PE CCJ Camera
- ★ "Mistral" Digital Clock Kit £12.50 (inc. VAT + 50p P. & P.); Built £18 + 50p P. & P.
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

CROFTON ELECTRONICS LTD

Dept. E, 35 Grosvenor Road, Twickenham, Middx. 01-891 1923

- MINIATURE PRINTED CIRCUIT ELECTROLYTICS 2uf 40VW, 64uf 70VW, 100uf 10VW, 100uf 25VW, 100uf 40VW, 150uf 16VW, 150uf 25VW, 300uf 10VW, 300uf 25VW, 330uf 25VW, 330uf 40VW, 470uf 16VW, 680uf 10VW, 680uf 25VW, 1,000uf 6VW. All at 6 for 30p.
- 400 PIV 1 Amp TRIACS 3 for 57p.
- ITT PMT2R METALLISED FILM CAPACITORS 1.5uf 100VW, 6 for 30p.
- VHF NPN TRANSISTORS 600 MHz Type BF 224 at 6 for 57p.
- 8 SILICON NPN PHOTO TRANSISTORS for 57p.
- 18 VOLT 1 Amp TRANSFORMERS 240 Volt Mains Input at 85p.
- TRANSISTOR SPLIT SECONDARY DRIVER TRANSFORMERS 5 for 60p.
- 25 METAL BC107-a-9 TRANSISTORS untested at 57p.
- 200 ASSORTED TUBULAR CERAMICS at 57p.
- TRANSISTOR RF CHOKES 2.5 MH at 12p, 10 MH Tapped at 5 MH at 15p.
- 500yd REEL OF 14 STRAND 0.0048 PVC CABLE at £3.
- 25 ASSORTED TRANSISTOR I.F. TRANSFORMERS at 44p.
- 50 PLASTIC SILICON NPN TRANSISTORS 85% at 57p.
- 50 PLASTIC SILICON PNP TRANSISTORS 85% at 57p.
- BF 180 or BF 181 R.F. TRANSISTORS at 25p each or 5 for £1.
- 250pf SOLID DIELECTRIC TUNING CAPACITORS at 33p.
- VHF DUAL NPN TRANSISTORS with data at 4 for 60p.
- 50 AC 128 TRANSISTORS, branded but untested at 57p.
- 1,000uf 40VW ELECTROLYTICS, size 1½in x ½in at 3 for 35p.
- 20 ITT BRANDED 250mW ZENERS at 75p.
- 20 STC 750mA SILICON RECTIFIERS, branded for 50p.
- TAPE RECORDER MECHANICAL COUNTERS at 20p each.
- MIXED POLYESTER CAPACITORS, approx. 300 to 500 pieces at £1.
- VOLTAGE DEPENDENT RESISTORS E2980-A285, 12 for 57p.
- 100 ASSORTED SILVER MICA CAPACITORS for 57p.
- 1,000pf 10 KVW, DISC CERAMICS at 4p each.
- F.M. I.C.'s similar to TAA 570, untested with data at 5 for 57p.
- SUB-MINIATURE TRANSISTORS, OC57 at 5p, OC58 at 10p, OC59 at 6p, OC60 at 10p.
- TUNING VARACTOR DIODES, type BB110 at 15p, BB121 at 15p.
- 240 VOLT GREEN MAINS NEONS at 25p each.
- POSTAGE STAMP TRIMMERS, 10pf, 30pf, 50pf, 150pf, 750pf, 1,000pf. All at 6p.
- 200 DISC CERAMIC CAPACITORS, assorted for 57p.
- 500 + 500 + 25 + 25pf TUNING CAPACITORS with S.M. Drive at 38p.
- DUAL GATE MOS FET's like 40673 at 33p each, 4 for £1.10.
- 50 ASSORTED TRANSISTOR ELECTROLYTICS at 57p.
- 200 ASSORTED POLYSTYRENE CAPACITORS at 57p.
- ZN 414 RADIO I.C. with data at £1.20.
- 60 ASSORTED WIRE WOUND RESISTORS 1 to 10W at 57p.
- BYX84, 1300 PIV 1 Amp SILICON DIODES 12 for £1.08.

Please add 15p for post and packing on orders under £1.50.

J. BIRKETT
RADIO COMPONENT SUPPLIERS

25 The Strait, Lincoln, LN2 1JF

Tel: 20767

ELECTROTIME

NEW RANGE OF QUARTZ CRYSTAL DIGITAL ELECTRONIC WATCHES

CONTINUOUS
LIQUID
CRYSTAL
DISPLAY
MODEL
TLC 4



£39.00

INC. VAT
and P. & P.

Features

- ★ Hours
- ★ Minutes
- ★ Seconds
- ★ Date
- ★ Backlight for night reading

£39.95

INC. VAT
and P. & P.

Features

- ★ Hours
- ★ Minutes
- ★ Seconds
- ★ Date
- ★ Alpha day

**LED
MODEL**




TLE5

BOTH MODELS AVAILABLE WITH GOLD OR RHODIUM PLATED BRACELET

THE BLACK WATCH

TLE 3
MODEL

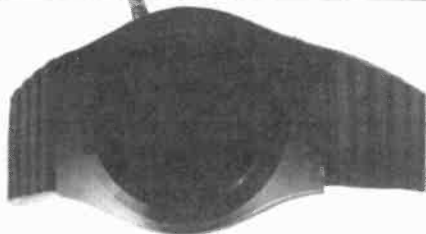- Features**
- ★ Hours
 - ★ Minutes
 - ★ Seconds



INTRODUCTORY
SPECIAL
OFFER
PRICE **£17.99**

INC. VAT
and P. & P.

ALL WATCHES FEATURE

- ★ Solid state—no moving parts
- ★ Quartz crystal controlled
- ★ Accuracy to 5 seconds per month
- ★ Attractive presentation case

ADD TO THE SOPHISTICATION OF YOUR LIFE WITH
THIS UNIQUE DIGITAL ELECTRONIC CLOCK



£14.50 inc. VAT and P. & P.

This remarkable example of modern technology is also available as a fully tested working module.

£13.50 inc. VAT and P. & P.

Money refunded if not completely satisfied.
One year guarantee with all models.

- ★ Large four digit easy read display
- ★ A.M./P.M. indicator
- ★ Flashing seconds indicator
- ★ Brightness control
- ★ Power interrupt indication
- ★ 24 hour alarm
- ★ 5 minute repeating snooze alarm
- ★ Tilt alarm cancel operation
- ★ Attractive white case

**ELECTROTIME, 111 Stortforth Lane Trading Estate
Chesterfield, Derbyshire**

Please supply.....
I enclose cheque money order/postal order

NAME

ADDRESS

.....

.....

SAXON

ENTERTAINMENTS LTD.

SYSTEM 7000

professional standards · realistic prices

NEW! NEW! NEW!

120 WATT RMS POWER AMPLIFIER MODULE —USES 150W 16A RCA DEVICES

Compare these features . . .


- 10 transistors, 4 diodes—fibre glass P.C.B.
- Typical distortion: 0.4%; noise: -80dB
- Short, open circuit proof—load line limiting
- Compact—6 x 3 x 1½ in (15 x 8 x 4cm)
- Only FOUR connections—Simplicity!
- High sensitivity (240mV) suits most mixers
- Frequency response—30Hz-40Hz ± 1dB
- Single supply line—no output capacitor needed (95V)
- Standard 8Ω output—will operate on other impedances



It's
the new
SA1208D
£19.50

ALSO AVAILABLE—60W RMS AND 30W RMS VERSIONS
WITH ALL THE ABOVE FEATURES

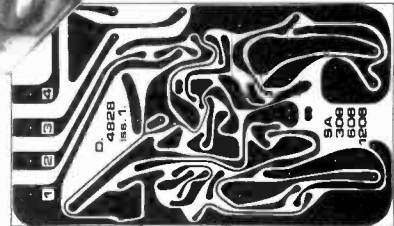SA608 60W RMS into 8Ω (65V) £12.50 **SA308** 30W RMS into 8Ω (48V) £9.50




■ **POWER SUPPLIES** with glass fibre P.C.B. high grade transformer, fully fused and ready to wire: ■ PM120/1 for one SA1208 £11.60; PM120/2 for two SA1208D £15.30; PM601/2 for one or two SA608 £10.50; PM301/2 for one or two SA308 £8.60

SYSTEM 7000 DISCOTHEQUE CONTROL UNIT

Design and performance to professional standards

- Complete and ready to plug in
- Totally encased—no soldering at all!
- Tough, bold, two tone stainless panel—for panel mounting or freestanding
- Mono or Stereo versions
- Front and rear output terminations to suit style of usage
- Inputs for 2 ceramic cartridges/tape/microphone
- Autofade with depth and threshold controls
- Wide range treble and bass controls on both channels
- Individual deck controls and left/right fader
- Low noise (-80dB) 20Hz-50kHz ± 1dB
- Suits all Saxon amplifiers and most other makes
- ½ watt headphone monitor—five-position switch with mute positions

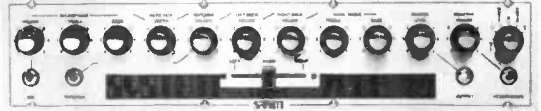

■ **CONTROLS**—Left to right: mic vol treble/bass, autofade depth, L/deck vol, R/deck volume, tape volume, treble, bass, master, monitor volume, monitor selector/on/off

■ **VARIABLE AUTOFADE STAINLESS STEEL PANEL**

Mono £34.50

Stereo £49.50

MODULAR DISCO MIXERS

Mono and Stereo

Printed circuit sub-assembly version of the above mixers—ideal for those wishing to incorporate Saxon's superb specifications into their own systems—all the electronics are provided.

You require only plugs and sockets plus one switch to complete the wiring. All other controls are already mounted on the P.C.B.

Comprehensive wiring instructions are supplied with circuit and diagrams.



Mono £18.50
Stereo £27.50


MULTI-PURPOSE MODULAR MIXERS

A SYSTEM 7000 BREAKTHROUGH—UP TO 20 CHANNELS MONO/STEREO

Both modular and complete types offer the same facilities

■ P.C.B. MODULES:

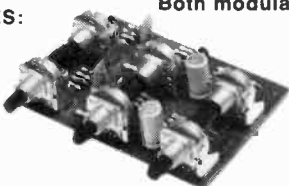- Ready assembled with all controls
- Simple terminations—solder or edge connector
- Consumption 10mA at 18V



■ COMPLETELY WIRED WITH STAINLESS PANEL:

- Inputs for all sources inc. mag. cartridge
- Wide range bass and treble controls
- Only one mixing module required
- Up to twenty channels
- ½W monitor power
- Mono and stereo modules may be used together
- Feeds most amplifiers
- Modern low noise circuitry
- 20Hz-30kHz ± 1dB
- Echo send/return facility
- Complete—ready to plug in or solder
- 5cm matrix—bold panel
- Individual monitor buttons
- Send for details


INPUT MODULES (up to 20 may be used)
Mono 1M7001M £5.50
Stereo 1M7001S £9.00

MIXING MODULE (only 1 required)
Mono 1M7002M £5.50
Stereo 1M7002S £8.00

Provides headphone output and mixes all inputs to output level
SUITS ALL MIXING REQUIREMENTS FOR GROUPS—CLUBS, DISCOS, ETC.

Mono Input module £8.50
Stereo Input module £12.00

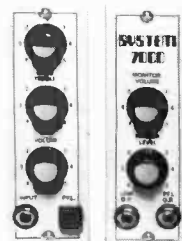Mono mixer module £8.50
Stereo mixer module £12.00



... the complete answer!

SEE SYSTEM 7000 AT OUR SHOWROOMS OR SEND FOR LOCAL STOCKIST LIST

New! TWO STROBES TO MEET ALL REQUIREMENTS

SUPERSTROBE

- Built in Saxon reliability
- 1 flash/2 sec up to 20 flashes/sec
- Compact black Bondene case
- Appearance matches other Saxon units
- Ideal for the mobile disco or smaller club

PRO-STROBE

- Giant 80 watt tube
- Discharge energy up to 6 Joules
- External trigger—audio up to 240V
- May be used with Soundlite to obtain rainbow strobe effect
- Smart, tough Bondene case
- 8in x 8in x 5in approx. (20cm x 20cm x 13cm)



SUPERSTROBE £24.75
PRO-STROBE £38.50

New!

150 WATT LIQUID WHEEL PROJECTOR

- Complete with wheel
- 150 watt tungsten lamp
- Wide range of extra effects may be attached
- Sturdy construction
- Adjustable feet




£29.00 Spare wheels £4.90

TOTAL CONTROL WITH THE SYSTEM 7000 LIGHTING CONTROL UNIT

- Full control of 3kW of lights (1kW/channel)
- Audio control *plus* sequence *plus* override
- Variable speed sequence with slider function control
- Stainless steel two tone panel—matches mixer
- 13 transistors 8 diodes—advanced control circuitry
- High audio sensitivity—operates from any amplifier
- Attractive Bondene case—free standing or panel mounting
- Individual tone controls *plus* master audio control


This exciting unit offers the performance of units offered at nearly twice the price

£38.00 inc. case and plug—ready to use.

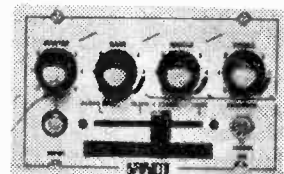

SUPERFECT MODULE

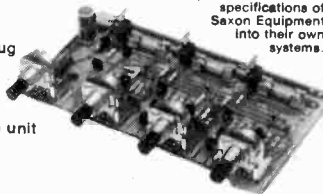- All features as the system 7000 lighting control unit
- Requires only panel and plug socket, etc.
- Slider control supplied
- Glass fibre P.C.B.
- 8 amp RCA triacs
- Complete light show in one unit




This P.C.B. sub-assembly of the system 7000 lighting control unit is recommended for those wishing to incorporate the excellent specifications of Saxon Equipment into their own systems.

With Instructions £24.75

SAXON SOUND-LITE

Our outstandingly successful 3kW converter in module form

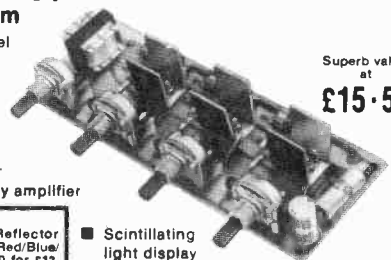- Up to 1kW/channel
- Individual tone controls
- Master control
- RCA 8A triacs
- Glass fibre P.C.B.
- Operates from any amplifier



Superb value at
£15.50

REFLECTORPOD

3-way light banks with twin plug socket complete with reflector lamps—attractive Bondene case with white front.

£15 each


SPECIAL OFFER—Reflector lamps (spots) 100W Red/Blue/Green £1.40 each or 10 for £12.

- Scintillating light display

SYSTEM 7000 MINOTAUR

THE LITTLE AMPLIFIER WITH THE BIG HEART
100W INTO 8Ω

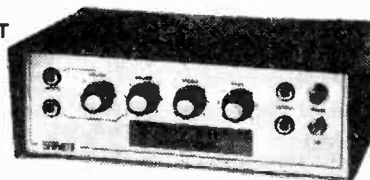- Twin mixed inputs
- Wide range bass and treble controls
- May be used as a slave amplifier
- Twin output sockets
- Two tone anodised front panel
- Fully protected against incorrect loads



With Bondene cover £49.00

£53.00 With Vynide covered wooden case

CHASSIS LOUSPEAKERS 12in 50 watt high-grade Saxon units with 14,000 gauss magnet *plus* presence dome. ONLY £14.50 EACH Full range professional quality

Ask for a quotation for a complete system to your specification—Systems from £280; Consoles from £180

We have a fine selection of consoles, loudspeaker cabinets, etc., on demonstration at our Croydon showroom.

Bona-fide trade enquiries to: NORMAN ROSE ELECTRICAL LTD.—LONDON (01-837 9111); MANCHESTER (061-273 1486); BIRMINGHAM (021-236 4710); BRADFORD (0274 28104).



Access or Barclaycard?



Send or Telephone your number for prompt attention.

After 5p.m. ring 01-684 6385 for our Answerphone service

PRICES include carr. and packing but VAT at 8% must be added to all orders. C.O.D. 65p extra—S.A.E. all enquiries please. CALLERS are welcome at our showrooms at

327-333 Whitehorse Road, Croydon, Surrey CR0 2HS

Orders by post to the same address—Please make cheques or crossed P.O.'s payable to

SAXON ENTERTAINMENTS LTD.

Telephone: 01-684 6385/0098

Shop Hours 9am-5pm (Lunch 12.30-1.30); Sat. 9.30am-5pm. Prices and specifications subject to alteration without notice

Mail Order desk 10am-4pm Mon.-Fri. VAT No. 218 8921 49 RGD ENGLAND 1091983

ENGINEERS

FREE



This 44 page FREE book shows how!

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? New opportunities shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44 page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

- | | | | |
|---|--------------------------|--|--------------------------|
| ELECTRICAL & ELECTRONICS | | Air Registration Board Certs. | <input type="checkbox"/> |
| Practical Radio & Electronics (with kit) | <input type="checkbox"/> | MAA/IMI Dip. | <input type="checkbox"/> |
| Electronic Engineering Certificate | <input type="checkbox"/> | CONSTRUCTIONAL | |
| General Elect. Eng. Certificate | <input type="checkbox"/> | Heating Ventilating & Air Conditioning | <input type="checkbox"/> |
| C. & G. Elect. Installations | <input type="checkbox"/> | Architectural Draughtsmanship & Design | <input type="checkbox"/> |
| Elect. Install. & Work | <input type="checkbox"/> | L.I.O.B. | <input type="checkbox"/> |
| C. & G. Elect. Technicians | <input type="checkbox"/> | Carpentry & Joinery | <input type="checkbox"/> |
| | | Plumbing Technology | <input type="checkbox"/> |
| | | General Building | <input type="checkbox"/> |
| | | Painting & Decorating | <input type="checkbox"/> |
| RADIO & TELE-COMMUNICATIONS | | MECHANICAL | |
| Colour TV Servicing | <input type="checkbox"/> | A.M.S.E. (Mech.) | <input type="checkbox"/> |
| C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> | General Mech. Eng. | <input type="checkbox"/> |
| C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> | Inst. Engineers & Technicians | <input type="checkbox"/> |
| Radio & TV Engineering Course | <input type="checkbox"/> | Maintenance Engineering | <input type="checkbox"/> |
| Radio, Servicing & Repairs | <input type="checkbox"/> | Welding | <input type="checkbox"/> |
| Radio Amateur's Exam | <input type="checkbox"/> | MANAGEMENT & PRODUCTION | |
| | | Computer Programming | <input type="checkbox"/> |
| | | Inst. of Cost & Managements Accts. | <input type="checkbox"/> |
| AUTO & AERO | | DRAUGHTSMANSHIP & DESIGN | |
| Motor Mechanics | <input type="checkbox"/> | General Draughtsmanship | <input type="checkbox"/> |
| C. & G. Motor V. Mechanics | <input type="checkbox"/> | A.M.I.E.D. | <input type="checkbox"/> |
| General Auto Engineering | <input type="checkbox"/> | Electrical Draughtsmanship | <input type="checkbox"/> |
| A.M.I.M.I. | <input type="checkbox"/> | | |

POST NOW

G.C.E.
 —58 'O' & 'A' Level Subjects
 —over 10,000 Group Passes!

Aldermaston College

Dept. TPE 16, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals)

ADDRESS


Postcode

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Build it yourself!

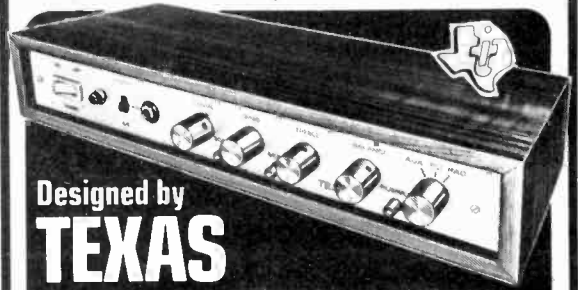

Designed by **TEXAS**

Featured by **PRACTICAL WIRELESS**
 SOLE U.K. DISTRIBUTORS - HENRY'S

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's Kit.

Look at the Texan specification

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall. 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

- ★ Can be built Stage by stage. Ask for leaflet 20.
- ★ Everything necessary supplied. Full after sales service and guarantees.

KIT PRICE
£35.00
 inc. VAT + £1.00 p&p

Built and tested **£45.00** inc. VAT + £1.00 p&p.

THE NATURAL FOLLOW-ON - THE TEXAN FM TUNER KIT!

KIT PRICE
£25.95
 inc. VAT + 50p p&p.

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

Built and tested £30.95 inc. VAT + 50p p&p.

VIDEO SPORT

... all the electronic excitement you could wish for!

★ OVER 10,000 ALREADY SOLD ★ IDEAL GIFT

An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered.



Henry's Price - ONLY **£29.50** inc. VAT + 50p p&p.

WHATEVER YOU DO, DON'T FORGET YOUR LATEST HENRY'S CATALOGUE!



For this new edition, we have made hundreds of changes and additions. It has over 200 pages, containing virtually everything for amateurs and professionals. And you'll have no bother at all finding everything you want, because there's a complete alphabetical index as well as a section index. Together, they put you right on course for the items you need. From Sinclair projects to educational kits. Oscilloscopes to panel meters. Coils to capacitors. Transistors to valves. Loudspeakers to microphones - all at competitive prices. Over 200 pages of vital statistics - just for you! So send now for your copy.

- Over 5000 items inside!
- Every copy contains a free 50p voucher.
- Many new items.
- Over 200 pages.

ONLY **50p**

20p Carr/Pack

FREE to Educational Establishments when ordered on official headed notepaper.

Henry's


SELF-SERVICE CENTRES 404 and 309 EDGWARE ROAD, LONDON W2
 Bargains galore - Call in and see for yourself!

404/6 EDGWARE ROAD, LONDON W2 01-402 8381

LOWER SALES FLOOR, 231, TOTTENHAM CT. RD., LONDON W1 01-636 6681

NEW MIDLANDS STORE 94/96 UPPER PARLIAMENT STREET, NOTTINGHAM. 0602-40403

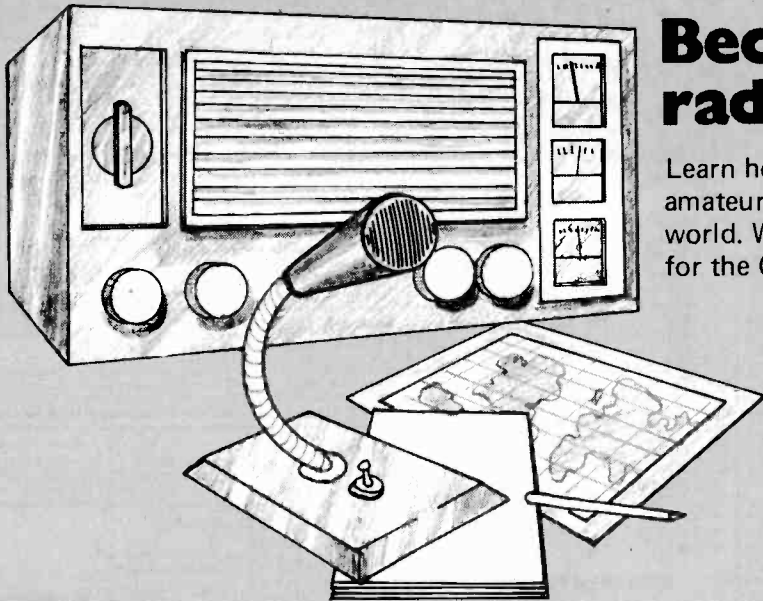All mail to Henry's Radio, 303 Edgware Road, London W2



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. EB46
 P.O. Box 156, Jersey, Channel Islands.

NAME _____
 ADDRESS _____ Block caps please

Free!

P. F. RALFE

10 CHAPEL ST. LONDON NW1 Phone 01-723 8753

MUFFIN INSTRUMENT FANS

Dimensions 4.5in x 4.5in x 1.5in. Very quiet running, precision fan specially designed for cooling electronic equipment, amplifiers, etc. For 110V, a.c. operation (practice is to run from split primary of mains transformer or use suitable mains dropper). CC only 11 watts. List price over £10 each. Our price, in brand new condition, is £4.50.

AVO VALVE TESTERS

Brief-case type 160. Full working condition throughout. £65.

CO-AXIAL CHANGE OVER RELAYS

Suitable for frequencies up to 1000MHz. 48V d.c. coil. Brand new £5.50. 'N'-type plugs available (3 required) at 50p each.

MINIATURE DEAC NI-CADMIUM

batteries type 70DK. 3 cells in package making 3.7V. 25x17x15mm. 75p each.

E.M.I. OSCILLOSCOPES

type RMO15. Response to 40MHz. 5in CRT. 10kV E.H.T. We can offer these quality oscilloscopes at the exceptional price of only £35 to callers only.

500V TRANSISTORISED INSULATION TESTERS

Small size, light-weight, 13x7x4cm. Reads insulation from 0.2 to 100MΩ. Brand new, only £16.50. Battery (PP3), leads and case £1 extra.

ADVANCE type 63A AM/FM R.F. signal generators. 7.5-230MHz Dev. 0-22.5 and 0-75kHz. X-sweep output. Crystal calibrator. Scope output. £75.

250V WEE MEGGER

Insulation testers (wind-up type). Quantity of secondhand, good condition, available at only £8.50.

METRIX TYPE 210

WOBBLATORS

0-25MHz. Sweep width 0.5-20MHz. Output 100mV attenuable in steps of 10 to 10µV. Last few of these left at only £15 each to callers only.

ICL 8-hole tape readers. As new £60.

TELETYPE 8-hole tape punches. £75.

APT power supply units. Stabilised and regulated. 8-10V at 10 amps and 21-25V at 10 amps available. Both supplies are extremely stable with low ripple voltage. £18.50 each.

ALL GOODS QUOTED ARE INCLUSIVE OF POSTAGE AND PACKING BUT EXCLUSIVE OF 8% VAT. USUAL DESPATCH TIME FOR GOODS 1-3 DAYS.

orchard electronics

TRANSISTORS

AC126 20p	ASY67 70p	BC147A 9p*	BC265A 16p*	BC309B 18p*
AC126 20p	BA146 15p*	BC147B 10p*	BC266A 15p*	BC317A 12p*
AC127 20p	BA154 10p	BC148 9p*	BC267A 11p*	BC319B 12p*
AC128 20p	BA155 12p	BC148B 10p*	BC268A 11p*	BC3221 15p*
AC129 35p	BC141 10p	BC149B 11p*	BC269H 13p*	BC327 20p*
AC141 20p	BAX13 4p	BC149C 11p*	BC212A 15p*	BC328 18p*
AC142 17p	BAX16 6p	BC152 8p*	BC212L 16p*	BC328 18p*
AC151 24p	BC107 11p	BC154 18p*	BC213B 12p*	BC338 16p*
AC159 27p	BC107A 12p	BC157B 12p*	BC213L 14p*	BC461 35p*
AC176 20p	BC108 10p	BC158A 12p*	BC214 15p*	BC557 8p*
AC188 20p	BC108B 11p	BC159A 12p*	BC214L 17p*	BC558 9p*
AD161 42p	BC109 11p	BC167A 11p*	BC237A 16p*	BC559 9p*
AD162 42p	BC109B 12p	BC168B 14p*	BC238A 15p*	BCY70 16p*
AF114 24p	BC109C 13p	BC171A 14p*	BC239B 15p*	BCY71 18p*
AF115 24p	BC115 15p*	BC172A 15p*	BC261A 16p*	BCY72 14p*
AF116 24p	BC116 15p*	BC173B 16p*	BC262A 15p*	BD115 60p*
AF117 24p	BC117 18p*	BC177 17p*	BC266A 18p*	BD121 90p*
AF118 47p	BC118 10p*	BC178B 18p*	BC267A 14p*	BD123 90p*
AF124 30p	BC119 28p*	BC179B 18p*	BC268B 13p*	BD124 65p*
AF123 30p	BC123 14p*	BC182B 19p*	BC269 13p*	BD131 38p*
AF126 25p	BC132 11p*	BC183L 11p*	BC287 20p*	BD132 38p*
AF139 34p	BC136 12p*	BC183L 10p*	BC300 27p*	BD133 65p*
AF186 60p	BC136 16p*	BC184B 12p*	BC301 28p*	BD135 37p*
AF239 37p	BC137 18p*	BC184B 12p*	BC302 24p*	BD136 39p*
AS226 30p	BC158 15p*	BC184L 11p*	BC303 30p*	BD137 44p*
AS227 34p	BC130 35p*	BC185 5p*	BC304 27p*	BD138 47p*
AS228 30p	BC142 22p*	BC187 28p*	BC307A 16p*	BD139 54p*
AS229 34p	BC143 24p*	BC204A 16p*	BC308A 14p*	BD135 75p*

INTEGRATED CIRCUITS LINEAR	ZENERS (400 mW)	VOLTAGE REGULATORS (TO3)	DIL Sockets	INTEGRATED CIRCUITS TTL Digital
749 (8 pin DIL) 40p	BZX88/BZY88	5V 1A £1.75	8 pin 13p	7400 18p
741 (8 pin DIL) 43p	4V3, 3V6, 4V9, 5V 1A	12V 1A £1.75	14 pin 15p	7401 20p
NE555 60p	4V3, 4V7, 5V1, 5V 1A	15V 1A £1.75	16 pin 17p	7402 18p
	5V6, 6V2, 6V5, 7V5, 8V2, 9V1			7403 18p
	10V, 12V, 13V, All at 12p each*			7404 23p
				7405 23p
				7406 40p
Bridge Rectifiers	SILICON RECTIFIERS	THYRISTORS	LED	
100V 3A 18p	100V 1A 30p	1N4002 8p	139R RED 20p	7407 40p
W 0 0124p	100V 3A 15p	1N4003 8p	125A AMBER	7408 24p
200V 1A	600V 1A 80p	1N4006 10p		7409 23p
W 0 0225p	200V 3A 18p	BT106 £1.20	125Y	7410 18p
400V 1A			YELLOW 27p	7411 24p
W 0 4 26p			TIL209 RED	7412 25p
			25p	7413 38p

VAT - Items marked * add 25%, remainder at 8%.
Flint House, High Street, Wallingford, Oxon OX10 0DE
 Tel.: Wallingford (0491) 35529 Telex 4SPWALFRD 849349

10% Off on orders over £10
15% Off on orders over £50
20% Off on orders over £100

TTL table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 7400, 7401, 7402, etc.

LOW POWER TTL table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 74100, 74101, 74102, etc.

HIGH SPEED TTL table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 74H00, 74H01, 74H02, etc.

8000 SERIES table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 8091, 8092, 8093, etc.

9000 SERIES table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 9002, 9301, 9312, etc.

CMOS table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 74C00, 74C01, 74C02, etc.

Table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 4060A, 4061A, 4062A, etc.

SHIPMENT MADE VIA AIR-POSTAGE PAID—3 DAYS FROM RECEIPT OF ORDER

APRIL SPECIALS

1/2 PRICE SALE table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 7425, 7430, 7441, etc.

8038 FUNCTION GENERATOR Voltage controlled oscillator sine, square, triangular output 16pin DIP with data £2-50
7001 CLOCK CHIP 4-6 digit, 12-24 hr. alarm, timer & date circuits with data £4-00
MV5020 LED Jumbo red dome 10p

MV5020 Jumbo green -15
XC209-R .125" red LED -10
L100 Red LED -08
L101 Red LED -08

DVM CHIP 4 1/2 DIGIT MM 5336 — P channel device provides all logic for 4 1/2 digit volt meter. 16 pin DIP with data £8

UV ERASABLE PROM 1702A — 2048 bit static PROM 256x8 elect programmable & erasable TTL/DTL comp. 24 pin DIP £8

POCKET CALCULATOR KIT 1 function plus constant — addressable memory with individual recall — 8 digit display plus overflow. Batteries saved — uses standard or rechargeable batteries — all necessary parts in ready to assemble form — instructions included. CALC. KIT WITH BATTERIES £10

CLOCK CHIPS WITH LED's

CT7001 4-6 digit, 12-24 hour clock with alarm, timer & date circuits plus 4 MAN 66.6" LED display above items plus 2 MAN 1 for date £7-95 £9-50

MM5314 clock chip 12-24 hour 4-6 digits Plus choice of 6 MAN 5 green 7 SEG LED .277" 6 MAN 7 red 7 SEG LED .277" 6 MAN 8 yellow 7 SEG LED .277" £5-50

8 DIGIT LED CLOCK KIT INCLUDES: MM5314 clock circuit 6 FN070 LED displays (.250" red 7 segment) All necessary transistors, resistors & capacitors 1 double sided PC board accommodates LED's & clock circuitry Schematic & instructions Does not include 12V-300 ma transformer, switches & case £6-50

NEW ITEMS

TTL table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 74132, 74H101, 74H102, etc.

LOW POWER SCHOTTKY table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 74L500, 74L502, 74L503, etc.

METAL FILM RESISTORS table with columns: QTY, PRICE EACH, PRICE PER VALUE, PRICE PER VALUE. Includes values like 0-10, 10-100, 100-1000, etc.

TANALUM CAPACITORS table with columns: solid-dipped +20% values like 1.0mld 35V 12p, 6.8mld 6V 15p, etc.

LINEARS table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 546, 733, 5556/MC1456, etc.

LED's table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like MV108, MV500, ME4, etc.

MEMORIES table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 1101, 1102, 2102-2, etc.

MULTIPLE DISPLAYS table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like NSN33, HP45082, etc.

CALCULATOR & CLOCK CHIPS table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 5001, 5002, 5005, etc.

SHIFT REGISTERS table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like MMS5013, MMS5016, etc.

DTL table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 930, 932, 936, etc.

Data included with order on request. Add 20p ea. if item is priced below 50p ea. Add 40p ea. if item is not ordered.


LINEAR CIRCUITS

Table with columns: part number, quantity, price, description, quantity, price, description. Includes parts like 300, 301, 302, 304, 305, 307, 308, 309K, 310, 311, 319, 320, 322, 324, 339, 340K, 340T, 372, 373, 376, 380, 380-8, 381, 382, 550, 555, 556A, 560, 562, 565, 566, 567, 709, 710, 711, 723, 739, 741, 742, 748, 1304, 1307, 1458, 1800, 1H2111, 5001, 5002, 5005, MMS5725, MMS5736, MMS5738, MMS5739, MMS5311, MMS5312, MMS5313, MMS5314, MMS5316, 7524, 8038, 8864, 75150, 75451, 75452, 75453, 75491, 75492, 7513, 75133.

MISC. DEVICES 2513 64 x 8 x 5 character generator 6-

Satisfaction guaranteed. Send bank cheque with order. If international money order is used, send receipt with order. The above prices do not include any taxes leviable by a purchaser's country of residence. Minimum order £2-50.

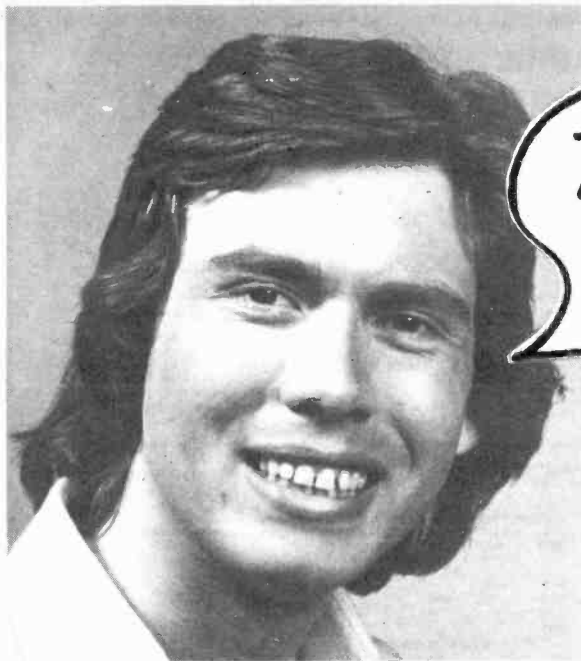INTERNATIONAL ELECTRONICS UNLIMITED P.O. BOX 1708/ MONTEREY, CA. 93940 USA PHONE (408) 659-3171 The above prices do not include any taxes leviable by a purchaser's country of residence



The Managing Director revealed all!



Sometimes I order my bits and pieces from Home Radio Components by post, but often I pop in to their Mitcham shop and buy over the counter. Over the years I've got quite pally with their Managing Director (nice bloke he is too) and the other day we got chatting about the mechanics of producing their catalogue. I was amazed at the amount of work that has gone into it. In fact, you could say that it has taken 20 years to produce, because the present 240-page edition de luxe has gradually evolved from the duplicated effort they turned out in 1956.

The Managing Director says that all through the years he has worked "up to a standard; not down to a price" in producing the catalogue. That principle is evident in every aspect of the catalogue—the illustrations, the indexing, the layout, the method of listing, the quality of printing and so on. It's not surprising that today it is in use all round the world, and is recognised as the finest components catalogue money can buy. Talking of money, the catalogue costs £1.30 (85p plus 45p post and packing) but every copy contains 14 vouchers, each worth 5p against orders, so there's 70p you soon get back. So the catalogue is quite inexpensive after all! And when you consider the time, care and effort that has gone into it to make it the superb production it is, it's almost a give-away! Talking of "give-aways" Home

Radio Components do literally give you a new updated catalogue *free* when you have been a credit account customer for one year. Full details about the many advantages of having a credit account are given in the catalogue.

Just fill in the coupon below and send it with your cheque or postal order for £1.30. You won't regret it. I can assure you of that because the Managing Director told me that as far as he knew not one of the thousands of electronic enthusiasts who had invested in their catalogue had regretted it. Their only regret was that they didn't know about it sooner!

Today's finest Components Catalogue 85p plus 45p POST & PACKING

POST THIS COUPON
with cheque or PO for **£1.30**

The price of £1.30 applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. PE
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No. 912966, London



HOME RADIO (Components) LTD., Dept. PE, 234-240 London Road, Mitcham, CR4 3HD Phone 01-658 8422

ORDER IN THE RANKS

DEPENDABILITY has become a well recognised quality where electronic equipment is concerned. Much of the reliability commonly expected or taken for granted is of course due to certain inherent characteristics of solid state devices; allied to this feature is the closely controlled manufacturing processes which ensure quality of performance to tight specifications.

The essential and important role of electronic equipment in industry and in defence has laid particular stress upon the quality of components. It was in recognition of such stringent requirements that BS9000 was drawn up by the British Standards Institution in 1967. A significant point has now been reached in the career of BS9000 with the making of this document's requirements mandatory in all military equipment sponsored by the Ministry of Defence. The national and international implications of this move are referred to in the news item in this issue.

Military equipment and industrial capital equipment may all seem very far from consumer products and the piece parts used by home constructors. Yet the widespread adoption of BS9000 by component manufacturers catering for the needs of the first two categories is bound to have repercussions throughout the entire industry. Certainly many more components emerging (fortuitously though it may be) onto the amateur market will be of unquestionable quality or standard because of their aristocratic origin. More humble applications will not deprive them of these high qualities. As the piece parts generally available for the amateur include an increasing proportion of the "top spec" devices, the performance and general excellence of home constructed equipment will be capable of further improvement.

In addition to ensuring quality control, the purpose of BS9000 backing by MoD is to introduce as much standardisation among components as is possible, in the interests of economy and efficiency. Standardisation is obviously a good thing. It is especially desirable in the electronics industry where new components are being developed at a startling rate, with identical or very similar devices often launched independently by different manufacturers. But it is probably too much to expect any serious reduction in the great abundance of type numbers in circulation. Individual manufacturers are jealous of their proprietary rights and will wish to preserve their identity for commercial purposes through their own house type numbers, though qualifying components will have a common identity via the relevant BS9000 number.

Arising from the action of the Ministry of Defence it can at least be hoped that a pattern has been marked out which will help eliminate some of the clutter of type numbers in the future. Any move in this direction can only be warmly welcomed by the component user. The "numbers game" is little fun to the uninitiated amateur. To the commercial dealer or user it must be a more serious hinderance—time consuming and a charge on efficiency.

F.E.B.

Editor
F. E. BENNETT

Editorial
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
R. W. LAWRENCE, B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF


Editorial Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: 01-634 4452

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-261 5148

P. J. MEW
Phone: 01-261 5190

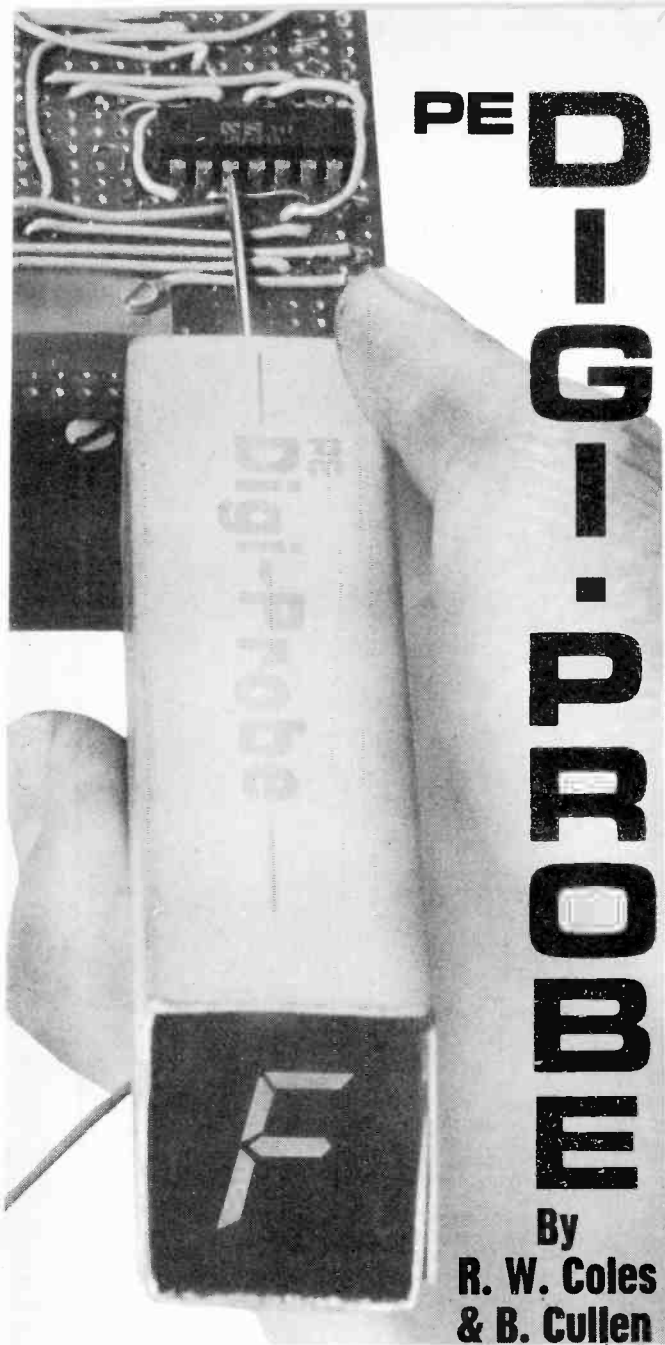C. R. BROWN *Classified*
Phone: 01-261 5000

Advertising Offices:
King's Reach Tower, Stamford St.
London SE1 9LS
Phone: 01-261 5000



PEELED DIGI-PROBE

By
**R. W. Coles
& B. Cullen**

A LOGIC probe can be a very useful instrument for finding one's way around a logic circuit, particularly when de-bugging is in progress. During the past few years the writer has had the opportunity to try out a number of different designs, ranging from the glossy (and expensive) commercial variety, to those made to serve an immediate need. This experience left him with strongly held views on just what combination of features would make the most accurate and easy to use logic probe for general use.

You can see right away that Digi-Probe is different to its predecessors because it sports a seven-segment l.e.d. as a read-out device to give a logic state indicator which it is just about impossible to mis-interpret!

The detection circuitry recognises three input conditions as defined by the TTL data sheets and displays an unambiguous 0 for input voltages between 0 and +0.8V, a 1 for input voltages between +2.4V and +5V, and an F for the disallowed conditions of an open circuit or an input voltage between +0.8V and 2.4V.

In addition to these steady state logic outputs, Digi-Probe is designed to give a positive indication when a gate output is switching at high speed. Digi-Probe does not give an ambiguous blur as all logic states are detected in quick succession, as, for example, could occur on connection to the output of a high speed counter, in fact all the display segments turn off and the decimal point is pulsed for 30ms. This pulse detection capability means that even isolated, short pulses are stretched and made visible.

POWER SUPPLY

Digi-Probe is designed to be powered by the 5V supply of the unit under test, and to ensure that the switching of the l.e.d. segments does not inadvertently introduce noise onto the V_{CC} line to which it is connected, a novel l.e.d. drive system is employed which makes the power drain substantially constant regardless of what is displayed. Incidentally, it is not absolutely essential to power the probe from the V_{CC} line of the unit under test, a separate supply can be used, providing of course that the two systems share a common earth line.

LIGHT LOAD

The input circuitry is designed so as to load the gate under test as little as possible and in fact a current of less than 500 μ A is drawn in both the logic one and the logic zero states, making operation possible even with low power t.t.l. circuits. This low current drain is gained at the expense of high frequency response however, and difficulty with triggering the decimal point may occur at very high pulse repetition frequencies. This was considered to be a better compromise than an excessive loading on the circuit under test as can occur with many other designs.

CIRCUIT OPERATION

The circuit blocks which make up Digi-Probe are shown in Fig. 1. The output of the logic "one" detector gives a logic "one" out when the input is between about 2.4V to 5V. The logic "zero" detector gives a "one" out when the input is between 0V and about +0.8V. For any other possible input voltage both detectors give a logic zero out. The output of the logic "zero" detector drives a transition detector, in fact a monostable, which will give a fixed length output pulse whenever the logic "zero" detector output goes to a logic one.

From the detector circuits, then, there are four logic outputs which have been labelled: x for the logic "zero" detector output, y for the logic "one" detector output, Q and \bar{Q} for the transition monostable outputs. These four logic signals are used as an input to the decoder block which produces the correct l.e.d. segment drive signals for each unique combination of input signals, so that an appropriate display will result.

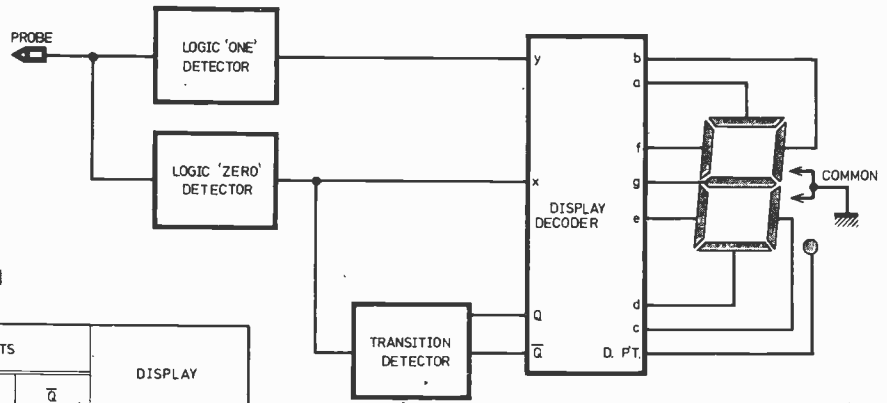


Fig. 1. Block diagram of the Digi-probe

Table 1

INPUT VOLTAGE	LOGIC OUTPUTS				DISPLAY
	x	y	Q	\bar{Q}	
+2.4 TO +5V	0	1	0	1	1
+0.8 TO +2.4V	0	0	0	1	F
0 TO +0.8V	1	0	0	1	0
1' TRANSITION 0'					NO SEGMENTS ON D.P. ON FOR 30ms

The operation of the block diagram can be best understood by reference to Table 1 which summarises the action of the circuit for various input conditions. Notice that there are redundant combinations of the three basic logic signals x, y and Q, because only four combinations can occur in practice whereas a three bit code is capable of defining up to eight unique conditions in theory. These redundancies can be used to simplify the decoding circuitry.

DETAILED CIRCUIT OPERATION

The detailed circuit description splits logically into two parts, i.e. the detector circuits and decoder circuits, but it is important to note that although the circuitry is built on two separate circuit boards, the division of the circuit hardware does not conform to the logical "split" suggested by the circuit diagrams.

DETECTOR CIRCUITS

The input to the detector circuit comes via a "needle" probe which is connected to what are, basically, two discrete component DTL logic gates. The classic circuit of a DTL gate is shown in Fig. 2, and many readers will recognise this configuration instantly as the most important predecessor of TTL.

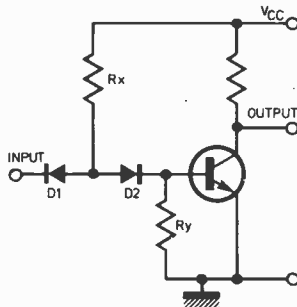


Fig. 2. A typical DTL gate arrangement

COMPONENTS

Resistors

R1, R2	4.7k Ω
R3, R4	12k Ω
R5	4.7k Ω
R6, R7	2.2k Ω
R8	4.7k Ω
R9, R10	330 Ω
R11	100 Ω
R12, R13, R14	47 Ω
R15	150 Ω
R16, R17	47 Ω
R18	330 Ω
R19	3.9k Ω

All resistors $\frac{1}{8}$ W 5% carbon

Capacitors

C1	30 μ F 10V elect.
C2	22 μ F 15V elect.

Transistors

TR1	BC107 or similar silicon npn
TR2	BC212 or similar silicon pnp
TR3	BC107 or similar silicon npn

Diodes

D1, D2, D3, D4, D5	1N914 or similar silicon type
D6	BZY88 or similar 3.0V type

Integrated circuits

IC1	SN74121
IC2, IC3	SN7405

Miscellaneous

Display DL704 or similar common cathode i.e.d. display
0.1in matrix Veroboard, needle for probe, aluminium sheet, crocodile clips

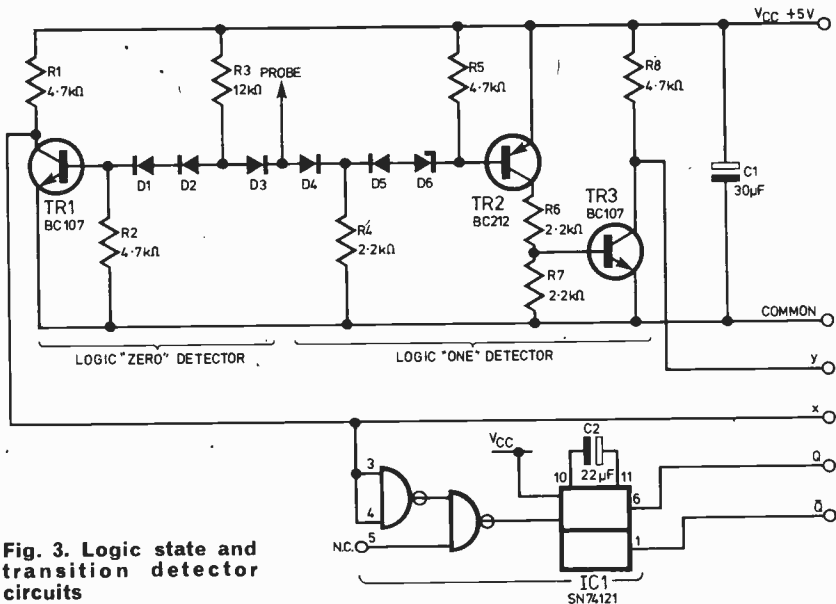


Fig. 3. Logic state and transition detector circuits

In the classic circuit the transistor is held in the saturated condition (logic 0 out) in the absence of an input, by the current flow into the base via R_x and the forward biased D_2 . To make the gate output go to a logic 1 condition it is necessary to take the input to 0 volts so that the transistor base current is diverted through D_1 and the transistor is turned off. The basic circuit can be realised just as easily with a *pnp* transistor, providing the supply polarity and the diodes are reversed, and if required the switching thresholds of the gate can be varied by increasing the number of diodes in the D_2 position.

As can be seen from Fig. 3 the input gates of Digi-Probe are based on the classic circuit, although the threshold levels have been varied by adding diodes, in one case a Zener. One of the gates is an *nnp* type while the other is a *pnp* version followed by a straightforward *nnp* inverter.

INPUT CONDITIONS

The easiest input condition to follow is that of an open circuit, a moments examination will show that both TR_1 (*nnp*) and TR_2 (*pnp*) will be "on" giving a logic 0 out at the collector of TR_1 , and a logic 0 at the collector of TR_3 . These conditions will be used by the decoder to form an "F" on the display. If the probe is connected to 0 volts the base current of TR_1 will be directed through D_3 and the collector of TR_1 will rise to a logic 1, but the output of TR_2 and 3 will stay the same as before. The third test case is with the probe connected to +5V and here it is TR_2 which turns off by virtue of the fact that it is starved of base current by the conduction of D_4 .

THRESHOLD LEVELS

The three test cases covered so far are extremes, but it is necessary for a practical probe to behave according to Table 1 where logic levels are each

defined by a range of voltages. It was mentioned earlier that these threshold levels are set by the diodes, in this case D_1 , D_2 , D_5 and zero diode D_6 . Although the diodes shown gave a very close correspondence with the table in the prototype, a certain amount of cut-and-try may be necessary to reproduce these results exactly if this is considered desirable.

For obvious reasons the possibility of adjusting the thresholds with a potentiometer was ruled out. If it is found necessary to trim the threshold voltages slightly this can be achieved by trying different types of silicon diodes, or in the case of the logic "1" detector, by changing the Zener breakdown voltage slightly, say to 2.7V or 3.3V.


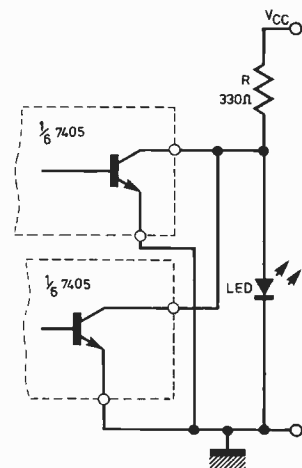


Fig. 4. WIRED-OR arrangement used for l.e.d. control

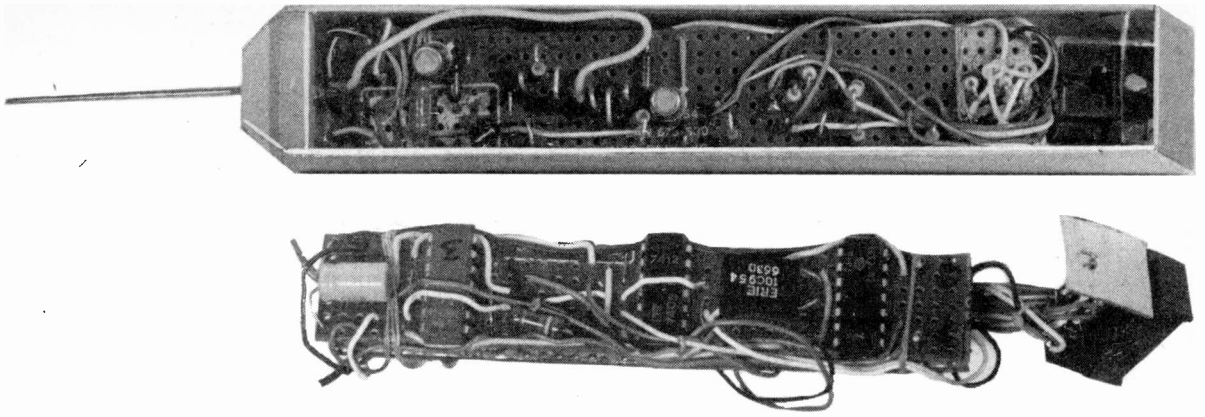

MONOSTABLE

A 74121 monostable is used as the transition detector, and in fact it is connected to the collector of TR1 so that it is triggered by a negative going transition at the probe tip. The monostable is acting as a pulse stretcher because a 1 to 0 transition will cause a 30ms pulse to be produced at the Q outputs. The pulse length is determined by the value of C2 and the internal $2k\Omega$ resistor available in the 74121, the relationship being $R \times C \times \ln 2$, i.e. $0.69 RC$.

DECODER

The operation of the decoder/driver is very simple but perhaps a little unusual at first sight. The first thing to note (Fig. 5) is that no gates, as such, are used, the logic being performed by the "WIRED-OR" logic operation using open-collector inverters. The next point of interest is the fact that the l.e.d.s are operated in the normally-on mode, where the output of a gate function is used to turn the l.e.d. segment off by diverting its current supply to ground, rather than turning it on by providing a current path to

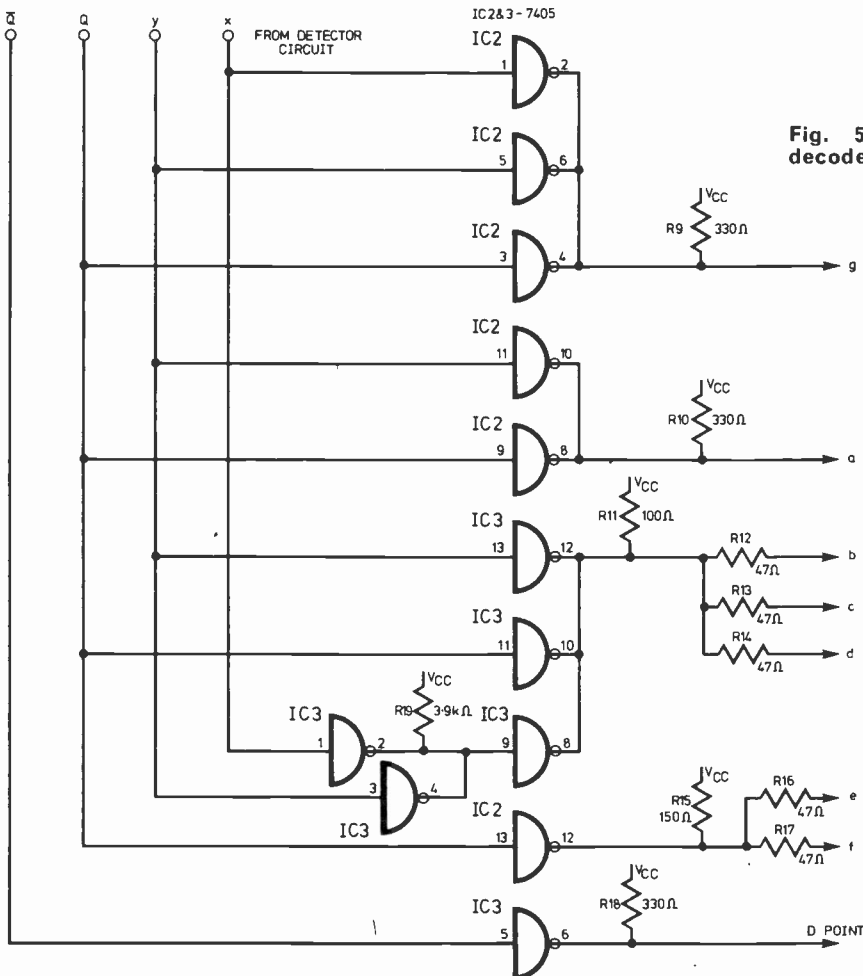


Fig. 5. Display and decoder circuitry

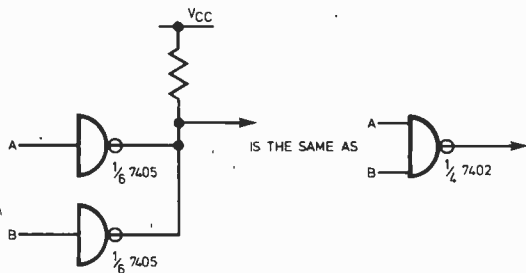


Fig. 6. Two 7405 open collector invertors used to simulate a 7402 two-input NOR gate

ground. Driving an l.e.d. in this way ensures that large current fluctuations do not occur when the segments switch on or off, the price, if you can call it that, is that current drain remains continuously high. The advantages of this approach were mentioned earlier.

WIRED-OR

The operation of the "WIRED-OR" logic is best understood with reference to Fig. 6 where two 7405 inverters are shown to be logically identical to a 7402 two-input NOR gate. Although the logic is the same, the 7405 approach has a couple of advantages for this particular application:

1. Flexibility—the logic required consists of two three-input NOR gates, two two-input NOR gates and two inverters. The 7405 inverters can be connected to form any combination required.

2. Open collector outputs—

A standard TTL totem pole output is not suitable for driving l.e.d. segments in the way necessary for Digi-Probe.

LED DRIVERS

The detailed l.e.d. driving circuit is shown in Fig. 4. R is a current limiting resistor required to set the operating point of the l.e.d. to about 10mA, and it can be seen that with both 7405 outputs in the logic 1, or non-conducting condition, the l.e.d. will be lit. If either of the 7405 outputs goes to the

logic 0, or conducting, state the l.e.d. will be starved of current and will turn off.

CURRENT SHARING

Several of the l.e.d. segments are driven in parallel, and in these cases it is not sufficient to simply reduce the value of R and hope that the current will divide equally between the segments because there are often small differences between the forward voltages of otherwise similar diodes. Small variations of V_f will cause large variations in the current, and hence brightness, and are overcome in Digi-Probe by the individual 47Ω segment resistors which can be seen in Fig. 5. This arrangement works very well in practice.

CONSTRUCTION

The electronic components are arranged on two small pieces of 0.1in matrix Veroboard which lay one above the other in the case separated by a piece of acrylic sheet as an insulating spacer. No particular problems should be encountered with wiring up the circuit boards but when it comes to inter-board and l.e.d. connections, fine flexible wire should be used to prevent fatigue fractures at the soldered joints. In the prototype the l.e.d. was mounted in a 14 pin d.i.l. socket and this is certainly recommended although not of course essential.

CASE

The case was cut and bent from 22 s.w.g. aluminium sheet resulting in a neat and lightweight probe which is very handy to use. A couple of coats of aerosol cellulose paint were applied to the finished probe, and this adhered very well to the aluminium to give a smart and durable appearance.

The nose of the probe was shaped from a piece of plastic scrap and cemented in place with contact adhesive. The probe itself was made from a large sewing needle—the type without a sharp point called a bodkin. It proved a simple matter to solder to the end of this probe. The l.e.d. socket is cemented, with Araldite, to a small aluminium plate which is then bolted to the case. ★

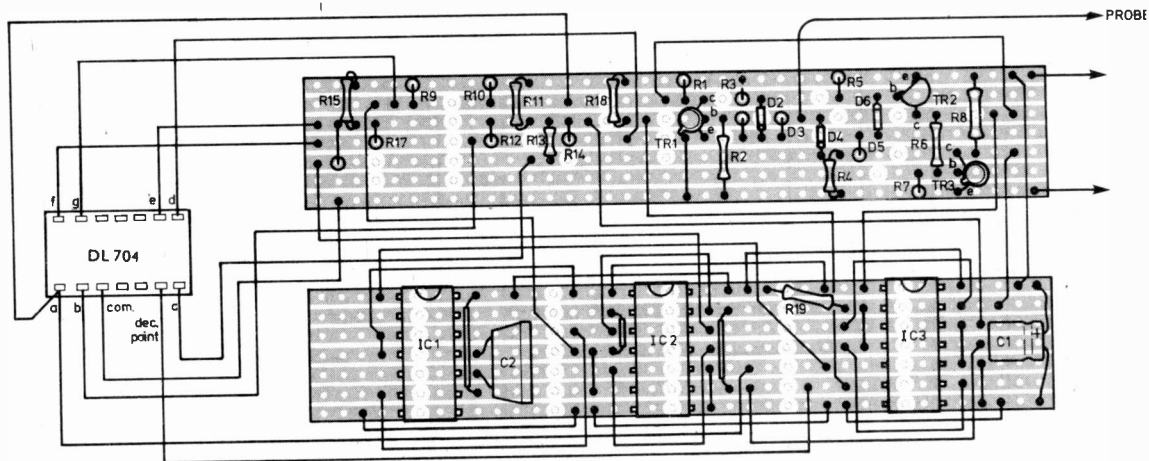


Fig. 7. Veroboard details and interwiring between the two boards of the Digi-probe

ENVELOPE SHAPER


By P. R. WILLIAMS

THE unit described here has been designed to fulfil the need for a more accurate synthesis of the amplitude envelope of musical instruments, particularly stringed, when used in conjunction with a music synthesiser and a keyboard.

The circuit achieves this in a very simple manner and the use of linear integrated circuits makes construction easy and keeps the cost low. In fact, this unit costs little more to build than a standard envelope shaper.

PRINCIPLE OF OPERATION

Most envelope shapers have two variables: attack time and decay time, as shown in Fig. 1a. Fig. 1b, however, shows that stringed instruments in particular have a much more complex amplitude envelope. Fig. 1c shows that a more accurate synthesis is obtained by splitting the decay slope of Fig. 1a into two parts and introducing a sustain level, the duration of which is governed by the point at which the effective key is released. Four variables are thus required: Attack time, Decay time, Sustain level and Release time (release time being the second half of the decay slope). Hence the abbreviation A.D.S.R.

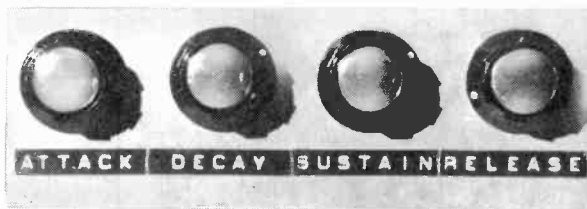

THE CIRCUIT

The complete circuit diagram of the envelope shaper is shown in Fig. 2. When the keyboard contacts are closed by the depression of a key, the positive-going voltage is differentiated by C1 and applied to the base of TR2 which along with TR1 forms a bistable.

TR1 is turned off and its positive-going collector voltage causes C2 to charge via D6, R13 and VR2 (ATTACK) until the voltage set at the potential divider, R16/R17 is reached—in this case, about five volts.

At this point, the output of the comparator, IC1 will go very rapidly positive, causing the bistable to reset via C3, when TR1 again conducts.

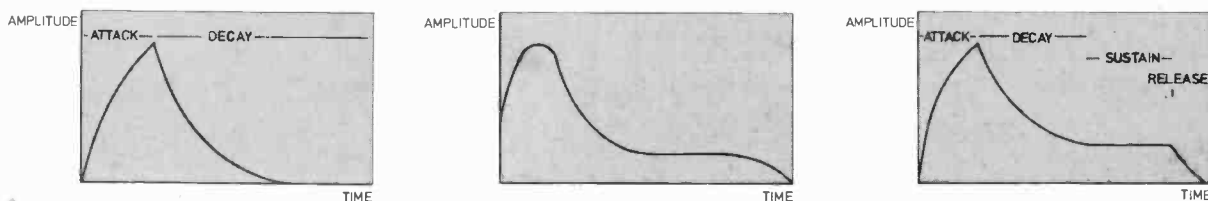


Fig. 1. Amplitude envelopes of (a) a standard envelope shaper, (b) a typical stringed instrument and (c) an A.D.S.R. envelope shaper

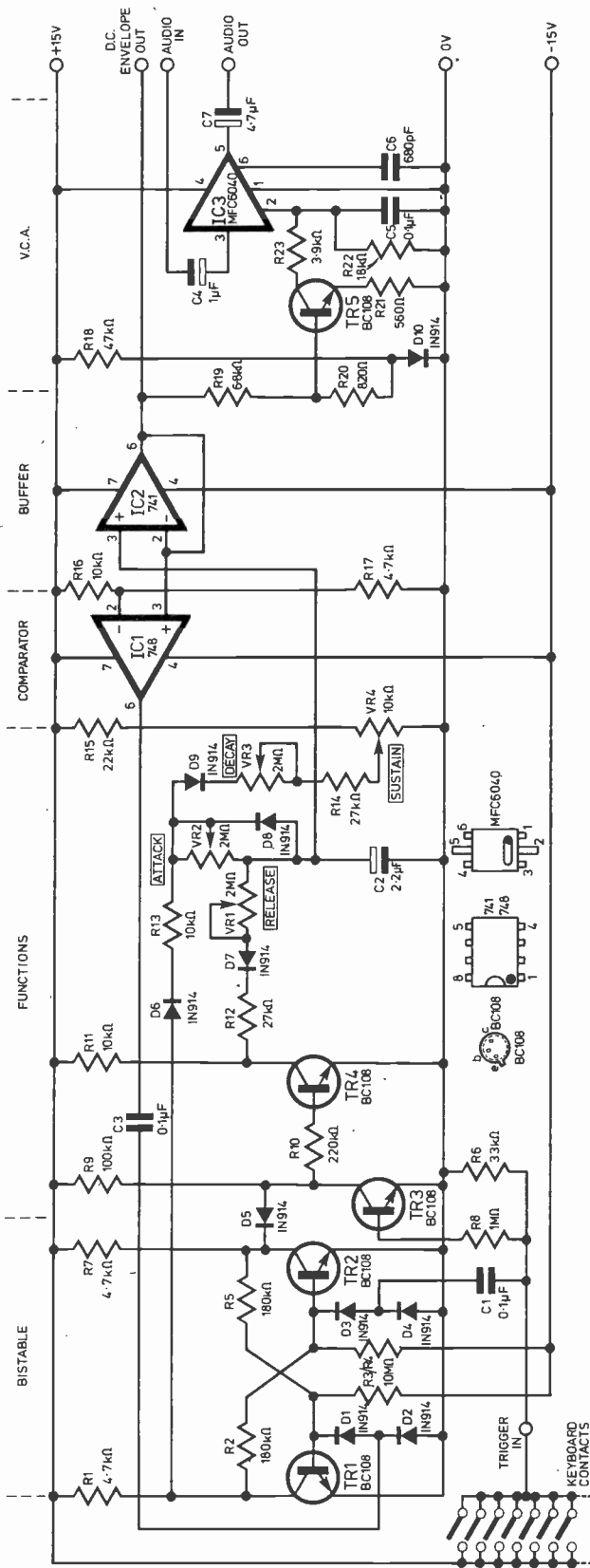


Fig. 2. Complete circuit diagram of the Envelope Shaper

COMPONENTS

Resistors

- R1 4.7k Ω
 - R2 180k Ω
 - R3 10M Ω
 - R4 10M Ω
 - R5 180k Ω
 - R6 33k Ω
 - R7 4.7k Ω
 - R8 1M Ω
 - R9 100k Ω
 - R10 220k Ω
 - R11 10k Ω
 - R12 27k Ω
 - R13 10k Ω
 - R14 27k Ω
 - R15 22k Ω
 - R16 10k Ω
 - R17 4.7k Ω
 - R18 47k Ω
 - R19 6.8k Ω
 - R20 820 Ω
 - R21 560 Ω
 - R22 18k Ω
 - R23 3.9k Ω
- All $\pm 5\%$ $\frac{1}{4}$ W carbon

Potentiometers

- VR1-VR3 2M Ω linear (3 off)
- VR4 10k Ω logarithmic

Capacitors

- C1 0.1 μ F polyester
- C2 2.2 μ F 16V elect.
- C3 0.1 μ F polyester
- C4 1 μ F 16V elect.
- C5 0.1 μ F polyester
- C6 680pF polystyrene
- C7 4.7 μ F 16V elect.

Semiconductors

- TR1-TR5 BC108 (5 off)
- D1-D10 1N914 (10 off)
- IC1 Type 748
- IC2 Type 741
- IC3 MFC6040

Miscellaneous

- 0.1in matrix Veroboard 102 \times 64mm (4in \times 2 $\frac{1}{2}$ in)

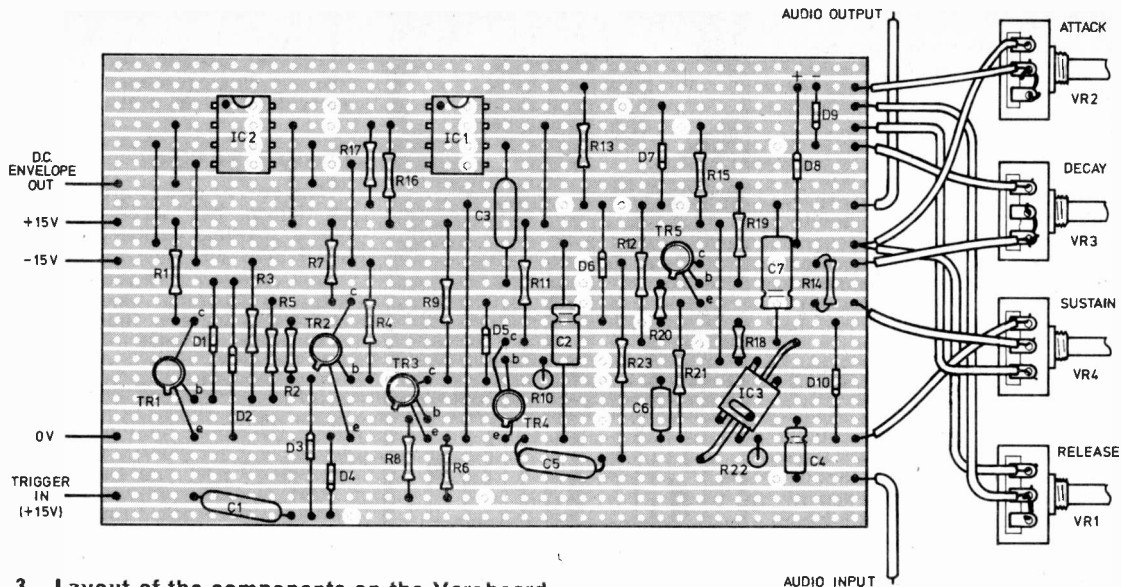


Fig. 3. Layout of the components on the Veroboard panel showing the cuts in the copper strips

Since there is no potential to charge C2, it discharges to the potential set at the wiper of VR4 (SUSTAIN). While this sequence is in progress, TR3 is biased on by the positive voltage from the keyboard contacts via R8 and will remain so until the key is released, when TR3 switches off, switching TR4 on. C2 is then discharged completely via D7 and VR1 (RELEASE), completing the A.D.S.R. sequence.

Diode D8 ensures that the full attack period is completed even if the key is released during attack. It does this by holding TR4 off while the bistable is "set", i.e. during attack.

The voltage on the positive plate of C2 is followed and buffered by IC2 to give 0 to 5 volts positive at the d.c. envelope output. This voltage is fed to TR5 which drives the voltage-controlled attenuator, IC3.

Because of the possible gain spread of TR5, the value of R19 and/or R18 may need adjusting so that the voltage at pin 2 of IC3 varies between 3.5 volts and 5.6 volts as measured with a high impedance voltmeter. This will give an attenuation range of 65dB, which was found to be adequate in the prototype. This range could be increased to about 80dB by increasing the value of R22 to 33kΩ but propagation delay might then be experienced due to the time taken to charge C2 to a voltage where the note has reached an amplitude that is audible.

CONSTRUCTION

The prototype was constructed on a small piece of 0.1in Veroboard prepared as shown in Fig. 3. Miniature resistors were used to make the unit neat and compact, but if standard resistors are used, R2 and R6 should be mounted vertically. Diode and capacitor orientation should be checked with Fig. 3.

The leads of TR1, 2 and 4 span a distance of half an inch or so and it should be checked that they do not short to the cases of the transistors. IC1 and 2 were soldered directly into the board since i.c. sockets were considered an unnecessary expense

using today's robust integrated circuits and a little care. The two longest pins of IC3 should be bent halfway along their length 10 degrees to the left, as viewed from their respective ends. This will ease insertion into the board. Thin insulated wire should be used for the nine inter-track links.

The four potentiometers are connected to the board by five wires which could be quite long allowing the circuit board to be located remote from the control panel if necessary. R14, D8 and D9 are mounted on these potentiometers.

USING THE CIRCUIT

The trigger input should be connected to one of the keyboard busbars so that when any key is depressed, 15 volts will be applied.

The audio input need not be screened unless spikes are found to be induced, when it can be screened to the 0V line. The input voltage should not exceed 500mV r.m.s. if distortion is to be avoided. The maximum gain of the electronic attenuator is 13dB; hence the output voltage could reach 2.2V r.m.s.

The d.c. envelope output could be used to control a voltage-controlled filter or even another voltage-controlled attenuator to provide a separate channel for stereo effects.

It will be found by experimentation the settings of the controls required to give an accurate synthesis of a particular instrument, but as a guide, strings, for example, have a very rapid attack followed by a fairly long decay and a low sustain level. The release time varies from instrument to instrument. For example, it will be short for a piano but long for a guitar.

Special effects can also be generated. An example of this is given by adjusting all controls to minimum. The resultant sound will be a short "pop" of the note every time a key is depressed. If the DECAY control is advanced slightly, the "pop" will become a "blip".



HELIOS 2

The second German spacecraft *Helios 2* for solar studies was successfully launched on January 15. This was nearly one month later than originally proposed due to problems at the launch site.

There was a limit to the time of the launch since the deep space network which is needed to monitor this mission will be fully occupied with the *Viking* mission to Mars later on. The final date would have been February 7. All is now well and the required coverage can be made.

Both structurally and operationally *Helios 2* is similar to *Helios 1*, carrying similar experiments. *Helios 1* was launched at the time of minimum solar activity. But since *Helios 2* was launched at the beginning of the high solar activity period it should have added advantages. It will therefore be of great value for collecting data as the Sun reaches its peak of high activity. Thus it will be possible to have a continuous record of the Solar events, which added to the *Skylab* data will bring a new viewpoint to the studies.

The flight trajectory will bring the spacecraft rather nearer to the Sun than for *Helios 1*. It will, in fact, have a perihelion point with reference to the Sun of about 30 million miles. In spite of the closer approach it was not necessary to make more stringent thermal protection than for *Helios 1*, whose performance was well within requirements.

The mission is expected to last 18 months and will form an agreed part of the American-German co-operation for the examination of space within Mercury's orbit. Though the mission for *Helios 1* was for the period of 18 months, it still continues to be operational. *Helios 2* will no doubt follow the same pattern, continuously adding to the value of the mission.

Spacecraft *Helios 2* was also built by the consortium of Messerschmitt-Bölkow-Blohm for the Federal Ministry of Research and Technology.

THE MOON

In the dust collected by *Apollo 16* there were 400 metallic objects in a cluster. These have been found to contain 92.5 per cent iron, 6.25 per cent nickel, which agrees with the general composition of iron meteorites.

THE SUN

A new dimension has been added to the Sun. It now seems that it pulsates at a regular rate of some 2 hours 40 minutes. This is an exciting confirmation of suggestions made by Dr Henry Hill of Santa



BY FRANK W. HYDE

Catalina Laboratory for Experimental Relativity by Astrometry, Arizona.

Resulting from more than 10 years' work, his suggestions for a "shivering period" of about 50 minutes, thought to be of seismic origin, led two independent teams of observers to investigate this phenomena. The two teams, one Russian with A. B. Severyn, V. A. Kotov and T. T. Tsap of the Crimean Astrophysical Observatory and the other consisting of J. R. Brookes, G. R. Isaak and H. B. van der Raav at the University of Birmingham.

The two teams were working on entirely independent experiments. The Russian team were using a solar magnetograph. This instrument is employed to record the magnetic field of the Sun by the Zeeman effect (splitting of the spectral lines) but modified in this particular experiment to measure the velocities in line of sight by doppler shift.

It was found that the Sun was pulsing in a regular period of 2 hours and 40 minutes. It was calculated that the amplitude of these oscillations was about 10 kilometres. This was based on more than a 100 hours of observation time during 1974 and early 1975.

The Birmingham team had set up an experiment to compare the Fraunhofer lines of absorption for sodium and potassium in the Sun with those generated in the laboratory to detect any possible doppler shift. Their apparatus was set up on the Pic du Midi mountain top in the Pyrenees.

The primary object of the Birmingham experiment was to determine gravitational shift in the red region of the spectrum. In making their assessment and given that

the effects of solar rotation and the differences of motion between the Earth and the Sun were accounted for, the final residual was within one second of the Russian result.

TARGET SATURN

The second spacecraft on its way to Saturn has successfully completed the mid course adjustments and is now on target for the ringed planet. *Pioneer 11*, the second of the successful reconnaissance vehicles to make a Jupiter fly-past, is expected to make its rendezvous with Saturn in 1979.

The correction on this occasion also added some 67mph to the speed. This was for the purpose of giving two optional trajectories at the time of near approach.

One of these options was to fly between the inner ring and the planet itself. The other is that it might be decided to approach on an upward path to pass outside the ring system. The choice no doubt will depend on what is decided for *Pioneer 10* which precedes it.

There is a fixed aerial on *Pioneer 11* and when orienting the course correction thrusters the aerial had to be disengaged from the Earth "lock". This necessitated a programme sequence which took it out of lock, made the reorientation and then once more come into lock with the Earth. At this point the vehicle was 287 million miles from Earth and out of communication for several hours.

This is the first time such a manoeuvre has been carried out where everything depended on the pre-planned programme aboard the craft itself. There will be a number of new corrections to be made before the planet is reached. If problems develop or if the narrow beam aerial is more than 25 degrees out of line then failure could result.

If the vehicle continues to function the first close-up pictures will be available in about three years' time. At the moment tests indicate that the cameras are working normally.

CHINA

It would seem that China is considering a manned flight in space. So far China has launched five unmanned spacecraft and have given little data to the media.

Some remarks in a newspaper relating to the return of spacecraft to Earth indicates that the manned possibility is being actively considered. It has been claimed that the fourth satellite launched was safely recovered.

Such data that has been released relating to orbit parameters suggests that the recovered capsule was a prototype suitable for manned operation.


This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

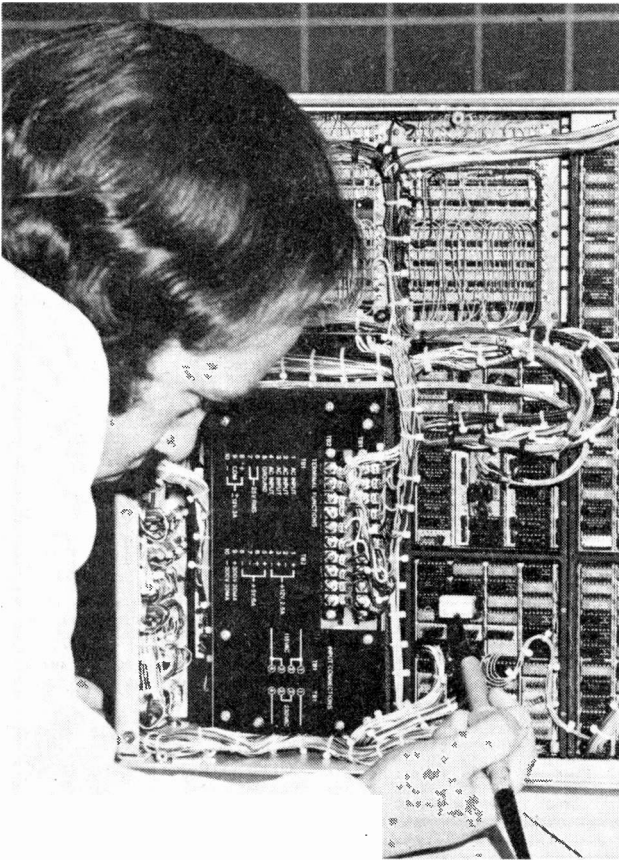
All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.




1

Build an oscilloscope.

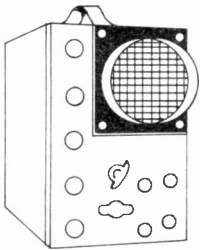As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.




2

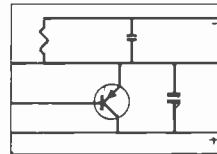

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

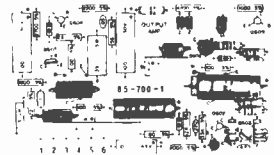


Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

PLUS FREE GIFT!

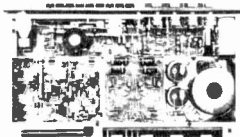ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE



Brochure without obligation to:
**BRITISH NATIONAL RADIO
 & ELECTRONICS SCHOOL, Dept. EL46**
P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

(Block caps please)



'HOW INVENTIVE ARE YOU' COMPETITION

HOW INVENTIVE WERE YOU?

INITIAL REPORT FROM THE JUDGES...

It may seem quite a while since last September/October when Practical Electronics and Plessey issued the challenge *HOW INVENTIVE ARE YOU?* but during that time quite a lot of discussion, investigation and head scratching has taken place. Our deliberations are now nearing completion and we thought at this juncture it would be of interest to readers to know what goes on behind the scenes in a competition of this type. Well, this is what we've been up to.

There was a very gratifying response, and the majority of entries were of a very high standard. Many entrants had gone to considerable lengths to describe their ideas, to draw up the circuit, mechanical design and styling of the product and in some instances had obviously made working prototypes to confirm their feasibility.

The panel of judges comprised of the under-mentioned:

Mr. F. Bennett	—Editor of Practical Electronics.
Mr. G. Godbold	—Technical Editor of Practical Electronics.
Mr. S. E. Gent	—Technical Executive of Plessey Windings.
Mr. E. A. Quincey	—New Products Manager of Plessey Windings.

considered five main criteria.

- Originality —was the idea novel to the judges.
- Technical merit —was the design and circuitry based on sound engineering principles.
- Practicability —would the device work in the form envisaged and be easy to use.
- Economic viability —would the benefits which arose from the device warrant its cost.
- Market potential —what would the gross market be for the product.

Initially the ideas were all grouped under headings dependent on the suggested application. The groups included:

- Flashing Lights (both neon novelties and emergency beacons)
- Welding Products (arc initiators)
- Insulation Testers (both for automotive applications and safety testers)
- Fencers and Cattle Goads
- Insect Killers

Gas Sensors

Physics Laboratory Products

Automobile Ignition Aids

Plus Miscellaneous Ideas which, as one might expect, included many of the most novel suggestions.

From each of these groups we selected the best ideas for further evaluation.

Novelty was confirmed by conducting searches at the Patents Office in London. This is where all U.K. patents are on file. Practicability was a little more difficult. Although there was a wide spread of experience amongst the panel for some ideas it was necessary to seek an expert specialist opinion of their merit. Some of the questions stretched our credibility. "Can you electrocute dandelions?"—we asked various authorities in matters botanical.

Others like "What electrical energy is required to stimulate the muscles of the body" required very careful consideration.

Assessing technical merit was not too great a problem as most of the devices were based on standard circuitry, however, a number of ideas incorporated elegant design solutions.

In a few cases circuits were proved or disproved by building prototype models and in one instance it was necessary for a judge to travel to a farm in Oxfordshire to confirm that the energy generated by a Cattle Goad was in fact sufficient to goad cattle.


To establish economic viability it was necessary to estimate the costs of products. As in the main 80 per cent of the circuitry was common to the portable ignitor again this procedure did not present many problems.

Gross market was taken as a measure of market potential. For example, a fly killer could be used in any home. In the U.K. there are some 18 million homes and thus the market potential for a product of this type would be very good. However, the requirement for a vacuum leak tester would be limited to laboratories and alike.

So from the total of ideas submitted to a short list of some fifty. From this list we have now selected those ideas which are Winners in the "How Inventive Are You" competition.

We hope to publish the full results in our May issue and in subsequent issues we will be describing some of the ideas and circuits that were entered. We also hope to keep you up to date with the progress of any of these ideas towards manufacture and launch on the market as commercial products.

Using CMOS digital I.C.s

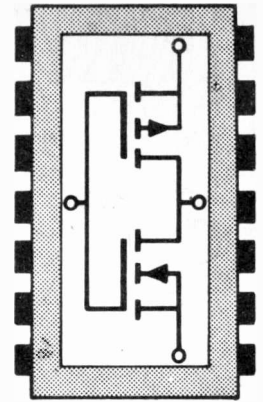

By D.B. JOHNSON-DAVIES & A.M. MARSHALL B.A.

PART 4

THIS month we will give linear applications of CMOS. Two bonus circuits included are a tachometer and an oscilloscope trace doubler.

LINEAR USE OF CMOS

Although most applications of CMOS are digital, it comes as a real bonus that many linear circuits can be constructed from CMOS devices, taking advantage of their extremely high input impedance, low power consumption and low cost. The next sections show how simple high-impedance linear amplifiers, and wide-range oscillators and monostables, can be constructed with very few external components. Any type of gate may be used in most of these circuits; however most B-series devices are unsuitable due to the two additional inverters at the output. Very often the gate used will be one left from the rest of the circuit.

The switching characteristics of the inverter has a substantially linear section where both the *p*- and *n*-channel devices are on simultaneously. The inverter can be deliberately biased into this region, when it will act as a small signal high-gain amplifier. The slope of the curve at the bias point gives the a.c. gain, typically 20dB or 100 times. Ideally the bias point should be at $V_{OUT} = V_{DD}/2$, but as the transfer characteristic is only guaranteed to lie within the limits shown in Fig. 4.1 for any particular device, the biasing circuit shown in Fig. 4.2 is usually used. This constrains the bias point to the line $V_{IN} = V_{OUT}$ and will give good results without needing tailoring to the particular device used.

The bias point can be trimmed to any particular value if required by the addition of a variable resistor from the input of the inverter to one or the other supply rail. The value of the feedback resistor will give the input impedance, and so it should be as large as is practical. High current buffer inverters such as the 4049 should not be used in such applications as they can dissipate excessive power if held in the linear region of their characteristic.

to the correct point on the characteristic. However, CMOS inverters are most usually used as a.c. amplifiers, as in Fig. 4.2. A good low frequency response can be obtained even with small values of coupling capacitor due to the 10 Megohm input impedance; with the values given the low-frequency cut-off is below 1Hz. To obtain more gain it is possible to cascade a number of inverters. As the transfer voltage of each inverter is only guaranteed within fairly wide limits, it is not usually possible to cascade inverters directly as one stage could be biased completely off by the preceding one. These difficulties are avoided by a.c. coupling the stages as in

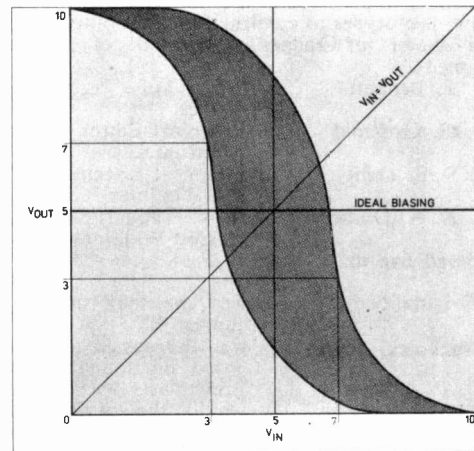


Fig. 4.1. Transfer curves of CMOS devices are guaranteed by the manufacturers to lie within the shaded region, for a 10V supply. Thus V_T , the transfer voltage, can lie between 30 and 70 per cent of the supply voltage

PRACTICAL AMPLIFIERS

The CMOS inverter may be used as a high impedance d.c. amplifier without any bias resistor provided that the mean d.c. level at the input biases it

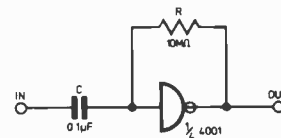


Fig. 4.2. Simple a.c. amplifier using a CMOS gate biased into the linear region. The value of R is not critical, and determines the input impedance

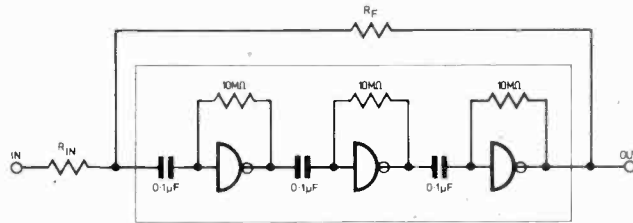


Fig. 4.3. Three-stage a.c. amplifier with gain stabilisation by negative feedback. The gain is approximately R_F/R_{IN}

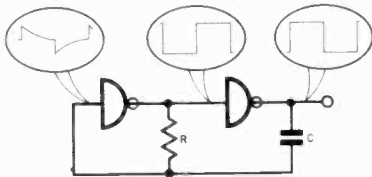


Fig. 4.4. Simple oscillator. The frequency is dependent on the supply voltage and the transfer voltages of the gates and is about $1/1.7RC$



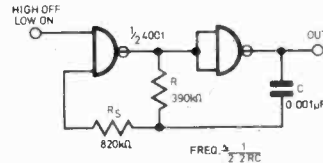



Fig. 4.5. Compensated oscillator circuit which is less sensitive to variations in supply voltage or temperature. It can be gated by the spare input of the first gate. The values shown give a frequency of 1kHz

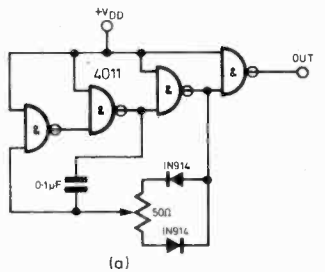

(a)

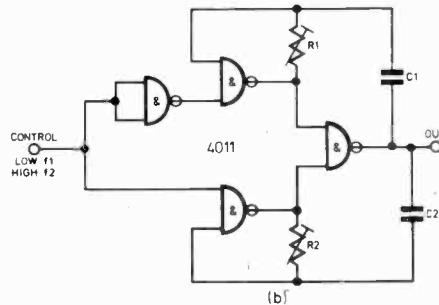


(b)

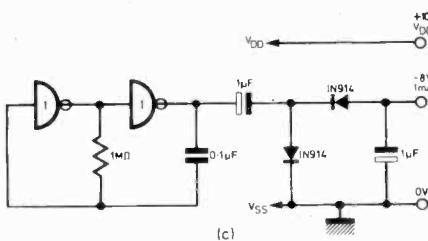

(c)

Fig. 4.6. Special purpose oscillator circuits. (a) Variable pulse-width oscillator, with mark/space ratio variable from 3 to 97 per cent. (b) Inter-gated oscillator. The two oscillators share the same output gate, giving a choice of two frequencies by the logic level at the control input. (c) Negative voltage supply. A standard CMOS oscillator feeds into a voltage doubler network to provide an additional supply of about $-8V$ at up to 1mA

Fig. 4.7. Tachometer front-end using one 4001 package. The first gate amplifies the input pulses to trigger the Schmitt trigger formed by the other three gates

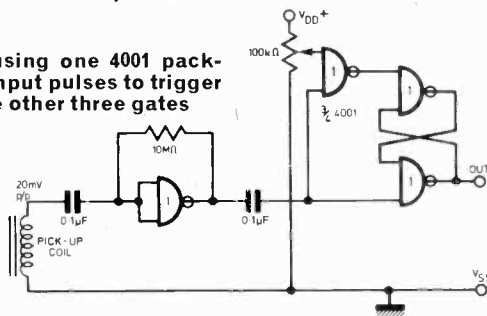

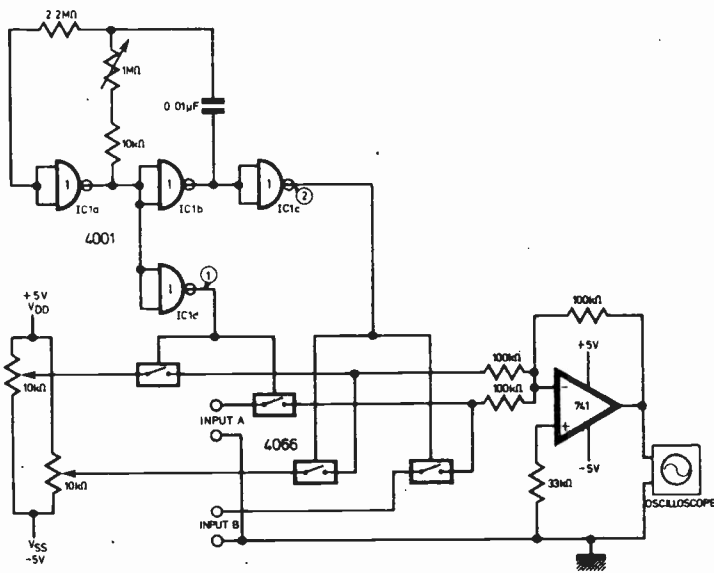


Fig. 4.3. The three cascaded amplifiers can be regarded as a single high-gain block, with the overall gain defined as R_F/R_{IN} . Noise becomes a problem as more stages are cascaded, and three will usually be the practical limit.

OSCILLATORS

With two gates from one CMOS package and just two external components, it is possible to construct the strikingly simple oscillator of Fig. 4.4. The circuit will oscillate from below 1Hz to about 10MHz, with values of R from 15MΩ down to 10kΩ, and values of C from 1μF down to a few pF.

The capacitor is charged in opposite directions on each half of the cycle, and so should not be an electrolytic type. The frequency of this circuit depends somewhat on the supply voltage, being in the range $1.4RC$ to $2RC$ for supplies of 3 to 15 volts, but can be made virtually independent of the voltage by the addition of R_S as in Fig. 4.5 This circuit suffers at worst a 5 per cent shift in frequency for a 10 volt change. The ratio of R_S to R should be at least 2, and preferably 10 for maximum stability.

In Fig. 4.5 a 2-input gate is used instead of the first inverter, the second input gating the oscillator. This circuit can be used as a pulse modulator, the signal to be modulated being fed to this input.

APPLICATIONS

Three circuits incorporating the basic CMOS oscillator are shown in Fig. 4.6. Circuit (a) has a fixed frequency, but the mark/space ratio can be varied from 3 to 97 per cent. The simple oscillator of Fig. 4.4 has a mark/space ratio of about 50 per cent depending on the thresholds of the two inverters. By connecting diodes in parallel with a portion of the timing resistor R it is possible to vary the charging and discharging currents of the capacitor independently, and so control the mark/space ratio. Circuit (b) shows how two oscillators can be combined to share the same output gate, so that one of the two frequencies can be selected by the

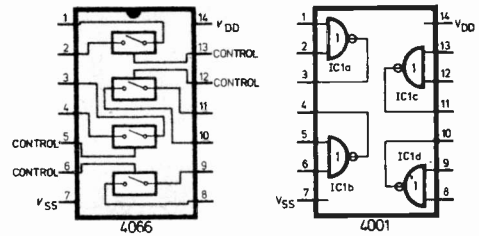


Fig. 4.8. Oscilloscope trace doubler using only two CMOS packages; the 4066 (or 4016) quad bilateral switch and the 4001 quad NOR gate. The potentiometers vary the positions of each trace on the screen. The circuit will display two signals of the same frequency simultaneously on any oscilloscope with an external trigger facility.

logic level at the control input. The circuit in (c) will provide a negative supply of about 8 volts at up to 1mA when only a positive one is available. Negative-going pulses from the oscillator charge up the output capacitor through the conventional voltage doubler network formed by the capacitors and the two diodes. For higher output currents a buffer may be added at the output of the oscillator.

The front-end of a simple tachometer circuit using only one CMOS package is shown in Fig. 4.7. Pulses of about 20mV p/p induced in the pick-up coil by the rotating magnet are amplified by a one stage gain-block (Fig. 4.2) and then squared up by the variable trigger level Schmitt. The squared output pulses would then feed into the measuring stages which depend on the application.

TRACE DOUBLER

The trace doubler circuit (Fig. 4.8) switches rapidly between the two input signals, presenting each to the oscilloscope input for half the time together with a d.c. offset to separate the two traces on the screen. The oscillator provides out of phase pulses at X and Y, these being used to switch between the two pairs of bilateral switches. One switch of each pair admits the input signal which should have an amplitude of less than 10V p/p, and the other sets the d.c. level varied by the potentiometers. These are both fed to a unity-gain summing amplifier made from a 741 op-amp. The frequency of the oscillator should be adjustable as the unit will not display a correct trace if it is an exact multiple of the frequency of the input signals. The oscilloscope is triggered from one of the input signals. Supply connections to the CMOS packages are, as usual, not shown and are at 5V above and below earth. The 4066 quad bilateral switch will transmit signals from d.c. to 40MHz, but the upper frequency response of the circuit is limited to 1MHz by the 741.

Next month: Basic oscillators and practical examples.

DORAM


A PROFESSIONAL DEAL FOR AMATEURS

*ORDERS BY RETURN OF POST *NO QUIBBLE REPLACEMENT PART SERVICE
*QUALITY 'BRANDED' PRODUCTS *FREE UP-DATE INFORMATION SERVICE


TOOLS

The handy EXPO 12V d.c. drill is supplied complete with drill kit containing 4 small drills, two spare collets, two cutters, wire brush, soft buffer, grindstone and 9 various milling and reaming tools.

Drill & kit £9.50 + s
Kit only £4.75 + s

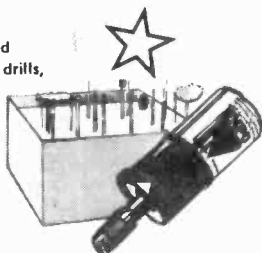

ORYX 50W SOLDERING IRON

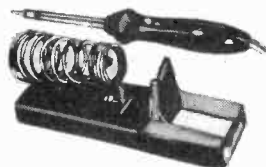

Temperature can be altered between 200-400°C.

Iron 240V £6.90 + s
Stand £2.80 + s

ISO-TIP CORDLESS IRON

Mains and 12V d.c. versions available
£11.50 + s



DE-SOLDER TOOLS

Three high-suction models available

SR2 £6.20 + s
SR3 £5.20 + s
SR3AS £4.80 + s
Spare nozzle 60p ea. + s
Please state type



NICKEL - CADMIUM RECHARGEABLE CELLS

	Sim. to dry cell	nom. capacity	charge cur. (mA)	
HP7	0.5Ah	50	£1.10 s	
—	1.2Ah	100	£1.24 s	
HP11	2.0Ah	200	£1.80 s	
HP2	4.0Ah	400	£2.70 s	

ELECTRONIC IGNITION UNIT

- * High performance
- * For 2 & 4 stroke engines
- * Improved start/running
- * 'Crisper' throttle response
- * Reduce battery drain

Neg. earth or pos. earth


£15.00 + s

Please state type required



BATTERY ELIMINATOR

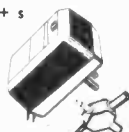Switched output 6, 7.5 or 9V at 250mA. D.C. pos. or neg. earth
£3.15 + s



SEMI-CONDUCTOR DEVICES

RECTIFIERS


IN 4001 - 8p ea.)
IN 4002 - 9p ea.) + s
IN 4003 - 9p ea.)



1-0A bridge (400V) - 36p + H
1-6A " (200V) - 48p + H
1-6A " (800V) - 70p + H
2-0A " (200V) - 72p + H
2-0A " (600V) - 90p + H

MULLARD MODULES

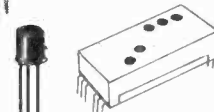LP 1173 - £6.75 + H
LP 1184/2 - £7.20 + H
LP 1185 - £5.60 + H
LP 1186 - £6.90 + H
LP 1400 - £7.25 + H



TRANSISTORS


BC 107 - 18p s
BC 108 - 17p s
BC 109 - 18p s
BFY 50 - 24p s
BFY 51 - 24p s
BFY 52 - 24p s
2N 3055 - 80p s
2N 2646 - 94p s
TIP 2955 £1.14 s
TIP 3055 - 61p s
BC 237B - 13p H
BC 238C - 12p H
BC 239C - 14p H
ZTX 107 - 12p H
ZTX 108 - 11p H
ZTX 109 - 13p H
ZTX 300 - 15p H
ZTX 500 - 16p H
MJE 340 - 62p H
TIP 31A - 36p H
TIP 32A - 40p H
2N 3819 - 32p H
3N 141 - 65p s
CS 715 - 18p H
(Similar to 2N 3819)

I.C.'s

T05 Reg - £1.10 s
MVR 5 - £1.55 s
MVR 12 - £1.55 s
MVR 15 - £1.55 s
LM 309K - £2.12 s
7805 - £1.50 s
7812 - £1.50 s
7815 - £1.50 s
7824 - £1.50 s
±15V D.I.L. - £2.82 s
TBA 231 - £1.75 H
TBA 800 - £1.60 H
TBA 810S - £1.80 H
TBA 820 - £1.20 H
ZN 414 - £1.30 H
ZN 424 - £1.25 H
741 Op-amp - 54p s
747 Op-amp (Dual 741) - 95p s
748 Op-amp - 48p s
555 TIMER - 84p s
556 (dual 555) - £1.44 s
HA 1156 - £1.60 H
(similar to MC1310P)
ORP12 - 72p s
8A Triac - £1.18 s
2N 1034E - £4.70 s

'INTERNATIONAL 25'

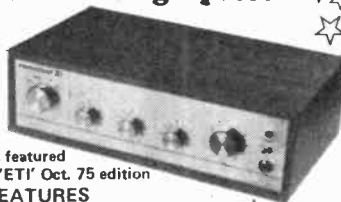Build yourself a **BIG SOUND** amp at a budget price



As featured in 'ETI' Oct. 75 edition

FEATURES

- * Triple Op-amp pre-amplifier
- * Power 'Darlingtons'
- * Modern styling
- * 25W per channel into 8 ohms.

Complete kit with assembly instructions
Overseas orders £34.50
S.A.E. for full spec.

£29-95
+ £7.48 VAT

BOOKS (z)

Hi-fi hints and tips 38p ea.
Towers international transistor selector £2.95 ea.
Electronic circuit design handbook — a must for electronic enthusiasts £4.50 ea.

CONDITIONS OF SALE


All prices are ex-VAT
If affixed with s add 8%
If affixed with H add 25%
Z = Zero rated
Package & posting free for orders over £3.00
Overseas orders add 15%
Cash with order. Cheques/Postal Orders to Doram Electronics Limited, P.O. Box TR8, Leeds, LS12 2UF
Small order handling charge of 40p for orders under £3.00

DORAM'S NEW CATALOGUE — THE AMATEURS GOOD COMPANION

ONLY 60p
inc. post & packing.
Free up-date service until Aug. 1976.

'SAMOS' CASES

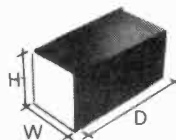Low-cost blue cover and white base PVC steel cases



S1	50W x 50H x 100D	£1.03 + s
S2	100W x 50H x 100D	£1.17 + s
S3	150W x 50H x 100D	£1.31 + s
S4	50W x 75H x 125D	£1.47 + s
S5	100W x 75H x 125D	£1.68 + s
S6	150W x 75H x 125D	£1.97 + s
S7	200W x 75H x 125D	£2.19 + s

SPECIAL OFFER!!

If catalogue ordered simultaneously with order for SAMOS cases - case price less 25%

DORAM
An Electrocomponents Group Company

"The Doorway to Amateur Electronics"

NAME.....


ADDRESS.....

POST CODE.....

I enclose 60p. Please send me by return my Doram Catalogue. (Overseas orders except B.F.P.O. please add 30p for post and packing surface only).

VOLTMETER

MILLI

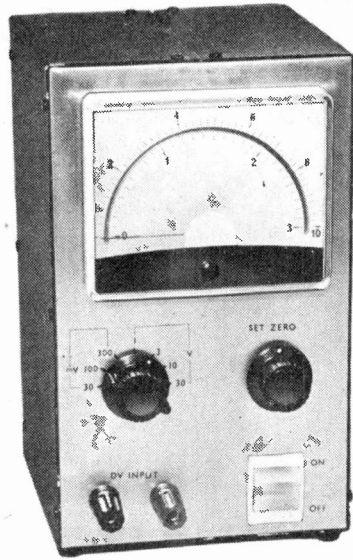

MILLIVOLTMETER

By H.T. KITCHEN

THE test meter to be described was designed and built to enable work to be carried out on transistor equipment involving low currents and medium to high impedances. Under these conditions, the loading effect of the old faithful Avo 8 at 50 micro-amps f.s.d. (20k Ω /volt) was too great, causing doubts to be cast on the validity of the readings so obtained. A test meter with a much higher input resistance was required, and in order to save money it was decided to build one. The requirements were plain from the onset; it had to be quick and easy to build, accurate, with good long term stability (an impedance transformer or meter amplifier was clearly necessary) and it had to be reasonably inexpensive. Since the meter movement

was already to hand, the project turned out to be surprisingly inexpensive, particularly in view of its specification.

CIRCUIT DETAILS

The instrument uses a 741 operational amplifier, the overall gain of the circuit being set by means of two resistors. In the circuit of Fig. 1 these two resistors R12 and R14, the actual voltage gain being given by $\frac{R12 + R14}{R12}$. The meter movement used had an f.s.d. of 100 microamps, and since it had been decided to aim for an overall sensitivity of 1 microamp (1 Meg ohm/volt) it was necessary for the amplifier to provide a current gain of 100 times. This is well within its capability, and, due to the negative feedback the linearity is excellent. The voltage gain required was 260 times, given by the meter resistance of 2,600 ohms, and current consumption of 100 microamps. The actual voltage gain was 270 times or 270k + 1k/1k allowing a small margin for component tolerances.

SPECIFICATION

Ranges

30mV : 100mV : 300mV : 1V : 3V : 30V : ∞
1M Ω /V

A divide by ten switch decreases the sensitivity of each of the above ranges by a factor of ten allowing measurement up to 300V. The sensitivity with the divide by ten facility in reduces to 100k Ω /V

Accuracy

Dependent on components (meter and multiplier resistors)

Drift

At 60°F 300 μ V max. in 5 mins. (one third scale division)

SET ZERO

Setting of the meter pointer to zero is accomplished by means of VR1. Since voltage change required for zero setting also has to be applied to the inverting input (along with the negative feedback) it is necessary to isolate the inverting input from any low impedance source, and the 470k Ω resistor R10 serves this purpose. R9 and R11 limit the swing obtained by VR1, so providing a finer zero adjustment. Even so, the resolution obtained is small, and a multi-turn potentiometer is highly recommended. Failing one of these, a low value

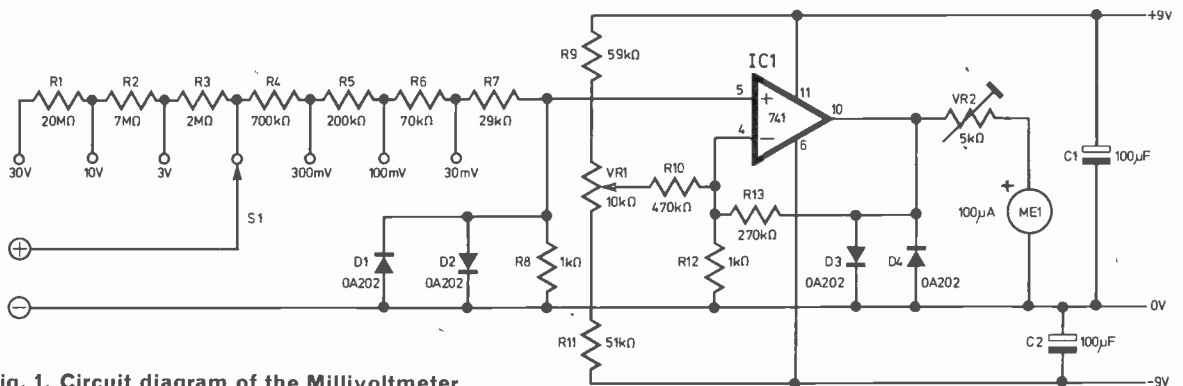


Fig. 1. Circuit diagram of the Millivoltmeter

variable resistor can be connected in series with, say, R9, this then serving as a fine zero adjust; initial, or coarse, zero being set by VR1.

PROTECTION

Although the 741 is a relatively sturdy device, it will not withstand the large overloads to its input circuitry that may result from an incorrect range setting. The diodes D1 and D2 have therefore been incorporated to restrict the maximum input voltage to about 650mV. Voltages less than this will pass through to the amplifier unaffected whilst under overload conditions the diodes will conduct excessive current to earth, thus protecting the 741. The maximum voltage swing at the output can be almost as much as plus or minus the supply voltage. This means that there is a very real danger of the meter movement being damaged by excessive voltage swings. Diodes D3 and D4 serve to limit the voltage swing at the output, starting to conduct, as do the input diodes, at around 600 to 700mV. Since the meter requires 260mV for f.s.d., the maximum overload cannot exceed some 200%, a figure well within the limits of any good meter movement. The 741 has a maximum output current limited to 20mA, hence no damage will result when the diodes are forced into conduction.

COMPONENTS . . .

Resistors

R1	20M Ω 1%	(two in 10M Ω in series)
R2	7M Ω 1%	
R3	2M Ω 1%	
R4	700k Ω 1%	
R5	200k Ω 1%	
R6	70k Ω 1%	
R7	29k Ω 1%	
R8	1k Ω 1%	All resistors $\frac{1}{4}$ W
R9	59k Ω 5%	
R10	470k Ω 5%	
R11	51k Ω 5%	
R12	1k Ω 2%	
R13	270k Ω 5%	
R14	27k Ω 5%	

Potentiometers

VR1	10k Ω
VR2	5k Ω
VR3	5k Ω
All 10 turn helical	

Capacitors


C1	100 μ F 12V elect.
C2	100 μ F 12V elect.

Semiconductors

IC1	741
D1-D4	OA202 (or similar low leakage silicon types)

Miscellaneous

S1	Two single pole 12-way wafers plus shaft ("Makaswitch") RS Components (access through Doram)
S2	Two pole on/off
M1	100 μ A 2,600 Ω internal resistance BPL type S30V or any 100 μ A meter movement of good accuracy

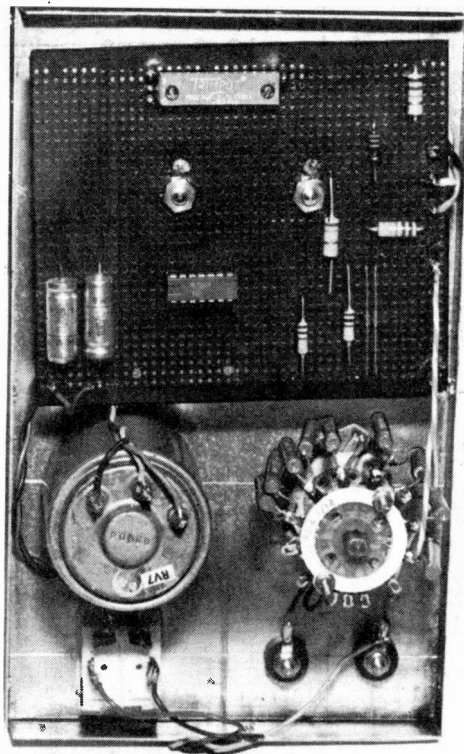

RANGES

For the purposes for which the test meter was built, an overall voltage range of 30mV to 30V was adequate, the steps being in the 1-3-10 sequence. Resistors R1 to R7, inclusive, are the series range resistors. Although the minimum range is 30mV, the meter scale permits reading very much less than f.s.d. to be taken in confidence.

The maximum voltage the instrument can read is 30V. However, this can be easily increased to 300V (see "Modifications").

COMPONENTS

The meter movement used on the prototype was a BPL type S30V, with an internal resistance of 2,600 ohms, and an f.s.d. of 100 microamps. Clearly, other meter movements can be used, but if these differ appreciably from the one used on the prototype, then it is desirable to alter R13 to keep the gain just above the minimum required. This way, the negative feedback is always as high as possible. The voltage required for f.s.d. can be calculated from a knowledge of the meter current rating and internal resistance, and as the input sensitivity of the amplifier is 1mV (1 microamp across 1,000 ohms) this will be the gain the amplifier must provide. R13 can then be calculated as outlined earlier, and for this purpose the formula can be simplified to R13/R12.

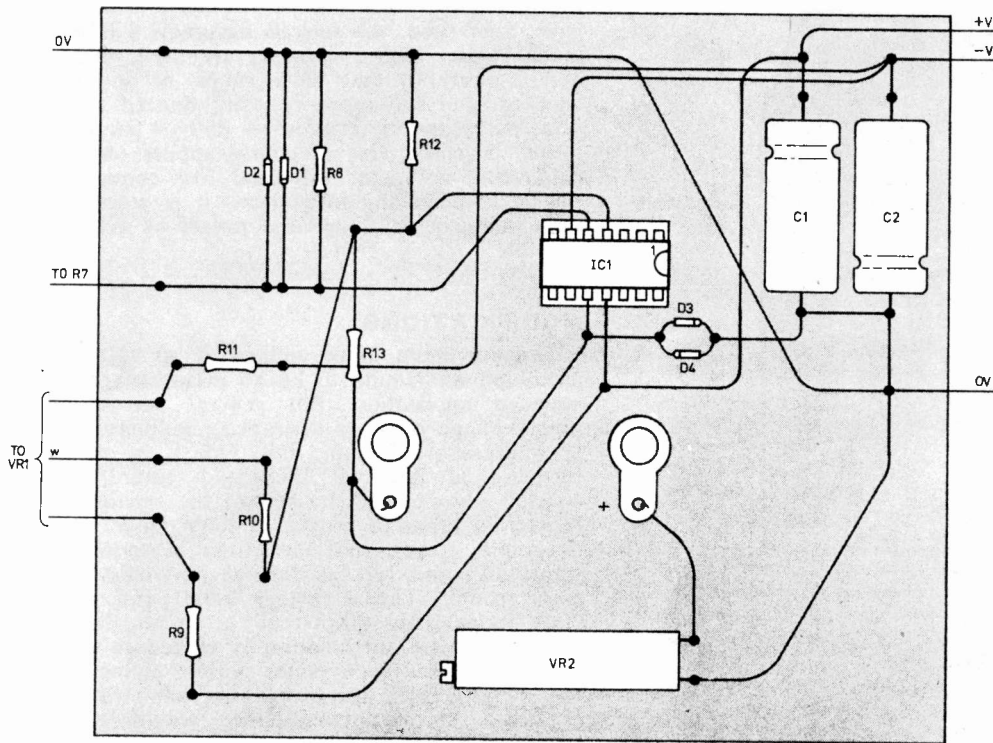


Fig. 2. Wiring arrangement used in the author's prototype. The components are mounted on perforated board and the wiring is carried out on the underside

Resistors R1 to R7 inclusive, must have a tolerance in the region of 1%, if the test meter is to have any pretensions to accuracy. The tolerance can be relaxed to 2% or even 5% with a corresponding degradation in overall accuracy. In the absence of 1% resistors, it is possible to use 5% resistors in a series/parallel arrangement especially if an accurate voltmeter is available for checking the calibration.

The set zero control on the prototype was a ten turn potentiometer purchased ex-equipment, and it is recommended that the advertisements columns of the various electronics magazines be searched for such a control. The resolution that such a control is capable of is such that no one who has used one would ever willingly return to the "ordinary pot".

Diodes D1 to D4 must be low leakage silicon types so as not to affect the normal operation of the instrument.

The current consumption of the complete amplifier is very low, and with intermittent use a pair of PP9 batteries should last a long time.

CONSTRUCTION


The complete instrument was built into a case as shown in photos. Any suitable case can be used; the author's was made of 22 s.w.g. aluminium, the panels being held together with small self tapping screws. The dimensions may require altering if components other than those specified are used.

The case was sprayed crackle finish black, the front panel being "brushed" aluminium. This is quite an easy finish to achieve, as well as being aesthetically pleasing. It also takes letter transfers well.

The "brushed" effect is obtained by rubbing the panel with very fine steel wool dipped in fine oil. The panel must be free from dents or marks. The steel wool is repeatedly drawn across the panel in as straight a line as possible until the desired effect is obtained. The panel is then thoroughly cleaned, dried, and then the transfers are put on. Finally, several thin coats of protective varnish are sprayed on. Carefully done, the effect is very pleasing, and rivals commercial panels.

The i.c. in the prototype was mounted in a socket, and this was fitted, along with the other amplifier components, on a piece of 0.1" wiring board. The layout is not critical. This is then secured directly onto the back of the meter movement, using the meter's terminal nuts, see Fig. 2.

The range resistors were mounted directly onto the range switch. This is a R.S. Components "Maka-switch", two wafers, single pole twelve way, being used. The wafer nearest the front panel does the range switching, the rear wafer being used as a slave, the range resistors being slung between the two wafers. This switch must have good insulation properties, as the maximum resistance on the 30 volt range is $30M\Omega$.

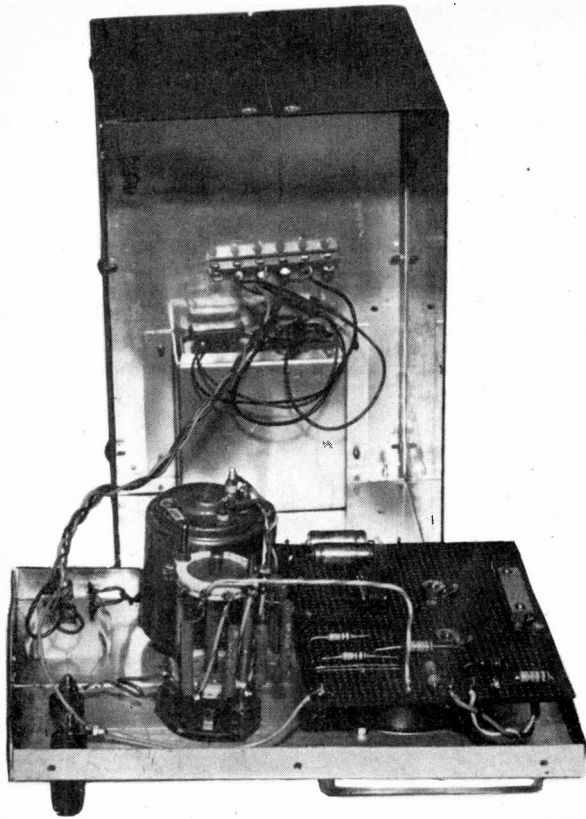

CALIBRATION

Calibrating the completed test meter is simple, provided an accurate voltmeter is available. Both meters are connected across a stable direct voltage, the range switches being appropriately set. VR2 is then adjusted to give the same reading as the calibrating voltmeter. If 1% resistors have been used for the range resistors, then it should suffice to set the

test meter to read at one point only. If 2% resistors have been used, the overall accuracy will be that much worse. If 5% resistors are used, then it is highly desirable that each range be individually checked, and the range resistor adjusted as necessary, by means of other series and/or parallel connected resistors. This of course applies only if the calibrating voltmeter will read low enough. Since this is a measuring instrument, it is worth taking time and trouble to get the ranges as accurate as possible.

MODIFICATIONS

The maximum input voltage of 30 volts of the prototype was found to be no disadvantage for its intended application. For general use, a higher input voltage range is desirable, and there are two possibilities of obtaining this. One is by means of further input resistors: this would require a 70M Ω resistor added on to the end of the existing 20M Ω resistor in order to provide a 100V range. Difficult to obtain, (seven 10M Ω resistors in series is one possibility) and leakage resistances would possibly cause trouble. Then a further 200M Ω resistor for a 300V range. This is not really a viable solution. A much more elegant solution is to reduce the gain of the amplifier by a factor of ten, giving a 300V top range. Since the range resistors would stay unaltered, the input resistance would go down to 100k Ω /volt, i.e. the input current would go up to 10 microamps. This would not be any serious disadvantage since most circuits operating at 300V can "afford" the 10 microamps the test meter would draw.

Fig. 3 shows how the test meter should be modified. The feedback resistors should be wired as shown to prevent feedback being lost during range switching. When the range is changed, another calibration resistor is switched in (VR3) which will allow the gain in the $\div 10$ range to be set exactly one tenth that of the normal range. ★

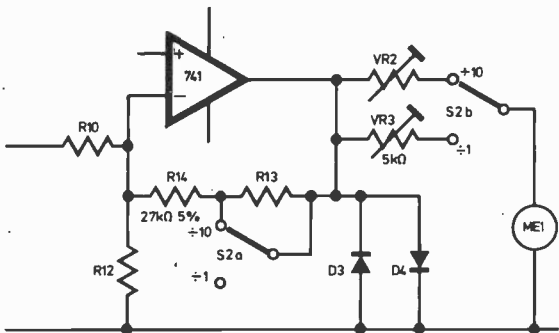


Fig. 3. The modifications required to add a $\div 10$ switch to the millivoltmeter

PE

A VOLUME OF PRACTICAL KNOW-HOW

... can be made using these new-look self binders for PRACTICAL ELECTRONICS to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At £1.00 incl. VAT and postage (as from the May Issue binders will cost £2.10) they are obtainable from:

**Post Sales Department, IPC Magazines Ltd.
Carlton House, 66-68 Great Queen Street
London, W.C.2**

I enclose P.O./cheque value..... for..... binders at £1.90 each for Practical Electronics Vol. No's.....

Name.....

Address.....

Date.....

PE

The purpose of this supplement is to list the various forms of electronic effects units popularly used in the production of modern music, and to give some idea of their principles of operation. Block diagrams and circuits are given to illustrate typical techniques used and some commercially available units are shown.

ELECTRONIC EFFECTS

CONTENTS

FUZZ	2	VIBRATO	5
WAA-WAA	2	OCTAVE DIVISION	6
SWELL	3	RING MODULATION.....	6
ENVELOPE SHAPER	3	PHASING	6
SUSTAIN	4	REVERBERATION	7
TREBLE BOOST	5	ECHO	7
TREMOLO.....	5	GUITAR SYNTHESISERS.....	8

FUZZ

Probably the first electronic effect to be used with guitars was fuzz. In its simplest form fuzz merely adds distortion to the original guitar signal, and in doing so provides an output which is rich in harmonics which can either be used on its own, or to enhance other effects such as waa-waa, sustain, etc.

The popular way of achieving the effect is with the use of non-linear devices (diodes, etc.) either directly in the signal path as shown in Fig. 1 or in the feedback loop of an amplifier. Either method results in a squaring or clipping of the incoming signal. A side effect from this type of process is that the output level will tend to remain much the same even though the signal from the guitar is naturally decaying. This in fact forms the basis of another effect (see SUSTAIN).

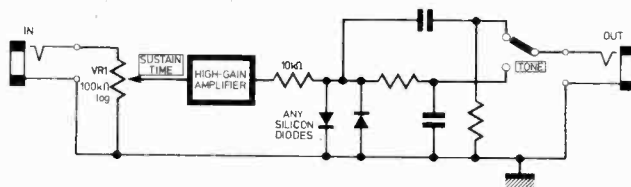


Fig. 1. A typical method used to obtain the Fuzz effect

In Fig. 1 the amount of fuzz is controlled by the setting of VR1 which sets the input level required to cause the diodes to conduct and thus square off the signal. Other fuzz circuits exist which provide distortion which does not depend on signal level. In general, these are more complex electronically

and it is a debatable point whether or not the increase in cost is worthwhile.

Some units couple the fuzz effect with some form of tone control, for example, the "Tone Bender" from Coloursound. This allows treble or bass boosting which mellows or sharpens the original fuzz sound.

WAA-WAA

One of the most popular effects used with guitars is that termed the Waa-Waa effect. This essentially consists of a band-pass filter whose centre frequency is varied up and down a portion of the audio spectrum (approx. 200Hz-3kHz).

In fact this simulates the operation of the mouth when pronouncing the sound waa-waa. The mouth cavity forms a resonator whose centre frequency is controlled by the actual volume of the cavity, and this in turn is controlled by the position of the lips and gums. Electronically, this is performed by a band-pass filter whose resonant frequency is controlled by a potentiometer usually mechanically linked to some form of pedal assembly. The filter usually takes the form of a band stop network (twin-tee, etc.) in the feedback loop of an amplifier. This produces the band pass function required to achieve the waa-waa. Such an arrangement is shown in Fig. 2 where a variable resistor is inserted between A and B.

The effect can be automated (then becoming known as auto-wah) where the sweeping is controlled by an internal oscillator. A typical circuit for this is shown in Fig. 3. In this case the transistor replaces the variable resistor,

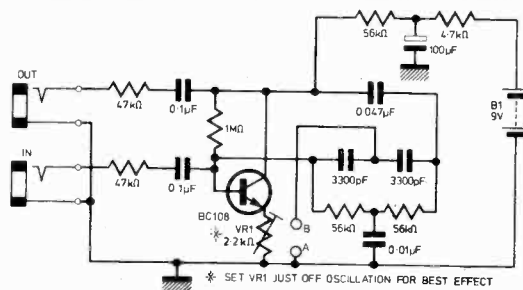


Fig. 2. For Waa-Waa (foot operated) insert a 100kΩ potentiometer between points AB. For Auto-Waa insert circuitry in Fig. 3

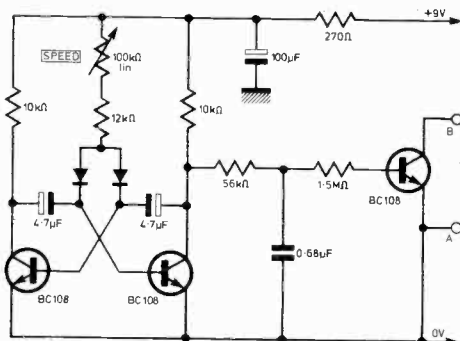


Fig. 3. Additional circuitry for Auto-Waa effect

and although a fair amount of non-linearity will occur with the transistor used in this mode, in practice the harmonics generated will tend to add to the general waa-waa sound.

By selectively boosting some harmonics and attenuating others, it is possible to change the harmonic structure of the signal and hence the actual sound by a considerable amount. As a filter can only boost what is already present in the signal, waa-waa's are often combined with fuzz or treble boost before the filter to obtain more harmonics for it to act on.

Popular commercial combinations are fuzz-waa, or wah-fuzz-swell, fuzz-phaser.

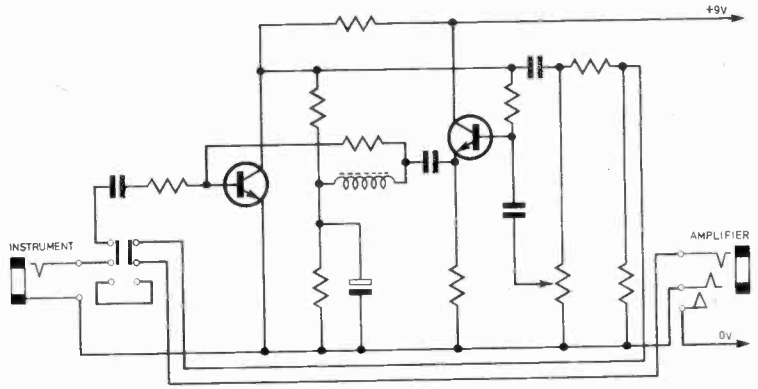


Fig. 4. A commercial Wah-Wah circuit (Colorsound). We regret that we cannot supply component values



Wah-Wah pedal (Colorsound)

—SWELL

Swell is simply a foot-operated volume control. However, despite its simplicity, it may be used to alter the envelope of the guitar signal for "violining", cutting off the guitar's sharp attack to give a smooth attack and decay, or any other envelope modification that may be desired. The so-called "violin" effect is obtained with a swell pedal and a guitar, by keeping the

level well down when the string is plucked, and then as the guitar envelope decays away, the pedal is "opened" to maintain the output at a reasonably constant level, thus simulating a violin type envelope.

Swell in commercial pedals tends to be included with other effects as an extra, and can increase the versatility of a waa-waa with negligible expense.



Wah-Fuzz-Swell (Colorsound)

—ENVELOPE SHAPER

The envelope shaper is best known in synthesiser applications where some form of envelope control is required to shape the various waveform or noise generators which are normally continuously running. Although the output from a guitar has its own envelope, if additional shaping is added, a new range of interesting effects can be obtained.

The shaper has in common with the swell pedal the ability to alter the volume of the signal passing through it; the essential difference being that the envelope shaper performs the operation automatically. After sensing the beginning of a note, from that point in time it allows independent control of

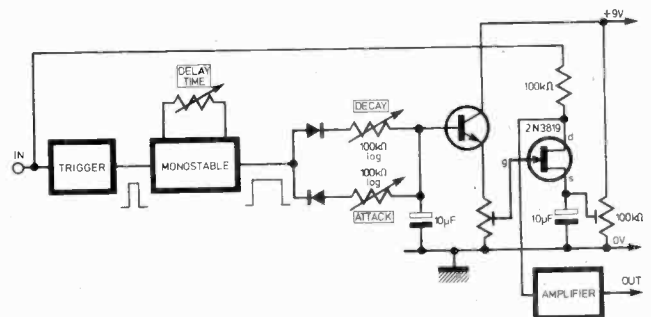


Fig. 5. Envelope Shaper block diagram

the attack, decay, sustain and release times in sophisticated envelope shapers, or just the attack and decay times in standard ones.

Although the term envelope shaper implies that the signal is processed by the shaper itself, in fact it merely provides a suitable control voltage for a VCA (voltage controlled amplifier) which is the device actually responsible for gain control. In the more simple attack—decay envelope shaper, the attack control determines the time taken for the VCA to reach minimum attenuation (i.e. fully "opened") and the decay control the time taken to reduce to minimum gain (fully "closed").

On some versions, another control is added which allows the decay mode to be delayed by a variable sustain time control.

ADSR ENVELOPE SHAPER

The more complex shaper almost exclusively found in synthesisers is termed an ADSR envelope shaper (a typical circuit appears in this issue). ADSR (attack-decay-sustain-release) provides two additional facilities to those of the attack-decay type: namely sustain and release. The ADSR attack control corresponds to the same control on the simpler shaper, and the release control to the decay. The ADSR decay control, however, determines the time taken for the VCA level to drop to a sustain level set by the sustain control. The sustain mode is only entered into when the key on the synthesiser keyboard is held down. If the key is raised prematurely the shaper will go directly into the release mode and the note will decay away at the release rate.

SHAPING

The guitar envelope has a very sharp attack, and if this is rounded off by an envelope shaper, it can be made to perform a similar type of operation to that performed by the swell pedal and provide, for instance, the violin effect. Likewise, a bass guitar can be made to sound like a cello. Also, by using a shaper to artificially remove the ends of the notes, it is possible to obtain sounds similar to pizzicato strings, or banjo. The two controls, attack and decay, can be exploited to produce an endless variety of envelopes and therefore effects.

A point in passing: when playing through an envelope shaper, it is worth mentioning that it is important to leave slight pauses between the notes to ensure correct triggering on each successive new note.

SUSTAIN

Another treatment in which gain change is involved is Sustain. As the level from the guitar decays away, the sustain circuitry increases the gain in the channel to maintain the output at a constant level.

A compromise has to be reached when deciding the range of gain change possible, as with too little gain variation the sustain effect will not be noticeable, whilst too much will result in excessive hum and noise pick-up when the strings are still.

The circuit functions by monitoring the output level and deriving a feedback signal which controls a VCA such that the output level is held constant.

In this application, the VCA must reduce its gain for higher control voltages and vice-versa. The voltage at the output of the follower (some form of rectification/integrator stage) is proportional to the output signal level and it is arranged that a small change in this voltage will cause a large gain change in the VCA which will result in a substantially constant output level until the VCA gain reaches its maximum value.

a high gain amplifier is fed into a squaring or limiting circuit (often two diodes back to back) and this has the desired effect of maintaining a constant output level but also, of course, adds a large amount of distortion. In order to

mask this distortion, a fair amount of h.f. feedback is incorporated which, although making the sound less bright, tends to create a less distorted sound, tending to be more like the original input.

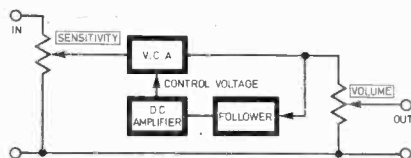


Fig. 6. Typical arrangement used in Sustain circuitry

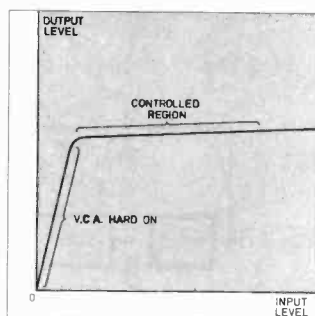


Fig. 7. The Sustain principle shown graphically



Maestro Sustainer (Henri Selmer & Co.)

OTHER SUSTAINS

The effect referred to above is sometimes known as sustain-without-fuzz since, in theory, signal distortion is not introduced. However, popular sustain effects units use similar circuitry to that of fuzz units to achieve constant output level with respect to input level. In this case, as in fuzz circuitry, the output of

TREBLE BOOST

Treble Boost, as the name implies, boosts the treble content of the input. The harmonics then overpower the fundamental of the signal and the sound is given a shriller quality. The effect combined with sustain and reverberation forms the basis of the "Floyd"-type sound.

The actual electronics involved in producing the effect are fairly simple. A high pass filter whose output rolls off at extreme h.f. (in terms of guitar frequencies) is formed around an op-amp (see Fig. 8). The input is first attenuated by R1 and R2. The amplifier has a maximum gain at around 3.5kHz, below this it decreases at 6dB per octave (C2R3) and at about 4kHz the response flattens out as C3 becomes effective. Finally at higher frequencies the gain falls off to unity as the effect of C3 becomes more and more predominant. This results in a response with a rounded peak occurring in the region of 3-4kHz and it is this that is responsible for the boost effect. Higher frequencies are rolled off since they are beyond the range required to contain the guitar passband.

A depth control is also included

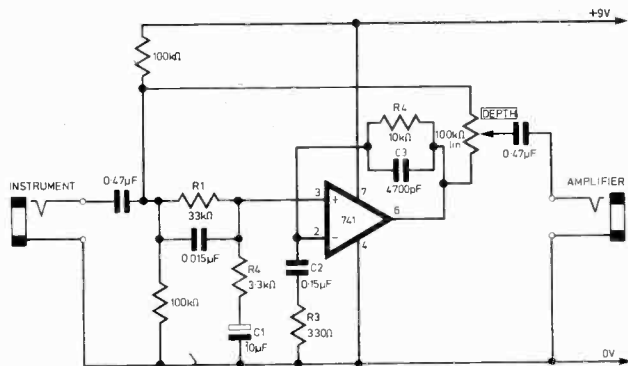


Fig. 8. Typical Treble-Boost circuitry

which merely allows adjustment of the ratio of treble boosted signal to unprocessed signal.

PRESENCE

On some amplifiers a presence control is included as well as an h.f. or

treble control. This can have a similar sort of effect to treble boost. The presence control boosts or cuts mid-band frequencies (1.5-3kHz) and has the effect of brightening the sound or giving the impression of bringing it forward.

TREMOLO

The Tremolo effect is generated by a repeating volume change at a rate usually between 1 and 10Hz. The volume change is accomplished by some form of VCA, which in turn is controlled by a low frequency sine or triangle wave generator.

There are two controls associated with tremolo: depth and rate. The depth control adjusts the amplitude

of the modulating waveform fed to the VCA, and the rate controls its frequency.

When tremolo was first introduced it was intended as an electronic substitute for vibrato, which is frequency modulation rather than amplitude modulation of the signal. The two are often confused, but there is a considerable difference. Tremolo is far simpler to achieve electronically than

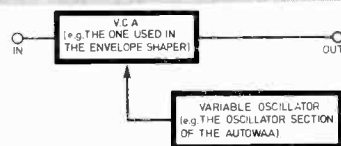


Fig. 9. Principle of the Tremolo effect

pitch modulation. Fig. 9 shows a typical arrangement that may be used to generate the effect.

VIBRATO

The vibrato effect is achieved by altering the pitch of a note up and down around the actual note being played. This can be performed relatively simply on organs, synthesisers, etc. by modulating the frequency of the oscillators.

The effect is also easily obtained manually on most musical instruments using normal vibrato techniques. However, it is possible to generate the effect electronically using the principle that

a rate of change of phase with time constitutes a frequency shift. Circuits exist which allow phase change without amplitude change, and if many of these are cascaded, considerable phase change can be made possible at any frequency. If the phase change is made voltage controllable, then with the help of a low frequency function generator, the vibrato effect can be produced automatically even though the input signal is at a constant frequency.

The Coloursound "Dopplatorne" achieves a spectacular sounding effect based on the frequency bending capabilities of so-called multi-segment phase shifting circuitry as outlined above.

It is interesting to note that electronic vibrato is not a new effect, however. In order to provide a vibrato effect for one of the organs in the Hammond range in the thirties, a valve circuit was added onto the output of the organ to create vibrato.

OCTAVE DIVISION

A note which is an octave below another is at half the frequency. This lower note is called a sub-octave, and can be generated electronically by squaring off the note to be divided and then passing it through a binary divider. The output from this will be at half the frequency of the incoming signal but it will contain a large amount of high frequency harmonics due to its being a square wave. These harmonics can be filtered out, however, to provide a deep bass sound.

The process can be continued further

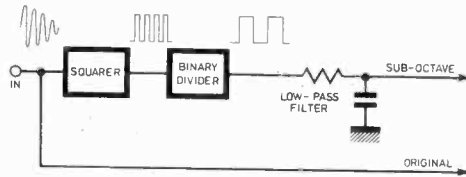


Fig. 10. The Octave Divider principle

to provide other frequencies of 2 or 3 octaves down from the fundamental, and then if mixing controls are also incorporated, independent control of

the levels of the various frequency sub-divisions, can be made.

The octave divider principle is shown in Fig. 10.

RING MODULATION

Ring modulation is an effect which produces complex signals from two inputs by multiplying them together. For two inputs at frequencies f_1 and f_2 the ring modulator produces two new frequencies $f_1 - f_2$ and $f_1 + f_2$. As these output frequencies are only harmonically related under certain conditions, the sound produced is often discordant.

A ring modulator needs two inputs to function. An internal oscillator is often incorporated in the same unit to act as one of these inputs, whilst the other input will be derived from a guitar. In this case one note on the

guitar will produce two notes from the ring modulator and the separation of the two notes in terms of frequency is determined by the frequency of the oscillator.

Alternatively, the same signal may be fed into both inputs, in which case a frequency doubling effect will occur. This happens because the $f_1 - f_2$ component of the output is zero, and the $f_1 + f_2$ provides an output of twice the input frequency. The arrangement will produce the characteristic ring modulation when a chord is played, and intermodulation effects are produced.

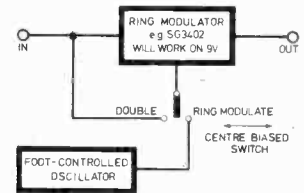


Fig. 11. The Ring Modulation effect

A typical ring modulator arrangement is shown in Fig. 11 where an i.c. is used to perform the multiplication function.


PHASING

Phasing or skyriding was first produced by simultaneously playing the same material on two different tape recorders, but slightly delaying one with respect to the other. The actual phasing sound occurs as the delay sweeps from zero to about 50ms. One method whereby this can be accomplished very effectively is with two tape recorders which should in all aspects be identical, except that one must be equipped with a "varispeed" facility.

The input signal to be phased is fed into the record inputs of both tape recorders and the "after tape" outputs of the tape recorders are mixed 1:1. If the varispeed recorder speed is set exactly at the other speed, then in theory, total signal cancellation should

occur. As the varispeed control is varied either way, all frequencies whose half-cycle periods divide into the delay time an odd number of times, will be cancelled out. This effect in fact forms a comb filter (so called due to the cyclic cancellations in the frequency response thus produced) and is responsible for the familiar phase sound when swept up and down the relevant part of the audio spectrum. The sweeping is performed by varying the delay, which in turn is done by altering the speed of the varispeed machine.

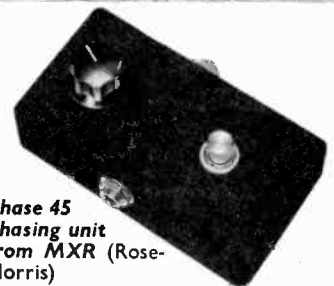A full phase cycle can be achieved in this fashion by commencing with the vari-speed machine adjusted to be running just faster than the other machine, and then by reducing the speed slowly



Phase 45 phasing unit from MXR (Rose-Morris)

(during which time the phasing effect will occur) until it is running just slower than the fixed speed machine.

Although producing a very deep phase effect, this method is really only suitable for studio work, since the delay caused by the tape recorders is not acceptable in live performances.


PURELY ELECTRONIC PHASING

All electronic phasers are now very much in vogue and there are several types available on the market. These are all based on the "phase shift without amplitude change" circuitry mentioned in the vibrato section.

In the sales literature associated with phasers, the word "segment" is often mentioned. A segment is a phase shifting element and, in theory, the more segments a phaser has the deeper will be the phase sound. This is the case in practice to a certain extent, but the greater amount of circuitry and general complexity of multi-segment types is considered by some to be unnecessary, as the sound produced by

those using only a few segments is "deep" enough. In fact, the difference between the two is that multi-segment phasers provide a better approximation to tape phase due to their having a greater number of cyclic dips in their frequency response, than those with fewer segments. As an extra bonus also, the far greater phase shifting ability can be exploited to generate other effects (vibrato, etc).

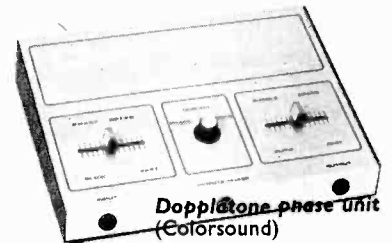As with the waa-waa effect, phasers can only subtract from the original sound, so the best effect is obtained when there are plenty of harmonics available. Hence the reason that a phaser is often coupled to some form of fuzz unit. White noise is particularly effective when phased, or other sounds with large harmonic content.




It is possible to simulate the Chorale or Leslie effect with a phasing unit controlled by a sine or triangle wave oscillator (as most of the commercial units are). When added to an organ or electronic piano, a good similarity to the sound produced by a Leslie speaker is obtained and when used as such can greatly improve the sound produced by cheaper organs and pianos.

REVERBERATION

Sound takes a finite time to travel through air. In an enclosed space, with hard walls (which will reflect sound), there are an infinite number of paths a sound can take from source to listener. As some energy is absorbed at each reflection, the reverberated sound gets progressively quieter. The reverberation time of a room is the time it takes for the sound to fall to one millionth of its original intensity.

This effect can be imitated electronically or electromechanically by a number of means. The cheapest is the spring line. There are two transducers coupled by a spring. One puts vibration into the spring, and these travel to the far end in a few milliseconds. Some of these vibrations are reflected back down the spring and some drive the output transducer. The vibrations are thus reflected back and forth along the spring eventually dying away.

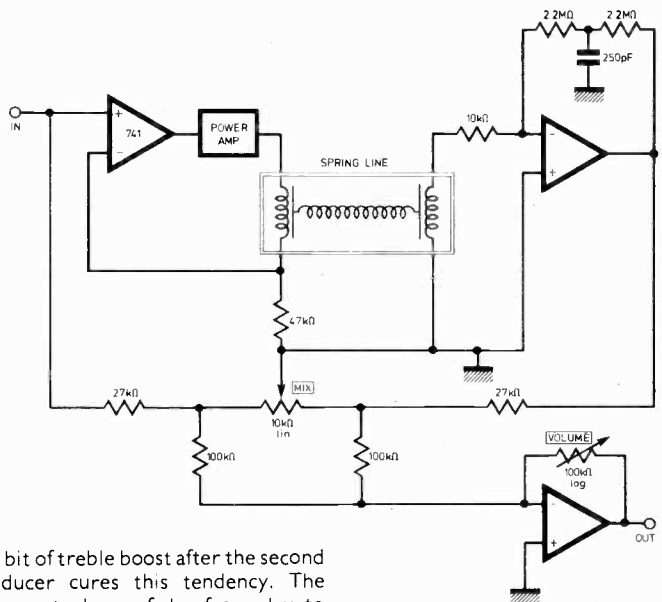Spring lines need a fair power to drive them, and the response is improved if driven by a constant current. The treble response is never very good,



but a bit of treble boost after the second transducer cures this tendency. The depth control crossfades from dry to fully reverberated by shorting out what is not needed.

Fig. 12. Typical Reverb. circuitry

ECHO

It is also possible to produce reverb with a digital delay line. This converts the incoming signal into a binary code, and this is then clocked along a series of shift registers and reconverted to analogue form at the other end. In its basic form, it provides echo of any delay time, governed by the number of shift registers and the clocking rate used. If outputs are picked off the line at various points and fed back to the beginning, complex patterns are set up

which give the effect of reverb. This is a rather expensive device, but will no doubt become cheaper as i.c. prices fall.

The more usual way of getting echo is with a tape delay. This usually consists of a tape loop with erase, record and a number of play heads. The output is any required mix of the play head outputs and the direct signal.

As the tape in a loop quickly wears out, better tape delays have an everlasting cartridge with about five

minutes of tape, as this is more reliable.

Echo without reverb is a rather unreal sound, beloved of Rock and Roll vocalists.

Some interesting effects can be obtained by reducing the delay time to a tenth or a twentieth of a second. At this setting it is no longer possible to recognise the delay and it sounds more like double-tracking, i.e. the same thing played on two identical instruments at the same time.

GUITAR SYNTHESISERS

The Synthi Hi-Fli "Guitar Synthesiser" is of interest in this article as it contains most of the effects discussed already plus several others. In addition, almost all the effects on the Hi-Fli are voltage controllable allowing, where appropriate, automatic control via either low frequency oscillators of various wave shapes or by a voltage derived from envelope detecting circuitry working off the input signal.

A block diagram of the unit is given in Fig. 13. After initial amplification in the foot pedal preamplifier, the signal is sent to the main unit where the various control voltages are generated and the signal processing occurs.

Two foot pedals allow independent control of both the left and right side of the Hi-Fli. The left-hand side has a top boost section, octave-shift facilities (based on the octave divider arrangement), a ring modulator-like system which generates the octave above, and a sustain-fuzz section which creates a fuzz sound whose amplitude is proportional to the signal level but whose harmonic structure varies with it.

The right-hand section (controllable by right pedal) deals solely with the Phase Filter. The speed of the modulating oscillator and the modulation ramp time, as well as the actual modulation voltage applied to the phase shifting circuitry, are all foot-pedal controllable.

The foot pedal control voltages are inverted in the main unit to provide both increasing and decreasing voltages as the pedal is operated. On each of the various controllable functions, there are switches marked +, 0 and -, which allow complementary operation of different effects whilst the pedal is operated.

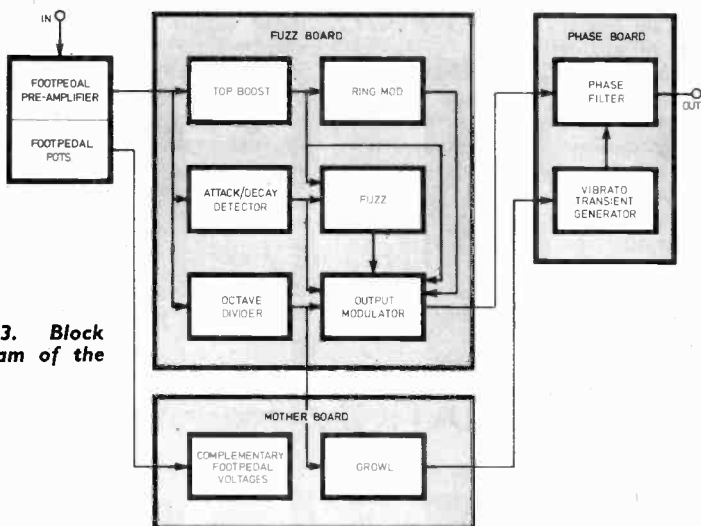


Fig. 13. Block diagram of the Hi-Fli

PHASE FILTER

This portion of the Hi-Fli is probably the most complex in the unit, but is responsible for creating the most dynamic sound effects. Phasing, frequency shifting (vibrato), waa-waa (one resonant peak), waw-waw (six resonant peaks) and meow (two sets of three resonant peaks moving in opposite directions) are all generated by the Phase Filter section.

A split 12-segment phase shifting arrangement is used. The great frequency bending capability of this circuitry is very evident when the frequency shift slider is moved and, depending on the rate, the note can be shifted by as much as several semitones.

This function is performed automatically with an oscillator to provide the vibrato effect. The oscillator can either be continuous, or triggered such that after the note is played the amplitude decreases or increases with time at a predetermined rate (either manually set or foot pedal controlled).


The oscillator and decay circuitry can also be used to control the phasing mode (of which there are two) or the other effects mentioned earlier.

In order to provide effects which are triggered at the beginning of a note (for example, a vibrato which gradually increases as a note decays away), some form of trigger signal must be derived. This is not as easy as it may first appear, since the trigger must not operate on random noise produced in the handling of the guitar. On the other hand, however, it must be able to operate correctly on low level outputs in quiet passages.

The derivation of the trigger pulses is therefore a relatively complex operation and requires a fair amount of circuitry. The signal is first equalised, then logarithmically compressed and finally differentiated. This produces a pulse which as accurately as possible defines the beginning of the note. The same circuitry is used to detect rapid reductions in level (the end of a note).



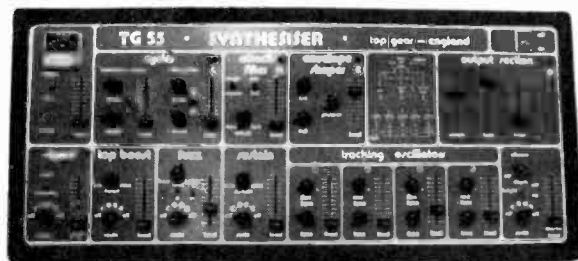Synthi Hi-Fli guitar synthesiser (Colorsound)



Another recently introduced Guitar Synthesiser from Top Gear

Time Constants

By D. MAYNARD

Most of us are aware of the fact that capacitors and inductors behave differently when a current or voltage in a circuit is suddenly changed. We may know that an exponential growth or decay is involved, but one usually finds that, when exact values need to be determined, the text books and slide rule have to come out.

This article sets out to put together some useful formulae, and also a set of curves for quick calculation of currents and voltages.

RC CIRCUITS

Fig. 1a shows the circuit for the first set of equations and waveforms. When dealing with capacitors, it is usual to consider voltage rather than current. Let us consider what happens if the square wave of Fig. 2a is applied to the input. The maximum value is E volts and there are two changes that have to be accounted for. The first is the leading edge where we have a positive going change, and the second is the trailing, or negative going edge.

SEQUENCE OF EVENTS

The voltage across a capacitor's plates cannot change instantaneously and so when the input goes from 0 to E volts, the whole E volts appears initially across the resistor. Then, as the capacitor charges up, the voltage across it increases, and the resistor voltage decreases. At all times the sum of the resistor and capacitor voltages are equal to the input voltage. Fig. 2 shows typical voltages and currents in the circuit. The actual shape of the resistor and capacitor voltage waveforms will depend on the time constant ($C \times R$) of the circuit.

The rising edge of the capacitor voltage is given by:

$$v_c = E \left[1 - \exp. \frac{-t}{CR} \right]$$

This is shown in detail by curve 1 of Fig. 3. The scale of the horizontal axis is in terms of the time constant CR. On the vertical axis unity is equivalent to E, so that if the square wave had an amplitude of 9 volts, all the values on the vertical scale are multiplied by 9. Using the curve we can find the actual voltage on the capacitor at any time after the initial change provided we know the time constant. For example, a $1\mu\text{F}$ capacitor and a $10\text{k}\Omega$ resistor produce a time

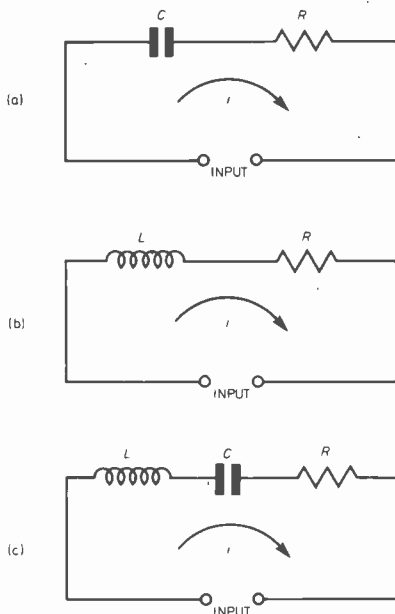


Fig. 1. (a) CR circuit, (b) LR circuit and (c) LCR circuit

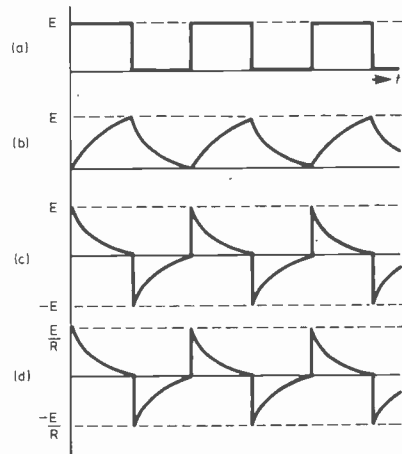


Fig. 2. Waveforms in CR circuit. (a) input voltage, (b) capacitor voltage, (c) resistor voltage, (d) current

constant of 10^{-2} seconds, or 10 milliseconds. After 5τ (one half of the time constant) the voltage is $0.39E$.

On the trailing edge, the capacitor voltage equation is:

$$V_c = E \exp \frac{-t}{CR}$$

This is shown by curve 2 of Fig. 3. The scales of the horizontal and vertical axes are the same as for the leading edge. The positive and negative impulses associated with the resistor voltage waveform are defined by the following two relationships:

$$v_R = E \exp \frac{-t}{CR} \text{ for the positive impulses.}$$

and

$$v_R = -E \exp \frac{-t}{CR} \text{ for the negative impulses.}$$

In the curves of Fig. 3, the leading edge produces curve 2 while the trailing edge produces curve 3. The vertical axis is in terms of E , and the horizontal axis is again in terms of the time constant CR . To find the initial voltages we only have to remember that, with $t=0$:

$$\exp \frac{-t}{CR} = 1.$$

CURRENT WAVEFORM

The current waveform is obviously similar to the resistor voltage waveform. The difference is that the maximum amplitude is now $\frac{E}{R}$. The leading edge has the form:

$$i = \frac{E}{R} \left[\exp \frac{-t}{CR} \right] \dots \text{curve 2, Fig. 3.}$$

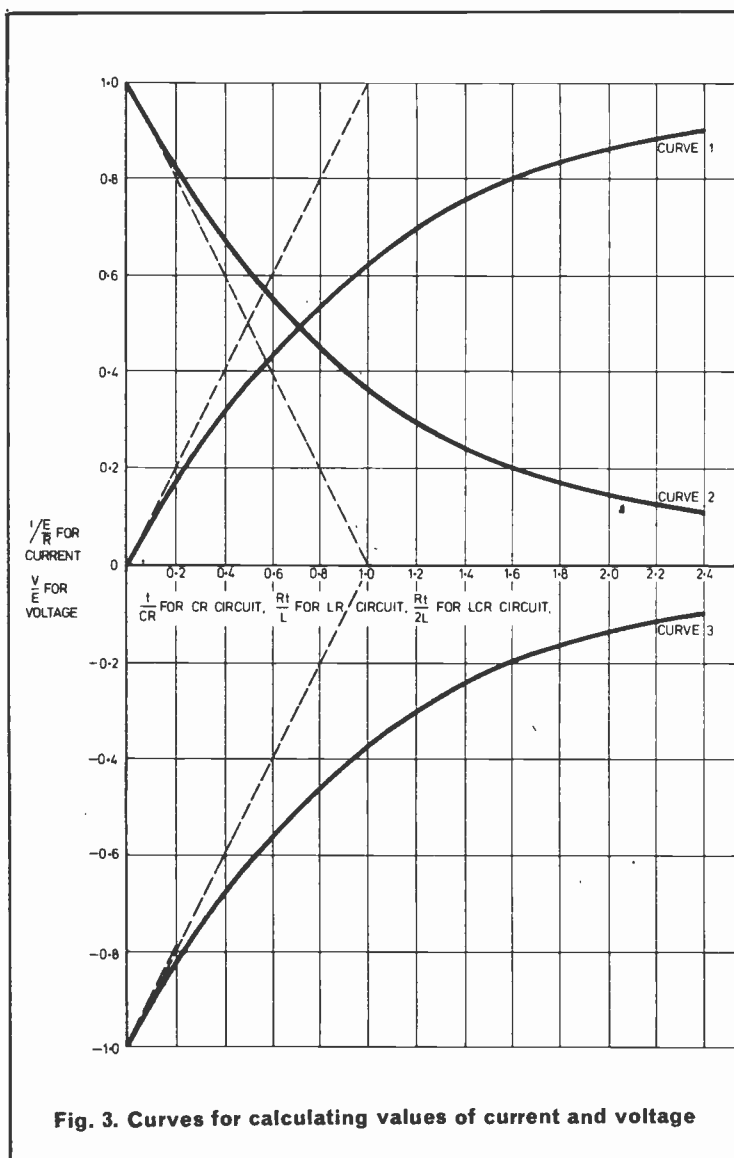


Fig. 3. Curves for calculating values of current and voltage

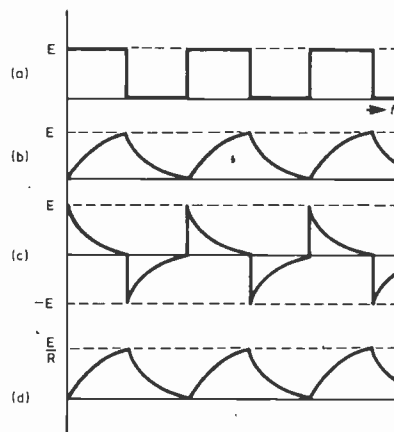


Fig. 4. Waveforms in LR circuit. (a) input voltage, (b) resistor voltage, (c) inductor voltage, (d) current waveforms

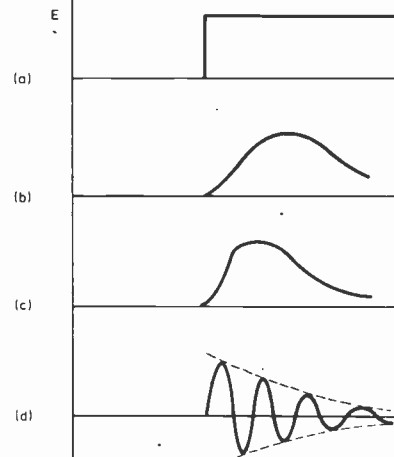


Fig. 5. Waveforms in LCR circuit. (a) input, (b) current overdamped, (c) current critically damped, (d) current underdamped

The trailing edge is a negative impulse:

$$i = -\frac{E}{R} \left[\exp \frac{-t}{CR} \right] \dots \text{curve 3, Fig. 3.}$$

The time constant, and therefore the scale of the horizontal axis, is still equal to CR.

LR CIRCUITS

It is usual to consider current when dealing with the LR circuit, but voltages can easily be obtained from the

fact that $v_L = L \frac{di}{dt}$ and $v_R = iR$. The circuit is shown

in Fig. 1b, and current and voltage waveforms for a square wave input in Fig. 4. Taking the current waveform first, the leading edge is given by:

$$i = \frac{E}{R} \left[1 - \exp \frac{-Rt}{L} \right] \dots \text{curve 1, Fig. 3.}$$

The trailing edge on the other hand has the form:

$$i = \frac{E}{R} \left[\exp \frac{-Rt}{L} \right] \dots \text{curve 2, Fig. 3.}$$

The starting point is zero for the leading edge and $\frac{E}{R}$ for the trailing edge. The time constant is now $\frac{L}{R}$.

VOLTAGE EQUATIONS

To complete the picture we can write down the voltage equations as follows:

For the rising edge,

$$v_L = E \exp \frac{-Rt}{L} \dots \text{curve 1, Fig. 3.}$$

$$v_R = E \left[1 - \exp \left(\frac{-Rt}{L} \right) \right] \dots \text{curve 2, Fig. 3.}$$

For the falling edge,

$$v_L = -E \exp \frac{-Rt}{L} \dots \text{curve 3, Fig. 3.}$$

$$v_R = E \exp \frac{-Rt}{L} \dots \text{curve 1, Fig. 3.}$$

Table 1: Voltage and Current Equations for CR and LR Circuits

	Current		Voltage	
	Leading Edge	Trailing Edge	Leading Edge	Trailing Edge
CR Circuit	$i = \frac{E}{R} \exp \left(\frac{-t}{CR} \right)$	$i = -\frac{E}{R} \exp \left(\frac{-t}{CR} \right)$	$v_C = E \left(1 - \exp \left[\frac{-t}{CR} \right] \right)$	$v_C = E \exp \left(\frac{-t}{CR} \right)$
			$v_R = E \exp \left(\frac{-t}{CR} \right)$	$v_R = -E \exp \left(\frac{-t}{CR} \right)$
LR Circuit	$i = \frac{E}{R} \left[1 - \exp \left(\frac{-Rt}{L} \right) \right]$	$i = \frac{E}{R} \exp \left(\frac{-Rt}{L} \right)$	$v_L = E \exp \left(\frac{-Rt}{L} \right)$	$v_L = -E \exp \left(\frac{-Rt}{L} \right)$
			$v_R = E \left(1 - \exp \left[\frac{-Rt}{L} \right] \right)$	$v_R = E \exp \left(\frac{-Rt}{L} \right)$

Table 2: Damping in LCR Circuit

	Overdamped	Critically damped	Under damped
	$4L < CR^2$	$4L = CR^2$	$4L > CR^2$
Current equation	$i = \frac{E \exp \left(\frac{-Rt}{2L} \right) \sinh Xt}{LX}$ $X = \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$	$i = \frac{E}{L} t \exp \left(\frac{-Rt}{2L} \right)$	$i = \frac{E \exp \left(\frac{-Rt}{2L} \right) \sin Yt}{LY}$ $Y = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$
Frequency of Oscillation	—	—	$f = \frac{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}{2\pi}$

RLC CIRCUITS

The behaviour of this circuit, shown in Fig. 1c, is dependent on the relative values of the inductor, resistor and capacitor. The three current waveforms shown in Fig. 5 correspond to three conditions known as underdamped, critically damped and overdamped.

The underdamped condition occurs when $4L$ is greater than CR^2 , critical damping is when $4L$ is equal to CR^2 and the overdamped condition occurs if $4L$ is less than CR^2 .

STEP FUNCTION INPUT

A step response is chosen as the input waveform to reduce the number of equations required. A trailing edge produces similar results but the waveforms are then negative-going. As the value of L is increased from a small value the rise and fall of the current waveform becomes more abrupt until the point of critical damping is exceeded when a decaying oscillation is produced.

For those interested in the mathematical process, we can write:

$$v = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt.$$

Differentiating with respect to t gives:

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

The solution to this equation is of the form:

$$i = A \exp(p-q)t + B \exp(-p-q)t$$

$$\text{where } p = \frac{-R}{2L}, \text{ and } q = \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

The final solutions are obtained by assuming certain relationships between the components. It is also necessary to know the shape of the applied voltage.

Let us assume a step voltage input from 0 to E volts.

(a) When $4L < CR^2$

$$i = \frac{E}{L \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}} \cdot \exp\left(\frac{-Rt}{2L}\right) \cdot \sinh \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} \cdot t$$

This is the overdamped case shown in Figure 5b. The precise shape will depend on the relative values of R , L and C together with the value of E .

(b) When $4L = CR^2$

$$i = \frac{Et}{L} \exp\left(\frac{-Rt}{2L}\right)$$

The critically damped case is very similar in shape to the overdamped and is the point where oscillation just fails to occur.

(c) When $4L > CR^2$

$$i = \frac{E}{L \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}} \cdot \exp\left(\frac{-Rt}{2L}\right) \cdot \sin \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \cdot t$$

From this, the frequency of oscillation is:

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

The underdamped waveform produced by the above expression is shown in Fig. 5d.

For quick reference the equations for the CR and LR circuits are laid out in Table 1. Table 2 does the same for the LCR circuit. ★

MAIL BAG


The on-going increase in postal and telephone charges does not seem to have made any difference to our post bag or our telephone bill. Enquiries continue to flood in.

We find that there are two points we are constantly mentioning. In the first place we just cannot afford to reply to any *readers' letters*, particularly those not associated with projects we have published, unless they are accompanied by a *stamped addressed envelope*. Were we to undertake to do so our post bill would become astronomical.

We cannot deal with *technical enquiries by telephone*. Readers should write in, giving details of symptoms and perhaps some test point readings, when requesting technical help so that we can at least give the relevant author some idea of the problems involved.

Finally, whilst we normally supply details as to source of components in each project we do assume that the constructor refers to advertisements and has an awareness of general sources. Thus, where goods are generally available we do not specify a source. You could save the cost of a letter by reading the advertisement pages first.

Test Equipment

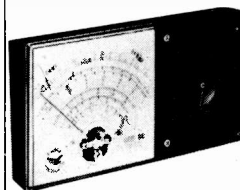

Multimeters


The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.

Please send me details of all your test equipment

NAME

ADDRESS

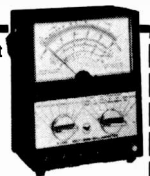

Eagle International Ltd., Precision Centre, Heather Park Drive, Wembley HA0 1SU
Tel(01)-902 8832

Eagle

PE

SEMICONDUCTOR UPDATE

By R.W. COLES

7150
MC8505P
SD600
Z10L, Z15L, Z21L

THERE can be little doubt that microprocessors are the most exciting new development to hit the electronic headlines in recent years, promising, as they do, the power of a computer for use in everyday applications. Until recently though, exciting promises are really all we have seen, and the predicted microprocessor car control chip and other down to earth ideas have never materialised as practical hardware.

I must confess to being a great fan of the microprocessor philosophy, but I am sure there are some readers who feel that computers in any shape or form, are more of a threat, than a promise.

NEW CHIP

Perhaps I can recruit a few more for the microprocessor bandwagon by describing a thoroughly practical new chip from ITT which provides all the programming required to control even the most sophisticated automatic washing machines, in a tiny fraction of the space required for the traditional electromechanical timers. The power of the microprocessor approach allows the **ITT7150** to do much more than just replace a conventional cam timer, improvements are possible to the fabric care wash programs, and the controllability of the machine is enhanced to make life simpler for the housewife (or should it be house person!).

ROMs

At the heart of the 7150 are two r.o.m.s (Read Only Memories) which store the control programmes to control up to ten machine functions in separate, 20 step, wash programmes. There are typically seven main wash programmes which conform to the system of fabric care labelling, but the flexibility of the microprocessor allows complete re-programming by the manufacturers to cope with new wash requirements, or to change the nature of the chip so that it can control a dishwasher, tumble dryer, or central-heating system. The ITT 7150 crams into a single 28 pin d.i.l. no fewer than 2,000 memory bits, about 400 gates and even some analogue circuitry for good measure.

REFRESHING CHANGE

There have been a number of special digital i.c.s produced for use with large m.o.s. memory systems used in computer applications, but in general these can have little interest for amateur constructors because they are too specialised. It makes a nice change therefore, to report on one of these specialised devices which could have wider uses than the manufacturers intended. I refer to the Motorola **MC8505P** "m.o.s. Memory Address Refresh Logic circuit" which sounds a bit of a mouthfull but is in fact a very useful 6 bit binary counter with parallel outputs via six AND-OR-INVERT gates in the form of a six bit multiplexer.

In a dynamic m.o.s. memory system this chip is used to sequentially step through the memory addresses in order that the memory contents may be refreshed before the limited data retention period expires. In between refresh cycles, the memory address is provided by the central processor so that data may be written in or read out, and this explains the need for the six bit multiplexer, which selects either the refresh counter outputs or the c.p.u. address.

The MC8505 operates from a 5V supply, comes in a 16 pin d.i.l., and is compatible with t.t.l. logic.


D.M.O.S.

D.M.O.S. is not a new logic family but a new process for making m.o.s. transistors which makes possible much better devices for linear and r.f. applications.

The D stands for double-diffused, and d.m.o.s transistors are *N* channel devices of the enhancement mode type made by employing a new diffusion technique to achieve precisely controlled channel lengths. Because of this precise channel geometry, gain, cut-off frequency, input capacitance, and on resistance can all be optimised, and an incidental benefit is an increase in drain/source voltage breakdown rating.

A prime example of the d.m.o.s family is the **SD600** from Mullard, which is in fact two dual-gate d.m.o.s devices contained in an 8 pin mini d.i.p. package for use in the front-end of equipment operating in the range 10–200MHz.

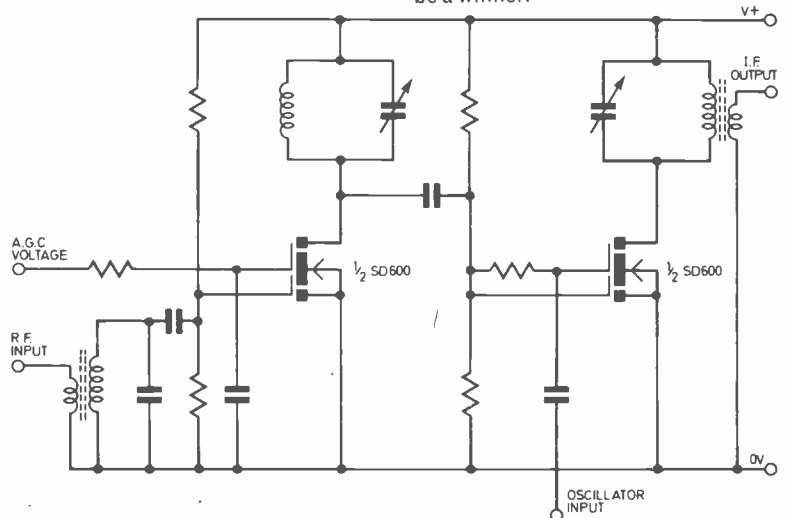A device of this type is ideal for use as the r.f. amplifier and mixer of a high quality f.m. tuner where all the advantages of the d.m.o.s technology give a significant improvement in performance when compared with conventional f.e.t. front-end. Add to these performance advantages the economy and ease of use of the practical minidip package, and you can see that the SD600 is sure to be a winner.



The SD600 in use in a typical mixer and r.f. amplifier stage

SURGE SUPPRESSORS

When incorporating triacs thyristors, or power transistors in high voltage circuits it is possible to allow a small safety margin in the voltage breakdown ratings to ensure that in normal circumstances there will be no catastrophic failures due to over-voltage.

Unfortunately normal circumstances do not always apply, and overvoltage conditions can occasionally occur due to lightning strikes, power grid surges and back e.m.f.s caused by the switching of inductive loads. Increasing the breakdown ratings of the semiconductors to cope with these freak occurrences is unfortunately no solution, since a drastic uprating of this sort will lead to much higher prices and a likely

decrease in switching performance.

The only practical protection which can be provided against transient overvoltages in high voltage equipment is the installation of surge suppressors of the voltage dependant resistor type, and an improved range of such devices has now been introduced by International-Rectifier.

The **Z10L**, **Z15L** and **Z21L** "Zenamic" series of devices are metal oxide varistors with a non linear current-voltage relationship so that they maintain an almost constant voltage across themselves over a very wide range of currents. That sounds a bit like a Zener, doesn't it, but the difference lies in the fact that although the average power dissipation of these transient suppressors is comparable to that of a Zener, the peak current handling capacity

extends to no less than 2,000 amps for the **Z21L**.

WIDE RANGE

The Zenamic devices are available for a wide range of voltages between 130 and 730 volts, and are housed in a two lead disc package of 13mm diameter (**Z10L**) 15mm diameter (**Z15L**) or 24mm diameter (**Z21L**).

To choose a device for a particular application one simply calculates the maximum steady state voltage applicable, and selects the voltage suppressor with the identical, or slightly higher, voltage rating. To protect, say, a thyristor, the Zenamic device is simply connected in parallel with it, so that any voltage spikes are safely absorbed without causing breakdown.

NEWS BRIEFS

A New Collection of Digital Watches

SLIMMER digital watches are on the way. Fairchild Camera and Instrument Corporation has entered the UK electronic watch market with two broad ranges of slim line digital watches. Less than 3/7th of an inch in thickness the Fairchild watches incorporate the latest ideas in miniaturised circuitry and use smaller batteries. Two lines will be marketed. An "up-market" range consisting of eleven men's and eight ladies models in either gold, stainless steel or chromium finishes. They will range in price from £43.95 to £97.50 and will be sold through fine jewellery stores. A low price range includes six men's and seven ladies' models priced from £19.95 to £32.95; these will be sold through retail outlets carrying similarly priced products.

Features of all these Fairchild watches are: single-button, five-function operation for hours, minutes, month, date and seconds; scratch resistant ruby coloured lenses; an attainable accuracy to within 60 seconds a year.

This California-based company will also be entering the UK consumer market with electronic clocks and television games, it has been announced.

Ministry of Defence Backs BS9000

FROM February 1 the Ministry of Defence introduced a new contracts clause requiring electronic components used in the design of MoD sponsored equipment to be approved within the BS9000 system. This unequivocal support for British Standards should ensure that BS9000 becomes the recognised authority for component quality and performance throughout the industry.

The BS9000 series was formulated by the British Standards Institution in 1967. The decision of MoD to make its use mandatory now is based on the fact that the range of components now included in BS9000 is sufficient to make the scheme practical for many requirements; plus the realisation that an accelerated expansion of the scheme is essential to keep pace with the rapid developments in electronics, and this is likely to be brought about most effectively by the full adoption of the scheme by a major and influential user

of components such as the MoD. The MoD also provides financial assistance towards the cost of obtaining qualification approval of components for defence projects.

This decision has the support of the BSI, and the British Electronics Industry, also of various US component manufacturers. It must enhance the prospect of BS9000 becoming a major part in any European and, ultimately, world wide scheme for component standardisation.

Fair Deal

A BOOKLET which summarises the current laws affecting every day trade and consumer transactions has just been published by the Retail Trading Standards Association.

Entitled "Honest, Fair and Legal", the booklet covers the rights of the shopper and where the retailer stands if he resists claims under the Sale of Goods Act 1893.

It covers law about descriptions of goods and services, selling methods and safety. Also, it refers to public authorities with which retailers will be mainly concerned, and the sanctions, prosecution and penalties which may be encountered.

The booklet concludes with the Association's advice on 14 rules for retailers, which could form the minimum basis for all voluntary codes of practice agreed with the Office of Fair Trading.

The booklet "Honest, Fair and Legal", price 75p, is available from the Retail Trading Standards Association, 360/366 Oxford Street, London, W1N 0BT.

IBA Handbook

THIS annual publication appears in its 14th edition with the new title "TV & radio 1976."

All facets of broadcasting undertaken by the Independent Broadcasting Authority come within the scope of this handbook. Programme matters receive much attention and the articles are well illustrated in black and white and colour. Facts are given about all the individual programme companies, ITV and ILR. Maps indicate normal service areas for each transmitter. ERP and aerial polarisation and physical details are given. There is advice on obtaining the best reception including stereo sound, and some peeps behind the engineering scenes. But perhaps the main appeal of this very attractively produced book will be in the programmes and the well-known personalities—whose pictures adorn many of the 224 pages.

TV & radio 1976 is available from newsagents and booksellers, price £1.30.

Next Month...

FREE

with every issue!




**A PIECE OF PRINTED
WIRING BOARD**

Plus these designs...

ADD-ON CAPACITANCE UNIT

Allows accurate measurement of capacitance from less than 1pF to greater than 30 μ F when used with any standard multimeter.

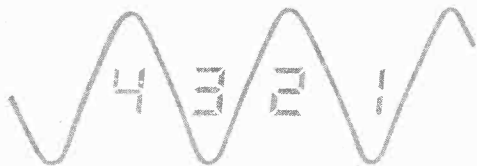As an added bonus this project can be built on the FREE Printed Wiring Board.



DIGITAL FREQUENCY METER


This design uses the latest integrated circuit technology to simplify construction.

Four frequency ranges covering 50kHz to 50MHz (extendable to 500MHz)—Resolution down to 10kHz at 50MHz—Variable input sensitivity—Simple calibration and maintenance.

AUDIO COMPASS

Originally developed as an aid to blind sailors, this unit can also provide an off-course alarm for use on self-steered yachts.

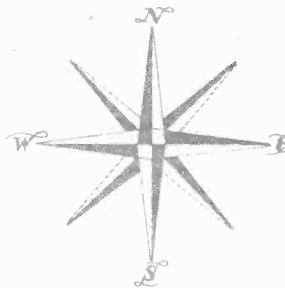The Audio Compass will prove invaluable for power craft and for night sailing since it allows ears to replace eyes when steering a compass course.



Our May Issue will be published on Friday, April 9, 1976

PRACTICAL ELECTRONICS

PLEASE NOTE:

It is in your interest to place a firm order with your newsagent—in advance. Back numbers are not available, so make sure of your copy now!


The Black Watch kit

£14.95!

★ **Practical**—easily built by anyone in an evening's straightforward assembly.

★ **Complete**—right down to strap and batteries.

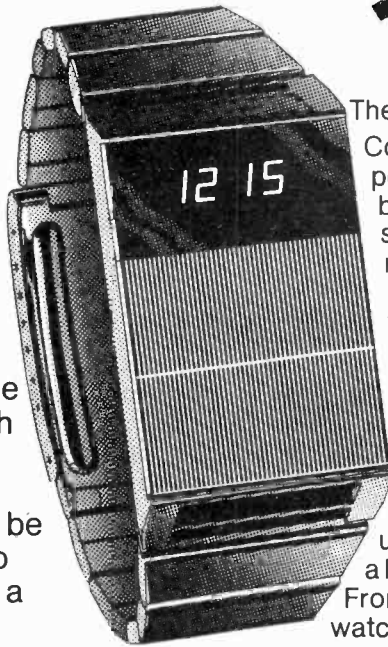★ **Guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day—but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.





The Black Watch by Sinclair is unique. Controlled by a quartz crystal, and powered by two hearing aid batteries, it uses bright red LEDs to show hours and minutes, and minutes and seconds. And it's styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.


The Black Watch kit is unique, too. It's rational — Sinclair have reduced the separate components to just four—and it's simple: anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.

Touch and tell

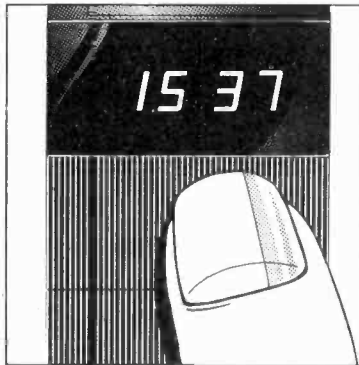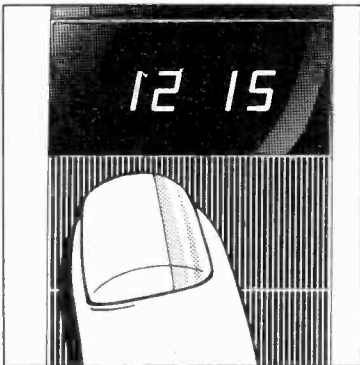Press here for hours and minutes... here for minutes and seconds.



Batteries easily replaced at home.

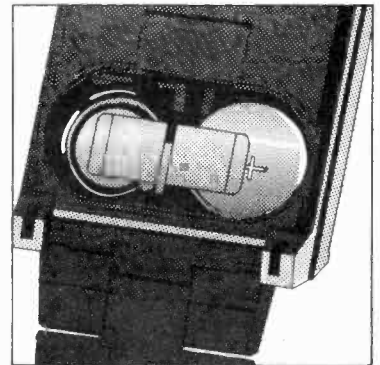

The specialist features of the Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra—see order form.)

Large, bright, red display—easily read at night. Touch-and-see case—no unprofessional buttons.

Runs on two hearing-aid batteries (supplied). Easily re-set using special button—no expensive jeweller's service.

The Black Watch—using the unique Sinclair-designed state-of-the-art IC.

The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology—integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate all circuitry for a digital watch on a single chip.

...and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

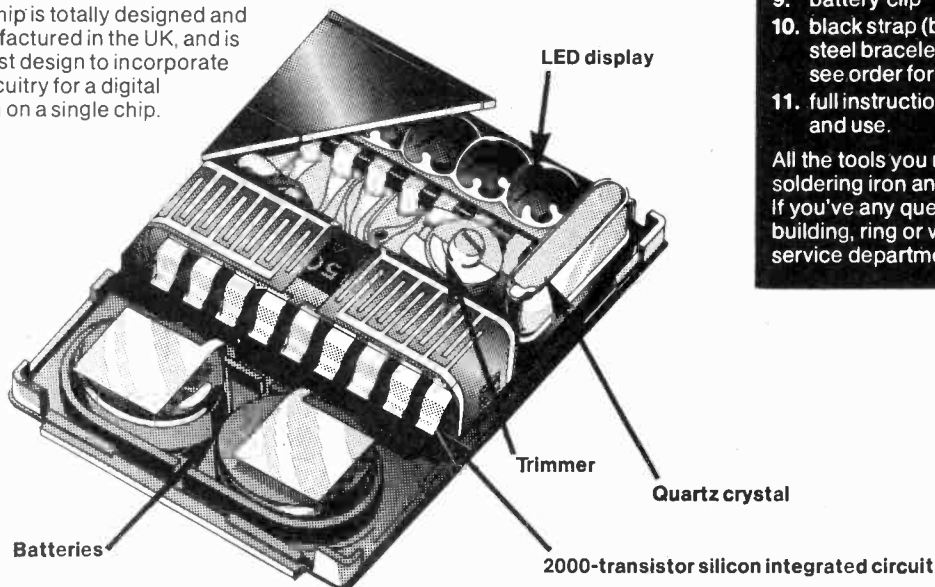

Complete kit £14.95!

The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra—see order form)
11. full instructions for building and use.

All the tools you need are a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to Sinclair service department for help.

Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit in original condition within 10 days and we'll refund your money without question. All parts are tested and checked before despatch—and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it—today!

Price in kit form: £14.95 (inc. black strap, VAT, p & p).

Price in built form: £24.95 (inc. black strap, VAT, p&p).

sinclair

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch kit(s) at £14.95 (inc. black strap, VAT, p&p).

* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.

..... (qty) Sinclair Black Watch(es) built at £24.95 (inc. black strap, VAT, p&p).

* Please debit my *Barclaycard/Access/ American Express account number

..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p).

Name (please print) _____

Address _____

Signature _____

PE/4

FREEPOST—no stamp required.

* Delete as required

SHOOT is a simple, inexpensive, electronic game of skill that tests the player's speed of reaction. Using TTL logic and a battery power supply it is small and self-contained, and an entertaining challenge to the player.

OBJECT OF THE GAME

The object of Shoot is, like a fairground rifle range, to shoot down a moving target, in this case a light moving along a row of l.e.d.s. The player "shoots" when he thinks the light is at the centre of the row. If he has "hit" the light it goes out but, unlike a rifle range, if he "misses" the light comes on and forms a second moving target, doubling the player's problem. This will happen each time he "shoots", and if the centre light is on at that instant it will go off, and if off it will turn on.

The speed at which the lights move along the row determines the degree of skill required to accurately "shoot" them down.

The player will soon find he can devise his own rules for the game and set himself problems. For example, he could progress from no lights travelling across to all nine lights full on in the minimum number of "shots". This ability for the player to determine his own rules makes Shoot an intriguing game to play.

Shoot is small and portable, simple to construct and is cheap at about £6. Operation is straightforward, consisting of only three controls. The game is quickly understood by a new player. The project also provides the chance to gain knowledge of working with TTL.

CIRCUIT DESCRIPTION

It can be seen, from the above description, that pushing the "shoot" button inverts the state of the centre l.e.d. The logic to achieve this consists of a nine-bit shift-register, its states indicated by l.e.d.s, with a conditional inverter between the fifth and sixth bits operated by the "shoot" button.

This conditional inverter is an EXCLUSIVE-OR gate. The truth table is shown below:

Inputs		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

If input B is a logic 0, then input A is the same as the output. However, if B is a logic 1, input A is inverted at the output. The conditional inverter forms the basis of Shoot.

The circuit diagram is shown in Fig. 1. IC1 and IC2 are 7496 five-bit serial-in parallel-out shift-registers. They are connected as a nine-bit shift-register, the nine l.e.d.s connected directly to the outputs via 270Ω current limiting resistors R2-10.

Between stage five and six there is an EXCLUSIVE-OR gate IC4a (a quarter of a 7486). In fact, the fifth stage l.e.d. (D5) is connected to the output of this gate. The output of the ninth bit of the shift-register is fed back into the serial input of the register so that the operation is cyclic. The other input of IC4a is connected to the "shoot" circuit.

Half a 7413 dual, four-input Schmitt NAND gate and C4, R11 and VR1 are connected in the usual Schmitt oscillator configuration, providing the clock pulses for the shift-register.

The output of IC3a is inverted by IC4b, a spare EXCLUSIVE-OR gate in the 7486 package, connected in its inverting mode by R12. IC3b, C5, C6, R12, R14, D10 and S1 form the "shoot" circuit.

CIRCUIT OPERATION


With S1 open, C5 and C6 charge via R13 and R14 to the Schmitt trigger level for the gates IC3. All other inputs are high (logic 1) so IC3a output goes low (logic 0) and starts the oscillator cycle. IC3b output then goes low. This is connected to IC4a which acts as a gated inverter and the shift-register cycles round clocked by IC3a oscillator. Light emitting diodes D1-9 give indication of states.

When S1 is closed C5 and C6 (via D10) discharge. Inputs to IC3a and IC3b go low causing their outputs to rise. IC3a can now no longer operate as an oscillator and because of the inverter IC4b, the

**Fun for all
the family...**

SHOOT!

By P. ADAMS

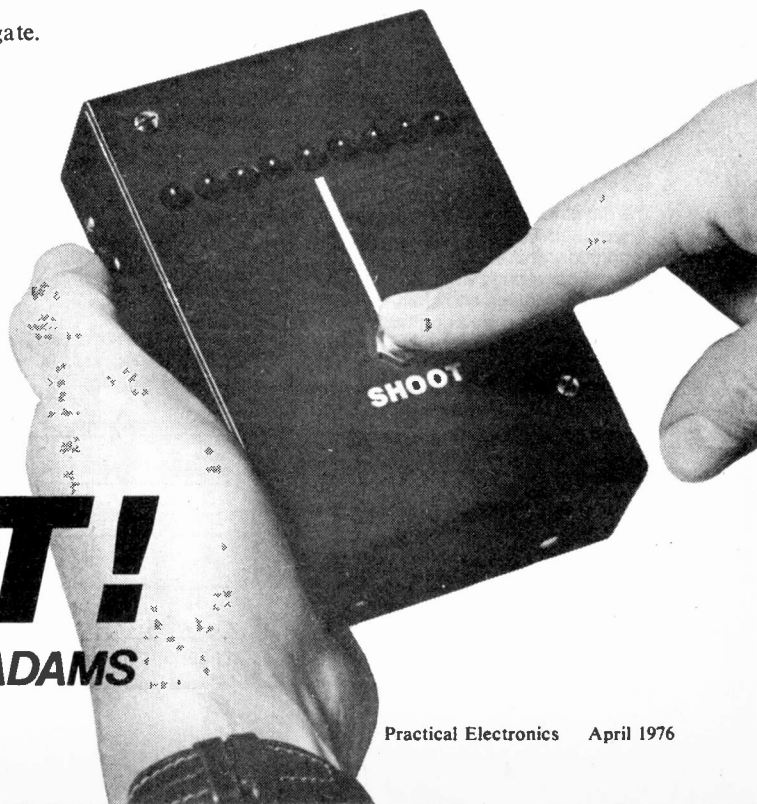


clock input to the register is held low. However, the input to IC4a is now high and it inverts the state of D5: if it was alight it goes out and vice versa. Meanwhile C4 charges to a logic 1 via R11 and VR1.

When S1 is released C5 and C6 charge. Because C6 is charged (via R14) from C5 the voltage across C6 lags that of C5. C5 reaches the Schmitt trigger level of IC3a and, all other inputs being high, its output goes low. The output of IC4b goes high and the register is stepped one state. (The 7496 changes state on the leading edge of the clock pulse.)

The inverted fifth state is thus moved to the sixth. IC3a is now again acting as an oscillator. The voltage of C6 now reaches Schmitt trigger level of IC3b whose output goes low. The conditional inverter IC4a returns to its non-inverting state before the next clock pulse and so the shift-register cycles as before until S1 is closed again.

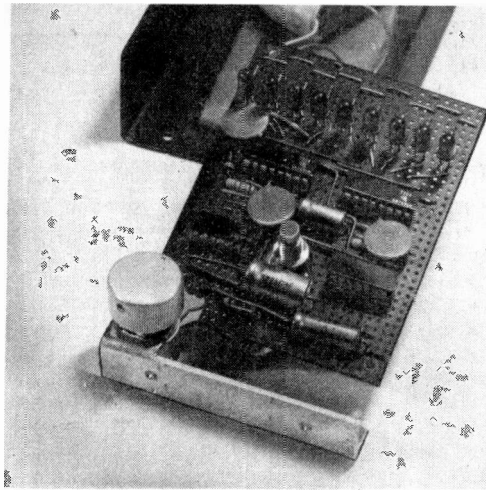Pushing the "shoot" button S1 stops the clock and inverts the state of the centre l.e.d. Releasing the button steps the register one state, returns the fifth l.e.d. to a non-inverted state and starts the clock. The fact that the lights stop moving when the button is depressed is very convenient to be able to study the pattern of the lights for the next "shoot".



COMPONENTS . . .

Resistors

R1	1k Ω
R2-R10	270 Ω (9 off)
R11	330 Ω
R12	2k Ω
R13	470 Ω
R14	330 Ω
R15	560 Ω
All	$\pm 5\%$ $\frac{1}{4}$ W carbon

Potentiometer

VR1	470 Ω (see text)
-----	-------------------------

Capacitors

C1-C3	0.1 μ F disc ceramic (3 off)
C4	100 μ F 6V elect.
C5	100 μ F 6V elect.
C6	10 μ F 6V elect.

Integrated Circuits

IC1, IC2	SN7496N (2 off)
IC3	SN7413N
IC4	SN7486N

Diodes

D1-D9	TIL209 or similar
D10	1N914
D11	50 p.i.v. 250mA silicon diode

Switches

S1	Miniature push to make
S2	Miniature slide switch

Miscellaneous

B1-B4	MN1500 1.5V (4 off)
Case	(see text), 0.1in matrix Veroboard 95 x 61mm (3.75 x 2.4in), battery clips, spacers, etc.

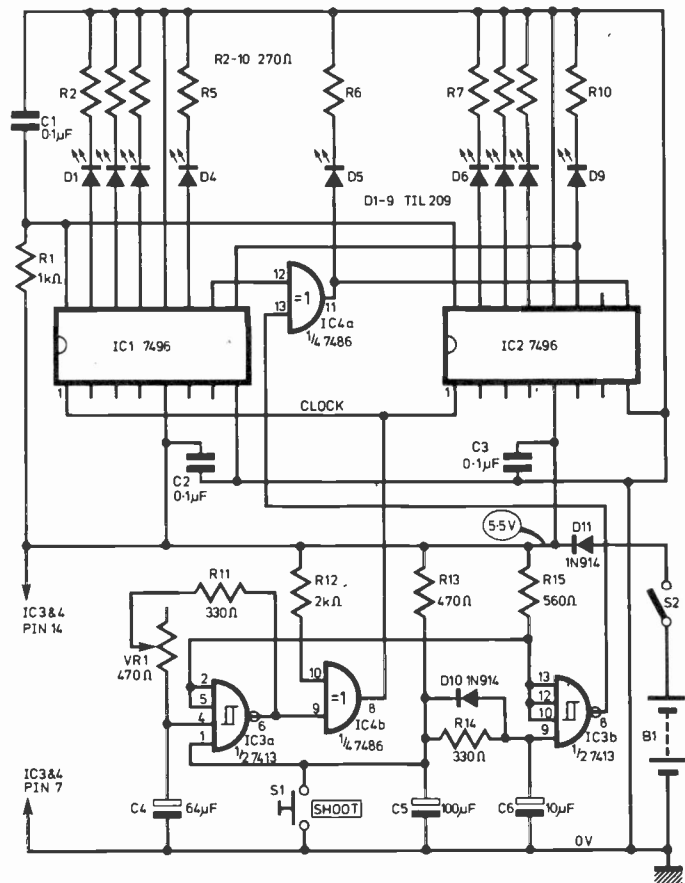


Fig. 1. Circuit diagram of the Shoot game


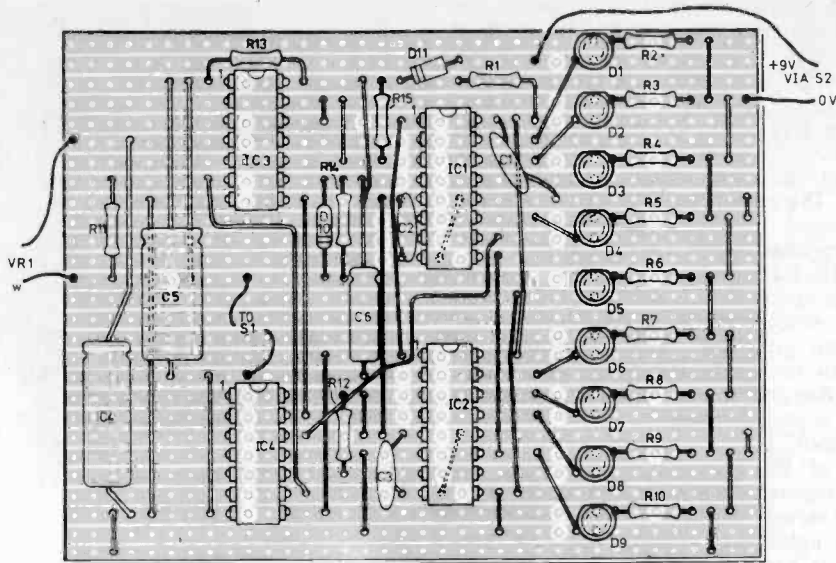


Fig. 2. Layout of the components and cuts on the Veroboard

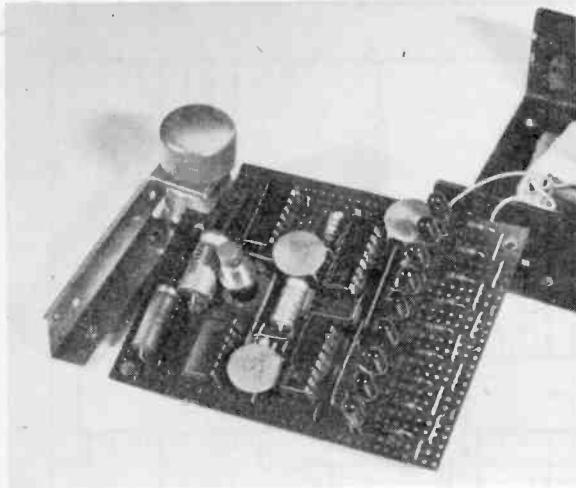

The completed Shoot game

On switching the power on (S2), R1 and C1 clear the shift registers. This provides a useful method of returning to the "all off" state. C2 and C3 suppress switching transients on the power supply rail which could upset the operation of the logic. VR1 varies the frequency of the clock and hence the rate at which the lights appear to travel. D11 limits power supply to 5.5 volts because of the diode voltage drop. Also it ensures against wrong polarity connection.

CONSTRUCTION

The circuit is constructed on Veroboard. The layout is shown in Fig. 2.

The game was housed in a plastic case 4in × 3in × 1½in, but any instrument case will do providing it is no smaller.


To leave the front panel clear of controls except for the "shoot" button it was decided to make VR1 an edge control. This was done by gluing an edge

control knob from an old transistor radio to a skeleton preset. There is no reason why an ordinary potentiometer could not be used. The batteries can either be held in holders or soldered together.

Components are not critical except C2 and C3 which must be disc ceramics. C4 gives a satisfactory range of speed for the display, but if the game proves too easy, reducing its value will increase the speed further. It was found that a switch with a heavy or long-travel action was best for S1. Alkaline Manganese batteries were used because of their higher power and longer life compared to dry batteries. However, HP7s could be used.

CONCLUSIONS


Shoot is an interesting project to construct and most compelling to play. The prototype has been in existence for some time and all who have played with it were most impressed and absorbed. Developments to the circuit such as a scoring system or firing delays, could easily be made but the added complexity would mean the game was no longer portable which was one of the major factors in the design of Shoot. ★

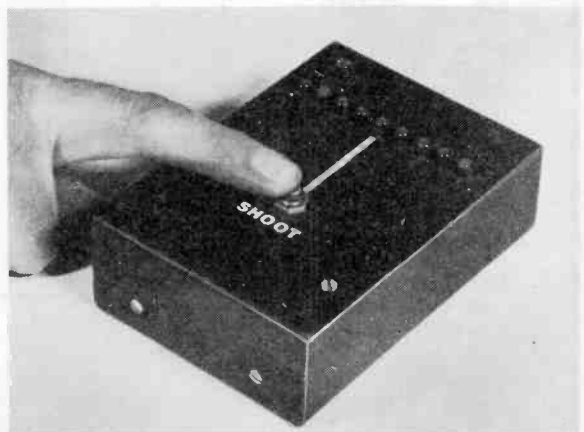

SOUND DESIGN

A PRACTICAL ELECTRONICS PUBLICATION

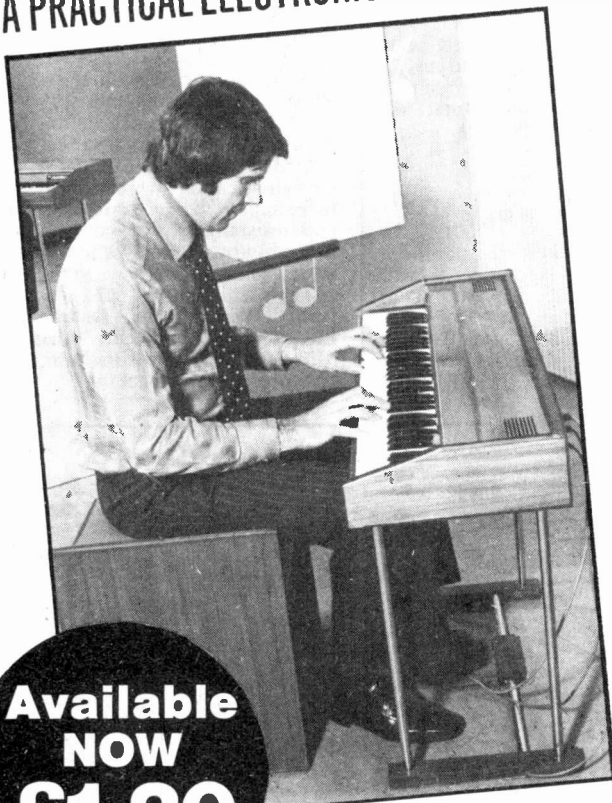A SPECIAL SELECTION OF MUSICAL PROJECTS FROM PE



Available
NOW
£1.20

by post only

(Please allow at least 2 weeks for delivery)

If you do not wish to mutilate your copy of the magazine, please send your order on a separate sheet.

THE JOANNA ELECTRONIC PIANO

has realistic piano effect with touch-sensitive keyboard and additional choice of harpsichord or honky-tonk voicing.

THE ORION STEREO AMPLIFIER

A hi-fi amplifier with output of over 20+20 watts. Compact and complete in one unit, it measures only 14" x 6" x 2".

THE MINISONIC MK2 SOUND SYNTHESISER

An up-dated version of the published Mk 1, the Mk 2 has an integral keyboard, two 250 mW monitoring channels and loudspeakers, and facilities for amplitude, frequency and harmonic modulation.

PLUS Some great sound effects units for guitars, keyboard instruments and general recording.

To: Practical Electronics (Sound Design),
IPC Magazines Ltd., Fleetway House,
Farrington Street, London EC4A 4AD.

Please send mecopy(ies)
of "Sound Design". I enclose a Postal
Order/Cheque for £1.20 (£1 + 20p post.
& pack.) or (state amount for more than

one copy
(p&p 35p for 2 copies).

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

PLEASE WRITE IN BLOCK LETTERS

Name

Address

..... Post code.....

Company registered in England. Regd. No. 53526. A subsidiary of Reed International Limited

CALCULATOR

Combining the most popular functions of a handheld memory calculator and a basic slide rule calculator, **Texas Instruments** have introduced the TI-2550-II 8-function calculator.

The new calculator features the basic five functions (add, subtract, multiply, divide and percent) with an automatic constant on all five functions plus a full four-key memory: memory plus, memory minus, memory recall and clear memory. In addition, it features the widely used slide rule calculator functions of square root, square and reciprocal.

The reverse key is especially useful to divide the quantity in the memory by the quantity in the display. The square root, square and reciprocal keys operate only on the displayed quantity; they do not complete any pending operation. Thus, it can easily solve problems such as the square root of the sum of squares without using the memory.

Used for the first time in a Texas calculator is a bright green vacuum-fluorescent display with large 0.2 inch-high digits.

For maximum readability, the negative sign is always displayed immediately to the left of the first displayed digit. A ninth character on the extreme left of the display is used to indicate a quantity stored in the memory and as an error and overflow indication.

The calculator can be set to operate in full floating operation or to round off the answer to two places after the decimal point.

Weighing less than 8oz (230g), the TI-2550-II comes with the BP-2 battery pack containing two fast-charge nickel cadmium cells, the AC9900 adapter/charger and an owner/users manual. The recommended retail price for the TI-2550-II is £29.95 including VAT and accessories.

Addresses of nearest stockists can be obtained from **Texas Instruments Ltd.**, 165 Bath Road, Slough SL1 4AD.

POWER AMPLIFIER

For the power enthusiasts **Bi-Pak Semiconductors** are now marketing the AL250 125W power amplifier module.

Capable of delivering 125W r.m.s. into 4 ohm loads, the module has a sensitivity of 450mV and a frequency response extending from 25Hz to 20kHz. Distortion levels are typically below 0.1 per cent and damage resulting from incorrect or short-circuit loads is prevented by a four transistor protection circuit.

Intended for use in applications such as disco units, p.a. systems and

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

background music players, the AL250 costs £15.95 plus VAT. The module is fully guaranteed and comes complete with instructions.

Further details can be obtained from **Bi-Pak Semiconductors**, 63 High Street, Ware, Herts.

STABILISED SUPPLY

The new low voltage stabilised power supply kit from **RCS** will give up to 100mA d.c. output at various voltages.

Operated from 200 to 240V a.c. mains input the stabilised output voltages available are 6V, 7½V, 9V

and 12V. The circuit is of the parallel Zener diode type, the output voltage is governed by the value of the Zener diode and the current is limited by the value of a resistor.

The kits are supplied for one output voltage and current as requested by the purchaser. All parts are available separately and a complete kit costs £2.95 including VAT; postage is 45p.

Further information and kits are available from **Radio Component Specialists**, 337 Whitehorse Road, West Croydon, Surrey.

RESISTOR CALCULATOR


To compliment their very large range of carbon film, wirewound and vitreous wirewound resistors, **West Hyde Developments** have designed and are marketing a 5in plastic resistor calculator.

One side of the calculator has a swinging cursor which enables you to calculate power, current, voltage and resistance (any two known and two unknown). The other side contains the slide rule.


The calculators are available from **West Hyde Developments Ltd.**, Ryefield Crescent, Northwood, Middlesex, price 61p including VAT and postage and packing.




Texas TI-2550-II 8-function calculator

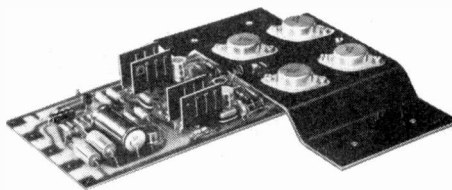

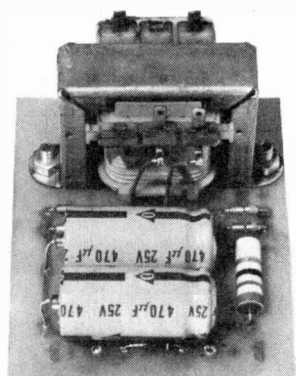The 125W power amplifier module from Bi-Pak Semiconductors



Stabilised supply from RCS

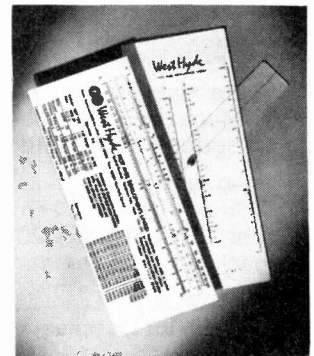

Resistor/Slide Rule calculator from West Hyde

Strictly

Instrumental
by K. Lenton-Smith

LATE last year, a horde of organ-building enthusiasts descended on the Hammond (U.K.) Sonorous Works at Edgware one Saturday afternoon—looking for bargains. The occasion was a sale of surplus circuit boards and spares due to certain models becoming obsolete. Keyboards, pedalboards, transistor generators and drum units were among the many items offered: as I was there (and did not come away empty-handed!), I can report that the trade was brisk.

Hammond (U.K.) have never manufactured organs as such, but have simply put together kits of parts made in America. Escalating costs are such that it is now cheaper to import complete organs from other parts of the Hammond organisation, so Bob Grant, their Sales Manager, tells me.

More expensive organs will still come from the U.S., whilst Japan will cater for the lower end of the market. Sadly, this makes economic sense.

Any Hammondophile who heard of this sale may therefore be assured that his favourite organ is still in the forefront.

SIDEMAN

Twenty years ago, the rhythm unit was not as commonplace as it is today. The Wurlitzer "Sideman" was typical then: completely valve-operated, its rhythm patterns were derived from a disc carrying concentric circles of contacts wiped by multiple pick-up brushes and motor-driven.

The voice circuits were much the same as they are today, but the whole unit was massive due to both the mechanical parts and the heavy engineering associated with valve equipment. Transistors and i.c.s subsequently reduced both size and weight, quite apart from the modern tendency to provide only a pre-amplified output.

Present prices are very different and today's version is at least portable, but there are still a few problems to contend with.

Given the choice between an electronic drummer and the real thing,

most musicians would prefer the latter. His main advantage lies in the fact that he can vary his rhythms, he can remain tacit for a bar or two, play *ppp* or *fff* as the case may be and even react to a raised eyebrow—rapport with his colleagues perhaps?

However, even the best drummers are occasionally guilty of slowly speeding up tempo and the worst of them can get off the beat! This is the one area where the electronic version scores, the oscillator supplying the counting/logic system will give a *strictly* measured beat, ad nauseam.

Monotony is the main criticism levelled at the Rhythm Unit, so Hammond have come up with a (partial) solution.

Their latest unit features the usual rhythms but, by means of four extra buttons A, B, C and D, alternatives to each rhythm are obtained. This means that there are four variables for each rhythm, i.e. four Waltzes, four Bossa Novas, etc. In addition, the unit may be programmed to scan across these alternatives automatically, making the changes at pre-determined intervals of half a bar, one, two, four, eight or 16 bars.

Short of using a recording of a live drummer as an accompaniment, this Hammond idea is about the best advance one could hope for in an electronic drum unit.

CLEAN FINGERING

The "Solovox" type of monophonic keyboard is long dead, but pianists who used these found that they had to devise a playing technique to suit its circuitry. The tone generator was an R-C multivibrator, usually a glowing 6SN7, and the playing keys effectively varied a resistive or capacitive value applied to the valve.

Though the player knew that you couldn't play a chord on a monophonic instrument, there was always a tendency to do so out of sheer habit. Normally there was no harm in this as, however many notes were keyed, only the top one affected the generator.

The same problems apply to the average Synthesiser with an added

complication. We still key into a chain of resistors, but they are now used as a divider to provide *voltages* rather than a single resistive value. The forgetful pianist who inadvertently plays a "chord" will produce an odd result because a number of resistors will be shorted out of the chain, causing the VCO to produce Eastern scales and upsetting the loading of the voltage sources.

Slurs from one note to another, though feasible on organ or piano, will not work very successfully for the same reason, even the *acciaccatura* will prove difficult. A nuisance? Not really, as anything that makes for better keyboard discipline can't be bad.

Although a strong *portamento* might help to disguise the problem, many listeners will object to the "cure". Let's just say that your VCO and Hold will love you for realising that clean fingering helps them enormously!

IN TUNE

The Synthesiser is a versatile device, but this column is concerned solely with its musical capabilities. Re-recording demands accurate tuning of VCOs and, even if an oven is incorporated in the circuitry, it is usually necessary to resort to tuning-checks from time to time. A piano, or other frequency reference, may not be always available: even if it is, there is a tendency to wear a track in the carpet!

It seems to me to be a good plan to incorporate a switched oscillator in the synthesiser, tuned to 440Hz for preference, to save both patience and shoe leather. On the natural assumption that the recording apparatus runs at a constant speed, the tuning of each track laid down can be closely controlled.

This arrangement will be found invaluable where the whole keyboard can be octave-shifted for recording the extreme ends of the frequency range. A 741 op. amp. can be made to produce a good sine wave, or a Hartley oscillator could be designed round a miniature driver transformer (such as Eagle type LT44).

BOOKNOTE

Some organ-builders prefer frills to good organ tones. Two highly experienced designers who believe that musical specification comes first are my colleagues Alan Douglas and Sid Astley.

The latest edition of "Transistor Electronic Organs for the Amateur", should prove invaluable to any reader contemplating, or engaged in, building his own instrument.

INGENUITY UNLIMITED

A selection of readers suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

Please Note

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

in the off position. This is performed by TR5. Its presence is essential as it would be impractical to modify the existing direction switch to a 2-pole 3-way type which would normally be used in such a case.

When S1 is moved either way from the off position, C3 is charged via D1 and TR5 is held on via R7. This activates the astable. The time constant C3/R7 is made to be large enough to allow TR5 to be held on whilst TR4 is on. TR4 is prevented from discharging C3 by the action of D1.

As soon as S1 is moved to the off position the bulbs stop flashing and after a short while C3's charge is insufficient to hold TR5 in a conducting state resulting in the bistable being switched off.

Chow Yow Soon,
Malaysia.

ELECTRONIC FLASHER

THE circuit shown in Fig. 1 is an electronic alternative to the conventional electro-mechanical flasher found in most vehicles. Some advantages of the electronic unit are an improvement in efficiency, adjustable flashing rate, and less dependence of the flashing rate on battery voltage.

TR1 and TR2 form an astable whose oscillation rate is just over 1Hz. (This can be adjusted by altering R2 and R3.) TR3 and TR4 act as a switch which is either on or off depending on the state of TR2.

A second switch is used to turn off the supply to the flasher unit when the direction indicator S1 is

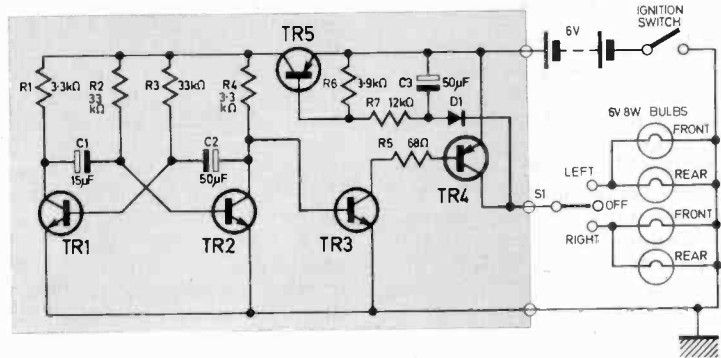


Fig. 1

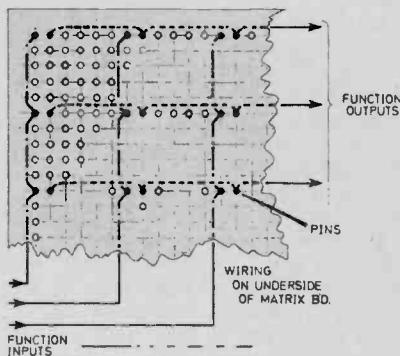


Fig. 1

ALTERNATIVE PATCH BOARD

THIS idea provides a cheap and workable alternative to a usually rather expensive piece of hardware—the patch board.

To make the patch board, pairs of Veropins are inserted into adjacent holes in a rectangular array of about 0.5in separation, on a piece of 0.1in matrix board. The pins are then wired up as in Fig. 1. Patching is then effected by clipping together the appropriate pair of pins in the array with a miniature insulated single crocodile clip. This gives a quickly changeable patching arrangement and at a fraction of the cost of commercial patch boards.

E. Swalski,
Leeds.

HERE is a design of a simple transistor tester which might be useful for many of your readers.

With this tester you can check transistors and see if they are in working order and measure h_{FE} .

By varying VR1 you change the current to the base from 0 to approximately $90\mu A$. Resistor R2 limits the current to the collector to about 12mA.

If you divide the reading on ME2 by the reading on ME1 you can determine the h_{FE} .

If using a multimeter as ME2 you can also measure the leakage current if you switch it to a more sensitive range.

By switching S1 you can measure both *ppn* and *npn* transistors.

Dan Warkander,
Helsingborg,
Sweden.

TRANSISTOR TESTER

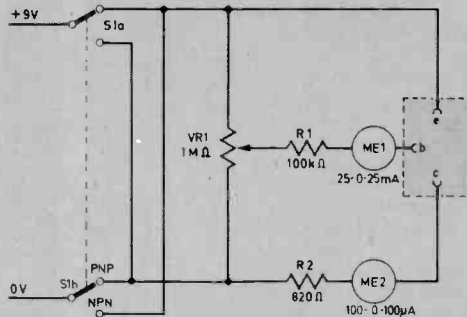


Fig. 1

CAR BATTERY CONDITION INDICATOR

THE voltage of a car battery under running conditions can tell the driver a lot about the condition of the dynamo, voltage regulator, and the battery itself. Meters to indicate battery condition are expensive but the circuit to be described performs the same function at a fraction of the cost. Typically, these meters are calibrated in sections marked "poor", "fair" and "good", and this unit utilises different coloured l.e.d.s to give the same information. This is enough to indicate a major fault, a less serious malfunction that requires checking or that the battery and electrical system are in good condition. A red l.e.d. lit denotes a battery voltage of less than 11.6V approximately, a yellow l.e.d. indicates 11.6 to 12.6V, and a green l.e.d. shows 12.6V or more.

Referring to Fig. 1, if the battery voltage is below about 11.6V, both transistors are turned off, and only the red l.e.d. is lit. If the voltage is between 11.6 and 12.6V, D3 conducts via R2, transistor TR1 turns on, the yellow D4 l.e.d. is lit and diodes D2 shunts D1, turning it off. Similarly for voltages above 12.6V, D6 conducts via R4, turning on TR2 which lights the green l.e.d. Diode D5 shunts TR1 and D4 turning off D4 and thus D1.

Construction is not critical, Veroboard or printed circuit techniques can be used remembering to mount the l.e.d.s at suitable spacings first, then group the other components around them.

The only testing needed is to connect the unit to a variable power supply, or to a potentiometer across a fixed supply. As the voltage is increased from zero first the red l.e.d. will turn on then at about 11.6V the red l.e.d. extinguishes and

the yellow comes on, whilst at 12.6V the yellow will go out and the green comes on.

The voltages at which the different l.e.d.s switch in and out can be easily varied for different applications by changing the values of D3 and D6. These can be "trimmed" to 0.6V limits by using an ordinary silicon diode in series with the Zener, but reversed in polarity with respect to the Zener, which will add about 0.6V to the Zener voltage.

The l.e.d.s can be increased in brightness by reducing the 470 ohm resistors to 390 or 330 ohms depending on the current capability of the l.e.d. used, not forgetting the ratings of TR1 and TR2.

The completed unit at the high voltage range consumes about 80mA, which is negligible from a car battery, but will prevent its use in battery portable equipment. The circuit has many other uses, however, where the current consumption is not critical, as a maximum detector for tuning applications, e.g. with multiple transistor stages incorporating smaller ranges at the maximum end. Also at a switch over point it is possible to have two

l.e.d.s half lit, which makes it a useful voltage indicator where the expense of a meter is not justified or extreme accuracy unnecessary.

The completed board can be built into a small plastic box for mounting on the car dashboard in a suitable position (some sort of cowling may prove necessary if daylight is too strong), or with care it should be possible to insert the l.e.d.s from behind the dashboard into a composite instrument panel incorporating a cowling. The only wiring necessary is positive and negative lines, one to a switched terminal on the ignition, and the other to chassis, appropriate polarities being observed.

If the red light remains permanently on, the battery voltage regulator or dynamo or any combination of these is faulty. The yellow l.e.d. warns of a fairly low battery voltage, which warrants investigation if it has not changed to green after a few miles driving. The green light indicates that the electrical system is functioning satisfactorily.

M. J. Larner.

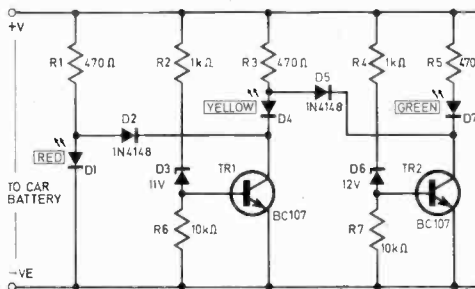


Fig. 1

ELECTRONIC DICE

THE circuit uses 74 TTL logic and component values are in no way critical. It consists of a counter with a cycle length of six driving an l.e.d. display via a decoder. This is arranged so as to illuminate the l.e.d.s as they would appear on the face of a dice displaying that number.

When S1 is depressed the bistable switches over (this is included to eliminate problems caused by contact bounce) and the output of IC1a goes high, driving the JK inputs of IC3a high, allowing the clock pulses from the multivibrator to toggle through and start the counter counting. Depressing S1 also removes the bias of TR1 cutting it off and this blanks the l.e.d. display.

When S1 is released the JK inputs of IC3a go low, holding the Q output fixed, thus stopping the counter. TR1 is also switched on, allowing the l.e.d. display to come on displaying whatever is in the counter.

M. M. Malek.
Sutton, Surrey.

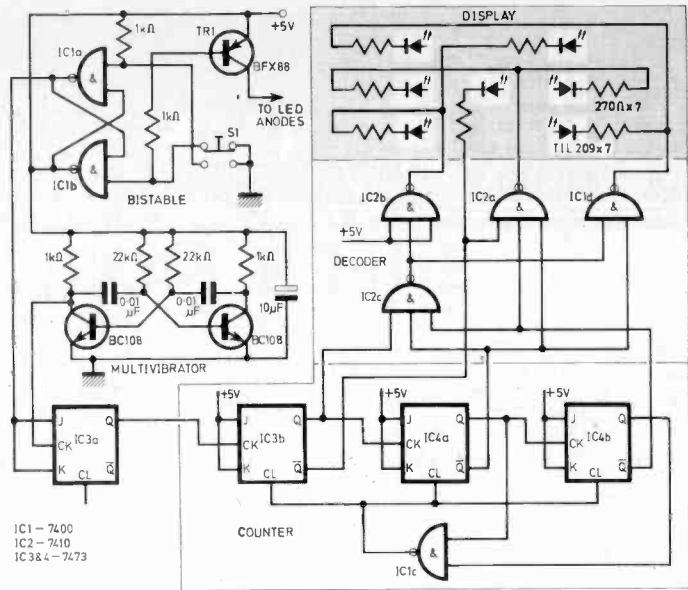


Fig. 1

FREQUENCY CHANGER FOR SYNTHESISERS

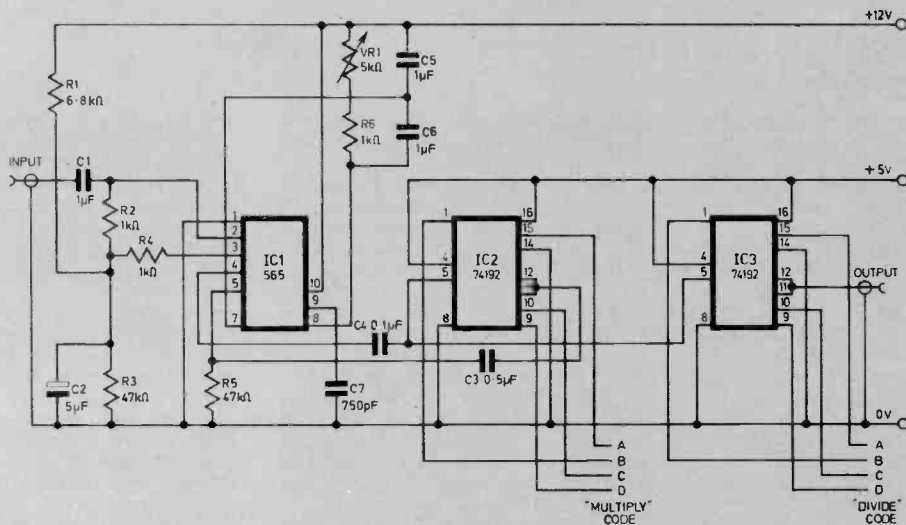


Fig. 1

THE circuit shown in Fig. 1 is a frequency changer which can be used with instruments such as synthesisers. A 565 phase-locked loop is used with a 74192 digital up-down counter which sets the multiplying value. A second 74192 then

divides it to give the final output. The multiplication and division are set by digital codes on the respective multiply or divide inputs to the unit. These inputs are set to 10N where N is the desired frequency multiplication/division. A


b.c.d. thumbwheel switch could be used here for fixed codes or a memory arrangement for controlled sequences.

B. Hatton.
Waltham Cross





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

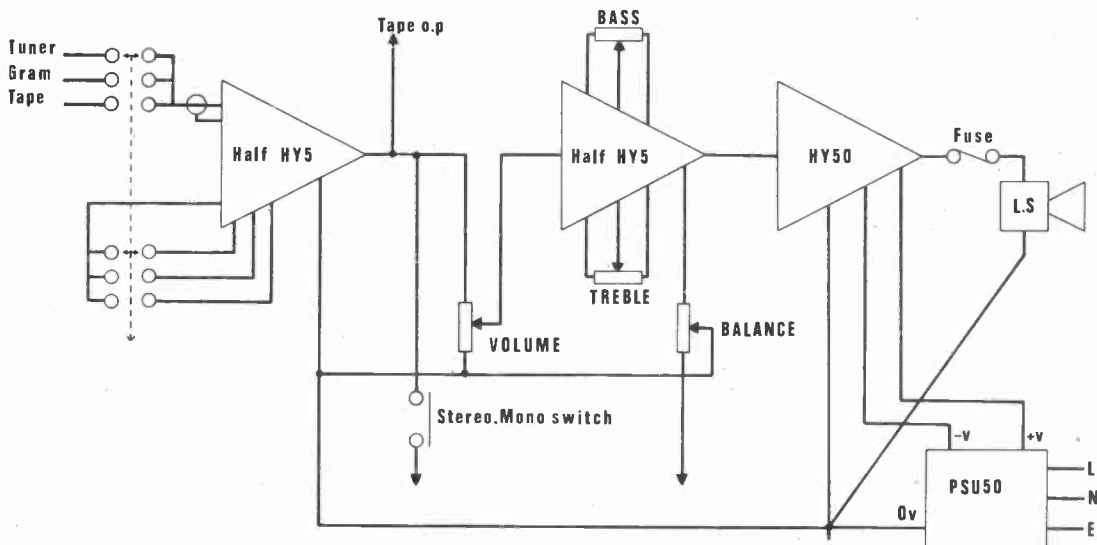

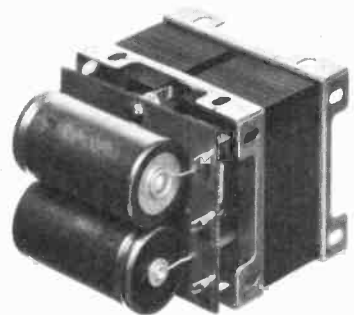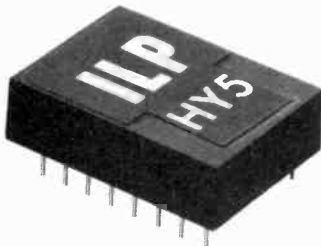MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA, Ceramic Pick-up 30mV, Microphone 10mV, Tuner 100mV, Auxiliary 3-100mV, Input Impedance 47kΩ at 1kHz. Outputs: Tape 100mV, Main output 0db (0.775V RMS). Active Tone Controls: Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: ± 16-25V.

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8Ω. Load Impedance: 4-16Ω. Input Sensitivity: 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 × 50 × 25mm.

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: ± 25V. Input voltage: 210-240V. Size: L.70, D.90, H.60mm.

PRICE £4.75

+£1.19 VAT
P. & P. free

PRICE £6.20

+£1.55 VAT
P. & P. free

PRICE £6.25

+£1.56 VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.

Crossland House,
Nacklington, Canterbury,
Kent CT4 7AD.
5 Dane John, Canterbury,
Kent

Tel. (0227) 63218

Regd. Office No. 1032630

Please Supply

Total Purchase Price

I Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

constructors guides

This exciting new series, under the general Editorship of **Morris COLWELL**, provides clear and easily understood descriptions, advice and general help for amateur constructors, students and technicians aimed at breaking down the barriers that often deter beginners in electronics.

Available Now...

ELECTRONIC DIAGRAMS

M. A. Colwell

One of the first things that newcomers to radio and electronics need to come to terms with is the language used. This book, which is aimed primarily at beginners, attempts to break down the barriers which so often deter students from taking up the subject. It takes the reader through the logical steps of building up circuit diagrams from elementary circuit symbols to complex systems.

112 pages 216 x 138mm Illustrated
0 408 00201 8 £1.80

PRINTED CIRCUIT ASSEMBLY

M. J. Hughes, MA, AMIERE and M. A. Colwell

This book takes the mystery out of techniques used in printed circuit assembly and encourages constructors to make their own printed circuit boards. The book describes the characteristics of the various bases used and guides the reader through the stages of translating circuit diagrams into printed circuit layouts.

96 pages 216 x 138mm Illustrated
0 408 00203 4 £1.80

ELECTRONIC COMPONENTS

M. A. Colwell

This Guide describes the characteristics of the various bases used in printed circuit systems and guides the reader through the stages of translating circuit diagrams into printed circuit layouts. Image transference, etching, milling and trimming methods are described. Some special techniques such as through-hole plating,

edge connector tabs and multi-layer assembly are also outlined, and reliability and maintenance procedures are discussed. The merits of alternative ready-made proprietary assembly systems are reviewed and tabular comparisons made.

112 pages 216 x 138mm Illustrated
0 408 00202 6 £1.80

Available June...

PROJECT PLANNING AND BUILDING

Morris A. Colwell

This guide will help the constructor to plan, design and lay out his electronic projects. The book explains planning, use of tools, component board layout, the design and layout of chassis and cases, and assembly and wiring. There is also an extremely useful Appendix.

SIMPLE CIRCUIT BUILDING

Morris A. Colwell

This Guide provides a logical introduction to general purpose circuits for the home constructor and to converting theoretical circuits into practical layouts. The book covers a wide range of easy to assemble circuits, including switching and logic circuits and their layouts, operational amplifiers, a.c. amplifiers and d.c. power supplies.

PRACTICAL ELECTRONIC PROJECT BUILDING

Alan Ainslie and Morris A. Colwell

A concise but informative guide to some of the current popular methods of construction and techniques employed in home construction. Contains hints on finishing and fault-finding methods.

For details of all Newnes Technical Books please write for a free catalogue and watch for announcements in following issues of Practical Electronics.



Newnes Technical Books



BOROUGH GREEN, SEVENOAKS, KENT TN15 8PH

RELAY OPERATION BY SHORT PULSE

FIG. 1 shows a relay RLA connected to a 12 volt power supply. When the switch S1 is momentarily closed the relay operates and locks through contact RLA1. The relay operating voltage was 8 volts and the time S1 had to be held closed for the relay to lock was 68ms. This length of time was far too long for the required application and therefore the circuit in Fig. 2 was developed to allow the relay to be triggered by a shorter pulse.

TR1 is connected as an emitter follower. In this circuit when S1

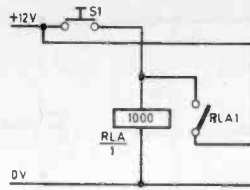


Fig. 1

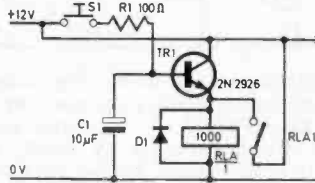


Fig. 2

operates C1 charges through R1 and the time constant is $C1R1$, in this case making about 1ms. Thus the holding voltage of the relay is reached within about 2ms. Once charged the capacitor will discharge at a rate determined by the h_{FE} of the transistor TR1. The impedance C1 "sees" looking into the base of TR1 is $h_{FE} \times$ relay resistance, i.e. in this case, assuming an h_{FE} for the transistor of 28, 28k Ω . The discharge time constant will therefore be $C1 \times 28,000$. Inclusion of the transistor has thus not only reduced the operating time of the arrangement but also the effective hold time.

R. Parfitt,
Croydon

ECONOMY DECODER FOR BCD TO 7-SEGMENT DISPLAY

FOR experimental purposes, two 7400 i.c.s can be used to decode from BCD to 7-segment display format. Whilst decoders are available in single packages they are considerably more expensive than the displays which they drive. The 7400 is the cheapest i.c. in the range and the one most commonly found on ex-computer panels.

The circuit in Fig. 1 was developed for the DL704 or MAN4 common cathode type of i.e.d. display. Pull up resistors are connected in the usual way between each segment anode and the positive rail. Current through these resistors is taken via diodes and sunk by gates which are at logic 0 thus extinguishing appropriate segments. A gate is at logic 0 when any one of the decimal numbers shown against the gate is being decoded.

The maximum sink capability of a 7400 gate output is 16mA. To allow for the heavier loading conditions at Gates 3 and 7 each segment drive is limited to 5mA by using a minimum resistor value of 820 ohms. Segment drive could be increased to 10mA by connecting the inputs and outputs of a further gate in parallel with Gate 3 and another across Gate 7. All pull up resistors could then be lowered to 390 ohms.

The diodes used without problem in the prototype were unmarked miniature silicon from a cheap pack of untested diodes but germanium diodes are preferable.

Unlike standard decoders this circuit does not decode non-decimal

states and the numbers 6 and 9 are slightly more stylised with an additional top and bottom bar respectively. A further package is required when the complementary BCD outputs are not available. This problem

does not arise if decade counters are built from flip-flops which are again readily available on ex-computer panels.

R. J. Shute,
Bracknell.

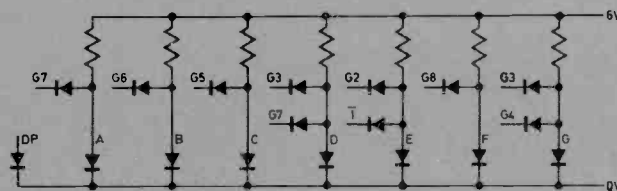
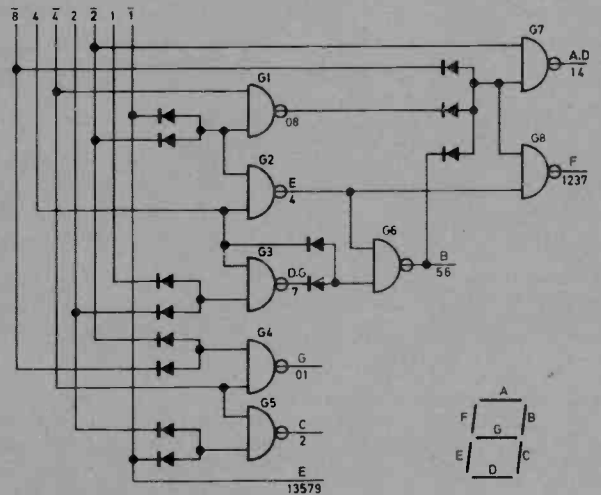



Fig. 1

ALTERNATIVE TUNING INDICATOR FOR VARICAP TUNER

Fig. 1

It was decided to build a tuning indicator to Mr Beeching's design (P.E. Ingenuity Unlimited, Oct. 1974) but unfortunately it proved impossible to obtain the MC1335P—Motorola having ceased production of the device early in 1973.

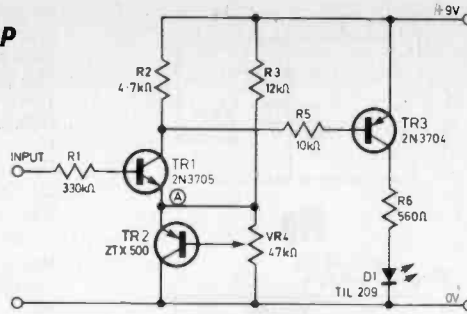An alternative discrete design was therefore embarked on, the initial



requirements remaining the same: (a) minimum loading on the output of the LP1185; (b) the extra current drawn from the 9V supply to be relatively small; (c) the indicator not to function on inter-station noise.

The circuit shown in Fig. 1 was eventually evolved and found to


satisfy all these requirements. Without a d.c. voltage applied to the input, TR1 and TR3 are non-conducting and consequently the l.e.d. does not light. The current from the 9V rail is about 4.5mA and flows through R3, R4 and TR2 in parallel. The potentiometer VR4 and TR2 form a V_{be} multiplier allowing a low impedance variable voltage to be set at point A to meet requirement (c).

When a voltage is applied to the input in excess of that at point A plus 0.65V, TR1 conducts causing TR3 also to conduct and the l.e.d. to turn on. The loading of the output of the LP1185 is minimised by the low base current of TR1 (1.2μA) and requirement (a) is met admirably.

B. W. H. Jesse,
Onpington.

CAR THEFT ALARM

Fig. 1

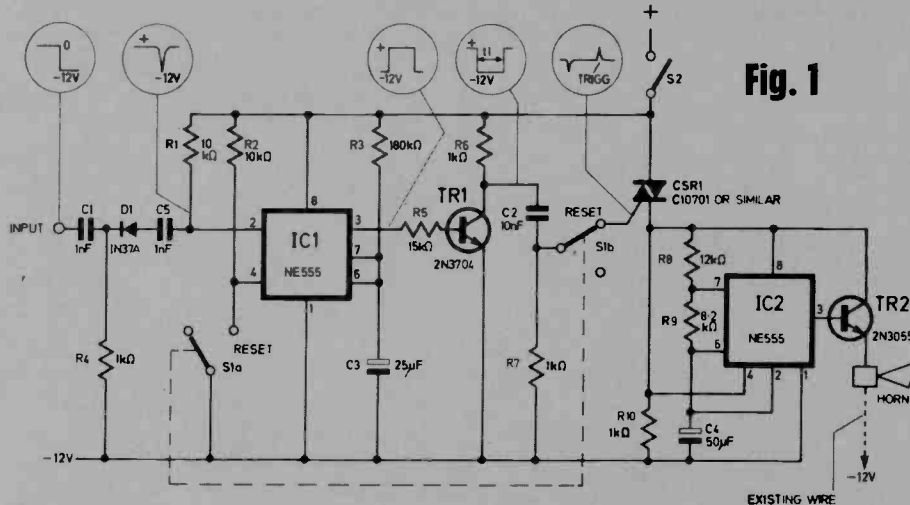

The alarm circuit shown in Fig. 1 produces an audible warning (pulsating bleeps on the car's horn) if an intruder opens one of the car doors.

The alarm uses the courtesy light switch to detect the opening of a door and this is used to trigger a delay circuit which, if the alarm is not reset, causes the horn bleeping routine to begin.

The negative going transient appearing across the bulb is differentiated and used to trigger a 555 timer in the monostable mode. The output of the 555 is inverted and differentiated once again to provide a firing pulse for the thyristor CSR1. When on this powers a further 555 operating in the astable mode, and the output of this stage is used to pulse the horn via a 2N3055.

When the circuit is initially switched on it must be reset immediately as the timer will have commenced an initial timing cycle.

An alternative, slightly simpler version may be constructed leaving out the delay timer and taking the input directly to TR1. The delay is a useful asset, however, as it allows sufficient time for one to reach the

reset switch before the horn sounds.

The circuit can be used on negative cars also, but the modifications shown in Fig. 2 must first be performed. TR3 is used to invert the voltage step to the input and the horn is connected in the collector circuit of TR2.

O. Jensen,
Oslo.


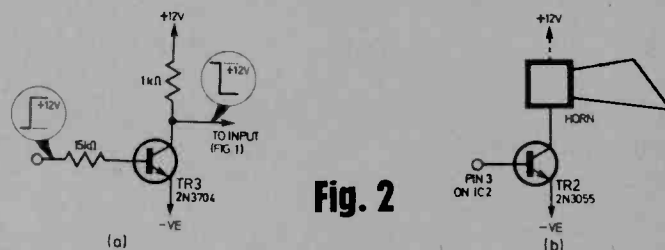


Fig. 2

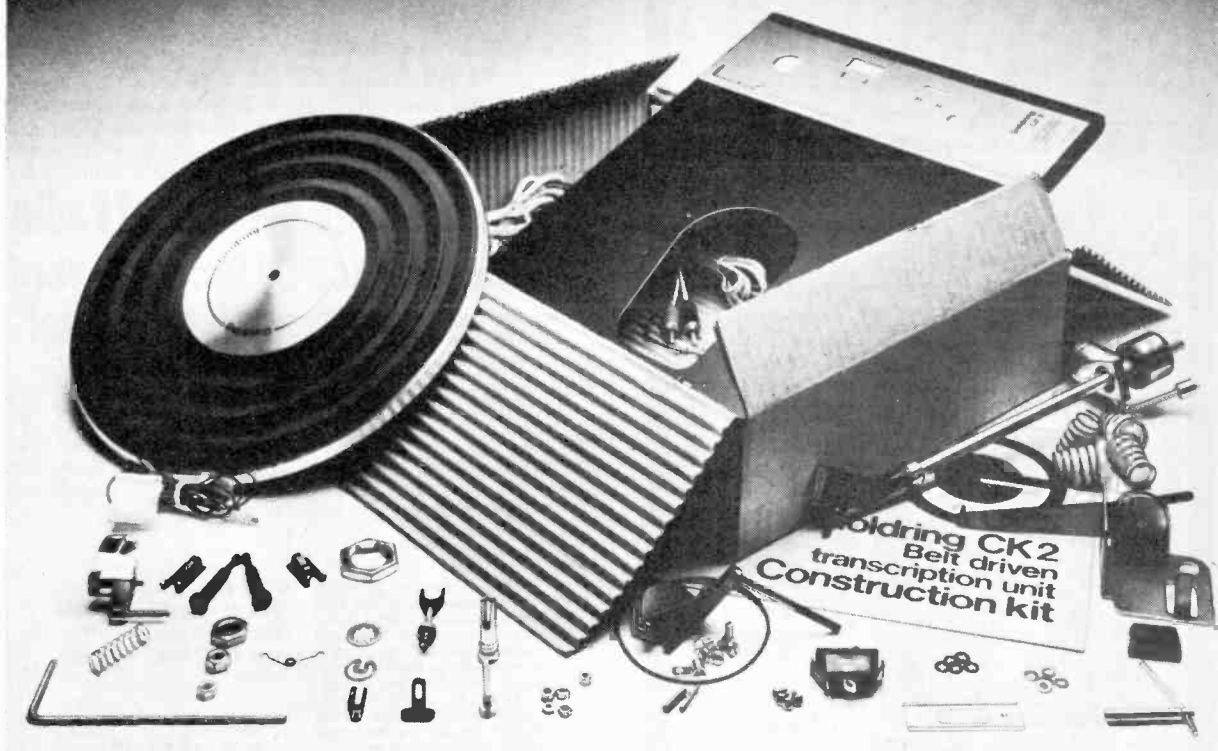How to get a reputation overnight for making Hi Fi equipment as good as ours.



To be perfectly honest, it's not that difficult.

Simply go out and buy a Goldring CK2 turntable construction kit. Follow the simple step by step instructions.

And in no time at all you'll be the proud owner of a superb, hand built, precision engineered deck.

Which can hardly fail to make your reputation amongst those who know about HiFi. And all achieved with the minimum capital outlay: around £28.00.

The Goldring CK2 kit is, in fact, based around the rather more widely known G102 turntable.

Which means it's belt driven, to reduce wow, flutter and rumble to an absolute minimum. (The same system most really expensive decks employ.)

The pick-up arm features a viscously damped raising and lowering device.


For the protection of your records, there's an anti-skate mechanism. And with an

easily adjustable playing weight, the arm will accept a wide range of cartridges, such as the Goldring G800.

A final touch is that both the on-off function and speed selection are via neat rocker switches.

If you fill in the coupon, we'll send you our free colour brochure, which describes the CK2 construction unit in detail.

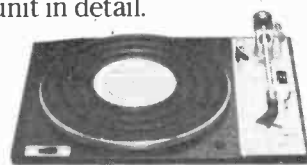And if you're serious about HiFi, you couldn't hope to ask for a better start than that.



To: Goldring Limited, 10 Bayford Street, Hackney, London E8 3SE.
Please tell me more about the Goldring CK2 Construction unit.

Name _____

Address _____

P.E.1

 **Goldring**

SOUND TO LIGHT MODULATOR

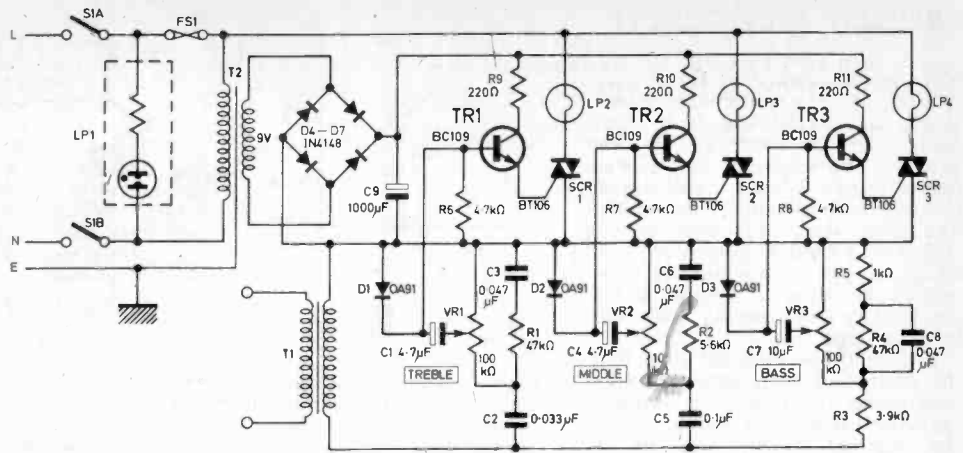


Fig. 1

THIS circuit (Fig. 1) uses cheap, easily obtainable components to make a simple but effective sound-to-light unit.

The input signals for the unit are derived from a 1:1 transformer which is wired in series with the speaker. The signal is then filtered into three channels (treble, middle

and bass). The level of each channel can be adjusted by the three potentiometers VR1 to 3. A thyristor is then fired by a transistor (operating as a switch) and this in turn illuminates the display light.

It is important that the negative supply rail of the unit is connected to neutral of the mains. With the

specified thyristors, 300W loads can easily be driven. A suitable transformer for T1 is an EL84 output transformer. T2 can be any 6-9V 500mA mains transformer.

By-pass switches can be fitted if desired to allow all displays to be on irrespective of sound level.

K. Coldwell, Sheffield.

THIS circuit was devised to convert the seven-segment outputs of the now widely-available l.s.i. calculator chips into a form of binary-coded decimal, for use in home-constructed calculators where BCD outputs may be required to feed into an external RAM i.c.

The basic circuit (Fig. 1) consists of a quad EXCLUSIVE OR two-input gate, type CD4030. Although more expensive than its TTL counterpart, the SN7486, this CMOS i.c. is far more versatile when one considers interfacing with other logic families.

Table 1 shows the outputs given by this circuit and, while the outputs are not pure BCD, they should be useful in most applications, and this should not prove to be a disadvantage.

For feeding these numbers from the external RAM back into the calculator input a BCD-to-decimal decoder can be used (except for the negative sign, but this cannot normally be entered directly on the keyboard, anyway).

It must then be remembered that the BCD-to-decimal decoder output would represent different decimal numbers.

If the input marked x is connected to -V instead of +V then the circuit will still produce the output shown in Table 1 if the seven-segment inputs are inverted illustrating the versatility of this circuit.

Andrew Cornish,
Teignmouth,
Devon.

SIMPLE 7-SEGMENT TO BCD ENCODER

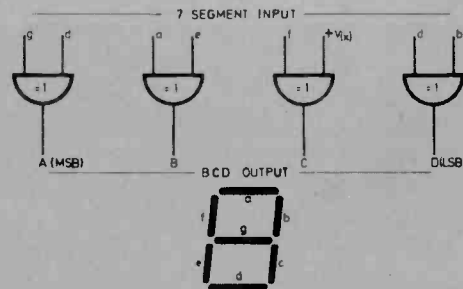


Fig. 1

Table 1.

Number	Segments on	Output			
		A	B	C	D
0	a b c d e f	1	0	0	0
1	bc	0	0	1	1
2	a b d e g	0	0	1	0
3	a b c d g	0	1	1	0
4	bc fg	1	0	0	1
5	a c d f g	0	1	0	1
6	a c d e f g	0	0	0	1
7	a b c	0	1	1	1
8	a b c d e f g	0	0	0	0
9	a b c d f g	0	1	0	0
Negative sign	g	1	0	1	0

AUXILIARY POWER SUPPLY

THE system described below was used as an additional power source for a portable radio normally running from a PP9 9V battery. The external supply was tapped from a 9½V d.c. transformed, rectified, and smoothed a.c. supply. The latter may, of course, be installed as a battery eliminator. This design is better than merely connecting the external supply across the battery for reasons that will be given later.

The circuit is designed such that the external system generally supplies power (provided it is stronger than the battery) but should it fail, the internal battery will supply power. A socket is used to provide easy connection to the auxiliary supply. A brand new battery when first used may supply a fraction of the power, but as it ages the voltage drop across the diodes will eventually isolate the battery.

S1 is an optional switch which may be used to switch off the external supply thus switching on the

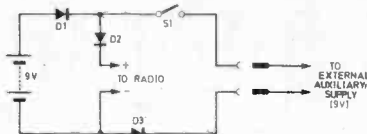


Fig. 1

battery. The diodes should be silicon and chosen so that they are capable of taking the maximum current drawn by the radio. D1 will prevent the battery from being "charged" by the external supply. D2 prevents the radio from being subjected to a reversed polarity. D3 will stop the battery from discharging if a short circuit occurs outside the radio with S1 closed.

When constructing the circuit cut the battery supply wires. In the positive line insert two diodes D1

and D2 in series and connect the external positive to the junction of D1 and D2. Join the two ends of the negative battery wire and connect D3 to this junction.

It is important to note that a brand new battery may have sufficient power to overcome the forward drop across D2 and will isolate the external supply. The actual p.d. of the external supply in the prototype was 9.35V which was enough to "overpower" the battery. D1 merely serves to prevent the radio being subjected to incorrect polarities. D3 is present to stop the battery being discharged should the external supply or associated components cause a short circuit to occur.

An additional component may be added namely a BZY88C10 Zener diode. This will conduct at approx. 9.4V and prevent spurious peaks from the external supply causing damage to the radio. It should be included across the external supply.

S. Bygrave,
Norwich,
Norfolk.

THIS wiper delay is suitable for cars with self-parking wipers. The delay can be continuously adjusted from 0 to 30 seconds (or more). I have used his device without trouble for a year in my Austin Mini.

The unit receives its power through the wiper motor. Capacitor C1 charges through VR1 and R1 until the stand-off voltage of the unijunction transistor TR1 is reached. Then C1 discharges through TR1 and R2 switching the thyristor CSR1 on. During the wipe the contact in the wiper closes and the current through the thyristor falls allowing it to switch off. At the end of the wipe the contact in the wiper opens and the unit receives power again, through the motor, and the delay commences. With VR1 at minimum the delay is 0.01 seconds, i.e. effectively zero.

R3 is included to ensure the current through the thyristor falls enough for it to switch off when the wiper contact closes. It may be necessary to increase the value of R3 and clean the wiper contact.

When the wiper opens at the end of a wipe the back e.m.f. of the motor can break down the thyristor and switch it on again without waiting for the delay. Diode D2 has a Zener breakdown less than that of the thyristor and so prevents this happening. (The diode used was a germanium diode from a computer panel. A 1N4001 would be suitable.)

Different values of C1 may be required to give the desired range of delays because of the differing stand-off ratios of unijunctions.

Polarity must, of course, be observed, when connecting this unit to the car.

M. P. Roberts,
Oxted, Surrey.

THYRISTOR WINDSCREEN WIPER DELAY

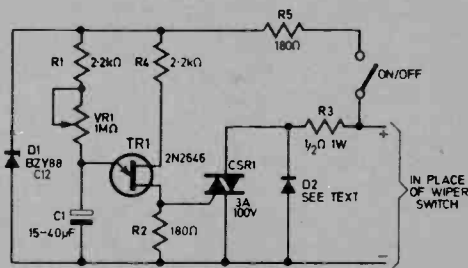


Fig. 1

PATENTS REVIEW...

CAR SOUND

BP 1 404 316

Lecturing recently to the Institution of Chemical Engineers, Dr Robert Aries, a prolific patent and trademark filer based in France, suggested that large firms frequently filed too many patent applications. He argued that research departments frequently felt obliged to file a reasonable number of patents per year, and so justify and maintain their annual budget.

Certainly this would explain the remarkable number of patents for trivial advances which continue to be filed, despite ever increasing official fees.

Although BP 1 404 316 from the Lucas Electrical Company Limited, appears to fall into this category, it is based on an interesting idea. In a car, it is conventional to mount the radio or tape deck speakers at the left and right of the dashboard or at the left and right of the rear window.

Lucas suggest that the ideal location is with one speaker under each of the front seats. The loudspeakers point in the direction of the longitudinal axis of the car, and it is claimed that this improves bass response by achieving a longer than usual unrestricted air path for the reproduced sound.

Ideally, each loudspeaker is open at its front and back except for a protective grille.

COMMUNICATION FOR THE DEAF

BP 1 400 042

In BP 1 400 042, Bruno Fracassi, of Rome, Italy, describes a fairly simple method of using the telephone to provide a morse code readout suitable for the deaf. Because the telephone is coupled only acoustically to the device described, there should be no Post Office objections to its use.

A cradle is provided, into which a telephone handset can be rested for transduction in the manner conventional for a temporary computer terminal. A morse key makes

and breaks an oscillator circuit which drives a small loudspeaker coupled acoustically to the handset microphone. Paper tape from a roll is guided by a motor between an electromagnet and the writing point of an ink-reservoir pen.

Incoming sounds reproduced by the headset are received by the microphone and amplified to energise the electromagnet to move the paper tape temporarily towards the pen point. Received morse code signals therefore cause the pen to inscribe dots and dashes on the paper tape.

Morse code signals produced by the morse key will produce similarly inscribed signals on the paper tape of a matching device at the other end of the telephone line connection.

HEAT/ENERGY

BP 1 404 689

In BP 1 404 689, Francis, Fergan and Christopher O'Sullivan, of Sydney, Australia, patent and apparently simple system for converting heat into electrical energy.

The fact that the Australian inventors have thought it worth while to file an application here, on the other side of the earth, and the fact also that the British Patent Office Examiners have accepted the case, suggests that although the idea is simple it may be new. Electronics enthusiasts should have no difficulty in establishing for themselves whether it works.

A liquid container made from electrically conductive material, such as aluminium, and containing an aqueous ionic solution, a 3 per cent solution of sodium chloride (salt) is instanced but it is suggested that the quantity and strength of the solution are not important.

An electrode is immersed in the liquid and another electrode is connected to the exterior of the container. The electrodes can be of any conductive material provided that it is different from the material of the container. The electrodes may, for instance, be of copper.

The claim is that if heat is applied to the container, for instance by focusing the sun's rays onto it or heating it with a natural gas flame, bubbles will appear in the liquid to produce four-phase interfaces, i.e. one electrode/bubbles (solid/gas); the container/bubbles (solid/gas); liquid/bubbles (liquid/gas); and liquid/other electrode (liquid/solid).

According to the inventors, electrical energy is available, as a result of the chemical reactions across the two electrodes.

IN BRIEF


BP 1 410 380 — Elektroakusztikai Gyar: *Tone control circuit*. An amplifier having an inverting and a non-inverting input, with feedback loops provided.

BP 1 414 260 — Elektromechanikai Vallalat: *Quadraphonic transmission*. The radio transmission of more than two channels of sound by multiplex techniques. This is one of numerous patents for surround sound radio, but is particularly interesting in that (like BP 1 410 380 mentioned above) it originates from Hungary, suggesting increasing interest in audio engineering from that country.

BP 1 411 994 — Cooper D. H.: *Signal matrixing for directional reproduction of sound*. These two patents from Duane Cooper, of the USA, describe the BMX matrix system used in the base band of the Nippon Columbia UD-4 surround sound system. The closely related Ambisonics system developed by a British team including Professor Fellgett, Michael Gerzon and backed by the NRDC was also recently the subject of a British patent, **No. 1 369 813**.

Both systems have in common the basic concept of matrixing different signals together according to coefficients which vary in dependence upon the original sound source direction. Even more recently a very similar system was patented by the BBC in **BP 1 414 166**.

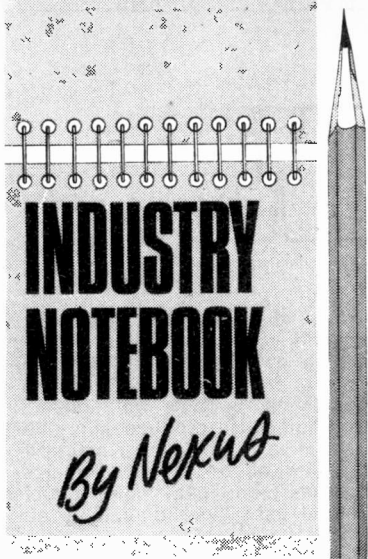Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 75p each



INDUSTRY NOTEBOOK

By Nexus

MEMORIES

Anno Domini 1975 was rough and tough and perhaps best forgotten as the world now edges upwards out of recession. But figures keep trickling through suggesting that 1975, although by no means one of the great years, still had a lot going for it for those who knew what they were doing and had something first-class to sell.

SPACE AND AVIONICS

Aerospace deserves yet another mention if only because this particular industry is the cradle of technology. British exports were £800 million, the highest level ever and in this grand total airborne navigation aids achieved a gain of over 20 per cent over 1974, flight simulators up by nearly 250 per cent and instruments up by some 75 per cent. BAC's Rapier missile system topped the £400 million mark on the order book and, apart from substantial deliveries due this year, there should be some more orders in the pipeline.

On the stocks for this year are the Ferranti Blue Fox airborne radar for the naval version of the Harrier V/STOL aircraft. Blue Fox is a further development of the Ferranti Seaspray designed for the Lynx helicopter. A very large contract has been placed with Hawker Siddeley for the XJ521 air-to-air missile following successful firings late last year.

Based on the US Sparrow missile it has all-British electronic guidance by Marconi Space and Defence Systems and a new fuse by EMI Electronics. The British update version is said to be so effective operationally that the missile is virtually a new generation

system which should see service through to the 1990s.

Then there is the continuing success of Marconi-Elliott's head-up display systems. A new version has a TV raster display superimposed on the ordinary flight information, coupled to low-light TV cameras or infra-red scanners enabling a pilot to see the landscape while flying at night.

Eight systems have been sold to the US Navy for evaluation and two are now being test flown in A-7E Corsairs of the US Navy. Other systems are on evaluation for the Royal Air Force at the Royal Aircraft Establishment.

The Raster HUD will keep Britain ahead. Marconi-Elliott has already built more HUD's than the rest of the world added together and most have gone for export.

Best news of all for British avionics is that the multi-role combat aircraft (MRCA) is still going ahead despite pressure from some quarters to cancel or cut the existing contracts.

CIVIL FRONT

On the civil front I will confine myself to three companies. STC took orders for £84 million for submarine cables and repeaters in 1975, all of which are for export. EMI continues the enormous success with medical brain and body scanners and although US General Electric has announced a competitive product EMI remains unconcerned.

Marconi Communications Systems working with the Post Office put North Sea Oil on the radio map with a quadruple diversity troposcatter system of unparalleled reliability in a little over a year. Further extensions will be added this year.

ENTERPRISE

It seems only yesterday that we were looking ahead to the big leap forward to the solid state 4k random access memory. Such is the rapid progress of solid state technology that samples of 16k devices are now available from several manufacturers.

Companies like TI, Intel, Mostek, Motorola and Fairchild are all in the race to supply the world with the best devices and, as volume grows, at the keenest prices. We may expect the subsequent economic war to be at its fiercest with frantic price-cutting in the now well-established tradition of the semiconductor industry.

I often think to myself what would have happened if world socialism and the doctrine of the nationalised industry had been

implemented a quarter of a century ago. Would a monolithic Global Solid State Corporation with monopoly powers and overloaded with bureaucracy have achieved so much in a single generation, both in basic research and in virtuosity of production?

SHEER COMPETITION

When I glance through the advertisement columns of this journal and see dozens of types of i.c.s available at less than half the price of a packet of cigarettes and in many cases less than the cost of postage and packing to the customer, I just cannot believe that any system other than competitive private enterprise with the real-life pressure of the market place could have done so well.

Companies who couldn't stand the heat in the early days retired hurt, financially speaking. Sheer competition sorted out the men from the boys and although painful to the losers, this was to the general good. The struggle for survival has not only forced prices down but has kept technology on the move at a cracking pace, far faster than would be possible in any "planned" enterprise.

My guess is that Global Solid State, after 25 years of major effort and a few billion pounds of money milked from taxes paid by World Citizens, might today be just getting round to a simple family of TTL devices to be marketed at around £5 per one-off, just about the price of a complete pocket calculator in free-market conditions. Let us be duly thankful that Global Solid State exists purely in the imagination.

COST OF PERFECTION

Electronic timepieces are going up in accuracy and down in price. Sinclair, for example, guarantees an accuracy of one second per day for £24.95 but suggests in his advertising that even better accuracies may be expected. But if you need greater guaranteed accuracies you need to pay the price, just like buying diamonds where each succeeding level of perfection demands a ten-fold increase.

Kelvin Hughes latest electronic ship chronometer is claimed to have an accuracy of better than 0.1 seconds per day. But the recommended price is £290, available for the traditionalist shipowner in mahogany case and for the avant-garde in either rosewood or aluminium.

Complete the coupon and we'll send you our complete, new catalogue.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now (enclosing a 10p stamp for postage) and we'll send you your copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.


So, when you receive your catalogue you should have hours of pleasant reading.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.


At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. PE-46 Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.


Digital IC tester.

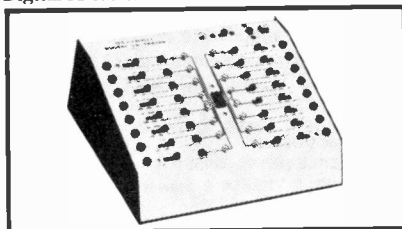

Digital electronic stop watch.

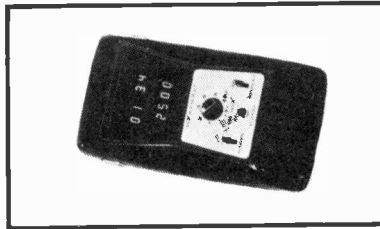

Heathkit Modulus. A new era in Hi-Fi.

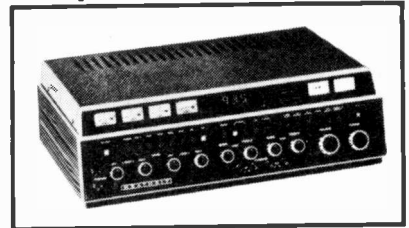

FREE
SOLDERING IRON
WORTH
£3.50
with all orders over £30

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. PE-46, Gloucester, GL2 6EE.
Please send me my Heathkit catalogue. I enclose a 10p stamp for postage.

Name _____ Address _____
Postcode _____

Full details in the catalogue. Offer available for limited period only.

HEATH
Schlumberger


EASY TERMS AVAILABLE
WITH HEATHKIT MONTHLY
BUDGET PLAN

RADIO EXCHANGE LTD.

ALL PRICES INCLUDE VAT

NEW EDU-KIT MAJOR

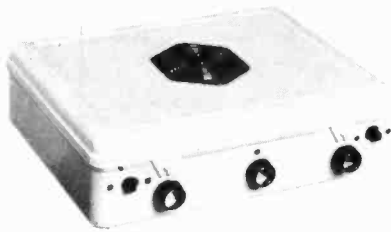COMPLETELY SOLDERLESS
ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER



- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN — PNP
- 4 Transistor Push Pull Amplifier
- 24 Resistors
- 3 12-way Connectors
- Ready Wound MW/LW/SW Coils
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- 10 Transistors
- 3 1/2" Loudspeaker
- 10 Transistors
- 3 1/2" Loudspeaker
- Earpiece
- 1 Tuning Condenser
- 3 Knobs
- 1 yard of wire
- 1 yard of sleeving, etc.

Complete kit of parts including construction plans
Total building costs **£9.99**
P.P. and Ins. 65p
(Overseas Seamail P. & P. £3.50)

V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the long wave band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc.

All parts including case and plans


£4.35 P.P. & Ins. 40p



POCKET FIVE

Now with 3 1/2" Loudspeaker 3 tunable wavebands. MW, LW and trawler band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" in approx.

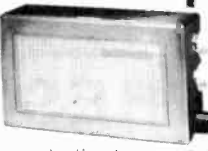Complete kit of parts including construction plans.
Total Building Costs: **£3.99** P.P. and Ins. 50p



NEW Everyday Series

Build this exciting new series of designs.

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5 1/2in. x 2 1/2in. approx. All parts including Case and Plans.

Total Building costs **£4.75** P. & P. + Ins. 50p

E.V.6. Case and looks as above. 6 Transistors 3 diodes. Powered by 9V battery. Ferrite rod aerial, 3in. loudspeaker, etc. MW/LW coverage. Push/Pull output.

All parts including Case and Plans.
Total Building costs **£5.50** P. & P. + Ins. 55p

E.V.7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band SW1, SW2, SW3, powered by 9V battery. Push pull output. Telescopic aerial for short waves. 3in. Loudspeaker. All parts including Case and Plans.


Total Building Costs **£7.05** P. & P. + Ins. 55p



ROAMER TEN MARK 2

WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket. 10 transistors. Latest 5" x 3" loudspeaker. 9 tuneable wavebands MW1, MW2, LW, SW1, SW2, SW3, trawler band, VHF and local stations, also aircraft band. Built in ferrite rod aerial for MW/LW. Chrome plated. 6 section telescope aerial, can be angled and rotated for peak short wave and VHF listening. Push pull output using 600mW transistors. Car aerial socket. 10 Transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for aircraft band. Volume on/off. Wave change and tone controls. Attractive Case in rich chestnut shade with gold blocking. 9in. x 7in. x 4in. Easy to follow instructions **£11.87** P.P. and diagrams. Total build- Ins. 65p costs:

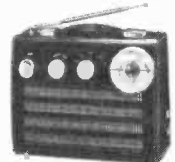

EDU-KIT

Build Radios, Amplifiers, etc., from easy stage diagrams



Five unit including master unit to construct


Components include: Tuning condenser, 2 volume controls, 2 slider switches, fine tone 3in moving coil speaker, terminal strip, ferrite rod aerial, battery clips, 4 tag boards, 10 transistors, 4 diodes, resistors, capacitors, 3 1/2in knobs, Units once constructed are detachable from master unit, enabling them to be stored for future use. Ideal for schools, educational authorities and all those interested in radio construction.
All parts including case and plans. **£6.99** P.P. and Ins. 55p

ELECTRONIC CONSTRUCTION KITS

E.C.K. 2 Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 3in loudspeaker, gain control, superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

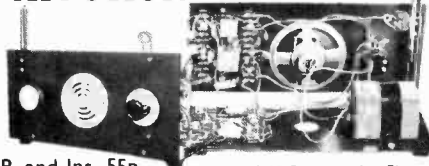Complete kit of parts **£7.95** P.P. and Ins. 55p




Including Construction Plans

E.C.K. 4

7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band. 3 Short Wave Bands. Receiver Kit. With 5in x 3in loudspeaker. Push pull output stage, gain control, and rotary switch. 7 transistors and 4 diodes. 6 section chrome-plated telescopic aerial. 8 in sensitive ready wound ferrite rod aerial, tuning capacitor, resistors, capacitors, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit).

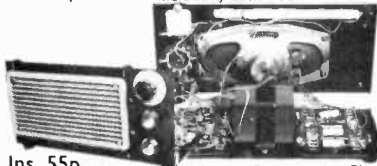Complete kit of parts **£7.25** P.P. and Ins. 55p



Including Construction Plans


EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including loudspeaker, earpiece, MW ferrite rod aerial, capacitors, resistors, transistors, etc.

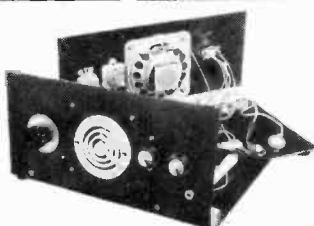
Complete kit of parts including construction plans **£7.25** P. & P. + Ins. 55p



JIFFY TESTER

Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Complete with earpiece, jack plug and socket resistors, capacitors, components, etc.

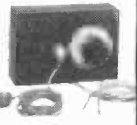Complete kit of parts including construction plans **£3.15** P. & P. + Ins. 30p



To: RADIO EXCHANGE LTD.
61A High Street
Bedford MK40 1SA

Tel.: 0234 52367, REG NO. 788372

- Callers side entrance "Lavella" Shop.
- Open 10-1, 2.30-4.30 Mon Fri. 9-12 Sat

I enclose £..... for


Name

Address

PE476

FULL SPEC. LEDs

Packs of 5—inc. clips and data

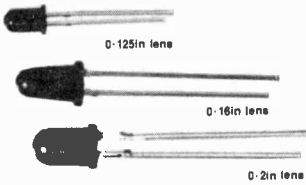

Red 75p; Green, Yellow, Orange £1-20.

ECONOMY QUALITY LEDs

Mixed bags. All colours of all sizes—ideal for experimenters: 50 for £5; 100 for £9.

FULL SPEC. LED SEVEN SEGMENT DISPLAYS

0.3in common anode.
L.H. decimal.
Red, Green, Yellow, £1-35 each inc. data.




ECONOMY QUALITY

0.3in common anode. L.H. decimal.
Red, 73p each.

PLASTIC BOXES

COLOUR GREY

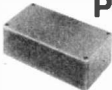

ABS—Ribbed inside on 5mm centres for 1.5mm PCB. Brass corner inserts for securing top with 3mm screws.

62mm x 112mm x 31mm, 1-9 52p each; 10 + 48p each.
120mm x 65mm x 40mm, 1-9 66p each; 10 + 82p each.
150mm x 80mm x 50mm, 1-9 75p each; 10 + 71p each.


POLYSTYRENE—Plain inside. Top secured by self-tapping screws. 61mm x 112mm x 31mm, 1-9 35p each; 10 + 32p each.

SPECIAL OFFER

Sample Pack, 4 boxes—1 of each size, £2-10.

NEON INDICATORS

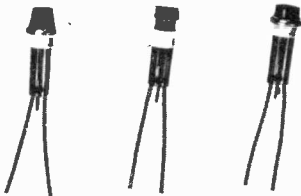240V (built-in resistance)—150mm lead out wires



Fit 8mm hole and include spire clip for fixing. Red, Amber, Clear, Opal—19p each; Green—28p each.
Type MP—Fits 6.4mm hole—nut fixing. Red, Amber, Clear, Opal, 22p each.

LAMPHOLDER DH

Takes either LES (with adaptor provided) or Midget Flange Bulbs. Fits 13mm hole—nut fixing. Red, Blue, Green, Amber, Clear, Opal, Orange, 25p each (bulbs not provided).



Quotations for larger quantities on request. All prices include VAT at 8%. Please add 20p P. & P. on orders under £10. On orders for boxes please add 25p per £1, minimum 25p maximum £1-50.

MICHAEL WILLIAMS ELECTRONICS

47 Vicarage Avenue
Cheshire Hulme, Cheshire SK8 7JP

GIRO NO. 331 7056. Access and Barclay-card accepted.
C.W.O. only. Terms of business as in our Catalogue.
Export Order enquiries welcome (£5 min.)
Official Orders accepted from Educational and Government Departments
ALL PRICES include VAT and P. & P.
E & O.E. SHOP HOURS 9-12.30, 1.30-5.00 6 days

86 PAGES—3,000 ITEMS FULLY ILLUSTRATED
*20p CREDIT VOUCHERS
*ALL NEW STOCK
*SATISFACTION GUARANTEED
*DISCOUNTS
*NEW PRICE LIST No. 1—S.A.E.

20p plus 10p postage

Boxes — Cases — Kits — PC Materials — Tools — Resistors — Test Meters — Capacitors — Hardware — Semiconductors — Books — Pots — Coils — Audio Accessories — Screws — Connectors — Audio — Modules — Veroboard — Transformers — Knobs — Calculators — Audio Leads — Batteries — 5 dec Storage Units — Heatinks, etc., etc.

Electronic Components Catalogue 4a

FOR LTD.

SPECIAL CAPACITOR KITS
C260 Kit—PC Mounting polyester, 250V, 5 of each value: 0-01, 0-022, 0-047, 0-1, 0-22uF, 2 of 0-47, 1uF, £1-98 net.
C266 Kit—Tubular polyester, 400V, 5 of each value 0-01, 0-022, 0-047, 0-1, 0-22uF, 2 of 0-47uF, £2-87 net.
Ceramic Kit—square plaque, 50V 5 of each value, 22, 33, 47, 100, 220, 330, 470, 1000pF, 220, 4700pF, 0-01uF, £1-68 net.

SPECIAL RESISTOR KITS (CARBON FILM 5%) (Prices include post & packing) 10E12 μ W or μ W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 £5-29 net
25E12 μ W or μ W KIT: 25 of each E12 value, 22ohms—1M, a total of 1425 £12-64 net

B. H. COMPONENT FACTORS LTD.

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator 20,000V/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—5 Ω —1M Ω in 4 ranges
Accuracy—5% of F.S.D.
OSCILLATOR—1KHz and 465KHz (A.M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8-84 net P. & P. 75p



U4323

MULTIMETER U4324
34 Ranges. High sensitivity. 20,000V/Volt.
Vdc—0.6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25 Ω —5M Ω in 5 ranges.
Accuracy—dc and R—2½% of F.S.D.
ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode and battery.
PRICE £10-84 net P. & P. 75p.



U4324

MULTIMETER U4341
27 Ranges plus Transistor Tester. 18,700V/Volt.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 8 ranges.
Idc—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2K Ω —2M Ω in 4 ranges. Accuracy—dc—2½% ac—4% of F.S.D.
Ite—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with carrying case, test leads, and battery.
PRICE £11-88 net P. & P. 75p



U4341

MULTIMETER U4313
33 ranges. Knife edge with mirror scale. 20,000V/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2.
Iac—0.6—1500mA in 8 ranges.
Iac—0.6—1500mA in 8 ranges.
Resistance—1K Ω —1M Ω in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1½%, ac—2½%.
Size—115 x 215 x 90mm.
Complete with carrying case, test leads, and battery.
PRICE £14-90 net P. & P. 75p.




U4313

(P.E.), LEIGHTON ELECTRONICS CENTRE, 58 NORTH STREET, LEIGHTON BUZZARD, LU7 7EG. Tel.: Leighton Buzzard 2316 (Std. Code 05253)


PRECISION PETITE LTD.

119A HIGH STREET, TEDDINGTON TW11 8HG
Tel. 01-977 0878

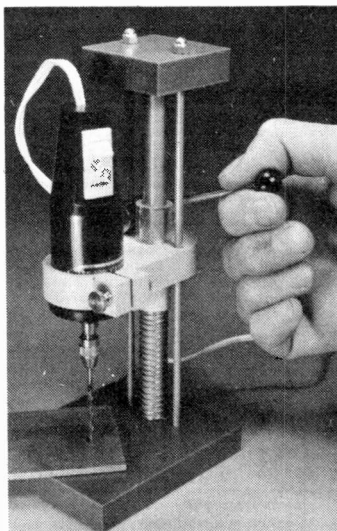INTRODUCING A MINIATURE PRECISION 12V. D.C. DRILL DESIGNED FOR THE ELECTRONIC ENGINEER



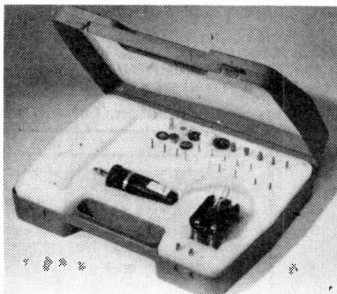Mk. II Drill only
£8-00 p.p. 35p
Stand
£3-76 p.p. 58p



Complete kit as illustrated (less batts.) with a variety of 30 tools. Space for Stand and Transformer.
KIT 30 TOOLS £16-00 p.p. 75p
STAND £3-76 p.p. 35p
TRANSFORMER £5-50 p.p. 75p


S.A.E. FOR DETAILS

barclay

TECHNOLOGICAL
PRECISION PRODUCTS

ELECTRONICS

The Superb CASIO fx-20

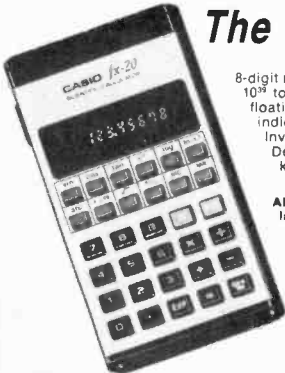

8-digit mantissa or 6-digit mantissa and 2-digit exponents 10^{39} to 10^{-39} . Algebraic logic. Bright Green display. Full floating point with underflow. Overflow and negative indicators. Sin, Cos, Tan, Inverse Sin, Inverse Cos, Inverse Tan, Log x and Inx, e^x , x^y , $\sqrt{\quad}$, Reciprocal, Degree Radian conversion, Memory Exponent key.

Also the larger fx-15, which includes in addition, larger display, x^2 key, π key, Reciprocal key

*£23.90 + 8% VAT

And the de Luxe fx-101 with similar functions to the fx-15 but 8-digits + 2 exponents, 10^{99} to 10^{-99}

*£27.90 + 8% VAT

All have sexagesimal decimal conversion
*Mains adaptor £2.75 extra.

ONLY
£18.50

+ 8% VAT

Optional mains adaptor £3

SCIENTIFIC

ALGEBRAIC	£
CBM SR4148 12 digit + 2 exp	39.95
CBM SR6120 10-digit + 2 exp	31.95
TEXAS SR16 8-digit + 2 exp	31.50
TEXAS 50A 10-digit + 2 exp.	35.50
TEXAS 51A 10-digit + 2 exp.	49.50
ROCKWELL 51R 8-digit conversion	23.95
ROCKWELL 63R 8-digit + 2 exp	29.99
ROCKWELL 61R 8-digit	27.50
SINCLAIR OXFORD 300 5-digit + 2 exp.	21.95
CASIO FX101 8-digit + 2 exp.	26.90
CASIO FX15 6-digit + 2 exp.	24.03
CASIO FX10 6-digit + 2 exp.	19.95
THE NEW Green VATMAN SCIENTIFIC 8-digit + 2 exp.	27.90
REVERSE POLISH LOGIC	
SINCLAIR SCIENTIFIC 5-digit + 2 exp.	11.50
NOVOUS 4510 8-digit mathematic	17.75
NOVOUS 4515 8-digit mathematic, 100 step programmable	36.50
NOVOUS 4520 8-digit 2 exp, 4 roll stack	25.50
NOVOUS 4525 8-digit 2 exp, 4 roll stack 100 step programmable	49.50
NOVOUS 6010 8-digit conversion	19.50
NOVOUS 6020 8-digit financial	19.50
NOVOUS 6025 8-digit financial, 100 step programmable	49.50
NOVOUS 6030 8-digit statistical	19.50
NOVOUS 6035 8-digit statistical, 100 step programmable	49.50
Add 8%VAT, P. & P. 55p	

VATMAN Scientific



8-digit and 2 exponents. Single function colour-coded keyboard with click-keys. bright Green display CE key, C key, Y key, E key, In key, Log key, 10^x, Sin, Tan, Cos, Inverse Sin, Inverse Cos, Inverse Tan, DMS key to change Radian to Decimal degrees. Exchange key, DR key to delete each 1 digit of last entry, π key, $\sqrt{\quad}$ key, x^2 key, Full memory Sign change key, Exponent key 10^{99} to 10^{-99} . Attractive soft Vynyl carrying case. Maximum battery life-20 hrs.

OUR PRICE
£29.95 + 8% VAT

Mains adaptor £3

THE SMALLEST SCIENTIFIC CALCULATOR WE HAVE EVER SEEN!

THE NEW sinclair SCIENTIFIC

Only 44in x 21in x 14in yet has 8 digits or 5 + 2 exponents. Using the new chip it has full algebraic logic and many more functions: 4 arithmetic functions +, -, x, \div , Algebraic logic constant on all four arithmetic functions, C, and CE key, Sin key, Cos key, Tan key, Arcsin key, Arccos key, Arctan key, Reciprocal key, E to the X key, Natural log key, Antilog key, key, Memory + key, Memory - key, Memory exchange key and Memory cancel key, EE exponent key, change notation key, Degree Radian switch and on/off key.



OUR PRICE
£13.50 + 8% VAT

ONE OF THE MOST ADVANCED CALCULATORS Texas SR50A

The SR-50 is the full function portable slide rule calculator. Complex scientific calculations are solved as easily as simple arithmetic problems. The SR-50 features an algebraic keyboard with single function keys for easy problem solving. 10 digits + 2 exponents. Deg/Rad Switch. π P1 Key. x^2 Square Key. $\sqrt{\quad}$ Square Root Key. $1/x$ Reciprocal Key. $x!$ Factorial Key. arc inverse Trigonometric Key. EE Enter Exponent Key. + - Change Sign Key. CE Clear Entry Key. C Clear Key. hyp Hyperbolic Function Key. D/R Angle Change Key. log Common Logarithm Key. $\ln x$ Natural Logarithm Key. e^x e to the xth Power Key. y^x y to the xth Power Key. $\sqrt[x]{y}$ The xth Root of y Key. xy Exchange Key. STO Store Key. RCL Recall Key. Sum and Store Key. Complete with rechargeable batteries, adaptor/charger, carry case and Owners Manual.

OUR PRICE
£49.50 + 8% VAT

The NEWEST from NOVOUS—4525 PROGRAMMABLE SCIENTIST

The NEW 100 Step Programmable Scientific Calculator. Saves time and effort with complicated problems.

THIS IS TRULY AN UN-BEATABLE MACHINE!

8-digit 3 exponents natural logs and anti log and their inverse. Common and their inverse. Sin, Cos, Tan and their inverse. Reciprocals. Y^x. X^Y. 4 roll stack. Register exchange + X². Degree Radian conversion. Memory chargeable (Recharger included in Price). Vynyl case (full instruction manual). Also available NOVUS 4520 non-programmable. Or the 4515 "MATHEMATICIAN" 8-digit 100 step programmable 3 level stack, recharger, case and instruction manual. And the 4510. As the Mathematician but non-programmable.



£49.50 + 8% VAT

£25.50 + 8% VAT

£36.50 + 8% VAT

£17.75 + 8% VAT

ALL THE ABOVE HAVE REVERSE POLISH LOGIC
Novous Mains Adaptor for the 4510, £3

FINEST QUALITY DIGITAL WATCHES FROM £22.95 + 8% VAT



ASTRO (1st illus.). 4-functions: Hours, minutes, secs, 3 sec hold. Stainless-steel matching bracelet and presentation box. £22.95 + 8% VAT

ONYX (2nd illus.). Presentation-packed, one of the finest digital watches available at this low, low price. Full 5-functions showing hours, mins, secs, month and date. Limited supplies. ONLY £27.50 + 8% VAT

ARNEX QUARTZ. As above with matching bracelet and case. Water resistant. Stylish face. 2-button operation. Full 6 functions: hours, mins., secs., date and day. OUR PRICE ONLY £32.50 + 8% VAT

MICROSONIC. Full 5-functions. Attractive oblong face with superb body-matching flexible bracelet. Gold plated or available in Stainless-steel. ONLY £35.50 + 8% VAT

TELON (3rd illus.). One of the finest and slimmest watches we have yet offered. FULL 7-FUNCTIONS! Beautifully styled flexible bracelet and case in satin Stainless-steel. Bright L.E.D., display with 3-sec. hold and fade-out—hours, mins., secs. (secs. displayed with mins.) month and date! Single button operation. OUR PRICE ONLY £37.50 + 8% VAT

All these watches have automatic computerisation for 28, 30 and 31 day months and arrive in beautiful presentation boxes

ORDER FORM

To: **BARCLAY ELECTRONICS** Dept PE5B
STANLEY HOUSE, 1115, FINCHLEY ROAD, LONDON N.W.11.

All goods fully guaranteed. If not satisfied—money refunded if returned undamaged within 7 days

PHONE CALLS AND PERSONAL CALLERS WELCOME MON-THURS BETWEEN 2 and 5 pm. 01-458 4755

Please send me

with/without optional mains adaptor. I enclose cheque/money order total value

£ including 55p to cover packing

NAME

ADDRESS

barclay
ELECTRONICS

More than just a catalogue

Projects for you to build

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc. . . .

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .




132 pages!

130 h/w/low

**MAPLIN
ELECTRONIC
SUPPLIES**
SUPERSONIC
SAME-DAY-SERVICE
QUALITY COMPONENTS
-FAST!

REALLY GOOD VALUE FOR MONEY AT JUST 40p.

ELECTRONIC ORGAN

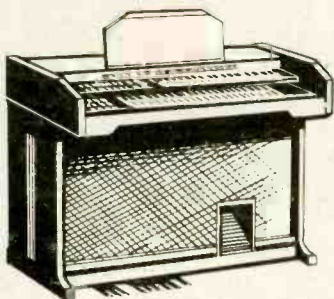

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops.

Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, priced at 35p. (Pre-publication price 15p.)

No more doubts about prices

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods—and we'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an S.A.E. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list—you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented!—plus details of any new lines, special offers, interesting projects—and clip-off coupons to spend on components to repay your 30p when used as directed.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to P.O. Box 3, Rayleigh, Essex, SS6 8LR.

SYNTHESISER



A reprint of the complete article giving full construction details published by "Electronics Today International" between January-

September '74 of the International Voltage Controlled Synthesiser, developed as a 'state of the art', now available, price £1.50. S.A.E. please for detailed price list.

GRAPHIC EQUALISER



A really superior high quality stereo graphic equaliser as described in the January edition of "Electronics Today International". We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

**MAPLIN
ELECTRONIC
SUPPLIES**

P.O. Box 3-Rayleigh Essex SS6 8LR.
Telephone: Southend-on-Sea (0702) 44101