

PRACTICAL

Australia \$1.25 New Zealand \$1.30 Malaysia \$4.95 IR 90p (inc. VAT)

ELECTRONICS

SEPTEMBER 1981

65p

FREE!

BOOKLET

U.K. ISSUES
ONLY



Introduction to Legal CB

Michael Tooley B.A.


AND

David Whitfield M.A. M.Sc.

- * TYPICAL PERFORMANCE
- * 934 MHz COMPARED WITH 27 MHz
- * WHAT IS FM?
- * FM VERSUS AM!
- * GENERATING FM
- * BASIC CONFIGURATION
- * USING CB

PRACTICAL
ELECTRONICS

IN THIS ISSUE!

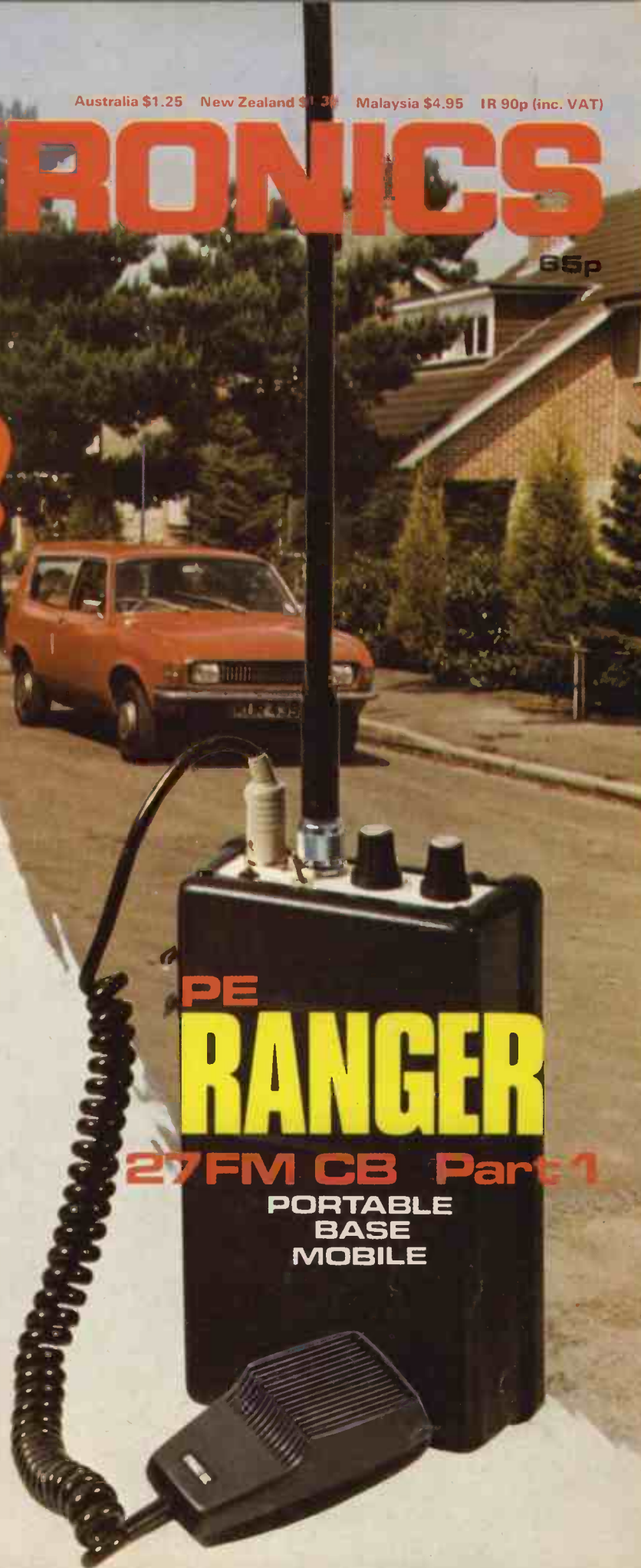

PE

RANGER

27FM CB Part 1

PORTABLE
BASE
MOBILE

Unique in concept—the home computer that grows as you do!

The Acorn Atom

£120


plus VAT and p&p

Special features include

- * FULL SIZED KEYBOARD
- * ASSEMBLER AND BASIC
- * TOP QUALITY MOULDED CASE
- HIGH RESOLUTION COLOUR GRAPHICS*

* optional

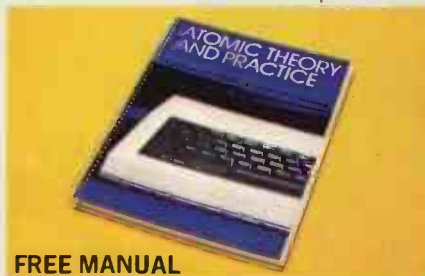The Acorn Atom is a definitive personal computer. Simple to build, simple to operate. A powerful, full facility computer with all the features you would expect. Just connect the assembled computer to any domestic TV and power source and you are ready to begin. (Power requirement: 8V at 800mA). There is an ATOM power unit available – see the coupon below.



FREE MANUAL

Free with every ATOM, kit or built, is a computer manual. The first section explains and teaches you BASIC, the language that most personal computers and the ATOM operate in. The instructions are simple and learning quickly becomes a pleasure. You'll soon be writing your own programs. The second section is a reference

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. All components are guaranteed with full service/repair facility available.

manual giving a full description of the ATOM's facilities and how to use them. Both sections are fully illustrated with example programs.

The standard ATOM includes:

- HARDWARE**
- Full-sized QWERTY keyboard
 - 6502 Microprocessor
 - Rugged injection-moulded case
 - 2K RAM
 - 8K HYPER-ROM
 - 23 integrated circuits and sockets
 - Audio cassette interface
 - UHF TV output
 - Full assembly instructions
- SOFTWARE**
- 32-bit arithmetic ($\pm 2,000,000,000$)
 - High speed execution
 - 43 standard/extended BASIC commands
 - Variable length strings (up to 256 characters)
 - String manipulation functions
 - 27 x 32 bit integer variables
 - 27 additional arrays
 - Random number function
 - PUT and GET byte
 - WAIT command for timing
 - DO-UNTIL construction
 - Logical operators (AND, OR, EX-OR)
 - Link to machine – code routines
 - PLOT commands, DRAW and MOVE

The ATOM modular concept

The ATOM has been designed to grow with you. As you build confidence and knowledge you can add more components. For instance the next stage might be to increase the ROM and RAM on the basic ATOM from 8K + 2K to 12K + 12K respectively. This will give you a direct printer drive, floating point mathematics, scientific and trigonometric functions, high resolution graphics.

From there you can expand indefinitely. Acorn have produced an enormous range of compatible PCB's which can be added to your original computer. For instance:

- A module to give red, green and blue colour signals
 - Teletext VDU card (for Prestel and Ceefax information)
 - An in-board connector for a communications loop interface – any number of ATOMs may be linked to each other or to a master system with mass storage/hard copy facility
 - Floppy disk controller card.
- For details of these and other additions write to the address below.



ACORN COMPUTER 4a Market Hill, CAMBRIDGE CB2 3NJ

Please send me the following items:

Quantity	Item	Item price inc. VAT+p&p	TOTALS
	ATOM KIT - 8K ROM + 2K RAM (MIN)	@ £140.00	
	ATOM ASSEMBLED-8K ROM+2K RAM (MIN)	@ £174.50	
	ATOM KIT - 12K ROM + 12K RAM (MAX)	@ £255.00	
	ATOM ASSEMBLED-12K ROM+12K RAM (MAX)	@ £289.50	
	1K RAM SETS	@ £11.22	
	4K FLOATING POINT ROM (inc in 12K Version)	@ £23.30	
	PRINTER DRIVE	6522 VIA @ £10.35	
	(inc in 12K version)	LS244 Buffer @ £3.17	
	MAINS POWER SUPPLY (1.3 amps)	@ £10.20	
		TOTAL	

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ

I enclose cheque/postal order for £ _____

Please debit my Access/Barclaycard No. _____

Signature _____

Name (Please print) _____

Address _____

Telephone No. _____

Registered No: 1403810. VAT No: 215 400 220

PE/9/81



CONSTRUCTIONAL PROJECTS

REMOTE KEYBOARD by <i>J. Lewis</i>	24
Interface the layman to your computer	
ANALOGUE FREQUENCY METER by <i>Andy Flind</i>	32
Up to 1MHz measured proportionally at better than 2%	
PE RANGER 27FM Part 1 by <i>Michael Tooley B.A. and David Whitfield M.A., M.Sc.</i>	40
Introduction to our CB rig	
DRUM SYNTHESISER by <i>P. Bailey</i>	50
Provides a range of sounds from a pulse input	
AUDIO ANALYSER Part 2 by <i>Michael Tooley B.A. and David Whitfield M.A., B.Sc.</i>	68
Construction and use	

GENERAL FEATURES

SPEECH RECOGNITION SYSTEM by <i>Anthony Young</i>	28
"How 'Katrina' got Big Ears!"	
THE ELECTRONIC CAR by <i>Walter Musty</i>	36
A look at present systems and future developments	
SEMICONDUCTOR UPDATE by <i>R. W. Coles</i>	59
Featuring MC13002 GL-105XX IR-2E01	
DIGITAL DESIGN Part 2 by <i>Tom Gaskell B.A.</i>	60
Power supplies, inputs and outputs	
MICROPROMPT	74
Exchange of software and ideas	

NEWS AND COMMENT

EDITORIAL	17
NEWS & MARKET PLACE	18
Including Countdown and Points Arising	
INDUSTRY NOTEBOOK by <i>Nexus</i>	23
A sceptical view of 'YIT'	
EXTRA CASE COUPON	27
Save yourself some money on another case	
PATENTS REVIEW	35
Improved PA	
SPACEWATCH by <i>Frank W. Hyde</i>	48
Packed with information on extra-terrestrial activity	
SPECIAL OFFER—GRAPHIC EQUALISER	49
To match our Audio Analyser project	
A NEW GENERATION OF SOFTYS	73
Mike Abbott takes a look at Softy 2	

OUR OCTOBER ISSUE WILL BE ON SALE FRIDAY, 11 SEPTEMBER 1981
(for details of contents see page 31)

© IPC Magazines Limited 1981. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS. ENGLAND
Tel. Watford (0923) 40588. Telex: 8956095

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P. & R. ADD 50p TO ALL ORDERS UNDER £10.00 EXCL. VAT. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost incl. p&p.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m. - 6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: (Axial Lead Type)
400V: 1nF, 1.5n, 2n, 3n, 4n, 6n, 11p; 10n, 15n, 18n, 22p; 33n, 47n, 68n 16p;
100V: 150n, 200n; 220n 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 58p; 2µF, 4µF 85p;
160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n 38p; 1µF 42p; 1µF 45p; 2µF 48p; 4µF 58p.
1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n, 100n 50p.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10n, 15n, 22n, 27n 8p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 19p; 1µF 23p; 1µF 40p; 2µF 42p.

TRANSISTORS	BC107	35	BC214L	10	BF910	95	OC170/1	85	2N918	95	2N5457	36
	AC107	25	BC237/8	14	BF939/40	23	OC200	85	2N930	20	2N5458/9	36
	AC126	25	BC237/8	14	BF939/40	23	OC200	85	2N930	20	2N5458/9	36
	AC127/8	25	BC308B	16	BF998	105	TP129C	60	2N1303/4	65	2N5775	36
	AC141	30	BC327	15	BFX29/84	28	TP130A	48	2N1305/7	60	2N6027	32
	AC142	30	BC328	15	BFX85/86	28	TP130B	50	2N1308	68	2N6109	60
	AC176	28	BC337/8	15	BFX87/88	28	TP130C	58	2N1671B	160	2SA715	60
	AC148	28	BC344	35	BFY35/1	23	TP131A	44	2N1671A	160	2SA714	60
	AC177/18	70	BC461	34	BFY52	23	TP131C	55	2N191A	28	2SC496	70
	AC192/20	75	BC477/8	40	BFY56	32	TP132A	48	2N2220A	26	2SC1096	85
	AC192/22	75	BC516	40	BFY64	35	TP132C	60	2N2221A	26	2SC1173	125
	AD128	75	BC517	40	BFY81	120	TP133A	65	2N2222A	25	2SC1306	150
	AD159/2	79	BC547/8	14	BFY90	80	TP133C	78	2N2369A	18	2SC1307	220
	AF118	95	BC549/9	14	BFY93	100	TP134A	60	2N2454	10	2SC1449	85
	AF139	40	BC556/7	18	BSX20	20	TP134C	88	2N2460	80	2SC1678	140
	AF178	75	BC558/9	15	BSX29	34	TP135A	160	2N2904	28	2SC1923	50
	BC107	35	BCY70	16	BSY95A	28	TP135C	185	2N2905A	28	2SC1945A	225
	BC178	12	BCY71/2	20	BU105	170	TP136A	170	2N2906	26	2SC1953	90
	BC108	12	BD121	95	BU109	240	TP136C	199	2N2907	26	2SC1957	90
	BC108B	12	BD124	115	BU109	210	TP141A	15	2N2908	19	2SC1959	180
	BC108C	12	BD131/2	48	BU205	190	TP141B	60	2N3053	26	2SC2028	85
	BC109	10	BD135	60	BU206	200	TP142A	60	2N3054	58	2SC2029	180
	BC109B	12	BD136/40	40	BU207	200	TP142B	75	2N3055	48	2SC2078	155
	BC157/8	28	BD136/40	40	E421	250	TP120	90	2N3442	140	2SC2091	85
	BC140/42	30	BD137/8	20	MPD8001	90	TP141	120	2N3614	199	2SC2166	165
	BC143	30	BD144	198	MJE350	54	TP142	120	2N3615	199	2SC1679	190
	BC147	9	BD105	110	MJE370	100	TP147	120	2N3663	15	2SD234	75
	BC147B	10	BD145	45	MJE371	100	TP2955	60	2N3702/3	10	2SK45	90
	BC148	10	BD178	70	MJE520	95	TP3055	60	2N3775/5	10	3N128	112
	BC148B	10	BD179	35	MJE525	95	TP3056	32	2N3776/7	10	4011	112
	BC148C	10	BD175	75	MJE505	70	TS44/45	45	2N3708/9	10	4009	8
	BC148E	10	BD695A	99	MPF102	66	TS48	50	2N3710	10	40100	215
	BC149	9	BD696A	99	MPF103	36	TS58A	50	2N3711	10	40101	130
	BC149C	12	BD956	180	MPF104	36	TS90	30	2N3771	179	40250	85
	BC153/4	27	BD960	160	MPF105	36	TS19/193	32	2N3772	195	40251	97
	BC159	11	BF167	29	MPF106	36	TS101/2	16	2N3773	270	4031	60
	BC160	45	BF173	27	MPSA05	25	TX107/8	11	2N3819	22	40213	130
	BC167A	10	BF177	25	MPSA12	25	TX1212	28	2N3820/3	65	40316	95
	BC168C	10	BF178	30	MPSA50	30	TX300	13	2N3866	90	40317/20	60
	BC169	10	BF179	35	MPSA50	30	TX301/2	16	2N3902	16	40360	48
	BC170	15	BF180	38	MPSA70	30	TX303	25	2N3905	15	40361/62	50
	BC171/2	11	BF194/5	12	MPSU02	85	TX304	17	2N3906	17	40406	75
	BC173	11	BF196/7	12	MPSU05	85	TX314	25	2N4037	46	40407	60
	BC177/8	20	BF198	16	MPSU06	58	TX320/26	30	2N4058	10	40408	70
	BC179	20	BF199	18	MPSU52	65	TX341	30	2N4061/2	10	40411	285
	BC182/3	10	BF224	25	MPSU01	30	TX500/1	10	2N4061/2	10	40412	285
	BC184	10	BF244A	28	MPSU26	60	TX502/3	18	2N4427	80	40467	130
	BC182L	10	BF244B	28	OC28	130	TX531	25	2N4859	78	40468	85
	BC183L	10	BF256B	35	OC36	120	TX550	25	2N4871	85	40494	105
	BC184L	10	BF257B	32	OC41/42	120	TX696	30	2N5135/6	20	40495	110
	BC185	10	BF258	35	OC47	60	TX701	23	2N5136	18	40603	110
	BC187	10	BF274	42	OC45/70	40	TX698	40	2N5137	18	40604	175
	BC188	10	BF336	40	OC71/72	40	TX699	48	2N5140	45	40673	95
	BC121C	10	BF451	35	OC76	50	TX706A	19	2N5191	75	40674	95
	BC121B	10	BF452	35	OC81/82	50	TX706B	19	2N5194	80	40675	95
	BC121A	10	BF459	39	OC82/84	50	TX714/5	32	2N5305	24		

ELECTROLYTIC CAPACITORS (Values in µF): 500V: 10 52p; 47 78p; 83V: 0.47, 1.0, 1.5, 2.2, 3.3, 8p; 4.7 9p; 6.8, 10, 15, 22 12p; 33 15p; 47 12p; 100 19p; 1000 70p; 50V: 47 12p; 68 20p; 220 24p; 470 32p; 220 90p; 40V: 4.7, 15, 22, 3p; 330 90p; 4700 120p; 25V: 1.5, 6.8, 10, 22 8p; 33 9p; 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 2200 60p; 3300 76p; 4700 82p; 18V: 4.0, 4.7, 100 9p; 125 12p; 220 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 3300 74p; 4700 79p.

TAG-END TYPE: 70V: 4700 245p; 64V: 3300 198p; 2200 139p; 50V: 3300 154p; 220 110p; 40V: 4700 160p; 25V: 10,000 320p; 15,000 345p.

TANTALUM BEAD CAPACITORS:
35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 15V: 2.2, 3.3 16p; 4.7, 6.8, 10 18p; 15 36p; 22 30p; 33, 47 40p; 100 75p; 220 88p 10V: 15, 22, 26p; 33, 47 35p; 100 55p.

MYLAR FILM CAPACITORS:
100V: 1nF, 2n, 4n, 4n7, 10 6p; 15nF, 22n, 30n, 40, 47 7p; 56, 100n, 200 9p; 470n/50V: 12p.

CERAMIC CAPACITORS: (50V)
Range: 0.5pF to 10nF
100nF/30V 3p; 33nF, 47nF 5p
15nF/20V 7p; 22nF/6V 8p

POLYSTYRENE CAPACITORS:
10pF to 1nF 8p 1.5nF to 12nF 10p.

SILVER MICRA (µF)	2, 3, 4, 7, 6.8, 9, 10, 12, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180	SIEMENS multilayer miniature capacitors 250V: 1nF, 1.5n, 2n, 3n, 4n7, 6n, 8n, 10n, 12n, 15n, 22n 7p 18n, 27n, 33n, 47n 8p 39n, 56n, 68n 9p 100V: 100n, 120n, 10p 150n 11p; 220n 13p; 330n 18p; 470n 23p; 680n 30p; 1µF 34p; 2µF 50p	RESISTORS - Erie make 5% carbon Miniature High Stability, Low Noise. RANGE Val. 1-99 100+ 0-25W 202-4-M7 E24 2p 1p 0-5W 202-4-M7 E12 2p 1p 1W 202-10M E12 2p 1p 2% Metal Film 100-1M 8p 4p 1% 0-5W 51Q-1M24 8p 6p
--------------------------	--	--	--

*100+ price applies to Resistors of each type not mixed values.

LINEAR IC's	LF351	48	NE560	325	ZN425E	350	8T26A	135
555 CMOS	80 LF355	75	NE561	395	ZN426	325	8T28A	135
702	75 LF366	85	NE562B	410	ZN427	625	8T31	350
709C 8 pin	35 LM10	295	NE564	435	ZN428	478	8T95N	78p
710	48 LM301A	36	NE565A	120	ZN429	210	8T97N	73p
741	14 LM308	90	NE566	180	ZN430	200	AY-5-1015	395
747C 14 pin	18 LM309	25	NE567	180	ZN431	200	AY-5-2013	700
748C 8 pin	36 LM318	95	NE568	180	ZN432	200	AY-5-2016	350
753 8 pin	185 LM324	50	NE571	420	ZN433	270	AY-5-2017	700
810	159 LM339	68	RC4136D	69	ZN434	270	AY-5-2018	700
9400C/1	350 LM348	90	S8668	265	2101-2	110	MC1488	62
AY-1-0212	875 LM349	115	SA8320	428	2112-2	250	MC1489	62
AY-1-1313A	660 LM358	50	SA83210	275	2114-450	99	RO-3-2513U	600
AY-1-1320	225 LM379	415	SA83271	485	2114L-300n	99	SFF9636E	950
AY-1-1505	99 LM380	80	SG3402	295	2114L-200n	130	SFC71301	820
AY-1-1505	160 LM381N	145	SN76003N	240	2118-3	250	TMS52716-3V	1050
AY-1-1701	840 LM382	125	SN76018	148	2123-450n	110	TMS6027	240
AY-3-8500	30 LM390	145	SN76023N	180	2128-450n	225	TMS6041	365
AY-3-8910	770 LM386	99	SN76033N	195	2716-5V	250	Z80CPU 2.5	400
AY-3-8912	650 LM387	120	SN76115N	215	2732-450n	725	Z80ACPU 4M	550
AY-5-1224A	235 LM389	95	SN76131	125	2147	240	Z80 P10	440
AY-5-1230	450 LM393	75	SN76227N	95	2107	240	Z80 P10	440
AY-5-13								

ZERO Insertion Force DIL Sockets
24 way 650p; 28 way 820p; 40 way 975p

DIODES	AA119	15
	BA100	15
	BY126	12
	BY127	12
	CR033	250
	OA9	40
	OA7	12
	OA70	12
	OA75	15
	OA85	15
	OA90	8
	OA91	8
	OA95	8
	OA200	8
	OA202	8
	IN914	4
	IN916	5
	IN4001/2	5
	IN4003	6
	IN4004/5	6
	IN4006/7	6
	IN4148	4
	IN541	15
	IN5404	16
	IN5406	17
	IN5408	19
	IS44	9
	IS921	9
	6A/100V	50
	6A/400V	55
	6A/800V	65

SPEAKERS	80 0-3W	13
	2" 2-25"	18
	4" 2-3" 80	18
	40Q 2.5" 80	18
	64Q 2.5" 80	18
	80Q 2.5" 80	18
	8x5" 80 6W	29
	HF Cone 425	29
	Piezo Tweeters	29
	Xovers etc.	29
	available.	29

ALUM. BOXES	3x2x1"	65
	4x2x1"	85
	4x2x2"	103
	4x4x2"	120
	5x2x1"	90
	5x2x2"	130
	5x4x1"	99
	5x4x2"	120
	6x4x2"	120
	3x4x3"	80
	7x5x3"	180
	8x6x3"	210
	10x4x3"	240
	10x7x3"	275
	12x5x3"	260
	12x8x3"	295


OPTO ELECTRONICS	LEDS including Clips	13
	TIL209 Red 125"	18
	TIL211 Green 125"	18
	TIL212 Yellow	18
	TIL220 Amber	18
	0 2" Yel. Grn. Amber	18
	Red, Green and Yellow	29
	Rectangular LEDs.	29
	Triangular LEDs R&G	55
	0 2" Flashing LED Red	55
	0 2" Red/Green LED	55
	0 2" Red High Bright	59
	2N5777 45; OCPT71	120
	ORP12	86
	LD271 Infra Red (emit)	48
	TIL32 Infra Red (emit)	52
	SH205 (detector)	91
	TIL78 (detector)	54

7 Segment Displays	TIL321 5° C.An	115
	TIL322 5° C.th	115
	DL704 .3" C.Ch	99
	DL707 .3" C.Anod	99
	DL747 .6" C.Cathod.	180
	-8° Orange C.A.	250
	FND357 or 500	120
	3° Green C.A.	140
	1 1/2" Red or Green	150
	Bargraph 10 seg.	225

OPTO	2" Attractive chrome Bezel LEDs. Nut fix.	18
	Ing	18
	Red	58p
	Yellow or green	65p
	Filament & Neon Indicators. Sub-miniature matching type.	58p
	Polycarbonate Lens & body. Nut fixing.	58p
	Neons with resistors	38p
	240V Red or Amber	38p
	Filaments, avail. in Red, Green & Amber	38p
	6V/40mA, 14V/40mA, or 28V/25mA	54p
	4 digit multiplexed display. 6° - 9 segment	320p
	Red GaAsP LED	320p

SPECIAL OFFER	1+	50+
	14p	12p
	17p	14p
	99p	90p
	10x4x2"	130p
	2708	225p
	2532	725p
	2716	250p
	2732	725p
	4027	240p
	4116	99p
	4334-3	325p
	6116-3	950p

Just phone your order through, we do the rest.



ANTEX Soldering Irons

C15W 410
CK17W 410
CM15W 420
X25W 420

Spare bits 200
Elements 200
Iron stands 160

Price £39.50

WANDER MIKE

Cordless microphone attractively finished in polished chrome. Operates on FM. All you require is an FM Radio.

(Also supplied is 5 metres of Cable to operate it as conventional Mike).

Price £39.50

GAS & SMOKE DETECTORS TGSB12 813 415 Sockets 40 |

DIL SOCKETS (TEXAS)	Low profile	Wire wrap
	8 pin	8p 25p
	14 pin	10p 35p
	16 pin	10p 42p
	18 pin	16p 52p
	20 pin	22p 60p
	22 pin	25p 70p
	24 pin	25p 70p
	28 pin	28p 70p
	36 pin	28p 105p
	40 pin	30p 99p

DIL PLUGS (Headers)	14 pin	44p
	16 pin	49p
	24 pin	88p
	40 pin	285p

Ribbon Cable multicouler	10 way	22p/ft
	20 way	40p/ft

D'CONNECTORS (Cannon type)	Plugs	Sockets	Covers plastic
	9 way	95p	125p
	15 way	135p	150p
	25 way	198p	284p
	37 way	290p	398p

AMPHENOL PLUGS	IEEE	575p, Centronics//	675p
-----------------------	------	--------------------	------

WATFORD'S ULTIMATE MONITOR IC

A 4K Monitor Chip specially designed to produce the best from your: Superboard Series I & II, Enhanced Superboard & UK101.

WEMON offers these superb facilities: Full screen editing - Fully programmable Cursor control with meaningful symbols on screen - Single Key Basic - Auto remote control of tape recorder (requires only a relay) - Open line facility - Named tape files - Cursor indication of quotes mode - Auto remote list on error (Displays faulty line on carriage return) - Single command save - Centronics compatible printer driver incl. high speed cassette Save & Load.

Monitor functions include: Scrolling - list in data mode - Warm restart vector - list memory - Search memory - Floppy disc Vector - Tabular display of Memory.

Only: **£19.95 + 50p p&p.**

TRANSFORMERS (mains Prim. 220-240V)	5-0-6V 100mA; 9-0-9V 75mA; 12-0-12V 75mA	98p
	8VA type: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A 220p	
	12VA: 4-5-1.3A; 4-5V-1.3A; 6V-1.2; 6V-1.2A 12V-5A 12V-5A; 275p (30p p&p)	
	24VA: 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A; 12V-1A 12V-1A; 15-8A; 15-8A; 20V-6A 20V-6A	320p (44p p&p)
	50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-8A 30V-8A	395p (60p p&p)
	100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A	920p (60p p&p)
	(N.B. P&P charge to be added above our normal postal charge).	

BRIDGE RECTIFIERS (plastic case)	1A/50V	20
	1A/100V	22
	1A/400V	29
	1A/600V	34
	2A/50V	35
	2A/200V	40
	2A/400V	46
	2A/600V	65
	6A/100V	83
	6A/400V	95
	6A/600V	125
	10A/600V	150
	25A/200V/240	240
	25A/600V/95	240
	8Y164	56
	5VM18	50

ZENERS	7 Range. 2V7 to 400mW	15p each
	39V 400mW	15p each
	33V 15p each	15p each

VEROBOARDS 0-1"	VQ Board	150
	Clad Plain	330
	'DIP' Board	330
	Vero Strip	144
	S100 Board	£14

PROTO-DECS	Veroblock	375
	S-Dec	350
	Euroboard	520
	Bimboard 1	685
	Superstrip SS2	998

IC Test Clips DIL Gold plated contacts.	8 pin	450
	14	275
	16	290
	18	599
	20	899
	22	795
	24	845
	28	925
	36	£12
	40	£13


- COMPUTER CORNER**
- **SUPERBOARD II** Series II, New Version, Software selectable Display 24 x 24 or 48 x 12. Ready built & tested - Requires only a 5V/3A PSU to be up and running. Still only **£149**
 - **5V/5A PSU** Ready built and tested **£20**
 - **Attractive Beige/Brown ABS CASE** for Superboard/UK101 **£26**
 - **Extra 4K of RAM** (8 off 2114L-300nS) **£7.95**
 - **Space Invaders** for Superboard **£6**
 - **UK101** - New issue Computik now with new extended Monitor, at the new low price of **£149**
 - **VIDEO GENIE** - A complete system including cassette recorder. Ideal for School/Colleges. Has 16K users RAM, 12K Microsoft Basic in ROM. 64 x 16 line display. **£279**
 - **SEIKOSHA GP80A** - Unihammer Printer, gives normal and double width characters as well as dot resolution graphics 8" tractor feed. Parallel Interface standard. **£195**
 - **EPSON TX80**: A complete 80 column dot matrix printer. Available in tractor or friction feed. Pat compatible graphics. Speed 125 cps. Special offer price **£239**
 - **SOFTY-2**. As reviewed in PE September 1981. The complete microprocessor development system for Engineers & Beginners. New powerful instruction. Accepts any 24 pin 5V single rail EPROM. Supplied fully built, tested & enclosed in a black ABS case. Price incl. encapsulated plug in power supply. **£169**
 - **VIDEO MONITOR 9"** fully cased. B&W. Fully guaranteed. Excellent value for money at only **£69**
 - **TEX EPROM ERASER**. Erases up to 32 ICs in 15-30 min. **£33**
 - **TEX EPROM ERASER** with integral 30 min. Electronic timer **£45**
 - **Spare UV lamp bulbs** **£9**
 - **Full ASC11** coded keyboard type '756' **£39**
 - **NUMERIC Keypad** (Ready built) **£9**
 - **4 x 4 matrix keypad** (reed switch assembly) **£4**
 - **ASTEC UHF modulators** 6MHz **£2.80**; 8MHz wide bandwidth **£4.50**
 - **8 1/2" Fan fold paper** (500 sheets) (no VAT) **£6**
 - **9 1/2" Fan fold paper** (500 sheets) (no VAT) **£6**
 - **Teletypewriter Roll** (no VAT) **£3.50**

VOLTAGE REGULATORS	1A TO3 +ve	-ve
	5V 7805 145p	7805 220p
	12V 7812 145p	7812 220p
	15V 7815 145p	7815 220p
	18V 7818 150p	-
	1A TO220 Plastic Casing	-
	5V 7805 50p	7805 58p
	12V 7812 50p	7812 58p
	15V 7815 50p	7815 55p
	18V 7818 50p	7818 55p
	24V 7824 50p	-
	100mA TO92 Plastic Casing	-
	5V 78L05 30p	78L05 65p
	8V 78L02 30p	-
	8V 78L02 30p	-
	12V 78L12 30p	78L12 65p
	15V 78L15 30p	78L15 65p

SWITCHES	TOGGLE 2A	33
	1A DPDT	14
	1A DPDT C/OFF	15
	1A DP on/on/off	40
	4 pole on off	54

WATFORD'S BOOKSHOP CORNER	Texas TTL Data Book (Revised Edition)	P 5
	Personal Computer Book	630
	Illustrating BASIC	390
	BASIC with Style	530
	A Bit of BASIC	540
	Basic Programme Primer	750
	Programming in Basic for Business	810
	Basic & the Personal Computer	1100
	Basic Handbook - 2e	1250
	Advanced BASIC	750
	BASIC Computer Games	550
	More BASIC Computer Games	550
	Some Common BASIC Programs	1150
	Practical BASIC Programs	1250
	6502 Software Design	900
	6502 Application Book	960
	Programming the 6502 (C202)	1050
	Programming & Interfacing the 6502	1100
	6502 Assembly Language Programming	1350
	6800 Assembly Language Programming	1100
	6809 Assembly Language Programming	1390
	Practical Intro to PASCAL	500
	Using CP/M: A self teaching guide	740
	8080A/8085 Assembly Lang. Programming	1250
	Z80 Instruction Handbook	390
	Z80/Z80 Assembly Lang. Programming	650
	Z80 Microcomputer Handbook	750
	8080/Z80 Assembly Lang. Techniques	840
	Programming the Z80 (C280)	1060
	Z80 Assembly Language Programming	1350
	Intro to TRS-80 Graphics	690
	TRS80 BASIC - A self teaching guide	720
	ZX80 Pocket Book	520
	30 programs for the Sinclair ZX80	700
	Making the most of your ZX80	790
	32 BASIC Programs for PET Computer	1250
	PET and the IEEE 488 Bus (GP1B)	1100
	PET Graphics	1000

Right first time.

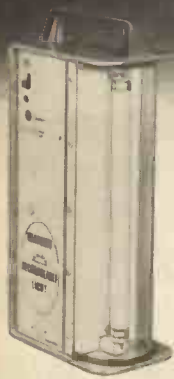

Portable VOM

Rechargeable Light

If you've never built a kit before, Heathkit have some very pleasant surprises for you. Their kits are easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need is there.

Follow the steps and you'll end up with a hand-crafted, well designed piece of equipment. Much better than shop bought, mass-produced. Because you built it yourself.



Digital Clock

There's a great range of kits to start you off. From a buzzer alarm to a digital electronic clock, or a portable rechargeable fluorescent light to a portable VOM.

With all this going for you, you can count yourself very lucky you started off with Heathkit. Because all first time kit builders will get a free soldering iron and 10% discount off ten selected kits.




Buzzer Alarm

To: Heath Electronics (UK) Limited, Dept (PE9), Bristol Road, Gloucester GL2 6EE.

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name _____


Address _____

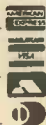

You build on our experience



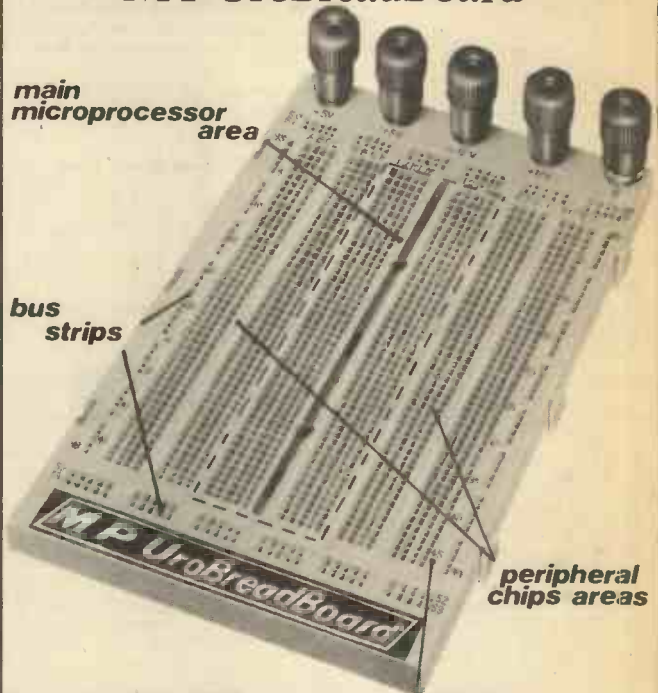If you're into
MICROPROCESSORS
then they should be into an
MP UroBreadBoard



alpha numeric indexing

- * MPU Section accepts 24, 28, 40 & 64 pin DIL microprocessors
- * Auxiliary Areas accept any .3" or .6" RAM, ROM or peripheral chip
- * Power Bus Strips on all sides
- * 5 incoming turret Power Terminals
- * Component Support Bracket included
- * Over 1400 contact points
- * Alpha-Numeric column and row indexing
- * Eurocard size (160mm x 100mm)
- * Slots onto all BIMBOARDS
- * Non-Slip rubber backing
- * Ideal for schools and colleges
- * Long life, <10m.ohms, nickel silver contacts

The PROFESSIONALS breadboard that BEGINNERS can start on

BOSS INDUSTRIAL MOULDINGS LTD

2 Herne Hill Rd, London SE24 0AU, England
Telephone 01-737 2383 Telex 919693
Cables & Telegrams: LITZEN LONDON SE24

Please send me MPUroBreadBoard(s) at £18.00

This price includes VAT & PP, is applicable from March 1981 but please add 15% for Overseas Orders, make cheques/P.O. payable to BOSS Industrial Mouldings Ltd and allow 10 days for order processing and cheque clearance etc.

I enclose a cheque/P.O. to the value of £.....

Name
Company
Address
.....
Telephone Number PE 9

CHROMASONIC electronics

DEPT P.E. 48 JUNCTION ROAD, ARCHWAY, LONDON N19 5RD

TELEPHONE 01-263 9493 01-263 9495

100 YDS FROM ARCHWAY STATION & 9 BUS ROUTES

YOUR SOUNDEST CONNECTION IN THE WORLD OF COMPUTERS

PET



4008 8K RAM
4016 16K RAM
4032 32K RAM
4040 Dual Drive Disk

4022 80 column tracks feed.
3023 80 column friction feed.
C2N Cassette Unit.

For the business man we stock the 8000 range inc. 8032 and 8050 with daisy wheel printers coming soon.

PHONE FOR MOST COMPETITIVE PRICES
WORD PROCESSING AND 32K SYSTEMS
PHONE FOR DETAILS

VIDEO GENIE



£279 EG3003

Utilises Z80, 12K level II Basic, Integral Cassette Deck, UHF O/P, 16K RAM, all TRS80 features. Simply plugs into monitor or UHF TV. With V.U. Meter.

PARALLEL PRINTER INTERFACE INC. CABLE.....£33.00
CHROMASONICS PROGRAMMABLE SOUND KIT.....£24.95
SOUND KIT (FITTING EXTRA).....£7.00
LOWER CASE KIT (FITTING EXTRA).....£27.50
COLOUR KIT (FITTING EXTRA).....£34.95
EXPANSION BOX WITH/WITHOUT RS232.....£215/£185
16K/32K RAM CARD.....£94/£129

APPLE

APPLE II PLUS

Complete Systems

48K Machines

Disk Drive with Controller £349.00

Disk Drive without Controller £285.00


Colour Card P.O.A.

Graphics Tablet P.O.A.


Accessory Cards, Software

All Available - Phone for details.

Apple II plus

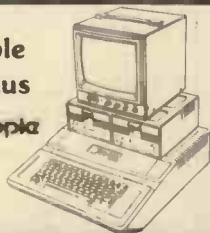

PRINTERS

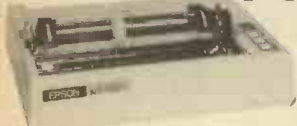

EPSON MX80 £359

Dot-matrix printer with Pet graphics interface. Centronics parallel and serial. Pet and Apple compatible. True bidirectional, 80 cps.

EPSON MX80 FT/1 £399

Dual single sheet friction and tractor, 9 wire head, true descenders.

Interfaces and Cables for APPLE II, PET, TRS80, RS 232, UK101, SHARP SUPERBOARD All Available
EPSON MX80 FT/2 £449
An FT/1 with high resolution graphics.
EPSON MX70 £259

Tractor feed, 7 wire head high resolution graphics.

SEIKOSHA GP80A £199

Dot matrix 5 x 7, 80 columns 30 cps. graphics, double width characters.

JUST PHONE FOR FURTHER DETAILS

MONITORS

MON 10" (illust) B&W £82.00

9" Green Monitor £98.00

Hitachi professional monitors

9" Black & White £99.95

12" Black & White £149.00



UK101

DOWN IN PRICE

UK 101 Kit inc. 8K Memory £125

Ready Built inc. 8K Memory £175

Complete in case £199

4K Expansion 8x2114 £14

Memory Expansion Kit

8K £79.95

16K £106.95

Printer Interface £29.95

Sound generator plus P10 Kit £29.95

Cases £24.50

NEW

Chromasonics Sound Kit £24.95

Colour Kit £84.95

Inc. Demo Tape & Full Documentation. Send for details.

VIC 20

Colours

24 total. 8 for characters, 8 for border, 16 for screen mixed as you wish. Basic colours on program keys are black, white, red, blue, light blue, green, yellow, and purple.

Sound

3 Tone Generator for music
"White Noise" Generator for language and sound effects.
Each Generator gives 3 octaves.
Reproduction is through tv speaker.

Character/Line Display

22 Characters by 23 lines
64 ASCII characters, pet-type graphic character set.

Keyboard

DIN typewriter keyboard with 8 programmable function possibilities via 4 special function keys. Colours are directly addressable from the keyboard.

Peripherals/Accessories

VIC Datasheet with special interface to guarantee high reliability read/write quality (PET/CBM compatible).

VIC 1515 - Low cost VIC DOT Matrix printer

VIC 1540 - Single disk unit with 170k Byte capacity.

Price only £165 cassette deck £34.95

V
I
C
2
0



TANTEL

PRESTEL BY TANTEL
COMMUNICATION AT YOUR FINGER TIPS FOR
BUSINESS & HOME. UP TO DATE INFO

180,000 pages of information on Travel, News, Investment, Holidays, Hotels Etc., Etc.

£170

TANTEL IS POST OFFICE APPROVED. SEND FOR DETAILS.
DEMONSTRATION AVAILABLE AT OUR SHOWROOM.



Please add VAT 15% to all prices. Postage on computers, printers and cassette decks charged at cost, all other items, P&P 30p. Place your order using your Access or Barclaycard (Min. tel order £5). Trade and export enquiries welcome. Official orders welcome.



D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFECTS



PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY
PRINTED CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE
MARKET

P.E. MINISONIC MK2 SYNTHESISER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant synthesiser the functions offered by this design give it great scope and versatility. 3 Oct KBD & GJ contacts needed.

Set of basic component kits (excl. KBD R's & tuning pots - see list for options available) and PCBs (incl. layout charts)
KIT 38-25 £80.14

"Sound Design" booklet
Knobs, skts, sw's
TEXT 101 £1.00
See our list

P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. 4 Oct KBD and GJ contacts needed.

Set of basic comps, PCBs and charts
KIT 76-7 £35.56
Set of text photocopies
TEXT 76 £1.36
Knobs, skts, sw's
HW 76 £6.62

P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the panel controls and fed into most voltage controlled synthesisers.

Set of basic comps, PCBs and charts
KIT 86-5 £32.10
Set of text photocopies
TEXT 86 £1.84
Knobs, sets, sw's
HW 86 £11.15

P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser.
Set of basic comps, PCBs & charts
KIT 77-8 £109.72

ELEKTOR CHOROSYNTH

A 2½-octave Chorus synthesiser with an amazing variety of sounds ranging from violin to cello and flute to clarinet amongst many others. Experienced constructors can readily extend the octave coverage. 3 Oct KBD and GJ contacts needed.

Basic comps, PCBs and charts
KIT 100-8 £44.39
Text photocopy
TEXT 100 70p
Knobs, skts, sw's
HW 100 £11.55

ELEKTOR FORMANT SYNTHESISER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic comps, PCBs (as publ.)
KIT 66-14 £255.45
Set of text photocopies
TEXT 66 £7.83
Knobs, skts, sw's
See our list

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90mS can be extended up to 450mS using the extension unit. Further delays can be obtained using more extensions.

Main unit basic comps and PCB (as publ.)
KIT 78-3 £49.95
Extension unit comps and PCB
KIT 78-4 £39.95
Text photocopy
TEXT 78 86p
Knobs, skts, sw's
HW 78 £2.94

ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100mS, and the additional set extends this up to 200mS. May be used in either mono or stereo mode.

Main unit basic component set
KIT 83-4 £29.23
Additional Delay basic components
KIT 83-2 £20.07
PCB (as publ.) to hold both kits included in Kit 83-4
Text photocopy
TEXT 83 67p
Knobs, skts, switch
HW 83 £2.84

ELEKTOR SEWAR

For use with Elektor Analogue Reverb to give greater flexibility to the reverb effects.

Basic comps, PCB (as publ.)
KIT 101-1 £18.19
Text photocopy
TEXT 101 60p
Knobs, skts, switch
HW 101 £2.44

BASIC COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".



NEW KITS

EE 3-CHAN STEREO MIXER

Full level control on left and right of each channel, and with master output control and headphone monitor.

Basic comps, PCB & chart
KIT 107-1 £8.61
Text photocopy
TEXT 108 65p
Knobs, skts & sw's
HW 107 £3.19

3-MICROPHONE STEREO MIXER

Enables stereo live recordings to be made without the 'hole in the middle' effect. Independent control of each microphone.

Basic comps, PCB & chart
KIT 108-1 £5.41
Text photocopy
TEXT 108 55p
Knobs, skts, & sw's
HW-108 £2.55

E.E. HEADPHONE AMPLIFIER

For use with magnetic, ceramic or crystal pick-ups, tapedeck or tuner, and for most headphones. Designed with RIAA equalisation.

Basic comps, PCB & chart
KIT 104-1 £9.79
Text photocopy
TEXT 104 85p
Knobs, & sockets
HW 104 £2.50

E.E. AUDIO EFFECTS UNIT

A variable siren generator that can produce British & American police sirens, Star Trek, Red Alert, heart-beat monitor sounds, etc.

Basic comps, PCB & chart
KIT 105-1 £4.87
Text photocopy
TEXT 105 65p
Knobs, skts & switch
HW 105 £1.91

GUITAR PRACTISE AMPLIFIER

A 3 watt mains powered amplifier suitable for instrument practise or as a test gear monitor. Drives 8 or 15 ohm loudspeaker.

Basic comps, PCB & chart
KIT 106-1 £9.81
Text photocopy
TEXT 106 65p
Knobs, skts, switch
HW 106 £2.02

SIGNAL TRACER & GENERATOR

Allows audio signals to be injected into circuits under test, and for tracing their continuity. Includes frequency & level controls.

Basic comps, PCB & chart
KIT 109-1 £5.80
Text photocopy
TEXT 109 55p
Knobs, skts, sw's & probes
HW 109 £3.17

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic comps, PCB & chart
KIT 75-1 £6.99
Text photocopy
TEXT 75 38p
Knobs & sets
HW75 91p

P.E. AUTO-WAH UNIT

Automatically give Wah or Swell sounds with each note played.

Basic comps, PCB & chart
KIT 58-1 £10.11
Text photocopy
TEXT 58 58p
Knobs & skts
HW58 £1.26

ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sine-wave, mark-space saw-tooth, regular triangle, or square-wave with variable mark-space.

Basic comps, PCB & chart, but excl. sw's
KIT 67-1 £9.24
Knobs, skts, sw's
HW 67 £4.23

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.

Basic comps, PCB & chart
KIT 89-1 £4.34
Text photocopy
TEXT 89 78p
Knobs, skts, sw's
HW 89 £1.89

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic comps & PCB (as publ.)
KIT 87-2 £6.84
Text photocopy
TEXT 87 38p
Knob, skt
HW 87 75p

ELEKTOR FUNNY TALKER

Incorporates a ring modulator, chopper & frequency modulator to produce fascinating sounds when used with speech & music.

Basic comps, PCB (as publ.)
KIT 99-1 £9.60
Text photocopy
TEXT 99 40p
Knobs & skts
HW 99 £1.22

ELEKTOR FREQUENCY DOUBLER

For use with guitars & other electronic instruments to produce an output one octave higher than the input. Inputs and outputs may be mixed to give greater depth.

Basic comps, PCB (as publ.)
KIT 98-1 £5.48
Text photocopy
TEXT 98 20p
Knobs & skts
HW 98 £1.24

P.E. SPLIT-PHASE TREMOLO

A simple but effective substitute for a rotary cabinet. The output of an internal generator is phase-split and modulated by an input signal from an electronic guitar or other instrument. Output amplitudes, depth & rate are variable. May be fed to one or two amplifiers.

Basic comps, PCB & chart
KIT 101-3 £17.68
Text photocopy
TEXT 102 65p
Knobs & skts
HW 102 £2.53

P.E. MINISONIC WAVEFORM CONVERTER

A simple converter that modifies the Minisonic sawtooth waveform to produce triangle and sine outputs. Ideally one should be used with each Minisonic VCO.

Basic comps, PCB & chart
KIT 96-1 £3.98
Knob, skts, switch
HW 96 99p

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Basic comps, PCB & charts (excl. SWs)
KIT 85-5 £49.23
Set of text photocopies
TEXT 85 £2.52
See our list

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic comps, PCB & chart
KIT 88-1 £10.91
2-Notch extension, PCB & chart
KIT 88-2 £6.36
Text photocopy
TEXT 88 68p
Knobs, skts, switch
HW 88 £1.63

ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato. Slightly modified to also include a 2-input mixer stage.

Set of basic comps, PCB & chart
KIT 70-2 £21.67
Text photocopy
TEXT 70 67p
Knobs, skts, sw's
HW 70 £3.27

P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic comps, PCB & chart
KIT 42-4 £7.68
Text photocopy
TEXT 42 28p
Knobs & skts
HW 42 £1.85

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic comps, PCB & chart
KIT 56-3 £11.22
Text photocopy
TEXT 56 68p
Knobs & skts
HW 56 £2.29

P.E. SMOOTH FUZZ

Basic comps, PCB & chart
KIT 91-1 £6.52
Text photocopy
TEXT 91 55p
Knobs & skts
HW 91 £1.22

**WE ALSO SELL
COMPONENTS
ASK FOR OUR LIST**

ADD: POST & HANDLING

U.K. orders: Keyboards add £2.70 each. Other goods: Under £5 add 50p, under £20 add 75p, over £20 add £1. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata Insurance must be added for credit card orders.
N. B. Eire, C.I., B.F.P.O and other countries are subject to higher export postage rates.

ADD 15% VAT

(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

EXPORT ORDERS ARE WELCOME

but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by International Money Order or through an English Bank. To obtain list - Europe send 50p, other countries send £1.00.
Note that we do not offer a C.O.D. service and that our terms are payment in advance.

PHONOSONICS · DEPT PE16 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.W.O., MAIL ORDER OR COLLECTION
BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 50p; other countries—send £1.00.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

KIMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) £25.50 4 Octave (49 notes) £32.25 5 Octave (61 notes) £39.75

CONTACT ASSEMBLIES (gold-clad wire) — 1 required for each K&D note:
Type GJ — SPCO 33p ea. Type GB — 2 pr N/O 37½p ea.

P.E. 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances

Basic comps & PCB's

KIT 90-8 £56.43

Extra 2-channel set with PCB

KIT 90-9 £10.21

Set of Text photocopies

TEXT 90 £1.50

Knob, skts, sw's See our list

RHYTHM GENERATORS

Several available, including programmable 16 beat 64000 pattern, and pre-programmed 15 pattern using either M252 or M253 rhythm chips. A selection of effects Instruments circuits is also available.

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.

Basic comps, PCB & chart KIT 28-1 £4.84

Text photocopy TEXT 28 28p

Knob, skts, sw's HW 28 £1.65

P.E. ENVELOPE SHAPER WITH VCA

Has an integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.

Basic comps, PCB & chart KIT 50-1 £8.03

Text photocopy TEXT 50 58p

Knobs, skts HW50 £1.32

P.E. TRANSIENT GENERATOR

An ADSR envelope shaper without VCA, and additionally providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.

Basic comps, PCB & chart KIT 63-2 £7.62

Text photocopy TEXT 63 58p

Knobs, skts HW63 £1.82

P.E. EXTERNAL-INPUT SYNTHESISER-INTERFACE

Allows external inputs such as guitars, microphone etc., to be processed by synthesiser circuits.

Basic comps, PCB & chart KIT 81-1 £3.90

Knobs, sets HW 81 £1.18

P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic comps, incl. power supply,

PCBs & charts KIT 46-3 £23.32

Text photocopy TEXT 46 97p

Knobs, skts, sw's HW 46 £2.89

P.E. TUNING INDICATOR

A simple octave frequency comparator for use with synthesisers and other instruments where the full versatility of KIT 46 is not required.

Basic comps, PCB & chart KIT 69-1 £8.19

Text photocopy TEXT 69 58p

Knobs, skts, sw's HW 69 £1.56

DIGITAL EXPOSURE UNIT

Controls up to 750 watts in ½ second steps up to 10 minutes, with built-in audio alarm.

Basic comps, PCBs KIT 93-3 £23.45

Text photocopy TEXT 93 £1.20

Knobs, skts HW 93 £2.48

P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic comps, PCB & chart KIT 57-3 £19.37

Text photocopy TEXT 57 78p

Knobs, skts, sw's HW 57 £7.30

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 4-digit counter for 1Hz to 99kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Basic comps, PCB & chart KIT 79-4 £31.61

Text photocopy TEXT 79 78p

Knobs, skts, sw's HW 79 £4.67

P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover — particularly useful for discos.

Basic comps, PCB & chart KIT 30-1 £4.37

Text photocopy TEXT 30 28p

Skts HW 30 32p

P.E. DYNAMIC NOISE LIMITER

Very effective stereo circuit for reducing the hiss found in most tape recordings.

Basic comps, PCB & chart KIT 97-1 £8.07

Text photocopy TEXT 97 75p

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Basic comps, PCB & chart KIT 62-1 £5.31

Skts HW 62 44p

ALL KITS INCLUDE SPECIALLY DESIGNED PRINTED CIRCUIT BOARDS

MORE KITS AND COMPONENTS ARE IN OUR LISTS

PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONOSONICS

Put your ideas in our box.

Meet the Idea Box. The shortest distance between idea and working prototype or one-of-a-kind instrument.

It's a great time-saver! You design the circuit, we provide the power supplies... assembled and tested... and the right case to house it all.

The Idea Box comes complete with three highly regulated low-ripple power supplies (fixed 5VDC @ 1A; + and -15VDC, variable, @0.5A). Plus your choice of a solderless breadboard, a pre-etched, pre-drilled PCB which emulates the hole connection of the solderless breadboard's pattern,

or a blank foil board you can use for existing PCB designs. All housed in our attractive, high-impact case (4"H x 10"W x 7"D), complete with aluminum front panel and hardware. Priced from £79.75.

The Idea Box has the capacity for big ideas as well as small ones. You can stack any of the three circuit cards, in any combination.

So, before you tackle your next project, get a head start with a little help from us — have an Idea Box on hand. After all, good ideas shouldn't be kept waiting.



GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 5Q
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682.
Telex: 817477.

For further information, and your FREE catalogue fill in this coupon NOW and return to:

G.S.C. (UK) Ltd., Dept. 5Q
Unit 1, Shire Hill Industrial Estate, Saffron Walden,
Essex CB11 3AQ.

NAME _____

ADDRESS _____




CUBE MANIA - FREE OF CHARGE

With purchases totalling over £17.50. Only on request at time of ordering. Offer closes 31/8/81. Subject to availability.

BECOME AN INSTANT MUSICIAN NO EXPERIENCE NECESSARY

The success story of 1981. Hundreds sold already! As featured on "Tomorrow's World"

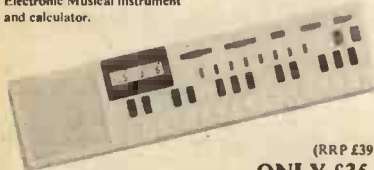Create your own music with a VL-TONE. You combine the sound, rhythm and tempo and the VL-1 plays it back... beautifully! CASIO VL-TONE (VL-1) Electronic Musical Instrument and calculator.




(RRP £39.95) ONLY £35.95

VL-1 records and plays back up to 100 notes as a melody. One Key Play or Auto Play of Piano, Violin, Flute, Guitar and Fantasy, or create your own unique sounds with A.D.S.R. 10 built-in Auto Rhythms and Tempo control. LCD digital readout of notes and tempo. Also a calculator. Battery powered with memory and program retention. Integral amplifier/speaker. Output jack. With Song Book. Dims: 1 1/4 x 1 1/4 x 3".

CASIOTONE POLYPHONIC KEYBOARDS

With built-in amplifier and loudspeaker

MT-30

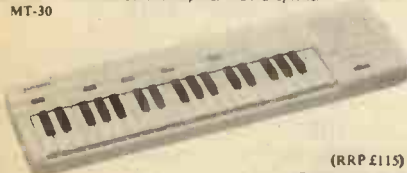

(RRP £115) ONLY £95

22 instruments over 3 octaves. 4-position sound memory. Battery or mains. O/P jack. Dims: 2 1/4 x 22 1/2 x 6 1/4". 6lb.

*** NEW *** CASIOTONE CT-202

"Son of success... The two harpsichords demonstrate the Casiotone's talent for sparkling, crystal clear tones... Even more impressive is the clav... (Melody Maker).



(RRP £325) ONLY £275

49 instruments over 4 octaves. 4 voice memory function with push button selection. 3 vibrato settings and sustain. Pitch control. O/P jacks. AC only. 3 1/2 x 34 x 11 3/16". 15.8lbs.

CT-301



(RRP £285) ONLY £245

14 instruments over 4 octaves. 8x2 rhythm accompaniments. Vibrato and delayed vibrato. Start/stop, synchro start, tempo control, tempo indicator, and rhythm volume. Pitch control. AC only. O/P jacks. 4 1/2 x 31 1/2 x 12 1/2". 27lbs.

CT-401



(RRP £345) ONLY £295

As 301 plus following: 16 rhythm accompaniments, will fill-in. Casio Auto Chord for one finger or auto accompaniment. Plays major, minor and 7th chords with bass. Balance control, C.A.C. lever, chord lever, memory lever and octave switch. Dims as 301. Weight 28.2lbs.



CASIO'S POWERFUL NEW PROGRAMMABLE THE VERSATILE FX602P (RRP £84.94) ONLY £74.95

- LCD alpha/numeric (dot matrix) scrolling display.
- Variable range of input capacity from 32 program steps with 88 independent memories to 512 steps with 22 memories.
- Memory and program retention when switched off.
- Up to 10 pairs of unconditional jumps (GOTO). Manual Jump.
- Conditional jumps and count jumps.
- Up to 9 subroutines, up to 9 depths (levels).
- 50 built-in functions, all usable in programs.
- 33 parentheses at 11 levels.
- An almost infinite number of programs can be stored on cassette tape via optional FA-1 adapter. (Price £19.95).
- Two lithium batteries last approx. 660 hours (continuous) with Auto Power Off after approx. 6 minutes non-use.
- Dims: 9.6x7.1x1.41.2mm (3/8x2 1/2x5/8"). Wallet.

CASIO SCIENTIFICS

With liquid crystal display for long battery life

*** NEW MODELS ***

FX5 Junior scientific with fractions, square roots, cube roots, squares, reciprocals, pi, three pairs of parentheses etc. (RRP £10.95) £8.95

FX7 Similar to above plus trigs. (RRP £12.95) £10.95

NEW FX550. Top of the range



FX550. 10 digits. 50 scientific functions. One lithium battery lasts 13,000 hours. Auto power off facility. 2 1/4 x 5 1/2" (RRP £21.95) £19.95



FX100. 10d, 44f, 7,500 hours from 2x AA batteries. APO 1/2 x 3 x 5 1/2" (RRP £18.95) £16.95



FX81. 8d, 30f, 4,000 hours (2x AA) APO (RRP £14.95) £12.95

SUPER SCIENTIFICS WITH TIME DIMENSION

FX8100. 46f. Clock, calendar, alarm, hourly chimes, countdown alarm, stopwatch. 2 1/2 x 5 1/2" (RRP £27.95) £24.95

FX6100. 39f. Hand held version without calendar. £17.95

CASIO PROGRAMMABLES

With APO and memory and program retention



FX2700P. 8+2d, 50f. 38 functional steps. Wallet (RRP £17.95) £17.95



FX180P. 10+2d, 55f. 38 functional steps. 2 programs. Integrals. Regressional Analysis 1/2 x 3 x 5 1/2" £19.95



FX3500P. Wallet version. 61f. 9/32 x 2 1/2 x 5 1/2" £22.95

SPECIAL OFFER while stocks last
FX502P+ Masterpack software kit ONLY £59.95
FX502P Masterpack only. (RRP £17.95) £7.50 to clear


MELODY ALARM CLOCK CALCULATORS £14.95

BQ1100 Biorythm calculating alarm clock £16.95

Digital Space Invader Game Calculators from £10.95

SYMPHONIC ALARM CLOCK MA-1 £9.95

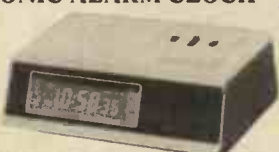Mozart No 40 or buzzer. Hourly chimes. Snooze facility. 1 1/2 x 4 1/2 x 3".



ILLUSTRATED CATALOGUE 20p

SUPER BARGAIN!

Casio's most amazing watch ever has been so successful we are able to reduce the price still further to

£19.95

CA90 (left) NOW ONLY £19.95



CA901 (right) £29.95

Time and auto calendar, calculator, alarm, hourly chimes, stopwatch, dual time. DIGITAL SPACE INVADER GAME.

100 METRE WATER RESISTANT watches with alarm and stopwatch



W150 £32.50



W150C £25.95



W100 £19.95

Time and auto calendar, alarm, hourly chimes, countdown alarm timer with repeat memory function, stopwatch. Time is always on display, regardless of mode. W-150, all stainless steel. W150C, s/s, resin strap. W100, resin case/strap.

OTHER BEST SELLING MODELS

With alarm, hourly chimes, stopwatch and calendar



UC50W £19.95



M12 £17.95



AA81 £29.95

UC50W, 50 metre water resistant. Universal full month calendar display with forward/backward stepping. S/s.

M12, 7 Daily melodies, one for each day. 3 anniversary melodies, 2 date memories, hourly chimes, countdown alarm timer with countup after zero, or stopwatch. Resin. £29.95

M1200. As above but s/s case and bracelet. £29.95

AA81, LCD digi/ana with amazing "starburst" display. Dual time (analogue and digital), alarm, hourly chimes countdown alarm timer, stopwatch, auto calendar.

AA81 Chrome £29.95

AA82 s/s £39.95

AA81G gold £49.95

RESIN SPORTS WATCHES

F5 Time and calendar display £6.95

F500 As above plus professional stopwatch £8.95

F81 Also has alarm and hourly chimes £10.95

PRICE includes VAT and P&P. Send cheques, P.O. or phone your ACCESS or BARCLAYCARD number to:


TEMPUS

Dept. PE, FREEPOST, 164-167 East Road, Cambridge CB1 1DB Tel. 0223 312866

ATOM OWNERS LOOK OUT

There are DODGEMS about!

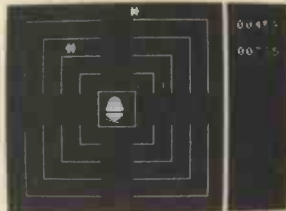Dodgems is just one of the brand new games packs from Acorn, the manufacturers of your Atom. You have to steer your car around the lanes collecting points. But beware! There's a computer controlled car programmed on a collision course. If you survive the game gets faster. Also in Games Pack 6 are Simon and Amoeba.



GET THE BEST—FORGET THE REST

All Acornsoft games are designed and produced by the manufacturers of the Atom. Trust the manufacturer to get the very best out of his product. Realistic sound effects, great graphics and colour too!

GAMES PACK 1

Asteroids Shoot them before they crash into you. Lists ten best scores. Program 4K, graphics 6K.

Sub Hunt Command a destroyer tracking a submarine, find its position and destroy it. Program 1K, graphics ½K, needs floating-point.

Breakout Score points knocking bricks from wall. Ball has two changes of angle and speed. Program 3K, graphics 1-2K. COLOUR

GAMES PACK 3

Rat Trap Move your rats without colliding with the trails left. Entangle your opponent before he entangles you! High-speed rat action-replay. Program 4K, graphics 6K.

Lunar Lander Land a spacecraft on a lunar crater; altitude velocity, fuel and drift. Program 1K, graphics ½K.

Black Box Deduce the position of four invisible objects in the Black Box by firing rays at them. Program 4K, graphics ½K.

GAMES PACK 4

Star Trek Classic computer game; rid the universe of Klingons. Short and long-range scans, galactic map, phasers, photon torpedoes, shields etc. Program 5K, graphics 2K.

Four Row Take turns in placing marbles on the board; the first to get a line of four wins. Program 5K, graphics 6K. COLOUR

Space Attack Repel the invasions of earth and avoid being hit by the gunner ships. Becomes progressively harder with each invasion. Program 3K, graphics 6K.

GAMES PACK 7

Green Things An alien life-form has invaded your space-craft; discover a way of destroying it with the weapons available on the ship. Program 5K, graphics 2K. COLOUR

Ballistics Take turns in firing shells at the other player, taking into account the wind and shape of the hill. Program 3K, graphics 6K, needs floating-point.

Snake Grow yourself a snake by guiding it towards digits which it eats. Program 2K, graphics ½K.

GAMES PACK 2

Dogfight Two-player game; each player controls a plane and tries to shoot down his opponent without crashing. Program 4K, graphics 6K.

Mastermind Guess the computer's code before the computer guesses yours; program 3K, graphics ½K. **Zombie Land** on Zombie island; try to lure all the zombies into the swamp. In desperation jump into hyper-space! Program 3K, graphics ½K. COLOUR



GAMES PACK 5

Invaders The most popular video game, with invaders, flying saucers, shelters, and full sound effects. Program 5K, graphics 6K.

Wumpus Wander in caves inhabited by the Wumpus. Find and shoot him before he eats you. Pits and bats make things harder. Program 2K, graphics ½K.

Reversi Reversi, or Othello played with counters that are black one side and white on the other; Program 3K, graphics ½K. COLOUR



ORDER TODAY!

Just send a cheque or money order. Only £11.50 per pack including VAT and post and packing. State which packs you want.

Or ring 0223 316039 or 01-930 1614 quoting your Access or Barclaycard number. Allow 14 days for delivery.

Or if you think you can wait for more details just write to

Acornsoft Limited, 4a Market Hill, Cambridge.

ACORNSOFT TAKE GAMES SERIOUSLY

BB for CB

CASH & CARRY

MAIL ORDER

BASE
ANTENNAS

MOBILE
ANTENNAS

TRADE

WHOLESALE

POWER
SUPPLIES

POWER
MIKES

PA-SPEAKERS

COAXIAL CABLE

SWR METERS

CONNECTORS

OPENING HOURS
MON-FRI 9.30 am-7 pm
SUNDAY 9.30-2 pm
by appointment

NO PARKING PROBLEMS
COFFEE AVAILABLE
ON THE HOUSE

SEND FOR OUR LATEST TRADE PRICE LIST

MINIMUM ORDER £100

B. BAMBER ELECTRONICS

COMMUNICATIONS HOUSE
5 STATION ROAD - LITTLEPORT -
CAMBS. TEL: ELY (0353) 860185

THE TELECOMMUNICATIONS SPECIALISTS



INTERESTED IN ELECTRONICS?

TRY A ZEDPACK! COMPONENTS AT A PRICE EVERYONE CAN AFFORD

- Z1 300 mixed 1 and ½ watt resistors £1-95
- Z2 150 mixed 1 and 2 watt resistors £1-50
- Z3 300 mixed capacitors, most types £3-95
- Z4 100 mixed electrolytics £2-20
- Z5 100 mixed polystyrene caps £2-20
- Z6 300 mixed printed circuit components £1-95
- Z7 300 mixed printed circuit resistors £1-45
- Z9 100 mixed miniature ceramic and plate caps £1-20
- Z10 25 assorted pots. £1-50
- Z11 25 assorted presets, skeleton etc. £1
- Z12 20 assorted vdr's and thermistors £1-20
- Z13 11b mixed hardware. Nuts, bolts self-tappers, sleeving, etc. £1-20
- Z14 100 mixed, new and marked, full spec. transistors. Pack includes:- BC148, BF154, BF274, BC212L, BC238, BC184L, PBC108 and, or lots of similar types £4-95
- Z15 100 mixed diodes including:-zener, power, bridge, signal, germanium, silicon etc. All full spec. £4-95
- Z16 20 1N4148 £1
- Z17 20 1N4003/10D2 £1
- Z18 20 assorted zeners, 1 watt and 400mw £1-50
- Z19 12 -125' TIL 209 RED. LED'S £1
- Z20 10 Assorted switches, including push button, slide, multipole, miniature etc. Fantastic value. £1-20.

UHF MODULATORS

Video In UHF out. Calibrated to channel 36 (625 line UHF) housed in metal box 2 1/2" x 2" x 1 1/2" with 9' coaxial lead, TV plug and connection data. £2-50 ea. 3 for £8. Aluminium finish slider knobs, standard fitting. 10 for £1

200µA Miniature level/batt. meters, as fitted to many cassette recorders. 90p

Deluxe FIBREGLASS printed circuit etching kits. Includes 100 sq ins. of copperclad F/G board, 1lb ferric chloride, (made for U.S. army to MIL, SPEC.), 1 dalo etch resist pen, abrasive cleaner, tweezers, etch resist dish and instructions. OUR PRICE £5-95

1lb of FeCl. £2-25.

- 150 sq. ins. single sided board. £2-20
- 150 sq. ins. double sided board. £3-30
- 100 Miniature reed switches. £2-30
- 100 Subminiature Reed Switches. £4-20

- SMALL MAGNETS 6 for £1
- With holes for SWITCH BANKS
- These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole c/o etc. Can be modified. Can't be repeated, 3 Banks for £1, KNOBS for Switch Banks 10 for £1. Chrome or spun aluminium finish.
- MINIATURE MAINS TRANSFORMERS
- Top quality. Split bobbin construction will give 4-5V-0-4-5V at 250MA, 1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. ONLY £1
- 3 for £2-50.
- PP3 Battery Connectors 10 for 50p.
- Miniature Press to Make Switches, Red knob. 3 for 50p.
- Subminiature S.P.C.O. Slide Switches. 6 for 50p.
- Miniature D.P.C.O. Slide Switches. 6 for 50p.
- Standard 2P. 3 Position Slide Switch. 4 for 50p.
- 4 x HP11 Battery Holders (2 x 2 Flat type) with leads. 2 for 50p.
- Assorted Fuse Holders including 20mm, P.C. Panel and chassis types. Pack of 7 for 50p.
- 3-5mm Jack Sockets, switched. Enclosed type, P.C. or panel mounting. With nuts and washers. 4 for 50p.
- 9 Section, Chrome on Brass Telescopic Aerial. Plugs into any 3-5mm socket. Approx 25" extended £1 each. 3 for £2-50.
- Hi Power Infra Red Transmitter 5mm LED. TIL 38 60p ea. 3 for £1-50.
- Crystal Clear 3mm LEDs very pretty Red, Green, Yellow. 10 of one colour £1. 10 of each £2-50.

- ALTERNATOR RECTIFIERS
- Make lovely 60 amp bridges. Ideal for High Power Battery Chargers. Type 4AFI. Set of 4 (2 neg. case + 2 pos. case) £2.
- Special Purchase enables us to offer Mullard C280 Polyester Capacitors (Liquorice Allsorts) at the unbeatable price of £2 for 100 mixed. £15 for 1000. These consist of factory clearance lots i.e. spillages, floor sweepings, cosmetic rejects etc. Also, Mullard Miniature Electrolytics, 200 mixed £2.


To: "GEMINI ELECTRONIC COMPONENTS" DEPT PE
"THE WAREHOUSE" SPEEDWELL ST. LONDON S.E.8.

Where shown. Send Cheque* or Postal Order. Plus 60p P&P. and 15% VAT.
Please Quote ZED Code. *Schools etc. SEND OFFICIAL ORDER
ZED PACKS now available for Callers at 50 Deptford Broadway, London, S.E.8.




EVERY DOOR SHOULD HAVE ONE

Whatever kind of door you have, our New Electronic Combination Lock will enable you to open it easily but make things very difficult for unwelcome visitors. The unit, which comes complete with a 10-way keypad, requires an easily remembered four digit code to be entered before the door can be opened, while the intruder has over 5,000 combinations to choose from. The code can be easily changed by means of a pre-wired plug and a momentary or latched output version can be made. The kit has even more uses in a car where it may be used to disable the ignition. Another useful feature is the Save Button. This stores the combination number, enabling the car to be used by authorised persons such as garage personnel without disclosing the code. The complete kit measures 7x6x3 cms. deep and consumes a mere 40uA when not in use, and will drive a 5V to 15V (750mA) solenoid or relay coil (not supplied) directly. So why not treat your door to a new lock for **ONLY £10.50** and think about all the keys you can lose or forget without ever locking yourself out. (As featured in P.E. May '81.)

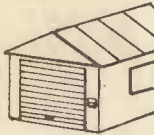

ARE YOU SITTING COMFORTABLY?

Our new TDR300K Touch Dimmer Kit will ensure that you are. Based on our highly successful TD300K touch controlled dimmer kit, the TDR300K incorporates an infra red receiver, enabling the lamp brightness to be varied and switched on or off by touch or remotely by means of a small hand held transmitter. The complete kit, which includes easy to follow instructions, will fit into a plaster depth box and the plastic front plate has no metal pads to touch, ensuring complete safety. Even a neon is included to help you locate the switch in the dark.

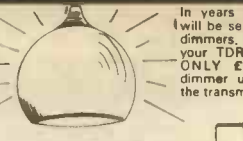

In years to come everyone will be selling remote control dimmers, but you can have your TDR300K kit now for **ONLY £14.30** for the dimmer unit and £4.20 for the transmitter.



For the more athletic of you the TD300K Touchdimmer kit is still available at **£8.50** and the TDEK Extension kit, for 2-way switching etc., is **£2.00**. **DON'T FORGET** to add 50p P&P and 15% VAT to your total purchase.

DISCO LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input. **DL1000K** This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates meter dimming control. **£14.60**



DL21000K A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**
Optional Opto Input **DLA1** **60p**



MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.
MK1 TEMPERATURE CONTROLLER/THERMISTAT Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. **1KW £4**
MK2 SOLID STATE RELAY Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

MK3 BAR/DOT DISPLAY Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**
MK4 PROPORTIONAL TEMPERATURE CONTROLLER Based on a new zero voltage switch IC, this kit may be wired to form a 'burst fire' power controller, enabling the temperature of an enclosure to be maintained within 0.5°C. Thermistor failure causes output to switch off. Temperature range ambient to 90°C. **3KW. £5.55**

MK5 MAINS TIMER Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load **1KW. £4.50**

24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions. **£14.90**
CT1000K Basic Kit **£17.40**
CT1000KB with white box (56/131x71mm) **£22.50**
Ready Built

TRIACS
400V Plastic Case (Texas)
3A TIC206D **49p**
8A TIC226D **58p**
12A TIC236D **85p**
16A TIC246D **96p**
25A TIC263D **190p**
6A with trigger Q4006LT **80p**
8A isolated tab TXAL2268 **65p**
Diac **18p**

3A TIC206D
8A TIC226D
12A TIC236D
16A TIC246D
25A TIC263D

6A with trigger Q4006LT
8A isolated tab TXAL2268
Diac

NEW RIDICULOUS LOW PRICE FOR DVM(THERMOMETER KIT) £13.50 VAT

STAR BUY

Based on ICL7106 DVM chip and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter - only a few additional switches and resistors required (details supplied) or make a sensitive digital thermometer (-50° to 150°C) reading to 0.1°C. The basic kit has a sensitivity for full scale of 200mV, automatic polarity and runs from a 9V PP3 battery.

At this price you can use this kit in place of moving coil meters in virtually any application from bathroom scales to bicycle speedometers - the possibilities are endless.

REMOTE CONTROL COMPONENTS AND KITS



LD271 IR Emitting diode **.36**
SFH205 Photodiode Detector **.90**
SL480 IC Pulse Amp. **1.70**
SL490 32 Command Encoder/transmitter **2.40**
ML922 10-channel receiver + 3 analogue outputs **4.20**

ML926 16-channel receiver 4 momentary binary outputs **1.40**
ML928 16-channel receiver, 4 latched binary outputs **1.40**
ML929 16-channel receiver, 4 latched binary outputs **1.40**
Clip-on Plastic Reflector for IR LEDs, increases range **.20**

ML925. A decoder designed for model/toy control, providing a 2-speed drive motor and three position latched steering system or a vehicle with momentary action steering and a third motor, eg. gun turret, wrench, etc. Outputs also available for other facilities such as horn, turn indicators, headlights, etc. **2.10**

To make things EVEN EASIER, we have designed several new kits:—
MK6 - Simple Infra Red TRANSMITTER. A Pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. **4.20**
MK7 - Infra Red RECEIVER. Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, but can be modified for use with 5 to 15V dc supplies and transistor or relay outputs. **9.00**
*Special Price *MK6 and MK7 together, Order as RC500K. **12.50**
MK8 - Coded Infra Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 8x2x1.3 cms. and requires a 9V (PP3) battery. **5.90**
MK9 - 4 Way KEYBOARD. For use with the MK8 kit, to make a 4-channel remote control transmitter. **1.90**

MK10 - 16-Way KEYBOARD. For use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. **5.40**
MK11 - 10 On-Off Channel IR RECEIVER with 3 analogue outputs (0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC. Includes its own mains supply. **12.00**

MK12 - 16 Channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. **11.95**


MK13 - 11-Way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and -, analogue + and - (3), mute normalise analogue outputs, and on/standby. **4.35**

VMOS POWER FETS

VN10KM 0.5A/60V (TO92) **52p**
VN66AF 2A/60V (TO220) **88p**

D.I.L. I.C. SOCKETS

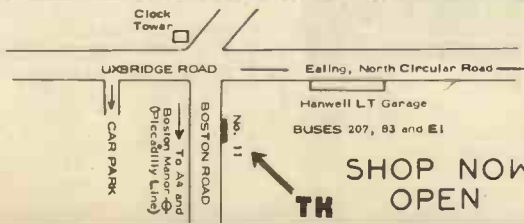8 pin **8p** 18 pin **17p**
14 pin **12p** 20 pin **24p**
16 pin **14p** 40 pin **36p**
Soldercon Pins **50p/100**



SHOP NOW OPEN

INTEGRATED CIRCUITS

555 Timer **21p**
741 Op Amp **19p**
AY-5-1224 Clock **£2.60**
AY-5-1230 Clock/Timer **£4.50**
AY-3-1270 Thermometer **£8.20**
CA3080 Transconductance Op. Amp. **72p**
CA3130 CMOS Op. Amp. **75p**
ICL7106 DVM (LCD Drive) **£7.00**
LM3377 Dual 2V Amp. **£1.45**
LM3375 Dual 6W Amp. **£3.50**
LM380 2W Audio Amp. **80p**
LM382 Dual low noise re amp. **£1.00**
LM386 250mW low level voltage amp. **75p**
LM1830 Fluid level Detector **£1.50**
LM2317 F/V Converter (14 pin) **£1.60**
LM3909 LED Flasher/oscillator **60p**
LM3911 Thermometer **£1.20**
LM3914 Dot/Bar Driver (linear) **£2.10**
LM3915 Dot/Bar Driver (log.) **£2.20**
MM74C911 4-digit Display Controller **£6.50**
MM74C926 4-digit counter with segment output **£4.50**
S5668 Touchdimmer **£2.50**
SL440 AC Power Control **£1.75**
SN76477 Complex Sound Generator **£2.52**
TBAB00 5W Audio Amp **£2.80**
TBAB10AS 7W Audio Amp. **£1.80**
TCM7555 CMOS 555 Timer **79p**
TDA1024 Zero Voltage Switch **£1.20**
TDA2020 20W Audio Amp. **£2.85**
TLO81 J-FET Op. Amp. **37p**
TLO82 Dual J-FET Op. Amp. **50p**
TMS1121 Clock/7 day timer **£8.50**
TMS1121 Data **£1.80**
ZN1034E Timer **£1.80**
All ICs supplied with Data Sheets.
Data Sheets only - per device **10p**

CMOS

4000	17p	4019	42p	4069	19p
4001	18p	4023	22p	4070	19p
4002	18p	4025	21p	4071	18p
4007	17p	4026	£1.30	4077	26p
4011	19p	4027	40p	4081	20p
4012	17p	4028	50p	4093	54p
4013	38p	4040	80p	4501	24p
4016	75p	4049	38p	4511	90p
4018	35p	4050	40p	4514	£1.80
4017	70p	4060	£1.08	4516	£1.80

MINI LEDs

0.1" Red **9p**
0.1" Yellow **12p**
0.2" Red **9p**
0.2" Green **12p**
0.2" Yellow **12p**
0.2" clips **3p**
Rectangular Red **16p**
Rectangular Green **17p**
Rectangular Yellow **17p**
Flat Face rectangular, Triangular, Arrowhead or Square **17p**
Triac **17p**
MOC3020 0-6A/10 400V **£1.10**
Rec. Yellow **20p**

VOLTAGE REGULATORS

Available in 5V, 12V, & 15V versions.
78L series 100mA pos. **26p**
79L series 100mA neg. **60p**
78 series 1A pos. **52p**
79 series 1A neg. 5V. **75p**
LM317T adjustable 1.2V-37V 1.5A **£1.80**

DISPLAYS

FND504 Red 0.5" c.c. pin compatible with DL504 **75p**
DL307 Red 0.3" c.c. pin compatible with DL707 **75p**
DL727 Dual 0.5" c.c. Red **£1.50**
MP463 0.5" c.c. Red, four digit multiplexed **£2.20**
DL 34M 0.1" Bubble magnified 4 digit c.c. multiplexed 14 pin DIL package. Red **£4.50**

TH Electronics
ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION ADD 50p P&P and 15% VAT TO TOTAL OVERSEAS CUSTOMERS ADD £1.50 (Europe) £4 (elsewhere) for P&P. Send see for price list and with all enquiries. Callers welcome 9.30-5.00 (Mon-Fri) 10.00-4.00 (Sat.)
LONDON W7 3SJ. 01-579 9794/2842

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electropop D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security change-over switch. Will work all rev counters.

Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates, Dept. PE1179, 82 Bath St., Walsall, WS1 3DE

Electronics Design Associates, Dept. PE/9/81
82 Bath Street, Walsall, SW1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REDD.

I enclose cheque/PO's for

X5 KIT £16.95

£

Cheque No. _____

ACCESS OR BARCLAY CARD No. _____

Send SAE if brochure only required

ELECTROVALUE

BEST SELLERS ...

RECHARGEABLE CELLS by SANYO-CADNICA. Size AA 99p, C 2.27, D 3.76, PP3 4.10 with tags: AA 1.06, C 2.43, D 3.89.
CHARGERS PP3 4.75, AA 4.95, A, C, D 7.60.
PLASTIC BOXES PB1 116 x 77 x 35mm 62p.
Breadboards Euro 5.70N, Veroblock 3.83.
Bimboard 8.03, Buzzer 6-15V 80p.
CAPACITORS polystyrene 47-4700pF ea 7p, C280 .01 6p, 1 7p, .22 9p (full range), Polyester (PCM 7.5mm) .001 6p, .0047 7p, .056 8p, .1 9p, (PCM 10mm) 1uF 26p. (Many more values in this range)
Variable Dilecon 100pF 2.08, 500pF 3.21.
ELECTROLYTICS (full range).
CONNECTORS 1/2" jack plug 32p, skt 12p, 3.5mm jack plug 17p, skt 14p, 2.5mm 12p, DIP header 14 pin 38p, 16 pin 43p.
Quick test mains block 5.25.
Fuse holders 20mm panel 22p, chassis 6p.
HALL-EFFECT devices from 1.89N.
Heat sinks Power 1.25° C/W 2.85; finger type T03 25p, T0220 25p.
INTEGRATED CIRCUITS - hundreds of types: 741 18p, 555 23p, CA3140E 40p, LM380N 99p, LM3914N 2.88, S566B 2.14, TCA965 1.20.
IC holders 8 pin 9p, 14-40 pin 1p per pin.
KNOBBS, screw fittings 1/2" from 15p.
Loudspeakers 2 1/2" 8 or 64 ohms 93p.
Magnet resistors from 1.60N.
Meters, panel 80 x 45mm 50uA-1A ea 4.80.
Opto LEDs red 7p, yellow 9p, green 11p; ultrabright 21p all colours.
LED drivers UAA170UAA180 ea 1.52.
POTENTIOMETERS carbon 20mm dia 100R-2M2 lin, 220R-4M7 log single 29p, 1K-2M2 lin, 4K-72M2 log duals, ea 81p, Add 51p if required with switch.
Sliders mono 72p, stereo 1.18, bezel 34p.
Wirewound 25R 10K, 3 watt ea 1.50.
PRINTED CIRCUIT MATERIALS, 300 x 150mm S/S SRP 1.25, 1/4 1.90, 500gm ferric chloride lab grade 3.40, Positiv 20 photo resist 75ml 1.65, Etch resist pen 1.05, silver paint 3g 4.14N, Relays 12v coil 3P2W 10A contacts 2.90, Resistors 1/4W, 1/2W, 1W 5% ea 2p, Metal oxide TRS 2% 5p, film MR25 5p.
SEMICONDUCTORS 1N4007 6p, 1N4148 3p, RCA2N3055 70p, BC107-9 family 14p, BC182/212 family 9p, BFR34A 83p, BFT65 1.19, C10601 45p, TIP31A/32A ea 44p, TIP41A/42A ea 45p, TIP2955/TIP3055 ea 55p.
Solder 500gm 60/40 205MW 7.30N.
IRONS Antec C, CCN, CX or X25 ea 4.40N, Dryx 50 temperature controlled 11.50N, ISO-TIP cordless with charger 24.00N.
SWITCHES slider DPDT min 18p, std 20p, Wavechange 1P12W, 2P6W, 3P4W, 4P3W ea 40p, Time switch 13A 3 on/3 off per day 14.68N, Min toggles silver contacts SPDT 57p, DPDT 80p, 3PDT 1.54, 4PDT 2.75, DIL gold plates 4PST 95p, 10PST 2.10.
Miniature drills, 12v dc TITAN 10.28N, TITAN kit 17.06N, Stand 12.00N.
Tools CK pliers 4.70, cutters 6.10, strippers 4.95.
Vero wiring system kit 4.42, wire 1.17.
Computers Nascom 1 built 140.00N.
NASCOM 2 kit £295.00 complete (less 8 x 4118's £225.00N), P/S kit, 3 amp 32.50N, 16K RAM kit 110.00N.

ELECTROVALUE LTD. DEPT. PE/8, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.
Phone Egham 33603 (STD 0784, London 87), Telex 264475
Northern Branch (Personal Shoppers only) 680 Gurnage Lane, Burnage, Manchester M19 1NA Phone (051) 432 4945.

BEST SERVICE

★ KEEN BUYERS!
A S.A.E. BRINGS COMPREHENSIVE

PRICE LIST

(Valid 3 mths.)

COVERING

CATALOGUE '81.

ACCESS AND

BARCLAYCARDS

ACCEPTED

EVERYTHING

BRAND NEW &

GUARANTEED

HARD TO FIND

ITEMS

KEEN PRICES &

DISCOUNTS

SPECIAL

QUANTITY

DISCOUNTS

SPEEDY

TURN ROUND

ON ORDERS

NO P/P CHARGES

ON U.K. C.W.O.

ORDERS OVER

£5.75. (Add

handling charge

of 40p if under).

★ PLEASE ADD 15%

VAT TO TOTAL

VALUE OF ALL

ORDERS.

★

Shop Hours -

9-5.30;

Sats. 9-1 pm.

The ONE catalogue you MUST have!



- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.

Send cheque or P.O. for £1.50

HOME RADIO Components LTD
Dept. PE, P.O. Box 92, 215 London Road,
Mitcham, Surrey. 01-543 5659

RADIO/TAPES BARGAINS

LW/MW/Malns/Battery Radios

£9.00 each (P&P £1.00)

LW/MW Car Radios with speaker

£9.00 each (P&P £1.00)

Small VHF/MW Battery Radios

£7.00 each (P&P 50p)

8-C60 High gain Cassettes

£2.00 (P&P 50p)

5-C90 High gain Cassettes

£2.00 (P&P 50p)

Stereo Headphones with lead and

Jack Plug £4.50 (P&P 50p)

Maximum Postage Charge £1.00.

Money refunded if not satisfied.

AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 - For Mono or Colour this is tunable over complete UHF television band.

B11 - For stereo or standard VHF/FM radio.

B12 - for VHF television band 1 & 3.

All amplifiers are complete and ready to use Battery type PP3 or 8V to 18V DC next to the set type fitting.

PRICES £6-70 each.

Signal Injectors with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts DC. Complete with leads £5.70 each.

All Prices Include VAT at 15%. P & P per Order 30p. S.A.E. for Leaflets. Access Cards

ELECTRONIC MAILORDER LTD,
62 Bridge St, Ramsbottom, via Bury, Lancs. BLO 9AGP.
Tel Rams (070 682) 3036.



Micro Circuits

Prime components - Low prices.

Dept. PE.9, Unit 9/10, 1st Floor, East Block, 38 Mount Pleasant, London WC1X 0AP. Tel: 01-837 1165, 01-278 7369. Telex: 8953084 Maclin G.

All our microchips are at micro prices. Don't be fooled by low prices. We do not offer for sale surplus, sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official orders from schools, colleges, universities and Gov. authorities accepted.

NEW, LOW, LOW PRICES ON MEMORIES

Compare our prices before you buy elsewhere! All devices are brand new, factory prime, full spec. and fully guaranteed! All prices exclude P&P and VAT.

Please refer to Ordering Information before ordering.

STATIC RAMS	1-24	25-99	100+
2114L 200 NS	1.60	1.45	1.30
Lower Power 4118 250 NS	6.25	5.95	5.25

DYNAMIC RAMS	1-24	25-99	100+
4116 150NS	2.50	2.25	1.95
4116 200 NS	1.40	1.25	1.15
HM4864 64K (64Kx1)			
Single 5V 200 NS	14.95	13.95	12.95
CMOS RAMS	1-24	25-99	100+
TC5514P 4K(1K x 4) same as 6514			
450NS	3.25	2.95	2.60
HM6116 16K (2K x 8)			
200 NS	12.95	11.95	9.95
EPROMS	1-24	25-99	100+
2708 450 NS	2.95	2.75	2.50
2716 5V 450 NS	2.95	2.75	2.50
2532 5V 450 NS	8.95	8.50	8.25
2732 450 NS	8.95	8.50	8.25

Ordering information: Unless otherwise stated, for orders under £50 add 50p p&p. Add 15% VAT to total (no VAT on books). All devices are brand new, factory prime and full spec and subject to prior sales and availability. Prices subject to change without notice. Minimum telephone order using ACCESS is £10. If ordering by post with ACCESS, include name, address and card no. written clearly. Please allow 4/6 weeks delivery on books.

DTL	74LS126	50p	4059	560p
830	74LS132	70p	4060	112p
935	74LS138	60p	4063	112p
937	74LS139	75p	4066	56p
944	74LS148	170p	4067	422p
946	74LS151	75p	4068	19p
947	74LS153	75p	4069	19p
962	74LS155	65p	4070	28p
969	74LS157	74p	4071	25p
9099	74LS160	115p	4072	25p
	74LS161	78p	4075	20p
	74LS163	90p	4076	88p
	74LS164	90p	4077	23p
	74LS165	150p	4078	29p
	74LS168	190p	4081	83p
	74LS173	120p	4082	26p
	74LS174	95p	4085	86p
	74LS175	99p	4086	66p
	74LS181	280p	4089	130p
	74LS190	110p	4093	68p
	74LS198	87p	4094	225p
	74LS196	120p	4095	99p
	74LS211	100p	4096	325p
	74LS220	210p	4098	110p
	74LS221	200p	4099	180p
	74LS242	220p	4501	25p
	74LS243	110p	4502	112p
	74LS244	175p	4503	68p
	74LS245	220p	4507	52p
	74LS251	120p	4508	288p
	74LS253	120p	4510	76p
	74LS257	110p	4511	125p
	74LS260	90p	4514	250p
	74LS266	75p	4516	109p
	74LS273	175p	4518	99p
	74LS279	120p	4520	99p
	74LS283	57p	4521	230p
	74LS373	170p	4526	105p
	74LS374	170p	4528	99p
	74LS375	140p	4529	140p
	74LS393	135p	4531	150p
	74LS490	140p	4543	160p
	74LS670	260p	4538	175p

KEYBOARD ENCODER

AY-5-2376	695p
KP3600	695p

SUPPORT DEVICES

65211	325p
6522	525p
6532	795p
6551	800p
6520	225p
6820	295p
6821	195p
6845	1400p
6850	200p
6852	375p
6810	150p
6812	425p
6816	160p
6824	250p
6826	225p
6828	350p
6835	495p
6840	395p
6845	445p
6857	795p
6859	795p
6893	1400p
8080A	400p
8085A	600p
Z80	495p
Z80A	595p
Z8001	£99
Z8002	£80

SUPER SALE!

Quantity	1-24	25-99	100+
ICL7106 3 1/2 digit LCD	£5.75	£4.75	£4.00
A/D Converter			
LCD 106 3 1/2 Digit LCD Display with "Lo Bat" sign for above	£5.95	£4.95	£4.00
AY-3-8910 Computer Sound IC	£5.95	£5.25	£4.50

NEW SUPER MUSIC MACHINE KIT!

AT LAST... an affordable kit that can be PROGRAMMED TO PLAY ANY SONG OR GROUP OF SONGS! Instead of a nightmare of numerous ICs and special expensive Bipolar ROMs, the SUPER MUSIC MACHINE uses a SPECIAL MASK PROGRAMMED COMPUTER CHIP. One CMOS gate and the most popular erasable EPROM, the 2708/2709 series. BASIC KIT includes drilled, plated and screened PC board and ALL components except the EPROM and 12V transformer. The basic kit will play short renditions of 25 tunes through its 7 WATT AMPLIFIER SECTION. Add an optional ROM and any tune programmed will be played. If you have the equipment to program 2708 EPROMs, we supply full information on programming your own music!

2564 (8Kx8)	£75.00
450NS 28 pin NEW!	

CPUs

6502	500p
6504	650p
6505	700p
6800	400p
6802	600p
6809	1400p
8080A	400p
8085A	600p
Z80	495p
Z80A	595p
Z8001	£99
Z8002	£80

3 1/2 in. DIGIT LCD DISPLAY with "Lo Bat" sign.

ICD106	£5.95
--------	-------

INTERFACE LINEAR

MC1488	70p
MC1489	70p
DM8123	125p
75150	125p
75154	125p
75182	195p
75322	250p
75324	325p
75325	325p
75361	350p
75385	295p
75451	50p
75491/2	75p
8726	140p
8728	140p
8795	140p
8797	155p

VOLTAGE REGULATORS

LM1817	375p
LM1872	315p
LM3900	45p
LM3914	200p
LM3915	200p
LM13600	100p
NE555	50p
NE556	50p
RC4135	70p
SN76477N	150p
TBA810DAS	85p
TL071	40p
TL074	72p
TL082	120p
TL084	100p
TL490	175p
XR2206	295p
XR2207	375p

DISPLAYS

FND500	80p
FND510	80p
FND567	125p
DL704	85p
DL707	85p
NV57164	225p

CHARACTER GENERATORS

RO-3-2513VC	£59p
SN74S262AN	£50p
CG4103	£95p

FLOPPY DISC CONTROLLERS

FD1771 B-01 S/D Inverted Bus	£18
FD1791 B-01 D/D Inverted Bus	£29
FDC 3400	£12

SE 01 Sound Effects Kit

The SE 01 is a complete kit that contains all the parts in build a programmable effects generator. Designed around the new Texas Instruments SN 76477 Sound Chip, the board provides banks of MIDI DIP switches and pots to program the various combinations of the SLF Oscillator VCO noises. One Shot and Envelope Controls A Quad Op Amp IC used to implement and Adjustable Pulse Generator. Linear Compressor and Multiplex Oscillator for even more versatility. The 3 1/4" x 3 PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosion Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multitude of applications. The low price includes all parts, assembly manual, programming charts and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mV amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included!)

COMPLETE KIT ONLY £12. £1 P&P. VAT £1.95 - £14.95 TOTAL

BOOKS BY HOWARD W. SAMS INC. SALE!

(Please order books by reference number and title. Please add 75p P&P per book. No VAT)

REF	TITLE	PRICE	NORMAL SALE PRICE
21168	Active Filter Cookbook	£10.95	£7.75
21440	Aviation Electronics	£6.75	£5.75
21558	Audio IC OP Amp Application	£5.95	£4.75
21586	Basic Programming Primer	£6.50	£4.75
21554	Boolean Algebra for Computer Logic	£4.50	£3.75
21447	The 8080A Bugbook Microcomputer		
	Interfacing & Programming	£5.04	£3.75
21465	Building and Installing Electronics Intrusion Alarms	£3.95	£2.75
21524	The Cheap Video Cookbook	£4.50	£3.75
21398	CMOS Cookbook	£7.75	£6.75
21652	Computer Dictionary 3rd Ed	£8.95	£7.75
21693	Computers & Programming Guides for Scientists & Engineers	£11.95	£8.75
21697	8085A Cookbook	£7.50	£5.75
21539	Design of Active Filters with Experiments	£5.95	£4.75
21536	DEBUG An 8080 Interpreter Debugger	£3.75	£2.75
21537	Design of Op Amp Circuits with Experiments	£5.95	£4.75
21686	Design of CMOS Circuits with Experiments	£5.95	£3.75
21550	Introductory Experiments in Digital Electronics & 8080A Microcomputer Programming & Interfacing Book 1	£9.95	£7.75
21551	Introductory Experiments in Digital Electronics & 8080A Microcomputer Programming & Interfacing Book 2	£9.95	£7.75
21351	How to Buy and Use Minicomputers and Microcomputers	£7.50	£5.75
21684	How to Program & Interface the 6800	£10.50	£7.75
21459	How to Program Microcomputers	£6.75	£4.75
21127	How to Read Schematic Diagrams	£4.25	£3.75
21613	How to Use Integrated Circuits Logic Elements	£4.50	£3.75
21527	IC Converter Cookbook	£10.50	£8.75

6809 S-100 SINGLE-BOARD COMPUTER

- Meets IEEE S-100 Standard!
- Uses Motorola's Powerful MC6809 CPU!
- 4K, 8K, 16K ROM!
- 2K RAM!
- RS 232 Handshake!
- Selectable BAUD Rates!
- Manual includes: 11 x 7 Schematic, Parts List, x 7 Notes, Software Listings and MORE!

BAREBOARD now only £35 ADSMON, MONITOR (2716). Now only £15 Total

3 1/2 in. DIGIT AUTORANGING LCD DMMs from KAISE

6200, as itemised. ONLY £39.95 exc VAT
8220, as 6200, plus 10amp AC/DC measurement ONLY £48.65 exc VAT
8110 with 10amp AC/DC measurement AND Continuity Check!
ONLY £74.74 exc VAT Optional vinyl carry case £2.30 exc VAT

- 1mv 100nA and 0.111 resolution!
- Measures AC voltage to 600V!
- Measures DC voltage to 1000V!
- Displays mV, V and mA!
- 0.8% accuracy!
- Zero adjustment!
- 3 other models too!

UNIVERSAL SCR NEW LOW PRICE

Only £5.95
The NEW GI COMPUTER SOUND CHIP

The amazing AY-3-8910 is a fantastically powerful sound and music generator, perfect for use with any 8-bit micro processor. Contains 3 tone channels, noise generator, 3 channels of amplitude controls, 16-bit envelope period control, 2 parallel I/O, 3D/A converters plus much more. All in 40 pin DIP Super easy to interface to the S 100 or other buses. ONLY £5.95 + VAT. Including FREE reprint of BYTE 79 article! Also, add £2.25 for 60-page data manual! "Perhaps the next famous composer will not direct a 150-piece orchestra but rather a trio of microprocessors controlling a bank of AY-3-8910s." BYTE July 79.

20 POWER AMPS

19 FUNCTIONAL MODULES

DAWN

POWER UP TO
480 WATTS RMS
SINGLE CHANNEL



AMPLIFIER WITH HEAT SINK

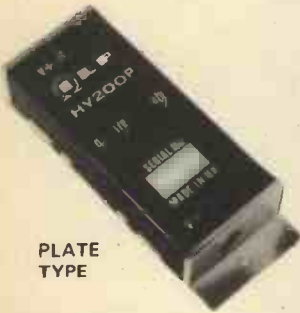


PLATE TYPE



PSU

Which amplifier?

I.L.P. Amplifiers now come in three basic types, each of which is available with or without heatsink. Having decided the system you want – home hi-fi (models HY30, 60 or 120 for example), super quality hi-fi with extra versatility (MOS120, MOS200) or Disco/PA/Guitar (HD120, HD200 or HD400) you will then decide whether amplifiers housed within their own heatsinks or plate amplifiers for bolting to a metal chassis will suit. With choice such as this and a brilliant new range of I.L.P. functional modules to choose from you now have the chance to build the finest audio system ever offered to the constructor.

BIPOLAR Standard, with heatsinks										Without heatsinks				
MODEL NUMBER	OUTPUT POWER Watts rms	DISTORTION		SUPPLY VOLTAGE TYP/MAX	SIZE mm	WT gms	PRICE	VAT	MODEL NUMBER	SIZE in mm	WT gms	PRICE	VAT	
		T.H.D. Typ at 1kHz	I.M.D. 60Hz/7kHz 4:1											
HY30	15w/4-8Ω	0.015%	<0.006%	±18±20	76x68x40	240	£7.29	£1.09						
HY60	30w/4-8Ω	0.015%	<0.006%	±25±30	76x68x40	240	£8.33	£1.25						
HY120	60w/4-8Ω	0.01%	<0.006%	±35±40	120x78x40	410	£17.48	£2.62	HY120P	120x26x40	215	£15.50	£2.33	
HY200	120w/4-8Ω	0.01%	<0.006%	±45±50	120x78x50	515	£21.21	£3.18	HY200P	120x26x40	215	£18.46	£2.77	
HY400	240w/4Ω	0.01%	<0.006%	±45±50	120x78x100	1025	£31.83	£4.77	HY400P	120x26x70	375	£28.33	£4.25	

Protection: Load line, momentary short circuit (typically 10 sec) Slew rate: 15V/μs Rise time: 5μs
S/N ratio: 100db Frequency response (-3dB): 15Hz - 50kHz
Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω/100Hz)>400

HEAVY DUTY with heatsinks										Without heatsinks				
MODEL NUMBER	OUTPUT POWER Watts rms	T.H.D. Typ at 1kHz	I.M.D. 60Hz/7kHz 4:1	SUPPLY VOLTAGE TYP/MAX	SIZE mm	WT gms	PRICE	VAT	MODEL NUMBER	SIZE in mm	WT gms	PRICE	VAT	
HD120	60w/4-8Ω	0.01%	<0.006%	±35±40	120x78x50	515	£22.48	£3.37	HD120P	120x26x50	265	£19.84	£2.98	
HD200	120w/4-8Ω	0.01%	<0.006%	±45±50	120x78x60	620	£27.38	£4.11	HD200P	120x26x50	265	£23.63	£3.54	
HD400	240w/4Ω	0.01%	<0.006%	±45±50	120x78x100	1025	£38.63	£5.79	HD400P	120x26x70	375	£34.28	£5.14	

Protection: load line, PERMANENT SHORT CIRCUIT (ideal for disc/group use should evidence of short circuit not be immediately apparent).
The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs. as for standard types.

MOSFET Ultra-Fi, with heatsinks										Without heatsinks				
MODEL NUMBER	OUTPUT POWER Watts rms	T.H.D. Typ at 1kHz	I.M.D. 60Hz/7kHz 4:1	SUPPLY VOLTAGE TYP/MAX	SIZE mm	WT gms	PRICE	VAT	MODEL NUMBER	SIZE in mm	WT gms	PRICE	VAT	
MOS120	60w/4-8Ω	<0.005%	<0.006%	±45±50	120x78x40	420	£25.88	£3.88	MOS120P	120x26x40	215	£23.32	£3.50	
MOS200	120w/4-8Ω	<0.005%	<0.006%	±55±60	120x78x80	850	£33.46	£5.02	MOS200P	120x26x80	420	£28.53	£4.28	
MOS400	240w/4Ω	<0.005%	<0.006%	±55±60	120x78x100	1025	£45.39	£6.81	MOS400P	120x26x100	525	£38.91	£5.84	

Protection: Able to cope with complex loads, without the need for very special protection circuitry (fuses will suffice).
Ultra-fi specifications:
Slew rate: 20V/μs Rise time: 3μs S/N ratio: 100db Frequency response (-3dB): 15Hz - 100kHz
Input sensitivity: 500mV rms Input impedance: 100kΩ Damping factor: (8Ω/100Hz)>400


POWER SUPPLY UNITS			
MODEL NO.	FOR USE WITH	PRICE	VAT
PSU30	± 15V combinations of HY6/66 series to a maximum of 100mA or one HY67 The following will also drive the HY6/66 series except HY67 which requires the PSU30.	£4.50	£0.68
PSU36	1 or 2 HY30	£8.10	£1.22
PSU50	1 or 2 HY60	£10.94	£1.64
PSU60	1 x HY120/HY120P/HD120/HD120P	£13.04	£1.96
PSU65	1 x MOS120/1 x MOS120P	£13.32	£2.00
PSU70	1 or 2 HY120/HY120P/HD120/HD120P	£15.92	£2.39
PSU75	1 or 2 MOS120/MOS120P	£16.20	£2.43
PSU90	1 x HY200/HY200P/HD200/HD200P	£16.20	£2.43
PSU95	1 x MOS200/MOS200P	£16.32	£2.45
PSU180	2 x HY200/HY200P/HD200/HD200P or 1 x HY400/1 x HY400P/HD400/HD400P	£21.34	£3.20
PSU185	1 or 2 MOS200/MOS200P/1 x MOS400/ 1 x MOS400P	£21.46	£3.22

All models except PSU30 and PSU36 incorporate our own toroidal transformers.

FP480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by I.L.P. for use with any two power amplifiers of the same type to double the power output obtained and will function with any I.L.P. power supply. In totally sealed case, size 45 x 50 x 20mm, with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8Ω. Contributory distortion less than 0.005%.

Price: £4.79 + 72p. V.A.T.

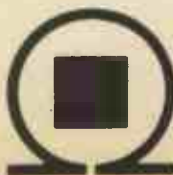

I.L.P. ELECTRONICS LTD.

FREEPOST 2 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0277)54778 (Technical (0227) 64723) Telex 965780

Available also from MARSHALLS, TECHNOMATIC, WATFORD ELECTRONICS and certain other selected retailers.

GOODS BY MAIL ORDER DESPATCHED WITHIN 7 DAYS

OF A NEW ERA



Which modules?

In launching eighteen different units all within amazingly compact cases to help make complete audio systems using I.L.P. power amplifiers, we bring the most exciting, the most versatile modular assembly scheme ever for constructors of all ages and experience. Study the list – see how these modules will combine to almost any audio project you fancy – and remember *all I.L.P. modules are compatible with each other*, they connect easily. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm. They are so reliable that all I.L.P. modules carry a 5 year no quibble guarantee.



MODEL NO.	MODULE	DESCRIPTION/FACILITIES	CURRENT REQUIRED	PRICE	VAT
HY6	MONO PRE AMP	Mic/Mag. Cartridge/Tuner/Tape/Aux + Volume/Bass/Treble	10 mA	£6.44	£0.97
HY7	MONO MIXER	To mix eight signals into one	10 mA	£5.15	£0.77
HY8	STEREO MIXER	Two channels, each mixing five signals into one	10 mA	£6.25	£0.94
HY9	STEREO PRE AMP	Two channels mag. Cartridge/Mic + Volume	10 mA	£6.70	£1.01
HY11	MONO MIXER	To mix five signals into one + Bass/Treble controls	10 mA	£7.05	£1.06
*HY12	MONO PRE AMP	To mix two signals into one + Bass/Mid-range/Treble	10 mA	£6.70	£1.01
*HY13	MONO VU METER	Programmable gain/LED overload driver	10 mA	£5.95	£0.89
HY66	STEREO PRE AMP	Mic/Mag. Cartridge/Tape/Tuner/Aux + Volume/Bass/Treble/Balance	20 mA	£12.19	£1.83
HY67	STEREO HEADPHONE	Will drive headphones in the range of 4Ω – 2KΩ	80 mA	£12.35	£1.85
HY68	STEREO MIXER	Two channels, each mixing ten signals into one	20 mA	£7.95	£1.19
HY69	MONO PRE AMP	Two input channels of mag. Cartridge/Mic + Mixing/Volume/Treble/Bass	20 mA	£10.45	£1.57
HY71	DUAL STEREO PRE AMP	Four channels of mag. Cartridge/Mic + Volume	20 mA	£10.75	£1.61
*HY72	VOICE OPERATED STEREO FADER	Depth/Delay	20 mA	To be announced	
*HY73	GUITAR PRE AMP	Two Guitar (Bass/Lead) and Mic + separate Volume/Bass/Treble + Mix	20 mA	£12.25	£1.84
†HY74	STEREO MIXER	Two channels, each mixing five signals into one + Treble/Bass	20 mA	£11.45	£1.72
†HY75	STEREO PRE AMP	Two channels, each mixing two signals into one + Bass/Mid-range/Treble	20 mA	£10.75	£1.61
†HY76	STEREO SWITCH MATRIX	Two channels, each switching one of four signals into one	20 mA	To be announced	
†HY77	STEREO VU METER DRIVER	Programmable gain/LED overload driver	20 mA	£9.25	£1.39

The modules are encapsulated and include latest design high quality clip-on edge connectors.

For easy mounting we recommend
B6 Mounting board for modules HY6 – HY13
78p + 12p. V.A.T.

B66 Mounting board for HY66 – HY77
99p + 13p. V.A.T.

All I.L.P. modules include full connection data.

I.L.P. Products are of British Design and Manufacture.

* Ready August – may be ordered now
† Ready September – may be ordered now

All the above modules operate from ±15V minimum to ±30V maximum – higher voltages being accommodated by use of dropper resistors. HY67 can only be used with the PSU 30 power supply unit.

SEE OUR AD ALSO ON PAGE 64

TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. If sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order. When ordering, U.K. customers must include the appropriate V.A.T. as shown.
PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED.

ALL WITH I.L.P.'S 5 YEAR NO QUIBBLE GUARANTEE

To: I.L.P. ELECTRONICS LTD. ROPER CLOSE CANTERBURY CT2 7EP

Please supply..... Total purchase price £.....

I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.....

NAME.....

ADDRESS.....

Signature.....

ALL U.K. ORDERS
DESPATCHED
POST FREE

PE9

15

OF RECEIVING YOUR ORDER

NEW

PRACTICAL ELECTRONICS

STEREO TUNER KIT



This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July Issue). For ease of construction and alignment it incorporates three Mullard modules and an LC IF. System

Features
VHF - M.W. - L.W. Bands. Interstation muting and A.F.C. on VHF. Tuning Meter. Two back printed P.C.B.s. Ready made chassis and scale. Aerial: AM - Ferrite Rod, FM - 75 or 300 ohms. Stabilized power supply with "C" core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/4" approx.

Complete with circuit diagrams and instructions.

INTRODUCTORY PRICE-ONLY

£17.95
plus £2.50 p&p

PRACTICAL ELECTRONICS CAR RADIO KIT (Constructors pack 7)



2 WAVE BAND MW LW
* Easy to build * 5 push button tuning
* Modern styling design * All new unused components
* 6 watt output * Ready etched & punched P.C.B.
* Incorporates suppression circuits * Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards.

Complete with instructions **£10.50** plus £2.00 p&p

CONSTRUCTORS PACK 7A

Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete **£1.95** p&p **£1.15**



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED


Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts: RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/4" x 10" approx.

READY TO PLAY **£32.90** plus £3.80 p&p

HI FI STEREO AMPLIFIER MODULES



- Mullard LP1183 built preamplifier suitable for ceramic and auxiliary inputs. **£1.95** plus 70p p&p.
- Mullard LP1184 built preamplifier suitable for magnetic/ceramic and auxiliary inputs. **£4.95** plus 80p p&p
- Matching I.C. 10 + 10 Stereo Power amplifier kit. **£3.95** plus £1.15 p&p
- Matching power supply kit with transformer. **£3.00** plus £1.96 p&p
- Matching set of 4 slider controls complete with knobs for bass, treble and volumes. **£1.70** plus 80p p&p.
- Complete with application notes.

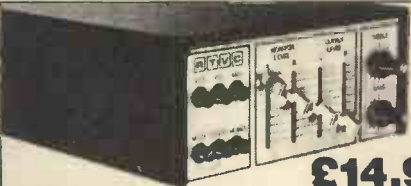

£14.95 plus £2.90 p&p

10+10 WATT STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier module.
- Attractive black vinyl finish cabinet. Size 9" x 8 1/2" x 3 1/2" approx.
- Converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit.

SPECIFICATIONS

Suitable for 4 to 8 ohms speakers
 Frequency response 40Hz — 20KHz
 P.U. 150mV Aux. 200mV Mic. 1.5mV
 Input Sensitivity
 Tone controls
 Distortion
 Mains supply

40Hz — 20KHz
 P.U. 150mV Aux. 200mV Mic. 1.5mV
 Bass ± 12db @ 60Hz
 Treble ± 12db @ 10KHz
 -1% typically @ 4 watts
 220-250 volts 50Hz

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge. **£8.50** plus £3.15 p&p when purchased with amplifier. Available separately **£10.50** plus £3.16 p&p.



8" SPEAKER KIT 2 8" approx. twin cone domestic use speakers. **£4.75** per stereo pair plus **£1.70** p&p when purchased with amplifier. Available separately **£6.75** plus **£1.70** p&p.

STEREO MAGNETIC PRE-AMP CONVERSION KIT

All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p.

RTVC

323 EDGWARE ROAD, LONDON W2
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
 All items subject to availability. Price correct at 1/8/81 and subject to change without notice.
 For further information send for instructions 20p plus stamped addressed envelope.
NOTE: Goods despatched to mainland and N. Ireland only. Persons under 16 years not served without parent's authorisation.
 R TVC LTD. reserve the right to alter, update or improve their products without notice.



HIGH POWER MODULE KITS

125 WATT MODEL **£10.50** plus £1.15 p&p (illus)
200 WATT MODEL **£14.95** plus £1.15 p&p

SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (OC) 50-80 Max
 Loads 4-16 ohms
 Frequency response measured at 100 watts 25Hz-20KHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.H.D. @ 50 watts 4 ohms load 0.1%
 Dimensions 205 x 90 and 190 x 36 mm

The power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES

- Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p.
- Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p.
- Suitable Mains Power Supply Unit for 125W model **£7.50** plus £3.15 p&p.
- Suitable Twin Transformer Power Supply for 200W model **£13.95** plus £4.00 p&p.

MULLARD LP1183 STEREO PREAMP

FREE!

Original listed price over £5.00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.

50 WATT MONO MIXER AMPLIFIER

Six individually mixed inputs for two pick ups (Cer. or Mag.), two moving coil microphones and two auxiliary for tape, tuner, organs etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic and aux. inputs. Power output 50 watt R.M.S. (continuous) for use with 4 to 8 ohms speakers. Finish: Attractively styled black vinyl case, with matching fascia and knobs. Complete and ready for use.

£39.95 plus £3.70 p&p



100 WATT MONO DISCO AMPLIFIER



Brushed aluminium fascia and rotary controls
 Size approx 14" x 4" x 10 1/4". Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level.
 Output 100 watts RMS 200 watts peak **£76.00** plus £4.60 p&p

THE PROTECTION RACKET

PROTECTION in this day and age has become a dirty word but don't knock it, we can provide some protection to you when buying by mail order from adverts in PE. Every so often you will find a statement in our ad. pages about the Mail Order Protection Scheme, it is in your interest to read and be aware of the protection this scheme provides. The protection is against advertisers that become insolvent or bankrupt, it does not cover classified ads. or orders placed as a result of receipt of a catalogue, so it is limited!

In some magazines you will find the protection further limited by a maximum amount being placed on payment of claims made against any one company and also on all claims made by readers in any one year. In such a case you could find yourself with no protection, especially in troubled times when a number of companies go to the wall. The protection offered by PE is not limited in this way but it is dependent on a claim being made in the specified manner and on the advertiser being declared bankrupt or insolvent, a

process which can take some time (claims against Metac, who last advertised in PE a year ago, have only recently been paid—but our readers did get their money back).

Unfortunately, the scheme is voluntary and not all publishers offer such protection. There is nothing to prevent the directors of an insolvent company, owing money to mail order buyers and to the magazines in which they advertised, from starting their own publication carrying mail order advertising and offering no protection scheme to readers. It's OK while the advertisers are solvent but what happens when one goes, owing mail order customers large sums?

VOLUNTARY SCHEME

It could be argued that this problem has been caused by the very publications that provide readers with protection—PE included—because the publishers operate the scheme voluntarily. This was thought to be preferable to being forced by the Director General of Fair Trading to instigate a scheme under law. Because the scheme has remained voluntary not all

publishers operate it and therefore not all buyers are covered. If in doubt, ask the advertisement department of the publication concerned, they should be able to give full details of the scheme, including the procedure for making a claim, and should be able to show a relevant statement made in the publication.

Not only because we operate this scheme, but also because we like to get paid for the adverts that appear in PE, we vet our advertisers carefully and it is not unusual for us to refuse to carry advertising material from some companies. If you do have a valid complaint against an advertiser we can help sort it out—everyone makes mistakes occasionally, and even the biggest companies can flounder.

PRICE

We regret to inform you that from next month the price of PE will be 75p, this increase is due to rising costs. We are only too well aware of the effects of increasing prices on us all, we will do our best to ensure that PE represents good value for money.

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Colette McKenzie SECRETARY

Editorial Offices:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

ADVERTISEMENT MANAGER

SECRETARY

AD. SALES EXEC.

CLASSIFIED MANAGER

D. W. B. Tilleard

Christine Pocknell

Alfred Tonge

Colin Brown

} 01-261 6676

}

01-261 6819

01-261 5762

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Back Numbers

Copies of some of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 95p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £4.30 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £11.80 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perryment Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Edited by David Shortland
& Jasper Scott

CB: Licence Proposals

Further proposals regarding the British CB service were detailed by the Minister of State at the Home Office, Mr Timothy Raison in a speech to the Radio, Electrical and Television Retailers Association on July 9th. Extracts from Mr Raison's speech are printed below.

"I now turn to the arrangements for bringing the new service into operation. Users will need a licence which will define what equipment may be used, and how it may be operated. CB apparatus which is to be marketed in the United Kingdom will be required, by interference regulations made under section 10 of the Wireless Telegraphy Act 1949, to conform to the technical standards outlined in the relevant Home Office performance specifications and to be certified accordingly.

These specifications cover the minimum requirements necessary to minimise interference to other services without unduly increasing the cost of the CB apparatus. To assist retailers and users to identify this interference free equipment a standard mark of compliance is recommended in the specification.

If equipment is marketed in contravention of the regulations it will be open to the Home Secretary, by issuing a notice under section 12 of the 1949 Act, to prohibit the manufacturer or importer concerned from selling such equipment.

I very much hope that British manufacturers will seize the opportunity of producing CB equipment. There was a good deal of initial interest, as witness the number of people who asked for a copy of our draft performance specifications, but my impression is that this interest has receded somewhat in recent months. It may be that some manufacturers here will be able to convert existing sets to the approved Home Office specifications at an economic cost, and we should certainly welcome this. There is a legal difficulty in that virtually every AM set in this country has been imported illegally and has therefore evaded the payment of import duty and VAT, but I understand that Customs and Excise are looking at this problem as sympathetically as possible.

Finally, I should say something about the licensing arrangements. I cannot give much by way of detail because the system is still being set up. It has to be able to cope with hundreds of thousands, possibly millions, of users and this constitutes no small task. The system will however be run by the Post Office, and will be

similar to that used for TV licences. Licences will be available at the counters of most Post Offices as well as by post from the central record keeping agency. Renewals will be dealt with in the same way. We have made good progress and there is no reason to suppose that the licensing system will not be ready to operate in the autumn. We have not yet established the licence fee; clearly it will have to cover the quite considerable costs involved in setting up a licensed CB service and dealing with the associated interference, but we have no intention of pitching the fee at a discouragingly high level.

We are giving some thought to the conditions of use. We shall want to make these as simple as possible and while it will be necessary to include standard conditions such as the usual prohibition on grossly offensive transmissions and on advertising or soliciting for business, we intend to make the conditions less restrictive than in most other radio transmitting licences. There are many points for consideration; for example, should the licensee be enabled to allow members of his household and his employees to operate his CB equipment, and how many items of equip-

ment should be covered by the licence fee? What arrangements should be made to control the use of equipment hired out by the licensee? It will be advisable to ban the use of CB equipment in aircraft: should any further restrictions be placed on where CB equipment is used, or are such matters better left to a code of practice to be negotiated with the CB organisations? All these matters have to be settled before the licensing system comes into effect.

To sum up, our aim has always been to have a legal service in operation by the autumn. This has dictated an extremely tight time-table; a complex licensing system has to be created and millions of licence forms and fee stamps have to be designed, printed and distributed. Manufacturers and importers have to know the permitted standards so that they may design, manufacture and market the equipment accordingly which means in turn that the order banning all 27 MHz equipment has to be amended. In addition we have to produce regulations on the criteria that will have to be met to prevent interference to other authorised services.

We are on course to complete all these stages in time. I have no doubt that legalised CB will give a great deal of pleasure to a large number of people, including many who have at present no thought of using such a facility. It is the Government's hope that with this credible alternative to the illicit equipment now in widespread use the many CB enthusiasts will turn to it and continue to enjoy their hobby with approved equipment that will reduce the amount of interference to other users of radio."

FUNCTION GENERATOR



The TG102 Function Generator is the latest product complementing the Thandar range of test instruments.

It is mains operated and has a frequency range of 0.2Hz to 2MHz producing sine square and triangle waveforms plus d.c. from a variable amplitude 50Ω output. TTL output is also provided. External sweep facility is available enabling >1000:1 frequency change within a selected range.

The TG102 comes complete with mains lead and 1 year warranty and costs £145 plus VAT.

A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA (01-624 8582).

MARKET PLACE

Items mentioned are available through normal retail outlets unless otherwise specified. Prices correct at time of going to press.

SAFGAN 'SCOPE

Safgan Electronics has recently introduced a new range of reasonably priced high performance dual trace oscilloscopes.

Designated the DT-400 Series, these oscilloscopes cover a bandwidth range from 10MHz to 20MHz, and all models have vertical sensitivities from 5mV/div to 20V/div in 12 calibrated 1-2-5 steps. DT-400 series is made up of the following models; DT-410 10MHz at £169. DT-415 15MHz at £175. DT-420 20MHz at £188 (all prices plus VAT).



Time base speed for all models range from 0.5s/div to 200ms/div in 18 calibrated 1-2-5 steps; the fastest sweep speed can be expanded by x5 to 100ns/div.

All three have Z-modulation and XY facility providing matched X and Y inputs. The series offer Bright Line Auto, Normal and TV field triggering modes with a sensitivity below 0.5 div for internal triggering sources which can be CH1 or CH2 and 100mV for external source. Trigger Level and (+)ve, (-)ve slope selection are also incorporated.

Safgan Electronics Ltd., 56 Bishop's Wood, St. John's, Woking, Surrey, GU21 3QB (04862 66836).

CASIO GO PRO



Following the success of Casio's first keyboard instrument, the Casiotone 201, Casio have now brought out its successor, the 202, which incorporates many refinements and can really be classed as a professional instrument.

The 202 has the same size (49 note) keyboard as the 201, and the same 8-note polyphony and method of voice selection. That, really, is where the similarities end.

Casio have added many new voices and duplicated some of the old ones from the 201 giving a total of 49 (the 201 had 29). Brass string and organ voices are particularly realistic.

Moving the control panel from the right to the left-hand end of the keyboard may not appear to be a great step forward, but for anyone playing at a gig it's a considerable advantage.

The 202 performs well as a home entertainment instrument, as it is very compact and has a built-in speaker and amplifier. However, it really comes into its own when used by the professional or amateur musician playing in a group—either as the player's sole instrument or as an add-on to another keyboard such as an electric piano.

The Casiotone 202 is available at a discount price of £275 (inc. VAT and p&p) from Tempus, Dept PE, 164-167 East Road, Cambridge CB1 1DB. (0223 312866)

New Government Green Paper on Copyright Reform...

A green paper giving the Government's views on future copyright reform was published on July 15. Mr Reginald Eyre, Parliamentary Under Secretary of State, who announced the publication, stressed that it was a green paper, and that it invites public reaction on a wide range of issues covering all aspects of copyright.

Points likely to be of particular interest to readers are: that the Government has not been convinced that it would be right to introduce a levy on audio and video recording equipment or blank tapes (this had been suggested to compensate for loss of royalties due to illegal copying), and, as regards computing, the Government proposes that all forms of stored program—i.e. on magnetic tape or in ROM—should receive complete copyright protection.

Briefly...

P.c.b.s for many PE projects are now available while you wait from Crofton Electronics Ltd. Crofton inform us that they can make up most p.c.b. designs very quickly, and callers can wait for single boards. They can also supply by mail-order. Crofton Electronics Ltd., 35 Grosvenor Road, Twickenham, Middlesex TW1 4AD.

● ● ● ●
Program Power the Leeds based software company are to produce a new magazine for Nascom enthusiasts. Called Micro Power the magazine will contain articles on a wide range of hardware and software topics.

The first issue will appear in August and will include articles on the design of a programmable character generator and the start of a series on interfacing printers to Nascom. The magazine is priced at 95p including p&p.

Program Power, 5, Wensley Road, Leeds, LS7 2LX.

● ● ● ●
Electronic kit manufacturers Powertran Electronics, who are known in particular for their musical designs, inform us that their 1981/82 catalogue is available free on request. It contains comprehensive details and photographs of all their kits as well as a current price list.


Powertran Electronics, Portway Industrial Estate, Andover, Hants SP10 3NN (0264 64455).

● ● ● ●
A new low-cost thermal printer has been introduced by Cricket Peripherals.

Features of the Cricket 101 include self-test initialisation message after power on, 97 characters including £ sign, single or double width selectable from control codes, quiet operation and simple mechanics. The standard interface is Centronics parallel, and there are optional interfaces available for PET, Apple, Nascom and Sorcerer. Other interfaces will be available soon.

The Cricket 101 is priced at £199.50 including VAT, carriage (mainland) and one roll of paper. Interfaces are priced at £35. Cricket Peripherals, 92 London Road, Knebworth, Herts.

ADVANCED IRON

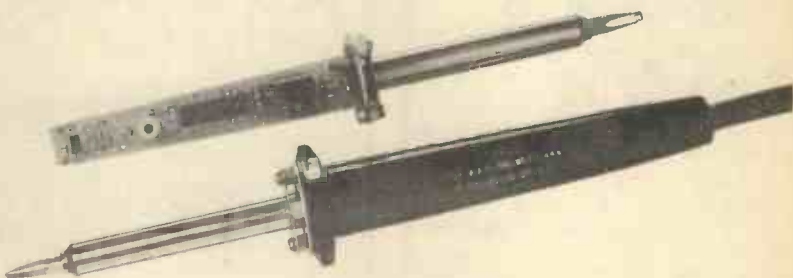

An electronic thermostat in Adcola's new 444 soldering iron is claimed to eliminate all the problems experienced by users of mechanically controlled soldering tools.

This soldering iron has been designed to operate off the majority of 24V 50Hz 50VA soldering stations, and has the control circuit contained in the handle. The temperature is fully adjustable within the range of 220°C to 420°C.

Adcola attributes the success of this instrument to the fact that the circuit contains an i.c. manufactured to their own design and specification. Incorporating a zero-crossing switch which eliminates switching transients, it controls the bit temperature through a thermocouple and a triac. The heating element has no magnetic effect and the instrument can be earthed.

The soldering tool is supported by a range of more than ten iron-plated 3/16"/4.75mm dia. profiles of soldering bits/tips.

As an introduction, Adcola is currently offering two evaluation kits at a special reduced price. Kit 1 comprises of the 444 instrument, a selection of 5 long-life bits/tips and a safety stand for £21.00, and Kit 2, without the safety stand for £17.00. The normal one-off price of the Unit 444 is £18.50, with the usual discounts for quantities.

Adcola Products Ltd., Adcola House, 113 Camden Rd., London SW4 6LH (01-622 0291).



BECKMAN 310

A hand-held 3½ digit multimeter, the Tech 310, has been added to the range of instruments manufactured by Beckman. The multimeter features a 2000 hour battery life, continuity and semiconductor test functions and overload protection on all 26 ranges.

Measurements can be made across five d.c. voltage ranges from 200mV to 1500V full scale; five a.c. voltage ranges spanning 200mV to 1000V full scale; five a.c. and d.c. current ranges, 200µA to 2A full scale (a separate input extends the range to 10A); and six resistance ranges with full scale values from 200 ohm to 20 Mohm.

The 310 is priced at £99 plus VAT and p&p Beckman Instruments Ltd., Electronic Components UK Sales, Mylen House, 11 Wagon Lane, Sheldon, Birmingham B26 3DU.

MARKET PLACE

Thorn erect Satellite Receiver

With satellite broadcasting of telecommunications and TV soon to become a reality in some of its export markets and interest in the medium developing in the UK, Thorn Consumer Electronics Limited have erected a 3 metre dish satellite receiver aerial at their Enfield engineering laboratories to establish a reference source for experimental satellite signals and for evaluation of various aerial technologies.

Each European country has been allocated five possible channels for satellite transmissions and both France and Germany are scheduled to begin direct broadcasting by satellite in 1984. In the UK, the Home Office has suggested that two out of the five available UK satellite channels could start broadcasting although a commencement date has not yet been fixed. A recent Home Office publication, indicated that a DBS system could operate four years after a go-ahead decision is taken.

POINTS ARISING . . .

EPROM PROGRAMMER (Jan. '80)

There is an error in the printed circuit layout as shown in Fig. 2.1, and the following correction should be implemented to make the track layout conform with Fig. 5 (December 1979): the track which serves \overline{CS} of IC5 and IC6 (pin 8) should be cut before it reaches the junction serving the link L7. Having been severed, the \overline{CS} track should be surface wired by hand to connect to IC13 pins 4 and 5. It will be found easiest to refer to component overlay diagram Fig. 2.3.

DIGITAL DESIGN PART 1 (Aug. '81)

Due to printing problems a number of errors crept into the first part of this article.

Fig 1.5 The 'new functions' should read $\overline{A} \overline{B}$, $\overline{A+B}$, $\overline{A} \overline{B}$, $\overline{A+B}$

Fig 1.6 The 'voters' column should read C B A (left to right)

On page 44 second column it should read 'Hence, $Q=A \overline{B} + \overline{A} B$. Expression number 8 just below should read $\overline{A} \overline{A} = \overline{A}$

At the bottom of the same page when we are looking at the truth table, the second and fourth lines should read: $A+B$ is the same as $\overline{A} \overline{B}$ and $A+B$ is the same as $\overline{A} \overline{B}$

On page 45 second column above Fig. 1.7a, we should read $A+B$ is the same as $\overline{A} \overline{B}$

On page 46 under 'Filling in the map', the first paragraph should read: we can say that the column=1 if $A=1$ AND $B=0$, so the column is $\overline{A} \overline{B}$

EPROM PROGRAMMER (Aug. '81)

In Fig. 1, R4 should go to pin 20 and not pin 21. In Fig. 2, R4 should be connected to comply with the revised Fig. 1. Also, there is an unnecessary break in the stripboard track at F24 which should be removed.

COLOUR BOARD REVIEW (Aug. '81)

Our apologies to Chromasonic Electronics of North London for mis-spelling their name throughout this article.

CAPACITANCE METER (July '81)

The connection from IC1 pin 6 to pin 7 (see Fig. 2) is absent from the p.c.b. diagram of Figs. 4 and 5. This connection should be made for correct operation.

Countdown . . .

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below.

Harrogate Int. Fest. of Sound Aug. 15-18. Royal Hall Exhibition Centre & Hotels. X

Solar Energy Exhibition Aug. 23-28. Brighton. M

BEX Cardiff Sept. 3-4. Centre Hotel. K

Business & Light Aviation Sept. 3-5. Cranfield Airport. Z1

Microprocessor Workshop Sept. 7-8. University of Liverpool. D

Laboratory Sept. 8-10. Grosvenor House, Park Lane, London. I

Personal Computer World Show Sept. 10-12. Cunard Hotel, London. M

West of England Electronics Show Sept. 15-17. Bristol Exhibition Centre. Q

Microtest Sept. 21-24. (Symposium) Kent University, Canterbury. S1

Business Telecoms & Electronic Office Sept. 23-25. Royal Lancaster Hotel, London. O

BEX Edinburgh Sept. 30-Oct. 1. Assembly Rooms. K

Viewdata Oct 6-8. Wembley Conference Centre, London. O

BEX Bristol Oct 14-15. Exhibition Centre. K

Video Show Oct. 16-18. West Centre Hotel, London. Z1

International Business Show Oct. 20-29. NEC Birmingham. A2

Testmex Oct. 27-29. Wembley Conference Centre, London. T

Computer Graphics (Ex. & Conf.) Oct. 27-29. O

BEX Southampton Nov. 4-5. Polygon Hotel. K

Viewdata & TV User Nov. 4-6. West Centre Hotel, London. Z1

Breadboard Nov. 11-15. Royal Hort. Halls. B7

IFSEC (Fire & Security) Nov. 17-19. RDS Dublin. V

Compec Nov. 17-20. Olympia, London. Z1

Electronics Nov. 17-20. Olympia, London. I

BEX Plymouth Nov. 18-19. Holiday Inn. K

INTRON Nov. 24-26. RDS Dublin. V

There are continuous events and permanent exhibition at the National Micro & Electronics Centre. L1

1982

Electronics OEM Assemblies Feb. 2-4. Royal Hort. Halls, Westminster, London. T

Electronic Test & Measurement March 30-April 1. The Forum, Wythenshawe. T

Laboratory, Edinburgh March 30-31. Assembly Rooms, George Street. E

Sensors & Systems March 30-April 1. The Forum, Wythenshawe, Manchester. T

Laboratory, Manchester April 7-8. New Century Hall, Corporation Street. E

All Electronics Show April 19-21. The Barbican, City of London. E

A2 Hart Browne & Curtis ☎ 01-439 8556

B7 Modmags ☎ 01-437 1002

D Liverpool Univ., Brownlow Hill, PO Box 147

E Evan Steadman, Saffron Walden ☎ 0799 22612

I ITF, Solihull ☎ 021-705 6707

K Douglas Temple, Bournemouth ☎ 0202 20533

L1 World Trade Centre ☎ 01-488 2400

M Montbuild Exhibitions ☎ 01-486 1951

O Online, Northwood, Middx. ☎ 09274 28211

Q Exhibitions for Industry ☎ 0883 34371

S1 Sert ☎ 01-403 2351

T Trident, Tavistock ☎ 0822 4671

V SDL ☎ Dublin 763871

X Exhibition & Conference, Harrogate ☎ 0423 62677


Z1 IPC Exhibitions, Sutton ☎ 01-643 8040

Conquer the chip.


Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

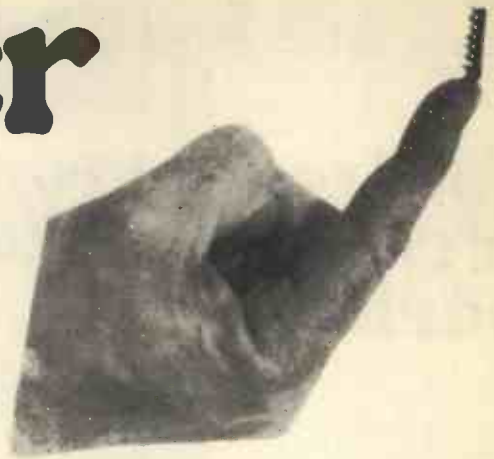Learn the technology of the future today in your own home.




MASTER ELECTRONICS

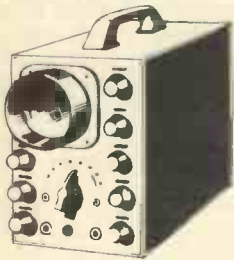

LEARN THE
PRACTICAL WAY BY
SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

MASTER COMPUTERS

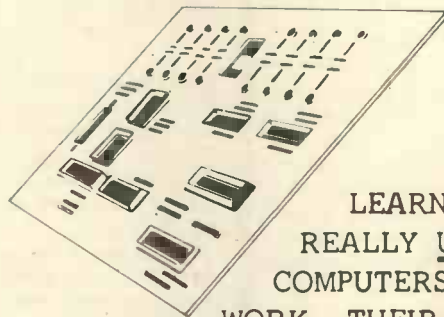

LEARN HOW TO
REALLY UNDERSTAND
COMPUTERS, HOW THEY
WORK - THEIR 'LANGUAGE'
AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.

FREE

Please send your **FREE** brochure without obligation to:-

Name

Address

.....

.....

BLOCK CAPS PLEASE

I am interested in :-

PE/9/811

PRACTICAL ELECTRONICS

COMPUTER TECHNOLOGY

OTHER SUBJECTS


(please state your interest)

.....

.....

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

READING, BERKS. RG1 1BR.



INDUSTRY NOTEBOOK

By Nexus



we are doing quite well. Taking as a yardstick the number of network termination points (NTPs), i.e. the interfaces between user equipment and the PTT services, Britain is leading the field in Europe by a handsome margin.

I take the figures from the last Eurodata Report which was researched in 1979. The United Kingdom was top user with 117,000 NTPs, followed by West Germany (61,700), France (54,000) and Italy (45,500). The also-rans at the bottom of the league were Ireland (966), Portugal (794), Luxembourg (649) and Greece (639).

Of course these figures are misleading for obvious reasons. Tiny Luxembourg with a population of only 356,000 people would clearly need less NTPs in total than the United Kingdom with its 56 million population.

A more realistic league table can be constructed by re-casting the figures as the number of NTPs installed per thousand of the working population. The UK then emerges with a figure of 5.2 per 1,000, still well ahead of West Germany (2.87), France (3.03) and Italy (3.16). Note that the three runners-up to the UK in the four biggest countries have now changed order with Italy rising and West Germany dropping from second to fourth in the big country group.

But in this new formulation, if we include all 17 countries in the Survey, the UK drops to second position behind Sweden with its 5.66 NTPs per 1,000 and is only marginally ahead of little Luxembourg (5.15) which has almost miraculously climbed from next to bottom to the number three spot.

Eurodata, when it crystal-balled in 1972 on what would happen in 1979, underestimated the growth rate of data communications by 100 percent. Undeterred by such a gross error, or perhaps inspired by it, the crystal ball has again been employed, this time to forecast the figures for 1987.

In 1987 the UK will still have the largest number of NTPs (377,000) of any country in Europe and Sweden will still be top of the NTP per 1,000 league table with a figure of 26.4. But, sadly, in this table the UK will have dropped back to sixth place (16.8), having been overtaken by Luxembourg (23.9), Switzerland (22.2), Belgium (21.3) and the Netherlands (17.0). Note that the top five are now all small countries. But of the 'big four' of UK, West Germany, France and Italy, the UK will still be top on either calculation.

Overall growth rate for Europe in installed terminals is forecast at 26 percent per year but only 10 percent in hardware value, confirming once again that electronics is the only field in which hardware costs relatively consistently fall.

Looking at the above figures a conclusion may be drawn that salesmen have been busy and potential users have snapped up opportunities offered. And that the UK, far from needing YIT, could teach the rest a few wrinkles. On reflection YIT may yet prove a boon if only to provide extra employment for exhibition specialists, advertising copywriters, printers and organising committees.

Honesty compels me to add a final footnote. If the forecast for 1987 is correct, top of the league in Europe, Sweden, will by then only have achieved the same level of usage as in the United States today.

First Hoppers

A major triumph for Britain was the launch of Racal's Jaguar-V VHF combat radio, claimed to be the world's first anti-jamming frequency-hopping transceiver. Already in production, it was a little ahead in time against Marconi's Scimitar, a similar private venture development, and is still well ahead of the United States Sincgars-V project. Racal has already taken orders for the British Army and for three other NATO countries. At this stage one assumes the orders are in sample quantities for field trials and evaluation by the armed forces concerned.

Racal is said to be in negotiation with other customers and forecast a sales potential for Jaguar-V running into hundreds of millions of pounds over the next ten years. Competition, however, will be fierce. The Marconi Scimitar was publicly shown within a month of the Jaguar launch and will be attacking the same market.

New Knights

Two new electronics Knights Bachelor were in the Queen's Birthday Honours list. They were Godfrey Hounsfield, 'father' of the EMI body-scanner and a Nobel prizewinner, and Ernie Harrison, chairman and managing director of Racal Electronics Group for his services to export. One a brilliant scientist, the other an outstanding man of business, both have served their country well.

Aerospace

Electronics was well represented at the Paris Air Show. A British breakthrough, shown publicly for the first time, was the holographic head-up display (HUD) which Marconi Avionics has developed for the United States Air Force for fitting in F-16 multi-role fighters and A-10 close-support tank-busters. The new HUD enables these aircraft to operate safely at low altitudes in total darkness.

British exhibitors came home with another £300 million of orders, mostly for export, of which about one third will find its way to the electronics industry. A good show in both senses.

Competition

The break-up of British Telecom's total monopoly is certainly having a galvanising effect. Nearly a thousand salesmen are to be recruited and trained by Telecom and will actually be given targets to attain and bonuses to be earned in the business sector where competition will be hottest. No need for a sales effort for the private user. There are still some 300,000 hopeful residential customers awaiting connection although, we are promised, they will not be forgotten.

Showbiz

So 1982 is to be designated the Year of Information Technology! I shall call it YIT and I'm already wondering just what it will do that wouldn't happen of its own volition.

My scepticism is based firmly on precedent. Older readers may recall the famous National Plan which foundered after a few months. The era of the White Heat of Technological Revolution left most of us stone cold.


National Productivity Year also left the nation unmoved. This was spread over 1962 and 1963 when Britain had the lowest percentage increase of national product per man-year than any other industrial nation. Japan, West Germany and Italy, the three defeated nations of World War 2, were already racing away with their respective economic miracles.

Sixteen years later Britain was still at the bottom of the productivity league table in heavy industry and the long period of drift ended only when harsh reality affected job prospects. In retrospect, National Productivity Year with its 1,500 separate events staged to explain the meaning of productivity, why an increase was necessary for national survival, and how to achieve it, was a waste of time.

Will YIT prove to be more effective? The Government is to top up the taxpayers' contribution to new electronics technology to £200 million. Not to be sneezed at but peanuts compared with the billions still being poured into nationalised steel, coal, railways, shipbuilding and BL.

Data Communications

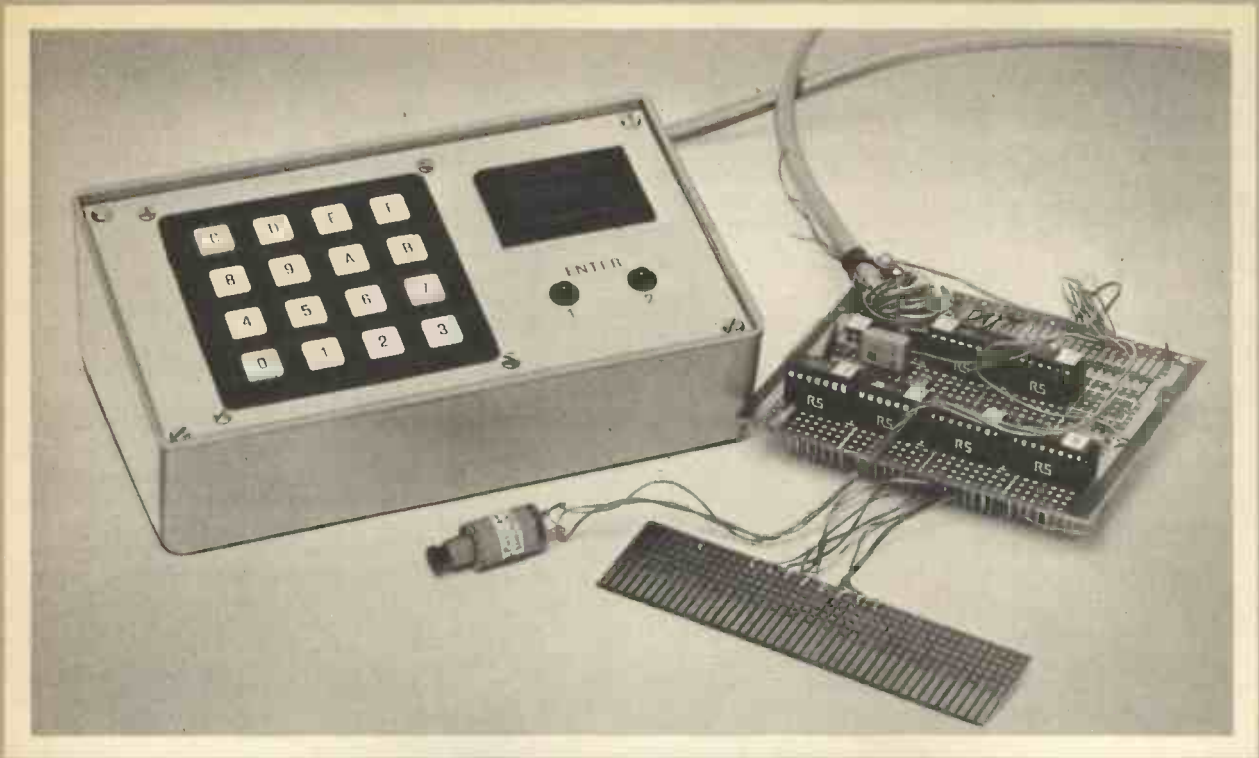If we really need YIT the assumption must be that we are lagging behind in information technology and need a good kick up the backside. If we look at data communications, the heart of the matter, in fact



REMOTE KEYBOARD

J. LEWIS

MICROCOMPUTERS are fine and great fun—especially for the first few weeks or even months when they are a novelty—but the honeymoon period wears off and one starts to wonder what useful purpose they can be put to. An obvious application is in the home, to provide control of the various systems e.g. heating, lighting and security. However, if this is to be done it becomes obvious that the microcomputer itself has to be located away from prying fingers which could so easily key in incorrect instructions or operate the Load or Reset switches and cause a horrendous crash. What is needed is a remote keyboard designed to be idiot-proof.

The circuit described here was specifically designed for a Elf II microcomputer to allow different modes of operation to be selected, and accept the entry of a six digit security code. The circuit (Fig. 3) is applicable to other microcomputers though the actual interfacing may differ according to input/output lines available. First thoughts might suggest that the new keyboard could be daisy chained to the existing one, but this raises all sorts of problems, not least that of the Input or Enter key. Many people find difficulty in accepting the concept that you actually need to "enter" the digit into the computer. This might be one reason why reverse polish notation as used on Hewlett Packard calculators never took the mass market by storm. What is needed is a keyboard which tells you what to do, and when it has been done automatically enters it into the microcomputer. The following circuit does just that.

HOW IT WORKS

A matrix type keyboard is used which has 8 output lines, four of which are connected to the columns and four to the rows (Fig. 1). When any key is depressed a unique contact is

made between one of the columns and one of the rows. Such keyboards are designed to be used in conjunction with a special decoder integrated circuit. Two of the most popular being the 74C922 and the 74C923. These are CMOS devices and can handle either a 16 key or 20 key keyboard respectively. For this application 16 keys were sufficient and so the 74C922 is ideal.

A block diagram of the 74C922 is given in Fig. 2. By connecting a capacitor between pin 5 and $-ve$ the internal oscillator is enabled so that the keyboard matrix is scanned to detect any key closures. Key bounce is, thankfully, eliminated by connecting another capacitor between pin 6 and $-ve$. The decoded output from the keyboard is present in BCD form on pins 14 to 17. As a keyboard entry is made so the "Data Available" line, pin 12, goes high and returns to low when the key is released even if another key is depressed. After the normal debounce period it will go high again indicating the acceptance of another entry. The 74C922 has tri-state capability on its 4 data output lines thus enabling it to be connected directly to a data bus. This tri-state feature is controlled by pin 13 which, when high, ensures the data outputs present a high impedance to the bus. On grounding this pin the decoded output from the keyboard—which has been stored in internal latches within the i.c.—is put on to the bus. In this particular application the tri-state mode is not required and so pin 13 is grounded.

The output from this i.c. is only half a byte wide and whilst software could handle it, the sensible course is to offer a whole byte at a time. This is easily done using a quad D type register such as the 4076. By connecting the clock line of this i.c. to the Data Available output of the 74C922 data can be latched into the 4076, thus giving the full byte required

which has a ROM monitor, cassette interface, provision for RS232C interface, an 8 bit parallel input port, an 8 bit parallel output port, decoding of the 14 input/output lines as well as address decoding for additional memory up to 64K. The other sockets accept 4K RAM boards etc. Thus one can easily build up a microcomputer which will readily interface with the real world. Tiny and extended BASIC are also available but in this particular application machine code was used.

To connect the remote keyboard to the Elf the following procedure was used though obviously there is no need to use the actual flag or input lines indicated since others serve the same purpose. For other microprocessors the system can be adapted to utilise the facilities they have. The Byte Ready signal from the 4013 was inverted using a 4011 and connected to the EF3 flag line. These flags are software monitored and when the appropriate signal is present a branch can be initiated. The interrupt line could also have been used and would have given a slightly faster response. The byte itself is read by sending a pulse originating from the 6D input instruction to the remote keyboard circuitry. This Read signal not only enables both the 4066 (IC3) and IC1, although this needs an inverted signal, hence the use of IC5, but also resets the flip-flop (IC4). Thus the input from the keyboard is entered into the computer and can cause a branch to a particular routine. It is helpful to repeat the byte entered on a display at the keyboard so that the user can see what has actually been accepted; not only does this allow any keying mistakes to be corrected but also serves as a reminder as to which routine is currently running. The additional circuitry for this is given in Fig. 4. Note that the driver i.c.'s for the two i.e.d.'s must be capable of decoding the full four line BCD into hexadecimal format—figures 0 to 9 and letters A to F. The 9368, a t.t.l. device, will do this. Some only decode the numerical portion whilst others give a different character set, for example H,E,L,P.

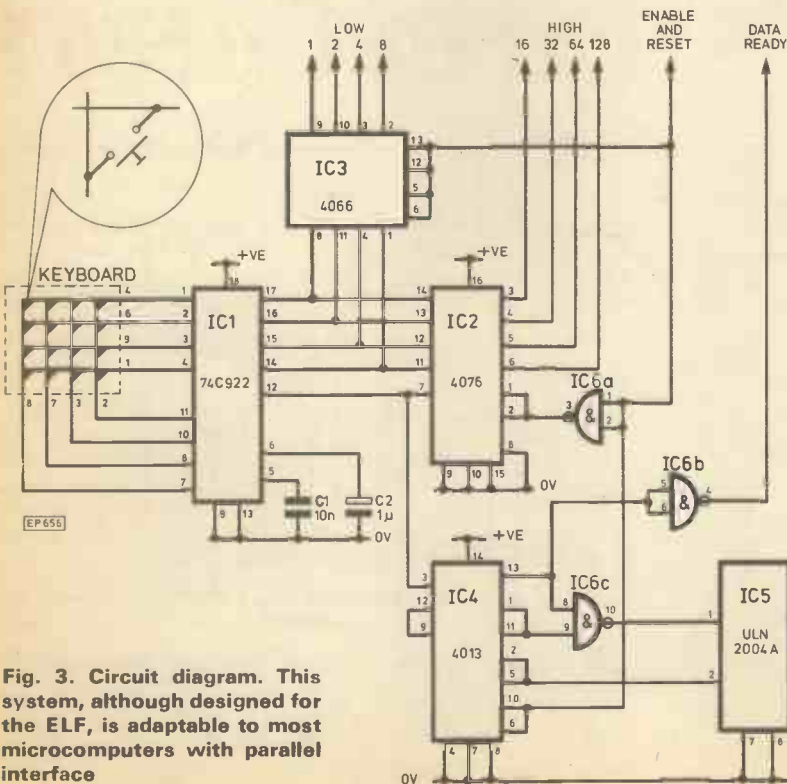


Fig. 3. Circuit diagram. This system, although designed for the ELF, is adaptable to most microcomputers with parallel interface

Example of entry program for the Remote Keyboard using the ELF

```

00 90
01 B3
02 F8
03 A0
04 A3
05 E3
06 3E
07 06
08 6D
09 64
0A 30
0B 06

```

Initialisation

Short branch if EF3=0

Input—enable/reset line goes high

Echo input to display on Elf motherboard*

Branch back

* May not be required.

LOCATION

Whilst this is called a remote keyboard the actual decoding circuit must be as close as possible to the microcomputer itself to minimise the length of the bus lines joining them. Shielded multicore cable can be used for interconnections to the keypad and displays, though ribbon cable is equally suitable.

When the six digit security number is being entered the user needs to be reminded which pair of digits are currently being entered. Again i.e.d.'s can be used with suitable labels and, with the other i.e.d.'s already provided for individual digit entry, makes the use of driver i.c. worthwhile. A suitable one is the UL2004 which incorporates an internal resistor allowing direct interface with CMOS circuits. These 3 i.e.d.'s

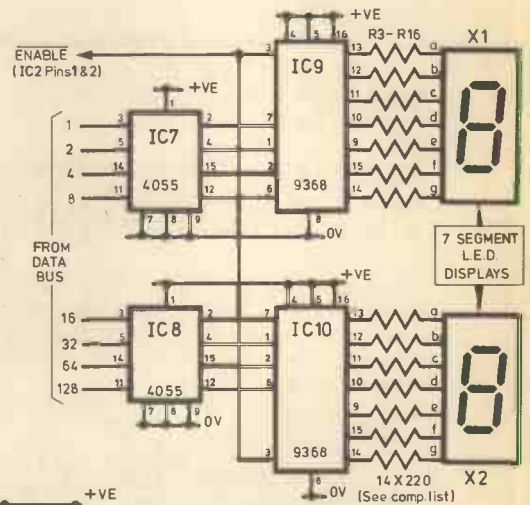


Fig. 4. Additional circuitry for 7-segment display

NOTE

The prototype was wire-wrapped on stripboard to suit space and other constraints. Since layout is not critical, no drawing is given because construction will largely be a matter of conforming to application requirements.

SWITCH POSITION	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
	Y1,X1	Y1,X2	Y1,X3	Y1,X4	Y2,X1	Y2,X2	Y2,X3	Y2,X4	Y3,X1	Y3,X2	Y3,X3	Y3,X4	Y4,X1	Y4,X2	Y4,X3	Y4,X4
D																
A	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
T	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
A	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	1
O	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
U																
T																

Table 1. Truth table for keyboard decode

should be under software control using three of the bits available from the 8 bit parallel output port on the Elf's Giant Board. As each pair of digits is entered it is checked but not repeated in the display and the program ensures that all 6 digits are entered before any indication that the number is wrong is given. Thus a person could not obtain the code by looking over the user's shoulder nor is any indication given as to which pair of digits is incorrect thus increasing the security aspect. If necessary another I.e.d. could be used to show a wrong sign and this could be derived from a spare bit on the output port. Software counts the number of attempts made and also the time taken. If either exceeds a preset number the computer refuses to accept any more security entries and would only respond to the two digit routine entries, one of which would override the block on security numbers.

Other remote keyboards could also be added, say, at the front and back doors, in the kitchen should any household functions need controlling etc., thus ensuring that what started out as an expensive toy actually does earn its keep. At the same time you will be one of the few people who have entered the silicon age with a micro that does practical tasks and can understand the instructions of dumb humans. ★

COMPONENTS ...

Resistors

All resistors for a 5 volt supply are 220/270 ohms

Capacitors

C1 10n poly or disc
C2 1µ tant.

Integrated Circuits

IC1 74C922
IC2 4076
IC3 4066
IC4 4013
IC5 ULN2004A
IC6 4011
IC7, IC8 4055 (2 off)
IC9, IC10 9368 (2 off)

Diodes

D1-D6 red
Displays red (check segment connections before use)

Keyboard

16 key matrix type

PE CASE COUPON

I enclose two completed case coupons cut from PE, a 30p postal order made payable to IPC MAGAZINES LTD., and a 15½p stamp. Please send me an extra instrument case.

NAME

ADDRESS

Only available to UK and BFPO addresses, allow 28 days for delivery. Incorrect or incomplete orders will be returned.

Extra Cases!

30p (plus postage) To Regular Readers.

FOLLOWING the Free Case gift with the May issue we have a quantity of cases available as extras to regular readers (at UK and BFPO addresses only) for 30p plus postage—the normal price from Lascar is £1.95 plus VAT and postage.

Extra cases—as used to house the Digital Thermometer, Digital Multimeter (May '81); PE Minitune, pH Meter, Continuity Tester (June '81); Capacitance Meter, Light Meter, and Noise Meter (July '81)—can be obtained from PE by sending in two correctly filled-in case coupons (name and address on both coupons please) cut from PE, a 30p postal order and a 15½p stamp (a case coupon is given here). **We can only accept 30p postal or money orders (NOT CURRENCY OR CHEQUES).** Do not enclose any correspondence. **Incorrect or incomplete orders will not be accepted**—your stamp will be used to return them.

Send two completed case coupons cut from PE with your 30p postal order (payable to IPC Magazines Ltd), and a 15½p stamp to:

PE Instrument Case Offer, IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset. BH15 1JG.

Sorry we cannot undertake to send extra cases to overseas readers.

PLEASE ALLOW 28 DAYS FOR DELIVERY.

SPEECH RECOGNITION SYSTEM

OR

HOW KATRINA GOT BIG EARS

BY ANTHONY YOUNG

THE advertisement announced **BIG EARS** in bold capital letters making me wonder if this was a joke from Toy Town; however, a quick scan of the text showed that this was another product from William Stuart Systems. As I already own an audio oscilloscope and a colour graphics system from the same stable I felt confident that my £45 + VAT was not going to buy a toy. I confess to being somewhat relieved that when I unpacked my parcel less than a week later the name Big Ears was not on the brushed aluminium front but in its place an impressive "Speech Recognition System Interface SR1."

Big Ears or SR1 can be connected to any personal computer like NASCOM, TRS 80, PET, UK101, Superboard or to any other via a spare user input port. In my case, an 8K UK101, hooking up couldn't have been much simpler with just five connections to be made. Five core ribbon cable and standard 5 pin DIN plug are provided so plugging in the SR1 is quite straightforward. Power requirements are low so the +5 volts needed comes from the motherboard via the ribbon cable. All this is explained in a very clear User Manual containing Connection Details, Software Loading Instructions, User Instructions, Demonstration Software, Theory of Operation and BASIC Software Listings. A small part of the software is written in machine code and is provided in a form to suit the most popular 6502 or Z80 based systems.

The purpose of the SR1, if you hadn't guessed, is to provide speech input to your computer and open the door to direct man-machine communication. For anyone who has formed a close interpersonal love affair with their computer (yes Ursula Katrina 101 is a person) then giving her Big Ears could well extend a beautiful relationship. To be more exact it is more like one Big Ear in that her ear comes in the form of an electret condenser microphone plugged into the smart aluminium fascia of a black metal case 15cm x 12cm x 5cm using a standard jack plug. Relationships can blossom in that with a speech recognition system it's conceivable that one's computer could be verbally commanded to execute various options in robot control, games programs, etc. Captain Kirk could command "Fire" to zap the Klingons or a remote controlled vehicle could be requested to move "Forward", "Back", "Left" or "Right". It is even conceivable that I could flirt with Ursula Katrina via an interactional conversation program in which she would only have learned (and thus understood) my voiceprint; such faithfulness!

The minimum amount of memory required by the SR1 is 5K but since machine code real-time input routines are loaded into the top of user memory the last one K must be located in the 8th

K sockets leaving the 5th, 6th and 7th sockets empty in the UK 101/Superboard. However, now that 2114 Rams aren't so expensive one might as well upgrade to 8K unless funds are very tight. 8K will allow a larger vocabulary to be stored.

The demonstration software (BASIC) is very interesting providing correlation tables for the words learnt and a 5 x 6 two-dimensional array of numbers as the individual word's "voiceprint". During the learning stage the computer asks for the word to be spelled and then spoken. The spoken word should be repeated 4 to 8 times to achieve optimum recognition and the voiceprint is printed each time. It is naturally important to speak clearly and consistently. Having taught the computer a number of words it is then possible to test its recognition. It can have problems understanding the difference between Fine, Pine and Wine but less problems distinguishing between Apples, Pears and Raspberries. The computer compares the voice it hears with its averaged memory voiceprints and perceives you to have said the word which has the highest correlation. It signals its understanding by printing "You said Raspberries" or whatever. Both the correlation table and voiceprint printout can be deleted by removing lines and the computer's response can be tailored to individual needs.

The computer's voice perception is based on frequency analysis of the first and second formants of the speech waveform. The interface unit SR1 separates the formants and delivers digital values to the computer which then performs frequency analysis for each of sixty-four 16ms sampling periods. This is implemented in machine code. For each period the two formant counts are then compared against threshold data values to determine which frequency ranges are present. The two range indices are then used to determine which location in a two-dimensional array will be incremented. Thus the sixty-four 16ms samples must all fit in this two-dimensional histogram forming a kind of "frequency-space". To learn a word four or more such histograms are averaged and normalised to have a mean value of zero with a uniform standard deviation. The resulting averaged voiceprint-histogram is stored for future correlation.

If necessary the sensitivity of the SR1 can be adjusted by going inside the cabinet with a small screwdriver and adjusting a preset potentiometer; clockwise to increase and anti-clockwise to decrease. The systems software is listening for the first sound in order to start sampling but if the system is too sensitive it could be triggered by background noise. In noisy environments this adjustment is very useful as sensitivity can be set low and the speaker can speak up. Don't clear your voice or stutter because Ursula (or whoever) will be less than understanding about it. Moreover one should remember that with sixty-four samples of 16ms any phrase or word to be learnt should not last longer than about one second. This is quite okay in practice as long as one avoids Welsh railway station names.

If one wishes to use the SR1 in the application of data enquiry (which might need a large vocabulary) then the secret of success is to use key words to define which group of words the computer can expect you to be using next. In this way the computer need only compare the word it hears with a reasonably small group of words and the chance of misunderstandings is thus correspondingly reduced. Words which the computer might confuse can be located in different groups. Vocabulary, therefore, can grow like a tree. An example of this is a Travel Reservation System which might initially ask "Inland, European or Intercontinental?" Each of these headings might access 8 or 10 destinations with further destinations to be found by "Other" always being one of the options.

In conclusion Ursula Katrina's Big Ear might not be quite as perceptive as a human ear but then it's not such fun to nibble either. Notwithstanding that I'm still convinced that she's got the hot-heatsinks for me... "Love me Katrina?"... "I DO HONEY"... If only things could always be that easy.

CHATTER-BOXES SERVED HERE.



Realistic is the biggest name in Citizens Band Radio and accessories – and you will be able to buy the full range at Tandy – the world's largest retailer of CB equipment!

REALISTIC®
CB from Tandy

Has seven years of success gone to our heads?



NEW IMPROVED

MINIMAX 2

With the Minimax II, Videotone revolutionised the market by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2, retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

POPULAR HI-FI

"Switching to the Minimax's from any of the others produced an open and natural sound as though something had been taken away. It had, the colouration had gone." Comparative test OCTOBER 1975.

HI-FI ANSWERS

Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound so big!" JANUARY 1975.

PRACTICAL HI-FI & Audio

"The depth, clarity and openness of sound produced is quite astonishing". JUNE '75

WHAT HI-FI

"... the ability of the Mini-

max to take a lot of power and still sound good could be decisive" - Comparative test, APRIL 1977.

PRACTICAL HI-FI

The little Videotone scored highly for such a small inexpensive loudspeaker". JANUARY 1981.

Specification:

Recommended amplifier power: 10 to 40 watts rms into 8 ohms.
Frequency Response: 80Hz - 20KHz ±5dB.
Finish: natural teak, veneer with black frets.
Size: 10 7/8" high, 6 3/4" wide, 7 1/2" deep.
Weight: 4.1 Kgs (9 lbs) each.

ONLY £69.95 A PAIR

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

VIDEOTONE 98 CROFTON PARK ROAD LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4. PE 9

NAME _____

ADDRESS _____

MICRO TIMES

19 Mill St. Bideford, North Devon EX39 2JR
Telephone Bideford (023 72) 79798 (Dept. PE3)

★ ★ ★ THIS MONTH'S SUPER SAVERS ★ ★ ★

TTL and CMOS RANGE available September 81

MEMORIES

2114 450ns	1+	25+
2114 300ns	£1.30	£1.25
From Toshiba TC5514P	£1.45	£1.40
4K (1k x 4) 450ns	£3.65	£3.45
CMOS RAM 5101	£3.45	£3.40

4116 200ns	1+	25+
4116 150ns	£1.20	£1.18
HM6116P-3 (18k 150ns)	£1.70	£1.65
	£15.50	£15.25

6809 single Board Computer *kit*

Complete kit £160 plus 15% VAT. £1 P&P. Uses Motorola's powerful MC6809 CPU. 4K/8K/16K ROM. 2K RAM. ACIA, PLA, 8000 simulated I/O, RS-232 Handshake, 8 sel 8aud Rates, Manual includes; 11 x 17in. Schematic parts list, User notes. Software listings and more!

Bare Board £48**
Uses 6809: 6850: 6821 - buy set for £18.50
ADMONS (2716) £24.00
Data available. S.a.e., please.

Low Profile D/Face Wipe DIL Sockets.

40 pin	39p
28 pin	29p
24 pin	25p
22 pin	24p
18 pin	20p
16 pin	18p
14 pin	16p
8 pin	12p
Quantities 100+	
Discount 5%	

LINEAR IC'S

NE555	18p
NE556	50p
RC4136	55p
LM301AN	26p
LM311P	48p
LM318	£1.50
LM324N	43p
LM339N	43p
LM348N	80p
LM358P	40p
LM380	65p
LM3900N	48p
LM3914	£2.10
LM3915	£2.10
LM13600	£1.20
SN76477N	£1.70

ENCODER/TRANSMITTER

LM1871	£1.90
--------	-------

RECEIVER/DECODER

LM1872	£1.90
--------	-------

VOLTAGE REGULATORS

7805	5V	55p
7812	12V	55p
7905	5V	60p
7912	12V	60p
	100mA	5V
78L05	5V	29p
78L12	12V	29p
	500mA	
79M12	12V	64p
79M05	5V	64p
723		32p

THYRISTORS

CT106D	28p
--------	-----

TIL's

TIL32	45p
TIL209 red	19p
TIL232 green	18p
TIL212 yellow	16p
TIL216 red	18p
TIL228 red	20p
TIL220 red	12p
TIL24	16p
TIL31	£5.50
TIL312/3	£1.00
TIL321/A	£1.15
TIL330/A	£1.15

CPU's

6502	£5.45
6504	£7.25
6802	£5.70
6809	£15.00
8080A	£4.15
8085A	£6.45
Z80	£5.45
Z80A	£5.80

SUPPORT DEVICES

6520	£3.15
6522	£5.00
6532	£7.60
6810	£2.50
6821	£1.90
6845	£15.00
6850	£1.95
6852	£3.30
8212	£1.75
8216	£1.75
8228	£3.95
8255	£4.00
Z80CTC	£4.25
Z80PIO	£4.25
Z80ACTC	£5.40
Z80APID	£5.40
Z80DMA	£16.00
Z80ADMA	£18.00
Z80S10/0	£18.00
Z80AS10/0	£24.00
Z80S10/1	£18.00
Z80AS10/1	£24.00
Z80S10/2	£18.00
Z80AS10/2	£24.00

SN76477N SOUND CHIP

£1.70

A single chip versatile SOUND EFFECTS GENERATOR SN76477N is ideally suited for applications such as arcade or home video games, alarms, sound effects boxes and toys. DATA 50p Large S.a.e.

£4.50

EPROMS

2708 450ns	£2.55	£2.50
2716 450ns	£2.65	£2.60
2732 intel type		£9.90 each

Buy 5 off for £49.00

AY-3-8910 GI SOUND COMPUTER CHIP

Features:
-Full software control of sound generation.
-Interfaces with most 8-bit and 16-bit microprocessors.
-3 independently programmed analog outputs.
-Two 8-bit general purpose I/O ports.
-Single +5 volt supply.

SPECIAL PRICE £6.95

Data 50p. Large S.a.e. please.

Data £1. Large S.A.E. please.

INTERSIL ICL 7660 £2.25

Voltage Converter. Now ex-stock.

★ Simple conversion of +5V Logic supply to ±5V supplies.

★ Simple voltages multiplication (V out = -In/Vin).

★ 99.9% typical open circuit voltage conversion efficiency.

★ 98% typical power efficiency.

★ Wide operating voltage range 1.5V to 10.0V.

★ Easy to use, requires only 2 external non-critical components.

DATA AVAILABLE 50p. Large S.a.e. please.

JUST ARRIVED FROM VERO

S100 Prototyping Boards.

Microboard Pattern 06-2175L £16.40*

Square Pad Universal Pattern 06-2338F £16.40

Prototyping Board for your APPLE/IT2020 £8.37*

FLOPPY DISC CONTROLLERS

FD1771 £19.50

FD1791-2 £32.00

WD1691D £14.50

WD2143-01 £5.00

*SPECIAL Complete Pkg. £50

includes FD1791-2 + WD1691D.

+ WD2143-01.

Individual Data available 50p per copy.

Large 50p S.a.e. please

Set of Data on the above £3.

COMBO CHIPS

Intended for Z80 Usage.

Z80 Combo Chip (MK3886) 2 1/2 meg. £25.00

Z80A Combo Chip (MK3886N-4) 4 meg. £29.95

ANTEX SOLDERING IRONS

Model CX17W £4.25

Kit SK.1 15W. £6.00

incl. base/stand + solder.

Kit SK.3 17W £6.00

Kit SK.4 25W £8.00

SK.3 and SK.4 complete with stand.

MLX Repair Kit can be used where no main elects available £4.80

VEROBLOC SOLDERLESS BREADBOARD

360 reliable contacts.

Will accommodate any size of IC.

Can be fully interlocked one with another.

SPECIAL PRICE £3.55 each.

KITS FOR BEGINNERS

AROUSE THE MICRO CHIP INTEREST IN THE YOUNGSTERS STARTER KITS.

ULTRONIC FLY REPELLER

A must for campers.

Features:
-LED indication.
-Pocket size case.
-Low Power consumption.

Kit + all parts + case with instructions for easy assembly. Battery not included.

£4.50

LIGHT ACTIVATED SWITCH

Used for automatic lighting control, elec. appliance control, electronic gun burglar alarm and auto-open door system.

Switch on/off 200W elec. appliances.

Kit + parts + instructions for easy assembly.

£3.50

ELECTRONIC WHEEL OF FORTUNE

Fun Kit.

Easy to assemble.

Case included.

Wonderful game.

£5.00

ORDERING INFORMATION

Please add 50p P&P.

Plus 15% VAT to all orders.

EXPORT ORDERS ACCEPTED.

Add 15% P&P on total order. VAT not applicable.

ACCESS/BARCLAY CARD WELCOME.



It is our policy to offer you brand new full spec. devices.

Prices subject to change without notice.

Schools, Colleges, Univ. Official Orders Welcome.

Practical Electronics

September 1981

NEXT MONTH... FREE I.C. REMOVAL TOOL

WITH EVERY U.K. ISSUE




New Series: **ROBOTICS**

DON'T MISS
PART 1

INDUCTIVE DISCHARGE CAR IGNITION PROJECT

Plus... **HOROLOGICUM**

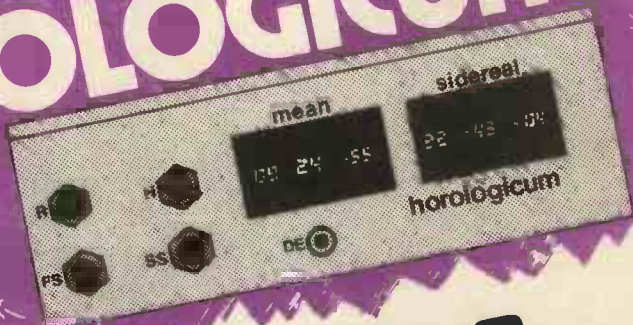Knowledge of the celestial co-ordinates and Local Sidereal Time enables an astronomer to find any object in the sky. This article describes a portable "star clock" which indicates both GMT and Local Sidereal Time.



Also... **HEADPHONES WITH A DIFFERENCE**

Use of normal stereo headphones gives rise to the "outside the head effect". This headphone amplifier provides some of the original sound perspective.

PRACTICAL

ELECTRONICS

OCTOBER ISSUE ON SALE FRIDAY SEPTEMBER 11th

Analogue FREQUENCY METER

Andy Flind

A FREQUENCY meter is a most useful item of equipment for the experimenter's workshop, but hitherto the choice of design for amateur constructors has been somewhat limited. Broadly speaking, there are two normal approaches to the problem; digital, in which cycles are counted over a fixed period and digitally displayed, and analogue where a pulse of fixed width is generated by each cycle and the pulses fed directly into a meter. The digital method is very accurate but is also complex and expensive; too much so for many would-be constructors. The analogue approach is far simpler and cheaper, but in general cannot measure frequencies much beyond 100kHz, and the accuracy, particularly at the higher end of this range, is usually so poor that it cannot be considered as much more than a toy.

HYBRID APPROACH


By combining these two techniques, a hybrid instrument can be built which falls nicely between the two above types in terms of accuracy, cost and complexity. The approach chosen for this project was to build a basic analogue with a fixed range of 0 to 100kHz, since at this low frequency calibration is simple and excellent accuracy can be obtained, and then extra ranges were added by prescaling with cheap C-MOS decade divider stages. Fig. 1 shows a block diagram of the instrument. The input signal is amplified and squared to make it suitable for driving digital circuitry, and it is then fed to four divide-by-ten stages. Each CMOS chip contains two such divider stages and costs less than one pound, so that the cost of providing extra ranges in this way is very reasonable indeed. The actual degree of division required is selected by a switch and the signal then passes to a monostable generating a fixed-width pulse for each cycle fed to it. These pulses could be mechanically integrated by feeding directly into the meter, but the linearity is improved


and meter flicker at low frequency reduced by the use of a further integrator circuit. A voltage regulator provides a constant supply voltage to maintain accuracy as the battery gradually deteriorates. It was intended originally to attempt to obtain an accuracy of 2% from this project; however, on test against a digital instrument it has proved better than 1% over most of its range, which is probably more than sufficient for most experimenters. The maximum frequency that can be measured with the top range is 1MHz.

The complete circuit diagram appears in Fig. 2. The power supply is similar to that used in *PE Magnum* metal detector projector, the main differences being the use of a 1458C dual op-amp, and the addition of an l.e.d. to indicate battery failure. The bias current required by TR2 in this circuit is normally too small to light an l.e.d., but when the supply voltage drops too far the bias circuitry saturates in an attempt to correct the output and the bias current jumps to about 10mA—just right for lighting the lamp. This semi-discrete circuit was used in preference to a three-terminal i.c. regulator, as firstly it delivers a symmetrically split output, ideal for op-amp circuitry, and secondly, it will function until its input is only a fraction of a volt above the required output, very useful where the current is supplied by batteries. Most i.c. regulators need a differential of at least two volts to operate.


The input signal is amplified and shaped by IC2, R7 and R8 provide positive feedback so that the output of this stage is never linear but switches rapidly from rail to rail. It will handle any input waveform. The minimum input that will operate it is about 200mV; at about 600mV protection diodes D1 and D2 start to conduct and clamp the level fed to IC2, so the maximum input voltage that can be applied is about 200V peak-to-peak, after which R6 would start to overheat. In practice, a maximum input of 50V is suggested.

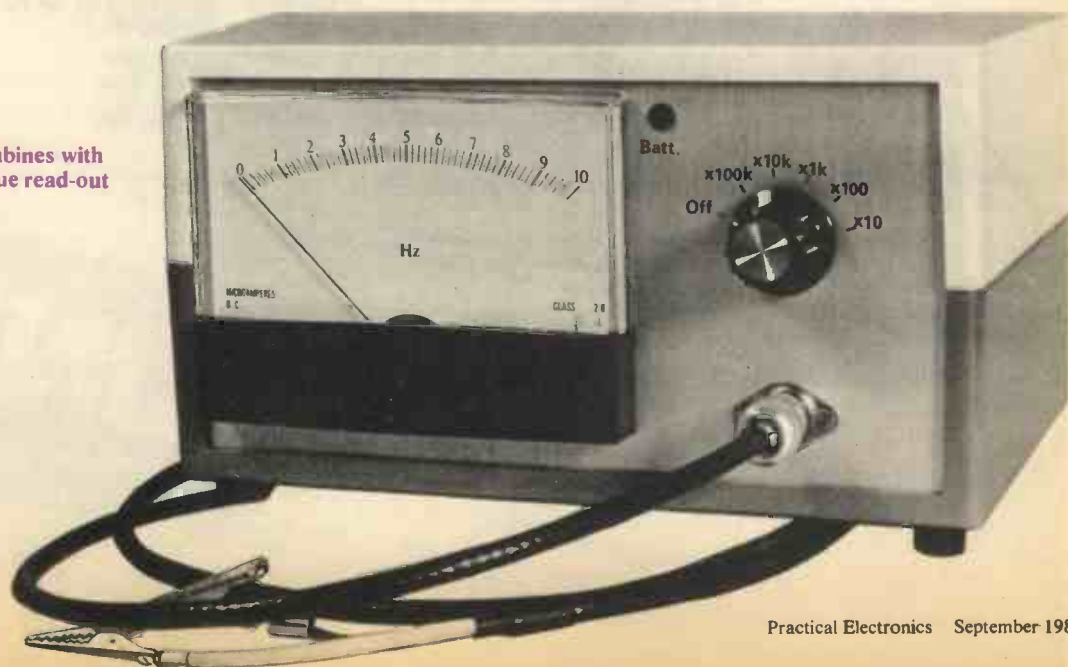Digital accuracy combines with
quantitative analogue read-out




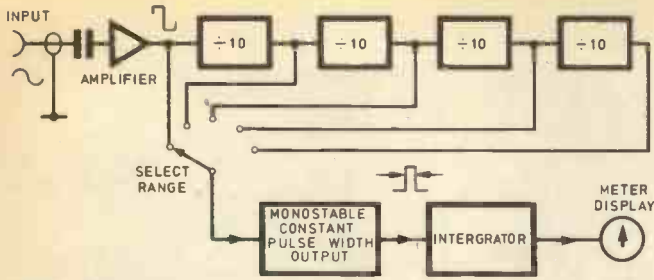

EG674 Fig. 1. Block diagram

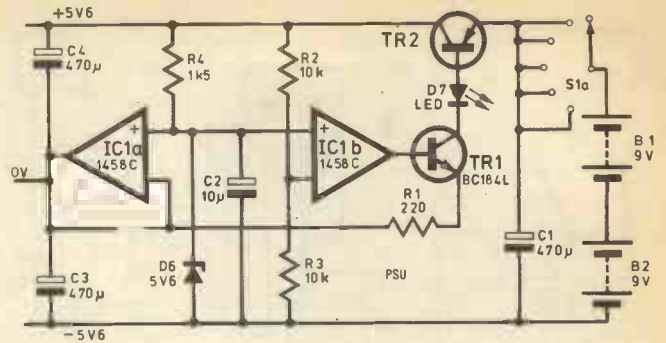

EG673 Fig. 2. Circuit diagram

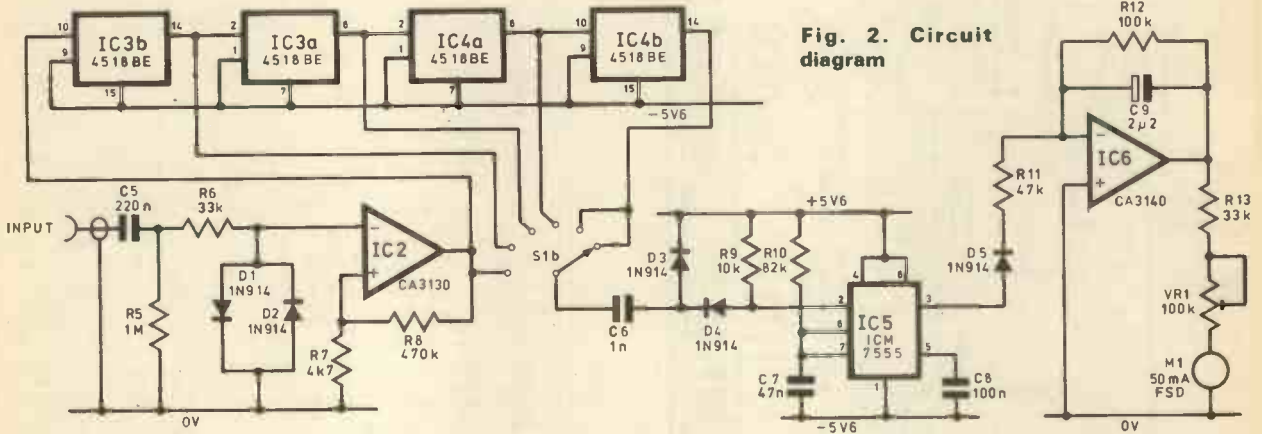

EG672

On test, this input circuit has been found reliable to beyond 1.2MHz. Two C-MOS 4518 dual decade dividers are ripple-cascaded to give four stages of division by ten, providing the instrument with a total of five ranges. The required output is selected by S1b. Capacitor C6, D3 and D4, and R9 differentiate the signal to provide short negative spikes for triggering the monostable timer IC5. If the input frequency is too high for the range selected, the period of the input signal to the timer may be shorter than the timer's output period, and in this condition the timer will trigger on multiples of the input cycles. To prevent false readings due to this, the timer period must be less than half the shortest input period expected, so that for any excessive input frequency the meter will simply read f.s.d. plus. The period of a frequency of 100Hz is 10mS, so R10 and C7 have been chosen to give a timer output about 4mS.

IC6 is essentially an integrator with a discharge resistor R12 across its capacitor. The inverting input will be maintained at 0V, so each timer pulse dumps a fixed packet of current through R11 into C9, regardless of the output voltage. This output voltage will, of course, alter until the current out through R12 balances the net current coming in through R11. VR1 and R13 were selected to provide a suitable f.s.d. point on a 50µA meter since this is readily available. Other meters may be used if the values of these two resistors are suitably altered. The use of an integrator confers two advantages; firstly the linearity of the output is improved, and secondly there is less needle flicker on the meter. In fact, the flicker is not apparent at all above 5% of meter scale.

CONSTRUCTION

All the electronic components for this project are mounted on a single p.c.b. It is suggested that this board is constructed in stages, testing at each step so that any problems can

be easily traced and dealt with as they arise. Start by fitting the five wire links on the board, followed by the power supply components R1, 2, 3, and 4, C1, 2, 3, and 4, ZD1, TR1 and 2, and IC1. Temporarily connect the l.e.d. and connect up the battery supply, preferably through a 100 Ohm resistor, which will limit the current somewhat if a fault is present. Check that the output voltages are correct. The l.e.d. will not light unless the supply voltage falls to around the 11V2 total output voltage. If there is no output, first check that l.e.d. and Zener polarities are correct.

Continue the construction with the input stage; R5, 6, 7, and 8, C5 and 10, D1, D2 and IC2. Apply power and an a.c. input of around half a volt. In many cases the house wiring induces a.c. and a wet finger will do. Then check the output from IC2 pin 6. This will appear on the link just above the i.c. and can be monitored with an oscilloscope, or heard as a loud buzz on an earphone (use a d.c. blocking capacitor). If it doesn't work, check R7 and R8 first, its easy to confuse the colours on these resistor values. Now go to the other end of the circuit and construct the integrator, with R11, 12 and 13, VR1, C9 and 12 and IC6. Temporarily connect the meter and supply, and check that the meter goes to zero. If you place one wet finger on the top end of R11 and another on a +5V6 point (positive end of C4) you should get a reading on the meter. If this works, fit the timer components R9 and 10, C6, 7, and 8, D3, 4 and 5 and IC5. Attach all the wires for the range selector switch and connect the two most right-hand ones together. Inject a 50Hz input using a few volts from a mains transformer. The meter should read, and VR1 can now be used to set it to mid-scale. This is the only calibration adjustment required for this project! If all seems correct, complete the board with C12 and the two divider chips, observing the usual C-MOS handling precautions. Use sockets for these two if you prefer, although on the prototype they were soldered directly to the board. The other ranges can be checked by shorting each switch lead in turn

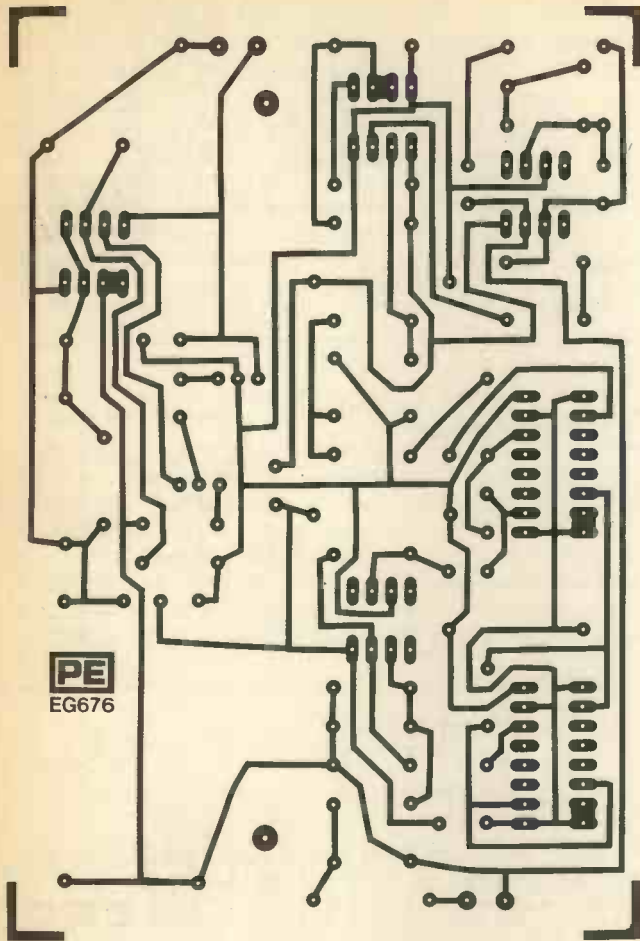


Fig. 3. Printed circuit

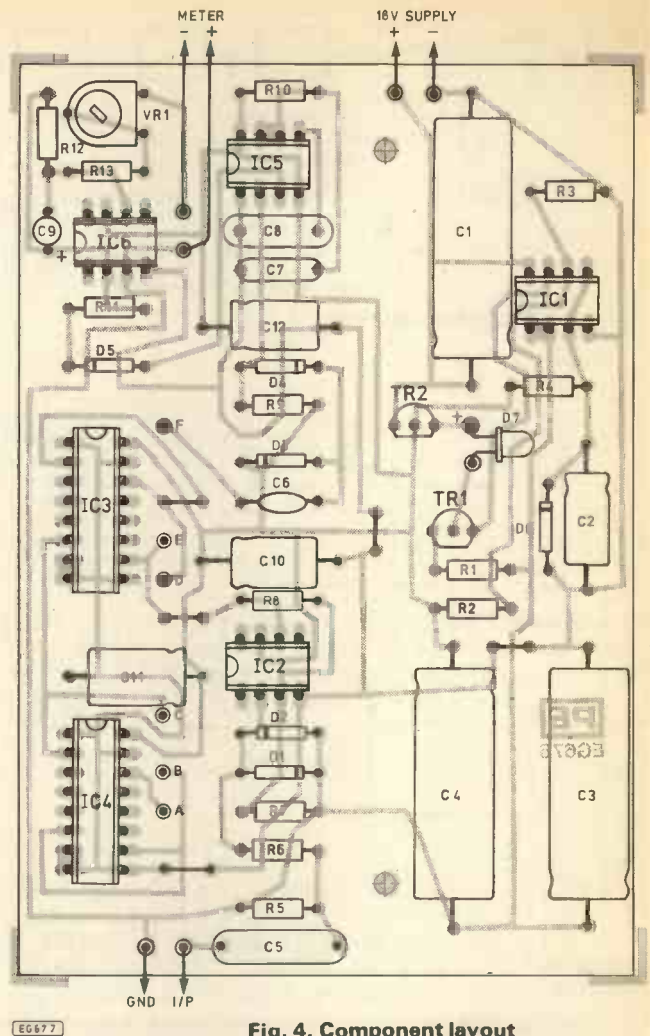


Fig. 4. Component layout

COMPONENTS ...

Resistors

R1	220
R2, 3, 9	10k (3 off)
R4	1k5
R5	1M
R6, 13	33k (2 off)
R7	4k7
R8	470k
R10	82k
R11	47k
R12	100k

Potentiometers

VR1	100k sub-min hor. preset
-----	--------------------------

Capacitors

C1, 3, 4	470 μ 25V electrolytic (3 off)
C2	10 μ 25V electrolytic
C5	220n polyester
C6	1n ceramic plate
C7	47n polyester
C8	100n polyester
C9	2 μ 2 25V tant. bead
C10, 11, 12	1 μ 63V electrolytic (3 off)

Transistors & Diodes

TR1	BC184L
TR2	BC214L
D1, 2, 3, 4, 5	1N914
D6	BZY88C5V6 5V6 400mW Zener
D7	TIL 209 red.


Integrated Circuits

IC1	1458C
IC2	CA3130
IC3, 4	C-MOS 4518BE
IC5	ICM7555
IC6	CA3140

Miscellaneous

P.c.b.
 Switch S1, 2 pole 6 way
 Meter, 0-50 μ A FSD
 Case, Verobox, Vero part no. 202-21036G, 205 x 140 x 110mm
 Coax socket
 Tagstrip
 Control knob
 2 x PP3 battery clips

Fig. 5. Inter-connections

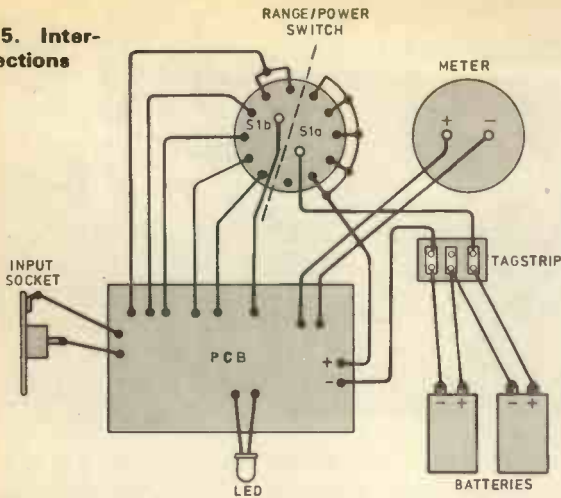

EG975

to the lead furthest to the right (the timer input), and applying an appropriate input signal. Alternatively, they can be functionally checked with a 50Hz input, as the meter needle will give a small kick for each timer pulse on any range. Note that on the top range, however, a 50Hz input will only give one kick every 200 seconds. If these ranges are working at all, though, they are automatically as accurate as the basic

100Hz range.

The board is designed to mount directly into the specified Verobox using two of the self-tapping screws provided. An "L" shaped aluminium bracket is fitted to the other end of the box with the other two self-tappers, and this holds the batteries firmly against the box side. The total drain of the circuit is only about 12mA so a pair of PP3 batteries is a perfectly adequate source of power. The meter is the large four-inch scale 50µA unit available from Maplin, chosen for its large clear scale, and also because this scale has 100 divisions. A little careful work on the scale plate with typing error ink and a letter transfer sheet provided the appropriate markings. The meter, switch, i.e.d. and input socket are all mounted on one of the aluminium panels, and interconnected as shown in Fig. 5. A small piece of tagstrip is used to make the necessary connections between the battery leads. A final check and adjustment of the calibration of the lowest range should be carried out when construction is complete.

The prototype instrument has proved very accurate and useful, and is extremely simple to use. The total construction cost is somewhere around £20, but of this a very large proportion is accounted for by the case and meter. If preferred, the board could be housed in an alternative, cheaper case and used in conjunction with the workshop test meter, providing accurate measurement of frequency at even lower cost. ☆

PATENTS REVIEW...

Copies of Patents can be obtained from:
the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price £1.45 each.

IMPROVED PA

The Marconi Company of Chelmsford, Essex, has a British patent (BP 1 586 441) on a public address system which automatically tailors the reproduced sound level to the ambient noise. All too many PA systems are inaudible or unintelligible and this is largely due to incorrect sound level setting; they either distort or get lost in the background noise. Manual control is possible but cannot cope with rapid fluctuations in noise level; it is also labour intensive.

The Marconi idea relies on the well-known phenomenon whereby a moving coil loudspeaker can be used "in reverse" as a microphone. This phenomenon is already relied on in areas of strict security where there is a PA system installed. The PA system is switched into the microphone mode whenever it is not in use. An attempt to bomb one of Britain's largest cruise liners was foiled through the use of just such a system.

Fig 1.

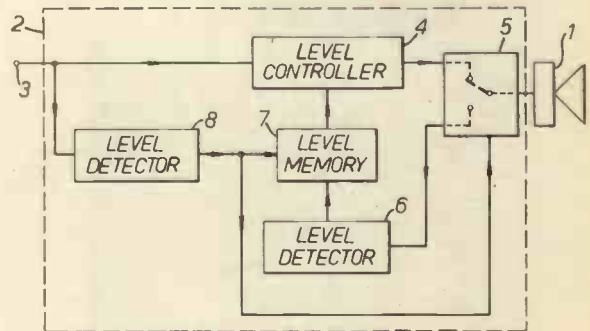


Figure 1 shows the basic Marconi layout. At a reproduction setting of switch 5, the loudspeaker 1 reproduces an audio signal from input 3. The signal is passed through a gain level controller 4. The switch 5 is held in the reproduction position whenever level detector 8 senses the presence of an audio signal at 3. When this signal disappears, or falls below a pre-determined threshold level, switch 5 changes state so that the loudspeaker 1 functions as a microphone and feeds a signal representative of the ambient background noise level to level detector 6. This detector provides a control signal

which is stored at 7. When the switch 5 changes back to the reproduction state the level memory 7 sets the gain of level controller 4 to a value which is appropriate for audible reproduction of the PA message through loudspeaker 1. The output of detector 8 also feeds memory store 7 to provide an update on the level of signal to be reproduced.

By correlation of the inputs to memory 7, the speaker 1 will produce audible announcements irrespective of the input level at 3 and the background noise in the vicinity of the loudspeaker.

THE Electronic Car

WHEN the implications of the 1970's fuel crisis finally sank home, the future for private motorised transport looked bleak. But the new decade has arrived and although the motor industry is in recession, it is facing the challenge of fuel economy legislation with a powerful new ally—micro-electronics. Instead of gloomy predictions that we would be driving around in converted milk floats (mass produced in Hong Kong), we have retained the comfort and performance levels and reduced fuel consumption.

This level of improvement has been achieved mostly by refining the mechanical design of petrol engines close to its theoretical efficiency limits. Further improvements will be more difficult and this is where the microprocessor comes in.

ENGINE CONTROL

The immediate answer to improve engine efficiency was mechanically controlled fuel injection, which had been developed to a sufficient degree in motor racing. In today's commercial environment of spiralling labour and raw material costs, hydraulic and mechanical controls are becoming more expensive to manufacture while microprocessors and associated electronics are becoming cheaper and more sophisticated.


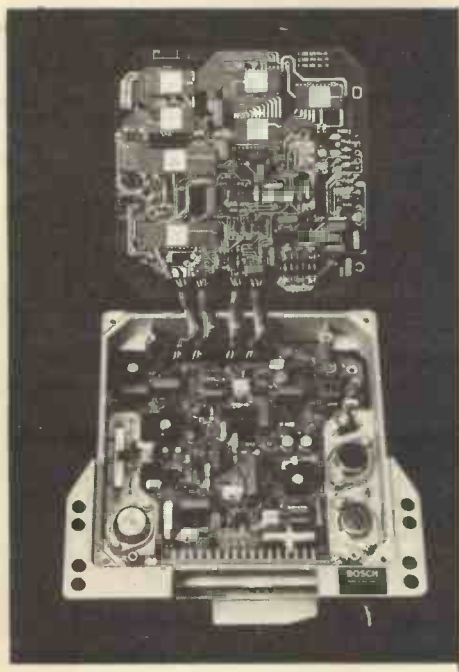



Fig. 1. (a) View of the Bosch "Motronic" electronic control unit.

Whilst a mechanical system cannot monitor any more than two input variables (say speed and load), without a drastic increase in complexity and bulk, a microprocessor can handle virtually all the information that the system generates. These can be engine and ambient temperatures, barometric and boost pressures, fuel variations and even instantaneous conditions in the combustion chambers and exhaust system. Additionally, the inherent flexibility of the microprocessor as a programmable device allows it to predict trends in ongoing conditions, such as rising engine temperature, and optimize efficiency at all moments in time. This compares with the somewhat crude correction of an unintelligent mechanical controller which is also subject to error through wear (and rust?).

Bosch, the West German automotive components group, have had in production since 1979 just such a system, called "Motronics" (Fig. 1) which is in use in certain up-market cars such as Porsche and BMW. The system controls spark ignition as well as fuel injection, exact settings are calculated from available data sampled 400 times a second. These settings are calculated using data stored in a fixed memory (ROM), which customises the module to the engine's performance characteristics, hence the system can be easily adapted for use with any petrol engine.

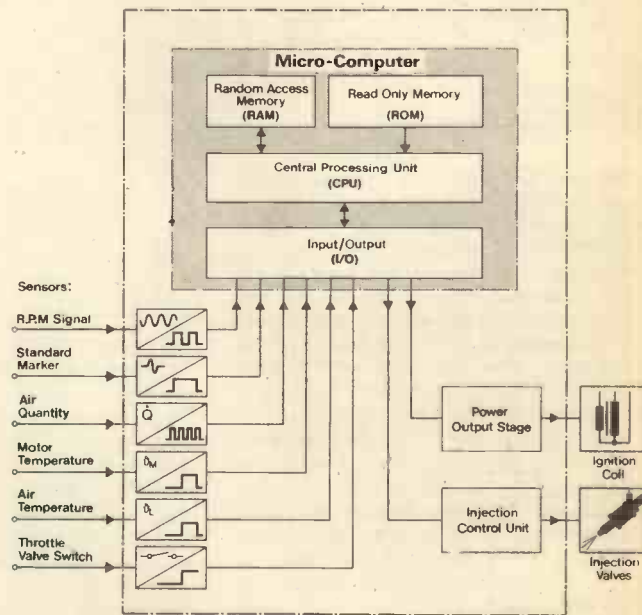

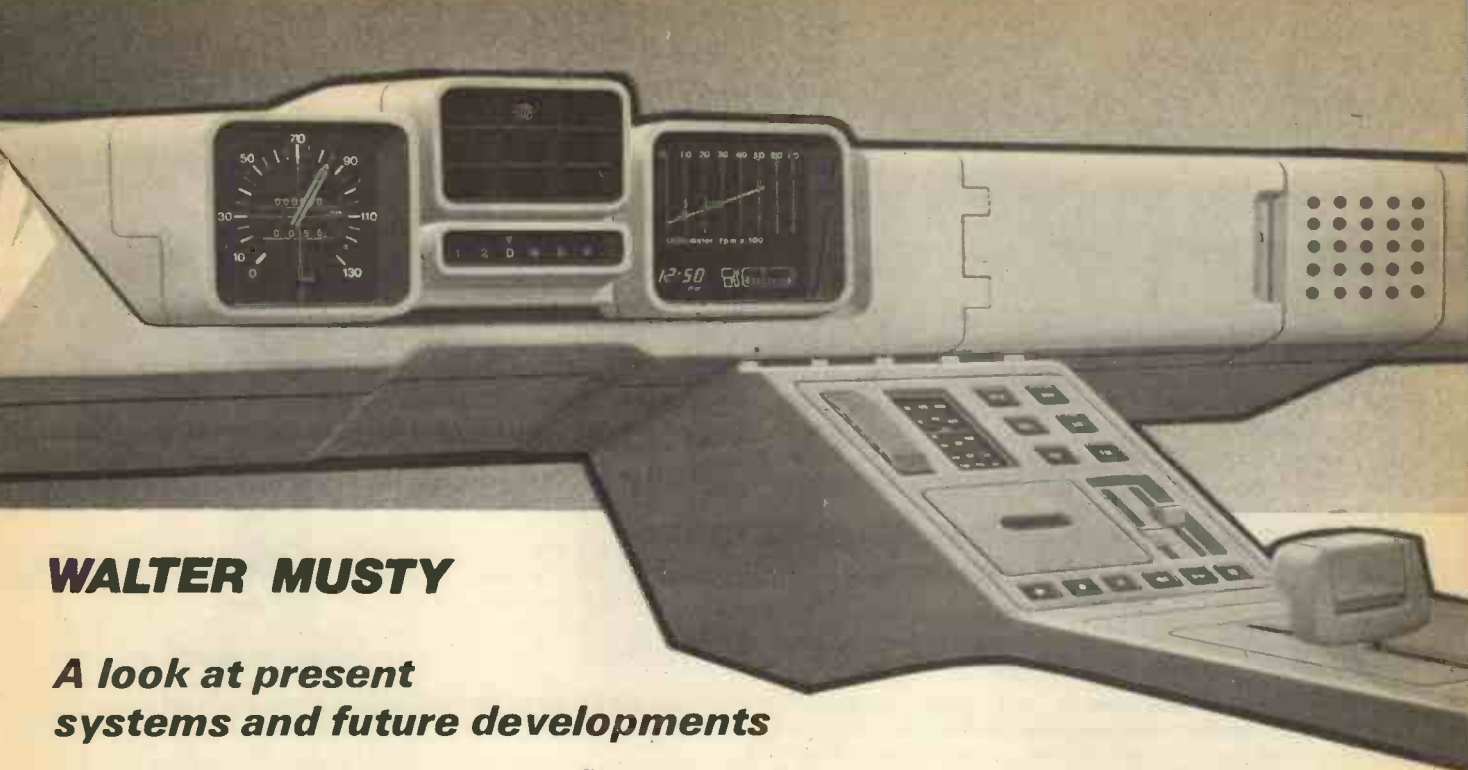(b) Simplified block diagram of the Motronic control unit. (Courtesy: Robert Bosch Ltd.)



WALTER MUSTY

A look at present systems and future developments

From its memory, the computer, with some processing, can output 4096 near ideal ignition dwell-angle settings for a particular load/speed situation. These are corrected with respect to ambient conditions such as air and engine temperature and atmospheric pressure. The same applies to fuel injection control with added functions such as fuel cut-off on the overrun (i.e. when you take your foot off the throttle), this alone gives a 5 per cent increase in economy. The system's efficiency is particularly pronounced in the case of engines which have a high compression ratio and run on lean mixtures of un-leaded petrol.

So while present claims for fuel savings are in the range of 5 to 20 per cent (dependent on the driving conditions), the system has the potential to adapt to and improve the coming generation of "clean" economy engines.

Although the microcomputer was designed around a standard microprocessor and memory chips, these and the other electronic components in the Motronic system have been selected to satisfy extreme environmental conditions. Whereas the normal operating range for commercial electronics is 0 degrees C to +70 degrees C, Bosch designers have allowed for a -40 degrees C to +130 degrees C temperature range. Mechanical impact up to 100 times the acceleration due to gravity is taken in its stride.


ELECTRICAL SYSTEM CONTROL

Apart from improving efficiency and performance, manufacturers are looking to electronics to rationalize and hence to reduce manufacturing costs of existing electrical systems in the car. The electrical wiring harness, which distributes power and controls accessories, is bulky, expensive and labour intensive to actually fit into the car during production. In use, it is also a major factor in unreliability of the car as a whole. The system planned for the future electronic car is a single power ring running around the body tapped into by solid state power switches. These will be controlled by a series digital data line.

Data transmissions are handled by a microprocessor which also interfaces with the driver's control panel. Each switch on the panel has a specific digital code which is matched to a unit on the control line. If, for instance, the rear window demister is selected, the microprocessor senses the switch closure and sends a digitally coded message down the line. Although all the units connected receive the data, only the rear window module responds to the unique code and latches its associated switch to energize the window heater element.

The module itself will be a general purpose one with several power switches, so it can be used throughout the car and control different functions which are physically grouped together. For example, the rear lamp cluster, which normally comprises driving, brake, reversing, fog and turn indicator lamps, would normally need 6 wires running the length of the car. In the digital system, the control module is built into the lamp cluster, with the power ring and data control line connected to it.

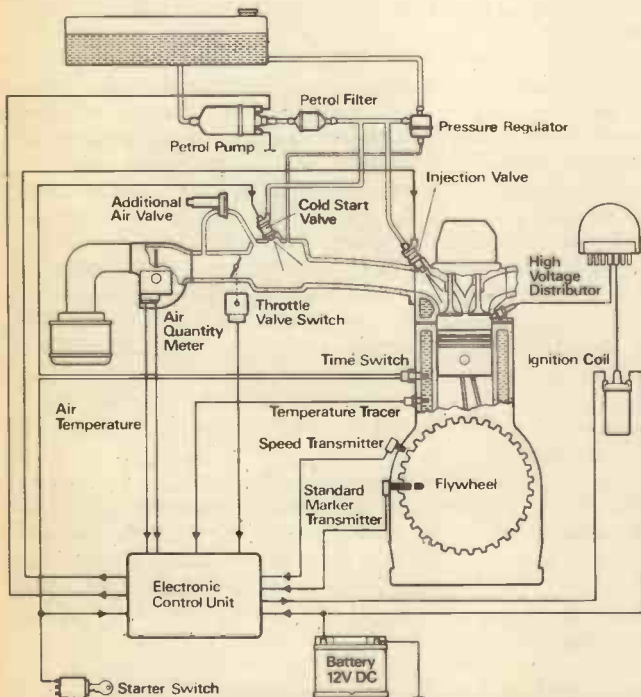When fully developed, the module electronics could well be a



(c) Diagram of the Motronic control system as used on cars such as Porsche or BMW. (Courtesy: Robert Bosch Ltd.)



Practical application of "ALI" driver guidance system, currently tested in the Ruhr area of West Germany. The display panel supplies the following information: distance to nearest petrol station; distance to nearest telephone; road hazard warnings and route directions

simple microprocessor with integral memory, a single integrated circuit which in quantity costs less than £5 at today's prices. Such a system can be further developed to be self monitoring, i.e. when a lamp is powered up the module senses this and sends a status message back to the microprocessor which gives the driver a direct panel indication.

The data message line will probably be a fibre optic cable, which transmits the codes in bursts of visible light rather than electric current. Optoelectronic sensors will replace traditional ones, such as mechanical micro switches, and will impart high reliability to more sophisticated sensing applications such as fuel/air flow and rotational speed.

ELECTRONIC DRIVER AIDS

A microprocessor makes an ideal system monitoring unit as the application requires a scan of a large number of subsystems such as fuel tank, oil pressure, engine temperature. These can be displayed continuously or only when they reach a critical value (with audible warning), the relationship between various parameters can be processed to give the driver better information without distracting him from the task of actually driving the car!

Up to now emphasis (especially in the USA) has been on fuel consumption and digital displays with GM's Tripmaster, the Ford Miles To Empty display and the Chrysler Tripcomputer. The nearest to a fully integrated electronic dashboard is Aston Martin's Lagonda, which utilizes l.e.d. technology but has no computer. AM's design department has developed an l.e.d. panel for their 200mph Bulldog, but are reluctant to introduce electronics in any other areas of their cars as the microprocessor in the first Lagonda had reliability problems.

In Europe, one of the most active companies in this field are BMW, whose top models boast an impressive range of electronics headed by the already mentioned fuel injection-ignition system designed by Bosch.

BMW's Check Control System is an on-board computer which supplements existing analogue instruments. The control panel has 12 calculator-type push-buttons and a four-digit illuminated display, each button doubles as a data entry or command function. Normally, the unit displays time but on command will display: outside temperature (with buzzer warning when below freezing point—for warning against black ice), average speeds (with preset speed limit buzzer warning),

estimated time to arrival, distance to destination, instant and average fuel consumption, and miles to empty. Additional interesting functions are digital code entry for ignition immobilization (as in cash dispensers), stop-watch function for checking acceleration, and programmable timer which can actuate the car heater before the driver actually gets in.

There are many possibilities for electronic driver comforts, a his/hers electronic seat adjustment memory is perhaps the ultimate in electronic extravagance. Perhaps the most effective driver aid is the incredible ALI system from Blaupunkt of Germany. ALI is an abbreviation in German for car driver leading and information system. The system consists of a relatively simple transmitter-receiver unit in the boot of the car, and a liquid crystal display and graphic display module with calculator push-buttons.


The roads contain aerial loops which communicate with the car's transceiver as it passes. Actual information handling is done partly in the roadside electronic control boxes, and these are all linked by cable to a large central computer which controls long-term traffic flow on the whole autobahn system.

At the moment, operation is limited to a pilot scheme covering 60 miles and 83 flyover intersections. The number of cars involved is about 400. In spite of the system's complexity, it is simple for the driver to use. The driver enters a map reference number for his destination and drives off. As the car approaches a junction, the unit gives a bleep and a simple diagram appears on its screen making it obvious whether to turn off or carry straight on. Should the driver make a mistake the unit will take this error into account and direct him to the next most direct route. If this is not worthwhile, then it indicates a U-turn at the next intersection.

The message exchanges are repeated three times to eliminate errors, the transfer takes about 20 milli-seconds which allows for cars travelling at speeds up to 155 mph. The cost of the car electronics is less than £100, but the pilot scheme has already cost £3 million. Nevertheless, the cost of converting the whole motorway system will still be only one per cent of the original construction costs.

BRAKING

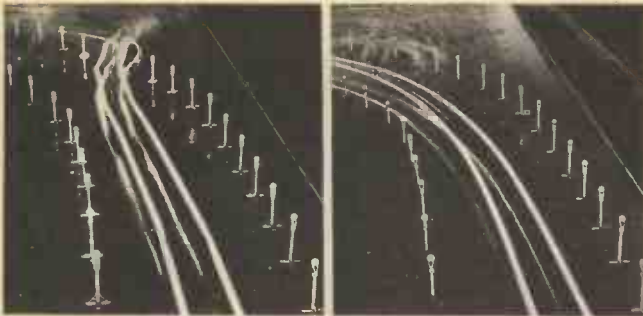Perhaps the biggest contribution of electronics to car safety is the anti-lock braking system. One system, the ABS, has been developed jointly by BMW and Bosch. ABS consists of a



This photo shows the benefits of the Bosch Anti-Skid Braking system (A.S.B.), which is the result of microchip technology. The situation is panic braking on a slippery road surface. Left: without A.S.B. Right: with A.S.B.

microprocessor and a series of sensors that measure the rotational speed of each wheel. If any wheel begins to lock, a solenoid valve adjusts brake pressure on that wheel to keep maximum traction with the road. This means the car will stop in a straight line on almost any surface, in the minimum possible distance, even if the driver applies excessive pedal pressure. In practice, ABS reduces the stopping distance on a wet road at 70 mph from 150 yards to 90 yards—well worth the £800 BMW charge as an option.

For \$6000 the infra-red goggles developed and marketed by CCS, Communication Control of New York, seem slightly worse value for money, but come in handy should the headlamps fail in an unlit tunnel. CCS can also fit your car with remote ignition control, bomb sniffer and electronic surveillance transmitters, plus the usual bullet proof windows, machine guns and tear gas ducts, all suitable for local shopping trips! With annual revenues of \$18 million, CCS seem to have carved a niche in this particular market sector, which consists mainly of extremely scared (and wealthy) industrialists or people with skeletons in their cupboards. The former Shah of Iran ordered a fully fitted Cadillac in 1979 for \$250,000 but never collected it, forfeiting his \$50,000 deposit.

With diagnostic computers in widespread use in garages, a logical progression will be to use the on-board computer to perform this task at the touch of a button. It can also give a readout of the state of serviceable items like brake pads, brake fluid and oil levels, using digital letter dashboard displays. A step in this direction has already been taken by Ford with their concept car Probe 1, the dashboard layout looking as if it may have been taken from the NASA space shuttle flight deck.

Before such a system can be fully implemented, low cost sensor technology must be further developed. Bosch seem to be the leader among car electronics firms with yet another innovative

but impressive safety feature, electronic tyre pressure monitoring. The tyre pressures are monitored in a non-contacting manner using high frequency pressure switch and sensor units, when pressure falls below a preset level, the switch stops radiating pulses which after a delay cause audible and visual warnings to be actuated by the processing unit.

COLLISION RADAR

Still in a state of early development, mobile radar is being tested in Germany with a view to helping drivers maintain correct distances between cars. The radar operating frequency is about 35 GHz. A microprocessor processes the input information and displays a correct driving speed for that particular distance. There are still quite a few problems to be overcome, for instance how to blank out spurious reflections on bends and interference from other cars working on the same frequencies.

Should the radar computer mistake an articulated lorry for a low-lying bridge, electronics still saves the day with Bosch's passive restraint control processor. It actually detects the onset



Futuristic instruments display including keyboard designed by Hugo G. Poole for Smiths Industries

of a collision and activates air bags to protect the car's occupants before death or injury; the system is claimed to positively distinguish a collision from normal driving!

THE FUTURE

When will the showrooms be flooded with these mobile amusement arcades? In the next few years we will see electronics slowly infiltrate the mass market cars just as Porsche and BMW are doing now. But it won't be until around the end of the decade before we have all-electronic computerized Cortinas available. Before then, the whole motor trade has to evolve sufficiently to cope with the service and back-up requirements of the built-in computer technology.

Labour rates for a skilled mechanic are around £12 per hour, how much will trained computer and electronic service engineers cost to the motorist? To employ such people will be unavoidable but the cost can be minimized by making the electronics in the car self-diagnostic to a large extent. This means faults will be traced as easily as they are in colour televisions, which match computers in complexity, but can be serviced at the customer's home by relatively unskilled technicians.

The design of the electronic car will have to be rationalized in a similar way with easily replaceable standard modules which if produced in large quantities can be made cheaply. The number of processors will be limited to say two, one for control and one for monitoring and diagnosis of the automotive parts and the electronics themselves. When a thorough service is necessary then the powerful garage diagnostic computers will be plugged into the car computer's diagnostic plug and will pin-point the fault. ★



Trip Computer from Smiths Industries

PE RANGER

IMPORTANT

The Home Office 27MHz CB Specification (MPT 1320) carries the following as part of the Foreword.

The Wireless Telegraphy Act 1949 provides that no radio equipment may be installed or used except under the authority of a licence granted by the Secretary of State. All Citizens Band Radio equipment, whether hand held, mobile or base station, must be covered by a licence; it is a condition of this that the apparatus fulfils, and is maintained to, certain minimum technical standards.

The manufacturer, assembler, or importer of citizens band equipment is responsible for ensuring that the apparatus conforms with the specification; and any additional requirements imposed by regulations under the Wireless Telegraphy Act 1949. Conformity with the required standards may be established by tests carried out by the manufacturer, assembler or importer, or by a reputable test establishment acting on his behalf, but in either case conformity with the specification will remain the responsibility of the manufacturer, assembler or importer.

At the time of going to press CB licences were not available to the general public but it is anticipated that availability will be announced shortly. However readers can be ready with the PE Ranger to use this new facility as soon as it becomes legal.

Copies of MPT 1320 (27MHz) and MPT 1321 (934 MHz) are available from Government Bookshops and booksellers for £1.90 each.

The PE Ranger 27FM will only meet the Home Office specification for UK CB if it is constructed using a complete kit of parts obtained from Modus Systems and assembled exactly in accordance with the instructions given in this article. We do not recommend this project to anyone who has not successfully completed the construction of other electronic equipment.

Readers who hold the appropriate radio amateurs licence may use the PE Ranger on the 10m band.

CITIZENS Band radio is shortly to become legal in the UK and the PE Ranger 27FM offers you the chance to take advantage of this new system and develop its potential to meet your personal needs. The Ranger provides an ideal starting point for the newcomer and experienced operator alike. The introduction of the new service is expected shortly after the publication of this article and you have the opportunity to be on the air as soon as licences are issued.


The Ranger is not just a rig which you will outgrow as your operating experience increases. It forms a part of an overall system which can expand with each new application you find for CB. The base and mobile adaptor will extend the range and facilities of the basic transceiver for use in the car, home and boat.

The first parts of the PE Ranger series describe the construction and basic principles of operation of a self-contained hand-portable transceiver for short-range personal communication. Future articles will cover the testing and alignment procedures, which will require a minimum of test equipment, and the construction of a base and mobile unit.

BUILDING A RANGER?

The first question asked by many would-be constructors will be, "Could I build a Ranger?". The basic requirements are: the ability to solder neatly, a few basic tools, the use of a d.c. voltmeter, and a complete set of components. With these requirements satisfied, the answer to the original question is, "Yes".

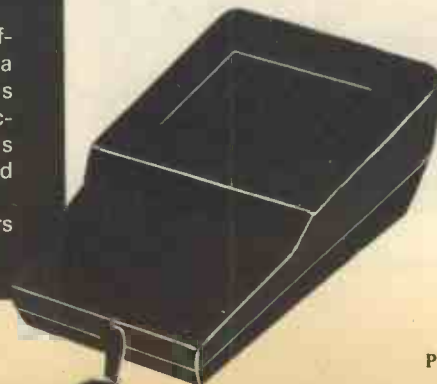The tools required are: a soldering iron (maximum 25W or temperature controlled) with a miniature bit, a supply of




27 FM CB

PART ONE

MICHAEL TOOLEY B.A.

DAVID WHITFIELD M.A. M.Sc.

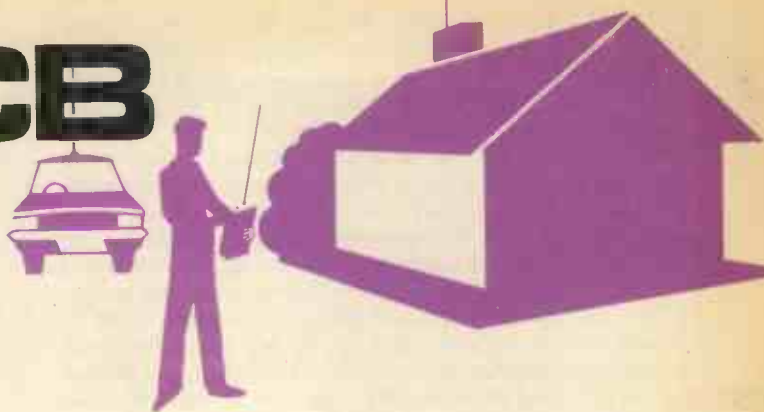

THE PE RANGER IS A HAND-HELD 0.5W CB TRANSCEIVER WHICH HAS BEEN DESIGNED TO BE EASILY EXPANDED USING A BASE/MOBILE ADAPTOR INTO A 4W BASE STATION SUITABLE FOR USE IN THE HOME, CAR AND BOAT.

SPECIFICATIONS

GENERAL

Modulation:	FM
Frequency range:	27.6 to 28.0MHz (CB version) 28.0 to 29.5MHz (Amateur version)
Number of channels:	Six
Channel spacing:	10kHz
Operating temperature range:	-5°C to +45°C
Power supply:	Internal 12V rechargeable battery 250mAh External 12V d.c. (nominal) negative ground External 240V a.c. (nominal) 50Hz
Battery drain:	Receive standby 46mA (typical) Receive average audio level 60mA (typical) Transmit 250mA (typical)
Battery charger:	Internal constant current charger operates when external supplies are connected and the transceiver is not in use. Full charge in 10 to 14 hours
Controls and external connections:	On/off switch combined with volume control Squelch on/off Channel selector switch Transmit and battery condition indicator l.e.d Microphone socket (5-pin d.i.n.) Mains input (2-pin) Aerial socket (u.h.f.) External d.c. input Auxiliary socket (6-pin d.i.n.)
Dimensions:	200mm x 120mm x 40mm
Weight:	1.2kg
Optional extras:	Base and mobile station adaptor Helical antenna 10dB fixed attenuator

TRANSMITTER

Power output:	0.5W (increased to 4W with the base/mobile adaptor)
Output impedance:	50Ω
Spurious output:	Less than 50nW above 80MHz Less than 250nW at all other frequencies
Frequency stability:	Better than 25 parts per million over the temperature range -5°C to +45°C and supply voltage range 9 to 14.5V
Audio response:	240 to 3.4kHz at -1dB referred to 1kHz 50Hz to 5kHz at -6dB referred to 1kHz Response falling at 12dB/octave above cut off
Deviation:	±2.5kHz maximum
Audio input impedance:	10kΩ
Microphone sensitivity:	Less than 10mV for rated system deviation
Speech processing:	Less than 3dB change in output for 20dB change in input level
Crystals:	9MHz fundamental HC18/U

RECEIVER

Sensitivity:	1μV for 10dB quieting or better
Input impedance:	50Ω
Selectivity:	Better than 20dB at ±10kHz
Audio output:	0.5W maximum
Audio response:	100Hz to 5kHz at -3dB referred to 1kHz
Frequency stability:	Better than 25 parts per million over the temperature range -5°C to +45°C and supply voltage range 9 to 14.5V
Intermediate frequency:	455kHz
Crystals:	27MHz third-overtone series resonant HC18/U

multicores solder, a pair of long nosed pliers, a pair of good quality side cutters, wire strippers (optional), a sharp knife or scalpel, a small screwdriver, a magnifying glass (optional), and a trimming tool (which may be made by filing down a plastic knitting needle to the correct dimensions). With the tools above and a set of components, it should be possible to follow the instructions given and successfully complete the PE Ranger 27FM without any previous experience of r.f. constructional projects. However, we suggest you do not build the PE Ranger if you have not successfully completed other electronic projects. It cannot be stressed too greatly that the recommended printed circuit board layout must be followed exactly if predictable results are to be obtained. Depending on the experience of the constructor, the Ranger may be built in 2 to 4 evenings, and the testing and alignment completed in a further 1 to 2 evenings, depending on the time spent and the facilities/test equipment available. In

will meet the Home Office performance requirements. Indeed, it is usually the case that there will be at least as many different designs produced as there are different designers working on a particular problem!

The main design aim was to produce a low cost, hand-portable FM transceiver suitable for personal communication. Operation from internal re-chargeable nickel-cadmium batteries, while involving a higher initial outlay than for dry batteries, was considered an essential feature for portable use. The life cycle cost of a unit powered exclusively from dry batteries will otherwise rapidly exceed the total cost of the equipment itself! To this end, the Ranger has been designed with re-chargeable batteries, a mains power supply and automatic battery charging circuits, all included inside the case. Operation from an external d.c. source such as a 12 volt car battery is also possible, and the NiCads may even be re-charged in this way.

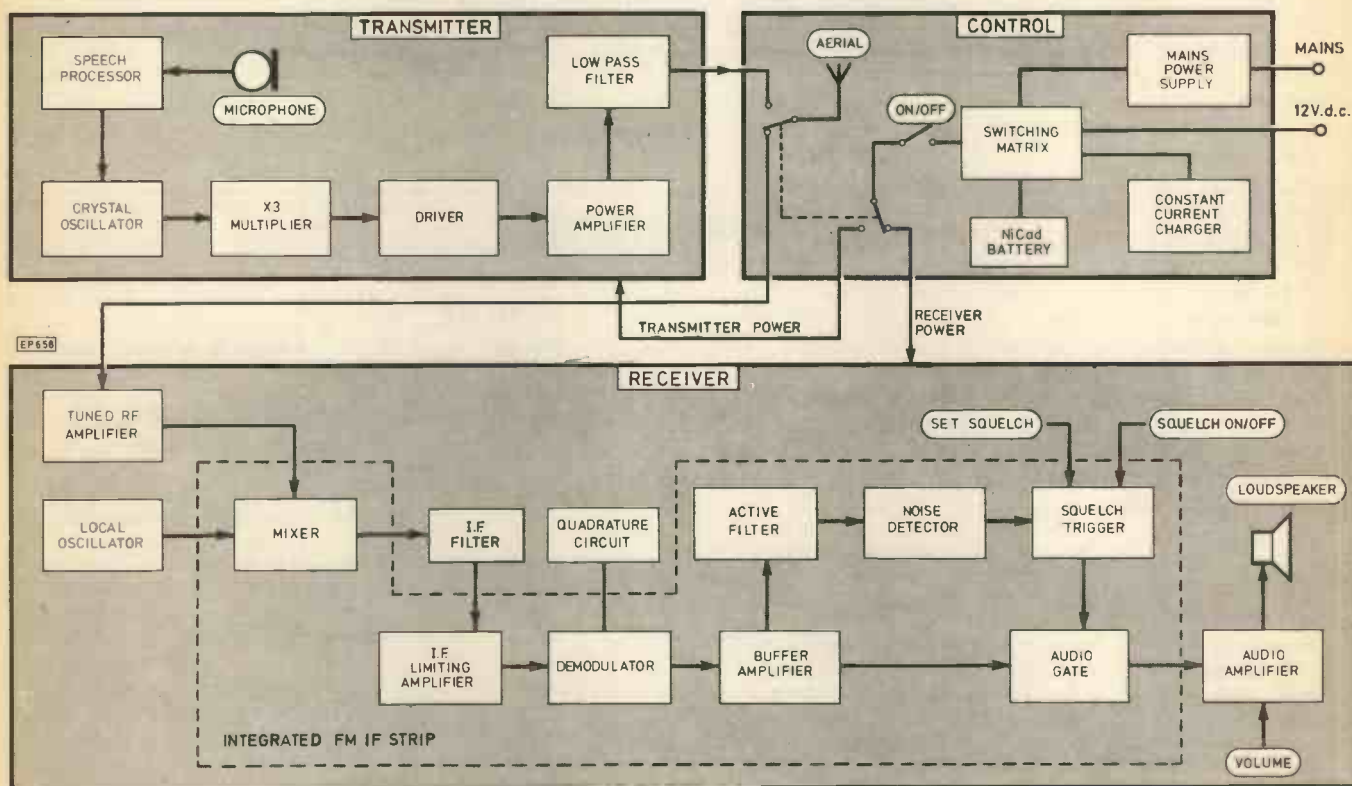


Fig. 1.1. Block diagram of the PE Ranger

the event of problems being encountered, a detailed fault finding guide is given in the latter part of the constructional notes. When care has been taken to check the identification and orientation of all components before soldering, and when the finished p.c.b. has been carefully inspected after completion, few problems should be experienced; the majority of problems arise from wrongly fitted components and poor soldering (solder splashes and dry joints in particular).

DESIGN PHILOSOPHY

The design of the PE Ranger 27FM inevitably represents an engineering compromise between the various design and performance parameters. One over-riding design constraint is, of course, the Home Office Performance Specification for "Angle modulated 27MHz radio equipment for use in the Citizens Band Radio Service". Within the limits of this specification, however, there is plenty of scope for many different practical implementations of an FM transceiver which

The transceiver itself makes use of integrated circuits in the design wherever possible. This allows a high level of performance to be achieved at low cost in the smallest possible space, while keeping to standard constructional techniques. Wherever possible, preset adjustments are kept to a minimum, with test points provided for simplifying the alignment procedure, and readily available components are used. Careful attention to the design of the p.c.b. ground plane and the component layout allows all of the components except the sockets and controls to be mounted on one single-sided p.c.b. The completed design is therefore compact, repeatable, cost-effective and straightforward to align. The robust case, flexible helical antenna, integral batteries and loudspeaker, detachable microphone, and rugged transmitter design all contribute to making the PE Ranger 27FM a self-contained transceiver which is suitable for a wide range of applications.

SYSTEM DESCRIPTION

The PE Ranger 27FM comprises four functional modules; transmitter, speech processor, receiver, and power supply. Fig. 1.1 shows how these modules are arranged in the basic transceiver.

In the transmitter, a low frequency (9MHz) fundamental crystal oscillator is used to define the output frequency. The speech processor amplifies the microphone signal, provides active limiting and low pass filtering, and then adjusts the level to set the maximum transmitter deviation. The output of the speech processor is used to frequency modulate the fundamental oscillator by means of a varicap diode. The modulated 9MHz signal then drives a frequency multiplier stage to produce an output on 27MHz. This 27MHz signal then undergoes two stages of RF amplification to provide an output of around 500mW (r.m.s.) into 50Ω. A multi-stage low pass filter is included in the path between the p.a. stage and the aerial to provide a high rate of attenuation of unwanted spurious. The overall design of the transmitter features bandpass coupling between stages, and this assists in achieving a low harmonic content in the output. The alignment procedure is simple, with test points provided for each stage, and only a simple d.c. voltmeter is required to complete the alignment of the transmitter.

The receiver features a conventional superhet arrangement with an intermediate frequency (i.f.) of 455kHz. The signal frequency is applied via the RF amplifier stage to one of the mixer inputs. The local oscillator drive for the second input is derived from an overtone oscillator running at 455kHz below the signal frequency. The 455kHz i.f. output from the mixer is filtered to remove unwanted mixing products, amplified in a five-stage limiter, and then demodulated. The combined i.f. amplifier and demodulator stage also provides the squelch facilities. Final audio amplification of the recovered signal is provided by an i.c. audio power amplifier. The use of a high gain amplifier, with its associated i.f. filter, ensures that alignment of the receiver is a very straightforward task, with a minimum of preset adjustments.

SPECIFICATIONS

In designing a piece of equipment for Citizens Band use consideration has to be given to meeting the specifications laid down by the Home Office. These are primarily concerned with the following aspects of equipment performance:

- (a) Maximum power output and effective radiated power.
- (b) Accuracy and stability of the transmitted frequency.
- (c) Frequency deviation and bandwidth of the transmitted signal.
- (d) Spurious radiation from the transmitter and receiver.

In each performance area limiting values are specified and these should not be exceeded under both normal and extreme conditions. To this end the Home Office require that tests be made either on a sample of the equipment type or, for simplicity's sake, on one item only. In this latter case equipment manufacturers, importers or assemblers must, from time to time, carry out subsequent tests to ensure that the specifications are still being met. In the case of the PE Ranger it is therefore necessary to establish that not only the performance of the prototype conforms to the given specification but also that sample units be tested, after assembly, to check that they also comply with the Home Office requirements. For this reason constructors are warned that the specifications quoted in this article are only likely to

be valid for transceivers constructed:


- (a) Using the components, p.c.b. and enclosure specified
- (b) Closely following the constructional details and alignment instructions given.

Any major departure from either the recommended components or alignment procedure may result in a finished transceiver which not only fails to perform to the quoted specification but fails to comply with the Home Office requirements. It should also be noted that, on any particular piece of equipment, performance specifications may be marginally different from those quoted due both to minor variations in individual components and to alignment tolerances.

CIRCUIT DESCRIPTION

The complete circuit diagram for the PE Ranger 27FM is shown in Fig. 1.2. To assist in locating a particular component, identification symbols are allocated distinctly to the transmitter, receiver and control sections, respectively, of the Ranger. Components in the transmitter and speech processor are numbered from 1, e.g. R1, C1, IC1, etc. Receiver components are numbered from 100, e.g. R100, C100, IC100, etc. The control section numbers components from 200, e.g. R200, C200, etc.

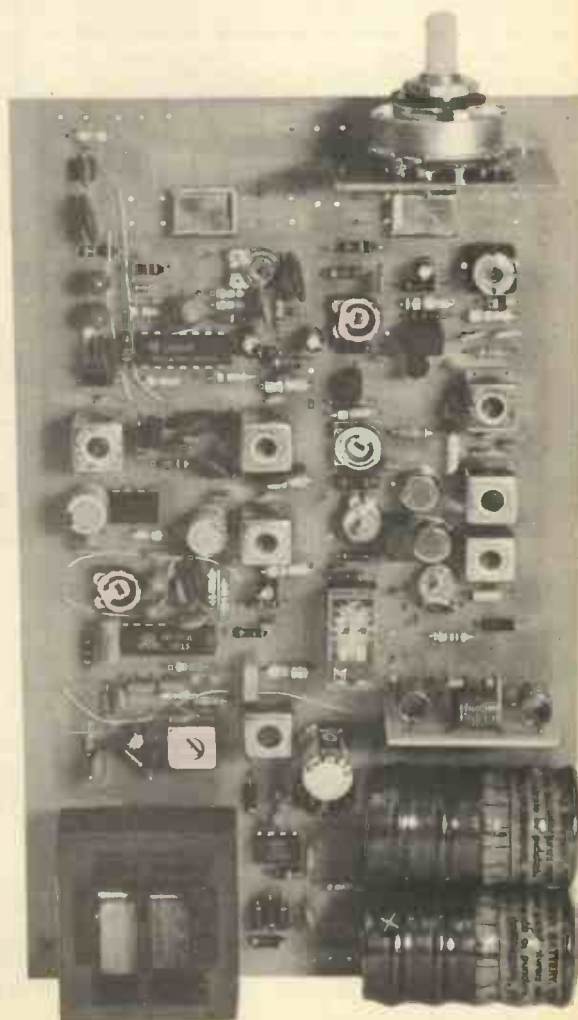The selection of transmit or receive is by means of the



Prototype p.c.b. design of the PE Ranger

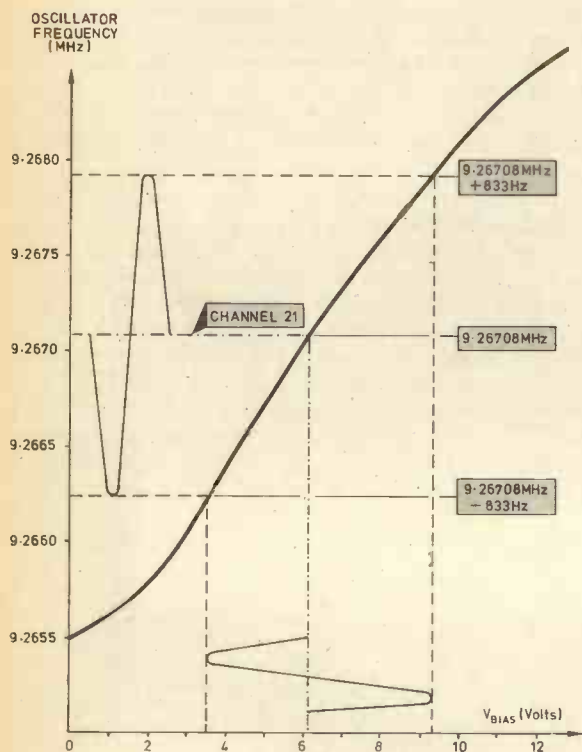


Fig. 1.3. Deviation characteristic for the frequency modulator

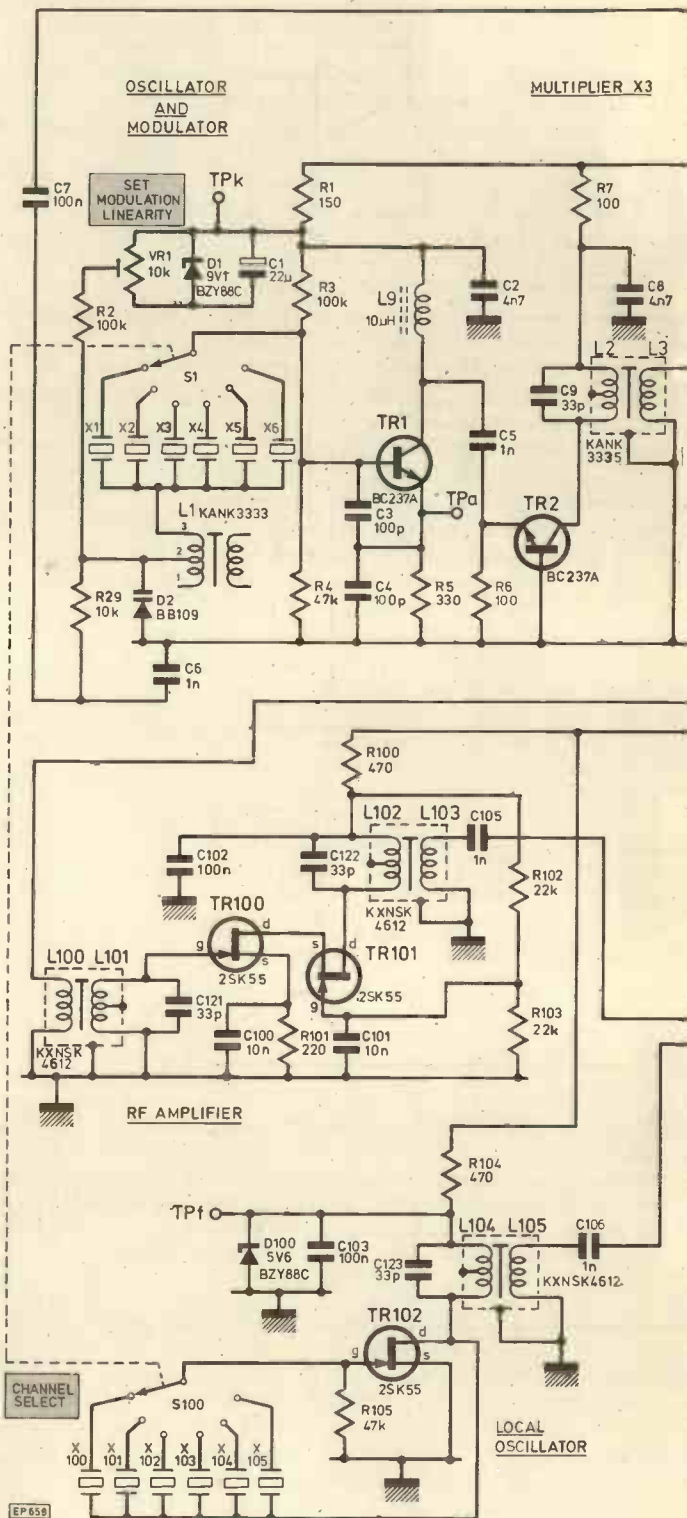
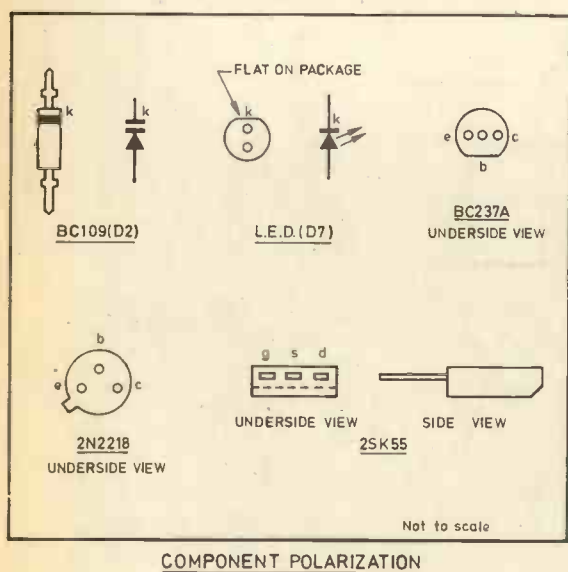


Fig. 1.2. Complete circuit diagram of the PE Ranger

COMPONENTS . . .

TRANSMITTER

Resistors

R1, R15, R28	150 (3 off)
R2, R3, R21, R24, R25, R26	100k (6 off)
R4, R19	47k (2 off)
R5	330
R6, R7	100 (2 off)
R8	2k2
R9	33k
R10	27
R11	47
R12, R13	10 (2 off)
R14, R22, R23	3k3 (3 off)
R16, R17, R20, R27, R29	10k (5 off)
R18	82k

All resistors $\frac{1}{4}$ W 5% carbon

Potentiometers

VR1	10k hor. preset
VR2	470 hor. preset
VR3	1M hor. preset

Capacitors

C1, C19	22 μ 10V elect. (2 off)
C2, C8, C11, C12, C14, C16, C17	4n7 ceramic (7 off)
C3, C4	100p ceramic plate (2 off)
C5, C6, C10, C13, C26	1n ceramic (5 off)
C7, C20, C21	100n ceramic (3 off)
C9	33p ceramic plate
C15	10 μ 16V elect
C18	22 μ 16V elect
C22, C24	22n ceramic (2 off)
C23	22 μ 16V elect
C25	2 μ 2 16V elect
VC1, VC2	3-45p trimmer (2 off)

All electrolytic capacitors are vertical p.c.b. mounting types

Semiconductors

TR1, TR2	BC237A (2 off)
TR3, TR4	2N2218 (2 off)
D1, D6	BZY88 C9V1 (2 off)
D2	BB109
D3	OA47
D4, D5	1N4148 (2 off)
D7	Red l.e.d.
IC1	LM 324N

Miscellaneous

L1	KANK 3333
L2/L3	KANK 3335
L4/L5, L7/L8	KXNSK 4612 (2 off)
L6, L9	10 μ H choke (2 off)
S1	2p 6w rotary p.c.b. switch
X1-X6	9MHz fundamental HC18/U crystal (6 off)
LPF	Low pass filter module
FB1	Ferrite anti-parasitic bead

RECEIVER

Resistors

R100, R104, R110	470 (3 off)
R101	220
R102, R103, R118	22k (3 off)

R105, R112, R113, R120, R121	47k (5 off)
R106, R109, R119	1k (3 off)
R107, R108, R114, R115	10k (4 off)
R111	2k2
R116	220k
R117	4k7
R122	4 Ω 7

All resistors $\frac{1}{4}$ W 5% carbon

Potentiometers

VR100	10k hor. preset
VR101	4k7 potentiometer with a s.p.s.t. switch

Capacitors

C100, C101, C116	10n ceramic (3 off)
C102, C103, C108, C111, C112, C114, C124	100n ceramic (7 off)
C104	22 μ 10V elect
C105, C106, C109, C110	1n ceramic (4 off)
C107	2 μ 2 16V elect
C113	10p ceramic
C115, C117, C118	10 μ 16V elect (3 off)
C119, C120	100 μ 16V elect (2 off)
C121, C122, C123	33p ceramic plate (3 off)

Semiconductors

D100	BZY 88 C5V6
D101	BZY 88 C6V2
D102	OA47
TR100, TR101, TR102	2SK55 (3 off)
IC100	MP 5071
IC101	LM 380N-8

Miscellaneous

L100/L101, L102/L103, L104/L105	KXNSK 4612 (3 off)
L106/L107	YHCS 11100 AC2 (2 off)
L108	YRCS 11098 AC2
FL100	CFM 2455D
S100	Combined with S1
S101	Toggle switch s.p.s.t
X100-X105	27MHz 3rd overtone HC18/U crystals (6 off)
Loudspeaker	50-75mm diameter 16 Ω

CONTROL

Resistors

R200	10k
R201	100k
R202	330

All resistors $\frac{1}{4}$ W 5% carbon

Capacitors

C200	470 μ 25V elect
C201	100n ceramic
C202	1n ceramic
C203	2200 μ 16V elect
C204	2 μ 2 25V elect
C205	1 μ 25V elect

Semiconductors

D200	W005
D201, D202, D203, D204, D205	1N4001 (5 off)
D206, D207	1N4148 (2 off)
IC200	NE555

Miscellaneous

RL200	Relay type 221 DO12 p.c.b. mounting 12V 2p c/o
S200	S.p.s.t. switch (see VR101)
SK200	Round SO239 socket
SK201	Reversible chassis mains plug
SK202 } SK203 }	5-way d.i.n. socket
SK204	5-way 180° d.i.n. socket
B200, B201	6.25V 250 mA NiCad pack
T200	0-12V 3VA p.c.b. transformer

General

- Case
- P.c.b.
- Knobs (2 off)
- Microphone with PTT switch
- Helical whip aerial
- Mains lead

Constructors' Note

The PE Ranger 27FM will only meet the Home Office specification for UK CB if it is built from a complete kit of parts from Modus Systems—exactly in accordance with the instructions given in this series of articles. No responsibility will be accepted by Modus Systems for sets which do not meet the specification due to incorrect assembly or alignment. The following prices have been specially arranged for PE readers.

The PE Ranger 27FM kit including injection moulded case, mains and car input, rechargeable batteries, microphone, helical $\frac{3}{8}$ wave aerial and crystals for two channels, £49.95 plus £1.40 p&p, plus VAT (£59.05 inclusive) or £97.00 for a matched pair of transceiver kits with crystals for two channels plus £2.80 p&p, plus VAT (£114.77 inclusive).

Extra sets of crystals are £2.25 for each channel plus 50p p&p (for any quantity), plus VAT.

Extra plastic covered helical $\frac{3}{8}$ wave aerials (overall length 50mm) for mobile or base station use, £3.95 each, plus 80p p&p, plus VAT.

Modus Systems Ltd., Dept AP, PO Box 30, Letchworth, Herts. SG6 3DQ (☎ 046 26 74468/76392).

press-to-talk (PTT) switch on the microphone. When the PTT switch is not depressed, RL200 is in the default position, and the receiver is selected. Depression of the PTT switch energises the coil of relay RL200, causing the aerial to be re-connected to the transmitter output, and d.c. power to be re-directed from the receiver to the transmitter and speech processor stages.

The overall block diagram for the PE Ranger 27FM shown in Fig. 1.1, will be used as the basis for the description of the circuit operation in the sections which follow.

TRANSMITTER

The transmitter output frequency is defined by a 9MHz crystal oscillator, the output of which subsequently undergoes frequency multiplication to produce a 27MHz signal on the channel frequency. Modulation is applied directly to the crystal oscillator to produce frequency modulation of the carrier.

The 9MHz oscillator stage uses a bipolar transistor, TR1, configured as a Colpitts oscillator, whose frequency is defined by the crystal selected by S1. A varicap diode, D2, is used to frequency modulate the oscillator. A varicap is a diode whose capacitance when reverse-biased varies inversely with the bias voltage, i.e. the capacitance decreases as the bias voltage is increased. Used in series with the crystal, the varicap diode increases the oscillator frequency as the bias voltage rises. This characteristic is exploited to allow the audio signal from the speech processor to modulate the carrier frequency. The deviation characteristic for the oscillator and modulator working on channel 21 is shown in Fig. 1.3. It can be seen that the overall transfer characteristic of the modulator is not quite linear, but that the deviation available is considerably more than is required. A limited operating range may therefore be chosen over which the response is linear for the deviation required (maximum ± 2.5 kHz). The maximum deviation allowed by the Home Office specification corresponds to a swing of ± 833 Hz on the 9MHz frequency; Fig. 1.3 indicates that the varicap bias could be set to approximately +6 to 7 volts for zero modulation input in order to give substantially linear performance. It also becomes clear from this graph that the bias voltage for

the varicap must be stabilised against supply voltage fluctuations if the carrier frequency is to be stable. VR1 provides the means of adjustment for the varicap bias voltage, and R1/D1/C1 stabilise the bias to the diode.

One result of inserting a varicap diode in series with the crystal in the oscillator is to increase the effective series capacitance. This has the effect of increasing the frequency of oscillation, and L1 is therefore included to compensate for this change by reducing the frequency. L1 also provides a fine adjustment for the zero-deviation oscillator frequency.

The oscillator output is taken from the collector of TR1 to minimise the loading effects, and the signal is used to drive the frequency multiplier stage. TR2 operates as a frequency tripler in common base configuration. This arrangement provides a high power gain and high output impedance, which is required to match to the output tuned circuit, L2/L3. The tuned circuit has a high Q factor to ensure that only the third harmonic (at 27MHz) is coupled to the driver stage.

TR3 is a tuned amplifier whose gain may be adjusted via VR2 to vary the drive level to the power amplifier. VR2 operates by varying the emitter current flowing in TR3. The tuned collector load for TR3, L4/L5, is arranged as an impedance step-up to simplify the matching arrangements; this type of arrangement is only appropriate for low power applications.

The power amplifier again uses the common emitter configuration, and TR4 provides around 10-13dB of gain. The output is coupled in a similar fashion to the driver stage, and is passed to the low-pass filter network, and then to the aerial. The output stage is matched to a 50 ohm impedance.

In the transmitter there is extensive decoupling of the supply rail for all of the stages. This decoupling, in conjunction with the short connections to the earth plane, is essential to ensure stability of the transmitter and to suppress the generation of unwanted spurious. On no account should the decoupling be omitted and good quality ceramic capacitors should be used throughout; the aim is to produce a supply rail which has negligible signal impedance. Test points are provided all along the transmitter chain to assist in the tuning up procedure.

NEXT MONTH: Circuit description and construction



Spectrographic studies of Saturn, Jupiter, asteroids and comets in the solar system have already been made. The more distant objects studies have been carried out on many stars, from those that are very young and those that are highly evolved. Extensive stellar winds have been detected in the hotter and more energetic stars. As a result some theories have had to be rewritten. Another area of surprise was the success in studying corona and the chromospheres of cool stars. It was not thought that these would be accessible to ultraviolet detection.

In the interstellar medium some exciting discoveries have been made. For example, the detection of a hot halo enveloping the galaxy itself. It extends out over a distance of 10,000 parsecs. The temperature is of the order of 10,000°K. It is possible to suggest also that this would apply to the nearby neighbours, the Greater and Lesser Magellanic Clouds. It is possible that the high redshift quasar which show multiple absorption lines could be partly caused by the halos of intervening galaxies. One of the most exciting of the observations carried out recently was on the 'twin' quasar which is believed to be a double image of a very distant quasar formed by a massive intervening galaxy which is acting as a gravitational lens. The ultra violet of the spectra are consistent with this interpretation.

The IUE was launched on 26th January 1978 from Cape Canaveral, Florida, by a NASA DELTA 2914 rocket. It is placed in a geosynchronous orbit over the Atlantic. It has a perigee of 28,000kms and an apogee of 46,000kms. Its design life was for three years but it is clear that it will last longer than this. It has been decided that observations will continue so long as useful data is being returned or the satellite remains operational.

GIOTTO AND HALLEY'S COMET

Giotto, which will be the first European Space Agency vehicle to go deep into space beyond the Earth will give the ESA an outstanding opportunity to come close to the comet if it arrives on time. Comets are believed to consist of some of the most primitive material in the Solar System. There will only be four hours of close study of the tail as the spacecraft passes through it. Thus high speed measurements must be made. The distance from Earth will then be greater than the distance of the moon. There are therefore technical problems for the radio link to the 60m Parkes radio telescope in Australia.

In addition to the observations of the cometary nucleus (if indeed there is a nucleus) the scientists concerned with the mission are particularly interested in investigating the cometary dust. The interaction of the tail with the solar wind is an important area for study because the conditions are not unrelated to the development of heating processes in fusion plasmas in the laboratory. Giotto will be equipped with a telescope with electronic colour imaging and with automatic micro-processor control to counteract the effects of the spinning spacecraft. The two dimensional tinted image of the comet will be accurately defined in contrast and transmitted to Earth in real time via the telemetry channel. The pictures will be used to control the vehicle on its course. The real time imaging is important

because the spacecraft may be damaged during hazardous parts of the encounter. Dr. Gary Hunt will be involved in the two dimensional imaging and also with the associated software. This will be principally for the analysis of the images so that the mass flows subliming from the nucleus to the coma and the tail can be quantified.

The spacecraft will speed through the cometary dust at 68km/sec. At that velocity a 0.1g of dust will explode through 8cm of aluminium. Since it would be impossible to provide for protection at such thickness in a space craft, an ingenious solution has been adopted to safeguard the vehicle from dust impacts. Two thin shields well separated will be sufficient. In the first contact the particle of dust will explode and will be vapourised to burst on the second shield 25cm away as a diverging ionised plasma which will be spread over a wide area. Tests have shown that this will work well and will enable a number count even with large masses. There is an enormous dynamic range to cover as the density of the tail increases as penetration proceeds into the denser layers. The range may well be from 10^{-17} g to 10^{-3} g.

Plasma analysers will be used to provide space-time resolution of the velocity distributions of the ions and electrons in the plasma and the impacting solar wind. A magnetometer will study the bow shock and the plasma flows and instabilities set up where the ionised atmosphere of the comet reacts with the solar wind. It is unfortunate that the United States fiscal plans have meant the maximum coverage of the mission will be decreased leaving the present mission to the European Space Agency, the Japanese with a lightly loaded probe and the USSR with the Venus orbiter on its return. The maximum effort will be from ESA and the USA will have to wait for the next return in 2062.

THE 30inch STEAVENSON TELESCOPE

Last October the Steavenson telescope was erected at the new observatory at an elevation of 3,000 feet in the Sierra Nevada, in Spain. The French 22inch was already installed. The Steavenson was moved from the Royal Greenwich Observatory where it had been refurbished. It was decided to ship it as nearly assembled as possible to avoid double testing and re-assembly. To this end only the optics and electronics were separated. The team of French, Spanish and British astronomers and technicians worked enthusiastically together. It is hoped that the 30 inch will be able to give its full use in the new and better observational conditions.

SHUTTLE EXPERIENCE

In a personal conversation with the Shuttle Commander John Young, he told me that he had expected a 'kick in the back of the neck' at take off. This did not happen and in fact it was smooth and easy with full voice communication throughout. A point that showed his past experience as an Astronaut was indicated by the fact that his own heart beat was normal but his co-pilot Astronaut Crippen experienced twice the normal rate.


THE INTERNATIONAL ULTRAVIOLET EXPLORER

The IUE has now passed its third birthday and provided data of outstanding excellence. This orbiting astronomical observatory is a joint venture between the United Kingdom Science Research Council, the eleven member European Space Agency and the National Aeronautical and Space Administration of the United States. During its continuing life more than 600 scientists have made use of its facilities. Data is collected continuously at three main centres, one at the Goddard Spaceflight Tracking Centre, another at the NASA ground station at Maryland, and for about ten hours a day at the ESA tracking station at Villafranco del Castillo (VILSPA) near Madrid in Spain.

In the three years of operation the satellite has obtained about 20,000 ultraviolet spectra of astronomical objects. The images which are stored on magnetic tape are kept at the Science Research Council, World Data Centre at Ditton Park, Great Britain. This data is accessible to all astronomers. The data Centre is unique in the world in that it is the largest and most important store of astronomical spectra in the world.

The actual time allowed for the SRC share of the IUE time is a maximum of 160 eight hour shifts during any one year. This is very much oversubscribed by United Kingdom observatories. The reason for this situation is the flexibility of the instrumentation on board the IUE. The design is such that the press of a button provides instantly different modes of operation. For example an astronomer could be focused on a bright source at very high resolution and by pressing the appropriate instruction button, move to a fainter object at lower resolution. The cameras are of remarkably high sensitivity and allow studies to be made of objects which to the ultraviolet eye are very faint such as quasars and external galaxies.

SPECIAL EQUALISER OFFER

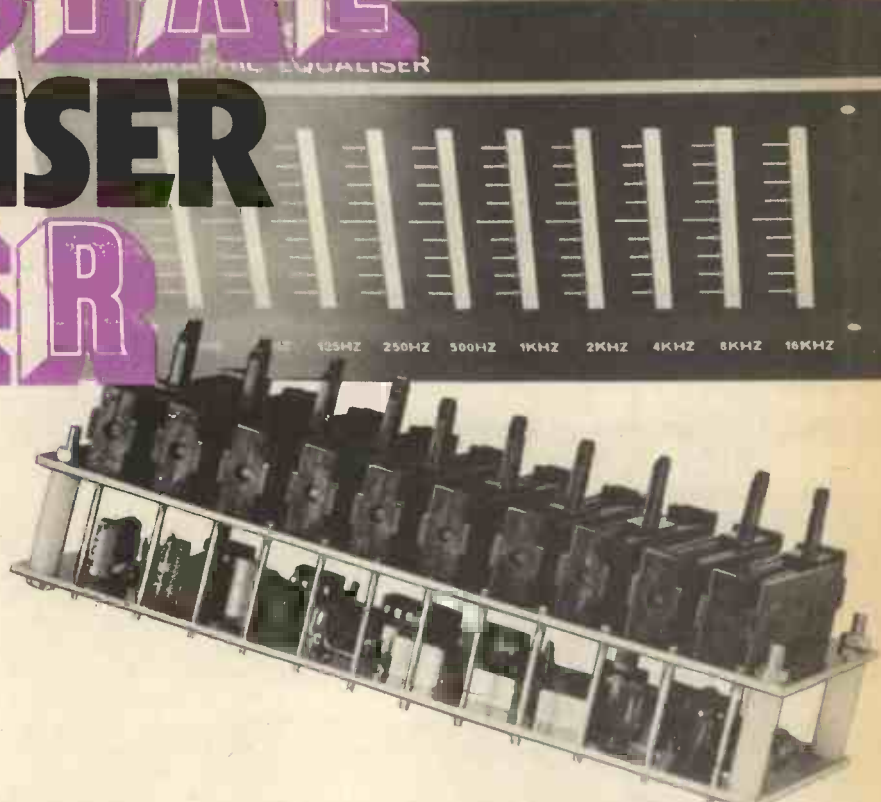

£21.50

INCLUDING V.A.T., POSTAGE
AND PACKING

A graphic equaliser to match our *Audio Analyser* project. This offer has been specially arranged by PE with BI-PAK to coincide with the publication of our *Audio Analyser*. The graphic equaliser on offer matches the analyser and provides ten channel audio correction. Knobs and a black aluminium front panel are also provided.

SPECIFICATION

Ten channel mono graphic equaliser (2 required for stereo)

Overall measurements: 155 x 66 x 55mm

Control Frequencies: 31, 62, 125, 250, 500, 1k, 2k, 4k, 8k and 16k (Hz)

Control Range: ± 12 dB cut or boost per channel

Dynamic Range: 110dB

Maximum Input: 3V r.m.s.

Maximum Output: +15dB

Frequency Response: 30Hz – 20kHz (± 1 dB)

T.H.D.: 0.005%

Power: 15V – 0 – 15V at 50mA

Offer closes Friday, October 16, 1981.

To: BI-PAK Semiconductors, PO Box 6, Ware, Herts. Tel. Ware 3182.

Please complete both parts of the coupon in BLOCK CAPITALS

Please send me graphic equaliser modules at £21.50 each inclusive. (Knobs and front panel provided.)

I enclose P.O./Cheque No Value

Make cheques payable to BI-PAK

Please charge my Access/Barclaycard account

No.

Signature

Name

Address

.

.

.

Please allow 28 days for delivery
OFFER CLOSES FRIDAY 16th OCTOBER 1981

Name

Address

.

.

.

From: BI-PAK, PO Box 6, Ware, Herts.

DRUM SYNTHESISER

P. BAILEY

THE synthesiser was originally developed using a keyboard, as the key contact was the easiest method of implementing the switching function required. However, as time passed by, other methods of controlling the basic synthesiser circuits were investigated, and the drum synth was born.

This works on the principle of a pick-up or sensor of some kind picking up the vibrations of a drum or pad and then feeding these signals to the circuitry which controls the synth. Note that this signal is only a trigger signal and that the synth produces the actual sound.

The unit to be described here can use one of a variety of methods to pick up the drum signal and trigger the envelope shaper etc. in the synth which is contained in a separate case. It runs off a regulated mains power supply which could be used to power external equipment if desired.



BLOCK DIAGRAM

Fig. 1 shows the basic arrangement of the circuits in the synth. The sweep generator circuit provides a rising or falling envelope (as selected) which is mixed with the triangle wave output from the modulation oscillator, and an external control voltage if desired, and fed to the voltage controlled oscillator (VCO) and voltage controlled filter (VCF) to control their frequencies. The output of the VCO (sinewave, squarewave or white noise as selected) is fed directly to the VCF and passes on to a voltage controlled amplifier (VCA) which is controlled by an envelope generator, triggered by the drum pick-up. This gives the sound its percussive envelope, essential in imitating drums etc. From here the sound is fed to the external amplifier or tape recorder as required via the output socket.

MODULATION OSCILLATOR

The circuit for this is shown in Fig. 2. It is a standard integrator/comparator oscillator circuit and its purpose is to generate a linear triangle wave, frequency variable over the low frequency range cycling the pitch of the VCO or cut-off frequency of the VCF as described earlier. IC1, R2, and C2 form an integrating network. C2 charges up linearly via R2 until it triggers IC2, which forms a comparator. On triggering, the output switches polarity and so charges C2 in the opposite direction at a rate dependent on the setting of VR1. When S1 is in the l.f. (low frequency) position, C1 is placed in parallel with C2, increasing its capacitance and thus decreasing the frequency. The range is about 0.5Hz to 200Hz on a.f. (audio frequency) and 1 cycle in 30 secs. to 10Hz on l.f. S3 routes the modulation voltage to the VCO or VCF in the proportion set by VR2, the oscillator being disconnected when not required by S2.

Fig. 1. Block diagram of the Drum Synthesiser

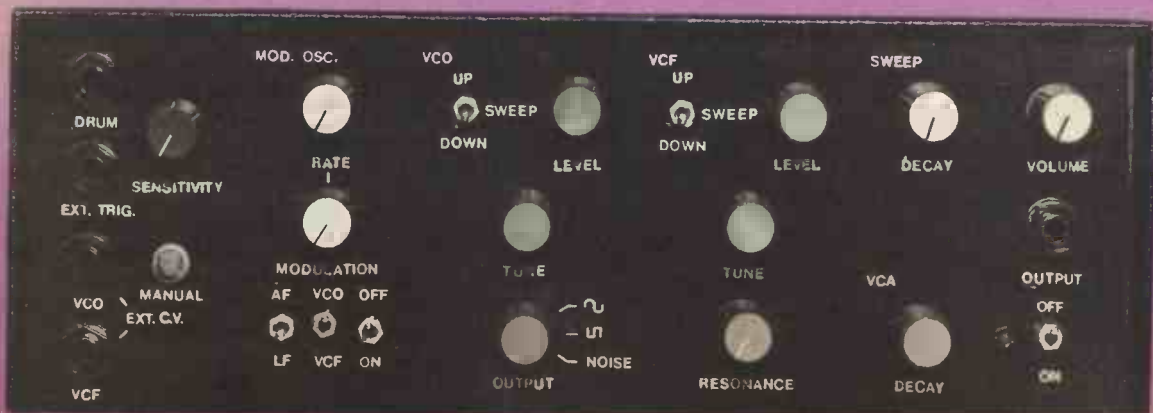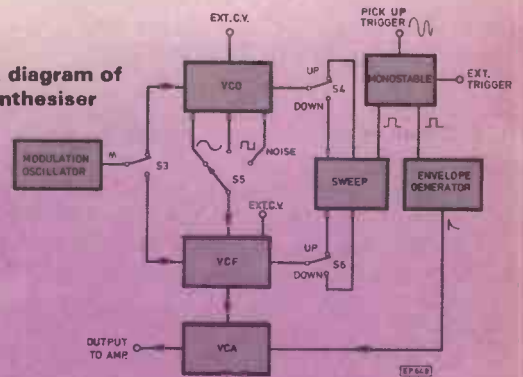

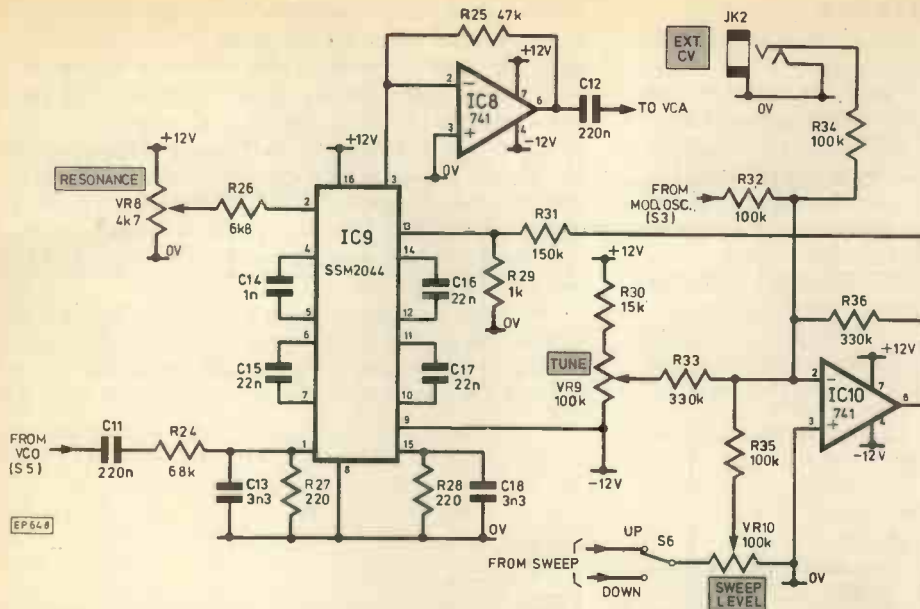


Fig. 4. Circuit of the voltage controlled low pass filter

by R13 and R12, and fed to pin 13 of IC5. Although some exponential oscillators using discrete components suffer from temperature drift problems in the exponential generating transistor, the on-chip exponential generator in the SSM2044 has circuitry which keeps this drift to a minimum and the prototype was found to be thermally stable, the oscillator settling down a few seconds after switch on.

The sine wave is fed to a simple comparator formed around IC4. This produces a square wave of adjustable amplitude by VR6.

The noise generator uses a reverse biased transistor emitter/base junction (TR1) to produce white noise which is amplified by TR2 and further amplified by IC7, the gain of which can be set by VR7.

Switch S5 selects the desired output waveform: sine, square, or noise. The presets VR6 and VR7 are adjusted so that all waveforms are at the same level.

VOLTAGE CONTROLLED FILTER

Once the basic signal has been generated, some way of controlling its timbre or tonal quality must be provided to give variation in the sound, since raw square wave or white noise becomes boring very quickly. This quality is affected by the voltage controlled filter which is a low-pass type. This filter has an exponentially voltage controllable cut-off frequency, variable over roughly the same range as the VCO, a cut-off slope of -24dB/octave , and resonance variable up to oscillation. It uses the same chip as the VCO, the SSM2044.

The circuit is shown in Fig. 4. The same combination of control voltages as in the VCO is used in the VCF, i.e. sweep, modulation oscillator, manual, and external. These are summed in the required proportions by IC10. This provides the control voltage for IC9. VR8 provides a variable voltage which is converted to a current by R26 and controls the filter's Q. The input signal is taken directly from the waveform selector switch of the VCO. IC8 converts the output current into a voltage and buffers it, this signal going directly to the next stage.

Since the VCF's cut-off frequency is exponentially related to control voltage, as in the VCO, the VCF and VCO will track each other with fair accuracy if controlled by the same voltages. Better tracking accuracy could have been achieved using close tolerance resistors, but in this application the added expense was felt to be unnecessary.

TRIGGER INPUT CIRCUIT

Each time a sound is required in any instrument, it must be initiated in some way, i.e. plucking a string, or pressing a key. In a drum synth the sounds are initiated by the signals from a transducer placed near to or on a drum, as mentioned earlier. These signals are of no use to the synth, since a sharp, high level pulse is required. For this reason an amplifier and pulse generator are used.

The circuit is shown in Fig. 5 and is very simple. The incoming low level signals are first attenuated to the desired amplitude by the sensitivity control VR11, and then amplified by a non-inverting, variable gain, op-amp circuit using IC11. The gain can be set by VR12 to any value between 1 and the op-amp's open loop gain (typically around 100,000). Thus by setting the gain high, when a low level signal is presented to the input, a high level, squared-up signal will appear at the output, due to the clipping action of the circuit.


To provide a stable voltage representing an on or off condition, a capacitor C20 is charged via D1 by this squared waveform so rectifying it. D1 allows only positive pulses to charge the capacitor and prevents it from instantly discharging when the op-amp output falls to zero. R38 controls the decay time of the capacitor and allows it to discharge quickly on removal of the input waveform. The voltage across this capacitor is used to trigger the monostable pulse generator formed around two gates from IC12. This triggers on the positive excursion of the voltage across C20, producing a positive pulse of around 0.01 s long. This is what is fed to the circuits requiring a trigger signal.

A manual switch is included so that sounds can be set up without the unit being connected to a microphone or pickup. Also included is an external trigger input which requires a positive d.c. pulse of about 8V or above (absolute maximum 12V). When a jack plug is inserted into the external trigger socket the drum input circuit is automatically disconnected. R39 ensures that the input to IC12a is never left floating, otherwise instability could occur, causing false triggering.

SWEEP MODULATION

This circuit, as explained earlier, provides a rising or falling voltage each time the synth is triggered. The speed of the change of voltage is controllable via the decay pot. The circuit is shown in Fig. 6. CMOS switches IC13a and IC13b, together with IC14, C22, R41, and VR13 form a simple envelope generator. IC12c is connected as an inverter so that when one of the CMOS switches is on, the other is off.

Fig. 5. Circuit of the trigger input

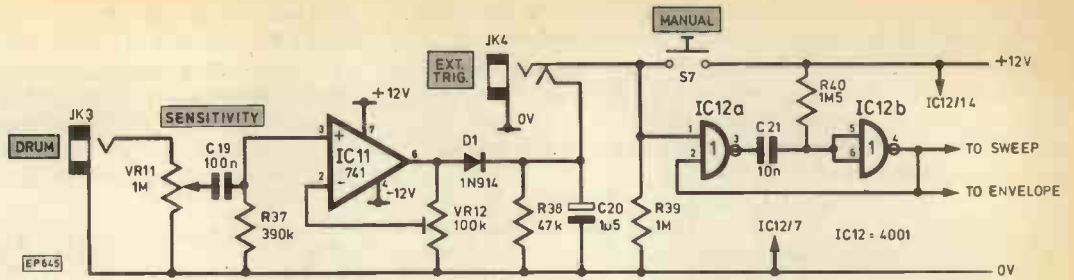

When the trigger input is low the input to switch IC13b is high and it is on, so holding C22 at ground potential via VR13. When the trigger input becomes high IC12c is switched, IC13a switches on, and C22 charges via R41 to approx. +10V. When the trigger pulse is removed IC13b switches back on again and C22 discharges to ground at a rate determined by the resistance of VR13. Thus a falling envelope as in Fig. 7a is produced. The voltage on C22 is buffered by IC14 to provide a usable output. This output is inverted by IC15 to provide the rising envelope as shown in Fig. 7b. The VCO and VCF each contain a switch which selects the direction of the sweep envelope, and a potentiometer to control the amount of sweep modulation. The decay control can vary the decay time from approximately 0.1s to 10s.

VOLTAGE CONTROLLED AMPLIFIER

So far, since the VCO and noise generator are on all the time, the output of the drum synth would be a continuous sound, hence some method of switching on the output and controlling its decay time is required. The circuit which does this is the voltage controlled amplifier together with the envelope generator. For simulating percussive sounds, which is what the drum synth does, an envelope with fast attack time and slower decay time is necessary. This means that the sound, when initiated by the trigger pulse, must increase in volume to its maximum almost instantly, and then die away to zero at a preselected rate. To produce this effect an envelope generator produces a positive-going envelope voltage with the above characteristics which is fed to the VCA, a device which gives an output signal proportional to its control voltage, so shaping the output signal.

The circuit can be seen in Fig. 8. The voltage envelope is generated in the same manner as in the sweep generator, C23 charging via R44 to give a fast attack, and discharging via VR14 giving variable decay. Since only a positive envelope is required no inverter is included.

The VCA is based on the CA3080 transconductance op-amp i.c. This functions similarly to an ordinary op-amp but its output is multiplied by a current injected into pin 5, called I_{abc} . Thus by feeding a signal into the inputs the gain and hence amplitude of the signal can be linearly controlled by varying I_{abc} . IC17 together with TR3 and R45 convert the envelope voltage into a current suitable for controlling IC18. When IC16's output is 0V then there is no output from the VCA since $I_{abc}=0$. VR15 converts the current output of IC18 into a voltage, and also sets the volume to the output socket via C24.

POWER SUPPLY

The synth is powered from a mains $\pm 12V$ stabilised power supply. This uses two integrated circuit regulators, the 78M12 and 79M12, to provide positive and negative voltage rails as can be seen from Fig. 9. Each rail can provide a maximum of 500mA before the regulator's current limit acts. Since the drum synth draws only around 40mA from each rail, external equipment could be driven from the PSU. For instance if two drum synths were built only one power supply could supply both via a socket on the back of the case for example. Note that if the maximum current is required to be drawn then the regulators will require heatsinks. D3 shows that the power is on.

CONSTRUCTION

Construction should begin with the preparation of the case. The prototype was housed in a rexine covered case size 13in x 8in x 4½in. The drilling dimensions are shown in Fig. 10. The diameters of the mounting holes for the switches and l.e.d. will depend on the particular components

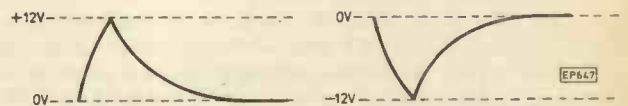


Fig. 7(a). Falling envelope

Fig. 7(b). Rising envelope

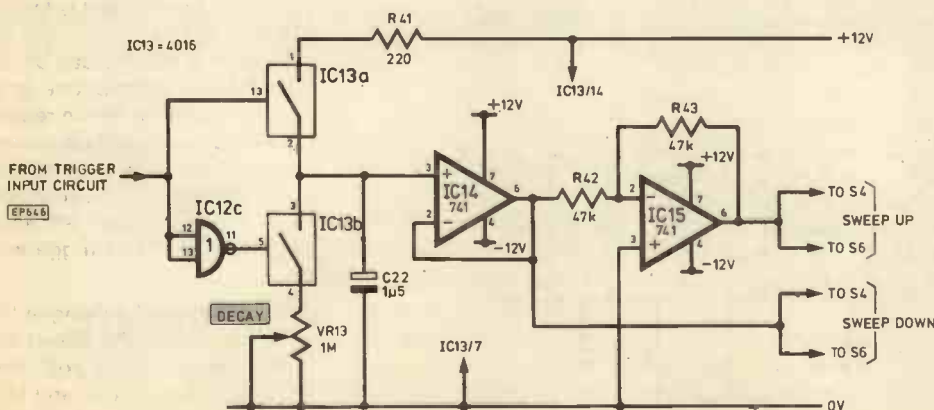


Fig. 6. Circuit of the sweep modulation generator

used by the constructor. Once all the case drilling has been completed, the front panel can be covered in Con-Tact or similar, or painted if desired. It can now be lettered with white rub-down lettering, and then sprayed with clear varnish to protect it. The transformer should be mounted to the back panel with 8BA bolts, and connected to the mains lead and mains switch as shown in Fig. 10.

damaged by leakage from a soldering iron tip. IC12 and IC13 should be left in their protective foam until all other circuit board construction is complete. Then they should be put into the sockets, keeping handling to a minimum.

Begin preparing the circuit board by drilling the mounting holes and making the breaks in the copper strips. Now the PSU can be constructed. When building the power supply,

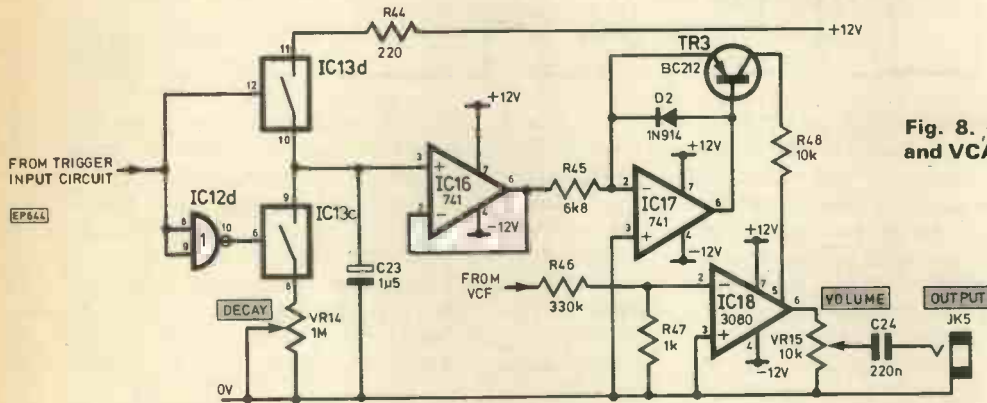


Fig. 8. Circuit of the envelope generator and VCA

All potentiometer spindles should be cut to length and the potentiometers, switches, sockets, and l.e.d. mounted to the panel. These should be wired up as shown, the panel mounted components being connected too. Uninsulated, single-core wire is used to link all the common connections at the back of the panel. Otherwise lightweight, stranded wire should be used for interconnection.

The use of coloured wire greatly helps in the identification of wires and their functions. A source of suitable wire is a metre of 25 or 36 core multicore cable. The wires to the circuit board need not be connected yet. Attention can now be turned to this circuit board.

Most of the components are contained on a 115 holes x 36 strips piece of Veroboard, excepting those soldered directly to the potentiometers and switches on the front panel so as to minimise the number of wires running to and from the circuit board. It is recommended that the power supply section be built and tested first. Once working this will provide power for testing the other sections. Circuit layout is shown in Fig. 11.

To make building, testing, and setting up easier, each circuit is laid out on the board so as to be completely isolated and independent from all the other circuits, apart from sharing power supply connections. This allows each one to be built and tested without having built any others onto the board. A convenient procedure is to build the circuit board up from left to right. It is recommended that i.c. sockets or Soldercon pins be used for all i.c.s particularly IC5 and IC9 to prevent them being overheated during soldering, and IC12 and IC13 since these are CMOS chips and could be

double check the polarity and positioning of all the components. Check carefully that the regulators have been inserted facing the right way round. The power supply constructed, the transformer should be connected (mains to the primary) and with a voltmeter across +12V and -12V the mains should be switched on. If there is no reading on the voltmeter then switch off immediately and check for any breaks missed out on the circuit board underside, and wiring errors. If a reading is obtained, then measure the voltage of the positive and negative rails with respect to ground. These should be approximately 12V. This being successful, the construction of the rest of the sections can begin.

The i.c. sockets should be soldered in place first since the presence of these will aid the positioning of the other components. Resistors and capacitors should be soldered in next, attention being paid to the polarity of the electrolytics and tantalums. The transistors and diodes should now be soldered, preferably using a heatshunt. Ensure that the diodes have been inserted the correct way around, the end with the red band is the end with the bar on the diagram (the cathode). Veropins are recommended to be used for all leads entering and leaving the board, as these allow wires to be connected and disconnected easily when testing etc.

TESTING

Preliminary testing of each section as it is built can be performed as follows.

Mod. Osc. Connect VR1 temporarily to the circuit board. Connect an amplifier, with its volume set very low, to pin K8

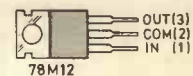
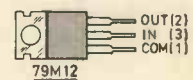
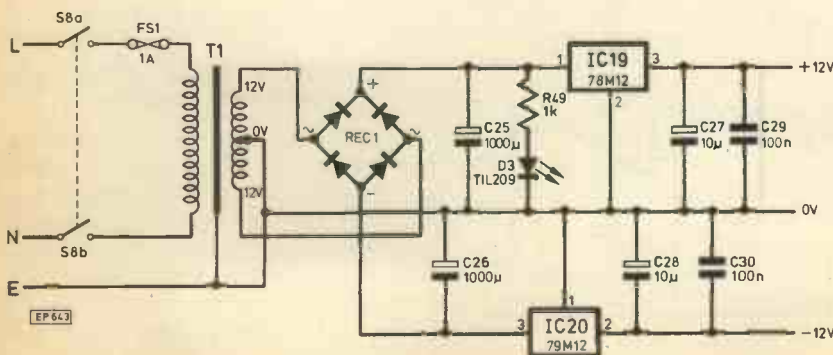


Fig. 9. Power supply unit

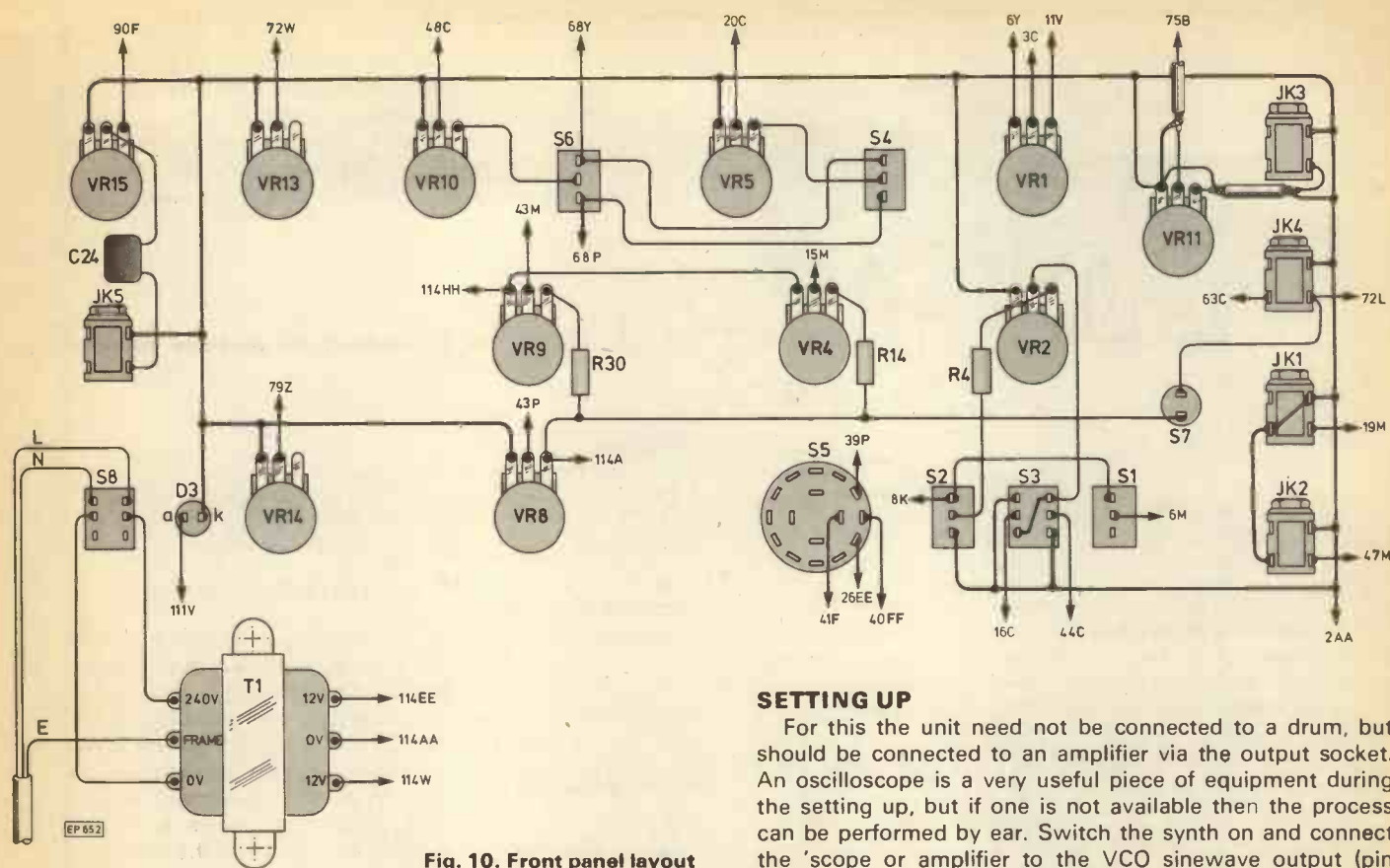


Fig. 10. Front panel layout

and check that a tone can be heard, VR1 altering the frequency. Short pins K8 and M6 together and the pitch should become a series of clicks.

VCO Adjust VR3 to max. (slider at +ve end). Connect an amplifier to pin EE26 and then pin FF40. Both should produce an audio tone.

Noise Generator Connect an amplifier to pin P39. The characteristic rushing sound of white noise should be heard.

VCF Connect pin P44 to the +12V rail and check that a tone can be heard at pin Y54.

Sweep Connect VR13 temporarily to the board and connect a voltmeter (25V d.c. range) with positive to pin Y68. Short pin L72 to +12V briefly and the voltage should rise on the voltmeter and then decay to zero at a rate adjustable by VR13. Also make sure that an inverted output is available at pin P68 (remember to reverse the voltmeter connections).

VCA Connect pin C82 to noise gen. pin P39 and solder VR14 and VR15 temporarily to the board. Connect an amplifier to pin F90 and short pin to +12V as before. The sound should be heard and then decay in volume to zero at a rate adjustable by VR14.

Trigger Input Adjust VR12 to nearly max. (slider near 0V). Connect a voltmeter to pin C63. The voltage should rise from zero in a positive direction when a finger is placed on pin B75 (the hum induced in a finger should be sufficient to trigger the circuit). The reading should return to zero when the finger is removed.

These tests having been successfully completed, then the circuit board can be mounted in the case using 1in 8BA bolts and ½in 8BA spacers. The wires to the front panel can now be connected too, as shown in Fig. 10. Note that screened lead should be used on all board/front panel connections on the drum input circuitry. This completes the construction of the drum synth although the circuits are still to be set up.

SETTING UP

For this the unit need not be connected to a drum, but should be connected to an amplifier via the output socket. An oscilloscope is a very useful piece of equipment during the setting up, but if one is not available then the process can be performed by ear. Switch the synth on and connect the 'scope or amplifier to the VCO sinewave output (pin EE26). Adjust VR3 for as pure a sinewave as possible. Make sure of the full range by observing the waveform whilst rotating VR4 between its extremes. If the waveform deteriorates or disappears then adjust VR3 until this is stopped. Note the sinewave amplitude, and now connect the 'scope or amp to the squarewave output (pin FF40). If this is impure then adjust VR3 once more slightly, rechecking the sine output. Adjust VR6 until the squarewave is at the same amplitude as the sinewave. Now check the noise output (pin P39) and adjust its level (via VR7) to that of the others. This done, if using a 'scope observe the output of the modulation oscillator (pin K8) which should be a triangle wave. All waveforms should be symmetrical about zero. The gain in the input section of the trigger circuitry should be set so that the wiper of VR12 is almost at the end connected to ground. If it is found that sensitivity is too high, or low, then this setting can be altered to correct this. Moving the wiper towards IC11 output reduces the gain. It now remains to check out each section of the synth, using the "Manual" front-panel push switch to trigger it.

USING IT

The unit will normally be triggered by a conventional drum, and several methods are possible. A contact microphone can be constructed using a small crystal microphone insert. A length of screened lead should be connected to this to allow it to be plugged into the synth. This insert can be taped onto the side of a drum so picking up the drum vibrations and triggering the unit. Low impedance transducers such as loudspeakers and earphones also will provide a trigger signal. A special drum can be constructed for use with the synth. This would include a pad for the drum stick to strike, and a miniature loudspeaker beneath this to collect the sound and provide a triggering signal. A cassette recorder microphone could be used, or virtually any other type of microphone. This would be mounted on a


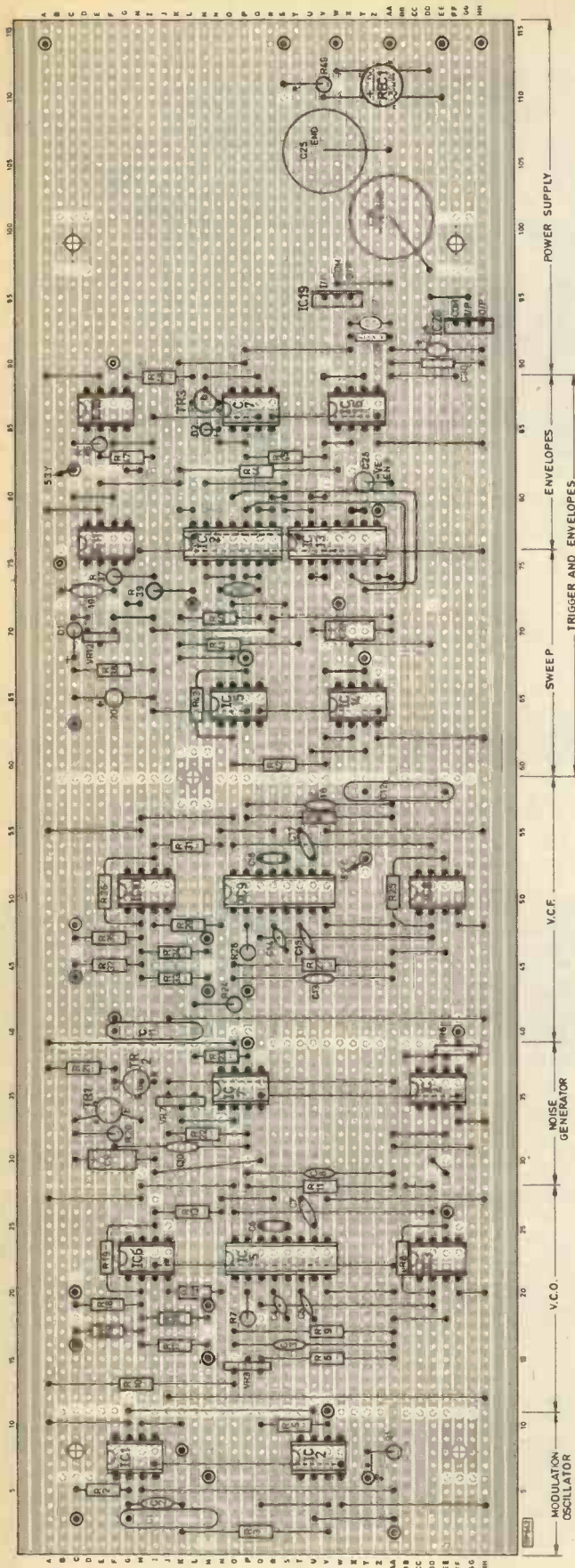


Fig. 11. Veroboard component layout

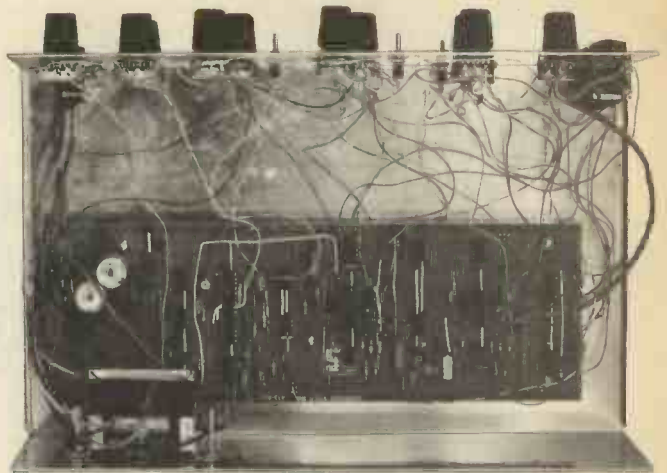

Internal layout

microphone stand and placed beneath a drum with the bottom skin removed. A Shure Unidyne B was found to trigger the synth reliably. The choice of triggering arrangement is really up to the constructor who can use a method best suited to the way he will be using the unit. It should also be borne in mind that when used with a microphone, a clap or even a shout can be used, so extending the versatility even further.

VCO/VCF CONTROL INPUTS

The external control voltage inputs for the VCO and the VCF are included so as to extend the usefulness of the synth. These may be used with any device which produces a control voltage (absolute maximum 12V) such as a foot pedal or another synthesiser. These sockets were primarily designed to allow the synthesiser to be connected to a sequencer, the ext. trig. input also being used, requiring a positive pulse. The control voltage law is around 3 volts/octave, but it should be noted that the VCO and VCF may not be accurately exponential over their full range since component tolerances, the lack of temperature compensation, and the use of 741 op-amps may cause inaccuracies. Nevertheless, they are fairly exponential over the central part of their range. The use of even a simple sequencer allows a wide range of rhythms to be generated.

With the VCA "Decay" control adjusted for a short, slight decay and the sine output of the VCO being used, an ordinary drum sound is produced, from a bass drum through to bongos and woodblocks as the VCO "Tune" control is adjusted. Increasing "Decay" and adding "Down Sweep" to the VCO produces the well-known "pew-pew" disco Syndrum sound. Using the square output of the VCO, synthesiser "waa-waa" sounds can be obtained by increasing "Sweep" on the VCF. Adding low frequency modulation to the VCF in large amounts produces a burbling noise. Using "Noise" and "Sweep" on the VCF, noises varying from sea and thunder to jet-plane whooshes can be achieved by varying the VCF "Tune" and "Resonance" controls. With a short, punchy VCA decay, and a suitably set VCF, snare drum sounds can be obtained using "Noise". Obviously these are just a few of the sounds which can be produced, and the limit is really the user's ingenuity. ★

NEW DISTRIBUTORS WANTED

Send 30p to cover P&P

PRB-1 Digital Logic Probe

Compatible with DTL, TTL, CMOS, MOS and Micro-processors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic re-setting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord). Eliminates need for heavy test equipment. A definite savings in time and money for Engineer and Technician.

PLS-1 LOGIC PULSER

The PLS-1 logic pulser will superimpose a dynamic pulse train (20 pps) or a single pulse onto the circuit node under test. There is no need to unsolder pins or cut printed-circuit traces even when these nodes are being clamped by digital outputs.

PLS-1 is a multi-mode, high current pulse generator packaged in a hand-held shirt pocket portable instrument. It can source or sink sufficient current to force saturated output transistors in digital circuits into the opposite logic state. Signal injection is by means of a pushbutton switch near the probe tip. When the button is depressed, a single high-going or low-going pulse of 2µ sec wide is delivered to the circuit node under test. Pulse polarity is automatic: high nodes are pulsed low and low nodes are pulsed high. Holding the button down delivers a series of pulses of 20 pps to the circuit under test.

ELECTROWARE*

DUTTON LANE EASTLEIGH SO5 4AA TEL(0703)610944/5

AVAILABLE FROM ALL LEADING ELECTRONIC DISTRIBUTORS

Cobbles Ltd., London. 01-699-2282

Microdigital Ltd., Liverpool. 051-227-2535

Electronica CG Ltd., Manchester. 061-788-0656

Spectron Electronics (Manchester) Ltd., Salford. 061-834-4583

Jee Distribution Ltd., Middlesex. 01-897-3429

Watford Electronics Ltd., Watford. 0923-37774

Technomatic Ltd., London. 01-452-1500

Transam, London. 01-402-8137

A. Marshall (London) Ltd., London. 01-624-0805

Interface Components Ltd., Amersham. 02403-22307

New Bear Computing Store Ltd., Newbury. 0635-30505

* A DIVISION OF OK MACHINE & TOOL (UK) LIMITED

Rapid Electronics

Hillcroft House
Station Road
Eynsford Kent

COMPONENTS KITS

1/2W Resistor Kit. Contains 10 of each value from 4.7Ω to 1M (total of 650 resistors). **480p each**
Ceramic Capacitor Kit. Contains 5 of each value from 22pF to 0.01µF (total 135 caps.). **370p each**
Polyester Capacitor Kit. Contains 5 of each value from 0.01µF to 1µF (total 85 caps.). **575p each**
Nut and Bolt Kit. Total 300 items. **140p each**

25 6BA 1/2 bolts	25 8BA 1/2 bolts
25 6BA 1/4 bolts	25 8BA 1/4 bolts
50 6BA nuts	50 8BA nuts
50 6BA washers	50 8BA washers

LINEAR

*741	15	*LM301A	25	LM3900	50	*SN76477	150
CA3080	70	*LM324	45	LM3909	70	TBA800	80
*CA3130	75	LM339	50	*LM3911	120	TBA810	95
CA3140	45	LM380	80	*LM3914	200	*TL081	30
*CM7555	80	LM381	120	*LM3915	200	TLO82	70
LF351	45	LM382	120	*NE555	17	XR2206	300
LF353	85	LM387	120	NE556	55	ZN414	100
LF356	90	LM1458	40	*RC4136	60	*ZN425E	350

CMOS

*4001	13	*4017	45	4028	80	*4066	35	4082	25
4002	25	4018	75	4040	85	4068	25	*4093	43
*4007	18	4020	85	4046	100	*4069	18	4510	85
*4011	14	4023	25	4047	100	4070	25	*4511	65
*4013	30	*4024	40	*4049	30	*4071	18	*4518	70
4015	80	*4025	18	*4050	30	*4072	18	4520	90
*4016	30	*4027	35	4060	105	*4081	18	*4528	75

SWITCHES

Submin. toggle SPST 55p; SPDT 60p; *DPDT 50p.
Miniature toggle SPST 80p; DPDT 90p.
Standard toggle *SPST 25p; DPDT 45p.
DPDT Slide switch *Min. 10p; Standard 16p.
Rotary switch. Adjustable stop. 55p each.
1 pole 12 way 3 pole 4 way
pole 6 way 4 pole 3 way
Miniature *Push to make 12p
 *Push to break 15p

58

RESISTORS

Carbon film 1/2W 5% 4.7Ω to 10M. Sold in packs of 10 per value. **10p per pack.**

Potentiometers
Preset miniature horizontal 100Ω to 1M. **7p**
Rotary 5K-1M Log or Lin ***26p**
Slide. 5K-500K Log or Lin. 60mm travel. **63p**
Mixer type control knobs to suit above pots. Available in red, black, green, grey, yellow and blue. For rotary pots. **16p**
Slide pots. **12p**

DIODES

1N4001 **4p**
*1N4002 **3p**
1N4006 **7p**
*1N4148 **2p**
400mW zeners 6p ea.

VERO

Size 0.1 matrix **22p**
2.5x1" **75p**
2.5x3.75" **75p**
2.5x5" **85p**
3.75x5" **95p**
VQ board **160p**
Veropins per 100
Single sided **50p**
Double sided **60p**
Spot face cutter **105p**

CONNECTORS

DIN	Plug	Socket	Jack	Plug	Socket
2 pin	9p	9p	2.25mm	10p	10p
3 pin	12p	10p	3.5mm	*7p	*9p
5 pin	13p	11p	Standard	*12p	*15p
Phono	10p	12p	Stereo	24p	25p

SUPER

All items marked * are our Summer Savers for '81 at specially reduced prices. Send 28p in stamps for our 28 page fully illustrated catalogue. FREE with orders over £5.

SAVERS

CAPACITORS

Polyester. Radial leads 250V. C280 type.
* 0.01 5p; 0.015 0.022 0.033 6p; 0.047 0.068 7p;
* 0.1 5p; 0.15 0.22 9p; * 0.47 10p; 1.0µF 23p.
Electrolytic. Radial leads.
0.47/63V 7p; 1/63V * 2.2/63V * 4.7/63V * 10/25V 5p;
22/25V 47/25V 8p; 100/25V 6p; 220/25V 14p; 470/25V 22p; 1000/25V 30p.
Tantalum bead
0.1/35V 0.22/35V 0.33/35V 0.47/35V 12p; * 1/35V 10p;
* 2.2/25V 12p; * 4.7/25V 15p; * 10/25V 15p.
Ceramic disc type. Sold in packs of 5 per value. 15p per pack. 22pF to 0.01µF.

TRANSISTORS

AC128	25	*BC182L	8	*BF244B	18	ZTX108	12
AC176	25	*BC184L	7	BF229	25	ZTX300	14
AD181	40	BC121L	10	BFY51	23	2N2369	17
AD162	40	*BC214L	8	*BFY52	18	2N2646	45
BC107	10	*BC478	20	MJ2955	10	2N3053	23
*BC108	8	BC547	10	TIP31A	45	2N3055	50
*BC108C	10	BC548	10	TIP32A	45	*2N3702	6
BC109	10	BC549	10	TIP41A	60	*2N3704	6
BC109C	12	BD131	35	TIP42A	60	2N3819	20
BC148	8	BD132	35	TIP2955	60	2N3904	10
BC178	18	BD139	35	TIP3055	55	*2N3906	6
BC179	18	BD140	35	*ZTX107	9	*2N5459	18

SOCKETS

Texas.		*78L05	25	*7905	50
*8 pin	7p	78L12	30	*7912	45
*14 pin	9p	78L15	30	7915	65
*16 pin	9p	*7805	45	LM723	40
*100 Soldercons	45p	*7812	45	*LM317T	99
TO5 or TO18 skt.	15p	7815	60	*LM323K	350

REGULATORS

*78L05	25	*7905	50
78L12	30	*7912	45
78L15	30	7915	65
*7805	45	LM723	40
*7812	45	*LM317T	99
7815	60	*LM323K	350

OPTO

*3mm red	7p	20 metre pack of connecting cable. 2m each
*3mm green	12p	10 colours
3mm yellow	14p	Lightweight screened
*5mm red	8p	Standard screened
*5mm green	12p	Stereo screened
5mm yellow	14p	4 core screened
*FNDS50	70p	Min. mains 3 core

CABLES

*3mm red	7p	20 metre pack of connecting cable. 2m each
*3mm green	12p	10 colours
3mm yellow	14p	Lightweight screened
*5mm red	8p	Standard screened
*5mm green	12p	Stereo screened
5mm yellow	14p	4 core screened
*FNDS50	70p	Min. mains 3 core

Please add 50p P&P on orders under £10. Please add VAT at 15% to total order value. Official orders welcome from schools, colleges etc.

The Rapid Guarantee

* Same day despatch * Competitive prices
* Top quality components * In-depth stock

Semiconductor UPDATE...

FEATURING MC13002 GL-105XX IR-2E01

R.W. Coles

ANALOGUE LSI

Large Scale Integration (LSI) is an everyday technology to be found in nearly every home in the country, living inside calculators, electronic games, door-chimes, personal computers and the like. The thing you may have overlooked about this new domestic revolution is that all of these LSI based gadgets are essentially *digital* in design and construction. In other words, they are either dedicated logic arrays made up of a custom arrangement of gates, or they are a form of dedicated micro-processor, made into a door-chime, for example, by a custom program inserted during the manufacturing process.

Any analogue functions that do crop up in these gadgets are either provided by external circuitry, perhaps using Small or Medium Scale Integration, or are implemented on the mainly digital LSI chip using a certain amount of "Electrickery" to bend digital gates to an analogue function. Needless to say, the performance of analogue circuitry produced using this latter method leaves a lot to be desired, although for interface to game paddles or other simple transducers, which do not require high precision or high frequency processing, the method can be made quite adequate.

The reason for all this is that making logic gates is kids' stuff in comparison with making, for example, a stable High Frequency amplifier with very low distortion, and anyway the High Frequency system would probably need bulky external reactive components such as i.f. transformers so in the past there hasn't been much commercial pressure to achieve the ultimate in miniaturisation. Technology marches inexorably on, and the thoroughbred microprocessor chips, now moving rapidly into the VLSI era (the V stands for Very!) are starting to look askance at their analogue "poor relations" and wondering whether they really relish the prospect of having to shake hands with tatty old analogue SSI chips which are not really in the same class of Silicon at all!

In addition to that rather whimsical interpretation of the situation, it can certainly be stated that there are now increasing commercial pressures to introduce radically new "miniature" analogue gadgets such as televisions in the mould of the Sinclair Microvision. The trouble seems to be that the manufacturers have saturated the market with televisions to the extent that most trade now comes from the trickle of sets bought as replacements for obsolete or expensive-to-repair models, and from those customers who are prepared to buy a new

set if it features innovations such as Teletext, Viewdata, or small size.

There isn't a lot that can be done about the wear-out market (Built-in premature wear-out would NOT be popular with the customer!) but new ideas and extra features will always find a market, and hence the pressure to produce LSI components for televisions, so that they can be turned into the equivalent of the humble "tranny" radio, small and cheap so that families will aspire to owning not two sets but three, or even four!

MONOMAX

One expression of the effect of this pressure is a new wonder chip from Motorola. Coded the MC13002 in its 625-line European version, this device makes possible a television using only two integrated circuits, a tuner module, and six transistors for power output stages. The chip carries out all the video processing functions required by a black and white television, and (this is the important bit) the chip requires only ONE external passive component, actually a high stability resistor for an on-chip oscillator, replacing hordes of resistors, capacitors, and chokes in the conventional layout. The nickname Monomax is meant to indicate that this is the maximum number of parts for a monochrome TV currently possible on one chip, but Motorola also predict that a COLOUR version will become available fairly soon.

On the MC13002 you get a 100 microvolt input sensitivity at an i.f. frequency of 35 to 60MHz, 2.5V of sound i.f. output, and 1.2V of video signal. Subsystems on the chip include a video i.f. amplifier, detector, AGC and noise processor system, horizontal and vertical sync generators and signal processors, a video processor and a power supply regulator. The second chip you need to add is a device such as the TDA1190P sound channel processor which is already with us, and also uses few external passive components. The Monomax will run from supplies between 10.8 and 15 volts, and dissipates less than 500mW, making it ideal for miniature battery powered TV sets. It is, however, not limited only to the portable sets, its signal processing is good enough for sets with much bigger screens using mains supplies.

The chip itself is not huge by digital standards but it does include 200 linear bipolar devices and 200 logic gates ('fraid you can't do anything these days without a FEW gates!), and it will soon be one of those jelly bean parts which will only set you back a couple of pounds or so.

BAR TALK

Digital displays are excellent for high precision measurements of parameters which change only very slowly with time, but if the rate of change or the peak value of a changing signal carries valuable information then a digital meter is excruciatingly difficult to use. (Hands up all those who decided to "get with it" by buying a digital multimeter, only to discover they still needed one of the steam versions for a surprisingly wide range of jobs. Me for one!)

If you need a simple analogue display device for a project, and you don't like the idea of using a delicate, bulky, and expensive moving coil meter don't despair, use a solid state bargraph display with a row of l.e.d.s which light up progressively to indicate signal level. This system isn't going to win any prizes for precision, but it will provide you with a compact and rugged indicator which gives easily interpreted information on rates of change and signal excursions. All you will need is a row of l.e.d.s, a handful of comparator circuits, a voltage reference generator, and a bunch of resistors to set the thresholds of each comparator and the l.e.d. currents. Oh, and if you need to respond to an a.c. signal, for a VU meter perhaps, then you will need a signal amplifier and a detector to give a reasonable drive for the comparators.

If that doesn't sound too simple to you, it's probably because you haven't run into a family of bargraph components recently introduced by Sharp of Japan, which actually make the whole job as easy as pie. The family consists of 11 l.e.d. bars, some with five points, coded GL-105XX, and some with seven points, coded GL-107XX, in a very wide choice of colours including composite types where the first (say) five points are in "restful" green, and the remaining two points are in "watch-it!" red. Complementing the displays, Sharp have two driver chips, the IR-2E01 for five point displays, and the IR-2E02 for the seven point versions. Inside these chips you get a signal amplifier, detector, voltage reference, comparators, resistor chain, and constant current l.e.d. drivers with the only extra components required being a single l.e.d. current setting resistor, and the smoothing and gain setting components of your choice for the signal amplifier, which is only required for low-level a.c. inputs anyway. There is even a pin which gives a logic output when a signal large enough to turn on the least significant l.e.d. is present.

Both drivers come in 16 pin plastic d.i.p.s and will perform on supply voltages of up to 18 volts. How's that for simplicity!

Digital Design Techniques...

Tom Gaskell B.A.(HONS) ELEC. ENG.

Part 2 Power Supplies... Inputs & Outputs

LAST month* we worked through some of the theory surrounding digital circuit design, and we looked at logic families and logic gates. This month we launch into some of the more practical aspects of designing and constructing with digital i.c.s.

As discussed in Part 1, TTL requires a 5 volt supply, well regulated and of a fairly high current. The range of voltage allowed is actually from 4.75V to 5.25V for normal operation; outside this range and the i.c.s may not work properly, and any voltage higher than 7 volts will destroy the i.c. Regulation and ripple should both be better than 5%. Standard TTL takes typically between 12 and 30mA per package, and LS (Low Power Shottky) TTL typically 1 to 3mA, hence the power supply should be well decoupled to prevent spurious voltages on the power supply rail from affecting logic operation. This is best done by connecting 0.1 μ F disc ceramic capacitors across the power supply rails, as near as possible to the i.c.s themselves, at a rate of one capacitor per 3 to 5 i.c.s. Several 10 μ F 25V capacitors can also be added, per board, across the supply rails. The power supply tracks should be as broad and short in length as possible.

The +5V supply to TTL is called Vcc (stands for Voltage to the Collectors).

The 0V supply to TTL is called Ground (abbreviated to GND).

It is usual to earth the "Ground" line to mains and chassis earth at one point only, to avoid hum and earth loops; there should be one connection from mains earth to the chassis, and one connection from mains earth to 0 volts; at the power supply preferably.

CMOS

This is a much more tolerant family with respect to power supply requirements. The supply to the latest "B" series of CMOS can be anything from 3 to 18V although it is usual to see it being used in the range 5 to 15V. Below 3V will cause the i.c. to malfunction, and above 18V can cause permanent damage. Because of this wide voltage range, ripple and regulation need not be as critically controlled as with TTL supplies, although it is always a good idea to have as smooth and well regulated a supply as possible; because of the lower power consumption of CMOS this is fairly easy to do. Decoupling is not necessary to the same extent as with TTL; one or two 0.1 μ F disc ceramic capacitors per board is more than adequate under normal conditions. Again, the shorter and wider the power supply tracks the better, but this is not as critical as with TTL.

*See the Points Arising on page 21

The +VE supply to CMOS is called V_{DD} (stands for Voltage to the Drains).

The 0 volts supply to CMOS is called V_{SS} (stands for Voltage to the Sources).

Although it is usual to earth the V_{SS} supply rail to mains and chassis earth at one point (as with TTL), it is occasionally more convenient to earth the V_{DD} supply instead. (If you ever do this, beware of incoming signals that may be of different polarity).

The majority of CMOS circuits can be quite easily and effectively run from a simple small battery; such as a PP9 and 9 volts is an ideal voltage. TTL is much more difficult to power by batteries as regulation is needed, and the battery life will be very limited. Whatever power supply you use, be very careful to connect it the right way round!! Both CMOS and TTL can be easily damaged by mis-connection of the supplies.

The use of mains powered supplies can be costly in small projects, but pays off very soon in larger systems. Quite simple supplies can be used, with i.c. voltage regulators providing control of the output. Fig. 2.1 shows a suggested mains power supply, which is conventional and self explanatory. The four diodes (or bridge rectifier) rectify the a.c. from the transformer to full-wave d.c., which is smoothed by C1. The voltage regulator stabilises and regulates this voltage, while C2, C3 and R1 prevent unwanted oscillation of the i.c. itself. For currents above 100 or 200mA, the voltage regulator should have a heatsink fitted, although it is well protected; these i.c.s have built in thermal overload and short circuit protection. Although 5 or 12 volt regulators can be used with the transformer intended for the 15 volt regulator, their power dissipation will be considerably more, and they are likely to require more heatsinking than if they used lower input voltages. Note, though, that the input of

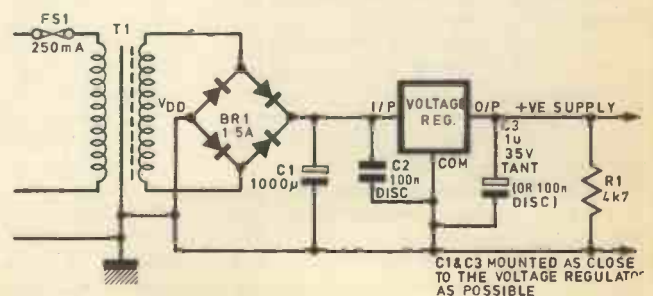


Fig. 2.1. Regulated mains power supply

the d.c. level should be 3 volts or more above the required output voltage to allow the regulator i.c. to work properly. Remember that the d.c. voltage level is the transformer secondary a.c. r.m.s. voltage multiplied by 1.414 minus 1.2V (the two diode drops);

$$V.d.c. (Unreg) = (1.414 V.a.c.) - 1.2$$

INPUTS AND OUTPUTS

Fig. 2.2a shows the circuit diagrams of TTL and CMOS input and output configurations. The TTL inputs have single protection diodes, and are frequently connected to multiple-emitters of the TTL input stage; these are specially formed transistors with several emitters. Each emitter can behave conventionally on its own, or can act together with the other emitters forming the relevant logic function. The use of this type of transistor removes the need for more active elements and diodes on the input, and speeds up operation of the circuit. The output stage has a fairly high current sinking transistor to speed up the change from logic 0 to logic 1. This configuration is known as a "Totem Pole" output.

Because of the very high input impedance of CMOS and the danger of static charges causing damage, the inputs have a resistor/diode network as shown in Fig. 2.2b. This input network should not be relied upon to "catch" high voltages applied knowingly to the inputs—that should be done using external diodes—but they are quite effective at protecting against static and other transient damage. The moderately high output impedance (usually in the range of 200 to 500 ohms) can also result in damage being done; hence the output protection diode configuration.

The relative performance of TTL and CMOS inputs and outputs is shown in Fig. 2.3; these are typical limits for the majority of logic inputs and outputs in each family.

UNUSED INPUTS

If the logic input to a TTL i.c. is left "floating", i.e. not connected to anything, it will naturally go to a logic 1 state. In this condition though, it is very susceptible to noise, transient spikes of voltage, etc. In critical cases the unused input should be connected to Vcc with a 1kΩ resistor. Note that

several inputs can be paralleled; only one 1kΩ resistor is needed for up to 10 paralleled unused inputs. (Never connect a TTL input directly to Vcc—transient voltages can very easily destroy it if this is done without a series resistor.) If the logic input is not critical of the occasional spurious pulse, of course, no resistors are needed because the input can be left to "float". If a logic 0 state is required for an unused TTL input, connect that input directly to ground, NOT via any resistor. Of course, any unused logic input can be connected to any logic output, as long as fan-out is not exceeded (see below). Note CMOS inputs must never be left floating.

FAN IN/FAN OUT

Any logic output can only satisfactorily drive up to a certain number of logic inputs. For standard TTL the limit is 10 logic inputs, for CMOS it is greater than 50. To increase the number in either case, it is necessary to make one or more of the logic inputs being driven that of a buffer (or two inverters in series). The output of this buffer stage can then go out to drive a further 10 or 50 gates, as appropriate.

DRIVING LOADS

The input/output performance chart of Fig. 2.3 shows that, whereas TTL can drive small loads reasonably successfully; 4mA for logic 1 typically, and 12mA for logic 0, CMOS is very poor indeed at load driving. (To be on the safe side, you should always use TTL load driving at logic 0, i.e. current "sinking". It is generally far better at this than current sourcing). In both families there are special i.c.s which are designed to make interfacing and driving loads somewhat easier.

In TTL this is mainly provided by "open collector" outputs; i.e. the final output is an npn transistor, with its

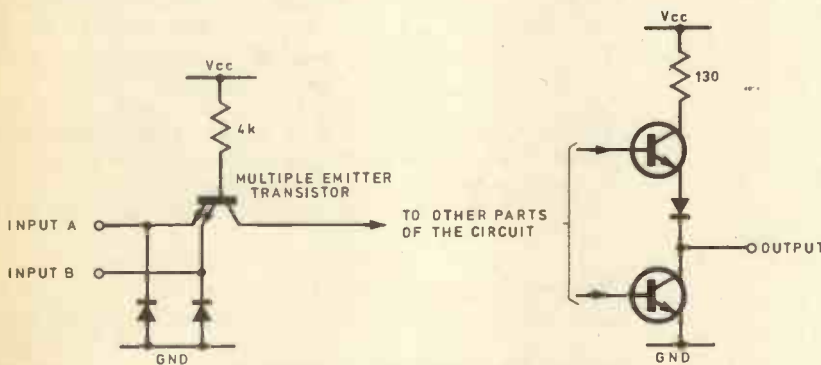


Fig. 2.2a. Typical TTL input/output configurations

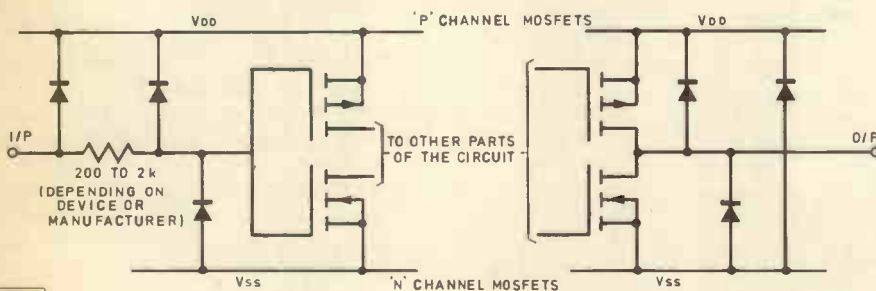


Fig. 2.2b. Typical CMOS input/output configurations

PARAMETER	STANDARD T.T.L. 5V SUPPLY	CMOS	
		5V SUPPLY	15V SUPPLY
Output voltage in logic 0 state (min)	0	0	0
Output voltage in logic 0 state (max)	0.4V	0.01V	0.01V
Output voltage in logic 1 state (min)	2.4V	4.99V	14.98V
Output voltage in logic 1 state (max)	3.3V	5V	15V
Typical max output current in logic 0 state	12mA	0.5mA	0.6mA
Typical max output current in logic 1 state	4mA	0.3mA	0.5mA
Typical quiescent supply current for whole i.c.	15mA	0.005μA	0.005μA
Maximum input current (typically)	1mA	10pAII	10pAII
Maximum voltage at input which is still seen as logic 0 (i.e. lower threshold)	0.8V	1.5V	6.5V
Minimum voltage at input which is still seen as logic 1 (i.e. upper threshold)	2.0V	3.5V	8.5V

Fig. 2.3. Input/output performance of TTL and CMOS

emitter connected to ground and its collector taken directly to the output pin; there is no pull-up to V_{cc} . Many logic gates and other logic devices can be provided with open-collector outputs; these can drive i.e.d.s, relays or other similar loads directly, fed from the V_{cc} supply rail or even a higher voltage than V_{cc} in some cases. Figs. 2.4a and 2.4b show the arrangement of such types of load driving. When an inductive load (e.g. a relay) is used, don't forget the statutory protection diode across it, to protect the TTL output transistor from huge reverse voltage spikes caused by the back e.m.f. from the load.

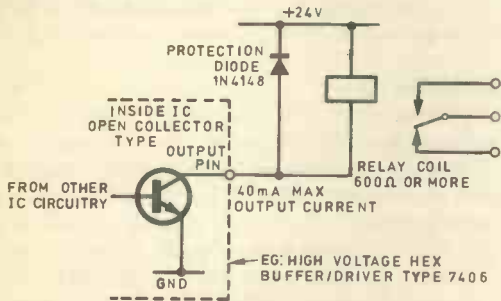


Fig. 2.4a. Open collector driving of a l.e.d.

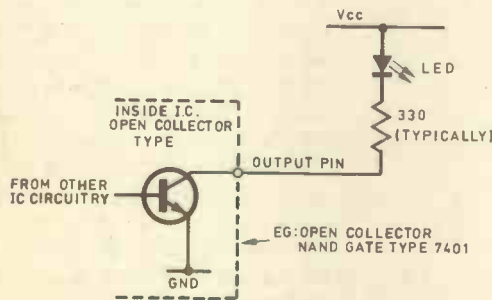


Fig. 2.4b. High voltage driving of a relay

CMOS i.c.s type 4049 and 4050 are inverting and non-inverting buffers respectively, with six buffers in each i.c. package. They are designed primarily to enable CMOS devices to drive TTL inputs, but are useful generally as high current drivers. Although their source current is only between 1 and 2.5mA, they can sink 6mA at 5V, and more than 16mA at 15V—a very handy amount of current, which can drive i.e.d.s, some relays and similar loads. The inputs of these devices are unusual, in that they can be fed with logic levels between +3V and +15V, yet the power supply can be different in voltage; for example, the i.c. can have an input range of 0 to 15V, yet a supply rail of only +5V, in which case the output voltage range is 0 to +5V. If the supply rail is 15V, then the output range becomes 0 to +15V. When using these devices to drive several loads simultaneously, be aware that the maximum power dissipation for the i.c. package is 200mW, and above this thermal damage can occur.

For displaying information on "7-Segment" i.e.d. displays (i.e. the type found in many calculators and clocks) a decoder/driver is available in CMOS; the 4511. This is designed to have a high current source capability to make interfacing with displays easier, and has a capability of driving up to 25mA per segment. We shall look into the driving of 7-segment displays later in the series.

Finally, the 4017 CMOS "Decade counter" is able to drive i.e.d.s directly, due to its internal current limiting on outputs. The actual device itself will be looked at later, so for the moment it is sufficient to mention that it has this output capability. See Fig. 2.5a. Direct driving is only safe at sup-

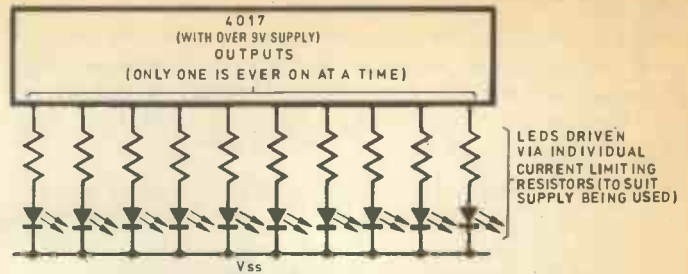


Fig. 2.5a. A 4017 driving l.e.d.s with $V_{dd} > 9V$

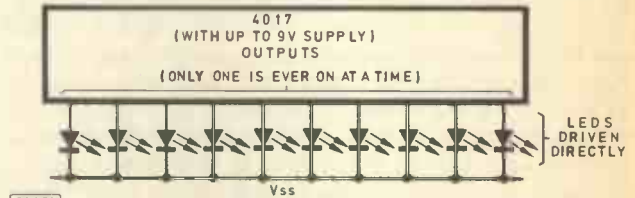


Fig. 2.5b. A 4017 driving l.e.d.s with $V_{dd} < 9V$

plies of up to 9 volts; above this, individual resistors should be used in series with each i.e.d. as shown in Fig. 2.5b. Since only one output is ever on at once, there may be a temptation to connect all the i.e.d. cathodes together, and take them down to V_{ss} with a single common resistor; this is a temptation to avoid! The i.e.d.s can break down when reverse biased, which they all would be with the exception of the i.e.d. that's turned on, and this can cause large currents to flow in the 4017 output stages, resulting in possible damage. So, for a V_{dd} of over 9 volts, stick with the circuit of Fig. 2.5a.

CURRENT BOOSTING

A simple way of doubling the output current of a CMOS logic gate is to connect another gate in parallel! Simply join up the inputs of the two gates and the outputs. The two gates (or more) should be in the same i.c. package, though, because variations in transfer characteristics between packages could cause large transition currents to flow. This paralleling procedure also applies to TTL but is used less due to the inherently higher output currents of TTL.

The usual method of boosting output current is to add a small extra circuit; examples are shown in Fig. 2.6. In prac-

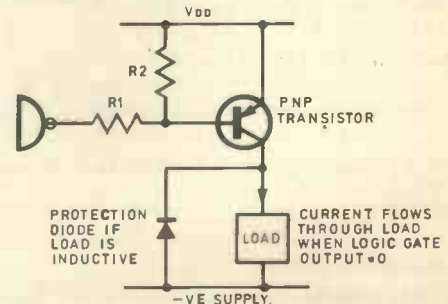


Fig. 2.6a. Load driving circuit for logic 1

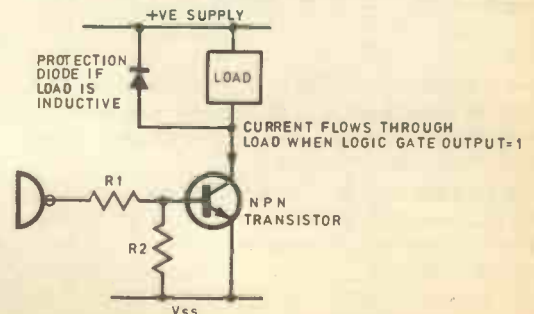


Fig. 2.6b. Load driving circuit for logic 0

tice, the values of R1 and R2 are determined by the gate output capability. If we assume 0.3mA maximum output current for the gate, then resistor R1 will be:

$$R1 = \frac{(V_{dd}-0.6)}{0.3} \text{ (approx.)}$$

R2 ensures that the transistor turns fully off when the logic gate output has gone back to the state which results in no current flowing through the load. A good "rule of thumb" is to make it very roughly one third of the value of R1, so:

$$R2 = \frac{R1}{3} \text{ (approx.)}$$

Since the transistor base current is limited by these resistor values, it follows that the transistor gain determines the maximum current that we can expect to drive through the load. For conventional medium to high gain silicon transistors we can obtain currents of at least 30mA using this technique, usually even more. If considerably more current than this is required it will be necessary to add extra stages of transistor drive circuitry in "darlington" or other fairly conventional circuit configurations.

One of the easiest ways to interface loads with CMOS and TTL logic is by using VFETs. These are high power handling f.e.t.s with extremely low input current requirements. The circuitry couldn't be easier; see Fig. 2.7. Note that many

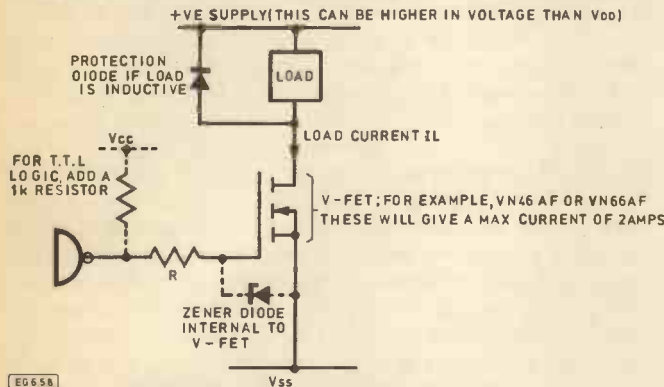


Fig. 2.7. VFET interface circuit

VFETs have a 15V Zener diode between their most negative point and their gate, as a protection device. If V_{dd} is 15V or lower, there is no problem and the resistor R can be left out, with the output of the CMOS device connecting to the VFET gate directly. For a V_{dd} of 15 to 18V, resistor R should be added to limit the current passing into the Zener diode; a typical value would be 100k. Although they are not cheap, these devices are slowly falling in price, and they do represent a very easy and effective way of interfacing logic with high current loads.

LOGIC AND SWITCHES

In most logic circuits there is a requirement for human intervention or operation by means of a switch. This is a simple matter if the switch function is basic; re-setting a counter, switching on a l.e.d. via some interface logic, or whatever. Fig. 2.8 shows these basic switch circuits. Note, that in order to reverse the switch action of the TTL circuit an inverter of some sort must be added; the switch cannot be taken to V_{cc} in the same way as with CMOS.

CONTACT BOUNCE

The problem with the circuits in Fig. 2.8 is that of "contact bounce". All mechanical switches suffer from this problem. When the switch is activated the "wiper" or moving contact swings across to touch a fixed contact. As they touch there is a momentary period when the contacts "bounce" apart,

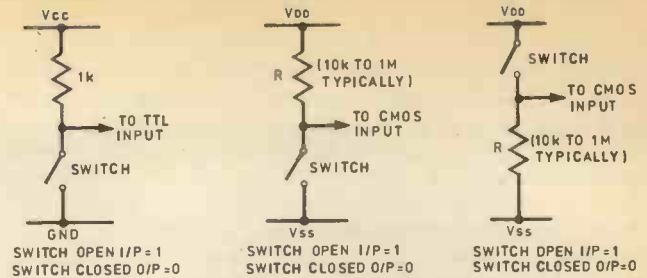


Fig. 2.8. Simple logic input switches

then make contact again, then bounce apart, etc., etc. This process can last for several milliseconds before the logic level coming out of the switch finally becomes stable. This "bounce" can result in spurious pulses being fed into logic inputs, in turn leading to false operation of the circuitry. In many cases these spurious pulses may not matter, but where they could cause problems a "de-bouncer" circuit is needed. The most simple of these simply stretches any pulses to such a duration that they all "merge" into one another, and the logic change is a single one without any pulses; this pulse stretching circuit is one that we looked at last month, and is shown again here in Fig. 2.9 (TTL should not use the versions shown in Fig. 2.9; the "latch" de-bouncer circuit described next month should be used instead.)

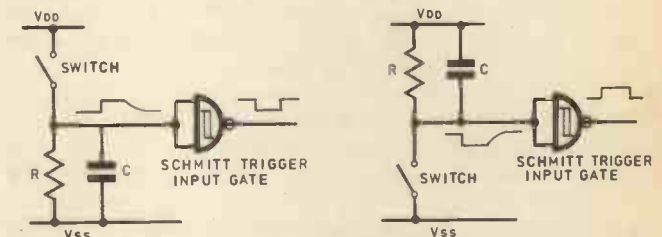


Fig. 2.9. Simple contact de-bouncing circuits for CMOS logic for either a 0 or 1 output.

The time constant RC should be long enough to maintain the logic level during the entire period of contact bouncing; typical values are 100k and 0.1μF, or even 1M and 0.1μF. These circuits can be effective in many applications. With poor switches, and in particularly critical circuitry, though, the occasional small pulse can still get through. Electrically noisy environments can exaggerate this problem, needless to say. Next month we shall be looking at a more sophisticated circuit for switch de-bouncing as well as touch switches, timers, oscillators and testing. But now we'll turn to the practical aspect of the series and look at constructional techniques and the first of our mini-projects the Multi-Alarm.

CONSTRUCTIONAL TECHNIQUES

There are two basic approaches to building logic circuits; the components and link wires can be plugged into and built up on a "breadboard" or a "printed circuit board" (p.c.b.) can be made up from a specially designed master artwork, and the components all soldered onto this, with most interconnections being done automatically by the p.c.b. tracks.

BREADBOARDS

These are wafer-shaped plastic blocks, with a large number of small holes in an 0.1 inch grid. Beneath this pattern of holes sit a number of high quality spring clips which grip wires and component leads pushed through the holes, and interconnect them in groups of five "holes" at a time. Interconnection between groups of sockets can be done by using insulated single cored wire, stripped back at each end.

Because no soldering is involved, there is no risk of heat damaging components. All parts can be used and re-used "ad infinitum" and component values can be experimented

with and selected very rapidly. Wiring changes and i.c. changes are, of course, virtually instantaneous. Along each long edge of the breadboards there are continuous rows of holes which act as power supply distribution to all parts of the circuit.

PRINTED CIRCUIT BOARDS

These are more robust and compact than breadboard circuits, but can take a long time to make, or are expensive to buy. Changing interconnections is very messy; tracks must be cut and wire links added. Changing components is a slow process, and if repeated several times it can cause the copper track to peel away from the board; for this reason, i.c.s are best fitted into good quality i.c. sockets. (Never use "cheap and cheerful" sockets, because unimaginable problems can be caused by oxides forming on the contacts, and the contacts losing touch with the i.c. pins).

"Stripboards" are a mixture of the flexibility of breadboards and the robustness of p.c.b.s. They have strips of copper on a p.c.b. type basis, with arrays of holes on an 0.1 inch grid. Connections are by soldering, and areas of the board are linked together with wire links again. The most well known type of stripboard is "Veroboard". Another type is called "Matchboard" which have the tracks ready cut and laid out in the same layout as breadboards. This enables breadboard designs to be instantly transferred across to the more permanent "Matchboard" without needing to cut tracks and without needing to re-lay the circuit.

CONSTRUCTIONAL AND CHECKING HINTS

For complex circuit layouts, a good idea is to trace or photocopy the circuit or layout diagrams then draw in the interconnection on this in red pen as you add them. In this way, should your train of thought be disturbed, you won't have forgotten how much you have done.

Beware of trying to force i.c.s into socket or breadboards if their "leg" spacing seems too wide. The solution is to lie all the legs on one side of the i.c. on a metal sheet or plate on the bench, and apply gentle pressure to the whole i.c. to bend the legs nearer to being at right angles to its body. Then turn the i.c. over, and repeat the procedure for the opposite row of legs. Only a tiny movement of the legs is needed, and BE GENTLE! The i.c. should then slot more easily into the socket contacts.

Before switching on, check that the power supply or battery is connected the right way round, and visually check for any obvious short circuits. If possible, check the inter-wiring. A short cut way of doing this fairly effectively is to look at the circuit assembly, and find any i.c. pins which are not connected to anything; check back with the circuit or layout diagram to see if those pins really should be connected to something or not. Not all i.c. pins are used, but this method can show up a surprising number of faults nonetheless. Finally, ensure that all CMOS inputs not being used are connected to the 0 volts supply (Vss) or the +ve supply (Vdd), or another CMOS output. Whatever you do, don't apply any signals into an i.c. without its power supply being turned on.

THE MULTI-ALARM



This is a multi-purpose project, which can be used in many different ways. Basically, it's an 8 input alarm system; a negative edge on any input switches on a relay (to drive an alarm bell or similar, external to the unit), and light up a front panel i.e.d. to indicate which channel or channels the alarm was triggered by. A "reset" switch is provided, as is an "arm" switch, which sounds a buzzer for 30 seconds and disables the alarm system, to allow you to get clear of the sensors before the alarm is activated.

The alarm sensors can be anything you want them to be! Make switches, break switches, touch switches, water-level switches, light level switches and even switches that sound the alarm when you break a light beam. Any of these, and more, can be incorporated, with any mixture of different types in the one unit. The Multi-Alarm, then, can be used not only as a simple burglar alarm, but as a general purpose monitor/alarm system.

CIRCUIT DESCRIPTION

The circuit diagram of this Multi-Alarm which is shown in Fig. 2.10 is based on Schmitt trigger input NAND gates, connected in pairs as latches. Because Schmitt devices are used, the inputs to these latches can be touch switches, slowly changing voltages, etc., which gives the system its flexibility. One output of each latch lights a l.e.d. via a conventional transistor driver circuit, to indicate that the channel has been triggered. The other latch outputs feed the input of an 8 input NOR gate, IC5. Hence, if any latch is operated; the output of IC5 goes to logic 0, which is inverted by IC6b, and turns on relay 1 via R33, R34 and TR11 (a standard transistor driving stage). D12 protects the transistor from back e.m.f. voltage surges. The relay contacts are used to sound an external alarm.

When the "arm" switch S2 is pressed, this starts the timing period of IC8, which is a standard 7555 i.c., connected as a timer. R28 and C3 set the timing interval of 30 seconds approximately. When the timing period starts, the output pin 3 of IC8 goes to logic 1, which is inverted by IC7d, and fed to IC7b pin 6. Since IC7a and IC7b are connected as an oscillator of approx. 1kHz, this input of logic 0 starts the oscillator, which feeds the loudspeaker via TR9 and TR10. Two transistors are used in a "darlington" configuration to give more current gain and hence drive the low resistance of the loudspeaker directly. RL is included if the loudspeaker is a low impedance (4 ohms to 40 ohms), and is a 1 watt resistor, to limit power dissipation in the loudspeaker . . . and reduce the very noisy level! D11 protects TR9 and TR10 from back e.m.f. voltage surges. The transistor driver stage is fed from pin 4 of IC7b, instead of pin 3 of IC7a (which would be more usual), in order that the input to the driver stage is at logic 0 when the oscillator is turned off, preventing a continuous current flow through the loudspeaker.

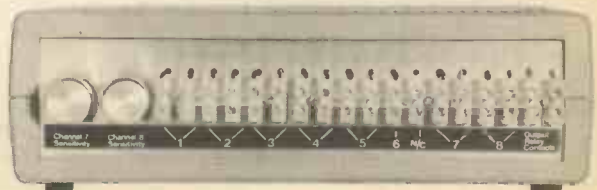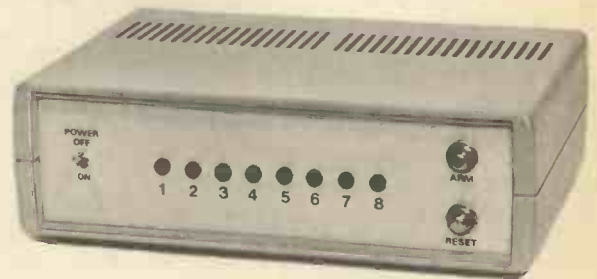

Front and rear views of the Multi-Alarm


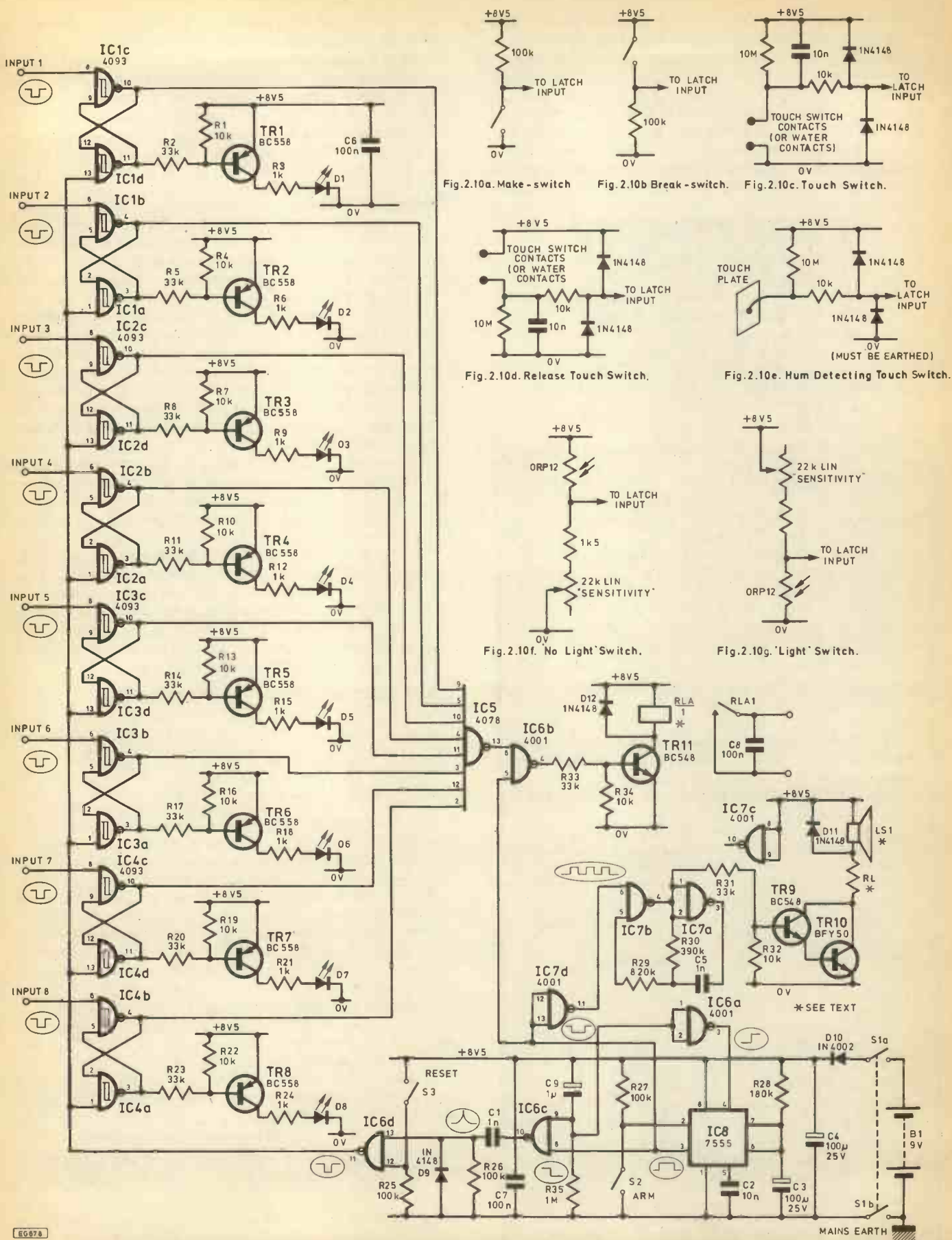


Fig. 2.10. Complete circuit diagram of the Multi-Alarm unit including alternative inputs for triggering alarm

Also during the timing period, pin 5 of IC6b is kept at logic 1, preventing any "latched" conditions of the input latches from turning on the relay. At the end of the timing period, the output of IC8 goes to logic 0, so pin 10 of IC6 goes to logic 1. The network of C1, R26 and D9 produces a short positive-going pulse from this logic level change, which is inverted by IC6d and passed to the "reset" inputs of all the latches. Hence, when the "arm" switch is pressed, a loudspeaker sounds while you have time to get out of the way, the alarm relay is prevented from operating, then as the

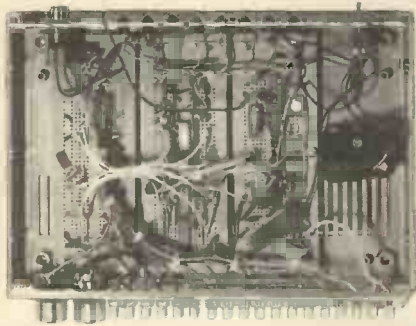

COMPONENTS . . .

Resistors

R1, R4, R7, R10, R13, R16, R19, R22, R32, R34	10k (10 off)
R2, R5, R8, R11, R14, R17, R20, R23, R31, R33	33k (10 off)
R3, R6, R9, R12, R15, R18, R21, R24	1k Ω (8 off)
R25, R26, R27	100k (3 off)
R28	180k
R29	820k
R30	390k
R35	1M Ω
RL	1W, see text

All resistors $\frac{1}{4}$ or $\frac{1}{2}$ W 10% carbon except where otherwise stated.

Capacitors

C1, C5	1n ceramic plate (2 off)
C2	10n polyester
C3, C4	100 μ 25V elect (2 off)
C6, C7	100n 25V disc ceramic (2 off)
C8	100n polyester
C9	1 μ 0 35V tant

Semiconductors

D1 to D8	Red I.e.d. 0.2in with fixing clips (8 off)
D9, D11, D12	1N4148 (3 off)
D10	1N4002
TR1 to TR8	BC558 (8 off)
TR9, TR11	BC548 (2 off)
TR10	BFY50
IC1, IC2, IC3, IC4	4093 (4 off)
IC5	4078
IC6, IC7	4001 (2 off)
IC8	ICM 7555

Miscellaneous

S1 single or double pole toggle switch
 S2, S3 pushbutton single pole push-to-make (2 off)
 Battery holder
 Small loudspeaker
 Matchboard EXP-300PC Global Specialties (3 off)
 Benchtopper case CTB-1 Global Specialties
 Terminal blocks

"arm" period ends the inputs are all reset, and wait to be triggered. Pressing S3 also causes a logic 0 level to be fed to the latch resets by IC6d. D10 protects the circuit against incorrect connection of the battery, and C4, C6 and C7 are to help smooth out any spurious pulses on the power supply rails. C9 and R35 form a power-on reset circuit, which provides a pulse to reset the latches after approximately 1 second, and which is inverted by IC6a to reset IC8 immediately after switch-on.

CONSTRUCTION

The prototype unit was made up on three Match boards. The front panel has the I.e.d.s fitted to it with conventional plastic I.e.d. clips. If required, the power switch (S1) could be hidden, or it could be a key-operated lock switch, to add security.

The arrangement of the rear panel depends somewhat on the particular inputs being used, but a good arrangement is that a length of terminal strip is fixed to the panel, with the interconnecting wires taken through holes in the panel immediately adjacent to their relevant termination. The relay contacts can also be taken to the rear panel in this way. The two potentiometers, which can be seen are sensitivity controls for two of the inputs of this unit which are "light level" inputs; they could equally well be pre-set potentiometers on the input board. The loudspeaker is glued over the grille in this top half of the case, and connected to the circuitry with a flying lead; don't forget to solder a protection diode across it the right way round!

All interconnections between boards and panels can be done in thin flexible wire, and the cathodes of the I.e.d.s can be joined together with one long length of bare copper wire, to simplify wiring. Be careful with the I.e.d.s—they are easy to damage if their leads are handled roughly. Finally the battery holder can be fixed to the bottom half of the case using "Sticky Fixers" self adhesive foam pads.

CONSTRUCTION OF THE INPUT DEVICES

When using resistive touch switches (or "water level detecting switches") in Figs. 2.10c and 2.10d, don't use offcut pieces of Matchboard or Veroboard; the base material can absorb moisture and the switch will "stick" on. Use instead pieces of "fibreglass" based p.c.b. material, or metal strips fixed to a piece of plastic. Note, though, that mains circuitry of any sort should never be taken near water, so ensure that the Multi-Alarm is being powered by batteries, not a mains power supply, if its to be used as a fluid level detecting system.

The hum detecting touch switch requires that the Vss (i.e. 0 volts) supply be connected to mains earth to operate reliably. The touch plate can be any piece of metal, so try a piece of p.c.b. material or Matchboard (moisture has no effect) or even a piece of aluminium foil. If a piece of double-sided p.c.b. material is used, you'll find that touching the reverse side from the one connected to the unit will also work! If you want to protect a metal object from being fiddled with or pilfered, simply place it on the touch switch plate; it then becomes a touch switch too!

Finally, the "light level" switch (Figs. 2.10f and 2.10g) are considerably improved if the ORP 12 light-dependent-resistor is housed in an opaque tube a few inches long, to "funnel" the light towards it, and cut out unwanted light effects. (Putting a lens in the tube to focus the light works even better.) The circuit in Fig. 2.10f can be used to detect the breaking of a beam of light in this way.

NEXT MONTH: As well as the topics mentioned above there will also be a special offer to PE readers of a GSC experimenters kit.

BUY BRITISH - BUY DOUGLAS TRANSFORMERS

MAIL ORDER FROM **TITAN** TRANSFORMERS & COMPONENTS
CENTRAL HALL CHAMBERS, DUNCOMBE STREET, GRIMSBY,
SOUTH HUMBERSIDE DN32 7EG



PRICES INCLUDE 15% V.A.T. SEND FOR OUR CATALOGUE

12/24V RANGE PRI 220/240V SEC: 00000000 00000000 OV 12V 12V OV 12V					15/30V RANGE PRI 220/240V SEC: 00000000 00000000 OV 12V 15V OV 15V 15V					25/50V RANGE PRI 120/220/240V SEC: 00000000 00000000 OV 20V 25V OV 25V 25V					30/60V RANGE PRI 120/220/240V SEC: 00000000 00000000 OV 24V 30V OV 30V 30V				
TYPE	amps	price	p-p		TYPE	amps	price	p-p		TYPE	amps	price	p-p		TYPE	amps	price	p-p	
242	0.3	1.70	0.40		112	1	2.84	1.10		102	1	3.29	1.43		124	1	3.30	1.43	
213	1	2.65	0.87		79	2	3.29	1.10		103	2	4.09	1.43		126	2	6.36	1.43	
71	2	2.77	1.10		3	4	6.18	1.43		104	4	7.85	1.73		127	4	7.86	1.73	
18	4	3.98	1.43		20	6	7.19	1.73		105	6	9.09	1.90		128	6	11.78	1.90	
68	3	3.46	1.43		21	8	8.52	1.73		106	8	12.24	1.90		123	8	14.72	2.20	
85	5	6.06	1.43		51	10	10.57	1.90		107	12	16.15	2.20		40	10	17.10	2.20	
70	6	6.67	1.43		117	12	11.94	2.05		118	16	22.46	2.55		120	12	19.44	2.35	
108	8	8.03	1.43		88	16	16.14	2.20		119	20	27.05	2.55		121	16	27.70	2.65	
72	10	8.66	1.73		89	20	18.54	2.35		109	24	32.44	3.50		122	20	32.05	4.00	
116	12	9.31	1.90		90	24	20.57	2.55							189	24	37.02	5.00	
17	16	11.46	2.05		91	30	23.63	2.65											
115	20	13.69	2.05		92	40	33.21	4.50											
187	30	15.23	2.35																
232	40	27.61	4.50																
226	60	35.35	4.00																

48/96V RANGE PRI 120/220/240V SEC: 00000000 00000000 OV 36V 48V OV 36V 48V					AUTOTRANSFORMERS 240/220-115V 65VA - 10KVA OV 115V 220V 240V					CASED AUTOTRANSFORMERS 240V LEAD IN-115V 2PIN SOCKET OUT					LINE ADJUSTMENT AUTOTRANSFORMERS 0 200 210 220 230 240 250				
TYPE	amps	price	p-p		TYPE	va	price	p-p		TYPE	va	price	p-p		TYPE	va	price	p-p	
430	1	0.5	1.43		25	65	3.90	1.10		56W	20	6.60	0.87		415C	50	2.31	0.87	
431	2	1	1.73		64	80	4.82	1.10		64W	80	8.43	1.43		416C	100	3.46	0.87	
432	4	2	2.05		4	150	6.21	1.43		4W	150	10.86	1.73		417C	200	4.00	1.10	
433	6	3	2.20		69	250	7.54	1.43		69W	250	13.17	1.90		418F	350	6.26	1.43	
434	8	4	2.45		53	350	9.73	1.90		67W	500	20.46	2.20		419F	500	6.74	1.73	
435	10	5	2.65		67	500	11.70	2.20		84W	1000	30.24	2.65		420E	750	8.33	1.90	
436	12	6	3.16	4.00	83	750	13.51	2.05		95W	2000	54.83	6.00		421F	1000	11.64	2.05	
437	16	6	39.47	4.60	84	1000	18.31	2.35		73W	3000	78.67	6.50						
					95	2KVA	34.36	5.00											
					73	3	64.74	5.00											
					73	5	97.85	6.50											
					101	10	179.05	10.00											

MAINS ISOLATORS (SAFETY SCREEN) PRI 120/220/240V SEC 60V 55V 0V 55V 60V 60V 55V 0V 55V 60V					MAINS ISOLATORS (SAFETY SCREEN) PRI 380/415/480V SEC 60V 55V 0V 55V 60V 60V 55V 0V 55V 60V					INVERTER					P.C.B. 120/220/240V. 0-12-0-12V.				
TYPE	va	price	p-p		TYPE	va	price	p-p		INV. 1.	price	P&P	6VA	price	P&P				
149F	60	8.40	1.73		243F	60	8.40	1.43		INV. 1. Cased, 13 amp, 3 pin	£49.95		9VA	1.89	0.58				
150F	100	9.71	1.73		244F	100	9.76	1.73		P&P £2.65.		12VA	2.24	0.58					
151F	200	13.84	2.05		245F	200	13.93	2.05		INV. 2. Open	£30.95	P&P £2.65.	25VA	2.52	0.87				
152F	250	16.59	2.20		246F	250	16.59	2.20					50VA	4.63	1.43				
153F	350	20.77	2.55		247F	350	20.77	2.55											
154F	500	26.03	2.65		248F	500	26.03	2.65											
155F	750	36.75	5.00		249F	750	36.75	5.00											
156F	1000	47.42	6.00		250F	1000	47.42	6.00											

SEND TODAY 50p (REFUNDABLE WITH FIRST ORDER) FOR CATALOGUE
TITAN TRANSFORMERS AND COMPONENTS
Dept. P.E. CENTRAL HALL CHAMBERS
GRIMSBY DN32 7EG HUMBERSIDE
MAIL ORDER - PRICES INCLUDE 15% VAT



5 HZ TO 100 MHz

TOMORROW'S TOOLS TODAY

GLOBAL SPECIALTIES CORPORATION



G.S.C.(UK) Limited Dept. 5D
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

Instant frequency indication from 5Hz to 100MHz; no range selection problems; a brilliant 8-digit LED display; mains or battery operation; an accuracy of 4 parts per million ± 1 count; and totally automatic operation - all this for only £77.55* with GSC's new Max-100 frequency counter.

Just take a look at our spec. Where else could you find anything similar at the price?
*Frequency range 5Hz - 100 MHz *Input impedance 1M shunted by 10pF *Sensitivity 30mV from 1KHz up to 50MHz; 120mV r.m.s. over full frequency range *Timebase accuracy ± 4 parts in 10⁶ (from 5 to 45°C) *Maximum aging rate 10 parts in 10⁶ per year *Over-frequency indication *Low-battery-power alarm *Operates from dry or rechargeable cells, an external 7.5 to 10VDC supply, or a car battery (via an adaptor) *Dimensions: 45 x 187 x 143mm *Options: 12V adaptor; battery eliminator; r.f. antenna, low-loss r.f. tap, carrying case.

Fill in the coupon for further details . . . *price excludes post, packing and VAT

G.S.C. (UK) Limited, Dept. 5D, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

MAX 100	FREQ. COUNTER	Unit price inc P&P 15% VAT £90.01	Qty	Reqd
---------	---------------	-----------------------------------	-----	------

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION - The G.S.C. 24 hour, 5 day a week service.
Telephone (0799) 21682 and give us your Barclaycard, Access, American
Express number and your order will be in the post immediately.

For Free catalogue tick box

AUDIO ANALYSER

Michael Tooley B.A. David Whitfield M.A. M.Sc.

PART 2

THIS second part concerns construction, testing and using of the samples together with possible extensions and modifications.

CONSTRUCTION

Construction of the Audio Analyser uses a Vero G-range case to house the various circuit boards and ancillary components. The case (type 4B) is approximately 298mm(W) x 170mm(D) x 80mm(H), excluding the aluminium sleeve. Assembly is best carried out in two phases; first the printed circuit boards should be constructed, and then these are mounted in the case along with the remaining components, and the wiring is added. The following notes are a guide to constructors and include points which may require special attention.

The printed circuit board design for the audio processor stage is shown in Fig. 10, with the corresponding component layout in Fig. 11. There are no special handling considerations for any of the components and the two i.c.s may be soldered directly onto the board, after the orientation has been carefully checked, or mounted in DIL sockets.

The eight octave filter channels and the monitor channel all make use of the printed circuit track design shown in Fig. 12. A component layout for the filter channels is shown in Fig. 13. The board has been designed to accommodate capacitors which have a mounting pitch of between 5mm and 15mm. Capacitors should be mounted so as to project no more than 7–8mm from the surface of the board, and the leads cropped close on the bottom. There is sufficient space on the board to allow vertical capacitor types to be mounted horizontally by bending the leads at 90°. As mentioned earlier, VR1 and/or VR2 may be replaced by fixed value resistors, typical values being 3.9k for VR1 and 10k for VR2. The board is shown wired for a bar graph display; the link 'a-b' should be replaced with a link 'b-c' for moving dot display. It is suggested that all filter channels are wired to operate in the same display mode to avoid the user suffering from mental indigestion! The i.c.s should be carefully checked for the correct orientation before being soldered to the board. Low profile DIL sockets may be used as long as the maximum height limitation is not exceeded; the filter boards are mounted on a 10mm pitch and allowance must be made for board thickness and component leads on the bottom of the adjacent board. The l.e.d.s should be mounted with their leads flat and parallel to the surface of the board. The lead length should be cut such that the rear of the l.e.d. body adjoins the front edge of the board. It is important, therefore, that the lead length of the l.e.d.s used is a minimum of 12–13mm to allow them to be mounted without having to extend the leads. The colour(s) of l.e.d.s used is a matter of personal choice; the prototype used green types since this colour is most restful to the eye for prolonged viewing.

The inter-p.c.b. connectors specified are a low cost type which are supplied with blanking plugs to obstruct any selected pin positions in the socket. This feature allows optional use of the three unused pin positions on each board to

code the actual filter boards to ensure that all 8 boards may only be inserted together in the correct positions. The suggested codings are given in Table 1 for the positions of the blanking plugs in the sockets. Should this coding system

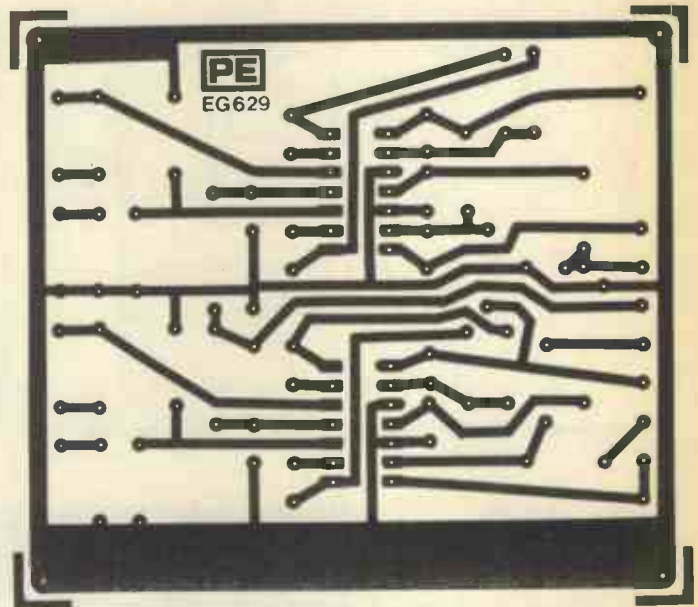


Fig. 10. P.c.b. track pattern for Audio Processor

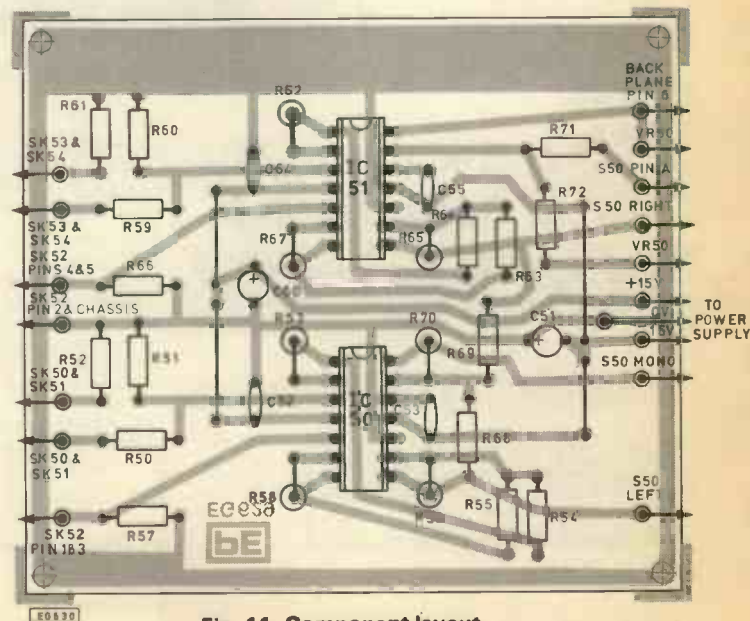


Fig. 11. Component layout

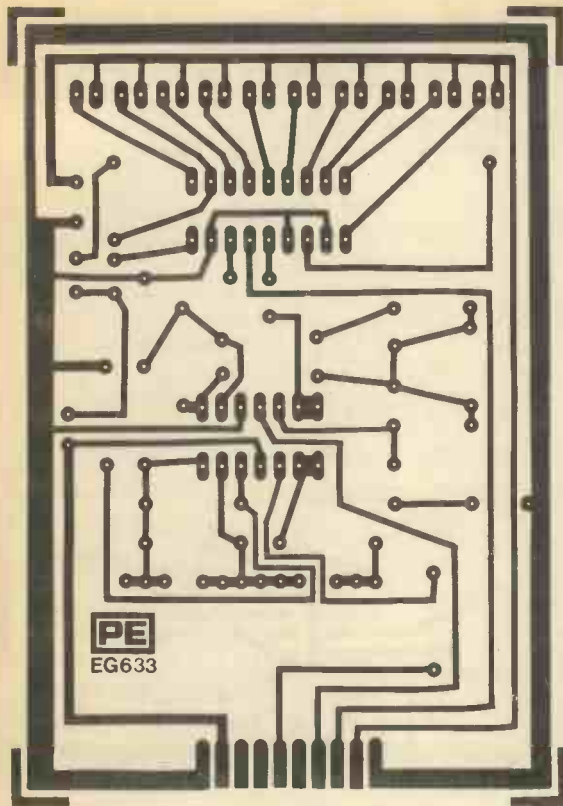


Fig. 12. Etching detail for the filter and display boards

be adopted, it is necessary to remove the corresponding pins from the associated plugs mounted on the backplane, otherwise only the 64Hz board will fit at all!

The monitor channel uses the same component layout as the filter channels with the following exceptions. R2 is omitted and R3 is replaced by a wire link. 'R' closest to connector pin 1 is replaced by R7, and 'R' closest to pin 10 is replaced by R8. 'C' adjacent to pin 10 is omitted, and 'C' next to pin 1 is replaced by C3. All other components are as for the filter channels.

PSU BOARD

The power supply printed circuit board track design is shown in Fig. 14, with the corresponding component layout in Fig. 15. The regulator i.c.s should have their leads preformed prior to being mounted on the heatsinks on the board. No insulating kits need be used, but the mounting hardware should be arranged to avoid contact with the case.

The final board in the case is the backplane on which the p.c.b. connector plugs and 3 capacitors are mounted. The track pattern is shown in Fig. 16 with a component layout shown below in Fig. 17. If preferred, the backplane p.c.b. may be fabricated from a piece of 0.1in pitch Veroboard of similar size, 135mm x 75mm. Where coded polarisation plugs have been used on the filter boards, the corresponding pins on the plugs should be cut off at this stage.

When all of the printed circuit boards have been assembled, a careful visual examination should be made to verify the correct orientation of all polarised components (diodes, capacitors, i.c.s and rectifiers), and to ensure that there are no inadvertent short circuits due to solder splashes or bridges. After this check, which may save many hours of toil at a later stage, has been completed, the second stage of assembly may proceed.


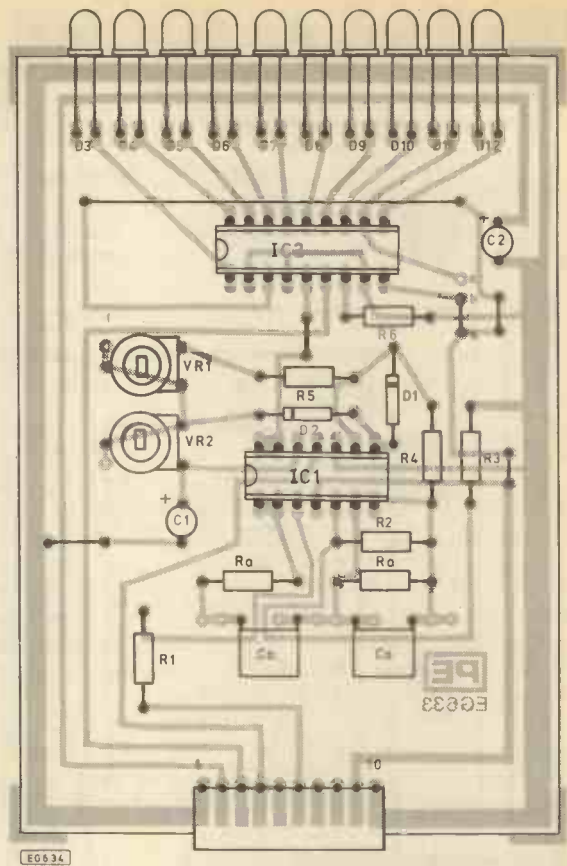


Fig. 13. Component layout

A suggested overall layout giving the positions of the p.c.b.s and major ancillary components is shown in Fig. 18. Initially the front and rear panels should be removed from the case to allow drilling of suitable holes for sockets and controls etc., and cutting of two display windows. A cutting diagram for the front panel is shown in Fig. 19, while sockets on the rear may be positioned as convenient, taking care to leave adequate clearance for the audio processor board and the two backplane support brackets. The mounting detail for the backplane and filter/monitor boards is shown in side view in Fig. 20. Two lengths, each approximately 135mm, of plastic binding comb (as used for edge binding reports etc., and available from stationers) are used to support the bottom edge of the backplane and to act as a locating and securing guide rail for the filter/monitor boards. Two bent aluminium brackets are used to secure the top of the backplane to the rear of the case. The locating strip should

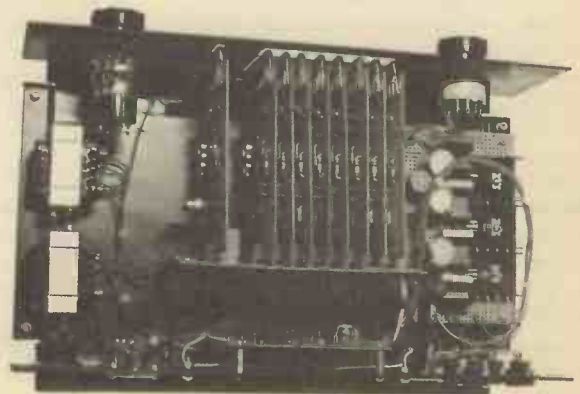

Internal assembly

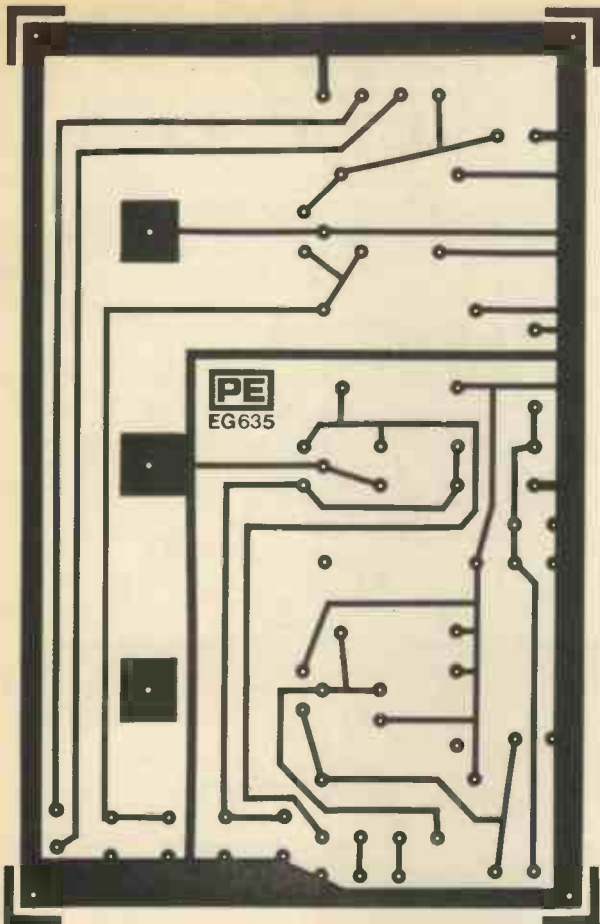


Fig. 14. Etching detail for p.s.u. board

have nine slots, one for each board, each of a width equal to the thickness of the p.c.b.s, cut with a hacksaw to the depth shown in the inset of Fig. 20. The position of these slots are given by the positions of the channel boards when fitted to the backplane. The lengths of binding comb are fixed to the base of the case with one of the cyanoacrylate 'super-glues'.

After the two strips have been fixed to the base of the case, the audio processor board and the various sockets should be mounted on the rear panel. A length of ribbon cable may then be used to link between the sockets and the PCB as this simplifies removal for fault finding or modification. Any inter-socket wiring should also be added at this time, e.g. SK50 → SK51, SK53 → SK54, etc. The rear panel is now re-attached to the base of the case, and the backplane p.c.b. secured in place with its two mounting brackets. The power supply p.c.b. and two mains transformers are now installed in the case, and the front panel temporarily re-attached complete with S50 and VR50 in place. All remaining interconnection wiring should now be added, with sufficient length included in the leads to VR50 and S50 to allow the front panel 1 to be folded down through 90° and move forward to facilitate installation/removal of filter/monitor boards.

After the interconnection wiring has been completed and checked, the unit is ready for testing. The filter/monitor p.c.b.s should not be fitted at this stage, but it is probably a worthwhile exercise to verify the correct mechanical alignment of the backplane, locating strip and front panel. It is also useful for future use if a p.c.b. extender card is made for the filter/monitor boards. This is no more than a piece of Veroboard 70mm wide with a 10-way plug at one end and a socket at the other, using the copper tracks to interconnect.

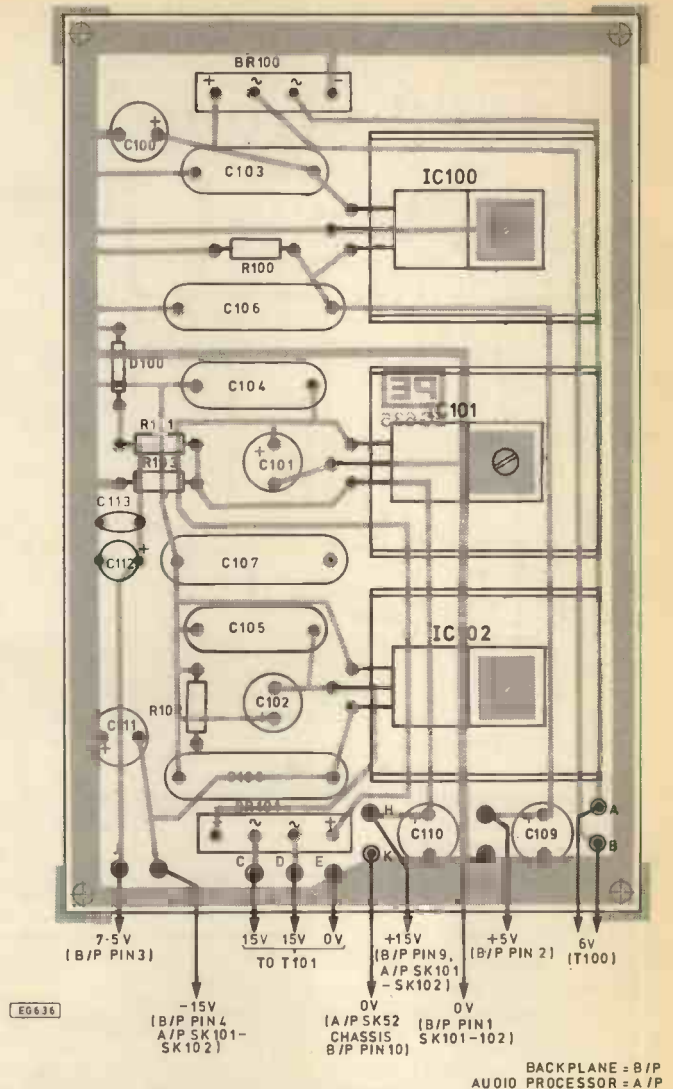


Fig. 15. Component layout

TESTING AND USING THE ANALYSER

The first stage in testing is to verify the correct operation of the mains power supply section. Power should be applied via SK100, and the unit turned on with S100. A multimeter is then used to measure the four d.c. supply rails: +5V, +7½V, +15V, and -15V. Should any of these be more than 5% in error, a check should be made on the regulator i.c. or Zener diode associated with that supply, paying particular attention to the device code number. For no output on a particular rail, the transformer input to the appropriate rectifier, the bridge rectifier itself, and the regulator should be inspected, with particular attention being paid to the orientation of the components. When the various outputs of the power supply p.c.b. are satisfactory, the power connections to the audio processor p.c.b., the backplane p.c.b., and SK101/102 should be checked with a meter before any filter/monitor p.c.b.s are installed or auxiliary units connected.

VR1 and VR2 on all filter/monitor boards should be set to their mid-value positions. The monitor channel p.c.b. should now be inserted into its socket on the backplane, S50 set to 'Left', and VR50 set to minimum sensitivity. A 500mV (r.m.s.) 1kHz sine wave signal should be connected to the left input on SK52 and VR50 increased to give a full-scale indication on the monitor channel i.e.d.s. The full-scale indication should be achieved with the sensitivity control set

near to the fully anti-clockwise position, otherwise the connections to VR50 should be changed to give minimum resistance in the 'Off' position. Selection of 'Right' should

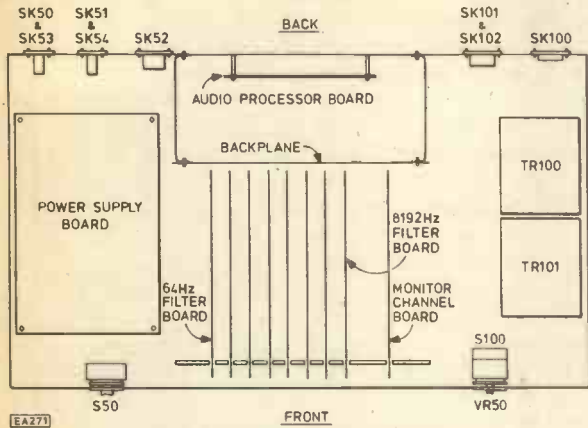


Fig. 18. Detailed overall assembly

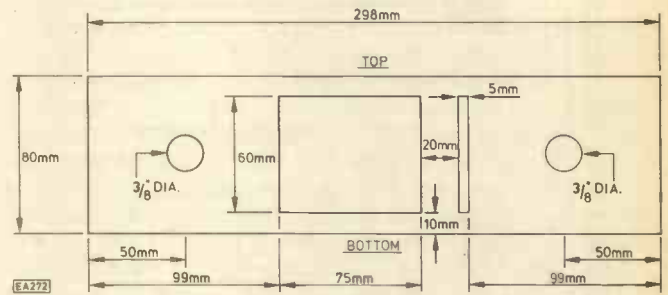


Fig. 19. Front panel detail

Fig. 16 (right). Printed circuit board of backplane


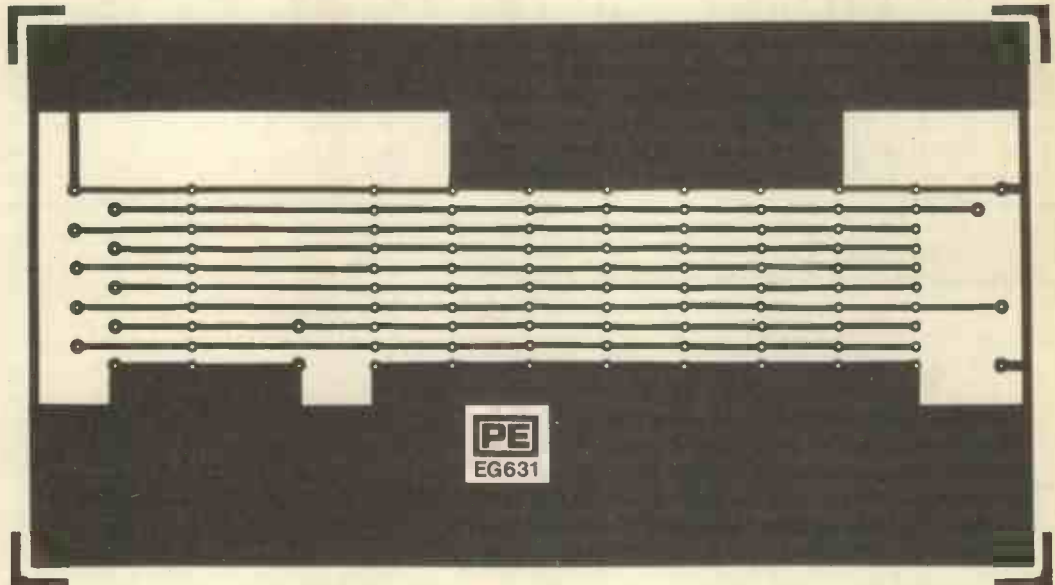


Fig. 17 (below). Component layout

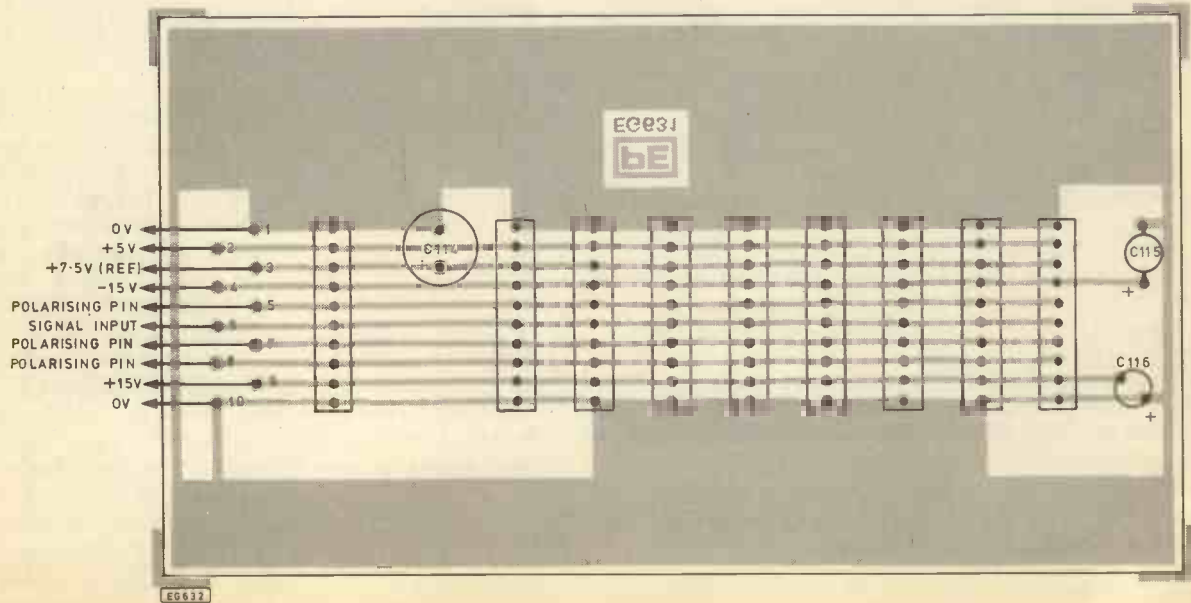

produce no display, while selection of 'Mono' should illuminate 80% of the scale (i.e. 6dB down), with approximately +3.8V on pin 5 of IC2 on the monitor board. The input signal should then be transferred to pin 3 of IC50 and a check made that full-scale indication is achieved with 'Left' selected. The tests above should then be repeated using the 'Right' input channel; the loudspeaker input is tested on pin 3 of IC51.

The final test on the audio processor section is to check that, with VR50 set to maximum sensitivity, a full-scale indication is obtained with an input signal to approximately 5mV (r.m.s.) at the tape monitor input. This confirms that the variable gain stage, IC51d, is operating with the expected gain ratio (100:1).

A 500mV (r.m.s.) signal at 1kHz should now be applied to the left channel tape monitor input and 'Left' selected on SW50. The eight filter channel p.c.b.s are now inserted in their appropriate positions, starting with the 64Hz board. As each filter is added, the display shown in Figure 21 should build up. When complete, this display actually represents the shape of the response characteristic of the 1kHz filter (see Figure 7), with the expected roll-off rate of 6dB per octave. Failure of any channel should be investigated using the extender board and with the signal generator adjusted to the filter's nominal centre frequency. Under these conditions an output of approximately $+7\frac{1}{2}$ volts is expected at pin 12 of IC1, and also at pin 5 of IC2. Otherwise, the voltage at these points will depend on the frequency separation between signal generator and filter centre, e.g. at 1kHz, the 512Hz filter output will be approximately +3.8V.

When the eight filters are installed and working correctly, the gain of each may be set if necessary. This is done by applying a constant amplitude sine wave input at the centre frequency of each filter in turn, and then adjusting the appropriate VR1 to give a voltage at pin 5 of IC2 of the channel under test which is the same (and less than $+7\frac{1}{2}$ volts) for all boards. The monitor channel is best set at 1kHz, and the analyser is ready for use when the adjustments are complete.

The analyser input sensitivities at the minimum setting of VR50 are approximately 500mV (r.m.s.) for tape monitor and 10V (r.m.s.) for the loudspeakers (equivalent to $12\frac{1}{2}$ watts into 8Ω). At maximum setting, these sensitivities are increased by a factor of approximately 100. The loudspeaker input sensitivity may be altered by changing the value of R51 and R60; these may even be fitted as switchable values or replaced by preset resistors. To obtain the sensitivities quoted for 4Ω speakers, the values should be reduced by approximately 2 times, while for 15Ω , an increase of 2 times is required. The equivalent power levels may seem rather low by comparison to the specification of many amplifiers, but in practice the drive signal may require a higher-than-expected setting. This is because the average signal level of typical programme material over the integration period of the filters is generally significantly lower than the instantaneous peak levels.

The analyser will handle inputs up to 10 volts r.m.s. at the

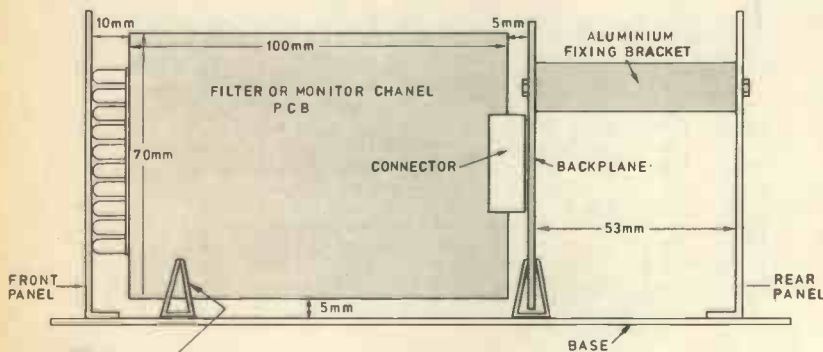


Fig. 20. Mounting detail for filter and monitor channel boards

tape monitor inputs without harm, and it presents an impedance of $47k\Omega$. With the component values shown, the inputs on the loudspeaker sockets may rise to 100 volts r.m.s. without harm, and the isolation between input and ground exceeds $30k\Omega$. The display is not affected by over-driving the input stages, but over-dissipation of the filter/display boards at maximum indication in bar mode should be avoided if the l.e.d. current has been programmed higher than 12mA/l.e.d. (i.e. if R6 has been reduced much below $1k\Omega$). Simultaneous full-scale indication on all channels in bar mode may cause the analyser to become warm if sustained for long periods, but no damage should result.

The setting of the display time constant (by means of VR2) is a matter of personal choice. Minimum setting of VR2 will produce a 'fast' display which will follow input peaks. This, however, tends to produce a visually 'noisy' display which can be tiring to the eye over long periods. A 'slower' display, on the other hand, can induce a feeling of vague frustration in the user. The optimum setting is best found by experiment, but a mid-way setting of VR2 will produce a generally acceptable result.

In addition to the uses of the analyser for equalising loudspeaker systems, using a microphone and preamplifier, as described in the first section of this article, many other applications will be found. The use of test material such as test records/tapes with the analyser connected in the loudspeaker outputs allows interesting comparisons to be made between equipment components. VHF radio material will be found to have a noticeably more restricted frequency range than, say disc, and many interesting spectral characteristics of source material will become apparent. For example, in a conversation between male and female speakers, it is quite possible to distinguish the sex of the speaker by the overall spectral shape of the voice alone; the male voice has a similar spectral shape, but generally lower in frequency, as expected. Despite the pre-existing bias of many observers to the possible 'gimmick' nature of the analyser as a component in an audio system, its use as a constant output monitor quickly gains acceptance due to the psychologically acceptable 'feel' of the display; unlikely, but true!

EXTENDING THE ANALYSER

The graphic analyser described is complete in itself, but it may also be used as the basis for a design to suit any particular application not catered for by the basic design. The possible extensions and modifications fall into three main areas: changes to the audio processor section; changes to the filter and display section; simple additions to the overall unit.

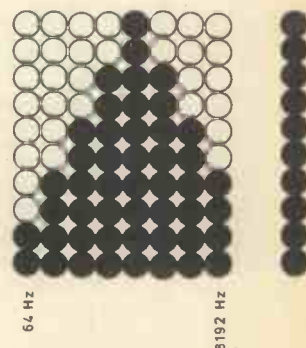


Fig. 21. Analyser response to a 1kHz sine wave

Possible changes to the audio processor section are limited only by the range of applications and the imagination/ingenuity of the user. A simple change might be the addition of multi-channel signal handling capabilities, with variable preset gain on each channel. Other modifications could include the derivation of a (left-right) difference signal, the inclusion of automatic sensitivity control, and the production of an absolute signal level indication. Many other changes will occur to constructors in the light of their own particular applications.

The addition of three further filter channels to the filter and display section has already been discussed, and the relevant filter component values are given in Table 1. The use of half-octave filters (i.e. spaced at $\sqrt{2}f_0$ multiples instead of $2f_0$) is simply achieved by modification of the filter Q by changing R_2 and R_3 , and the reduction of the overall gain by the same factor as the change in Q (change R_4). The new Q is 2.915 and R_3/R_2 is 1.657, compared to 1.5 and 1.333, respectively, in the basic design. The extension of the display range from 30dB to 60dB is readily achieved, as shown in Fig. 22, by the addition of an operational amplifier and a second LM3915. In this circuit the reference to both i.c.s is held at +7.5 volts and the signal input to the lower i.c. is amplified by 30dB. The use of 1% resistors allows the gain to be set within ± 0.2 dB, but it should be noted that an op-amp offset voltage of 5mV will move the first i.e.d. threshold by as much as 4dB, and an offset trim may be required in some cases. Extension to a 90dB display range is possible,

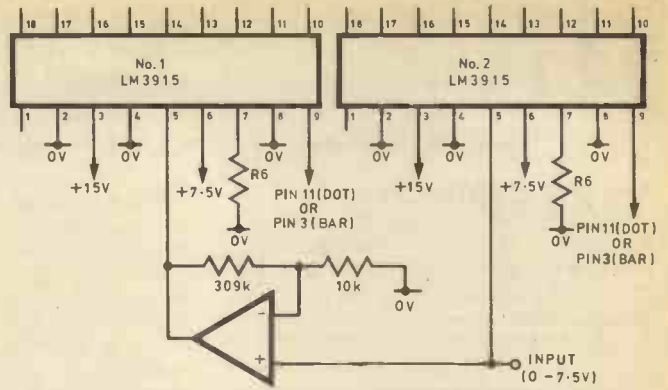


Fig. 22. Circuit for a 60dB display using two LM3915s. All pins shown with no connection are i.e.d. drive outputs

but presents a number of practical difficulties. These mainly arise from the fact that the threshold of the lowest i.e.d. will be set around 0.5mV, i.e. 500 μ V! Several offset nulls are required and careful attention to wiring design is essential.

Add-on units for the analyser are a simple way of extending the range of facilities without change to the basic design.

Next Month; a microphone preamplifier for matching a wide range of microphones to the low level input to the analyser, and a noise source.

New Generation of SOFTYs

Whilst being primarily an EPROM programmer, one could say that SOFTY is to the microprocessor software engineer what the oscilloscope is to the straight-forward electronics engineer, certainly when there are limited funds.

Anyone who has tried to investigate the working (or non-working) of a microcomputer system using conventional equipment such as a scope, will appreciate the purpose behind Softy's existence. However, the basic characteristics of this unique engineering tool will not be repeated here since these were covered in the Softy review of *PE January 1980* by Dr. A. A. Berk. Suffice it to say that Softy, apart from being a stand-alone control type microcomputer in its own right (based on SC/MP μ P), is primarily intended to aid microcomputer firmware development by allowing memory analysis and manipulation on any system, irrespective of the processor used.

Now there is Softy 2, and the question is: How does this new generation machine differ from its forefather?

SINGLE SUPPLY EPROMS!

Immediately apparent in the photograph is that Softy 2 is housed in a ABS plastic case; this comprising two halves which clip together, and being of the same ilk as that used on the Sinclair ZX80. The power supply is also enclosed in a plastic "battery eliminator" type case with integral three-pin mains plug. The case incorporates an anti-static tray, using conductive foam for EPROM storage, and the zero insertion force (ZIF) socket has a "personality Switch" to accommodate the pin-out requirements of the various EPROM devices. Notably, Softy 2 may be used to program single supply rail EPROMs too, such as the 2716, 2516, 2732 and 2532.

EXTRA MEMORY

Memory size has been doubled to now give a 2K static RAM buffer (working RAM), 2K monitor ROM, and PIA with scratchpad RAM (INS 8154).

The ROMULATOR facility, which is an in-circuit ROM emulator for dynamic program development, has been improved with buffering on address and data lines, and a ROMULATOR ribbon cable with terminating 24-pin d.i.l. plug is to be supplied as standard.

In addition to the original Transwift software based cassette interface, there are serial and parallel I/O routines for interfacing to another computer, a printer (RS232 and Centronics etc.) tape reader and punch etc.

NEW COMMANDS

Among the new or improved commands added to Softy's repertoire are INSERT and DELETE. The former looks ahead for the first

Softy 2 is available direct from Dataman Designs of Lombard House, Dorchester, Dorset, and costs £169 plus VAT ready built and tested. No kits are available. It is also available from Watford Electronics and other general suppliers.

occurrence of three unused bytes (FF FF FF) and shifts the preceding code rightwards to allow space further back in memory to insert

another instruction. The latter, DELETE, is more or less the reverse of this. The first three unoccupied bytes are found and the code shifted left to remove the instruction under the cursor. Both these commands will shift as much of the 2K as is necessary but will not work if there is no free space. This kind of flexibility means that you do not need to be a computer to program one. In all, there are seven extra keys on the Softy 2 keyboard.

Softy 2 has not changed its role and all the original features remain. Essentially an intelligent memory module designed to reveal as much of its contents as possible on a standard TV screen, it has its own UHF modulator.

The editing capabilities benefit from a double cursor system which is intended to take the pain out of offset calculations for relative jumps, there are numerous useful functions like a match-byte which will seek out the occurrence of any byte of code throughout the memory, and highlight it on Softy's unique multi-intensity display.



MICRO PROMPT.

The hardware and software exchange point for PE computer projects

A BLANK EXPRESSION

Sir—Like R. J. Newman (*Microprompt*, May '81) I was troubled with the blank character apparently inserted by the STR\$ function at the front of strings derived from numeric values.

Adrian Waters, founder of the UK101 user group (now Computer User Aids) then explained to me that the blank was already there, before the application of the STR\$ function if the value is positive, its place otherwise taken by the negative sign. He also pointed out that this was a feature of BASIC which was probably present in a number of versions, apart from the UK101. The statement X\$ = "8" accepts "8" as a literal, not a numeric value, so there is no leading blank in this case.

To demonstrate the presence of the leading blank in positive numeric values, give your UK101 the following instructions: PRINT "8" : PRINT 8 : PRINT -8, when you will note that the first statement yields an 8 in the first print position, the second an 8 in the second print position, thus indicating the presence of the leading blank and in the third case the negative sign takes the place of the blank.

The following BASIC subroutine removes the blank character. If the application cannot possibly yield a string with other than a leading blank, the first line may be omitted.

```
5000 IF LEFT$(XS, 1) <> " " THEN
RETURN
5010 XS = RIGHT$(XS, LEN(XS) - 1) :
RETURN
```

On the subject of the UK101 User Group I must say that Adrian Waters has been most helpful in helping me to sort out little problems such as the above. My one disappointment was the apparent lack of response to his idea that we should form local groups within the User Group. Since local contact can be useful on occasions, especially when one is a fair distance from London, I would be interested to hear from other UK101 and OSI Superboard users in the Edinburgh and Lothian area—whether or not they are members of a national group—if they are interested in forming a local association.

An S.A.E. would be appreciated to facilitate replies. Hopefully such local groups can be run to complement rather than compete with the national groups.

David J. Giles,
Edinburgh.

It should be emphasised that material presented in Prompt has not necessarily been proven by us. Neither can compatibility with all generations of the computer equipment to which it relates be guaranteed.

SOFT BAUD RATE

Sir—I wonder if any of your readers would be interested in the following cassette Baud rate modification of the Compukit UK101. All the previous Baud rate modifications have been to allow teleprinters etc., to run from the ACIA. This modification allows true software control of the cassette interface Baud rate selectable between 300/600 and is working perfectly in my system.

The modification isn't as difficult as one might at first think to install, as the p.c.b. has a track taking IC14 pin 5 up to IC68 pin 13 anyway, a spare inverter/buffer is available on IC62 and thus only a small amount of wiring is necessary.

After reset pin 5 of IC14 is at a 0 and K57 then, when reaching 1100 is loaded with 0110 and thus only divides by 6, this causes the ACIA to run at 600 Baud, the diode and 4k7 resistor allow C11 to charge faster and remove any problems when loading data at the 600 Baud rate.

To select 300 Baud simply POKE 61440, 81 which causes IC57 to be loaded with 0000 after reaching the count of 1100 thus dividing by 12, as pin 2 of IC62 is now at a 0 the 4k7 resistor has no effect on the charging time of C11 due to the diode series with it.

Remember after reset and entry into machine code F0004 must be set to 51H for 300 Baud machine code load. In BASIC POKE 61440, 17 selects 600 Baud.

The following machine code routine modifies the beginning of the subroutine to move the display up one line and enables the user to have the top one or more lines static, as a heading, whilst the data beneath scrolls.

Suggested start address:

0230	A2D4	LDX
0232	A0000	LDY
0234	84E3	STY
0236	A080	LDY
0238	4C66 FB	JMP

80 leaves top 2 lines unscrolled
40 would leave only one line
C0 would leave 3 lines etc.

Now when printing lists, say,
**IF PEEK 520 = >15 THEN POKE
11,48:POKE 12,2:X =USR(X)**

and screen will scroll up leaving top lines unmoved.

NB. All above addresses are with new monitor.

* If difficulties are experienced in receiving data from tape try varying the resistor value.

NEW MONITOR SAVE/HEX DUMP

Sir—In the UK101 Manual a very useful cassette save/hex memory dump routine is described. This works with the OLD monitor, but is not compatible with the NEW one.

Since a number of Compukit owners have upgraded their systems with the new monitor—and new kits are delivered with it, there seems to be a definite demand for a routine with the new monitor. The following program will do just that.

Like before, the starting address of the code to be saved should be placed in \$00F7 (LOW) and \$00F8 (HIGH). The end address goes into \$00F9 (LOW) and \$00FA (HIGH). However, the program starts at \$0228 instead of \$0222 previously. The reason for this is that the new monitor occupies addresses \$0222-\$0224 for NMI—and \$0225-\$0227 for IRQ—vectors. See opposite page.

At the same time, I should like to express appreciation of the very useful Memory and Address Decoding Maps submitted by Mr. David McDonnell in the March issue of P.E. However, a slight correction should be made to his Hardware Memory Map, in accordance with the previous description of new monitor usage. His line:


"\$0222 to \$02FA: UNUSED—USING NEW MONITOR EPROM"

should instead read:

"\$0228 to \$02FA: UNUSED—USING NEW MONITOR EPROM"

I have found the Compukit UK101 to be a system of great potential for a reasonable price, but have experienced a very particular and unexpected difficulty; that of obtaining a detailed monitor listing, for the old as well as the new version. I think a responsible attitude on behalf of the producer amounts to considering such documentation as being an integral and necessary part of the combined hardware/software product sold, and that such monitor listings should be available at a reasonable price for those who feel they need them to take full advantage of the computer's potential. Do you not agree?

Mr. Gisle K. Dyvik,
Norway.

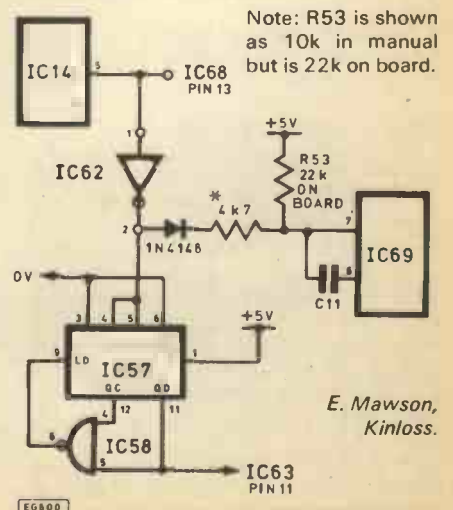

DISASSEMBLED LISTING

0228	A90D	LDA	#\$0D	0288	98	TYA		02DB	9D0702	STA	\$0207, X
022A	208202	JSR	\$0282	0289	48	PHA		02DE	CA	DEX	
022D	207AFF	JSR	\$FF7A	028A	AD0202	LDA	\$0202	02DF	10F7	BPL	\$02D8
0230	A92E	LDA	#\$2E	028D	F033	BEQ	\$02C2	02E1	BE5003	LDX	\$0350, Y
0232	207B02	JSR	\$027B	028F	AC0602	LDY	\$0206	02E4	A920	LDA	#\$20
0235	A5F8	LDA	\$F8	0292	F008	BEQ	\$029C	02E6	A02F	LDY	#\$2F
0237	206902	JSR	\$0269	0294	A240	LDX	#\$40	02E8	EA	NOP	
023A	A5F7	LDA	\$F7	0296	CA	DEX		02E9	C020	CPY	#\$20
023C	206902	JSR	\$0269	0297	D0FD	BNE	\$0296	02EB	3001	BMI	\$02EE
023F	A92F	LDA	#\$2F	0299	88	DEY		02ED	0A	ASL	A
0241	207B02	JSR	\$027B	029A	D0F8	BNE	\$0294	02EE	8D0802	STA	\$0208
0244	A200	LDX	#\$00	029C	C90A	CMP	#\$0A	02F1	A000	LDY	#\$00
0246	A1F7	LDA	(\$F7, X)	029E	F02B	BEQ	\$02CB	02F3	200702	JSR	\$0207
0248	206902	JSR	\$0269	02A0	C90D	CMP	#\$0D	02F6	D0FB	BNE	\$02F3
				02A2	D006	BNE	\$02AA				
024B	A90D	LDA	#\$0D	02A4	202A03	JSR	\$032A	02F8	EE0902	INC	\$0209
024D	20B1FC	JSR	\$FCB1	02A7	4CC202	JMP	\$02C2	02FB	EE0C02	INC	\$020C
0250	A920	LDA	#\$20	02AA	8D0102	STA	\$0201	02FE	EC0902	CPX	\$0209
0252	208202	JSR	\$0282	02AD	201703	JSR	\$0317	0301	D0F0	BNE	\$02F3
0255	E6F7	INC	\$F7	02B0	EE0002	INC	\$0200	0303	200702	JSR	\$0207
0257	D002	BNE	\$025B	02B3	A92F	LDA	#\$2F	0306	CC0202	CPY	\$0202
0259	E6F8	INC	\$F8	02B5	EA	NOP		0309	D0F8	BNE	\$0303
025B	38	SEC		02B6	18	CLC		030B	A920	LDA	#\$20
025C	A5F9	LDA	\$F9	02B7	69CD	ADC	#\$CD	030D	200A02	JSR	\$020A
025E	E5F7	SBC	\$F7	02B9	EA	NOP		0310	CE0802	DEC	\$0208
0260	A5FA	LDA	\$FA	02BA	CD0002	CMP	\$0200	0313	D0F8	BNE	\$030D
0262	E5F8	SBC	\$F8	02BD	3009	BMI	\$02C8	0315	F0A8	BEQ	\$02BF
0264	10DE	BPL	\$0244	02BF	203303	JSR	\$0333	0317	AE0002	LDX	\$0200
0266	4C30FE	JMP	\$FE30					031A	AD0102	LDA	\$0201
				02C2	68	PLA					
0269	85FC	STA	\$FC	02C3	A8	TAY		031D	A000	LDY	#\$00
026B	20ACFE	JSR	\$FEAC	02C4	68	PLA		031F	EA	NOP	
026E	AD64D1	LDA	\$D164	02C5	AA	TAX		0320	D004	BNE	\$0326
0271	207B02	JSR	\$027B	02C6	68	PLA		0322	9D00D3	STA	\$D300, X
0274	AD65D1	LDA	\$D165	02C7	60	RTS		0325	60	RTS	
0277	207B02	JSR	\$027B	02C8	202D03	JSR	\$032D	0326	9D00D7	STA	\$D700, X
027A	60	RTS		02CB	201703	JSR	\$0317	0329	60	RTS	
027B	20B1FC	JSR	\$FCB1	02CE	A9CD	LDA	#\$CD	032A	201703	JSR	\$0317
027E	208202	JSR	\$0282	02D0	EA	NOP		032D	A9CD	LDA	#\$CD
0281	60	RTS		02D1	29E0	AND	#\$E0	032F	EA	NOP	
0282	8D0202	STA	\$0202	02D3	8D0202	STA	\$0202	0330	8D0002	STA	\$0200
0285	48	PHA		02D6	A207	LDX	#\$07	0333	AE0002	LDX	\$0200
0286	8A	TXA		02D8	BD4803	LDA	\$0348, X	0336	BD00D3	LDA	\$D300, X
0287	48	PHA						0339	A000	LDY	#\$00

HEX DUMP OF HEX DUMP

	8	9	A	B	C	D	E	F	0	1	2	3	4	5	6	7
0228	A9	0D	20	82	02	20	7A	FF	A9	2E	20	7B	02	A5	F8	20
0238	69	02	A5	F7	20	69	02	A9	2F	20	7B	02	A2	00	A1	F7
0248	20	69	02	A9	0D	20	B1	FC	A9	20	20	82	02	E6	F7	D0
0258	02	E6	F8	38	A5	F9	E5	F7	A5	FA	E5	F8	10	DE	4C	30
0268	FE	85	FC	20	AC	FE	AD	64	D1	20	7B	02	AD	65	D1	20
0278	7B	02	60	20	B1	FC	20	82	02	60	8D	02	02	48	8A	48
0288	98	48	AD	02	02	F0	33	AC	06	02	F0	08	A2	40	CA	D0
0298	FD	88	D0	F8	C9	0A	F0	2B	C9	0D	D0	06	20	2A	03	4C
02A8	C2	02	8D	01	02	20	17	03	EE	00	02	A9	2F	EA	18	69
02B8	CD	EA	CD	00	02	30	09	20	33	03	68	A8	68	AA	68	60
02C8	20	2D	03	20	17	03	A9	CD	EA	29	E0	8D	02	02	A2	07
02D8	BD	48	03	9D	07	02	CA	10	F7	BE	50	03	A9	20	A0	2F
02E8	EA	C0	20	30	01	0A	8D	08	02	A0	00	20	07	02	D0	FB
02F8	EE	09	02	EE	0C	0A	EC	09	02	D0	F0	20	07	02	CC	02
0308	02	D0	F8	A9	20	20	0A	02	CE	08	02	D0	F8	F0	A8	AE
0318	00	02	AD	01	02	A0	00	EA	D0	04	9D	00	D3	60	9D	00
0328	D7	60	20	17	03	A9	CD	EA	8D	00	02	AE	00	02	BD	00
0338	D3	A0	00	EA	F0	03	BD	00	D7	8D	01	02	A9	9A	D0	D5
0348	B9	00	D0	99	00	D0	C8	60	D3							

(After entering manually first time, the program can save itself to cassette tape, directly)

**SAVE/HEX
DUMP
PROGRAM**

GRAPHICS MANIPULATION

Sir—Although the Compukit has a quite extensive graphics set, it is difficult to use them to their full potential. This is because a) there is no graphic documentation supplied with the machine and b) the graphics are not directly accessible from the keyboard. The program, Graphics-Aid, described below, overcomes both these problems and is a very useful tool for producing good graphic displays.

In use, the graphics section of the character set is displayed as the top half of the screen. The bottom half is clear and is used as the display area. The required graphic is selected by moving the top cursor over it. The bottom cursor is moved into position, and then by pressing the space bar the graphic character is deposited in that position. The bottom cursor is moved using the keys U, D, L and R (Up, Down, Left and Right) and the top using SHIFTED U, D, L and R.

RUB-OUT deletes the character under the bottom cursor (for correcting).

SHIFT ' ' restarts program (used as a clear screen function).

RETURN causes both cursors to flash revealing characters under them. Mode exited by pressing SHIFT.

SHIFT '+' (ie '+') this causes the machine to scan the display area with a visible cursor and when it encounters a character, its value along with its position relative to the original cursor is displayed: press any key to continue on to the next character. This function is very useful since many small displays (eg cars, spaceships etc) are poked into position relative to one pointer, so by setting the cursor to the centre of the display and using this function, it is possible to produce a working system quickly and easily.

10 REM GRAPHICS AID: BY ADL

```
20 FOR I=128TO242
30 IF(I+10)/23=INT((I+10)/23)
THENPRINT:A=(A+1) AND I
40 IFA=1 THENPRINTCHRS(I)
";GOTO60
50 PRINT" CHRS(I);
60 NEXT:PRINT
70 FORI=0TO22:PRINT"
";POKE54220+POS(8),I:NEXT
80 FORI=1TO10:PRINT:NEXT
100 CI=54221:C2=53261:POKE11,0:
POKE12,253:S=32
102 GOTO350
110 POKECI,154:POKEC2-1,18:
POKEC2+1,22
120 X=USR(X):
AS=CHRS(PEEK(531))
130 IFAS="n" THENRUN
140 D=0:IFPEEK(57100)
<254 THEN230
150 IFAS="U" THEND=-64
160 IFAS="D" THEND=64
170 IFAS="L" THEND=-1
180 IFAS="R" THEND=1
190 IFAS=" " THENS=PEEK(C2):
GOTO120
192 IFPEEK(531)=13 THEN350
```

```
195 IFPEEK(531)=28 THENS=32:
GOTO120
200 IFD=0 THEN120
210 X=C1+D:IFX>54269 ORX
<53645 THEN120
220 POKECI,S:S=PEEK(X):CI=X:
GOTO110
230 IFAS="e" THEND=-65
240 IFAS="T" THEND=65
250 IFAS=" " THEND=-2
260 IFAS="b" THEND=2
265 IFAS="+" THEN300
270 IFD=0 THEN120
280 X=C2+D:IFX<53261 ORX>53626
THEN120
290 POKEC2-1,32:POKEC2+1,32:
C2=X:GOTO110
300 POKECI,S:D=32:FORI=
53645TO54269:POKEI-1,D:D=
PEEK(I):POKEI,154
310 IFD=32 THEN340
320 PRINTD,I-C1;:POKE54221+
POS(8),32:X=USR(X)
330 PRINTCHRS(13)TAB(20)
CHRS(13);
340 NEXT:POKEI-1,32:
POKE54221,32:GOTO110
350 POKEC2-1,32:POKEC2+1,32:
POKECI,S
360 FORI=1TO500:NEXT
370 POKEC2-1,18:POKEC2+1,22:
POKECI,154
380 FORI=1TO500:NEXT
390 IFPEEK(57100)=254 THEN350
400 GOTO120
```

Note: Lines 40 to 70 there are two spaces between the quotes. Lines 50 & 190 there is one space between the quotes.

A. D. Love,
Swansea.

INDEXED SOFTWARE

Sir—Here is an easy way of loading only one program from several filed on one cassette, which works on the UK101 and presumably the Superboard. When SAVE-ing start each program with:

```
1 A=X
9 A=O: poke 515,0
```

X is the sequential number of the program.

At the end of the program, while the tape is still running, type RUN (Return). Repeat this routine for each program.

When LOADING first type in these two program lines:

```
5 IF A=Y THEN NEW
6 END
```

Where Y is the number of the wanted program minus one.

Then LOAD the tape in the usual way. Each program will LOAD and then RUN. Until the program before the required one is reached, line 5 will do nothing and line 6 will stop the current program so that LOADING can continue.

When the penultimate program RUNs, line 5 promptly erases it, any surviving line of previous programs, and itself. The wanted program then LOADs and RUNs. Line 9

puts A=0 in case A is a variable in the program and POKE 515,0 returns the computer to normal operation from LOAD. If you do not want any particular program actually to run, make line 9 STOP.

If the wanted program is the first on the cassette there is no need to enter lines 5 and 6. Just LOAD in the usual way. If there are to be only two programs on the cassette, do not bother with A=X, A=0 and lines 5 and 6. To LOAD the second program, simply type 5 NEW before LOADING.

A. H. Whitfield
Maidenhead

SIMPLE DECODE

Sir—There is a very simple way of address decoding for the UK101 which can be used to control up to 8 external devices, and which seems to have escaped attention.

IC17 pin 11 is selected (active low) when the address is A15.....A0 = 1111 XX01 XXXX XXXX (X = don't care). To make use of this, a wire can be taken from this pin to one of the unused pins of the 40-pin expansion socket (pin 29 for instance, the earth connection having been cut). On the external decoding board, this is connected to pin 5 of a 74LS138 3-to-8 line decoder, pins 1,2,3,4 and 6 being respectively connected to A7, A10, A11, 0V and +5V.

Y0 (pin 15) is then selected when the address is F100 to F17F (61696 to 61823), Y1 (pin 14) for F180 to F1FF (61824 to 61951) etc.

W. Gough,
Cardiff.

A SMART PROBLEM

Sir—I have built a UK101 and a Smart 2 8K expansion board from kits. The UK101 works well; it has the new monitor ROM and 8K on board.

On powering up the expansion board in the manner suggested in its instructions, a fault became evident after inserting ic's WNM and V. The UK101 would reset from its random screen pattern to show "select M, C or W", etc. but the cursor would not flash and several symbols (CHR 27) were present on the screen. These were the same at every switch on.

I have examined the board for soldering faults, both visually and with a meter. There are none that I can find. I have swapped all of the ic's around where possible. The fault is still present when the 8T28's on the UK101 are removed, these chips working OK when substituted elsewhere. If the expansion board is left plugged into J1 on the UK101, but not powered up, the computer works normally with its own 8K.

I presume the fault is on the expansion board, but I am not sure. Can anyone give me any advice on what to check? Or even, where to take it to have it checked?

I am not an electronics man, but I do have access to a scope and various meters, etc. Any help would be greatly appreciated.

Roger Cannon,
Basingstoke.

BATTERIES NiCAD rechargeable 1.2v vented to ICEL 1001, 4 year life, B.C.E. S&T. Please indicate if buttons or tabs required. ITEM 1 (AA) 1/2 AH 70p, 2 (C) £1.10, 3 (D) 4AH £1.60.

CABLE PVC coated Grey by BICC. Filotex, etc. 13 Audio screened overall 2 core 7/2mm per core, 15p mtr., 14 Conn. wire 16/2mm x 15' 1 each in Black, Red, Yellow, 5p Lot. 15 Mains 3-core 3 amp 12p mtr., 16 TV Download 202. 12p mtr.

CAPACITORS CERAMIC Auto Insertion
TOL 10% 100v IN PFS PCM 5mm

3p	4p	4p	5p
10	21	47	25 150
18	15	22	26 220
19	23	82	27 330
20	33	24	28 470
			32 3K3

ELECTROLYTIC TOL -10% +50% IN MFDS
AXIAL 63V TUBULAR

PLUG IN	LEADS
7.5mm	PCM 5mm

All at 8p	mm	43 2.2/63v	11x5 5p
33	13x6	44 4.7/63v	11x6 7p
34	2.2	13x6	45 10/63v
35	3.3	13x6	46 22/35v
36	4.7	13x6	47 47/35v
37	6.8	13x7	48 100/25v
			50 470/6v3
			20x10 11p

By ELNA, MULLARD RUBYCON, PLESSEY ETC.
42 220 31x13 51 1000/100v S/E tags 70p

CONNECTORS
90 DIN plug 5 pin 180deg. 10p
91 DIN chassis SXT 5-pin 180deg. 15p
92 Jack plug stereo 1/2" 15p
93 Jack chassis SKT Stereo 1/2" 39p
94 Mains plug rubber white 3 pin 13a sq pin 55p

DIODES BY IIT, MULL, SESCOSEM, TEXAS, etc. All coded.

95 AAZ15	250ma 100v 9p	105 OA47	30ma 30v 5p	115 IN4148	75ma 75v 13p
96 BAX13	75ma 150v 2p	106 OA90	10ma 30v 5p	116 IN4151	150ma 75v 2p
97 BAX16	200ma 150v 3p	107 OA91	50ma 115v 7p	117 IN5297	1.5A 200v 7p
98 BAY71	75ma 35v 9p	108 RPE108	1A 100v 3p	118 IN5404	3A 400v 11p
99 BY127	2A 1250v 12p	109 S2BN71	70A 200v 90p	119 IN5407	3A 800v 13p
100 BY206	400ma 350v 19p	110 IAV30	10ma 3KV 9p	120 IS44	75ma 40v 3p
101 BY255	3A 1K3v 9p	111 IN914	75ma 100v 3p		
102 BYX10	360ma 1K6v 30p	112 IN916	75ma 100v 3p		
103 BYX5/600	1A2 500v 20p	113 IN4002	1A 100v 23p		
104 CV8790	200ma 150v 5p	114 IN4004	1A 400v 33p		

DIODES ZENER BY MOTOROLA MULLARD, SESCOSEM, etc.

ITEM	130	131	132	133	134	135	136	137	138	139	140	141
	3V3	3V6	3V9	4V3	4V7	5V1	5V6	6V2	6V8	7V5	8V2	9V1
142	143	144	145	146	147	148	149	150	151	152	153	154
10x11	11v	12v	13v	15v	16v	18v	20v	22v	24v	27v	30v	33v

FUSES OC 20mm x 5mm OB 183 100ma 4p 164 500ma 4p 165 1A 4p 166 2A 4p CLIPS PCB to suit 167 1p

ICs DIL PINNING (-)

168 301181	170 324141	173 381114	176 565114	179 710141	182 747114	185 3046141	188 3814118
24	37p	90p	97p	55p	3p	75p	192
169 308181	171 346114	174 555181	177 567181	180 725181	183 1310114	186 3080181	189 13600181
45p	60p	24p	192	95p	75p	95p	

ICs 40 -- N BUFF MROLA NATIONAL RCA

ITEM	15p	34p	45p	74p	£1.14
196	216	138	240	01	239
197	01	217	139	241	02
198	02	218	159	242	06
199	03	219	157	243	07
200	04	220	180	244	08
201	05	221	161	245	09
202	08	222	163	246	10
203	09	223	164	247	11
204	10	224	174	248	12
205	11	225	193	249	13
206	20	226	221	250	14
207	27	227	240	251	15
208	32	228	244	252	16
209	74	229	245	253	17
210	86	230	251	254	18
211	90	231	259	255	19
212	93	232	283	256	20
213	109	233	367	257	21
214	122	234	347	258	22
215	123	235	393	259	23

ICs 40 -- N BUFF MROLA NATIONAL RCA

ITEM	239	240	241	242	243	244	245	246	247	248	249	250	251	252	253	254	255	256	257	258	259	260	261	262	263	264	265	266	267	268	269
	270	271	272	273	274	275	276	277	278	279	280	281	282	283	284	285	286	287	288	289	290	291	292	293	294	295	296	297	298	299	300

Crison Components Ltd., 101 St. Leonards Road, Windsor, Berks. SL4 3BZ

ORDER FORM CUT ALONG DOTTED LINE AND FOLD
PRICES FIRM UNTIL 30.12.81

NAME _____
ADDRESS _____
Credit 60 days to companies giving two trade refs. Itemised invoice included with every consignment.
Pay CASH WITH ORDER £ _____
Carriage is free.
VAT 15% extra UK Only £ _____ **TOTAL £** _____
Quality: Alternatives are not supplied without authorisation with the exception of resistors which may be supplied as 1/2W. Components proving faulty shall have double their value or alternatively twice the quantity refunded.

BRIDGES ITEM 5 BY281-400 25A £3
6 KBPC10 10A £2
7 MDA100 1.5A 32p
8 W005 1A 18p
9 W02 1A 20p
10 W04 1A 24p
11 55B40 5A £2
12 10DB1A 1.8A 28p

POLYESTER PLUG IN RECT BOX STYLE TOL 10% BY EXOV MULL PLESSEY ROEDSTEIN SIEMENS

All at 4p	PCM	All at 6p	PCM
52 .001400v	10	62 .22/250v	15
53 .0022/400v	10	63 .33/100v	15
54 .0033/400v	10	64 .47/250v	22
55 .0047/400v	10	65 .68/100v	15
56 .01/630v	10	66 .10/100v	15
57 .02/250v	10	67 All at 12p	
58 .033/250v	10	68 1.5/100v	22
59 .047/100v	10	69 2.2/100v	22
60 .068/100v	10	70 All at 18p	
61 .1/250v	10	69 3.3/100v	22
		70 4.7/100v	27

POLYESTER AXIAL STYLE TOL 10% IN MFDS

All at 9p	All at 11p
71 .1/160v M312	76 1/250v MKT
72 .22/400v M312	75 1/250v MKT
73 .33/160v KT1853	74 .47/250v MKT
74 .47/250v MKT	75 .68/400v MKT1813

TANTALUMS - BEAD * SOLIDS!

Val Tol V	9p*	84	85	86	87	88	89	90
77 .1	20	35	9p*	10	10	10	30p*	
78 .1	20	35	9p*	10	10	10	40p*	
79 .1	20	35	9p*	10	10	10	35p*	
80 .1	20	35	9p*	10	10	10	20p*	
81 .2	20	35	9p*	10	10	10	5p*	
82 .3	20	35	9p*	10	10	10	64p*	
83 .4	7	10	25	12p*			89	220

LEDS 125" TIL 209C SERIES
155 GR 13p 156 RED 9p 157 YEL 15p
2" TIL 220 SERIES
158 GR 12p 159 RED 10p 160 YEL 14p

POTS Cermet 20 turn 1/2" rect. plug in 358 50R 70p. 359 100R 60p. 360 500R 60p. 361 1K 55p. 362 10K 55p. 363 25K 55p.
Cermet Horiz. round plug in 364 50R 90H 9p. 305 10K TM10K 11p. 366 100K TM10K 11p.

RESISTORS
E12 IN OHMS 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82.
ITEM 370 Carbon Film 1/2W5% 9x3mm 250v 10R-1 MEG 1p
E12 377 Metal Film 1/2W2% 10x3mm 350v 10R 680K 3p
By ElectroSil/Welwyn. When ordering resistors state item no. qty. and resistance value. *Types are mixed to make sorting easy.

RESISTORS MISC Minimum 50

per value	10% 4W	208-5	2p	820R	2% 1W	TR6	4p
1R8	5% 1W	PRO5	1p	1K	5% 1W	MR5	3p
3R3	5% 1W	RC32GF	2p	2K4	5% 1W	MR6	4p
4R7	5% 1W	UPM075	1p	3K3	10% 2W	RC42GF	2p
5R6	5% 1W	OC30	3p	4K3	5% 4W	MR5	3p
8R2	5% 1W	PRO5	1p	4K3	5% 1W	UPM100	3p
11R	5% 1W	OC30	4p	4K7	5% 1W	MR6	3p
15R	5% 1W	OC338	6p	4K7	10% 5W	208-0	6p
22R	5% 1W	UPM100	3p	6K2	2% 1W	MR5	3p
22R	5% 2W	118-0	2p	7K5	2% 1W	TR4	3p
36R	5% 1W	18T1	1p	9K1	2% 1W	CF1	3p
47R	10% 5W	208-0	6p	10K	5% 1W	MR6	3p
56R	5% 4W	292	5p	10K	2% 1W	TR6	4p
100R	2% 1W	TR6	5p	11K	5% 1W	MR4	3p
120R	10% 2W	MR	2p	15K	5% 5W	294	2p
120R	10% 4W	292	3p	22K	5% 4W	FA74	3p
150R	10% 4W	OC330	3p	30K	2% 1W	MR5	3p
160R	5% 1W	CR25	2p	56K	5% 1W	CR16	3p
180R	5% 1W	MR6	4p	91K	5% 1W	TR5	3p
220R	5% 1W	TR6	3p	150K	5% 1W	MR5	3p
220R	5% 4W	206	3p	180K	5% 1W	PRO5	1p
270R	10% 2W	202	2p	1M5	5% 1W	VR37	1p
430R	2% 1W	MR4	3p	30M	5% 1W	CF1	2p
430R	2% 1W	TR5	2p				
470R	5% 1W	UPM100	1p				
620R	2% 1W	TR4	1p				
750R	1% 1W	TR4	1p				

SWITCHES
386 Push button PCB mtg Pins 4mm apart space 1/2" make/break 250v 19p
387 Rocker panel mtg fits 1 1/2" x 1 1/2" hole on/off 15p
388 Toggle panel mtg fits 10mm hole on/off 3A 250v chrome 19p
389 Micro single button 1A Burgess. GVCSF 19p

TRANSISTORS

AC107	19p	BC183B	6p	BD135	22p	BUY87	£1.35	2N1309	89p
AC127	19p	BC183L	6p	BD136	22p	GET111	19p	2N1613	19p
AC128	25p	BC184	9p	BD139	59p	ME4104	19p	2N1711	19p
AC141B	19p	BC184B	6p	BD176	29p	MJ2501	£1.09	2N1890	29p
AC142	19p	BC184BL	6p	BD232	29p	MJ3001	£1.09	2N1893	29p
AC153	11p	BC207	9p	BD236	29p	MJE340	30p	2N2218	19p
AC176	25p	BC212	6p	BD238	29p	MJE520	42p	2N2219	19p
AC187	25p	BC212B	6p	BD239A	6p	MPSA11	21p	2N2219A	19p
AC188	19p	BC213	6p	BD240A	33p	MPSA42	12p	2N2221	19p
AC177	59p	BC213A	6p	BD241A	30p	MPSA43	12p	2N2222	19p
AC189	59p	BC213B	6p	BD242A	30p	MPSA54	21p	2N2222A	19p
AC191	59p	BC213C	6p	BD246A	54p	MPS6534	42p	2N2368	16p
AD149	69p	BC214B	6p	BD2537	33p	MPSU10	39p	2N2369A	16p
AD161	39p	BC214BL	6p	BD2538	33p	OC28	89p	2N2613	29p
AD162	39p	BC237	9p	BD675A	49p	OC45	29p	2N2905	19p
AF127	27p	BC237A	9p	BDY55	89p	OC71	21p	2N2905	19p
AF139	39p	BC237B	9p	BF167	19p	OC75	19p	2N2906	19p
ASV27	49p	BC238B	9p	BF179	25p	OC76	19p	2N2907A	19p

The WORLD of RADIO & ELECTRONICS

AMBIT INTERNATIONAL



CONCISE PARTS CATALOGUE


OUT NOW!

AMBIT'S NEW CATALOGUE

In an attempt to collate and organize our burgeoning ranges of 'stock' components (now over 7000 line items), we have at last produced a 'concise' 80 page parts catalogue to supplement the popular 'Tecknowledgey' series of 'wordy' applications catalogues, which now lists a wide range of basic components - as well as our unique RF and Communications components. The *World of Radio and Electronics* contains everything the informed electronics user needs, at prices which we guarantee will match the lowest on the market for equivalent product.

Prices appear on the page alongside the part numbers, and the catalogue is now updated quarterly - available either direct from here (60p all inc) or at most newsagents and bookstalls where you can find electronics publications. So as well as all the 'run-of-mill' items like resistor, capacitors, hardware, solder etc - you now have the first genuinely complete parts source for the radio, communication, electronics, computer user.

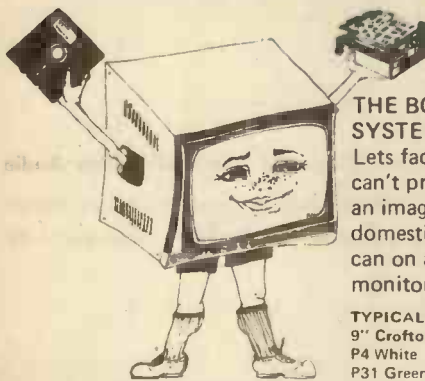Ambit International
200, North Service Road,
Brentwood,
Essex CM14 4SG



THE BODY OF ANY SYSTEM

Lets face it - you can't produce as crisp an image on a domestic T.V. as you can on a Crofton monitor.

TYPICALLY
9" Crofton Monitors
P4 White £64.97
P31 Green £77.62

These Monitor prices are dependant upon Sterling/Dollar conversion rates. Phone us for up to date prices.

SHUGART FLOPPY DISK DRIVES

No case, No Power Supply		
SA 400	5 1/4" S.S.S.D.	£149.05
SA 450	5 1/4" D.S.S.D.	£283.31
SA 800	8" S.S.S.D.	£340.52

FLOPPY DISKS - BOXES OF TEN

Single sided	35/40 Track		£ 26.45
Double sided	35/40 Track	5 1/4"	£ 37.95
Single sided	77 Track		£ 41.40
Double sided	77 Track	5 1/4"	£ 47.15
Single sided		8"	£ 40.25

IKEGAMI 12" MONITORS

P 4 White	£171.50
P31 Green	£184.97

2/3" FULLY INTERLACED C.C.T.V. CAMERAS £149.00

ALL THE ABOVE PRICES INCLUDE V.A.T. AND CARRIAGE



ALL MAJOR CREDIT CARDS
ACCEPTED - Small surcharge



CROFTON ELECTRONICS LTD

35 Grosvenor Road, Twickenham, Middx TW1 4AD
01-891 1923/1513

RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS



- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASED WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture. Tested & fully guaranteed. Ex-stock delivery



FREE
RE-CHARGE SERVICE
AFTER PURCHASE

£6.95 INC VAT
Post & Pack 60p

Ideal for the experimenter
COMPLETE WITH DATA

HENRY'S

404 EDGWARE ROAD, LONDON W2 1ED

PARNDON ELECTRONICS LTD.

Dept. No. 21 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.

£1.00 per hundred mixed. (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)

Special stock pack 60 values, 10 off each £5.50

DIODES: IN4148 3p each. Min order quantity - 15 items
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each.



DIL SOCKETS: High quality, low profile sockets.

8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
MIN. ORDER - UK. £1 00. OVERSEAS £5 - CASH WITH ORDER PLEASE

PANTEC INTRODUCES THE NEW MAJOR 20K

An outstanding new entry to the world of Electronic Servicing

**FULL PROTECTION
NO MORE
COSTLY REPAIR
CHARGES**



**VALUE FOR MONEY
ONLY £28.50 + VAT
incl. of P & P in UK**

- * 45 Ranges
- * High Accuracy: 20kΩ/VDC
- * Full Protection: Mains across resistance ranges? no problem just replace the quick-blow fuse.
- * Anti-parallax mirror.
- * Shock resistant ABS Case.
- * Optional high voltage probe for TV - Radio servicing.
- * Supplied with shock proof plastic case, test leads, spare fuse and multilingual instruction manual.

DC VOLTS: 0.15-1.5-5-15-50-150-500-1500V
 AC VOLTS: 7.5-25-75-250-750-1500V
 DC Current: 50μA-0.5-5-50mA-0.5-2.5A
 AC Current: 2.5-25-250 mA-2.5-12.5A
 Resistance: 0.5Ω to 2MΩ in 4 ranges.
 dB: -10 + 69
 Ballistic capacitance: 100-1000 μF-10-100mF

PANTEC Division of CARLO GAVAZZI (UK) LTD
 162/164 Upper Richmond Road London SW15 2SL
 Tel: 01-785 9022/5 Telex: 8952493
 Please send me further details on the
 new PANTEC MAJOR 20k.

NAME: _____
 ADDRESS: _____

ACORN COMPUTER announces the RGB PAL ENCODER

Acorn announce a reliable, high quality, off-the-shelf RGB-input PAL encoder with intercarrier sound.

High Quality Colour Graphics

The Encoder accepts Red, Green, Blue and synchronisation signals and converts them to a composite PAL colour video signal. This is then modulated onto a UHF carrier to produce an output on Channel 36 suitable for feeding the aerial socket of a standard domestic TV.

Standard System - Outstanding Features

The board is a short Eurocard operating from a single 5 volt supply and designed to fit a standard Eurocard rack. The board will also drive a monochrome TV to give a black and white picture with the intermediate colours appearing as different levels of grey.

The circuit includes a sound input, and the sound sub-carrier oscillator may be tuned to either 5½ MHz or 6.0 MHz. Separate presets are provided for accurate setting of the spot frequencies for the colour and sound sub-carriers.

Ideal for Prestel/Teletext Systems



For more information and price structure write to:
RGB/PAL Encoder Department,
Acorn Computers Ltd.,
4A Market Hill,
Cambridge, CB2 3NJ.



Just **50p** will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our listening lounge.
(Customer operated demonstration facilities)
- ★ Ample parking ★
- ★ Access Visa American Express accepted ★



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



TRANSFORMERS +VAT 15%

30 VOLT RANGE (Split Sec)
Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref.	Amps	Price	P&P
112	5	2.90	1.00
79	1	3.93	1.00
3	2	6.35	1.20
20	3	7.39	1.44
21	4	8.79	1.60
51	5	10.86	1.60
117	6	12.29	1.72
88	8	16.45	1.96
89	10	18.98	1.84
90	12	21.09	1.84
91	15	24.18	1.84
92	20	32.40	O.A.

UK Postage. Overseas extra.
Voltages stated are on full load
Continuous Ratings

60 VOLT RANGE (Split Sec)
Pri 120/240V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref.	Amps	Price	P&P
124	5	4.27	1.20
126	1	6.50	1.20
127	2	8.36	1.60
125	3	12.10	1.72
123	4	13.77	1.96
40	5	17.42	1.84
120	6	19.87	2.04
121	8	27.92	O.A.
122	10	32.51	O.A.
189	12	37.47	O.A.

50 VOLT RANGE (Split Sec Pri 120/240V)
Sec Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V.

Ref.	Amps	Price	P&P
102	5	3.75	1.20
103	1	4.57	1.20
104	2	7.88	1.44
105	3	9.42	1.60
106	4	12.22	1.72
107	6	16.37	1.84
118	8	22.29	2.20
119	10	27.48	O.A.
109	12	32.88	O.A.

MAINS ISOLATORS (SCREENED)
Pri 0-120V: 0-100-120V (120, 220, 240V) Sec 60-55-0-55-60 twice to give 55, 60, 110, 115, 120, 125, 175, 180, 220, 225, 230, 235, 240.

Ref.	VA	Price	P & P
*07	20	4.84	1.20
149	60	7.37	1.20
150	100	8.38	1.44
151	200	12.28	1.72
152	250	14.61	2.04
154	500	22.52	2.20
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	58.22	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-240V Sec 115 or 240V
State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 15V USA flat pin outlets

VA	Price	P & P	Ref
20	6.55	0.95	56V
75	8.50	1.20	64W
150	11.00	1.44	4W
250	13.39	1.44	69W
500	20.13	2.04	67W
1000	30.67	2.20	84W
2000	54.97	O.A.	95W

AUTO TRANSFORMERS
Voltages available: 105, 115, 190, 200, 210, 220, 230, 240, for step up and step down.

Ref.	VA (Watts)	£	P&P
113*	15	2.73	1.00
64	80	4.41	1.20
4	150	5.89	1.20
53	350	10.00	1.44
67	500	12.09	1.84
84	1000	20.64	2.20
93	1500	25.61	O.A.
95	2000	38.31	O.A.
73	3000	65.13	O.A.
80S	4000	84.55	O.A.
57S	5000	98.45	O.A.

*0, 115, 220, 240.

Constant Voltage Transformers (1%)
Clean mains to computers/peripherals

250 VA	£98.00
500 VA	£129.00
1000 VA	£149.00

Also I.C. "sensing pipes" for low mains voltage fluctuations.

Appointed Distributors of Galatruk stabilisers & Voltsafe cutouts.

15V CT Range (7.5V-0-7.5V)

Ref.	500 mA	2.30	0.60
172	1A	3.26	1.00
173	2A	3.95	1.00
174	3A	4.13	1.20
175	4A*	6.30	1.20

96/48/36V RANGE
Pri 120/240V

Amps	Ref.	Price	P&P
2	72v 36v	8.12	1.44
96v 48v	2	4.32	1.22
3	6	4.33	1.67
6	8	4.34	2.05
5	10	4.35	2.20
8	12	4.36	2.69
8	16	4.37	40.03

SCREENED MINIATURES

Ref	mA	Volts	£	P&P
238	200	3-0-3	2.83	0.50
212	1A, 1A	0-6-0-6	3.14	1.00
13	100	9-0-9	2.35	0.50
235	330, 330	0-9-0-9	2.19	0.60
207	500, 500	0-8-9-0-8-9	3.05	0.95
208	1A, 1A	0-8-9-0-8-9	3.88	1.20
236	200, 200	0-15-0-15	2.19	0.60
214	300, 300	0-20-0-20	3.08	1.00
221	700(DC)	20-12-0-12	20.75	1.00
206	1A, 1A	0-15-20	5.09	1.20
203	500, 500	0-15-27	4.39	1.20
204	1A, 1A	0-15-27	6.84	1.20
239	50	12-0-12	2.88	0.50
234	500	6-0-6	2.19	0.44

Split Bobbin Type. Pri 0-115, 0-115. Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V, or 12-0-12V or 15-0-15V.
1 amp (09) £2.06+98p. PP
2 amp (10) £4.11 + £1.10p PP +VAT.

OTHER PRODUCTS

AVO TEST METERS

AVO 8 MK5. Latest Model	£116.40
AVO 71 Electronics & TV Service	£45.40
AVO 73 Electronics	£63.90
AVO MM5 Minor	£40.50
AVO EM272 316KΩ/Volt input Z	£67.10
AVO DA116 L.C.D. Digital	£121.70
AVO DA211 L.C.D. Digital (Hand Held)	£57.00
AVO DA212 L.C.D. Digital	£74.00
Battery MEGGER BM7/500V	£65.30
Wee MEGGER hand crank	£97.20

Plus P&P £1.32 + VAT 15%
All Avos Meggers & accessories available.

Personal Attack Alarm
Emits ear deafening "SCREECH" warning tone. Lipstick size.
£3.45 P&P 30p.

EDUCATIONAL METERS (M. Coil)
0-10A, 0-30V. Freestanding large scale easily read meters with top screw terminals for quick connections. £4.50 P&P 65p +VAT. Size 75x75mm scale.

SPECIAL OFFER
25W Soldering Iron to BS Spec. £1.75 P&P 30p + VAT 15%.

ANTEX Soldering Irons CN240 15W & 25W £4.58 each. Safety Stand £1.75 P & P 5p each.
P.W. Purbeck oscilloscope transformer 250-0-250; 6-3V; 12-9V (author approved) £9.42 £1-04

Precision De-Solder Pumps - Spring loaded quick action button release for one hand working. Large £5.86 P&P 35p+VAT. Small £5.17 P&P 30p+VAT. Replacement tips Small 65p+VAT. Large 86p+VAT.

Telephones - Latest model 746, new, 2 tone grey £11.50 + VAT. Ivory £12.50 + VAT. P&P £1.20 + VAT.

METAL OXIDE RESISTORS £1 per 100 (Electrosil) TR4 5% 47Ω/75Ω/180Ω/360Ω/390Ω/430Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K3/1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K/110K/120K/130K/180K/220K/270K/300K P&P 50p + VAT.

100W Soldering Gun includes bulb for spot-on joints £5.39 + VAT.

PANEL METERS

43mm	43mm	82mm	78mm
0 50mA	6.20	0 50mA	6.70
0 500μA	5.95	0 500μA	6.70
0 1mA	5.95	0 1mA	6.70
0 30V	5.95	0 30V	6.70

BATTERY ELIMINATORS
Plugs into 13A socket 3, 6, 7-5, 9, 12V DC + 300 mA output £5.10 P&P 60p + VAT.
6, 7 x 5, 9v 300mA £4.60

BRIDGE RECTIFIERS
100V 25A £1.80 500V
100V 50A £2.20 PM7A6
200V 2A £0.52 12A
200V 4A £0.75 £3-75
400V 1A £0.25
400V 4A £0.98 P&P 20p
400V 6A £1.44 + VAT.

Cables, tools, transformer winding service. Send us your requirements.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

SEMICONDUCTOR DATA BOOK

11th Edition A M Ball

- Half a million sales since first publication
- 10,000 American, European and Japanese devices
- Alphanumeric listing of devices
- A completely revised edition

In this completely new and rewritten edition of Radio Valve and Semiconductor Data the devices are listed in alphanumeric order to simplify reference. It presents data on more than 10,000 semiconductor devices from the major American, European and Japanese manufacturers and there are separate sections devoted to resistors, FETs, UJTs, diodes, rectifiers, optical semiconductors, triacs and SCRs. Device outlines and pinouts are also included. This collection of data is essential for all designers and constructors of electronic equipment.

276 x 219 mm 184 pages Illustrated
0 408 00479 7 £5.50 Paperback

Write for full details of all our books — or in case of difficulty send cash with order to Patricia Davies, Marketing Manager at the address below.

Newnes Technical Books a division of Butterworths

(PE 9/81)

ORDER NOW from your local bookseller

NICKEL CADMIUM BATTERIES

AA (HP7) 0.5Ahr	SUB 'C' 1.2Ahr	'C' (HP11) 1.65Ahr	'C' (HP11) 2.0Ahr	'D' (HP2) 4.0Ahr	PP3 0.1Ahr
1-24	£0.85	£1.38	£1.89	£2.25	£3.79
25-49	£0.82	£1.28	£1.58	£2.10	£2.77
50-99	£0.80	£1.24	£1.52	£2.02	£2.67
100 up	£0.70	£1.15	£1.41	£1.87	£2.47

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are 'VENTED' devices suitable for fast charge.

CHARGERS - single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04
DUAL O/P CHARGER £5.72

TRANSFORMERS - as used in chargers, 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections £1.57 each.

Data and charging circuits free with orders over £10 otherwise 30p post.
P&P 10% if order less than £10, 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order.

Cheques, P.O.'s Mail Order to:-
SOLID STATE SECURITY,
Dept. (PE), Bradshaw Lane,
Parbold, Wigan, Lancs.
Telephone 02576-3018.

CELESTION



RICHARD ALLAN

WE SELL FANE, GOODMAN
High quality power speakers
12 in 50W 8 ohms
12 in 50W 16 ohms
12 in 80W 8 ohms
12 in 80W 16 ohms
15 in 150W 8 ohms
15 in 150W 16 ohms

PIEZO HORN TWEETERS
Up to 100 watts each. No over required. Flared Horn. Mid range. Flared Horn. In stock now. Large range of speakers, public address equipment, microphones, music, nam equipment. Heavy chromed Floor Stand £9.95
Boom Arm £8.50
Echo Chamber £59.95
Analogue Echo Chamber £69.95

CB Antenna & Accessories in stock now!!

CROSSOVERS

100W	8 ohm	2 way
100W	8 ohm	3 way
80W	8 ohm	4 way
60W	8 ohm	2 way

Stockists of leading makes of Disco Units & Lighting Equipment.

CITRONIC, FAL, TK, ICE, OPTIKINETICS, PLUTO.

Give your cabinets the professional finish.

Send 2 x 14p stamps for illustrated catalogue.

All prices include VAT at 15%. Mail Orders welcome.

MUSICRAFT
303 EDGWARE ROAD,
LONDON W.2, ENGLAND
TELEPHONE: 01-402 9729 / 01 402 2898

UK101/VIDEO GENIE/ SUPERBOARD

PRINTERS:::

The EPSON MX80

Friction and tractor feed printer with very high quality output, true lower case characters etc. We are able to offer these units at a very special price to members. Telephone now for further details of the printers and our special offer.

GRAPHICS::: Only £67.85 or £72.35 (ready built). A complete unit to plug into the UK101 or Superboard. Any display size or monitor, the PCB suits all systems. Design your own graphics, 3d diagrams, Hi res graphs and much more. Send now for complete details.

VIDEO GENIE & UK101:::

Sound Board. This ever popular kit (or ready built unit) is now available for the Video Genie. The only totally complete kit on the market. A1 leads, speaker amp and software supplied. Proper 40 pin to 40 pin Jumper, simply plug in and go. Only £40.20.

PERSONAL COMPUTER WORLD SHOW::: Come and see us at Stand T7 of the PCW show. All our products will be on show and we will be selling various kits etc at special Show prices.

All our prices INCLUDE VAT & P&P, User Group membership is still £4.60 per 6 months.

Callers by appointment only please.

COMPUTER USER AIDS

9 Moss Lane, Romford, Essex RM1 2QB.
Romford 64954.

HERE AT LAST!

The Beginners Guide To Programming By Adrian Waters

This booklet will provide you with simplified, easy to understand instruction on programming your computer. The booklet covers, BASIC, Machine Code Hardware and in greater detail PEEK, POKE USR(X) and Graphics. It also explains real time programs and games as well as a handful of simple hardware modifications.

This will shortly be followed by Intermediate and Advanced instruction booklets to cover every level of programming.

Learn and get the most from your Superboard or UK101 - details about availability and cost by telephone or post.

A REAL ALTERNATIVE TO DISC

Are you put off by the price of a disc system? Then perhaps our file handling & fast tape storage unit will be of interest. High speed storage of data and programs with complete computer control, absolute security with a really low error rate. Further details on request.



4 1/2 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £5.10. 50p P. & P.

MICROPHONES FOR TAPE RECORDERS

DM228R 200 ohm with 3-5 and 2-5mm Jack Plugs £1.70
DM229R 50K with 3-5 and 2-5mm Jack Plugs £2.25
DM18D 200 ohm with 5 and 3 pin Din Plugs £1.99
Postage on above microphones 17p



CARDIOID DYNAMIC MICROPHONE

Model UD-130 Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £8.02. 50p P. & P.

2in x 2in meters 500µA, £4.14. 17p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £4.00. 26p P. & P.

6V BUZZERS. 50mm diameter 30mm high, 52p. 15p. P. & P.

MULTI-METER

7 N 360TR
20,000 ohm/volt
RESISTANCE
RANGES
X1, X10, X1K,
X10K
£13.30
P.&P. 75p



LP30 LOW PASS FILTER

Cut off frequency 30MHz
£3.50 post 75p

SWR9-SWR & FS METER

£10.20 Post 75p

CX3 CO-AX SWITCH

For one transceiver to 3 aerials or 3 aerials to one transceiver.
150 watt £5.65 Post 75p

PL259 Plug 33p; Socket 33p; PL259/SO239 Angled Connector 70p; 1 watt dummy lead 95p; 2m Rubber Neck Aerial with PL259 Plug £3.30. POST ON ABOVE ITEMS 14p.

All above prices include V.A.T. Send 50p for new 1980 fully illustrated catalogue, S.A.E. with all enquiries. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, T.V. Electronics Technicians
Radio Amateurs
Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
CCTV Engineering
Electronic Engineering & Maintenance
Computer Engineering and Programming
Radio, T.V. and Audio, Engineering & Servicing
Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE
BOOK

Post this coupon or 'phone today for free Electronics careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept 273L, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)



SELLING OR BUYING

A classified advertisement could solve your problem at very little cost.

RING LINDA
01-261 5846

RECEIVERS AND COMPONENTS

2716's (5V) MOTOROLA/JAPANESE. £4.40, 4 off £17.20. 2732's to order. 1N4148 50 £1.25, 100 £2.00. BC107/8/9 Sprague equivalents 8.0p. VAT is included. P&P 40p under £10.00. Wessex Trading, 17, Cripsted Lane, Winchester.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 Mfd. — 5p.
22 & 47—8p 100—7p. (50V—8p). 220—8p.
(50V—10p). 470—11p. (40V—16p). 1000/15V—15p.
1000/25V—18p. 1000/40V—35p.
Subminiature bead tantalum electrolytics.
0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.
2.2/35V, 4.7/25V—15p. 10/25V, 15/16V—20p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V—30p.
15/25V, 22/28V, 47/10V—35p. 47/16V—80p.
Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.
10% 390 pf. to 47 pf. to 4700 pf.—4p.
Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. £6 1500 pf. to 47000 pf.—2p.
Polystyrene E12 Series 63V. Horizontal Mtg.
10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.
Miniature Polyester 250V Vert. Mtg. E6 Series.
.01 to .068—4p. .1—5p. 15, 22—6p. 33, 47—10p.
.68—12p. 1.0—15p. 1.5—22p. 2.2—24p.
Mylar (Polyester) Film 100V. Vertical Mounting.
.001, .0022, .0047—3p. .01, .022—4p. .04, .05, 0.1—5p.
Miniature Film Resistors Highstab. E12 Ser. 5%.
0.125W mixed carbon/metal 10Q to 1MΩ—1p.
0.25W Carbon 1Q to 10MΩ (10% over 1MΩ)—1p.
(E24 Series av. in 1/4W C. Film 1Q to 5MΩ).
0.25W, 0.5W & 1.0W Metal Film 10Q to 2MΩ—2p.
1N4148—2p. 1N4002—4p. 1N4006—8p. 1N4007—7p.
8C107/8/9, 8C147/8/9, 8C157/8/9, BF195 & 7—10p.
8 Pin I.C.s. 741 Op. amp.—18p. 555 Timer—24p.
DIL Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.
LED's 3 & 5mm. Red—10p. Green & Yellow—14p.
Grommets for 3mm.—1 1/2p. 2 pc. holders 5mm.—2 1/2p.
20mm. Q.B. Fuses 1/25, .5, 1, 2, 3 & 5A—3p.
20mm. Anti Surge 100mA. to 50A—8p.
20mm. Fuseholders P.C. or Chassis Mtg.—8p.
Solid A1. knobs 15mm.—25p. 25mm.—35p. 30mm.—50p.
400mW Zener diodes E24 series 2V7 to 33V—5p.
Prices VAT inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

300 SMALL COMPONENTS, transistors, diodes £1.60. 7 lbs Assorted Components £3.95. 10 lbs £5.25. PCBs 11 1/2" x 8", 60p. 1 lb weight assorted 80p. Fibreglass 11" x 5" £1. 11" x 10" £1.80. Fourty 74 series ICs on panel £1.60. 500 capacitors £3.00. List 20p refundable. Post 50p. Optional insurance 20p. J.W.B. Radio, 2, Barnfield Crescent, Sale, Cheshire M33 1NL.

PRINTED CIRCUIT BOARDS designed. Realistic prices. Manufactured/delivered assembled or unassembled. Quick delivery on one-offs or multiples. Complete artwork/silk screening service. Enquiries to: Bental Designs, 66, Harwood Close, Arnold, Nottingham. Tel. Nottm. 202049.

T & J ELECTRONIC COMPONENTS — Quality components, competitive prices, catalogue 45p. 98 Burrow Road, Chigwell, Essex.

SMALL ADS

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £9.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

MY CATALOGUE contains thousands of surplus electrical and mechanical items. Price 40p or sent free with large tin of aerosol freezer price £1 plus 85p postage. J. A. Crew (PE) Spinney Lane, Aspley Guise, Milton Keynes.

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

COLOUR TV TUBES

Only the best. Two Year Guarantee. To fit most makes of TV. Supplied by mail order or delivered free Manchester area. 22" £38, 26" £39. Complete fitting and setting up in your home (Manchester area) only £20 or bring TV to me for fitting while you wait. 061 799 0854 24 hour answering service.

APOLLO ELEKTRONIKS

43 Clarke Crescent, Little Hulton, near Manchester.

PLEASE PHONE FIRST. MANY THANKS

BALLARD'S OF TUNBRIDGE WELLS have moved to 54, Grosvenor Road, no lists. S.A.E. all enquiries phone Tunbridge Wells 31803.

GET LOST. UK 101e 3D Maze. 16K, 32 lines CEGMON only. Animated demo. £5.00. Dave Henniker, 59 Moreuden Park Gardens, Edinburgh EH17 7LQ.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. Foresters (National Radio Supplies), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

BLACKPOOL AND THE FYLDE. For components come to Eteson Electronics, 15B Lower Green, Poulton-Le-Fylde. Tel. 885107. Mail order too — S.A.E. lists.

1920's ONWARD VALVES, wireless. SAE Sole Electronics, PE 37, Stanley Street, Ormskirk, Lancs. L39 2DH.

MZ80K NUMERIC KEYPAD and unshifted cursor controls — replaces graphics characters, epyr details. SAE Antronics, 1 Cairnhill Gdns, St Andrews KY16 8QY.

BOOKS AND PUBLICATIONS

DUT OF PRINT Book Service, 17, Fairwater Grove (E), Cardiff. Send SAE for details.

ANY SINGLE SERVICE SHEET £1 L.S.A.E. Thousands are different repair/service manuals/sheets in stock. Repair data your named T.V. £6 (with circuits £8). S.A.E. Newsletter, pricelists, quotations. AUS (PE), 76 Church Street, Larkhall, Lanarkshire. (0698 883334).

SOFTWARE

CARDBOARD COMPUTER. Learn Assembly Language Programming and Computer Architecture. £8.97 inc. VAT. Also Solar Cells, Science Kits, Energy Books, Stirling Engines, Space Blankets etc. Send 25p for lists. Edencombe Ltd., Dept. PM34, Nathans Road, North Wembley, Middlesex HA0 3RX.

UK 101/SUPERBOARD OWNERS

Do your string handling programs sometimes lock up? Does FRE(X) sometimes cause a crash? If so, then you need our genuine mask programmed BASIC 3 ROM with corrected Garbage Collection. Direct replacement — no mods. or soldering.

£7.50 incl. P&P and leaflet.

R. W. Stibbons,

3 Mansfield Drive, Hayes, Middx.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

EPRM PROGRAMMING SERVICE for 2716(5v) devices. £1 per 256 bytes. £1 per copy. P&P 50p. N. J. Tobin, 8 Kingsfield Road, Dane End, Nr Ware, Herts.

NEW IMPROVED CHARACTER set in Eprom for your UK 101/Superboard (Please state which). Includes double-density graphics, maths, electronic and gaming symbols for only £8.95 (+50p P&P). Reprogramming service available. J. O. Linton, 110 Duchy Road, Harrogate, HG1 2HB.

YOUR UK101 BASIC PROGRAM in EPROM. Switch on an run! Using 5V, 2716. SAE for details. 22A, Hyde Road, Mottram Hyde, Cheshire.

UK101 SOFTWARE ON TAPE

from the guy who wrote "Le Passe-Temps"

GALACTIC HITCHHIKER (8K). An adventure, all in machine code. A beauty! (£7.00)
SUPERTREK (8K). Sail boldly through the universe zapping moving Klingons in real time. Superb graphics. (£7.00)
STARTREK (8K). The old favourite, beautifully presented. (£6.00)
LUNAR LANDER. A real challenge. You won't get down in less than 3 hours. (£3.00)
HANGMAN. Excellent graphics. P.E. said so! (£3.00)
BASIC TUTOR (8x4K). The only way to learn — at the keyboard. (£12.00)
LE PASSE-TEMPS. YOU NEED this, if you haven't already got it. (£3.00)
These ORIGINAL PROGRAMS are compatible all 2K Monitors and are available for 16x48 and 32x48 displays (including enhanced Superboards).

HARDWARE

I am now sole UK distributor for the exciting new TADWA range of add-ons, designed specifically for the UK101/Superboard. These kits are complete in every way: fully socketed high quality PCB, all components, switches etc, plus preformed cable assembly for easy interconnection to J1, or out...
MOTHERBOARD SYSTEM. Now you can add on all those extras easily. Provides eight, yes EIGHT, fully buffered J1 type sockets. (£28.50)
8K STATIC RAM BOARD. (£47.25)
HI-SPEED CASSETTE INTERFACE. At last, a system that works. COMPLETELY RELIABLE 4000 band (8000 with reasonable cassette) plus software for named file handling. A delight to use. (£19.50). For software in EPROM, add £8.00
VIDEO ENHANCEMENT. Switch selectable 16x48 or 32x48 displays without butchering your computer. (£19.50). Monitor EPROMS re-blown to suit for 2.50
8K EPROM BOARD (£24.50). A 2K Extended Monitor is available in EPROM for £12.00 plus, coming soon, TOOLKIT in EPROM and BASIC V.
MONITOR BOARD. Plug into Monitor socket to provide switch selection of up to 4 EPROMS. (£11.70)
AVAILABLE SHORTLY: EPROM Programmer, PIA/Sound Board, Analogue Board and something rather nice on the graphics side...

All inclusive prices — absolutely no hidden extras. Please write or phone for further details:

A. KNIGHT (Dept. PE),
28 Simonside Walk,
Ormsby,
Cleveland,
Tel. (0642) 321266.

SERVICE SHEETS

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

**PLEASE MENTION
PRACTICAL ELECTRONICS
WHEN REPLYING TO
ADVERTISEMENTS**

EDUCATIONAL

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272L Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272L Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 272L Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CAREERS in Marine Electronics. Courses commencing September and January. Further details, the Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

**TELEVISION COMPUTER
RADIO &
RADAR SERVICING**

**2½ YEAR full-time Modular
Diploma course to include a high
percentage of practical work.**

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- MICROELECTRONICS & DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS
- RADIO & RADAR

Each of the above Modules are 13 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £1500 per year (i.e. £500 per Module).

Next session starts September 14th.

Prospectus from:

**LONDON ELECTRONICS
COLLEGE**

**Dept: AA, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721.**

MISCELLANEOUS

FREE CATALOGUE. Send 14 pence stamp to Logic Designs, 168 Cauldwell Hall Road, Ipswich IP4 5DB. Free 50 pence voucher with first 100 catalogues.

**THE SCIENTIFIC WIRE COMPANY
PO Box 30, London E.4. 01-531 1568.**

ENAMELLED COPPER WIRE				
SWG	1lb	8oz	4oz	2oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	5.90	3.40	2.39	2.00
48 to 49	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	6.50	3.75	2.20	1.40
TINNED COPPER WIRE				
14 to 30	3.85	2.36	1.34	0.90

Prices Incl P&P, VAT.

Orders under £2 please add 20p.
SAE for List of Copper/Resistance Wire. Dealer enquiries welcome.
Reg. Office, 22 Coningsby Gardens.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer – now greatly improved and very much faster. Aerosol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibreglass. Board approx. 1mm thick £1.70 sq. ft. Post/packing 75p. **WHITE HOUSE ELECTRONICS. P.O. BOX 19, Castle Drive, Penzance, Cornwall.**

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low £1.05. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. **BAZELLI (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.**

BURGLAR ALARM EQUIPMENT. Latest Discount Catalogue out now! Phone C.W.A.S. Alarm 0274 682674.

SENSATIONAL FREE OFFER. Buy a Casiotone VL-1 Electronic Musical Instrument and get a semi conditor pack absolutely free. Comprising 10 7400, 10-BC183L, 1-7805, worth £2.60. Send cheque/PO for £35.95 (no postage required) to—Micro Musical Ltd., Freepost, 37 Wood Lane, Coventry, CV7 9BR. Offer closes 31/10/81.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics).

NAME

ADDRESS

.....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager
PRACTICAL ELECTRONICS
Classified Advertisements Dept., Room 2337
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846
Rate:
28p per word, minimum 12 words. Box No. 60p extra.

MISCELLANEOUS CONTINUED

LEARN ELECTRONICS WITHOUT SOLDER



Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.

Send cheque or P.O. to:
Roden Products, Dep PE
High March, Daventry,
Northants, NN11 4QE.

£3.85 plus 40p p.&p. each

PARAPHYSICS JOURNAL (Russian Translations): Psychotronic Generators, Kirlianography, Gravity Lasers, Telekinesis. Details: SAE 4x9", Paralab, Downton, Wilts.

WRONG TIME?

MSF CLOCK is ALWAYS CORRECT - never gains or loses. SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also record BCD output for computer and audio to parallel and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000KHz range, GET THE RIGHT TIME, £62.80.

V.L.F. 7 EXPLORE 10-150KHz, Receiver £16.50.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so GET yours NOW.

CAMBRIDGE KITS
45 (FW) Old School Lane, Milton, Cambridge.

GRUNDIG STABILISED POWER SUPPLY 2 amp pushbutton selection 0-25 volt. Meter indicates voltage/current, overload protected, strong metal case £20 + £5.00. Also millivoltmeters, multimeters, isolation transformers, signal generators/tracers. All in working order. Ring 0391 841 631 (after 6pm) or S.A.E. to: A. Moore, 5, St. Joseph's Park, Ballycruttle, Downpatrick.

QUARTZ LOCKED ULTRASONIC ALARM

Detector and Control Unit - Type UAQ+P Features:- No alignment reqd. - No interaction between units. Kit inc: F/G, PCB, punched ABS box, all comp, inst. Single unit construction - PCB battery back up, 15 to 20 ft detection range, externally presettable, 20 sec delay on leaving; 10 sec delay on entry; 1 sec invalid movement delay; 2 min self cancelling alarm; latching panic button facility included.

240V AC UAQ+P Multitone Drive Kit **£18.65**
240V AC UAQ+P Multitone Drive & Relay Output Kit **£21.65**


Above kits built & tested = Kit Price Plus **£8.00**
Multitone Sounder 95dB ±1mtr, 9 Tone Options **£9.20**
Keyswitch in ABS box £5.95; 2 x NI-CAD Batteries **£9.50**

All prices inclusive. CWO UK. SAE for further details.

GJD ELECTRONICS
105 Harper Fold Road,
Radcliffe, Manchester M26 0RQ.

DIGITAL WATCH BATTERIES. Any sort £1.20 each + p.p. Send S.A.E. or 15p with number or old battery to: Dislec, 511 Fulbridge Road, Werrington, Peterborough.

DIGITAL WATCH BATTERY REPLACEMENT KIT




These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, also one doz. assort. push pieces, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send **£9.00** for complete kit and get into a fast growing business. Prompt despatch.

BOLSTER INSTRUMENT CO. (PE28)
11 Percy Avenue, Ashford, Middx. TW15 2PB.

CAR RADIO SERVICE SHEETS. S.A.E. 49, Westbourne Terrace, Reading RG3 2RP. 0734-53046.

SUPERB LOUDSPEAKER CABINETS built to your specification or choose from standard range. S.A.E. for leaflet M. G. Saville. 63 Upper Shelton Road, Marston, Moretayne, Beds.

RYDER ORGAN SYSTEM



The WW classical design for full-size keyboards, including couplers. Expanded range of p.c. boards & data available includes chorus, vibrato, combination stop control.

Reverberation. A new compact solid-state unit gives smooth natural sound. Demo cassette, on loan, deposit £1.50, refund £1.00. (Prices UK only).

HIYKON LTD. (P), Woodside Croft, Ladybridge Lane, Bolton BL1 5ED.

ELECTRONIC KITS. Largest range of kits in the U.K. Everything from stroboscopic lights to transmitters, at unbeatable prices. Send S.A.E. for free catalogue to: Eastling Electronics (Kits), 64B Hawthorn Road, Winton, Bournemouth.

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) **£2.00.** Large range of single sheets in stock at 43p per sheet.

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. 2 sheets negative paper, 2 sheets positive film (A4) **£2.10.** Photo-resist spray (200 ml) **£3.25** (p+p 55p). **Drafting Film (A4) 25p.** **Precision Grids (A4) 65p.**

20p stamp for lists and information. P&P 35p per order except where indicated.

Closed for holidays July 20th to August 15th

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE.

PRINTED CIRCUITS BOARDS. Glass fibre tinned and drilled Prototypes to batch runs. Quick turn-round, competitive prices. Send S.A.E. for quotations. R. D. Electronics, 12 Whiteoaks Road, Oadby, Leicester. 0533 716273.

PRACTICAL ELECTRONICS P.C.B.'s

Drilled, 1.5mm Glass fibre Fry's Roller Tinned

APR 81 Speech processor EP502	97p.	Intruder alarm EG513	£1.82
MAY 81 Digi Sounder EG518-20	set of two	Multimeter EC 21/2	£2.29
Thermometer EC 20	98p	JUNE 81 pH meter EC24	£1.49
Minute chimer	£2.10	Minitune EC25	£1.94

For full list and current pcb's send SAE. Pcb's also produced to customers own masters. Trade enquiries welcomed Write for quote. CWO Please Postage - add 35p postage and packing to complete order. Europe 70p.

PROTO DESIGN
14 Downham Road, Ramsden Heath, Billericay, Essex CM11 1PU. Telephone 0268-710722

SECONDHAND ELECTRONIC TEST EQUIPMENT including oscilloscopes, generators, PSU's. Norfab., Telephone Potter Heigham (069-27) 721.

Cabinet and Flightcase Fittings

Fretlocks, Coverings, Handles, Castors etc., Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilar Compression Drivers, AKG Mics, Celestion Speakers, ASS, Glassfibre Horns.

Send 30p Postal Order for illustrated catalogues to:-

ADAM HALL (P. E. SUPPLIES)
Unit G, Carlton Court, Gringoir Road, Southend-on-Sea, Essex SS2 5BZ.

CLEARING LABORATORY: scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

KORTING COLOUR GENERATOR Model 82512, completely overhauled by Decca. Perfect condition. £75.00. 01-886. 4057.

RECHARGEABLE BATTERIES

Private & Trade Enquiries Welcome
FULL RANGE AVAILABLE. SAE FOR LISTS. £1.45 for Booklet. Nickel Cadmium Power plus Catalogue. Write or call: Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764.
NEW SEALED LEAD RANGE AVAILABLE

ULTRASONIC TRANSDUCERS. £2.85 per pair + 25p P&P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

SEEN MY CAT? 5,000 odds and ends. Mechanical. Electrical. Cat Free. Whiston Dept. PRE, New Mills, Stockport.

PRE-PACKED. Screws, nuts, washers, solder tags, studding. Send for price list. A1 SALES (PE), P.O. Box 402, London SW6 6LU.

TUITION

PAY AS YOU LEARN, postal mathematics tuition. 23, St. Lukes Close, Middlestown, Wakefield.

FOR SALE

TELETEXT P.E./Marshall's project. Complete kit almost built cost £200 want £125 o.n.o. Telephone Scarborough (0723) 863564.

UK101 8K CASED plus Tape Recorder, 1-2 megahertz. 300-600 band. Cegmon with tool kit in EPROM. Much software and extras **£275.00** negotiable. Phone Stevenage 69612 after 6pm.

CADCOCAT: Components, Grabbags, Correspondence Courses, Kits, Equipment. Write: Cadco, 67A, Jalan Periasia, Johore Bahru, Malaysia.

HARTLEY DUAL TRACE OSCILLOSCOPE. Excellent condition £90. J. Price, Bridge House, St. Davids, Dyfed, SA62 6PD.

SUPER BUY Hilki 25W Soldering Iron £3.90 plus 30p P&P. Orders with cheque/P.O. McDonald, M.O. Dept. 72, Strawfrank Road, Carstairs Junction, Lanark ML11 8RE, Scotland.

P.E.s NOVEMBER 1964 - OCTOBER 1972. Complete (minus one). Offers? Buyer collects. Southampton (0703) 860360.

NEW BACK ISSUES OF 'PRACTICAL ELECTRONICS' available 90p. each Post Free. Cheque or uncrossed P/O returned if not in stock. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

WANTED

WE BUY SURPLUS electronic components, PCB's etc for cash. Tel. (0703) 785862.

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.


L&B ELECTRONIC TEL: 01
MODULES -689 4138

PROGRAMMABLE - 8

£114.90

P/P INS

£1.50

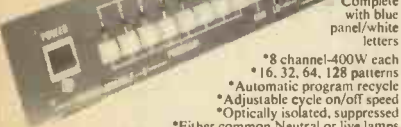

Complete with blue panel/white letters

- *8 channel-400W each
- *16, 32, 64, 128 patterns
- *Automatic program recycle
- *Adjustable cycle on/off speed
- *Optically isolated, suppressed
- *Either common Neutral or live lamps

An advanced lighting module allowing any chase or sequence effects to be programmed, stored and recalled. Up to 128 patterns can then be replayed in the stored order, with control over the cycle on and off time. At the end of the program the system re-cycles to the start to maintain a continuous display. Full monitoring on the control panel over the outputs and control status is provided, and the program may be halted at any time. Although removing the mains supply to the module will delete the stored patterns the use of calculator type push buttons allows speedy programming ready for the following nights performance. The module obviously provides unlimited effects and is a must for all serious lighting shows.

MULTI - 4 £54.90

P/P 50p

- *4 channel
- *Sound modulation
- *Forward/reverse chase
- *Random direction chase
- *Zero suppression/fusing
- *Sound on chase modulation
- *Audio AGC or level control

The Multi-4 is a comprehensive sound and chase module, offering a wide range of forward, reverse or random effects, with additional sound modulation facilities. Modes of operation are set on control pots which act as electronic switches. The unit has a wide speed range and will accept virtually any sound level input. The multi-4 also provides monitor circuits for LED driving. The three outputs may be used to drive up to 4000W of lighting or up to 70 metres of rope lights.



Multi-4 P/P panels 50p
£9.70

Attractive blue panels with white letters, complete with LED monitors, knobs and mains illuminated switch.

NEW POWER DIMMING MODULES

- *Fully isolated
- *Multi channel common wiring lines
- *Master dimming over banks
- *Remote override
- *Dead "kill" and "all on"
- *Low voltage feed lines
- *Common neutral or live outputs

Power Dimming Modules

A range of isolated, digitally controlled dimming modules, complete with panels. Each type requires connection to the supply/reference board.

Slave power controllers (SPC)
Controls up to 1000W via the slider.
RFI suppressed/fused.
MC - £11.90
RS - £7.20
Supply/reference - £8.50
Master controllers (MC)
Will master dim from 1 to a bank of 20 SPC units.
- £18.20

Remote slaves (RS)
Will override an SPC at a remote location to the main system.

Supply/reference board
Provides the necessary supply voltages and signals to all units. Facilities for "Kill" and "all on". Supplies up to any combination of 50 modules.



3 CHANNEL SOUND/LIGHT CHASER

The famous high performance s/light system which automatically switches to chase upon absence of a music signal.

- *Zero suppressed
- *1000W/chan.
- *5Hz to 70KHz
- *Ultra sensitive input

£32.70

Our module systems are manufactured from the highest quality components, are fully tested, supplied with connection diagram and carry a twelve months guarantee.

Please note our prices include VAT, post-packing is shown separately. To order send either a cheque/postal orders/cash (registered) C.O.D. service £1 extra (max £100 C.O.D. limit) or your Access number. For further information send a S.A.E.

WE ALSO WELCOME OVERSEAS ENQUIRIES

UK Sales/Distribution Sweden/Norway
L&B Electronic, Wetab
45 Wortley Road, Drottin Kristinas,
West Croydon, vaeg 31,
Surrey CR0 3EB. 190 30 Stugna,
Tel: 01-689 4138 Sweden.

Please note L&B have no connection with LB Electronics of Hillingdon.

**"SPECIAL PRICES" POST £1-50
BAKER LOUDSPEAKERS**

Model	Ohms	Size Inch	Power Watts	Type	Our Price
Major	4, 8, 16	12	30	Hi-Fi	£14
Deluxe Mk II	8	12	15	Hi-Fi	£14
Superb	8, 16	12	30	Hi-Fi	£24
Auditorium	8, 16	12	45	Hi-Fi	£22
Auditorium	8, 16	15	60	Hi-Fi	£34
Group 45	4, 8, 16	12	45	PA	£14
Group 75	4, 8, 16	12	75	PA	£22
Group 100	8, 16	12	100	PA	£24
Group 100	8, 16	15	100	PA	£32
Disco 100	8, 16	12	100	Disco	£24
Disco 100	8, 16	15	100	Disco	£34

DE-LUXE DISCO MIXER. 240V, 4 stereo channels, 2 magnetic, 2 ceramic/tape, 1 mono mix channel, twin v.u. meters, headphone monitor outlet, slider controls, suitable for panel or desk mounting, attractive grained aluminium fascia, silver knobs. £40. Post £1.

2 CHANNEL STEREO MIXER. 9 volt operated £9.50 p&p 85p.

MINI MODULE LOUDSPEAKER KIT £10-95

EMI 15 x 8 1/2 in. 3-way Loudspeaker Baffle, 5in. Bass, 5in. Middle, 3in. Tweeter; 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response 60 to 20,000 c.p.s. 12 watt RMS 8 ohms £10-95 per kit. Two kits £20. Suitable Bookshelf Cabinet £10-50 each. Post £1-50

GARRARD 6-200 SINGLE PLAYER DECK

Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. £22. Post £2.

METAL PLINTH CUT FOR GARRARD

Size: 16 x 14 x 3in. £4-00 Silver or Black finish. Post £2.

ISKRA SINGLE RECORD PLAYER £8

Fitted with auto stop, stereo cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable size 7in. diameter, a.c. mains 240V 3 speed plays all size records. Post £1.

B.S.R. SINGLE PLAYER P170/2 £20.00

3-speeds 11in. aluminium turntable. "slim" arm, cueing device, stereo ceramic cartridge, silver trim, bias compensator, adjustable stylus pressure, plays all records, spring suspension, 240V AC. Post £2.

B.S.R. DE-LUXE AUTOCHANGER £20

with stereo cartridge, plays all size records. Post £2

WOODEN PLINTHS CUT FOR B.S.R. £4

Size: 15 x 15 x 3in. Teak effect. Post £2.

BSR P200. Belt drive deck, snake arm, cueing device, less head, £28-50. Post £2. Magnetic cartridge £5 extra.

TINTED PLASTIC COVERS POST £1-50

Size: 14 1/2 x 12 1/2 x 3in. £4. 17 1/2 x 9 1/2 x 3 1/2 in. £3. 18 x 13 1/2 x 3in. £6. 18 x 12 1/2 x 3in. £6.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £2-95 Post 65p

All parts and Instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7 1/2 or 9 or 12V d.c. up to 100mA or less. Please state voltage required.

PP BATTERY ELIMINATOR BRITISH

Mains stabilized power-pack 9 volt 400mA max. with overload cut out. Size 5 x 3 1/2 x 2 1/2 in. £4-50. Post 50p. Switched 3; 6; 7; 9 volt—stabilized £7-50.

MAINS TRANSFORMERS

	Post
250-0-250V 70mA 6-3V 2A	£4-50 £2-00
250-0-250 80mA 6-3V, 3-5A, 6-3V 1A	£5-00 £2-00
250-0-350V 150mA 6-3V 5A, 5V 2A	£12-50 £2-00
350-0-350V 250mA 6-3V 5 amp, 5V 2A	£14-50 £2-00
300-0-300 120mA 2 x 6-3V 2A C.T., 6-3V 2A	£10-00 £2-00
220V 45mA, 6-3V 2A	£2-50 £1-00
250V 60mA, 6-3V 2A	£2-75 £1-00

GENERAL PURPOSE LOW VOLTAGE

2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£6-00 £2-00
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6-00 £2-00
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£9-50 £2-00
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12-50 £2-00
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£18-00 £2-00

Post

	Post
5, 8, 10, 16V, 1A	£2-50 £1-00
12V 300mA	£1-50 80p
10-0-10 2A	£3-00 £1-00
12-0-12V 2A	£3-50 £1-00
20-0-20V 1A	£3-50 £1-00
32-0-32V 6 1/2A	£11-00 £2-00
15-0-15V 2A	£3-75 £1-00
2 x 18V 6A	£11-00 £2-00
AUTO TRANSFORMER 115V to 240V 50W	£12-00 £2-00

CHARGER TRANSF. Post RECTIFIERS

	Post
6-12v-3A	£4-00 £2-00
6-12v-4A	£6-50 £2-00
6-12v-6A	£8-50 £2-00
6-12v-1A	90p
6-12v-2A	£1-10
6-12v-4A	£2-00

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in. sides

6 x 4in. £1-20; 8 x 6in. £1-50; 10 x 7in. £1-90; 14 x 9in. £2-50; 16 x 6in. £2-40; 12 x 3in. £1-50; 16 x 10 in. £2-70; 12 x 8in. £2-20. ANGLE BRACKET, 6 x 1/2 x 1/2 in. 25p.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 30p; 8 x 6in. 60p; 10 x 7in. 80p; 12 x 5in. 60p; 12 x 8in. 90p; 18 x 6in. 90p; 14 x 9in. 1-20; 12 x 12 in. £1-30; 16 x 10in. £1-40.

ALUMINIUM BOXES, MANY OTHER SIZES IN STOCK

4 x 2 1/2 x 2 1/2 in. £1-00; 3 x 2 x 1 1/2 in. 80p; 6 x 4 x 2 1/2 in. £1-30; 8 x 6 x 3in. £2-10; 9 x 4 x 4in. £2-60; 10 x 7 x 3in. £2-50; 12 x 8 x 3in. £3-00; 12 x 5 x 3in. £2-30.

HIGH VOLTAGE ELECTROLYTICS

8/450V	45p	8+8/450V	75p	50+50/300V	50p
16/350V	45p	8+16/450V	75p	32+32/500V	£1-80
32/500V	75p	20+20/450V	75p	100+100/275V	65p
50/500V	£1-20	32+32/350V	75p	150+200/275V	70p
8/800V	£1-20	32+32+32/325V	90p	220/450V	95p

Post 65p Minimum. Callers Welcome. Access-Barclay-Visa. Lists 30p. Closed Wed.

Radio Component Specialists

337 WHITEHORSE ROAD
CROYDON, SURREY, U.K. Tel. 01-684 1665

CLEF ELECTRONIC MUSIC

FIRST

FOR PIANOS
FOR STRINGS
FOR ROTORS
FOR RHYTHM

IF MUSIC IS YOUR INTEREST

Since 1972 Clef Products have consistently produced designs in the field of Electronic Musical Instruments, many of which have been published under the authorship of A. J. Boothman. With musical quality of paramount importance new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability.

PIANOS

Kits or Manufactured
SPECIALISTS
SINCE 1972

Back up TELEPHONE advice to our customers is available direct from the Designer of all kits advertised.



STRINGS
P.E. STRING ENSEMBLE

Versatile String Synthesizer with split keyboard facility and impressive voices. 49 note organ diode keyswitch system with four pitches plus two phase Chorus generator. Kit includes Swell Pedal.

COMPONENT KIT
£174

The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique.

SIX OCTAVES £207

(component kits include keyboard and may be purchased in four stages)

7 1/2 OCTAVES £232

Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. & Manufactured Pianos.

ROTOR-CHORUS

Comprehensive two speed organ rotor simulator plus a three phase chorus generator on a single 8" x 5" p.c.b. The kit includes all components for mains operation and a stereo headphone driver p.c.b. Easily integrated with existing organ/amplifier system.

COMPONENT KIT
£89.00

KEYBOARDS

Our Square Front Keyboards are chosen for their superior feel to the discerning musician whilst giving adequate physical strength for the high impact playing present in the Piano application.

49 NOTE C-C £25.00
73 NOTE F-F £41.00
88 NOTE A-C £49.50
Quantity enquiries welcome



MASTER RHYTHM

As published in Practical Electronics

FULLY PROGRAMMABLE TWENTY-FOUR PATTERNS EIGHT PARALLEL TRACKS TWELVE INSTRUMENTS SEQUENCE OPERATION



Kit includes all components to build this comprehensive User Programmable Rhythm Generator in an attractive metal case with finished case, hardware and wire.

KIT - £79.00
BUILT - £114.00

OUR PRICES INCLUDE V.A.T., CARRIAGE & INSURANCE

Please send S.A.E. for complete lists or use our telephone BARCLAYCARD service. Very competitive EXPORT rates—in Australia please contact JAYCAR in Sydney.

ALL INSTRUMENTS MAY BE SEEN IN OUR SHOW ROOM.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept. P.E.) 44A Bramhall Lane South, Bramhall, Stockport, Cheshire SK7 1AH 061 439 3297

MICROCOMPUTER COMPONENTS

LOWEST PRICES — FASTEST DELIVERY

DEVICE	PRICE	DÉVICE	PRICE	DEVICE	PRICE
CPU's		74LS12	0.15	74LS378	0.73
6502	3.75	74LS13	0.29	74LS379	0.56
6800	3.60	74LS14	0.51	74LS386	0.29
6802	5.40	74LS15	0.15	74LS390	0.68
6803	14.53	74LS20	0.13	74LS393	0.61
6809	12.00	74LS21	0.15	CMOS	
8085A	5.99	74LS22	0.19	4001	0.12
Z80 CPU	4.00	74LS26	0.19	4002	0.12
Z80A CPU	5.92	74LS27	0.15	4006	0.69
SUPPORT CHIPS		74LS28	0.17	4007	0.14
6520	3.18	74LS30	0.14	4008	0.61
6522	5.60	74LS32	0.17	4009	0.31
6532	7.75	74LS37	0.17	4010	0.37
6821	1.75	74LS38	0.17	4011	0.13
6840	4.60	74LS40	0.14	4012	0.19
6850	1.75	74LS42	0.40	4013	0.39
6862	7.09	74LS47	0.42	4014	0.62
6871A1T	20.90	74LS48	0.70	4016	0.64
6875P	4.16	74LS49	0.62	4016	0.28
6848BP	9.38	74LS61	0.14	4017	0.54
6880	1.07	74LS62	0.15	4018	0.59
6887	0.80	74LS64	0.15	4019	0.36
8212	1.69	74LS73	0.22	4020	0.46
8216	1.95	74LS74	0.18	4021	0.70
8224	2.50	74LS75	0.30	4022	0.68
8228	4.20	74LS76	0.22	4023	0.19
8251	3.95	74LS78	0.25	4024	0.39
8253	7.95	74LS83	0.54	4025	0.15
8255	3.95	74LS85	0.77	4026	1.12
Z80 CTC	4.00	74LS86	0.18	4027	0.36
Z80A CTC	4.90	74LS90	0.36	4028	0.64
Z80 DMA	11.80	74LS91	0.81	4031	1.55
Z80A DMA	17.25	74LS92	0.40	4033	1.30
Z80 DART	7.20	74LS93	0.39	4034	1.60
Z80A DART	7.67	74LS95	0.45	4035	0.45
Z80 P10	4.00	74LS109	0.26	4038	2.25
Z80A P10	4.40	74LS112	0.26	4039	2.45
Z80 S10-0	17.90	74LS113	0.26	4040	0.67
Z80 S10-1	17.90	74LS114	0.26	4041	0.70
Z80 S10-2	22.90	74LS122	0.45	4042	0.56
Z80A S10-0	22.90	74LS123	0.45	4043	0.62
Z80A S10-1	22.90	74LS124	1.07	4044	0.62
Z80A S10-2	22.90	74LS125	0.29	4045	1.30
MEMORIES		74LS126	0.29	4046	0.75
2114 200ns low power	1.29	74LS132	0.51	4047	0.78
2708	1.99	74LS136	0.29	4048	0.44
2716 (5v)	2.67	74LS137	0.40	4049	0.28
2732 2532 (specify)	7.89	74LS139	0.40	4050	0.27
4116 150ns	1.25	74LS145	0.78	4051	0.62
4116 200ns	0.99	74LS148	1.13	4052	0.62
4118-3	4.29	74LS151	0.35	4053	0.82
6116	12.00	74LS152	0.35	4054	0.22
6810P	1.43	74LS155	0.50	4055	1.00
REGULATORS		74LS156	0.50	4060	0.88
7805	0.55	74LS157	0.36	4063	0.94
7812	0.55	74LS158	0.40	4066	0.38
7905	0.60	74LS160	0.43	4067	0.22
7912	0.60	74LS161	0.43	4068	0.21
CRT CONTROLLERS		74LS162	0.43	4069	0.15
9364AP	8.64	74LS163	0.43	4070	0.23
6845	9.90	74LS164	0.51	4071	0.20
BUFFER		74LS166	0.37	4072	0.20
81LS95	1.20	74LS173	0.77	4073	0.20
81LS96	1.25	74LS174	0.78	4074	0.20
81LS97	1.20	74LS175	0.60	4076	0.67
81LS98	1.25	74LS181	1.50	4077	0.23
8726A	1.50	74LS180	0.61	4078	0.20
8728A	1.50	74LS191	0.61	4081	0.20
8795A	1.50	74LS192	0.69	4082	0.20
8797N	1.50	74LS193	0.69	4085	0.45
8798	1.50	74LS194	0.42	4086	0.56
MISC. SUPPORT CHIPS		74LS195	0.42	4093	0.43
AY-3-1015 (or equiv.)	3.49	74LS196	0.68	4502	0.80
AY-5-1013 (or equiv.)	3.19	74LS197	0.68	4507	2.25
AY-5-2376 (or equiv.)	7.00	74LS221	1.01	4510	0.67
MC1488	0.75	74LS242	0.85	4512	0.63
MC1489	0.75	74LS243	0.85	4514	1.53
MC14411	6.99	74LS244	0.84	4515	2.38
MC14412	7.99	74LS245	1.21	4516	0.22
DATA CONVERTERS		74LS247	0.41	4518	0.72
ZN425E	3.50	74LS248	0.74	4519	0.56
ZN426E	3.00	74LS249	0.74	4520	0.71
ZN427E	6.28	74LS251	0.46	4521	1.65
ZN428E	4.78	74LS253	0.46	4522	1.15
ZN429E	2.10	74LS257	0.57	4526	0.75
ZN432	28.09	74LS258	0.40	4527	1.00
ZN433	22.59	74LS259	1.15	4528	0.79
Data converter Handbook	1.00	74LS261	3.12	4532	0.90
74LS SERIES		74LS266	0.25	4541	1.15
74LS00	0.11	74LS273	0.97	4543	1.15
74LS01	0.15	74LS279	0.37	4853	2.50
74LS02	0.14	74LS283	0.45	4555	0.40
74LS03	0.14	74LS290	0.60	4556	0.47
74LS04	0.13	74LS293	0.53	4585	1.05
74LS05	0.15	74LS365	0.39	CRYSTALS	1.80
74LS08	0.14	74LS366	0.38	4MHz	
74LS09	0.13	74LS367	0.38	DIL SOCKETS	
74LS10	0.15	74LS368	0.38	8 14 16 18 20	
74LS12	0.13	74LS373	0.79	Price	7 8 9 14 16
74LS15	0.15	74LS374	0.79	Price	22 24 28 40
74LS16	0.13	74LS375	0.50	Price	18 20 24 32
74LS17	0.15	74LS377	0.97	E. & O.E.	

OFFICIAL ORDERS WELCOME - QUANTITY DISCOUNTS AVAILABLE

Midwich Computer Co., Ltd.,

(Dept. PE),

Hewlett House, Northgate Street,
Bury St. Edmunds, Suffolk IP33 1HQ.
Telephone: (0284) 701321

All prices exclude post and packing on orders under £10 (50p) and VAT (15%).

ALL ORDERS DESPATCHED ON DAY OF RECEIPT WITH FULL REFUND FOR OUT OF STOCK ITEMS IF REQUESTED.

24 hour Telephone Credit Card Orders
Telephone: (0284) 701321.

CREDIT CARD ORDERS WELCOME

RADIATION DETECTORS

BE PREPARED WITH THIS DETECTOR

Recommended for General use.
CIVIL DEFENCE • FIRE SERVICES • MEDICAL

VIEW THRU LENS

R

FREE RE-CHARGES AFTER PURCHASE

THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS:

UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.

PRECISION INSTRUMENT, METAL CASED, WEIGHT 2 oz.

CONTAINS 3 LENSES. RUGGED CONSTRUCTION.

MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.

Choice of 2 types
0-5 or 0-50R
ONLY

£6.95 inc. VAT
Post & Packing 60p

Be prepared, buy whilst available.

Henry's


404 EDGWARE RD, LONDON W2 1ED

Telephone: 01-723 5095



COMPLETE WITH DATA

STORAGE CABINETS

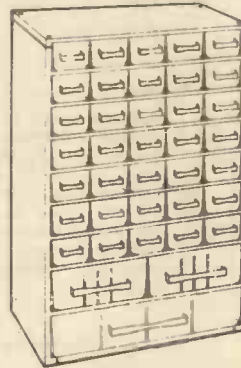

Type 1838

Metal Cabinets 12" wide x 5 3/4" deep, finished blue with transparent plastic drawers.

Type	H (ins)	No. of Drawers	Price
1118	11	15 2 1	£10.75
1633	16	30 2 1	£13.95
1838	18	35 2 1	£15.95
2236	22	30 4 2	£18.55
2260	22	60 -	£18.55

Access/Barclaycard welcome

Prices include VAT and Post. Cheque/P.O. to:

Millhill Supplies (Tools),

35 Preston Crowmarsh, Benson, Oxon OX9 6SL.

TTL	74151A	55p	4060	100p	LS107	44p	Regulators	IN4001/4	6p
7400	11p	74153	65p	4069	20p	LS109	64p	IN4006	7p
7402	11p	74157	65p	4081	25p	LS123	60p	IN5401/4	14p
7403	14p	74160	75p	4082	25p	LS126	55p	IN5407	24p
7404	14p	74161	75p	4511	90p	LS157	55p	W001	26p
7407	30p	74164	99p	4518	88p	LS160	85p	W005	30p
7410	14p	74174	80p	4520	140p	LS161	85p	W04	36p
7413	30p	74175	80p	4543	140p	LS164	90p	7912	65p
7414	35p	74175	80p	4555	70p	LS174	99p	DIL SOCKETS	
7416	25p	CMOS-B		74LS		LS175	99p	Low Profile	
7420	15p	4001	14p	LS01	13p	LS221	105p	BC107/9	10p
7426	35p	4002	15p	LS02	15p	LS390	110p	BC147/8	9p
7430	16p	4011	17p	LS03	15p	LS393	110p	BC157/8	9p
7441	64p	4012	18p	LS04	15p	MEMORIES	16 pin	BC184	9p
7442A	64p	4013	18p	LS10	18p	2102	95p	BC214	9p
7447A	48p	4016	32p	LS12	20p	2112	250p	BD131/2	40p
7451	16p	4017	66p	LS13	38p	2114-3	195p	BF194-7	10p
7454	16p	4023	20p	LS14	48p	4116-3	210p	BF259	32p
7473	26p	4024	48p	LS20	18p	2708	350p	BF373	38p
7474	27p	4027	40p	LS26	26p	2716	450p	LINEAR	
7486	30p	4029	90p	LS30	20p	CA3130	90p	BU208	150p
7490A	30p	4040	84p	LS42	64p	DL704	95p	LM301A	27p
7492A	40p	4046	96p	LS51	22p	DL707	95p	LM311	70p
7493A	40p	4049	32p	LS54	22p	DL747	150p	LM381A	160p
74107	32p	4050	32p	LS73	44p	LED's		NE555	32p
74109	44p	4051	68p	LS74	27p	Green, Red	12p	NE556	60p
74121	32p	4052	68p	LS90	30p	Small	12p	NE558	60p
74123	48p	4053	68p	LS91	64p	Large	15p	DIODES	
74141									



I.L.P. TRANSFORMERS

INCREASED PRODUCTION CAPACITY BRINGS LOWER PRICES

TYPE	SERIES	SECONDARY Volts	R.M.S. Current	PRICE
30va 70 x 30mm 0.45 Kg regulation 18%	1X010	6 + 6	2.50	£4.48 + 0.87p P&P + 0.80p VAT
	1X011	9 + 9	1.66	
	1X012	12 + 12	1.25	
	1X013	15 + 15	1.00	
	1X014	18 + 18	0.83	
	1X015	22 + 22	0.68	
	1X016	25 + 25	0.56	
2X010	30 + 30	0.50		
50va 80 x 35mm 0.9 Kg regulation 13%	2X010	6 + 6	4.16	£4.93 + £1.10 P&P + 0.90 VAT
	2X011	9 + 9	2.77	
	2X012	12 + 12	2.08	
	2X013	15 + 15	1.66	
	2X014	18 + 18	1.38	
	2X015	22 + 22	1.13	
	2X016	25 + 25	1.00	
2X017	30 + 30	0.83		
2X028	110	0.45		
2X029	220	0.22		
2X030	240	0.20		
80va 90 x 30mm 1.0 Kg regulation 12%	3X010	6 + 6	6.64	£5.47 + £1.43 P&P + 1.04 VAT
	3X011	9 + 9	4.44	
	3X012	12 + 12	3.33	
	3X013	15 + 15	2.66	
	3X014	18 + 18	2.22	
	3X015	22 + 22	1.81	
	3X016	25 + 25	1.60	
	3X017	30 + 30	1.33	
	3X028	110	0.72	
	3X029	220	0.36	
3X030	240	0.33		
120va 90 x 40mm 1.2 Kg regulation 11%	4X010	6 + 6	10.00	£6.38 + £1.43 P&P + £1.17 VAT
	4X011	9 + 9	6.68	
	4X012	12 + 12	5.00	
	4X013	15 + 15	4.00	
	4X014	18 + 18	3.33	
	4X015	22 + 22	2.72	
	4X016	25 + 25	2.40	
	4X017	30 + 30	2.00	
	4X018	35 + 35	1.71	
	4X028	110	1.09	
4X029	220	0.54		
4X030	240	0.50		

Also available from ELECTROVALVE, MAPLIN, MARSHALLS, TECHNOMATIC and WATFORD.

TYPE	SERIES	SECONDARY Volts	R.M.S. Current	PRICE
160va 110 x 40mm 1.8 Kg regulation 8%	5X011	9 + 9	8.89	£8.44 + £1.43 P&P + £1.48 VAT
	5X012	12 + 12	6.66	
	5X013	15 + 15	5.33	
	5X014	18 + 18	4.44	
	5X015	22 + 22	3.63	
	5X016	25 + 25	3.20	
	5X017	30 + 30	2.66	
	5X018	35 + 35	2.28	
	5X026	40 + 40	2.00	
	5X028	110	1.45	
5X029	220	0.72		
5X030	240	0.66		
225va 110 x 45mm 2.2 Kg regulation 7%	6X012	12 + 12	9.38	£10.06 + £1.73 P&P + £1.77 VAT
	6X013	15 + 15	7.50	
	6X014	18 + 18	6.25	
	6X015	22 + 22	5.11	
	6X016	25 + 25	4.50	
	6X017	30 + 30	3.75	
	6X018	35 + 35	3.21	
	6X026	40 + 40	2.81	
	6X025	45 + 45	2.50	
	6X028	110	2.04	
6X029	220	1.02		
6X030	240	0.93		
300va 110 x 50mm 2.6 Kg regulation 6%	7X014	18 + 18	8.33	£11.66 + £1.73 P&P + £2.01 VAT
	7X015	22 + 22	6.82	
	7X016	25 + 25	6.00	
	7X017	30 + 30	5.00	
	7X018	35 + 35	4.28	
	7X026	40 + 40	3.75	
	7X025	45 + 45	3.33	
	7X033	50 + 50	3.00	
	7X028	110	2.72	
	7X029	220	1.36	
7X030	240	1.25		

5-YEAR GUARANTEE

Toroidals have only half the weight and height of laminated equivalents, are appreciably more efficient, cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. All I.L.P. Toroidal Transformers carry our full 5-year guarantee.

95 TOROIDAL TYPES From 30va to 625va

TYPE	SERIES	SECONDARY Volts	R.M.S. Current	PRICE
500va 140 x 60mm 4.0 Kg regulation 4%	8X017	30 + 30	8.33	£15.53 + £2.05 P&P + £2.64 VAT
	8X018	35 + 35	7.14	
	8X026	40 + 40	6.25	
	8X025	45 + 45	5.55	
	8X033	50 + 50	5.00	
	8X042	55 + 55	4.54	
	8X028	110	4.54	
	8X029	220	2.27	
	8X030	240	2.08	
	625va 140 x 75mm 5.0 Kg regulation 4%	9X017	30 + 30	
9X018		35 + 35	8.92	
9X026		40 + 40	7.81	
9X025		45 + 45	6.94	
9X033		50 + 50	6.25	
9X042		55 + 55	5.58	
9X028		110	5.68	
9X029		220	2.84	
9X030		240	2.60	

All voltages quoted are for FULL LOAD. Add regulation figure to secondary voltage for OFF LOAD voltage.

● CHOICE OF 3 PRIMARY INPUTS
I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows (Secondaries can be connected in series or parallel):
For 110V Primary insert 0 in place of "X" in type number. For 220V Primary (Europe) insert 1 in place of "X" in type number. For 240V Primary (U.K.) insert 2 in place of "X" in type number.
THUS: 50va 240v. 6 + 6v 4. 16A = 2.2010.
● WHEN ORDERING (U.K. only). Simply send your order in envelope marked FREEPOST. NO STAMP REQUIRED.
Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd. or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. U.K. customers must include V.A.T. with payment.
GOODS DESPATCHED WITHIN 7 DAYS OF RECEIPT OF ORDER

To: I.L.P. ELECTRONICS LTD., CANTERBURY CT2 7EP
Please supply Transformer(s)..... No.(s).....
Total purchase price £.....
I enclose Cheque Postal Order International Money Order
Debit my Access/Barclaycard Account No.....
NAME.....
ADDRESS.....
Signature.....



I.L.P. TRANSFORMERS

FREEPOST T.2. GRAHAM BELL HOUSE ROPER CLOSE
CANTERBURY CT2 7EP Phone (0227) 54778 Technical (0227) 64723 Telex 965 750

MAINS INTERCOM



NO BATTERIES
NO WIRES
ONLY
£37.99
PER PAIR
+ VAT £5.70

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1/2 mile on the same mains phase. On/off switch. Volume control, with 'buzzer' call and light indicator. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. Also F.M. 2 channel 'touch' model £55.95 + VAT £8.40 + P & P £2.15

NEW AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£18.95
+ VAT £2.85
+ P & P £1.65

Latest transistorised Telephone Amplifier, with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording, model at £20.95 + VAT £3.15. P & P £1.65.

DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged, and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock); mains power unit, cable (4 pairs) 50 ft. and wiring diagram. Price £59.95 + VAT £9.00 + P & P £2.25. Kit with two Telephone's £69.95 + VAT £10.50 + P & P £2.45.

10-day price refund guarantee on all items
WEST LONDON DIRECT SUPPLIES (PE9)
169 KENSINGTON HIGH STREET,
LONDON, W8. 01-937-5548.

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, PRACTICAL ELECTRONICS will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of PRACTICAL ELECTRONICS summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc. received as a result of answering such advertisements. Classified advertisements are excluded.

THE ART OF ELECTRONICS

by Horowitz & Hill Price: £13.50

THE PPL SYNTHESIZER COOKBOOK
by H. Kinley Price: £5.25

THE MC6809 COOKBOOK
by C. D. Warren Price: £5.00

DIGITAL ICs... HOW THEY WORK &
HOW TO USE THEM
by A. W. Barber Price: £5.75

ELECTRONIC DESIGN WITH OFF THE
SHELF INTEGRATED CIRCUITS
by Z. H. Melksin Price: £6.25

EXPERIMENTER'S GUIDE TO SOLID STATE
ELECTRONICS PROJECTS
by A. W. Barber Price: £5.50

COMPLETE GUIDE TO READING
SCHEMATIC DIAGRAMS
by J. Douglas-Young Price: £5.50

PRACTICAL SOLID STATE CIRCUIT DESIGN
by J. E. Oleksy Price: £6.50

WORLD RADIO T.V. HANDBOOK
by J. M. Frost Price: £10.50

1981 THE RADIO AMATEUR'S HANDBOOK
by A.R.R.L. Price: £8.00

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

MAPLIN make it easy...



in SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



in HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.

On sale now in all branches
WH Smith price £1.

In case of difficulty check the coupon below.

make it easy... with MAPLIN

The Maplin Matinée
Amazing value for only £299.95 plus £99.50 for cabinet if required (Carriage Extra)

Easy to build, superb specification.
Comparable with organs selling for up to £1,000.



MAPLIN ELECTRONIC SUPPLIES LTD.

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911

by MAIL ORDER

A fast service you can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____

Address _____