

PRACTICAL

FEBRUARY 1985 · £1.00

ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING

**8
EXTRA
PAGES**

**MODULAR AUDIO
POWER SYSTEM**

**SPECTRUM
DAC/ADC BOARD**

**SIGNAL
GENERATOR
F-V CONVERTER**


MICROWRITING

**The Principle
and the Product**

Have you one of these?



Then you need one of these

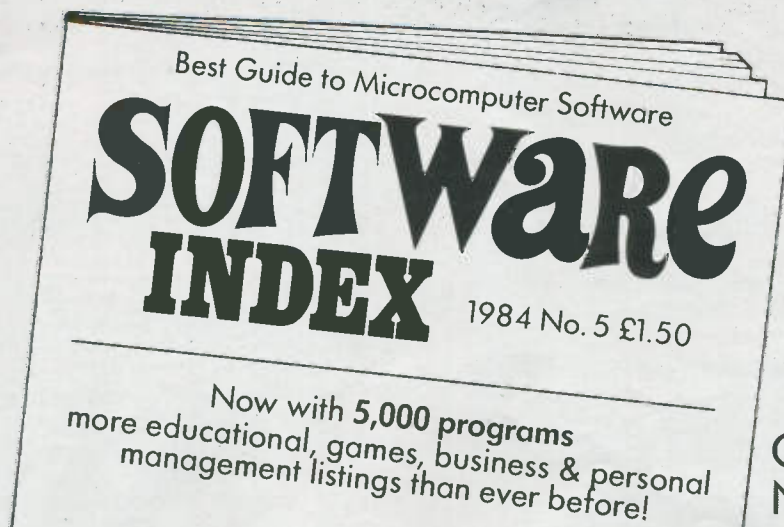

**ON SALE
NOW!**

CONSTRUCTIONAL PROJECTS


MODULAR AUDIO POWER SYSTEM—Part 1 by M. Tooley BA and D. Whitfield MA MSc CEng MIEE . . .	10
Main power amp module	
SPECTRUM DAC/ADC BOARD by R. A. Penfold	15
Interface board for control applications	
MICROPROCESSOR CONTROLLED D.C. MOTOR DRIVERS by Tom Gaskell BA(Hons) CEng MIEE . .	31
Enables analogue driving of d.c. motors	
SIGNAL GENERATOR & F-V CONVERTER by John M. H. Becker	34
Quality test instrument	
NEPTUNE AND MENTOR ROBOTS by Richard Becker and Tim Orr	49
Part Six: Commissioning and testing of Neptune	
MONO/STEREO CHORUS & FLANGER by John M. H. Becker	59
Part Two: Construction and setting up	

GENERAL FEATURES

MICROWRITER by Tom Gaskell BA(Hons) CEng MIEE	22
An ingenious six-key alternative to the QWERTY keyboard	
SEMICONDUCTOR CIRCUITS by Tom Gaskell BA(Hons) CEng MIEE	28
Power Op-Amps (TCA 365 and TCA 2365)	
SPACEWATCH by Dr. Patrick Moore OBE	40
INGENUITY UNLIMITED	42
Readers' circuit ideas	
SEQUENTIAL LOGIC TECHNIQUES by M. Tooley BA and D. Whitfield MA MSc CEng MIEE	55
Part Five: Data multiplexers	



NEWS & COMMENT

EDITORIAL	7	BAZAAR	18, 48	MICROBUS	65
NEWS & MARKET PLACE	8	INDUSTRY NOTEBOOK	21	VERNON TRENT	67
		LEADING EDGE	25	P.C.B. SERVICE	68

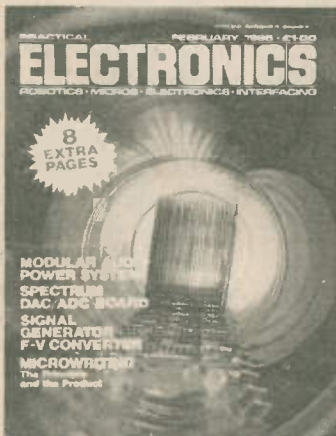

THIS MONTH'S COVER...

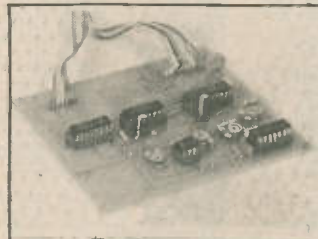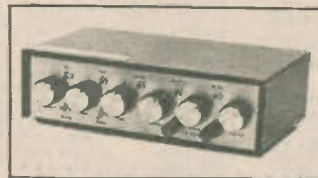Our cover photograph shows silicon wafers in a furnace during the production of integrated circuits. Photograph courtesy of National Semiconductor.



OUR MARCH ISSUE WILL BE ON SALE FRIDAY, FEBRUARY 1st, 1985 (see page 47)

© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WATFORD ELECTRONICS

33, CARDIFF ROAD, WATFORD, HERTS, WD1 8ED, ENGLAND

Tel. Watford (0923) 40588. Telex: 8956095 WAELEC

ORDERS NORMALLY DESPATCHED BY RETURN OF POST

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. SEND CASH, P.D. OR CHEQUE WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (ACCESS DRDRS BY TELEPHONE 0923-50234). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 70p TO ALL CASH ORDERS. OVERSEAS POSTAGE AT COST. PRICES SUBJECT TO CHANGE.

VAT

Export orders non VAT. U.K. customers please add 15% VAT to total cost incl. p&p. We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Open Monday to Saturday, 9.00am to 6.00pm. Ample FREE Car parking.

POLYESTER RADIAL LEAD CAPACITORS: 250V: 10µ, 20µ, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 8p; 150n, 220n 10p; 330n, 470n 15p; 680n 19p; 1µ 23p; 1µ5 40p; 2µ 246p.

ELECTROLYTIC CAPACITORS (Values in µF): 50V: 10µF 52p; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 8p; 4.7 9p; 10 10p; 15 12.2p; 33 15p; 47 12p; 68 16p; 100 19p; 220 26p; 1000 70p; 2200 99p; 50V: 68 20p; 100 17p; 220 24p; 40V: 6.8 15p; 22 9p; 33 12p; 330 47p; 1000 48p; 2200 50p; 3300 76p; 4700 92p; 10 15p; 15p; 22 10p; 33 12p; 47 15p; 68 18p; 100 20p; 150 22p; 220 24p; 470 27p; 1000 31p; 2200 36p; 4700 39p.

TAG-END TYPE: 64V: 4700 245p; 3300 198p; 2200 129p; 50V: 2200 154p; 2200 110p; 40V: 4700 160p; 25V: 4700 98p; 1000 320p; 15000 345p.

TANTALUM BEAD CAPACITORS: 35V: 0.1µ, 0.22, 0.33 15p 0.47, 0.68, 1.0, 1.5 16p 2.2, 3.3 18p 4.7, 6.8 22p 10 28p 16V: 2.2, 3.3, 16p 4.7, 6.8, 10 18p 15 36p 22 36p 37 45p 100 95p 220 100p 10V: 1.5, 2.2 26p 33, 47 50p 100 75p.

SILVER MICRA (pF)
2, 3, 3.3, 4.7, 6.8, 8.2, 10, 12, 18, 22, 27, 33, 39, 47, 56, 68, 75, 82, 85, 100, 120, 150, 180 15p, 220, 250, 270, 330, 360, 390, 470, 600, 800 & 820 19p 2.2p, 3.3p, 4.7p, 6.8p, 8.2p, 10p, 12p, 15p, 18p, 22p, 27p, 33p, 39p, 47p, 56p, 68p, 75p, 82p, 85p, 100p, 120p, 150p, 180p 11p, 220p 13p, 330p 18p; 470n 23p; 680n 30p; 1000p 34p; 2200p 38p; 4700p 42p.

GAMIC CAPACITORS: 50V
Range 1pF to 6800pF 5p, 10nF, 15n, 33n, 47n 5p; 100nF/30V 7p.

POLYSTYRENE Caps:
10pF to 1nF 8p, 1n5 to 12nF 10p

RESISTORS S.I.L. Package: 7 Commedon, 100Q, 470Q, 680Q, 1K, 2K, 4K, 10K, 27K, 47K, 100K 26p. 8 Commedon: (9 pins) 150Q, 180Q, 270Q, 330Q, 330Q, 1K, 2K, 4K, 10K, 27K, 47K, 100K 26p.

TRANSISTORS

AC127/8	35	BC308B	16	BFR98	105	TI30C	37	2N1945	32	2N5458/9	30
AC141/2	35	BC327B	15	BCP1	35	TI31A	38	2N1981	40	2N5485	36
AC176	35	BC337B	15	BCP2	35	TI32A	43	2N1981	40	2N5485	36
AC187/8	35	BC44	34	BCP5	35	TI33A	43	2N1981	40	2N5485	36
AC188	35	BC45	34	BCP6	35	TI34A	43	2N1981	40	2N5485	36
AD142	120	BC477B	40	BCP8	35	TI35A	43	2N1981	40	2N5485	36
AD149	79	BC517B	40	BCP9	35	TI36A	43	2N1981	40	2N5485	36
AD161/2	42	BC547B	12	BCP10	35	TI37A	43	2N1981	40	2N5485	36
AF118	95	BC549C	15	BCP11	35	TI38A	43	2N1981	40	2N5485	36
AF139	40	BC567F	15	BCP12	35	TI39A	43	2N1981	40	2N5485	36
AF239	55	BC59	35	BCP13	35	TI40A	43	2N1981	40	2N5485	36
BC107/8	12	BC514/2	30	BCP14	35	TI41A	43	2N1981	40	2N5485	36
BC107B	14	BCY70	18	BCP15	35	TI42A	43	2N1981	40	2N5485	36
BC108B	14	BCY21	20	BCP16	35	TI43A	43	2N1981	40	2N5485	36
BC108C	14	BCY72	25	BCP17	35	TI44A	43	2N1981	40	2N5485	36
BC109	12	BCY75	25	BCP18	35	TI45A	43	2N1981	40	2N5485	36
BC109B	14	BCY78	25	BCP19	35	TI46A	43	2N1981	40	2N5485	36
BC109C	14	BD133	60	BCP20	35	TI47A	43	2N1981	40	2N5485	36
BC114/5	30	BD135	45	BCP21	35	TI48A	43	2N1981	40	2N5485	36
BC117/8	25	BD136/7	40	BCP22	35	TI49A	43	2N1981	40	2N5485	36
BC140	38	BD138/9	40	BCP23	35	TI50A	43	2N1981	40	2N5485	36
BC142/3	38	BD140	40	BCP24	35	TI51A	43	2N1981	40	2N5485	36
BC142/4	38	BD142	40	BCP25	35	TI52A	43	2N1981	40	2N5485	36
BC147B	15	BD245	65	BCP26	35	TI53A	43	2N1981	40	2N5485	36
BC148C	10	BD434	70	BCP27	35	TI54A	43	2N1981	40	2N5485	36
BC149	12	BD695A	150	BCP28	35	TI55A	43	2N1981	40	2N5485	36
BC149C	15	BD696A	150	BCP29	35	TI56A	43	2N1981	40	2N5485	36
BC153A	30	BF115	45	BCP30	35	TI57A	43	2N1981	40	2N5485	36
BC154/8	30	BF125	45	BCP31	35	TI58A	43	2N1981	40	2N5485	36
BC159	11	BF167	35	BCP32	35	TI59A	43	2N1981	40	2N5485	36
BC167A	14	BF173	35	BCP33	35	TI60A	43	2N1981	40	2N5485	36
BC168C	12	BF178	35	BCP34	35	TI61A	43	2N1981	40	2N5485	36
BC169C	12	BF178	35	BCP35	35	TI62A	43	2N1981	40	2N5485	36
BC171/2	12	BF179	40	BCP36	35	TI63A	43	2N1981	40	2N5485	36
BC172/3	12	BF179	40	BCP37	35	TI64A	43	2N1981	40	2N5485	36
BC177/8	16	BF198/9	18	BCP38	35	TI65A	43	2N1981	40	2N5485	36
BC179/81	20	BF200	30	BCP39	35	TI66A	43	2N1981	40	2N5485	36
BC181	30	BF224	40	BCP40	35	TI67A	43	2N1981	40	2N5485	36
BC182/3	10	BF244A	28	BCP41	35	TI68A	43	2N1981	40	2N5485	36
BC181	10	BF244B	28	BCP42	35	TI69A	43	2N1981	40	2N5485	36
BC182	10	BF245	55	BCP43	35	TI70A	43	2N1981	40	2N5485	36
BC183L	10	BF256B	50	BCP44	35	TI71A	43	2N1981	40	2N5485	36
BC184L	10	BF257B	32	BCP45	35	TI72A	43	2N1981	40	2N5485	36
BC186/7	28	BF259	40	BCP46	35	TI73A	43	2N1981	40	2N5485	36
BC121/3	12	BF394	40	BCP47	35	TI74A	43	2N1981	40	2N5485	36
BC121L	10	BF435	40	BCP48	35	TI75A	43	2N1981	40	2N5485	36
BC121/3L	10	BF435	40	BCP49	35	TI76A	43	2N1981	40	2N5485	36
BC121A	10	BF594/5	30	BCP50	35	TI77A	43	2N1981	40	2N5485	36
BC214L	15	BF839/40	25	BCP51	35	TI78A	43	2N1981	40	2N5485	36
BC237/8	15	BF841/2	25	BCP52	35	TI79A	43	2N1981	40	2N5485	36
BC307B	15	BF808/1	25	BCP53	35	TI80A	43	2N1981	40	2N5485	36

POTENTIOMETERS: Carbon Track, 0.25W Log & Linear Values.

500W, 1K & 2K (LIN ONLY) Single 35p
5KQ-2MΩ single gang 95p
5KQ-2MΩ single gang D/P switch 95p
5KQ-2MΩ dual gang stereo 99p

SLIDER POTENTIOMETERS: 0.25W Log and linear values 60mm track
5KQ-500KΩ Single gang 80p

PRESET POTENTIOMETERS: 0.1W 50Ω-2.2M Mini Vert. & Horiz. 8p
0.25W 220Ω-4M Vert. & Horiz. 12p

RESISTORS Hi-stab, Miniature, 5% Carbon.
RANGE Val. 1-99 100+
0.25W 202 -4-M7 E24 3p 1p
0.5W 222 -4-M7 E12 3p 1p
1W 202 -10M E12 6p 9p
1/2 Metal Film 5% I-ME24 3p 6p


LINEAR IC'S

555 CMOS	95	LM334Z	160	SB4209	595	ZN428E	450	8216	£3	TMS9914	895	745280	70	7453	30	74196	120	LS83	70	LS320	210	4035	70	4519	32
702	75	LM335	135	SL924	200	ZN1429E-8	245	8224	£0	TMS9927	895	745262	£7	7454	30	74198	100	LS86	35	LS322	360	4037	115	4521	115
709C 8 pin	35	LM337	275	SL924	200	ZN1034E	200	8228	£2	TMS9928	895	745275	£0	7470	50	74199	200	LS90	50	LS324	150	4038	75	4522	125
710	48	LM339	40	SN76013N	350	ZN1040E	695	8243	£2	TMS9980	£20	745280	£0	7472	50	74221	200	LS90	50	LS325	150	4039	280	4526	60
741	16	LM348	60	SN76033	350	ZN2434E	925	8250	£1	TMS9995	£12	745281	£0	7473	50	74246	130	LS92	55	LS326	290	4040	60	4527	65
747C 14 pin	70	LM349	125	SN76488	525		8251	8251	£0	ULN2003	500	745283	£0	7474	45	74247	120	LS93	59	LS327	290	4041	57	4528	70
747C 8 pin	90	LM358	100	SP0256AL	475		8253	8253	£2	Z80CAPUM	£45	745284	£3	7475	12	74248	145	LS94	110	LS328	350	4042	55	4529	100
753 8 pin	185	LM377	210	TA1720	140		8256A	8256A	£1	UPD7002	£60	745288	£0	7476	45	74249	175	LS96	90	LS348	140	4043	42	4530	90
810	159	LM379	495	TA7130	125		8257A	8257A	£0	UPD7007	£15	745289	£0	7478	60	74251	90	LS107	45	LS352	110	4044	50	4531	130
9400CJ	375	LM380	120	TA7204	150	2102L	160	8259	£7	WD1710	£19.95	745299	£50	7481	175	74259	150	LS109	45	LS353	110	4045	110	4532	65
ADC0808	885	LM381N	175	TA7205	100	2114	325	8271	POA	Z80CPU 2.5	300	745305	£25	7483	100	74273	180	LS113	40	LS356	200	4047	60	4536	275
AY-11320	225	LM382	200	TA7222	150	2147.3	425	8272	£25	Z80CAPUM	£45	745323	£3	7484	375	74274	100	LS114	40	LS357	200	4048	60	4537	80
AY-15050	99	LM384	275	TA7232	150	2516	350	8279	£5	Z80OACT	£20	745374	£3	7485	100	74278	160	LS122	70	LS364	150	4049	38	4539	70
AY-15051	160	LM386	90	TA9A000	295	2532-4	400	8282	£40	Z80B	£11	745412	£30	7486	40	74279	80	LS123	100	LS365	50	4050	35	4541	95
AY-16720	210	LM387	200	TA9A621	295	2532-3	450	8283	£45	Z80BDART	795	745420	£32	7489	200	74283	100	LS124	125	LS366	50	4051	70	4543	90
AY-38910	390	LM389	160	TA9A661	190	2564	700	8284	£50	Z80BDART	820	745471	£60	7490	60	74284	440	LS125	50	LS367	50	4052	60	4544	150
AY-38912	500	LM393	85	TA9A700	275	27108	450	8288	£50	Z80ADMA	920	745472	£40	7491	70	74285	300	LS126	50	LS368	50	4053	60	4545	400
AY-5-1317A	630	LM394CH	385	TA9A700	159	2716-5V	350	8288	£45	Z80ADMA	920	745473	£3	7492	100	74286	300	LS127	100	LS369	100	4054	38	4546	275
AY-13011	1																								

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thank to I.L.P., PRICE.

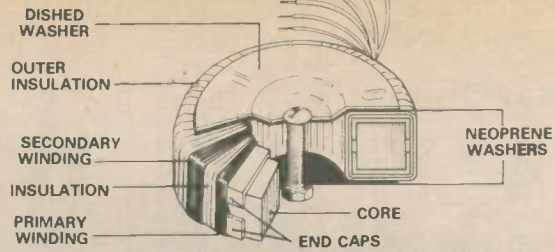Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 14 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA			50 VA			120 VA			225 VA			500 VA		
62 x 34mm Regulation 19%			80 x 35mm Regulation 13%			90 x 40mm Regulation 11%			110 x 45mm Regulation 7%			140 x 60mm Regulation 4%		
0.35Kg			0.9Kg			1.2Kg			2.2Kg			4Kg		
SERIES	SECONDARY	RMS	2x010	6+6	4.16	4x010	6+6	10.00	6x012	12+12	9.38	8x016	25+25	10.00
No.	Volts	Current	2x011	9+9	2.77	4x011	9+9	6.66	6x013	15+15	7.50	8x017	30+30	8.33
0x010	6+6	1.25	2x012	12+12	2.08	4x012	12+12	5.00	6x014	18+18	6.25	8x018	35+35	7.14
0x011	9+9	0.83	2x013	15+15	1.66	4x013	15+15	4.00	6x015	22+22	5.11	8x026	40+40	6.25
0x012	12+12	0.63	2x014	18+18	1.38	4x014	18+18	3.33	6x016	25+25	4.50	8x025	45+45	5.55
0x013	15+15	0.50	2x015	22+22	1.33	4x015	22+22	2.72	6x017	30+30	3.75	8x033	50+50	5.00
0x014	18+18	0.42	2x016	25+25	1.00	4x016	25+25	2.40	6x018	35+35	3.21	8x042	55+55	4.54
0x015	22+22	0.34	2x017	30+30	0.83	4x017	30+30	2.00	6x026	40+40	2.81	8x028	110	4.54
0x016	25+25	0.30	2x028	110	0.45	4x018	35+35	1.71	6x025	45+45	2.50	8x029	220	2.27
0x017	30+30	0.25	2x029	220	0.22	4x028	110	1.09	6x033	50+50	2.25	8x030	240	2.08
(encased in ABS plastic)			2x030	240	0.20	4x029	220	0.54	6x028	110	2.04			
			4x030	240	0.50	6x029	220	1.02	6x030	240	0.93			

30 VA			80 VA			160 VA			300 VA			625 VA		
70 x 30mm Regulation 18%			90 x 30mm Regulation 12%			110 x 40mm Regulation 8%			110 x 50mm Regulation 6%			140 x 75mm Regulation 4%		
0.45Kg			1Kg			1.8Kg			2.6Kg			5Kg		
1x010	6+6	2.50	3x010	6+6	6.64	5x011	9+9	8.89	7x013	15+15	10.00	9x017	30+30	10.41
1x011	9+9	1.66	3x011	9+9	4.44	5x012	12+12	6.66	7x014	18+18	8.33	9x018	35+35	8.92
1x012	12+12	1.25	3x012	12+12	3.33	5x013	15+15	5.33	7x015	22+22	6.82	9x026	40+40	7.81
1x013	15+15	1.00	3x013	15+15	2.66	5x014	18+18	4.44	7x016	25+25	6.00	9x025	45+45	6.94
1x014	18+18	0.83	3x014	18+18	2.22	5x015	22+22	3.63	7x017	30+30	5.00	9x033	50+50	6.25
1x015	22+22	0.68	3x015	22+22	1.81	5x016	25+25	3.20	7x018	35+35	4.28	9x042	55+55	5.68
1x016	25+25	0.60	3x016	25+25	1.50	5x017	30+30	2.66	7x026	40+40	3.75	9x028	110	5.68
1x017	30+30	0.50	3x017	30+30	1.33	5x018	35+35	2.28	7x025	45+45	3.33	9x029	220	2.34
			3x028	110	0.72	5x026	40+40	2.00	7x033	50+50	3.00	9x030	240	2.60
			3x029	220	0.36	5x028	110	1.45	7x028	110	2.72			
			3x030	240	0.33	5x029	220	0.72	7x029	220	1.36			
						5x030	240	0.66	7x030	240	1.25			

Why a Toroid?

- * Smaller size & weight to meet modern 'slimline' requirements.
- * Low electrically induced noise demanded by compact equipment.
- * High efficiency enabling conservative rating whilst maintaining size advantages.
- * Lower operating temperature.

Why ILP?

- * Ex-stock delivery for standard 240v range.
- * Fast prototype service available.
- * 3 weeks despatch for special orders.
- * 2 year no quibble guarantee.
- * No price penalty for call-off orders.


Prices including P&P and VAT

VA	Size	£	VA	Size	£
15	0	7.06	160	5	12.17
30	1	7.67	225	6	13.75
50	2	8.90	300	7	14.97
80	3	10.06	500	8	19.60
120	4	10.65	625	9	22.30

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.
Trade - We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 2
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 454778 Telex: 965780

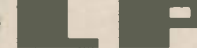For 110V primary insert "0" in place of "X" in type number.
For 220V primary (Europe) insert "1" in place of "X" in type number.
For 240V primary (UK) insert "2" in place of "X" in type number.
IMPORTANT: Regulation - All voltages quoted are FULL LOAD.
Please add regulation figure to secondary voltage to obtain off load voltage.




ELECTRONICS LTD.

IF YOU'RE CRAFTY, YOU'RE BOUND TO PICK UP A LOT OF TIPS AT OUR SHOW



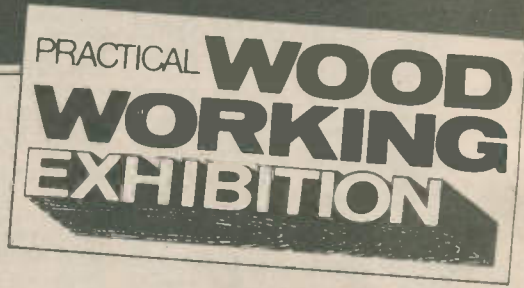WEMBLEY CONFERENCE CENTRE
10-13 JANUARY, 1985
Thursday to Saturday 10am-7pm
Sunday 10am-6pm



Whether you're a craftsman creating fine furniture or a beginner making a simple bookshelf, you'll find everything you could possibly need under one roof.
See the latest ideas and equipment for woodworking. Talk to the experts about timber and finishes.


★ **CRAFT MARKET** See the very latest ideas and equipment for woodworking. ★ **FREE CHRISTIES VALUATIONS** Let Christies value your antiques. An expert will be available at the show, so bring along your interesting pieces, or photographs of them, if you prefer.
Admission prices: Adults £2.50 Children under 16 and Senior Citizens £1.50. Advanced Party Booking for groups of 20 or more. Adults £2.00 Children £1.00 (Plus one free ticket per 20 sold for the organiser or teacher).

Further details from: Practical Woodworking Tickets, Reed Exhibitions, Surrey House, 1 Throley Way, Sutton, Surrey SM1 4QQ

Sponsored by Practical Woodworking Magazine

Cirkit. Making it bigger and better.

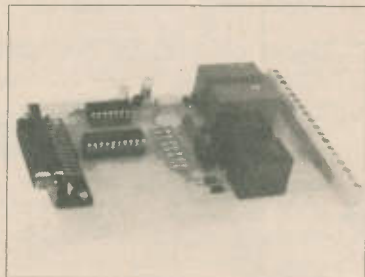Cirkit stock all the components, accessories and tools and the kits you're looking for. Designed and selected to offer the best possible standards at the best possible price.



Centronics Interface

Cirkit Kits

CIRKIT ELECTRONICS TOOL KIT

Contains: 15W Soldering Iron 2 spare bits, heat shunt, solder, pliers, cutter, screwdriver 40-00007 12.00

AUDIO FUNCTION GENERATOR

Versatile waveform generator with sine, triangular and square wave outputs. On board mains PSU 41-01302 27.00

STEREO 40W AMPLIFIER

Single board 40W per channel stereo amplifier 41-01301 38.00

STEREO VU METER

5 LED per channel stereo VU meter for use with stereo amplifiers 41-01401 11.50

5W AUDIO AMP

A very compact audio output stage for use in a wide range of equipment 41-01406 4.60

UNIVERSAL AMP

A universal audio pre-amp with a gain of 10 41-01604 6.45

MONO REVERBERATION UNIT

Single channel, spring line reverb unit to add echo effects to tape recording etc. 41-01602 10.00

TONE GENERATOR AND DETECTOR

Very low distortion tone generator and signal detector for circuit fault finding 41-01603 40.16

10MHz DFM

8 Digit LED digital frequency meter and period measurement 41-01500 54.10

50MHz PRESCALER

Extend the range of the 10MHz DFM to 50MHz 41-01501 8.55

1-5MHz PRE AMP

Low frequency pre-amp and waveform shaper for the 10MHz DFM 41-01502 5.13

70cm PRE AMP

Low noise, miniature pre-amp for the 70cm amateur band 41-01506 4.78

70cm CONVERTER

70cm to 144MHz low noise converter featuring pre-aligned helical filter, schottky diode mixer and low noise transistors 41-01405 21.50

1-30V 1mA-2A PSU

Adjustable 1-30V Power supply with pre-settable current limit from 1mA-2A 41-01600 37.46

5-12V 1A PSU

Adjustable PSU from 5-12V with current protection, 1 amp max output 41-01504 6.45

1-30V 1.5A PSU

1-30 volt adjustable PSU with protected output up to 1.5 Amps 41-01402 10.45

3 DIGIT LED DVM

DVM to read up to 99.9 volts or configured as an ammeter to read up to 9.99 amps 41-01403 17.00

INFRA RED LINK

Single channel IR Link with relay output 41-01300 9.60

TEMPERATURE SENSOR

Thermistor based temperature sensor with relay output 41-01303 6.20

LOCOMOTIVE SOUND GENERATOR

Realistic steam sound and whistle for model railways 41-01304 9.20

LAMP DIMMER

Control lamps and drill speed 41-01305 5.70

WATER LEVEL ALARM

Alarm to indicate high water level or flooding 41-01601 2.70

3 NOTE CHIME

Doorbell chime with adjustable tones 41-01503 7.00

2M PRE AMP


Miniature low-noise MOSFET pre-amp for the 2m amateur band 41-01307 3.91

2M CONVERTER

Low noise 144MHz-28MHz amateur band converter 41-01306 17.35

2M POWER AMP

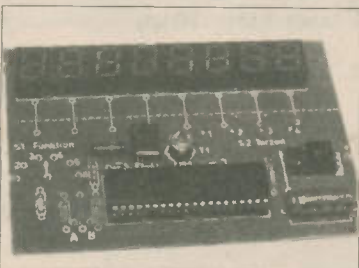20W - 10dB gain - power amplifier for the 2m band. Automatic TX switch over, RX pre-amp, robust construction 41-01404 32.87



10MHz DFM

CRYSTAL CALIBRATOR

Crystal reference calibrator for alignment of receivers, outputs at 4.2, 1MHz, 100, 50 AND 10KHz 41-00801 4.32

CB NOISE SQUELCH

Improves the mutp performance of the majority of CB rigs 41-01605 5.40

CENTRONICS INTERFACE


Connect your personal computer to the outside world via the Centronics printer output 41-01606 22.50

70cm PA

10W Power amp to boost the output of handheld and portable 70cm transceivers 41-01505 33.82

Selected Lines

BBC to Centronics Connect Cable	03-10019	7.25
Dragon to Centronics Connect Cable	03-10017	7.25
C12 Computer Cassette Interface 84 multiplexed Ram Card	21-00012	0.55
Z80A industrial controller	40-84000	59.95
EPROM Eraser 84T	40-82000	54.95
6802 Micro Controller	40-65020	54.95
6802 Micro Controller	40-68020	54.95
PB2720 80dB Piezo Buzzer	43-27201	0.55
10M15A 10.7 Center Freq.	20-10152	2.10
10M08AA 10.695 Center Freq.	20-11152	3.49
FC177 LCD (Freq.)	39-17700	20.00
CM161 LCD Clock	40-80161	8.25
8 x 0.3" IC socket	28-00800	0.12
14 x 0.3" IC socket	28-14000	0.13
16 x 0.3" IC socket	28-16000	0.13
6V KUIT-A Relay	46-80000	0.48
9V KUIT-A Relay	46-80001	0.48
12V KUIT-A Relay	46-80002	0.48
CX120P COAX Relay	46-90120	11.96
CX520D COAX Relay (N-type)	46-90520	26.98
CX540D COAX Relay (BNC)	46-90540	26.98

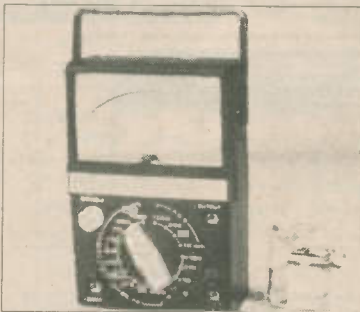

HT-320 Multimeter (20kΩ-V) 56-83201 14.00

Please add 15% VAT to all advertised prices and 60p post and packing. Minimum order value \$5 please. We reserve the right to vary prices in accordance with market fluctuation.

Just send for our catalogue or visit one of our three outlets at:

200 North Service Road, Brentwood, Essex, CM14 5SG;
53 Burfields Road, Portsmouth, Hampshire, PO3 5EB;
Park Lane, Broxbourne, Hertfordshire, EN10 7NQ
Items in stock despatched within 48 hours

To: Cirkit Holdings PLC, Park Lane, Broxbourne, Hertfordshire, EN10 7NQ.
I enclose 85p. Please send me your latest catalogue and 3 x £1 discount vouchers!
If you have any enquiries please telephone us on Hoddesdon (0992) 444111.

Name _____

Address _____

Telephone _____

Area of Special Interest _____
PE2

Cirkit

Bigger Stock. Better Service.

New Winter Catalogue Out Now!

ELECTRONIC SIREN KIT

Produces an extremely loud piercing swept frequency tone from a 9-15V supply. Enable input for easy connection to alarm circuits. Includes 5in. Horn Speaker **£7.90**



Mini Siren
As above, but with a small speaker (instead of horn speaker) for internal use. Complete with box **£4.30**

SECURITY PRODUCTS


Protect your home and property and save by building your own burglar alarm system.



- Stair Mat 23 x 7 in (950 120) **£1.70**
- Floor Mat 29 x 16 in (950 125) **£2.60**
- Tamper-proof connecting block (950 110) **£0.30**
- Door/Window Contacts. Flush mounting, 4 wire. Magnet/switch Per Pair (950 140) **£1.05**
- Window Tape 0.5" wide 50m (950 145) **£2.50**
- Window Tape Terminations Per pair (950 150) **£0.36**
- Key-operated Switch, 1 5A 250V (950 128) **£4.50**
- Passive Infra-Red Detector**
Detects intruder's body heat. Range 10 metres. 12V DC, n/o & n/c contact. (950 135) **£40.00**
- Alarm Control Unit**. 4 input circuits, 2 instant and 2-delayed. Adjustable entry, exit and alarm times. Built and tested. Full instructions supplied. Size: 180 x 130 x 30mm. Supply 12V DC. (950 160) **£26.00**
- Ultrasonic Burglar Alarm**. Self-contained mains or battery powered unit complete with horn and AC adaptor. Impuls for pressure mats and other sensors together with exit/entry delays enable this unit to be used as a complete system. **£45.00 + p&p £2.20**
- BW Horn Speaker**. 5.5 ins. 8 ohm. Ideal for sirens, etc. 2.5m lead and 3.5mm jack plug. (403 148) **£6.15**

IR GARAGE DOOR CONTROLLER KIT

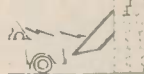For controlling motorised garage doors and switching garage and drive lights on/off up to a range of 40 ft



Lots of applications like controlling lights and TVs, etc. in the home. Ideal for aged or disabled persons. This coded kit comprises of a mains powered infra-red receiver with a normally open relay output plus two latched transistor outputs, battery powered transmitter and opto-isolated solid state mains switch.

KK103 **£25.00**
KK105 Extra transmitters **£10.50**

PANTEC KITS

- PN2** FM Micro Transmitter **£7.50**
- PN3** Stabilised Power Supply **£13.70**
- PN5** 2 x 10W Stereo Amplifier **£14.50**
- PN6** 2 x 40W Stereo Amplifier **£24.95**
- PN7** Pushbutton Stereo Preamp **£12.80**
- PN8** Tone & Volume Control **£13.60**
- PN11** 3w FM Transmitter **£11.95**
- PN13** Single Channel FM Transmitter **£9.80**
- PN14** Receiver for above **£15.50**

TOP QUALITY... TOP SERVICE BOTTOM PRICES!

For FREE CATALOGUE send 9" x 6" SAE - contains full list of stock range all at very competitive prices. Cash with order (except account customers). Access or Barclaycard telephone orders welcome. Add 75p p&p + 15% VAT to all UK orders. Overseas customers add £2.75 p&p Europe, £6.50 elsewhere. Giro No. 529314002. Goods by return subject to availability. Shop open 9am - 5pm (Mon-Fri), 10am - 4pm (Sat). ALL PRICES EXCLUDE VAT



INFRA-RED REMOTE CONTROL KITS




These kits are designed to enable infra-red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The application will determine the interface circuitry between the receiver and the controlled device. General instructions and applications are supplied. The kits are coded and provide a high degree of security and noise immunity.

- MK 18 Transmitter Kit** - for use with MK 11/MK 12 receivers. Requires PP3 battery. Size: 8 x 2 x 13cms. Range approx 60 ft. **£6.80**
- Keyboards for MK 18**
- MK 9 4-way for use with MK 12 **£1.90**
- MK 10 16-way for use with MK 12 **£5.40**
- MK 13 11-way for use with MK 11 **£4.35**
- MK 11 Receiver Kit** - mains powered. Provides 10 latched plus 3 analogue outputs ideal for controlling audio amplifiers, TV or lighting where control of light brightness is required. **£13.50**
- MK 14 AC Power Controller Kit** for (phase) controlling AC loads from MK 11 analogue outputs. eg lamp dimming. **£5.20**

MK 19 Stereo Amplifier Controller Kit - for remote control of bass, treble and volume (or balance) by MK 11. Includes a one of 10 decoder remote channel or input selection. May be connected between the pre-amp and power amp of almost any audio system. **£10.70**


MK 12 Receiver Kit - mains powered with 16 latched or momentary outputs. Latched version is for applications requiring one output on at a time, eg TV channel selection. Momentary type gives an output only during transmission. Lines may be latched as required. **£13.50**

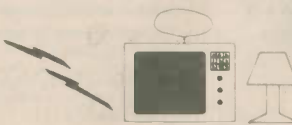MK 15 Dual Latched Solid State Relay for switching mains loads such as lamps, TVs, etc. from the outputs of the MK 12 (momentary). 15 items may be switched independently using 8 MK 15s. Traces (not supplied) switch at mains zero to reduce interference. **£4.50**



COMPONENT PACKS

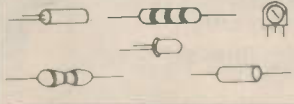- PACK 1** 650 Resistors 47R 10M 10 per value **£4.00**
- PACK 2** 40 x 16V Electrolytics 10 1000µF 5 per value **£3.25**
- PACK 3** 50 x Polyester Capacitors 0.01 1µF 250V 5 values **£5.55**
- PACK 4** 45 Presets 100R 1M **£3.00**
- PACK 5** 30 x Low Profile IC Sockets 8 14 & 16 pin **£2.40**
- PACK 6** 25 Red LEDs (5mm) **£1.75**



BT STYLE PHONE CONNECTORS



- Line Jack Units (Master Unit (first line unit) has bell capacitor and surge arrester)
- Master (flush) (960 110) **£3.00**
 - Master (surface) (960 112) **£3.00**
 - Master (mini surface) (960 113) **£3.50**
 - Secondary (flush) (960 114) **£2.65**
 - Secondary (surface) (960 116) **£2.65**
 - Secondary (mini surf) (960 117) **£3.00**
 - Dual outlet adaptor (960 118) **£4.20**
 - 4-way line cord with plug to spade terminals (960 120) **£2.00**
 - 4-way line cord (960 130) **£0.20 per m**

LCD DIGITAL MULTIMETERS

LOW COST! 10M ohm, 3 1/2 digit, 0.4 in display. Auto zero and polarity, low batt. indication, overload protection. Includes test leads, battery, spare fuse, manual, carrying case.

AC Volts: 0-200-500
DC Volts: 0-2.20-200-1000
DC Current: 0-20m-200mA
Resistance: 0-2k-20k-200k-2M.
Size: 138 x 86 x 36mm. **£25.95**

Professional - 10M, 0.5 in, 3 1/2 digit. Overrange and low battery indication. Overload protection. Includes leads, spare fuse, battery, manual and case. Transistor Checker. Size: 175 x 93 x 42mm.

AC Volts: 0-200-750
DC Volts: 0-200m-2-20-200-1000
DC Current: 0-20u-2m-20m-200mA. 0-10A
Ohms: 0-200-2k-20k-200k-2M. 0-20M. (405 204) **£33.50**



Auto Ranging, 3 1/2 digit 10mm display. Continuity buzzer, low battery, overload and range indication. 10A internal shunt for AC/DC current measurement. Carrying case supplied.

AC Volts: 0-2-20-200-600
DC Volts: 0-0.2-2-20-200-1000
AC Current: 0-200mA, 0-10A.
DC Current: 0-200mA/0-10A.
Resistance: 0-200-2k-20k-200k-0.2M.
Size: 160 x 85 x 29mm. (405 206) **£44.85**

High Sensitivity Temperature Probe. For use with a multimeter to measure temperatures from -50°C to +250°C. Accuracy: 1.5°C @ 25°C, 2°C @ 100°C. Response time (in water), 5 seconds. Includes case, calibrated scale and instructions. (405 220) **£8.50**

MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at preset times over a 7 day cycle. LED display of time and day, easily programmed via 20-way keyboard. Ideal for central heating control (including different switching times for weekends). Battery back-up circuit. Includes box. 18 time settings.



- CT6000K** **£39.00**
- XX 114**. Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays 3A/240V c/o contacts **£3.90**
- 701 115** Additional Relays **£1.65**

ELECTRONIC LOCK KIT

With hundreds of uses indoors, garages, car anti-theft devices, electronic equipment, etc. Only the correct easily changed four-digit code will open it! Requires a 5-15V DC supply. Output 750mA. Fits into standard electrical wall box. Complete kit (except front panel) **£11.50**

KK101 Electronic Lock Mechanism for use with existing door locks and the above kit. (Requires relay. 112V AC/DC coil (701 150)) **£14.95**

HOME LIGHTING KITS

These kits are designed to replace a standard wall switch to control up to 300w of lighting



- TDR300K** Remote Controller Light Dimmer **£14.95**
- MK6** Transmitter for above **£4.50**
- TD300K** Touch Dimmer **£7.75**
- TS300K** Touch Switch **£7.75**
- TDE/K** 2 way extension for above kits **£2.50**
- LD300K** Rotary controlled Light Dimmer **£3.95**

DISCO LIGHTING KITS

DL1000K - This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. **£15.95**

DL21000K - A lower cost uni-directional version of the above. Zero switching to reduce interference. **£8.95**

Optional opto input allowing audio 'beat' / light response (DLA/1) **70p**

DL3000K - 3 channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. **£12.95**

DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (50°C to +150°C) reading 0.1°C. The kit has a sensitivity of 200mV for a full-scale leading automatic polarity and overload indication. Typical battery life of 2 years (PP3). **£15.50**

ELECTRONICS

11-13 Boston Road
London W7 3SJ

ORDERS **01-567 8910** ENQUIRIES **01-579 9794**

01-579 2842 TECHNICAL AFTER 3pm



SAFETY

ELECTRONICS has done much to benefit our way of life and standard of living in all areas from entertainment to safety at sea and in the air. Of course it has also enabled development of more sophisticated weapons and defence systems but that is another story. Our exploration of space is totally dependent on electronics and navigation about our own planet is also now based mainly on high technology.

What a pity then that the modes of transport we all use every day have not benefited more from the introduction of electronics to aid safety. The car you drive may have a computer to show fuel consumption, it may have a talking dash panel or even an engine management computer, but have the electronics been used to improve safety? How many vehicles are fitted with an anti-locking braking system? How often do you see vehicles skidding even on dry roads? How often do the back wheels of unladen lorries lock up when they stop? How many motorcyclists come off in the wet when braking or skid into the back of the car in front?

Admittedly many of the skids that do occur result in no damage or injury but of course some do. Surely it is better to make vehicles safer with an electronically controlled failsafe braking system than to get them talking to you? This is one area where the amateur in electronics can do little himself. We would not encourage readers to modify any


vehicle braking system, so we cannot fit a system to help ourselves.

The sad thing is that the technology and mechanics to perform the necessary tasks has been around for some years. Perhaps the manufacturers feel we will not pay for the extra safety; maybe they do not feel it is necessary? The next time you see a minor skid that could have been dangerous, a motorcyclist fall off, or a lorry stopping slightly sideways just think about what could have gone badly wrong and see if you feel anti-skid braking would be worth another couple of hundred pounds on the already inflated price of a new vehicle in the UK.

LEGISLATION

Maybe you will even think that legislation would be a good thing, even if it might not save as many lives as compulsory seat belt wearing!

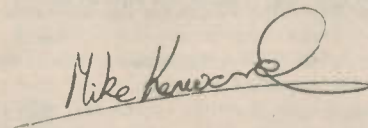Incidentally, the motorcyclist I saw come off this morning was shaken but not badly injured, although his bike was probably a write-off and the car he ran into badly damaged. Think about it if you buy a new vehicle! The extra cost could be worth the time, trouble and headache alone.



Editor Mike Kenward

Secretary Pauline Mitchell

Editorial Tel: Poole (0202) 671191

Advertisement Manager
David Tilleard 01-261 6676

Secretary
Christine Pocknell 01-261 6676

Classified Supervisor
Barbara Blake 01-261 5897

Ad. Make-up/Copy
Brian Lamb 01-261 6601

Queries and letters concerning advertisements to:
Practical Electronics Advertisements,
King's Reach Tower,
Stamford Street, London SE1 9LS
Telex: 915748 MAGDIV-G

Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to **one published project only**.

Components are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Old Projects


We advise readers to check that all parts are still available before commencing any project in a back-dated issue, as we cannot guarantee the indefinite availability of components used.

Technical and editorial queries and letters to:
Practical Electronics Editorial,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG

BACK NUMBERS and BINDERS...

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. Please state month and year of issue required.

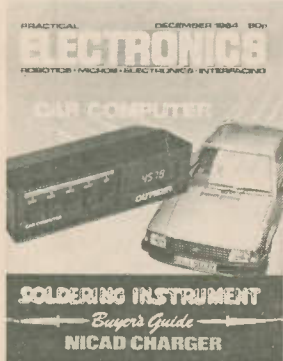Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including postage, packing and VAT.



SUBSCRIPTIONS

Copies of Practical Electronics are available by post, inland for £13, overseas for £14 per 12 issues, from: Practical Electronics, Subscription Department, IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment for subscriptions can also be made using a credit card.

Phone:
Editorial Poole (0202) 671191

We regret that lengthy technical enquiries cannot be answered over the telephone.

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

HIGH COST INSULATION

Most constructors will be painfully aware of the annoying shrink-back properties of insulation, encountered when soldering wires into place. Over the years manufacturers have developed heat-proof insulation materials for specialised cable applications which eventually filter through industry to the home-constructor—and very welcome they are, too. It may surprise you to know, however, just how far, and to what expense, manufacturers will go in order to optimise the insulating properties of the materials they use.

B.I.C.C. for instance has just completed the installation of a new electron beam accelerator plant at its Electronic Cables factory in Cheshire, the cost? A staggering £2.5 million. The facility is considered to be the most sophisticated and versatile of its kind in the Western world. The accelerator produces high velocity electrons which have sufficient energy to penetrate the cable insulation.

Once inside a polymeric insulation, the electrons initiate chemical reactions which lead to the formation of chemical bonds or crosslinks. Increasing the number of crosslinks leads to eventual formation of a three-dimensional network which substantially enhances the physical properties of the insulant.

The most obvious effect of crosslinking is that the material loses its thermoplastic characteristics and becomes a non-melting



thermoset with a better balance of mechanical properties at both high and low temperatures; chemical resistance is also enhanced.

The whole facility is enclosed in 1500 tonnes of concrete for personnel protection during plant operation. The picture shows the plants computer control room.

PATENTLY OBVIOUS

All too often the most worrying aspect for the creator of an original design is, how to protect that idea from those who would copy and exploit it for their own gain. This has been the case since the first inventor brought forth a brainchild, only to stand by helplessly as someone else marketed his idea and made a fortune. The laws governing Patents, Trademarks, Designs and Copyright are complex indeed, without guidance the layman may be forgiven for getting confused. Laurence Shaw's recently reprinted guide can be of great help to inventors and innovators alike.

The *Practical Guide for people with a new idea* is a book which explains in clear language how to protect a new idea, product or scheme and exploit it to the full. Market research, approaching a manufacturer, telling the world about an idea without losing your rights and patenting an invention are all covered together with secret patents.

This publication is available from booksellers at £5.50, or by mail order at £5.95 from The Patent Eye, George House, George Road, Edgbaston, Birmingham B15 1PG. (021 454 2165).

MAGIC LANTERN

Question: If you are exposed to radiation do you glow in the dark? Answer: Of course not. Not unless you are first coated with a phosphor of some kind. It is a useful fact that beta particles from a radioactive source will, when they strike a phosphor such as zinc sulphide, cause light to be emitted from it. Battelle's Pacific Northwest Laboratories are testing a novel application of this phenomenon. Scientists are evaluating a portable runway lamp for setting up landing strips in out-of-the-way places, or during emergencies in which the electricity supply is lost.


The lamp comprises a glass tube, its inside surface coated with a phosphor, and which is filled with tritium gas, the radioactive isotope of hydrogen. The lamp can not be turned off, it simply continues to glow for the twelve years half-life of the gas. Keeping the glass clean is the only maintenance operation required during that time. The quantity of radioactive material used is so minute that it is harmless even if the glass breaks, it is claimed.

During field tests in Alaska pilots reported that they perceived light from the radio-luminescent lamps differently from that of conventional light, and human response now needs to be assessed to find out how useful these lamps may be.

TX TELEVISION/MONITOR

The latest in the TX range from Ferguson is a 14 inch monitor/colour television. It will offer those who can afford a second or even third set a very flexible visual display tool.

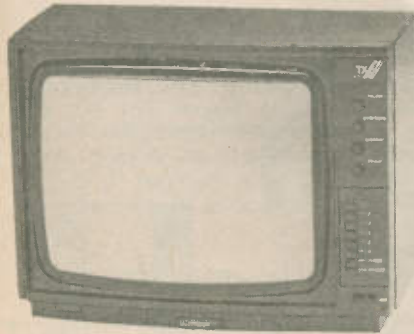The MCO1 has separate RGB, composite video and aerial inputs enabling the user to get the best possible display from broadcast TV, video recorders, teletext and home computers.



Perhaps the most interesting of these options is the ability to directly connect a home computer without the modulation/demodulation problems that occur when using a standard TV set. It must be borne in mind that not all currently available home computers have a direct video output. The machines without this facility have on-board modulation/demodulation and were so designed for use with a visual display medium that most people already possessed—a standard TV set.

The provision of separate RGB, composite video and aerial sockets also allows the home computer, video recorder or game and TV aerial to be connected simultaneously; the set senses the signal selected and switches to it automatically.

A range of special connector leads is available to cover the different home computer options. The set is manufactured in the UK at the company's Gosport plant. It is expected to retail at circa £230.

MARKET PLACE

BT's rumble machine



*It's new from British Telecom,
For paging far-off staff.*

*A little pocket thing,
That could well cause a laugh.*

*You see instead of 'bleeping',
It's been made to 'vibrate'.*

*So you're the only one that knows,
HQ and you have got a date.*

*The waveforms coming through the air,
Will go right through your pants.*

*And trigger-off this rumble-box,
Like a herd of elephants.*

*So if you're in a meeting,
Friends might still get the rise.*

*When they notice that your eyeballs,
Are looking like mince pies.*

HEADS-U-WIN

Ensuring peak response and high-quality reproduction, Electrolube's Video Tape Head Cleaner is a safety solvent designed for use on all magnetic tape heads.

The cleaner loosens and removes accumulated deposits of dirt and tape oxide and dries quickly without leaving any residues on the tape. The cleaner is non-flammable, and non-conductive, it will not damage plastics or rubber.

The solvent comes in handy 110 gram aerosols and is conveniently applied by spraying directly onto the heads and mechanisms. In addition, the cleaner is ideal for spraying onto cleaning tapes and other tape cleaning devices, such as cotton buds or felt and chamois leather sticks.

Available on its own at circa £1.20, or with 25 extra long cotton buds at circa £1.60 from electrical retail outlets.



'BBC's go Bang'

Following a tongue-in-cheek comment from Mike Cook, the Technical Editor of Micro User, several hundred BBC micro owners recently returned their machines to their respective dealers, in the fear that they were about to detonate.

The unfortunate comment was printed in the magazine's problem page as part of a reply to a reader's query regarding an 'error message'. Mr Cook, believing himself to be the subject of a 'wind-up', answered in kind. "Take your computer immediately to the dealer as this error message indicates that it is about to explode."

The manufacturers, Acorn Computers, were not amused, neither was the middle-aged housewife who reportedly surrounded her machine with a bucket of water.

POINTS ARISING...

RING MODULATOR

December, 1984

Alterations to this project must be made as follows:

In Fig. 9 the component marked C35 should be marked R35.

The capacitor C21 should have its +ve terminal connected to R10.

In Fig. 10 the unmarked component mounted between JK1 and JK2 is R47.

A wire link should be connected between JK3 (C25 -ve) and JK4 (C26 +ve).

Countdown ...

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Mike Abbott.

International Light Show Jan. 14-28. Olympia. E6
British Toy & Hobby Fair Jan. 18-Feb. 2. Olympia. D6
Component Fair March 10. Carleton Community Cntr., Pontefract (on A1 to Darrington). F2
London Medical March 12-15. Earls Court. S2
IFSSEC (fire/security) April 15-19. Earls Court, London. S
Cast (Cable & Satellite) April 16-18. NEC, Birmingham F5
Communications April 23-25. Olympia. I
Photoworld April 23-May 6. Earls Court. I
CAD April 26-28. Metropole, Brighton. K2
Fibre Optics & Lasers April 30-May 2. Olympia. E
Custom Electronics & Design Techniques April 30-May 2. E

All Electronics Show/ECIF April 30-May 2. Olympia 2. E
Circuit Technology April 30-May 2. E
Field Service & Repairs April 30-May 2. Olympia 2. E
Automan (manufacturing) May. NEC. T1
Scotelex June 4-6. Royal Highland Soc., ex. Hall, Ingliston, Edinburgh. A1
Personal Computer World Show Sept. 18-22. Olympia 2. M

S2 Fairs & Exhibitions Ltd., ☎ 01-831 8981
D6 ☎ 01-701 7127
E Evan Steadman ☎ 0799 26699
E6 ☎ 058 84 658
F2 Pontefract Am. Rad. Soc. N. Whittingham ☎ 0977 792784
F5 ☎ 01-487 4397
I ITF ☎ 021-705 6707
K2 Reed Exhibitions, Surrey Ho., 1 Throwley Way, Sutton, Surrey
M Montbuild ☎ 01-486 1951
O Online ☎ 01-868 4466
S ☎ 01-387 5050
A1 Institute Electronics ☎ 0706 43661
T1 Cahners ☎ 0483 38085

MODULAR AUDIO POWER SYSTEM

PART 1
M. TOOLEY BA
D. WHITFIELD
MA MSc CEng MIEE

In recent years, improvements in semiconductor technology and, in particular, the introduction of a number of highly versatile consumer integrated circuits and power Darlington stages, have resulted in audio equipment which is both compact and very straightforward. This new series deals with the construction of a variety of modules for use in the custom design of sound reinforcing systems and for public address work generally.

We start, this month, with full constructional details of a 50W power amplifier module. This unit forms the basic building block for several complete designs to be described later. Details of suitable pre-amplifiers, line drivers, tone controls and mixers will also be included; the aim being that of affording the individual constructor the widest possible choice of audio system configuration.

THE 50W POWER AMPLIFIER MODULE

The power amplifier module is electrically robust, is simple to construct, and uses low-cost readily available components. In its basic form, the module is capable of delivering a continuous r.m.s. sine wave output of 50W into a 4 ohm load. The design may be easily modified for operation with alternative output transistors and/or supply rails, as shown in Table 1.

Whilst every effort has been made to avoid the pitfalls, it should be stated at the outset that this project, together with its higher power derivatives, is not for the faint hearted. Indeed, the prototype amplifier was not developed without a few disasters, including four output transistors which literally melted during the testing stage!

An important requirement of this project (and one which readers ignore at their peril) is that the loudspeaker systems employed should be capable of handling the full amplifier output power. However, readers who do not have immediate access to correctly rated loudspeakers need not despair since we shall, next month, be describing a calibrated test load rated at continuous r.m.s. powers well in excess of 100W. A dummy load of this type should prove to be an

invaluable accessory for those wishing to "run-up" the amplifier without destroying their ear drums.

Having started on a cautionary note it is perhaps worth saying that, provided readers carefully follow the setting-up procedure and observe the recommendations concerning heat sinks, component ratings, and supply rails, there should be few, if any, problems.

CIRCUIT DESCRIPTION

A simplified block schematic of the power amplifier module is shown in Fig. 1. The corresponding circuit diagram is shown in Fig. 2. The module consists essentially of a differential input stage followed by a driver and complementary power Darlington output stage. The unit runs from balanced (i.e. separate positive and negative) supply rails with a common OV rail at earth potential.

The input stage is formed by TR1 and TR2 which are connected as a long-tailed differential pair with TR3 acting as a constant current source. The emitter currents of TR1 and TR2 are determined by VR1 which provides a range of adjustment from about 1.5mA to 3.0mA total current. The signal input is applied to the base of TR1, via a switched d.c. blocking capacitor arrangement, whilst negative feedback (both d.c. and a.c.) is applied to the base of TR2. The overall voltage gain of the module is determined by the amount of feedback applied and is approximately equal to the ratio of

Max. r.m.s. output power	Rec. supply rail voltages	Max. rec. heatsink thermal resistance	TR6 (npn)	TR7 (pnp)	T1 sec. rating 2 x
30W	± 30V	4 deg.C/W	TIP121	TIP126	20V/1.5A
45W	± 30V	2 deg.C/W	TIP141	TIP146	20V/2A
80W	± 40V	1 deg.C/W	10K80	11K80	25V/2.5A
			MJ3001	MJ2501	
			2N6058	2N6051	
120W	± 50V	0.5 deg. C/W	MJ11016	MJ11015	32V/3A

Table 1. Output device selection table



**CUSTOM DESIGN
YOUR OWN HIGH
POWER AUDIO SYSTEM**

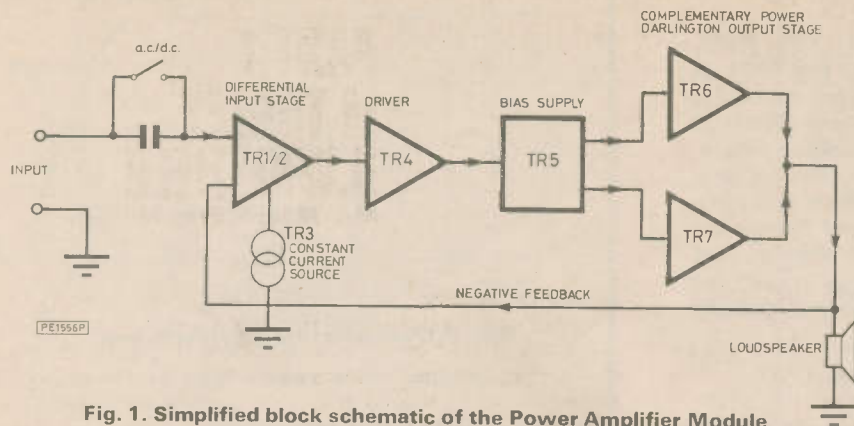


Fig. 1. Simplified block schematic of the Power Amplifier Module

R3 to R4.

Direct coupling of input signals is provided by means of S1 which bypasses the d.c. blocking capacitor, C1. In order to preserve symmetry of the differential stage, the following resistors are made equal: R2 and R3, R5 and R6, R1 and R4 (note that the latter assumes that the amplifier is fed from a relatively low-impedance source).

TR4 forms a conventional common emitter driver stage using an npn transistor. Since the quiescent power

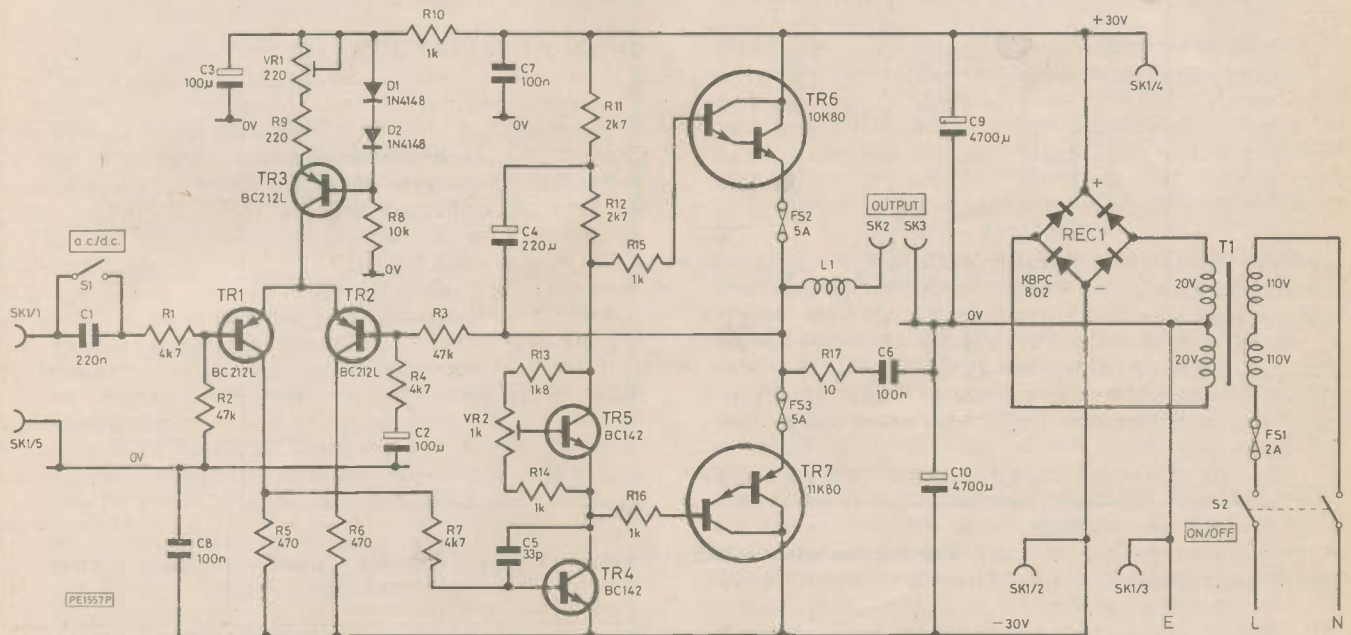


Fig. 2. Complete circuit diagram of the Power Amplifier Module

SPECIFICATION

Maximum power output: (measured at 1kHz)	60W r.m.s. into 3ohm 50W r.m.s. into 4ohm 40W r.m.s. into 8ohm 25W r.m.s. into 15ohm
Minimum recommended load impedance:	3ohm
Voltage gain:	10
Input voltage for max. rated output:	less than 2V r.m.s.
Input impedance:	50k approx.
Recommended source impedance:	600ohm
Total harmonic distortion:	0.05% typical at 30W output into 8ohm
Frequency response (a.c. coupled):	15Hz to 50kHz at -3dB
(d.c. coupled):	d.c. to 50kHz at -3dB
Hum and noise:	less than -85dB related to max. rated output

dissipation for this stage is in the region of 125mW, a metal cased TO5 style device is much to be preferred. Bias for the output transistors is provided by TR5 which acts as a constant voltage source, adjustable by means of VR2. The output stage is a conventional complementary symmetrical arrangement using Darlington pairs, TR6 and TR7. A variety of different devices may be employed in the output stage depending upon output power requirements and the available supply voltage rails. These configurations are summarised in Table 1. The output stage is protected by means of two 5A quick-blow fuses, FS2 and FS3. It should perhaps be mentioned that this form of protection is not completely foolproof but will normally cope with a short-circuited load or failure of one of the output Darlings.

C6 and R17 form a Zobel network whilst L1 ensures unconditional stability of the amplifier when operating into a severely capacitive load. Bootstrap feedback is applied via C4 in order to raise the effective impedance of the collector load for TR4. C5 provides high-frequency roll-off since the bandwidth of the amplifier is otherwise somewhat excessive. The power supply arrangement is fairly conventional and

provides symmetrical supply rails of nominally +30V and -30V.

CONSTRUCTION

With the exception of the power supply (T1, FS1, REC1, C9 and C10) and the output transistors (TR6 and TR7), all components are mounted on a single-sided p.c.b. measuring approximately 65mm x 115mm. The component overlay of the p.c.b. is shown in Fig. 3. Components should be assembled on the p.c.b. in the following sequence: terminal pins, resistors, capacitors, transistors, pre-set resistors, fuse clips, and inductor. The latter component consists of 20 turns of 20 s.w.g. wire wound with an inside diameter of 8mm. Care should be taken to carefully remove the enamel at each end of this component in order to facilitate an effective soldered connection to the p.c.b.

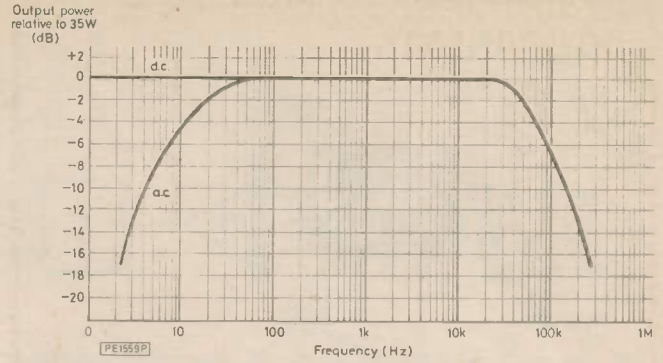


Fig. 5. Frequency response (8ohm load)

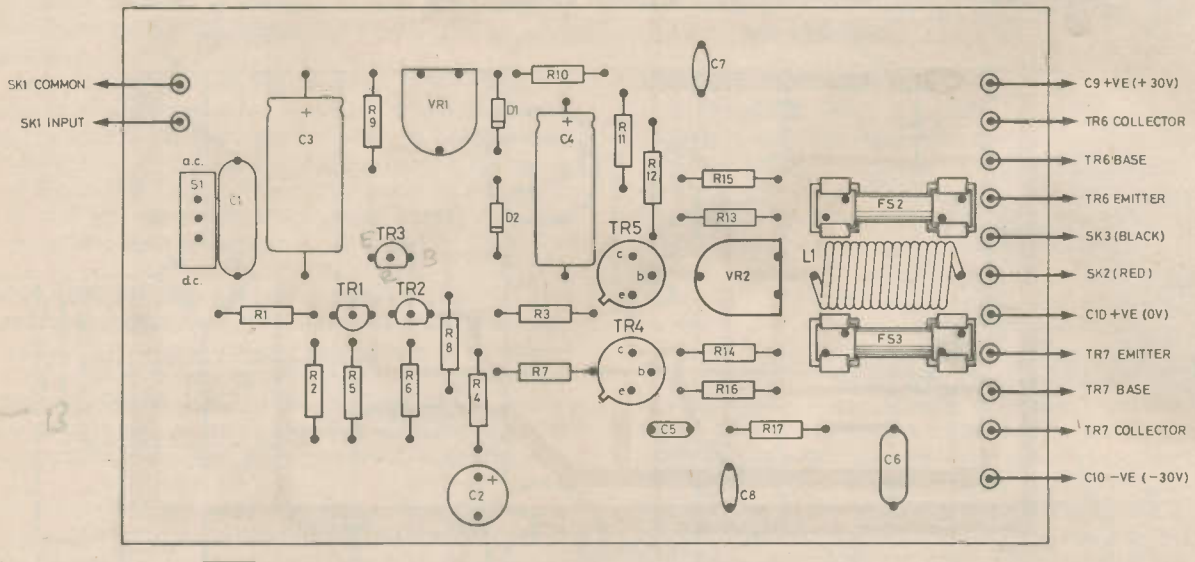


Fig. 3. Component layout of the p.c.b.

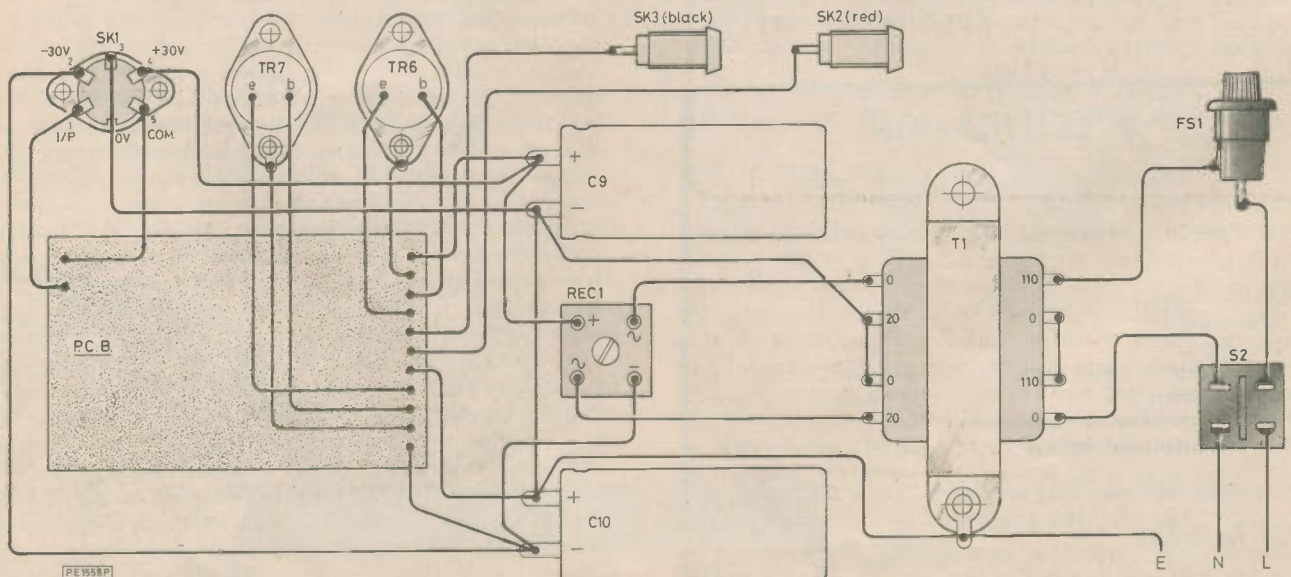


Fig. 4. Wiring diagram for the Power Module

COMPONENTS...

Resistors

R1,R4,R7	4k7 (3 off)
R2,R3	47k (2 off)
R5,R6	470 (2 off)
R8	10k
R9	220
R10,R14,R15,R16	1k (4 off)
R11,R12	2k7 (2 off)
R13	1k8
R17	10 0.5W 5% carbon

VR1 220 min. hor. skeleton pre-set
VR2 1k min. hor. skeleton pre-set

Except where otherwise stated, all fixed resistors are 0.25W 5% carbon.

Capacitors

C1	220n 250V polyester
C2	100 μ 16V p.c. electrolytic
C3	100 μ 63V p.c. electrolytic
C4	220 μ 25V tubular electrolytic
C5	33p ceramic
C6	100n 250V polyester
C7,C8	100n 100V disc ceramic (2 off)
C9,C10	4700 μ 63V can elect. (2 off)

Semiconductors

D1,D2	1N4148 (2 off)
TR1,TR2,TR3	BC212L (3 off)
TR4,TR5	BC142 (2 off)
TR6	10K80 (see Table 1)
TR7	11K80 (see Table 1)
REC1	KBPC802 (200V/6A)

Miscellaneous

p.c.b. s.p.d.t. miniature p.c. slide switch
T1 80VA mains transformer with 220V primary and two secondary windings each rated at 20V/2A minimum (see Table 1)
L1 (see text) p.c. mounting fuse clips (4 off)
FS1 2A 20mm quick-blow mains fuse and holder
FS2 and FS3 5A 20mm quick-blow fuses
Heatsinks (see text)
Silicone impregnated heatsink washers (thermal resistance 0.33 deg.C/W) and bushes (two sets required)
Terminal pins (13 required)
SK1 5-pin 270 deg. DIN socket
SK2 and SK3 4mm sockets (1 red and 1 black)
Mains connector
Printed circuit board (502-01)

The Darlington transistors must be mounted on a substantial heatsink of no more than 1 deg.C/W thermal resistance. To facilitate effective heat transfer the use of silicone impregnated washers is highly recommended (it should be noted that the collector connections of the Darlington power transistors are formed by their respective cases and these will have to be insulated from a heatsink which will invariably be at earth potential).

The encapsulated bridge rectifier, REC1, also requires mounting on a heatsink. The requirement for this heatsink is somewhat less stringent than that needed for the output transistors and a rating of 5 deg.C/W (or approx. 110mm x 110mm 16 s.w.g. aluminium) should prove to be quite adequate. Happily, with this component, there is no need for an insulating washer but a liberal application of silicone grease is recommended before assembly. For most practical pur-

TR1	$\left\{ \begin{array}{l} c \\ b \\ e \end{array} \right.$	-28.4V 0V +0.6V
TR2	$\left\{ \begin{array}{l} c \\ b \\ e \end{array} \right.$	-28.4V 0V +0.6V
TR3	$\left\{ \begin{array}{l} c \\ b \\ e \end{array} \right.$	+0.6V +20.8V +21.4V
TR4	$\left\{ \begin{array}{l} c \\ b \\ e \end{array} \right.$	-1.0V -28.5V -29.2V
TR5	$\left\{ \begin{array}{l} c \\ b \\ e \end{array} \right.$	+1.0V -0.5V -1.0V
TR6	$\left\{ \begin{array}{l} c \\ b \\ e \end{array} \right.$	+29.2V +1.0V 0V
TR7	$\left\{ \begin{array}{l} c \\ b \\ e \end{array} \right.$	-29.2V -1.0V 0V


All test voltages measured with a 20k ohm/V multimeter.

Table 2. Test voltages

poses the rectifier heatsink can simply be provided by the external case or chassis of the equipment. This expedient will, however, not normally apply to the output transistors unless the case is specially designed with heat sinking in mind!

When the p.c.b. wiring is complete, the underside of the board should be carefully checked for solder bridges and dry joints, whereas the component side should be examined, paying particular attention to the correct placement and orientation of polarised components.

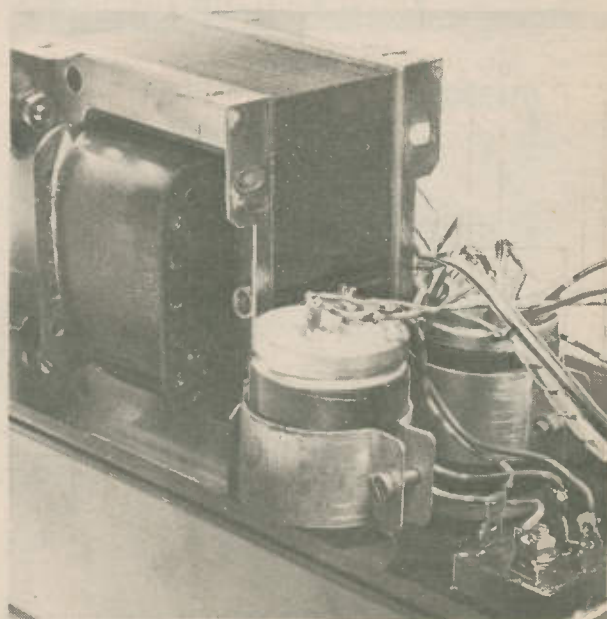Connections to the heatsink mounted components (TR6, TR7 and REC1) and reservoir capacitors (C9 and C10) should be made by short lengths (typically not more than 150mm) of 16/0.2mm (0.5mm²) stranded pvc covered wire. A typical wiring layout is shown in Fig. 4.






Internal view of the Power Amp

INITIAL TESTS AND SETTING-UP

Before connecting to the mains supply and switching 'on' it is important to observe the following procedure:—

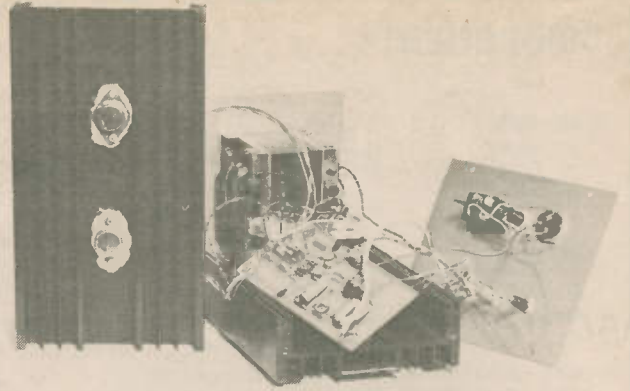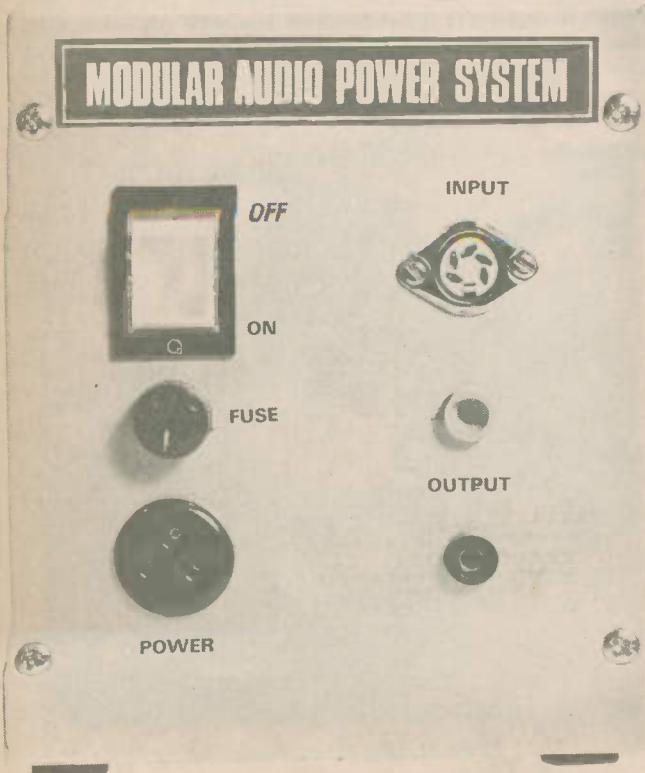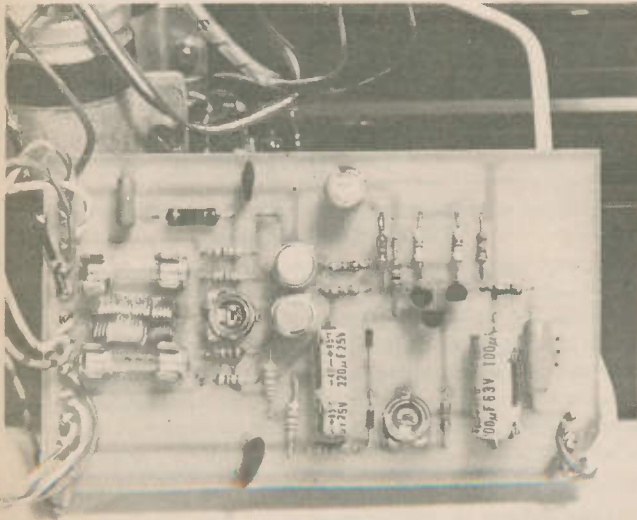1. Adjust VR1 and VR2 so that they are both in the fully clockwise position.
2. Switch S1 to d.c. and temporarily short-circuit the signal input connector, SK1.
3. Connect the loudspeaker (or dummy load described next month). The loudspeaker should have an impedance in the range 4ohm to 16ohm and should be rated for a continuous power dissipation of 50W.
4. Switch 'on' and measure the positive and negative supply rail voltages. These measurements can be most conveniently made using the terminal voltages developed across C9 and C10, respectively. The supply rail voltages, in the quiescent state, should be in the range $\pm 27V$ to $\pm 30V$. If the voltages differ appreciably, or if FS1 blows on switching 'on', the wiring



of the transformer and bridge rectifier should be carefully checked.

5. Switch-off and disconnect from the mains supply. Temporarily insert two 10ohm 1W resistors in place of FS2 and FS3. This can be done quite simply by trimming and folding back the leads of the resistors so that the body of the resistor is gripped firmly by the fuse clips whilst electrical connection is achieved without the need to solder.
6. Transfer the d.c. voltmeter to the output terminals, SK2 and SK3. Reconnect the mains supply and switch 'on'. Adjust VR1 for exactly 0V. If the adjustment has no effect or if the resistors get hot, carefully check the p.c.b. and wiring to the output transistors.
7. Switch 'off' and transfer the d.c. voltmeter to the



10ohm resistor fitted in place of FS2. Switch 'on' and adjust VR2 to produce a reading of 0.2V. Check that a similar reading is obtained across the 10ohm resistor fitted in place of FS3.

8. Switch 'off' and disconnect from the mains supply. Replace FS2 and FS3 and remove the shorting link from SK1. Finally, select normal operation by switching S1 to the 'a.c.' position.

This completes the setting-up procedure and the amplifier is now ready for use. It is advisable to check the adequacy of the heat sinking arrangements by observing the temperature rise of the output transistor after, say, 15 minutes continuous operation at a reasonable output level (i.e. 10W or more). If the rise in temperature is more than 25 deg.C above ambient, the heatsinking should be improved.

NEXT MONTH: We shall provide constructional details of a 100W dummy load and a simple pre-amplifier/line driver.

Spectrum DAC/ADC Board

R.A. PENFOLD

WITH something like a million ZX Spectrum computers now in circulation there are, no doubt, a great many in the possession of electronics enthusiasts who would like to use them in computer based measurement and control applications. One of the ZX Spectrum's main shortcomings is a lack of built-in interfaces, and there are no ports ready fitted to the machine that are suitable for applications of this type. However, it is quite easy to fit interfaces onto the expansion port, and an analogue interface is one of the most useful from the electronics enthusiasts' point of view.

The port featured in this article gives both analogue-to-digital and digital-to-analogue conversion. Both have 8 bit resolution, which is more than adequate for most practical applications. The analogue output has an output voltage range which is adjustable from 0 to 2.55 volts to about 0 to 10 volts, but with additional circuitry the output voltage range could easily be converted to any desired span within reason. The analogue input has adjustable sensitivity, with the full scale value variable from 2.55 volts to about 25 volts. Again, with suitable additional circuitry practically any input voltage range could be accommodated. The maximum rate of conversion is guaranteed to be no less than 66000 per second, and in most cases in excess of 100000 per second can be achieved. Even the guaranteed rate is fast enough for most high speed applications such as digitising audio signals.

SYSTEM OPERATION

The block diagram of Fig. 1 helps to explain the overall way in which the unit functions. The digital-to-analogue converter is the more simple of the two converters. This consists basically of a precision 2.55 volt reference source, a resistor network (known as an R-2R network) and eight electronic switches. The electronic switches are controlled by the eight

digital inputs, and when activated they connect the precision reference source through to the output via some or all of the resistors in the R-2R network. Things are arranged so that each input, when set high, causes the output to be incremented by the appropriate amount. The operation of this type of converter has been covered in past issues of this magazine, and will not be considered in more detail here.

In order to drive the DAC from the data bus of the Spectrum an 8 bit latch is needed, so that data written to the converter can be stored in the latch and used to drive the inputs of the converter. The converter then gives a continuous output, and ignores signals on the data bus that are intended for other devices. The converter used in this project has a built-in data latch, and it can therefore be fed direct from the computer's data bus. An address decoder circuit provides the latching pulse when data is written to the converter.

The DAC has a 2.55 volt reference source, which sets the maximum output voltage at the same figure. This gives a nominal 0 to 2.55 volt output range in 10 millivolt (0.01 volt) steps. A variable gain amplifier enables higher maximum output voltages to be obtained, up to a maximum of a little over 10 volts. Of course, with a higher maximum output voltage there are still only 256 different output levels, and the output increments in steps of more than 10 millivolts. However, for most applications, such as motor speed controllers and even audio applications, the resolution of an 8 bit converter is at least adequate. The amplifier gives the unit a low output impedance, but without additional buffering output currents of no more than a few milliamps should be drawn.

The analogue-to-digital converter is of the successive approximation type. This incorporates a digital-to-analogue converter which is driven by a fairly complex control logic circuit. The eight outputs of this control circuit constitute the


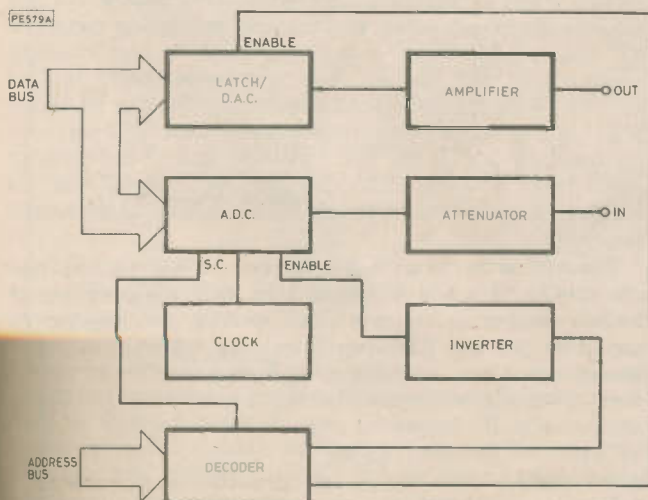


Fig. 1. Block diagram

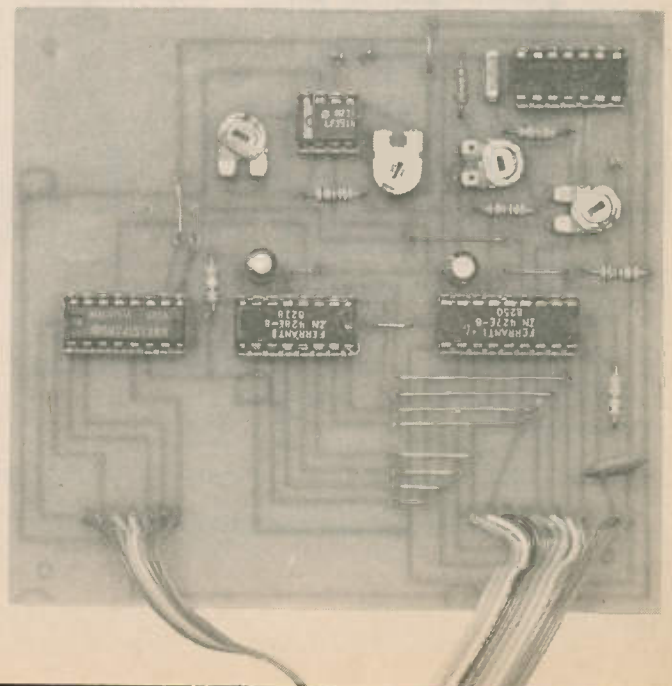

output of the ADC. The output of the DAC is fed to one input of a comparator, and the input signal is fed to the other input of the comparator. When a trigger pulse is received at the "start conversion" input the most significant bit is set at one, but the other bits are all set at zero. If the output from the DAC is at a higher potential than the input signal the most significant bit is left at one, otherwise it is reset to zero. On the next clock cycle bit 6 is set to one, and, as before, it is either left at one or reset to zero depending on whether or not the output of the DAC is at a higher voltage than the input signal. On the next clock cycle bit 5 is set to one, and the process is repeated with this bit. In fact the same process is used for all eight bits, and at the end of this procedure the 8 bit binary number fed to the DAC is a valid digital representation of the input voltage. This method is reasonably fast, with the conversion taking no more than nine clock cycles, but successive approximation converters are reasonably inexpensive.

The device used in this project does not have a built-in clock oscillator, and a simple C-R oscillator is used to provide the clock signal. The "start conversion" pulse is provided by the address decoder. The converter provides its output via an 8 bit buffer which has three-state outputs, and it can therefore be connected direct to the Spectrum's data bus. The "enable" pulse for the outputs is obtained from the address decoder, but an inverter is needed to give a signal of the right polarity. The converter has a nominal full scale sensitivity of 2.55 volts, but a variable attenuator at the input of the unit enables this to be reduced somewhat if required.

CIRCUIT DESCRIPTION

The full circuit diagram of the Spectrum Analogue Board appears in Fig. 2.

All the address decoding is carried out by IC3 which is a 74LS138 3 to 8 line decoder. The Spectrum has a Z80A microprocessor, but it uses a non-standard method of input/output mapping. The general scheme of things is to have the address lines normally high, with one of the lower lines being taken low to activate an input/output device. Some of the upper address lines are occasionally used to provide additional information to an input/output device. This leaves address lines A5 to A7 free for user add-ons. In this case A5 and the IORQ lines are fed to the negative enable inputs of IC3, and A5 must be taken low when reading from or writing to either section of the port (the IORQ line automatically goes low when a BASIC IN or OUT instruction is used).

The three main inputs of IC3 are fed from the read (RD) and write (WR) lines plus address line A6. This gives four usable outputs from IC3, two when reading and two when writing (four outputs are always high since the read and write lines never go low simultaneously). This is adequate for our purposes as only two write outputs and one read output are needed in this application. When writing data to the DAC the instruction OUT 65439,X is used, where X is the value written to the converter. This takes the write and A6 lines low while the value written is present on the data bus, giving an output pulse from output 2 (pin 13) of IC3. Other addresses can in fact be used, but it is best to use 65439 as this places the address lines apart from A5 and A6 high, so that unwanted operation of any internal input/output circuits is avoided.

IC1 is the DAC device, and this is the popular Ferranti ZN428. It has an integral 2.55 volt reference source, but this requires discrete load resistor R1 and decoupling capacitor C1. IC4 is an ordinary operational amplifier non-inverting mode circuit, and this amplifies and buffers the output of IC1. VR1 enables the closed loop voltage gain to be varied from unity to about 5 or so, but in practice the +12 volt supply used for IC4 limits the maximum output potential to about 10 or 11 volts. VR2 is the offset null control, and this is adjusted to trim the minimum output voltage of the unit to zero volts.

The ADC is based on IC2 which is a Ferranti ZN427. Like the ZN428, this has a built-in 2.55 volt reference source which requires a discrete load resistor and decoupling capacitor (R3 and C2 respectively). R1 is part of the high speed comparator, and this is fed from a negative supply so that comparator will respond properly to voltages right down to zero volts. R7 biases the input of IC2 to the earth rail and VR3 plus R5 are used to provide a small positive bias which gives improved accuracy at low input voltages. VR4, together with the input resistance of the circuit, acts as a variable attenuator.

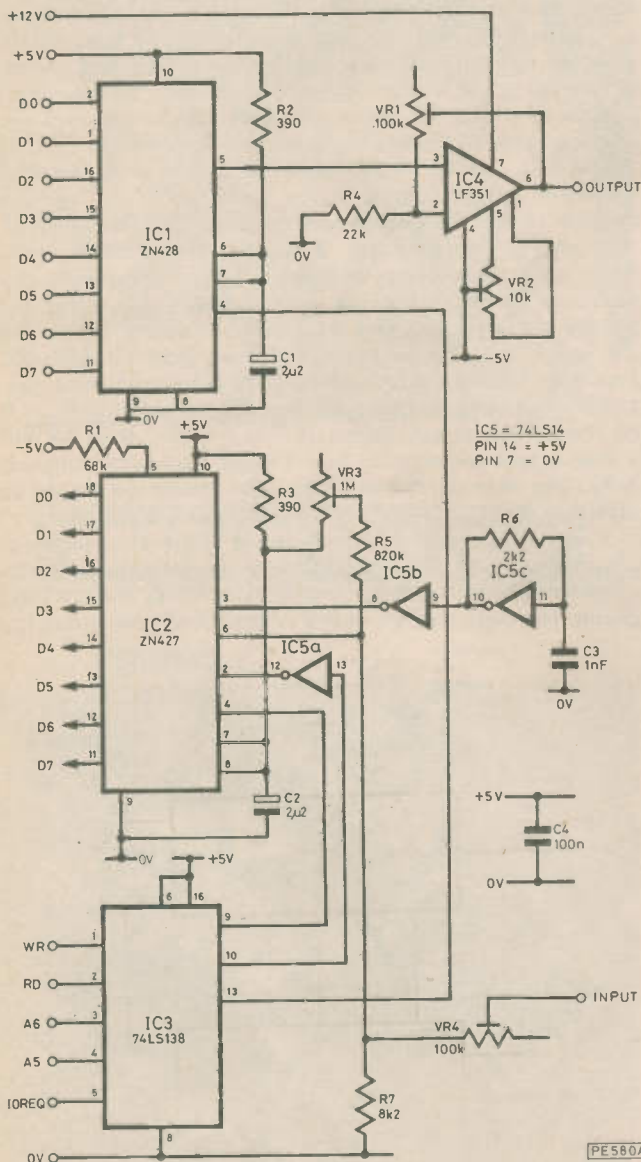


Fig. 2. Circuit diagram of the DAC/ADC board

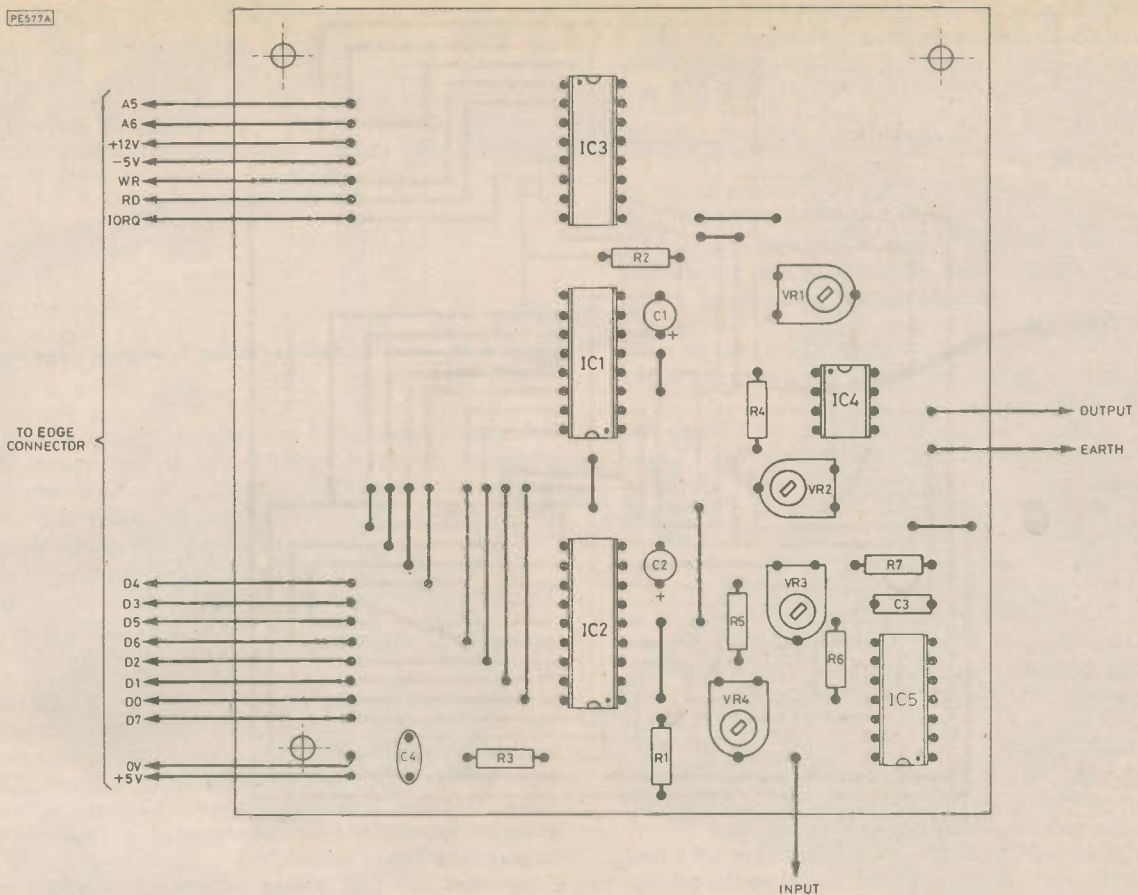


Fig. 3. Component layout of the p.c.b.

COMPONENTS . . .

Resistors

R1	68k
R2, R3	390 (2 off)
R4	22k
R5	820k
R6	2k2
R7	8k2
VR1, VR4	100k 0.1W hor. pre-set (2 off)
VR2	10k 0.1W hor. pre-set
VR3	1M 0.1W hor. pre-set

All fixed resistors are 0.25W 5% carbon

Capacitors

C1, C2	2 μ 2 63V radial elect (2 off)
C3	1nF carbonate
C4	100nF ceramic

Semiconductors

IC1	ZN428E
IC2	ZN427E
IC3	74LS138
IC4	LF351
IC5	74LS14

Miscellaneous

Printed circuit board (502-02)
 2 x 28 way 0.1 inch pitch edge connector
 8 pin d.i.l. i.c. socket
 14 pin d.i.l. i.c. socket
 Two 16 pin d.i.l. i.c. sockets
 18 pin d.i.l. i.c. socket
 Ribbon cable, wire, Veropins, solder, etc.

IC5 is a 74LS14 hex inverting Schmitt Trigger, but in this circuit only three sections of IC5 are utilised. One of these (IC5c) acts as the clock oscillator in conjunction with feedback resistor R6 and timing capacitor C3. IC5b merely acts as a buffer at the output of IC5c. The clock frequency is approximately 600kHz, which is the maximum guaranteed clock frequency for the ZN427. However, with most devices a substantially higher clock frequency is quite acceptable, and where high operating speed is essential using a somewhat lower value for C3 to give a higher clock frequency of up to about 1MHz should give satisfactory results.

The "start conversion" pulse is taken from output 6 (pin 9) of IC3, and is generated using the instruction "OUT 65503,0" (the value written can be any valid quantity since the pulse is obtained direct from the address decoder and not from the data bus). The port is read using the instruction "IN 65503". This gives a negative pulse from output 5 (pin 10) of IC3, but this is inverted by IC5a to give the required positive pulse to IC2.

At least nine clock cycles must be allowed to elapse between sending the "start conversion" pulse and reading the port, to ensure that the circuit has had time to complete the conversion. There is no problem in BASIC since the slow speed of this language means that the conversion will always have been comfortably completed before the port is read. The situation is different when using machine code, and it may then be necessary to use a delay loop to prevent a premature reading of the converter from being taken. The ZN427 has an "end of conversion" status output, but no means of reading this have been included in this unit, and as

the length of time taken for a conversion is virtually constant a delay loop is a perfectly practical way of doing things.

The circuit requires +5, +12, and -5 volt supplies. These are all provided by the Spectrum from its expansion bus, and no other power source is required.

CONSTRUCTION

The component layout of the printed circuit board is shown in Fig. 3. There are a number of link wires and it is probably best to fit these first. 22 s.w.g. tinned copper wire is suitable for the links. None of the integrated circuits are MOS types, but it is advisable to use sockets for these, especially in the cases of IC1 and IC2 which are not the cheapest of devices. The integrated circuits do not all have the same orientation, so be careful to fit them onto the board the right way round.

Connection to the Spectrum is via a piece of 17 way ribbon cable about 0.5 metres long. It is unlikely that 17 way cable will be available, but it is easy to cut down a piece of 20 way cable to the required number of ways. Connection to the board should not prove to be difficult provided the end of each lead first has a small amount of insulation removed and is tinned with a small amount of solder. A 2 by 28 way 0.1 inch edge connector is needed to make the connections to the expansion bus of the Spectrum. Suitable connectors complete with a polarising key are now readily available. Fig. 4 gives connection details for the edge connector.

ADJUSTMENT

Connect the unit to the Spectrum prior to switching on. The Spectrum should then operate normally — switch off immediately and recheck all the wiring if it does not.

Assuming all is well, adjust the DAC first. Set VR1 and VR2, at a roughly midway setting, and then type the following command into the computer:—

```
OUT 65439,0
```

This should give a low output voltage from the unit, and by adjusting VR2 it should be possible to trim the output potential to precisely zero volts. Next type into the computer the command:—

```
OUT 65439,255
```

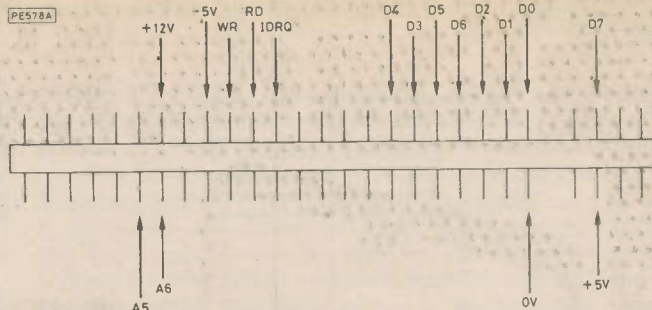


Fig. 4. Connection details for the Spectrum edge connector

An output potential of around 7 to 8 volts should then be obtained. By adjusting VR1 any desired maximum output voltage of between 2.55 volts and about 10 volts or so can be set. Repeat this procedure a couple of times to make sure that everything is set up as accurately as possible.

To check the ADC and facilitate its adjustment type in the following short test program:—

```
10 OUT 65503,0
20 PRINT IN 65503
30 GOTO 10
```

When the program is run it should return a series of very low readings (0 or 1). Set VR4 at maximum resistance (fully counterclockwise), VR3 at a midway setting, and connect an input voltage to the unit that is equal to the desired full scale value. This should be in the range 2.55 to 25 volts. Run the program and set VR4 just far enough in a clockwise direction to give returned values of 255.

In order to adjust VR3 an input voltage that produces 5 millivolts at pin 6 of IC2 should be applied to the circuit. In other words an input potential that is 1/510th of the full scale input voltage is required. VR3 is then adjusted to give a series of reading that (more or less) alternate between 0 and 1. It is not essential to carry out this procedure, and accurate results will be obtained if VR3 is simply set for about half maximum resistance. ★

BAZAAR

SWOP Brothers EP44 computer printer/typewriter RS232 for oscilloscope. Mr. Small, 8 Cherrytree Road, Chinnor, Oxon.

WANTED Texas Microprocessor TMS 1000. Please write to: Abbass Rezaei, PO Box 62, Najafabad, Isfahan, Iran.

FREE—sacks of old components. Mostly TV/valves, to be collected in Oldham. Details: 0923 20751, Mr. V. R. Halsall.

FOUR pairs matched boxed speakers, £8 per pair. T. A. J. Cooling, 4 Norfolk Road, East Ham, London E6 2NJ.

WANTED Manuals for Cossor oscilloscope type 1035, and Harley oscilloscope type 13A. M. O. A. Chari, Ladersattravagen 97 3 Tr, 175 70 Jarfalla, Sweden.

PAL: information on PCBs making, from amateur and experts. A. Larry, 56 Becher Street, Derby DE3 8NN.

UK101 software for sale or swops. Send for list of programs. Mr. P. Hale, 31 South Road, Stourbridge, West Midlands DY8 3YA.

'NIGHTRIDER' car lights sequencers, drives nine channels vari-speed. Easy wiring all negative-ground cars £40 complete. Mr. S. M. Budzinski, 16 Laburnum House, Malpas Road, London SE4 1BL.

SURPLUS to requirements MC6809E, SN74LS783 Synchronous address multiplexer chips. £4.00 each. 10+ £35. SN74LS783 data £2.50. Mr. N. E. Spiers, 114 Green Way, Tunbridge Wells, Kent TN2 3JN.

CLEARTONE graphic equaliser (battery) 7 channel mono, with master volume control. New £22 inc. p&p. F. C. Smith, 283 Leeds Road, Newton Hill, Wakefield WF1 2JQ. Tel: 0924 374122.

10 x 8255A £70 the lot or £8 each. Also printer leads for Dragon 32, BBC £9.95 each. R. Vowles, 3 Orchard Way, Uxbridge, Middx. UB8 2BN. Tel: 0895 54720.

WANTED two SN76001 i/c as used in the Heathfield TV. Mr. Kendall, 4 Howlets Terrace, Chelmondiston, Ipswich IP9 10X.

5 x 7 dot Matrix printer 7 colours: 80 cols. parallel interface adjustable tractor feed VGC £220 o.n.o. S. Walker. Tel: 0865 750600 evenings.

CAR battery voltage monitor — grades any car. As new in immaculate condition £3.45. Russell Oakes, 32 Wigan Road, Winstanley, Wigan, Lancs. WN5 7XS.

COPIES available from private collection early service sheets radios TVs etc. £1 + large SAE. State make, model. Maurice Small, 8 Cherry Tree Road, Chinnor, Oxon. OX9 4QY.

HAMEG oscilloscope HM203-4 dual beam 20MHz with probes £195. Tel: Southampton 557386. Mr. D. Couchman, 8 Grosvenor Gardens, Southampton.

OSCILLOSCOPE Heath 10-4555 £150 one also other instruments P.C. bridge etc. Offers, good condition, sold separately. Mr. A. Ewing, 9 Croft Crescent, Markinch, Glenrothes, Fife KY7 6EH, Scotland.

WANTED AY-3-1270 linear i.c. or RS-3-1270. Mr. J. F. Wilson, 233 Broomlee Close, Newton Aycliffe, Co. Durham. Tel: Aycliffe 312130.

WANTED two track record head for B & O record 1800 RTOR deck. Mr. C. Bressington, 17 Station Road, Ystrad Mynach, Mid-Glamorgan. Tel: 0443 813005.

EIGHT Philips LVC 150 2 1/2 hr. video tapes. Hardly used. Offers plus postage. Mr. L. T. Hill, 14 Rothesay Terrace, Bedlington, Northumberland. Tel: Bedlington 825967.

WANTED data or specimens of early transistor types. Good prices paid. Write for full details: Mr. Andrew Wylie, 18 Rue de Lausanne, 1201 Geneva, Switzerland.

MICROSYNTH Synthesiser built and tested with speaker and homemade stand £150. 8 Stourton Road, Witham, Essex. Tel: Witham 514556.

COMPONENTS transistors mainly OC/AC/BC, capacitors, resistors, chips, pots, relays, motors and other. 16 lb. £20. Mr. Turner, 4 Mill Fields, Newtown, Powys. Tel: 0686 27862.

WANTED service circuit diagrams Sugden C51 A51 purchase hire to copy. Good price paid. Richards, Maesyffynnon, Caehopkin Road, Abercrave, Swansea. Tel: 0639 730629.

Tandy® Top Value In Test Equipment



£19⁹⁵

[A] 25-Range Folding Multimeter. Features include fuse and surge-absorber protection, banana-type probe jacks and 4" 3-colour mirrored meter with automatic shunt protection (when folded shut). DC Volts: 0 to 1200. AC Volts: 0 to 1200. DC Current: 0-60µA, 3-30-300 mA. Resistance: 0-2-20-200K-2 megohms (centre scale 24). dB; -20 to +63 dB. Requires "AA" battery. 22-211 £19.95

Select the Function and It
Selects the Range
Automatically



£64⁹⁵

- Automatic Power Off When Case Is Shut
- Automatic Polarity

[B] Folding LCD Multimeter With Autoranging. Features extra large 1 1/16" non-glare display with adjustable viewing angle, a "beep" indicator for quick continuity testing, and zero-ohms adjust for super-accurate low resistance measurements. DC volts to 1000. AC volts to 500. Up to 10 amps AC and DC. Resistance to 2 megohms. Open: 107 1/8 x 4 5/8 x 1 1/2". Requires two "AA" batteries. 22-193 .. £64.95

Transistor Checker and Digital Logic Probe




£9⁹⁵

[A] Dynamic Transistor Checker. Makes Go/No-Go tests on small-signal and power types and allow you to match similar transistors. Indicates relative current gain, "opens" and "shorts". Requires "AA" battery. 22-025 £9.95

£12⁹⁵

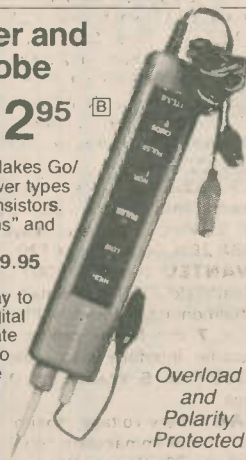[B] Digital Logic Probe. The fast way to "peek inside" TTL, LS and CMOS digital circuits. Colour-coded LEDs indicate high, low or pulsed logic states (up to 10 MHz). Minimum detachable pulse width: 50 ns. 36" leads with clips obtain power from circuit under test. Low current drain. 22-302 £12.95



Overload
and
Polarity
Protected

Reference Books



[A] Semiconductor Reference Guide. 1985 edition! Exclusive cross-reference and substitution section lists over 80,000 types. 276-4008 £3.49

[B] Getting Started In Electronics. The perfect introduction to the exciting world of electronics. Learn to build your own circuits. 128 pages. 276-5003 £2.49

[C] Timer IC Mini-Notebook. An excellent reference and hobby book. Large schematic diagrams. 32 pages. 276-5010 99p



Take A Look At Tandy, Today!

Visit your local store or dealer and see these and many more bargains. We service what we sell - over, 2,800 exclusive lines!

See Yellow Pages For Address Of Store Nearest You




Ask about
Your Tandy
Personal Charge
Card Today!

OVER 9,000 STORES & DEALERSHIPS WORLDWIDE

Prior to this advertisement, all quoted regular prices have been charged during the last six months at the Tandy Store, Tameway Tower, Bridge Street, Walsall, West Midlands. WS1 1LA.

Known As Radio Shack In The U.S.A.

Prices may vary at Dealers
Offers subject to availability



INDUSTRY NOTEBOOK

By Nexus

Outlook

Everyone in business breathed a sigh of relief once the US presidential election was over. The two-year run-up is almost unbearable for its unsettling effect.

All indications are that 1985 will be a good, though possibly hard year for the electronics industry. In 1983 the number of small companies starting up provided a net gain of 47,000. The 1984 figures, not yet available, are expected to beat this record and there is no reason why 1985 should be worse. A significant number of the new start-ups will be in or associated with the electronics industry.

Foreign investment in the UK continues at a high level. The prolonged miners' strike was apparently seen overseas as a one-off out-of-character industrial relations problem and not typical of the 'new realism' in British industry. In any case no foreign companies would want to invest in coal mining and potential investors may be impressed by the relative ease with which British industry carried on through what was intended to be a crippling exercise.

Expansions and new starts planned last year will begin to take effect. If we look at Scotland's Silicon Glen there are now nearly 300 electronics companies employing more than 40,000 people. Inward investment since the *Locate in Scotland* agency was founded in 1981 has now topped £1,000 million, most of it finding its way into high-tech projects. And substantial investment is similarly going into other areas. Even so they will not create many new jobs, one recent estimate being for 10,000 in the electronics industry this year.

Intense competition in personal computers will force prices down so intending buyers would probably profit by delaying purchase. Alternatively, prices could stabilise but the product improved in the classic 'more-bits-per-buck' context. But despite all the difficulties it will still be possible to score well in the consumer market as proved by Alan Sugar's Amstrad whose pre-tax profits topped £9 million in its last financial year.

Information Technology

Information Technology which seemed so novel (although hardly new) only three years ago has now become accepted as the norm and no more exciting than radio or television. Some pessimists are already saying that Britain has been losing ground in this growing sector of industry. Their fears are based on the increase in imported equipment compared with indigenous production.

At the higher levels of the technique the Alvey programme is now gaining momentum. Two new major contracts were awarded towards the end of last year. One carries the painfully contrived acronym of ADMIRAL derived from Advanced Mega Internet Research for ALvey. The other is merely called the Speech Recognition Project.

The ADMIRAL contract is a £3 million joint venture being coordinated by GEC Research Laboratories. Partners are University College, London, The University of London Computer Centre and British Telecom Research Laboratories.

The system will link local area networks (LANS) through a 'mega' internet overlay to produce a single large system of data networks. The key feature is to allow high speed intercommunication between dissimilar equipment. It appears to be a feature of part of the Project Universe programme originally initiated by the Department of Trade and Industry and later transferred to the Alvey Directorate.

The voice recognition project is funded with £2 million and is centred on British Telecom Research Laboratories with collaboration from Cambridge University and Logica. Although most schoolchildren are acquiring keyboard skills it is also recognised that speech is the most natural form of communication between people and the same applies between people and computers.

Present voice recognition systems are primitive and generally respond only to single-word voice commands. It is hoped to expand into true verbal dialogue between person and computer so that anyone who can talk can, for example, find what is required from a data base without necessarily having any keyboard skill.

Time for Schools

It is heartening to see that schools are now to be networked through The Times Network for Schools (TTNS) which will give any school access to more than 200,000 pages of information by the end of the year. Secondary schools of which there are 6,500 will be first to join, followed by 27,000 primary schools.

Future plans exist to network British schools to those on the continental mainland. Joining the network will be optional but the fees are modest and the scheme should prove popular and exciting.

Then we have the proposal for a university devoted entirely to information technology. It has the backing of a host of leading electronics companies but students

will have to pay fees to make the university self-financing.

Fears have already been expressed by egalitarians that the university will be anti-social because it will create an elite of the already advantaged who can afford the fees. Nonsense, of course. We need more, not less, centres of educational excellence.

Improvisation

I remember at a press conference organised by a Ministry of Defence electronics establishment asking how we would get on in a real war when the time scale of equipment development stretched over a period of years even when the equipment was comparatively simple. I had in mind the very few weeks which elapsed in 1940 between the alarming discovery that the Germans were using magnetic mines and the countermeasure (degaussing of ships) devised and implemented. And this was only one example of many rapid developments of that war.

I contrasted this with over 10 years of development of the Clansman radio system before it came into service. I was not very impressed with the reply which was more or less that we would probably muddle through as we always had done in the past.

My confidence has now been restored (well, almost) by Alfred Price in his new book 'Harrier & Sea Harrier at War', published by Ian Allan Ltd. In it he describes 'Blue Eric', an electronic countermeasure system needed urgently for the Falklands war. If Harriers were to be operationally successful in the South Atlantic they would need self-protection against Argentine radar installations.

The threat was evaluated from normal military intelligence which already had details of the characteristics of radar equipment in service with Argentine forces. Existing electronic warfare pods (e.g. for Tornado and Buccaneer) were too large and heavy for the Harrier so it was decided to use elements of the Sky Shadow equipment and fit them in a modified gun pod which would meet the weight and size requirements as well as the jamming capability.

Marconi Defence Systems were prime contractors and completed the design, testing and delivery of operational units within 15 days instead of an estimated two years at normal pace and at a quarter of the cost.

Blue Eric (named after its MOD project officer Squadron Leader Eric Annal) was never used in the Falklands. When the EW-equipped Harriers arrived they were grounded for four days by bad weather and by the time they got airborne the conflict was virtually over, the Harriers then being used for front line ground attack where the radar threat was negligible or non-existent.

While it is comforting to know that the improvisational skills of yesterday have not been lost, one is still left wondering why an EW pod for Harrier was not already available and why, in peacetime conditions, equipment development times are so long and the cost so great.

Microwriter...

The Principle and the Product

Tom Gaskell BA (Hons) CEng MIEE

THE electronics industry is one of extremely rapid change. New products, ideas, and standards spring up continually, promoting a continuous state of flux and development. As a fairly young industry it is successful in discarding old and outdated principles in favour of newer, more beneficial ones; if change can be shown to be worthwhile in any specific situation, then that change is almost invariably made.

It comes as somewhat of a surprise, therefore, that for the production of documentation, text, correspondence, and computer programs, the primary means of interface between the human being and the machine is still a QWERTY keyboard. QWERTY is the standard layout of typewriter keys which was devised very many years ago with the principle intention of *Slowing Down* the typist to prevent jamming of the mechanism. In this age of mechanical sophistication and electronic keyboards the same requirement is no longer true since we can easily prevent jamming by other means. Hence, we are left with a legacy from a bygone age. The QWERTY layout is slow and complex to learn, with months of training being required before any proficiency is achieved. For many people such training is impractical, so they are reduced to 'two finger' typing, which is usually a slow and frustrating exercise.

A NEW IDEA

When a company brings-forth a new idea for entering text into machines, it is bound to attract considerable interest. A few years ago a device called the 'Microwriter' appeared. It is a small, self-contained machine with only six keys, which is used with one hand only. The Microwriter company has been producing these devices in modest quantities ever since, and has recently started to advertise and promote the product in a more aggressive way, with various options and accessories now available.

WHAT IS A MICROWRITER?

A Microwriter is no less than a battery powered portable word processor. It is just a little larger than a paperback book and has very few controls—some connectors, an ON/OFF switch, a liquid crystal display, and six keys. It is placed on a desk or held in the left hand, and typed on with the right hand. (As yet there isn't a left handed version since there would be problems connected with the way that the 'alphabet' of letter shapes are formed, as we shall see later.) The Microwriter can communicate over a bi-directional RS232 serial link with printers, full-sized word processors, computers, etc., and can store text either internally on battery backed-up RAM, or on any conventional external cassette recorder.

Characters or numerals are entered into the machine by pressing combinations of keys, rather than one key at a time as in the case of the QWERTY system. There are no markings on the keys since they can have different functions at different times, so the user is immediately forced into the excellent principle of touch typing, and looks at the display rather than at the keys being pressed. The user, therefore, has to learn all the sequences of keys to be pressed before being able to type correctly. This is the make-or-break aspect of the Microwriter—many people are immediately put off by having to learn a potentially complex typing language. Fortunately, the people at Microwriter Ltd. have been very clever indeed in the choice of

keys to be pressed per character. The right hand is always held in the same place above the keyboard, one finger above each key, and the shape formed by the fingers pressing the keys bears a relationship with the shape, or some aspect, of the character which becomes entered into the machine. That relationship is sometimes obvious and direct, sometimes humorous, sometimes very corny, but inevitably is easily memorable. Fig. 1 shows some of these relationships, based on a slightly stylised layout of keys. The manufacturers suggest that they can be memorised in typically one hour, and certainly I have found this to be the case as far as friends, colleagues, and myself have been concerned. It is very easy indeed to learn to Microwrite; far, far easier than touch typing, and I have tried both!

USING THE MACHINE

As each character is entered from the keyboard it is displayed on a single line liquid crystal display which can show up to 14 characters and two control symbols. The display acts as a 'window' on the text, and can be moved around within the text, either following new characters entered or to review what has already been written under the control of special commands. The text, as shown by the display, normally appears to shift to the left as each new character is entered by the keyboard and appears at the right hand end of the display. The sixth key on the Microwriter is a second thumb key, a little below the normal one, and it acts as a control key, allowing comprehensive control of the machine's functions. It is used either on its own, or with other keys in place of the normal thumb key. For example, entering the letter 'f' (the First Four keys pressed), but using the control key instead of the thumb key, moves the display window in the text Forward one position; 'f' for Forward—it is corny, but it works! Doing the same thing with the letter 'k' moves the window backwards. In this case, 'k' stands for Korrekt, so you use it when Korreecting errors!

WILL THIS EVER REPLACE THE 'QWERTY' KEYBOARD?





Pressing the control key once, on its own, puts the Microwriter into upper case characters for just one entry, after which it reverts to lower case. Pressing it twice in succession, on the other hand, locks the machine into upper case continuously until the two thumb keys are pressed together to revert to lower case. The status of the machine is continuously shown by two control symbols in a yellow coloured area at the right of the display.

Simple punctuation is provided as part of the normal lower case letter set, but more complex punctuation and numerals have to be accessed by a 'numerals shift' function. Entering the letter 'n', but with the control key pressed at the same time, shifts the Microwriter into the numerals mode for one character only; entering this combination twice in succession locks in the numerals mode, just like the upper case mode. There's another set of character/key relationships for the punctuation, with numbers being entered by a 'count on the fingers of one hand' type of technique. The requirement to shift for numerals is acceptable for word processing applications, but would make the Microwriter somewhat laborious for writing computer programs, for example.

To avoid timing problems when keys are pressed together, the Microwriter works on a key accumulation principle, and the character is only entered when all the keys have been released. Hence, you can start to press keys in any order, so long as at least one of them is being held down at any given time. When all the keys are eventually released, the result is as if all the keys that were depressed in that sequence, irrespective of their chronological order, were pressed simultaneously. This makes the keyboard action very 'forgiving', and allows characters to be entered very slowly and deliberately when required. The speed which can be obtained after only a few weeks' use is very high—not as fast as touch typing, but certainly up to twice as fast as handwriting.

EDITING AND WORD PROCESSING

When text has been written it can be edited (both deletion and insertion) and reviewed by appropriate use of the control key. To read through the written material, the user has to Jump back to the beginning (control + j) then scroll Forwards (control on its own, followed by control + f); this then moves the display window along the text one word at a time, at a user selectable slow or fast rate, until you tell it to stop. The machine automatically enters 'carriage returns' at the end of each line, and ensures that these are between words, not in the middle of them. Via the control key the user can access tabulation, margin indents, document markers, page separators, alter line length, and do many other complex word processor functions. These become very difficult to memorise, and even more difficult to implement, and I would have thought that they would have only limited usefulness to most people.

The control key is also used to suitably configure the RS232 link. Although this can be used to load text into the Microwriter, its primary use is to transmit text to a computer, word processor, or printer from the Microwriter. Full handshaking is provided, and there are user selectable baud rates, data lengths, etc., so it will interface with most RS232 based systems. All settings and text are stored in RAM with battery back-up, so nothing is lost when the power is turned off. The machine even turns the power off itself if it is not used for a few minutes, to

ALPHABET - RECOMMENDED LEARNING SEQUENCE

 Straight line up for I	 add a bar at the top for R	 add a bar at the bottom for L	 Reverse L for mirror image J	 Main feature of G is downstroke (opposite to I)
 Horizontal of the H	 Top of the T	 Press completely for P	 First Four Fingers for F FM Radio Make M	 Most Fingers
 Space	 Most Common finger (Index) for most common letter E	 The central target - bulls eye	 Signet ring finger	 Very non-U
 The dome of the D	 The bump of the B	 Looks like a V	 First upstroke of the A	 Adjoining downstroke of the N
 First downstroke of the V	 The upstroke of the K	 The two sides of the W	 Curl round for C	 Make a tail from the central O
 Everything except your index	 Zig zag between the keys for Z	 Full stop come to a point	 Hyphen	 Comma
 Apostrophe	 Command Key	 Pairs of letters have been highlighted by outlining		

84228-1 (1/83) © Copyright Microwriter Ltd 1982

07-022

Fig. 1. Sometimes corny, but inevitably memorable

conserve battery life. The batteries are rechargeable types, and a suitable charger is provided with the machine. Up to 1600 words, or typically 5 pages of A4 size, can be stored in the memory of the machine. (Much more if cassettes are used.)

THE HARDWARE

The packaging of the Microwriter inspires confidence! It is housed in a very solid injection moulded plastic case. The keys are ultra-low activating-force microswitches with moulded keys. Their action is light but positive, and their positioning is ergonomically spot-on. Inside there is just one main p.c.b. holding the RCA CDP1802A CMOS microprocessor, four HM6116 CMOS 2k Byte static RAMs, and a 2564 8k Byte CMOS EPROM, along with an 'intelligent' liquid crystal display above it as a sub-assembly, and other assorted CMOS i.c.s. The batteries are housed between the microswitches in the upper half of the case. It's a well laid out and professionally built product.

With the Microwriter itself comes a good quality soft carrying case, a battery charger, a cassette recorder connecting lead, some 'crib cards' giving a quick reference to control codes, characters, punctuation, etc., and two instruction manuals; a new user's guide, and a more complex systems manual for setting up communications protocol and the like. The new user's guide is effectively the main instruction manual for the machine, and without doubt is the best manual that I have seen for a piece of consumer electronics. The cartoon characters used might annoy some, but they will drive the points firmly home to just about anybody, whatever age or ability. Other product manufacturers would do well to study this manual and compare its high standards with their own!

There is an optional television interface unit available for the Microwriter which I'm somewhat less happy with. It interfaces to the RS232 port, and allows the display of text on a domestic television set or a composite video monitor. It is expensive (around the £100 mark) and gives very limited facilities. Writing onto the screen as you enter text works reasonably well, but if you just want to dump a letter, for example, onto the screen to check its layout, the use of the Microwriter becomes somewhat more contrived. It's very difficult to put a letter onto the screen without the top of the letter scrolling off the screen as soon as the bottom of the screen is reached. The unit that I tested also failed to get the ends of the lines correct when dumping onto the screen; parts of words were left at the end of some lines, then the whole word reappeared again on the next line. For the majority of potential Microwriter users I would question the necessity for the television interface unit—when you've got the hang of Microwriting you probably don't need it. It seems to be more suitable as a shared facility between several users, and generally seems to be somewhat of an afterthought rather than an integral part of the Microwriter system.

THE QUINKEY

For many people, the cost of a Microwriter (£299 plus VAT), although low by office equipment standards, is too high for them to consider it as a personal purchase. However, they could consider investing in a 'Quinkey'. This appears to be an ordinary Microwriter at first glance, but lacks most of the connectors and the display. In fact, it contains no electronics, just a set of microswitches and resistors which enables up to four of them, ingeniously, to plug into the analogue inputs of a BBC microcomputer. For just under £50 the full Quinkey package provides good value, consisting of the Quinkey itself, a manual, some crib cards, a connecting lead, and the software to run the system. Further Quinkeys on their own cost around £30.

The software enables the Quinkey to be used as well as the standard BBC QWERTY keyboard, not only with software within the BBC micro such as BASIC, the Acorn DFS, etc., but

also with software packages such as Wordwise and similar. A version for the Spectrum is soon to be made available, and Microwriter are working on versions for other popular personal computers too. All this helps to bring the unique qualities of Microwriting to the private individual, schools, colleges, etc.

APPLICATIONS—WHO USES IT?

The most obvious market for the Microwriter is with professionals on the move—salesmen, executives, engineers, and anybody who does an amount of documentation, report writing, letter writing, etc. On the train or 'plane they can write their meeting reports, or they can keep notes in the field or by their work benches, and either print the results out so that they are legible to themselves and to their colleagues, or if necessary dump them onto the office computer or word processor to be tidied up before final printing. There's no duplication of effort, the typists no longer having to work from handwritten notes.

The small size, portability, and ease of use of the Microwriter are attractions which a QWERTY keyboard has never had. Microwriting can never be as fast as good touch typing, so it will not be used to replace QWERTY keyboards in typing pools or secretarial offices, but for thousands of unqualified typists it offers a refreshing alternative to the two-fingered struggle, so it should be of great interest to small businesses, the police, sales personnel (especially those working from home), budding novelists, and even to the writers of magazine articles! For schools it has the advantage of allowing the connection of four Quinkeys to each BBC microcomputer, which immediately shares out normally limited resources to many more children. If accepted for these applications, it can only help establish Microwriting as a world-wide standard in years to come.

THE FUTURE OF MICROWRITING

Until recent months the promotion of the Microwriter was a very low-key process, although some rather more prominent advertising is now being seen. Over 7000 have been sold, which can only be the very tip of the potential iceberg. I must express reservations, however, about the approach that Microwriter are making on the market place, which seems to be rather uncertain and lacking in self-confidence. I first saw a Microwriter 'in the flesh' in the latter part of 1983, when I had a demonstration and a loan from a distributor for a couple of weeks. I expressed a great interest when I returned the machine to him, and was promised more information and a follow-up call shortly. I never heard from him, or another distributor I contacted, ever again. At the end of January 1984 I approached Microwriter themselves for information and a review sample to help prepare this article. I also ordered two Quinkeys for my own use. I am writing this article in mid August; the review sample only arrived three weeks ago! The Quinkeys arrived in the middle of June, some 19 weeks after they were ordered, and only after telephone calls at the rate of once per fortnight for most of that period. I persevered—I wonder how many others did not?

I hope that the future is very rosy for Microwriting. Amongst friends and colleagues the Microwriter has created more interest than any other piece of equipment that I can remember. The concept of the Microwriter is a work of genius. The market is potentially vast, the product works well, and the presentation is superb. The price is a little high, but should not deter the professional market, with the lower cost market being satisfied by the Quinkey. Let's just hope that Microwriter can improve on the delivery and planning side of it, put some more aggression into the marketing, and produce a commercial, not just a technical winner. What a great shame it would be if the Microwriter concept was lost to an overseas supplier, as has happened to so many other viable products from the UK.

More information can be obtained from Microwriter Ltd., 31 Southampton Row, London WC1B 5HJ. (01-831 6801).

THE LEADING EDGE

DIGITISATION

Everyone talks about the information explosion. The key is digitisation. With digital telephone systems what goes down the line is a series of PCM pulses, rather than analogue waves. Once you have that situation, the sky's the limit.

PCM pulses can carry telephone quality speech, high quality stereo radio, TV pictures, computer data, teletext, viewdata; in fact any information that can be converted into an electrical signal. Switching is by microchip, instead of the primitive Strowger electro-mechanical relay which phone systems have used for the best part of a hundred years.

By interleaving different calls in the same data stream, the capacity of a link goes up around 15 times, i.e. a pair of copper wires that normally carry one analogue telephone call, can carry fifteen digitals. With optical fibres, and the signals carried as light pulses rather than electrons, capacity rises much, much higher.

The British Post Office started working on PCM phone links 20 years ago. Few people know that the PO installed an experimental digital exchange at Earl's Court in 1968 and had it running until 1975. That was when talk about System X started.

Cynics say that the System was called X because no-one really knew what it was going to do or how it was going to do it. Essentially it's a computer switching service for PCM streams and there are now six System X exchanges working in London. One is at Baynard House in the City of London. The first five were prototypes.

Once data streams are digitally switched and connected, the options available open up wide. There is no problem in providing conference calls, automatically re-directing calls to other numbers or displaying the telephone number of origin when you receive a call.

ELECTRONIC MAIL

Already many people in Britain are using electronic mail, which is a hybrid system of sending digital data down an analogue telephone line. I'm one of them and there are quite a few stories to tell about how the system works in practice, as opposed to theory!

More of that in a future month. At the moment I am trying to find out why the main computer used by Telecom Gold for electronic mail keeps going wrong and leaving users like me stranded!

Why worry about information technology? There's a very short answer. *It is always far cheaper to send electronic data down a telephone line, or over a wireless link, than shift people or bits of paper from town to town or country to country.*

The best example of this is what happens at the *Economist* magazine. This London-based publication also prints in America and the Far East. Printing master plates are sent by airline courier to the Orient. Until a year ago they were also sent to America.

The plum job on the *Economist* was to take a day trip on Concorde to New York and back, with the print plates, for safe keeping. Now the magazine text is converted to digital data and sent by satellite direct to a Connecticut printing works, which publishes virtually simultaneously with London.

Wisely the *Economist* still sends a back up text by plane just in case the satellite link breaks down. But no-one gets the plum job of going along with them any more.

VIDEO NEWS

Polaroid has joined Kodak in 8mm video. Sony may follow next year but so far everyone else is sticking with their existing VHS and Beta formats. Ironically by joining Kodak, Polaroid may well have helped its rival succeed. The extra name gives the new format credibility.

At the Chicago Consumer Electronics Show both companies were demonstrating NTSC camcorders using the 8mm cassette. Picture quality was good and sound, using f.m. mono, seemed OK. The big question mark is over tape supply.

Video writing speed is very low; 3.8 metres a second for NTSC and 3.1 metres a second for PAL and SECAM. So packing density must be very high. You can get it either from tape coated with metal powder (MP) and coercivity around 1600 oersted. But this needs video heads which are expensive and may be short lived. The other way is to use lower coercivity tape coated by evaporation of cobalt-ferric metal in a vacuum (ME). No one has yet succeeded in making ME tape reliably in bulk.

Kodak started shipping 8mm camcorders to US traders last September. A 90 minute cassette costs \$24 and the system \$2000. There is no sign yet of a PAL or SECAM prototype. Although 8mm video almost certainly comes too late and too expensive to catch the domestic market, it could well form the basis of a new professional camcorder format.

Sony has both domestic and pro interests. Kodak and Polaroid are paying Matsushita, Toshiba and TDK to get the technology right for domestic use. Professional use is the logical follow on.

CLEAN CUT

I have now seen inside several compact disc and videodisc manufacturing plants in Britain, Germany and Japan. They all have one thing in common with a microchip factory, that is absolute cleanliness.

Exactly the same situation exists in magnetic tape factories, where any dirt in the atmosphere will end up as non-magnetic blemishes in the coating and cause dropout.

Air in the so-called "clean areas" is filtered to Class 100, that is to say less than 100 particles of less than 0.5 micron size in every cubic foot of air. The pressure of air inside these clean areas is higher than the atmosphere outside, so when a door opens clean air blows out and dirty air leaks in.

The staff must wear full length lint-free jump suits, like space clothing, and only a few visitors are allowed in. Usually there is an air shower, where blasts of clean air flush dirt, dust, dead skin and dandruff off every human passing through.

If only, I think every time I visit one of these plants, factories which press ordinary records would take even remotely comparable steps to preserve cleanliness. The official answer is that it's not necessary.

Certainly, by comparison, the technology of LP production looks like a blunt instrument. But it is easy to forget that a vinyl LP record is by far the most precise product mass produced from plastics!

The groove of an LP record is specified by IEC standard to be never less than 25 microns (or millionths of a metre) wide and preferably not less than 35 microns wide. As a "yardstick" a human hair is around 50 microns in width. The IEC puts stylus tip radius at between 15 and 18 microns.

Now let's look at a Laservision videodisc, and a compact disc digital audio record. Both have a spiral of information pits with a track pitch of 1.6 microns.

For videodisc the pits are 0.5 microns wide, and for compact disc they are 0.6 microns wide. Video pit depth is 0.1 micron and CD depth 0.12 microns.

In other words there is very little difference in the dimensions; both are at least 50 times smaller than the LP groove. The laser spot for videodisc playback is focused to a circle of 0.9 micron diameter and for compact disc it is 1 micron. The layer of protective lacquer in a compact disc has to be exactly 1.2 millimetres thick, or it will affect the laser focus.

PARTY TURN

If you collect useless information to bring out of the bag at boring cocktail parties, here's one for the bag. A CD player rotates the disc at a speed which varies between 3.5 revolutions a second and 8 revolutions a second, to give a constant tracking velocity of 1.25 metres a second.

That means that for a one hour disc there are 4.5 kilometres of track on a single side. For a laser videodisc the track length is 31 kilometres!

BARRY FOX

components

GILRAY ROAD, DISS, NORFOLK. TEL: 0379 4131

PART NO.	DESCRIPTION	MAIL ORDER PRICE
BBC MICROS AND ACCESSORIES		
ANB01	BBC Model B Micro	£325.00
ANB02	BBC Model B Micro with Econet I/F	£385.00
ANB03	BBC Model B Micro with Disc I/F	£406.00
ANB04	BBC Model B Micro with Disc & Econet	£445.00
ANB21	DNFS ROM	£17.91
ANB23	Disc Interface Kit (Excl DNFS ROM)	£4.00
ANB14	Speech Interface	£283.00
ANK01	IEEE488 Interface Adaptor	£35.00
ANB22	Econet I/F Kits	£8.00
BBC 45	2 BBC Joysticks	£7.50
STAND	Monitor Stand	£25.95
SRE1	Sideways ROM Expansion Board for BBC Micro	

BBC DISC DRIVES		
HC1	Single 100k 40 track single sided	£75.00
HC15	Single 100k (expandable to dual) 40 track	£90.00
HC1D	Dual (2 x 100k) 40 track single sided	£160.00
BBC44	Single 400k 80 track double sided	£156.50
BBC44S	Single 400k (expandable to dual) 40/80 track switchable double sided	£180.00
BBC44SW	Single 400k 40/80 track switchable double sided	£159.00
BBC44D	Dual (2 x 400k) 40/80 track switchable double sided	£310.00

INSULATION DISPLACEMENT CONNECTOR SYSTEM			CABLE ASSEMBLIES		DIP JUMPERS	
HEADERS			IDC JUMPERS SINGLE ENDED		Single Ended — 24" cable	
	SHROUDED	OPEN — 90°	36" cable	IDC socket	14 pin	1.73
		OPEN — 90°	10 way		16 pin	1.90
10 way	0.86	0.65	14 way		24 pin	2.73
14 way	1.22	0.83	16 way		40 pin	3.96
16 way	1.34	0.92	20 way		Double Ended	
20 way	1.36	1.13	26 way		6" cable	12" cable
26 way	1.70	1.40	34 way		18" cable	
34 way	2.04	1.78	40 way		14	2.74
40 way	2.28	2.07	50 way		16	3.03
50 way	2.70	2.54	60 way		24	4.18
60 way	3.20	3.02			40	5.89
					50	6.18
					60	6.47
SOCKETS			DISC DRIVE CONNECTING CABLES			
DIP PLUGS			34 way card edge to 34 way card edge 1M		11.30	
D-TYPE PLUGS			34 way card edge to 2 x 34 way card edge 1.5M		18.00	
9 way 1.38			34 way card edge to 34 way IDC SKT (BBC) 1M		8.50	
15 way 1.60			34 way card edge to 2 x 34 way IDC SKT (BBC) 1.5M		14.50	
25 way 2.52			BBC Power Cable — Single Drive		3.50	
37 way 3.34			BBC Power Cable — Dual Drive		4.75	
TRANS. CONNS.			BBC MICRO CONNECTORS			
10 way 0.86			DIN PLUG 7 PIN		0.40	
16 way 1.17			DIN PLUG 6 PIN		0.40	
20 way 1.37			DIN PLUG 5 PIN 180°		0.40	
26 way 1.67			DIN PLUG 5 PIN DOMINOE		0.40	
34 way 1.87			POWER PLUG (36" CABLE)		3.00	
40 way 2.23			ANALOGUE INPUT PLUG		2.25	
D-TYPE SOCKETS			5 WAY DIN SKT 180°		0.90	
9 way 1.47			5 WAY DIN SKT DOMINOE		0.90	
15 way 2.02			6 WAY DIN SKT		0.90	
25 way 2.90			7 WAY DIN SKT		0.90	
37 way 3.97			15 WAY DIN SKT		2.15	

MECHANISMS		
	100k single sided Alps	£70.00
	400k double sided Epson	£140.00

FLOPPY DISCS		
MD-1C/B	Nashua single sided, single density 40 track (10 discs)	£12.00
MD-1DC/B	Nashua single sided, double density 40 track (10 discs)	£13.00
MD-2DC/B	Nashua double sided, double density 40 track (10 discs)	£15.50
MD-2FC/B	Nashua double sided, quad density 80 track (10 discs)	£17.85

SPECIAL OFFER		
BBC40TD	BASF double sided, double density 40 track (10 discs)	£14.00

DISC STORAGE BOXES		
MDT25/3	3 1/2" Flip 'N' file Micro disc box (cap. 25)	£7.75
DT25/5	5 1/4" Flip 'N' file lockable disc box (cap. 25)	£18.77
DT60/5	5 1/4" Standard lockable disc box (cap. 60)	£10.65

MONITORS		
9MON	9 inch green screen high resolution NEC high quality monitor	£125.00
12MON	12 inch green screen high resolution NEC high quality monitor	£135.00
1431	Microvitec 14" RGB colour monitor	£175.00
1441	Microvitec 14" RGB colour monitor high resolution	£410.00
1451	Microvitec 14" RGB colour monitor medium resolution	£295.00
1431/AP/MS	Microvitec 1431 PAL & RGB inputs and sound facility	£225.00

EPSON COMPUTERS AND ACCESSORIES		
PX-8	Epson portable computer (incl. CP/M and s/w) 64k	£798.00
PX-8/120	120k RAM	£998.00
CX-21	Acoustic coupler	£160.00
PF/10	Disc drive for PX-8	£360.00
P40	Thermal printer for PX-8 and HX-20	£86.91
HX-20	Epson portable computer	£411.00

MATRIX PRINTERS		
RX80	Epson RX80 100cps matrix printer	£204.00
RX80FT	Epson RX80FT 100 cps matrix printer friction or tractor feed	£231.00
FX80	Epson FX80 150cps matrix printer	£328.50
MT80SP	Mannesmann Tally MT80 matrix printer friction or tractor feed with film ribbon and tear off facility	£217.00

LETTER QUALITY PRINTERS		
HR5	Brother HR5 Thermal printer A/C mains or battery	£130.00
HR15	Brother HR15 Daisy wheel printer (13cps)	£326.00
HR25	Brother HR25 Daisy wheel printer (23cps)	£550.00
UCHIDA	Uchida DWX305 Daisy wheel printer (20cps)	£227.00

PRINTER SUPPLIES		
11241P160	11 x 9; 1 part plain listing paper (2,000)	£12.56
11241P2C1	11 x 9; 2 part (otc) plain listing paper (1,000)	£15.93
11241P3C1	11 x 9; 3 part (otc) plain listing paper (700)	£17.86
11370R160	11 x 14; 1 part ruled listing paper (2,000)	£16.20
11370R2NC	11 x 14; 2 part (ncr) ruled listing paper (1,000)	£22.50
11370R2C1	11 x 14; 2 part (otc) ruled listing paper (1,000)	£15.00
12235P160S	12 x 9; 1 part plain listing paper with side perms. (2,000)	£12.00
HR1R	Brother HR1 ribbon	£2.20
RIB119	Diablo Hytype II Multistrike film ribbon	£1.75
GP205	Diablo Hytype II fabric ribbon	£2.50
MX80	Epson MX80, RX80, FX80, fabric ribbon	£3.00
MT80	Mannesmann Tally MT80 film ribbon	£6.50
RIB117	Uchida DWX305 multistrike film ribbon	£2.75
HR5R	Brother HR5 ribbon	£2.20
HR15R	Brother HR15 multistrike ribbon	£4.00
HR25R	Brother HR25 multistrike ribbon	£4.00
	Brother daisy wheels	£14.00
	Uchida/Qume daisywheels	£4.00
LAB089361C	3 1/2 x 1 7/16 Labels — 1 wide (8,000)	£20.00
LAB089361S	3 1/2 x 1 7/16 Labels — 1 wide (2,000)	£13.00
LAB070363F	2 1/2 x 1 7/16 Labels — 3 wide (1/10") (2,000)	£8.00

Connecting cables for personal computers
A comprehensive range of high quality interconnecting cables for popular micro computers. All cables utilise high quality connectors and are individually tested to ensure trouble free use.

Part number	Description	Computer	
Video cables			
CON100	Phono plug to phono plug (2M)		1.20
CON101	Phono plug to BNC plug (2M)		2.95
CON102	BNC plug to BNC plug (2M)		3.95
CON107	6 pin DIN to open end (1M)	BBC	1.05
CON108	6 pin DIN to 6 pin DIN (1M)	BBC	1.50
CON119	Phono plug to coax plug		1.35
CON160	DIN plug to 2 phono plugs	Dragon	1.20

Cassette recorder cables			
CON109	7-pin DIN to open end	BBC	1.25
CON110	7 pin DIN to 2 x 3.5mm + 1 x 2.5mm J/plug	BBC	2.50
CON111	7 pin DIN to 5 pin DIN + 2.5mm J/plug	BBC	2.50
CON118	5 pin DIN to 2 x 3.5mm J/plugs	Spectrum/ZX	2.50
CON117	5 pin DIN to 2 x 3.5mm + 1 x 2.5mm J/plug	Dragon	2.50

Parallel printer cables			
CON130	36 way plug to 36 way plug (2M)	Sirius/Apricot	18.00
CON131	36 way plug to 36 way plug (5M)	Sirius/Apricot	26.50
CON132	36 way plug to 36 way socket (2M)		18.00
CON133	36 way plug to 36 way socket (5M)		26.50
CON144	36 way plug to 25 way male D type (2M)	IBM/TL PC	19.00
CON145	36 way plug to 25 way male D type (5M)	IBM/TL PC	27.50
CON134	36 way plug to 25 way male D type (2M)	RML/Apple	19.00
CON135	36 way plug to 25 way Male D type (5M)	RML/Apple	27.50
CON142	36 way plug to 20 way IDC socket (2M)	Dragon	13.95
CON139	36 way plug to 26 way IDC socket (2M)	BBC	9.95
CON140	36 way plug to 26 way IDC socket (5M)	BBC	22.95
CON141	36 way plug to 34 way card edge (2M)	TRS80 Lev 1	18.50
CON143	36 way plug to 34 way IDC socket (2M)	TRS80 Lev 2/ Memotech	10.95

RS232 Cables			
CON106	25 way male D type to 5 pin DIN	BBC	5.85
CON128	'Universal' RS232 cable (pins 1-8, 20 connected and 20 jumpered as required) 2M		15.95
CON164	'Universal' RS232 cable as above but 5M		20.95
CON120	25 way male to male 1-25 connected (2M)		16.95
CON121	25 way male to male 1-25 connected (5M)		22.50
CON122	25 way male to male 1-25 connected (10M)		32.50
CON123	25 way male to male 1-25 connected (30M)		68.00
CON124	25 way male to female 1-25 connected (2M)		15.45
CON125	25 way male to female 1-25 connected (5M)		21.00
CON126	25 way male to female 1-25 connected (10M)		31.00
CON127	25 way male to female 1-25 connected (30M)		66.50
CON129	25 way male to 9 way male	Spectrum	15.95
CON162	25 way male to 9 way male	Mackintosh	15.95
CON163	25 way male to 5 pin DIN	RML 480Z	14.95

SEMICONDUCTOR CIRCUITS

TOM GASKELL BA(Hons) CEng MIEE

POWER OP-AMPS (TCA365 and TCA2365)

ONE of the most important components available to the analogue circuit designer is the operational amplifier, or 'op-amp'. The majority of these, however, are somewhat limited in their load driving capabilities. Simple devices such as the 741 can only output 25mA under short circuit conditions, or 10mA in normal operation. For much higher currents it is usually necessary to add extra driving transistors to a conventional op-amp.

The TCA365 and TCA2365 are power op-amps which allow the designer to use a single i.c. in high power applications rather than the more cumbersome 'op-amp plus components' approach. In practice, they behave as fairly ordinary op-amps with the exception that their output stages can drive up to 3 amps in the case of the TCA365, or 2.5 amps per amplifier in the case of the dual op-amp TCA2365. The two i.c.s are very similar, with both sets of specifications being given in Fig. 2. The main points to watch are supply voltage maxima, output currents, and power dissipation; these all vary between the 365 and the 2365. (Note that the output current shown for the TCA2365 is 2.5A per amplifier, not for the whole i.c.) Fig. 1 shows the pinouts of the i.c.s. For moderate to high power applications, heatsinks should be used. These should be insulated from the i.c.s' tabs if the internal connections to the -ve supply could cause short circuits or problems.

The TCA2365 has an 'inhibit' input which can be used to turn the outputs of the op-amps off, ie. high impedance (approximately 4k). Inhibiting is effective when pin 6 is taken to the -ve supply rail, and the amplifiers operate normally when pin 6 is taken above 3.0V referred to the -ve supply, or left unconnected. Both the TCA365 and the TCA2365 have extensive protection; they are d.c. short circuit proof and have thermal overload and safe operating area protection. The internal current limiting makes them ideal for driving complex loads, and especially for driving filament lamps, whose low resistance in the 'cold' state can cause problems with other types of driver.

BASIC CIRCUITS

Some basic circuits for use with these power op-amps is shown in Fig. 3. In all cases there is an external Zobel network (sometimes known as a Boucherot network) fitted between the output and 0 volts to help to maintain stability under widely varying load conditions.

The 1 ohm resistor does not have to be high power ($\frac{1}{4}$ watt will do) and the capacitor must be 100nF for the TCA365, or 220nF for the TCA2365. It is unimportant which way up the network is fitted; the capacitor can be connected to 0V and the resistor to the output, or vice versa. Both power op-amps can be used with either split or single rail supplies, just as would be possible with most conventional op-amps.

Figs. 3a and 3c are very straightforward conventional op-amp circuits, and apply perfectly well to the TCA365 and TCA2365. For minimum offsets, R_2 in Fig. 3a and R_1 in Fig. 3c should be included as shown, although in many circuits these are unnecessary and can be replaced by short circuits for economy. Both these circuits, however, should really only be used for higher gain circuits; +10dB or more, or preferably +20dB. For lower gain circuits, and certainly for anything less than 10dB (approximately $\times 3$), the configurations of Figs. 3b and 3d should be used. For unity gain, use typically between 10k and 100k for both R_1 and R_2 , with R_0 approximately one tenth of that value, in Fig. 3b, and typically between 10k and 100k for R_1 in Fig. 3d, with R_0 one tenth of that and R_2 an open circuit. The reason for all this is concerned with stability.

STABILITY

There are many factors influencing stability in operational amplifiers. These tend to be involved, complicated, steeped in complex-plane mathematics, and certainly beyond the scope of *Semiconductor Circuits*! Empirically, most electronics engineers and enthusiasts learn some straightforward rules of thumb about how to keep amplifiers stable and prevent problems of self-oscillation at several megahertz. A common 'cure-all' is to connect a small value capacitor, typically less than 100pF, between the output and the inverting (-ve) input. Don't do this to a TCA365 or 2365! Even if it doesn't actually cause oscillation (which it probably will) it will certainly make oscillation much more likely. This is basically due to the fact that the op-amps have poor stability at low gains, and a capacitor across the feedback loop ensures low gains at high frequencies. For gains of more than 20dB ($\times 10$ gain) the i.c.s are normally quite stable, assuming that the Zobel network is fitted and that P.S.U. decoupling is taken care of. More than 10dB ($\times 3$ gain) is normally acceptable, but below this there can be problems with transient response

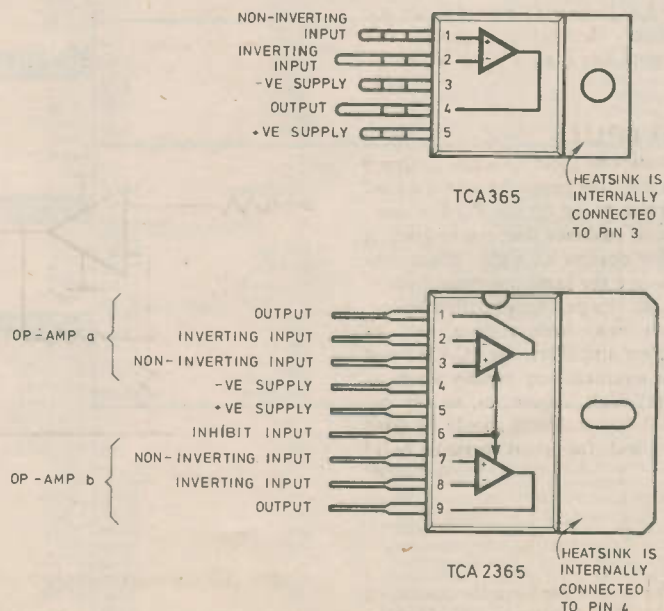


Fig. 1. Pin outs for the TCA365 and TCA2365

Characteristic	Notes	TCA365 (Single Op-Amp)			TCA2365 (Dual Op-Amp)			Units
		Minimum Value	Typically	Maximum Value	Minimum Value	Typically	Maximum Value	
Supply voltage	All spec's quoted at $\pm 15V$ for TCA365 and $\pm 10V$ for TCA2365 (In normal operation: with amps inhibited: (TCA2365 only))	+4 *(or 8V)	± 15	± 18 *(or 36V)	+4 *(or 8V)	± 10	± 13 *(or 26V)	V
Quiescent current		—	20	40	—	30 5	50 8	mA mA
Temperature range		0	—	+70	-25	—	+85	$^{\circ}C$
Maximum O/P current		Per amplifier	—	—	3.0	—	2.5	A
Maximum I/P voltage	(Differential)	—	—	Supply rails	—	—	Supply rails	
I/P offset voltage	(Of input offset current)	-10	—	+10	-10	—	+10	mV
I/P offset current		-0.2	—	+0.2	-0.1	—	+0.1	μA
Temperature coefficient		—	—	0.1	—	—	—	nA/ $^{\circ}C$
Input current		—	0.2	1.0	—	0.25	1.0	μA
Input resistance	At 1kHz	—	—	—	1.0	5	M Ω	
Output voltage	Load resistance = 470 Ω at 1kHz Load resistance = 4.7 Ω	± 13.0 ± 11.7	± 13.2 ± 12.0	—	+8.0	+8.5	—	V
Slew rate	—	—	4	—	—	4	V/ μs	
Voltage gain	Open loop, at 100Hz	—	90	—	70	80	dB	
I/P common mode voltage range	Load resistance = 470 Ω	+13.4 -15.0	+13.5 -15.0	—	+7.0 -10	+7.5 -10.5	V	
Common mode rejection ratio	Load resistance = 470 Ω	75	83	—	70	80	dB	
Supply voltage rejection ratio	Gain = x100, frequency = 20Hz Gain = x10, frequency = 100Hz	50	62	—	70	80	dB	
Power dissipation	Total for package, at 90 $^{\circ}C$	—	—	15.0	—	—	6.0	W
Equivalent I/P noise	Gain = x11, I/P resistor = 10k	—	—	—	—	3.0	—	μV
Inhibit input (TCA2365 only)	For i.c. turned off For i.c. turned on	—	—	—	0 3.0	1.0 (+ve supply)	—	V V

*= For single supply rail operation


Fig. 2. Specifications (note different supply rails used in measuring spec's.)

(overshoot of the output on square waves) and stability.


Hence, the circuits of Figs. 3b and 3d should be used for low gain applications. Although the actual voltage gains of these circuits are exactly the same as the equivalent gains of Figs. 3a and 3c, the inclusion of R_o actually causes the op-amps to be working in a 'high gain' way. Normally, this is rather undesirable, since there is no apparent benefit to the user and the amplifier has a much noisier output voltage, but in this application the 'pseudo gain' helps to ensure stability at low real gains, and is to be recommended for use with any circuitry demanding a gain of less than x4, or even less than x10 to be on the safe side.

POWER SUPPLIES


The capabilities of these op-amps to dump several amps from the supply rails into a load puts considerable strain on the P.S.U.s used. The best general guidance that can be given is to consider the devices as audio power amplifiers, and to use the same constraints about removing earth loops, supply decoupling, keeping inputs away from outputs, etc. As with audio power amplifiers, the TCA365 and TCA2365 will overheat very rapidly when oscillating at very high frequencies, so any debugging of stability problems should be done very rapidly, and for short periods only! Specifically, it is good practice to take the 0V connection to the feedback resistor, input resistors, input decoupling, etc, as appropriate, to the power supply as a separate connection from the load, Zobel network, etc, to isolate the input as far as possible from the output. In all cases, each power op-amp should have

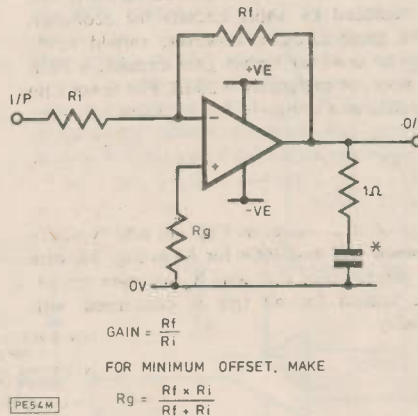


PE54M

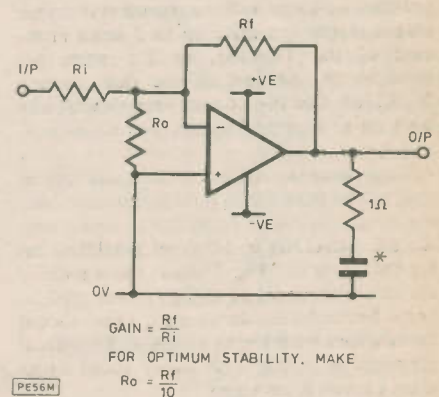

PE56M

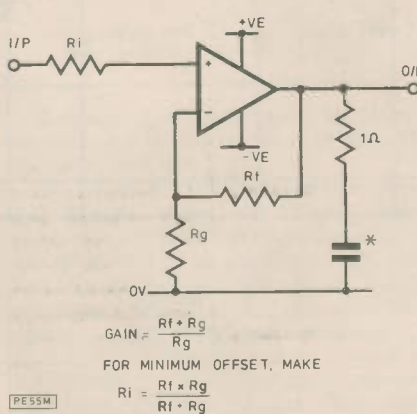

PE55M

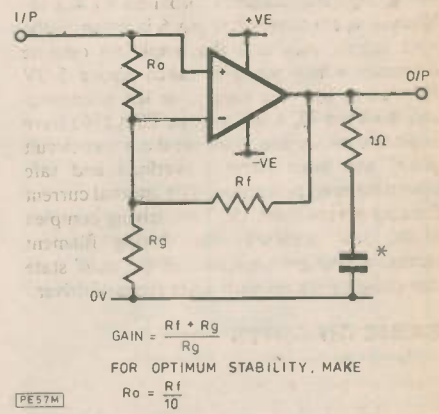

PE57M

Fig. 3c. Non-inverting, high gain

Fig. 3d. Non-inverting, low gain

Fig. 3. Basic power op-amp circuits

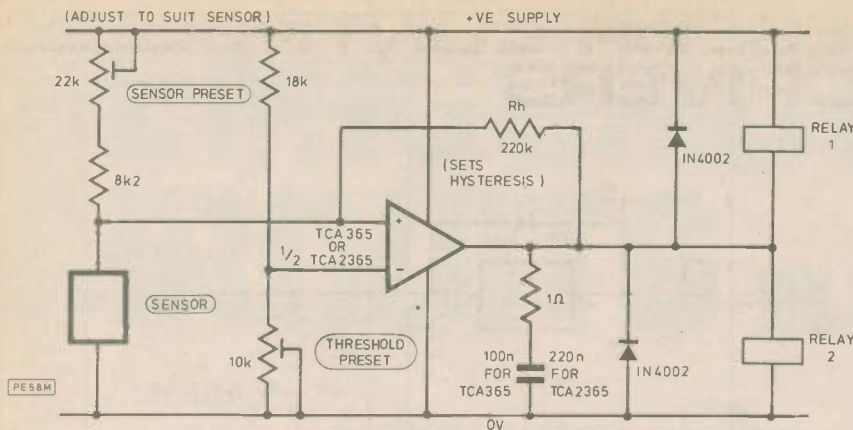


Fig. 4. Simple sensor detector and switch

100µF capacitors between its supply rails and 0 volts, or simply across its rails in the case of single supply systems.

When inductive loads are to be driven, diodes should be connected between the op-amp output and the supply rails, as shown in Figs. 4, 6 and 8. This protects the op-amp's driver transistors from the huge back e.m.f. spikes generated when inductive loads are suddenly turned off.

APPLICATIONS

The uses for these i.c.s fall mostly into the realms of control and switching. They will amplify and drive audio signals, but not with the fidelity that can be achieved by audio power amplifiers specifically designed for the task. Essentially, these i.c.s are excellent for use on many occasions when an ordinary op-amp simply runs out of drive capability. Some examples of switching applications are shown in Figs. 4, 5 and 6.

A simple sensor circuit is shown in Fig. 4 using the power op-amp as a comparator and directly driving relays 1 and 2. The sensor can be any device which varies in resistance in

proportion to a required effect. For example, a light dependent resistor (e.g. ORP12) or thermistor would allow the sensing of light level or temperature respectively. The sensor preset scales the voltage range produced by the sensor at the op-amp's non-inverting input, while the threshold preset alters the level at which the op-amp changes state. R_h provides some hysteresis to stop the op-amp 'hunting' or 'chattering' when the sensed value is just on the threshold point.

A square wave oscillator is formed by the power op-amp in Fig. 5. The mark/space ratio potentiometer adjusts the charge and discharge paths for C_T such that their sum is always constant (i.e. the frequency does not vary) but the mark/space ratio can be adjusted over a wide range. The frequency itself is set by a combination of the value of C_T and the setting of the 100k 'frequency' potentiometer. This circuit is capable, by virtue of the power op-amp, of driving pulses of several


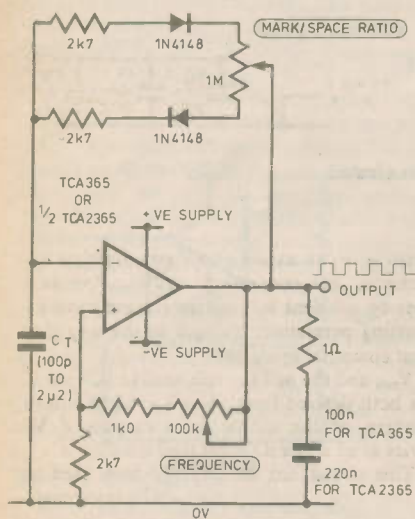


Fig. 5. Power pulse generator

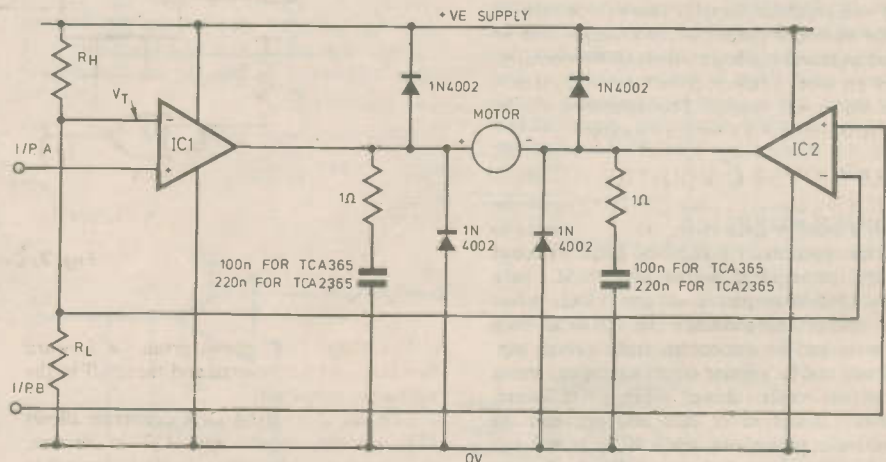

INPUTS		EFFECT
B	A	
0	0	STOPPED
0	1	RUN CLOCKWISE
1	0	RUN ANTICLOCKWISE
1	1	STOPPED

Fig. 6. Bi-directional motor control

amps into any suitable load. Output diodes should be added, as shown in the other circuits, if the load is to be an inductive one.

DIFFERENTIAL DRIVING

Finally, Fig. 6 shows two power op-amps driving a d.c. motor in a 'bridge', or differential drive mode. This allows the direction of rotation of the motor to be changed. IC1 and IC2 are arranged as comparators with R_H and R_L setting the threshold voltage V_T , and are designed to be driven by logic signals A and B. If both inputs A and B are at a low level (logic 0), both sides of the motor will be at a low level (0V). If both inputs are high (logic 1), then both sides of the motor will be at a high level, near to the +ve supply rail. In both these cases the motor will not run, since there is no differential voltage across it—both terminals of the motor are at the same voltage. However, if one input is high, and the other low, the motor will run in one direction or the other. Normally, V_T should be set to a suitable level for the logic family which is used to control IC1 and IC2; ideally, R_H and R_L should be taken from the logic's power supplies, not the +ve power supply as shown, to ensure accuracy of the threshold voltage.

The TCA365 and TCA2365 are ideal for use in controlling motors, relays, magnetic valves, and solenoids. They can also make a good basis for the design of regulated power supplies. Their current limiting makes them especially suitable for driving filament lamps and other unusual loads, and their op-amp configuration makes for easy interfacing of these loads with both analogue and digital circuitry. When stability is taken into consideration these are easy and effective to use, and provide an economic solution to many power driving problems. Both i.c.s are available from Electrovalue, 28 St. Jude's Road, Englefield Green, Egham, Surrey.

MICROPROCESSOR CONTROLLED DC MOTOR DRIVERS

LAST month we looked at a timer circuit triggered by a microprocessor. This month we have another microprocessor based project, to allow the analogue driving of d.c. motors. Again, the circuit assumes the use of the Z80 microprocessor, although it is very easily adaptable for other devices. The circuitry is shown in Figs. 7 and 8 and the Veroboard layout in Fig. 9. The circuit consists of two separate sections; the decoder, and the driver. Up to 8 drivers can be operated by one common decoder.

The address decoding is done in a similar way to last month's project. IC1 compares the most significant nibble (4 bits) of the 8 bit port address with the settings of S1 to S4. Each switch is turned off to correspond to a logic 1, and on for a logic 0. The comparison is only enabled when both \overline{IORQ} and \overline{WR} are at logic 0 (determined by IC5c), corresponding to the microprocessor performing an I/O write instruction. IC2 is a 3-to-8 line decoder used for the least significant nibble of the port address. Address line A3 must be held at logic 0 and the other 3 lines then provide the address of the driver circuit required. The least significant nibble of the driver address will therefore be 0 to 7, as determined by the latch output of IC2 used. The outputs of IC2 are inverted, and are wired to the LATCH inputs of any required driver circuits. Hence, if one particular driver circuit LATCH input was connected to LATCH output 3 of IC2, switch S1 was off and switches S2 to S4 were all on, that driver circuit would respond to address 13H (i.e. 19 in decimal). Driver circuits can thus be provided at port addresses 00H to 07H, 10H to 17H, 20H to 27H, 30 to 37H, etc.

IC3, with associated components, provides a 5 volt regulated supply. This can be omitted if the microcomputer's own 5V supply is to be used to power the logic supply to the circuitry. IC4 provides a reference voltage which tracks the V_p power supply. This reference will be approximately 1.8V for a 12V supply.

THE DRIVER CIRCUITRY

IC6 is a digital to analogue (D/A) converter with a built-in data latch, which connects to the microprocessor's data bus. Data is latched in by the required output of IC2. IC7 is a TCA2365 dual power op-amp which drives the motor differentially to provide both forward and reverse control from a single supply voltage. (It's based on an analogue version of the differential driver in Fig. 6). IC7a amplifies the output of IC6 and provides the positive output phase, while IC7b inverts this positive drive signal about a half-rail reference voltage set by R17, R18 and VR2, and provides the negative output phase.

When the output of IC6 is at 0V, pin 1 of IC7a is near to 0V and pin 9 of IC7b is near to the +ve supply. When the output of IC6 is at V_{ref} , the reverse is true. When IC6's output is at half V_{ref} , both power op-amp outputs are at half the supply rail and the motor is stationary. Presets VR1 and VR2 alter the gain and offset of the output voltages, and D1,

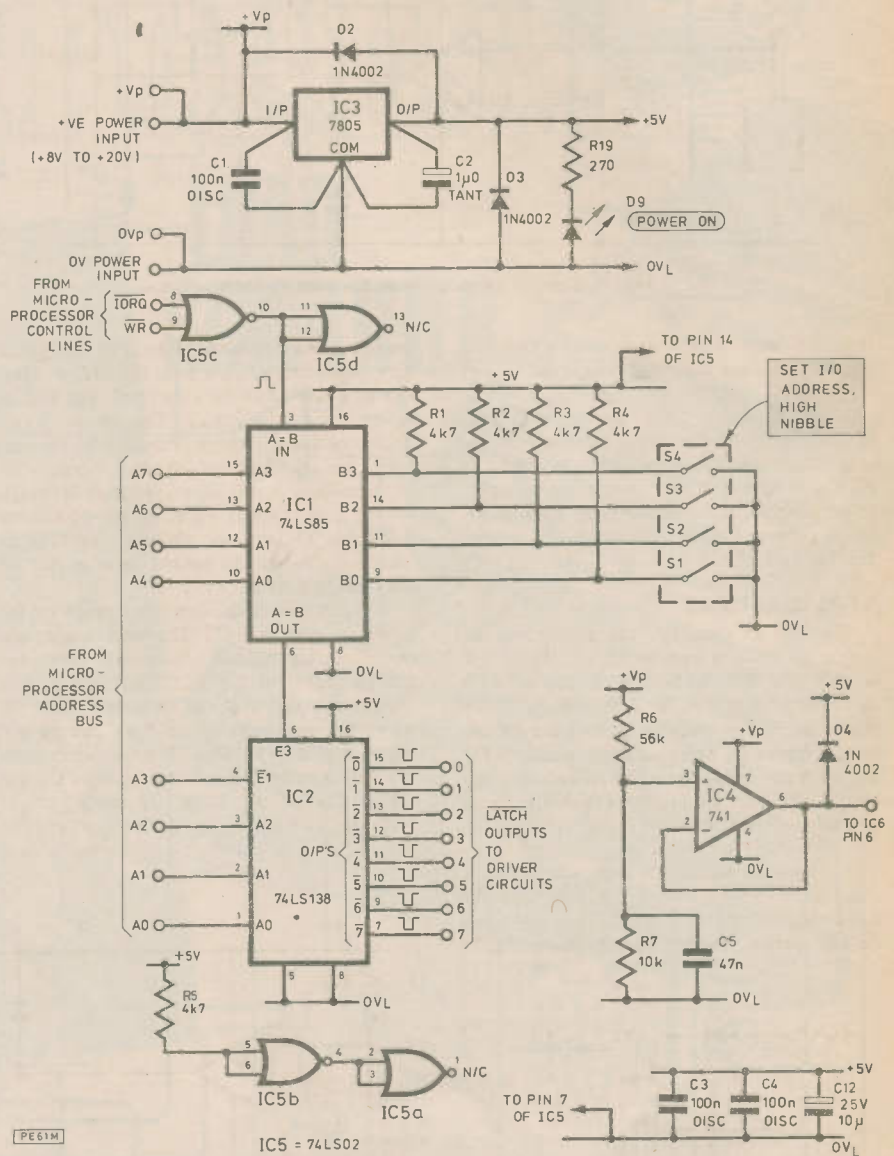


Fig. 7. Decoder circuit

a 'Bi-Colour' i.e.d., glows green for forward direction, red for reverse and turns off in the stationary condition.

The use of an 8 bit D/A converter allows 127 forward speeds and 127 in reverse, although it is unlikely that the electric motor in use will operate all the way down to 0V. Note that 0V_L, the logic zero volts supply, and the power zero volts 0V_p, have been wired back separately to the power input area around IC3 to help ensure stability and an absence of noise problems with the logic supplies. GREAT CARE must be taken when wiring up the circuitry and assembling components on the Veroboard, and tests should be done prior to connecting to the computer as far as

possible. I can assure you, from practical experience, that connecting +12V to the data lines by accident will certainly cause some interesting permanent changes to the way that your computer operates!

V_{ref} and the half rail reference to IC7 pin 7, are both derived from the +V_p rail to ensure tracking of the motor drive outputs if V_p varies at all under different load conditions.

This circuit has successfully been used to control a 12 volt model train set by microcomputer. The only programming requirement is to output the relevant motor speed values to the port or ports in question. Hence, for a port address of 24 (Hex) for example, the assembled Z80 machine code for full speed forwards

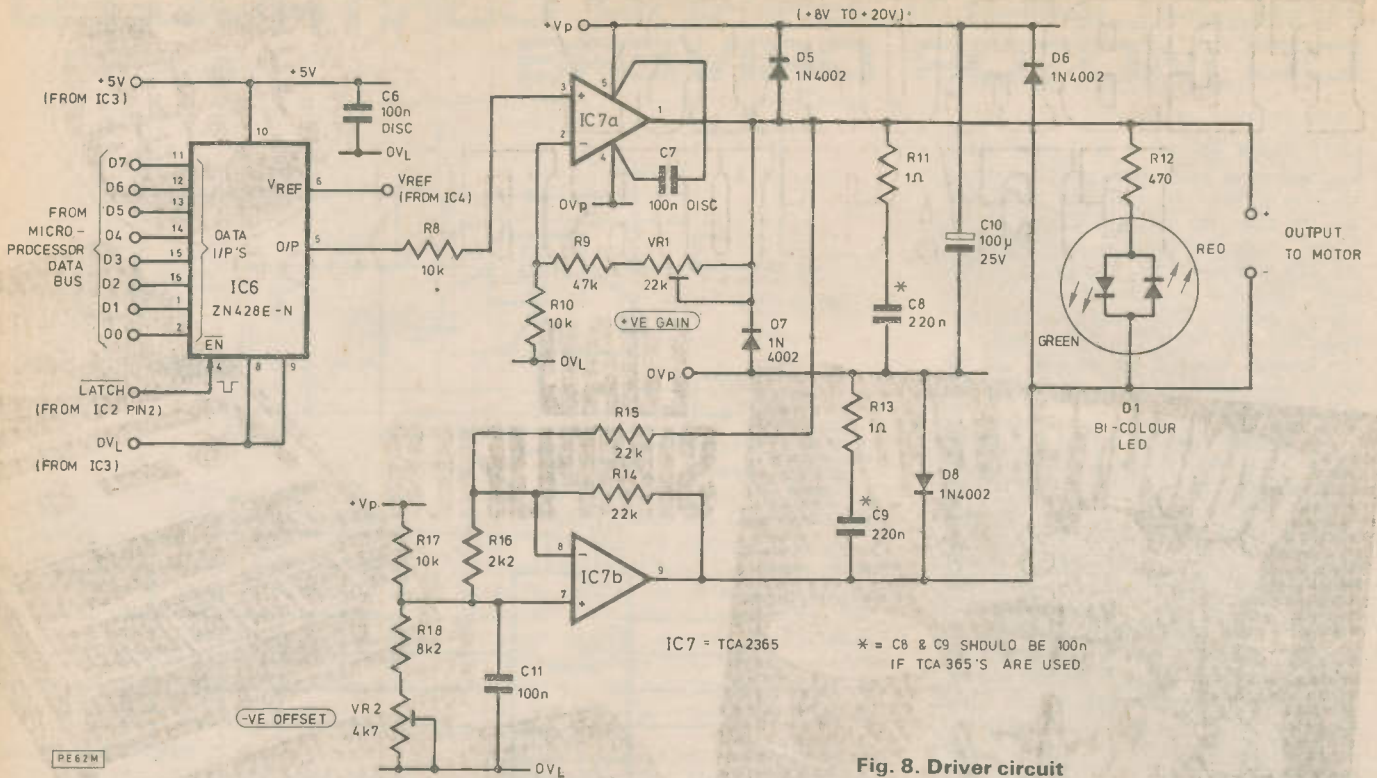


Fig. 8. Driver circuit

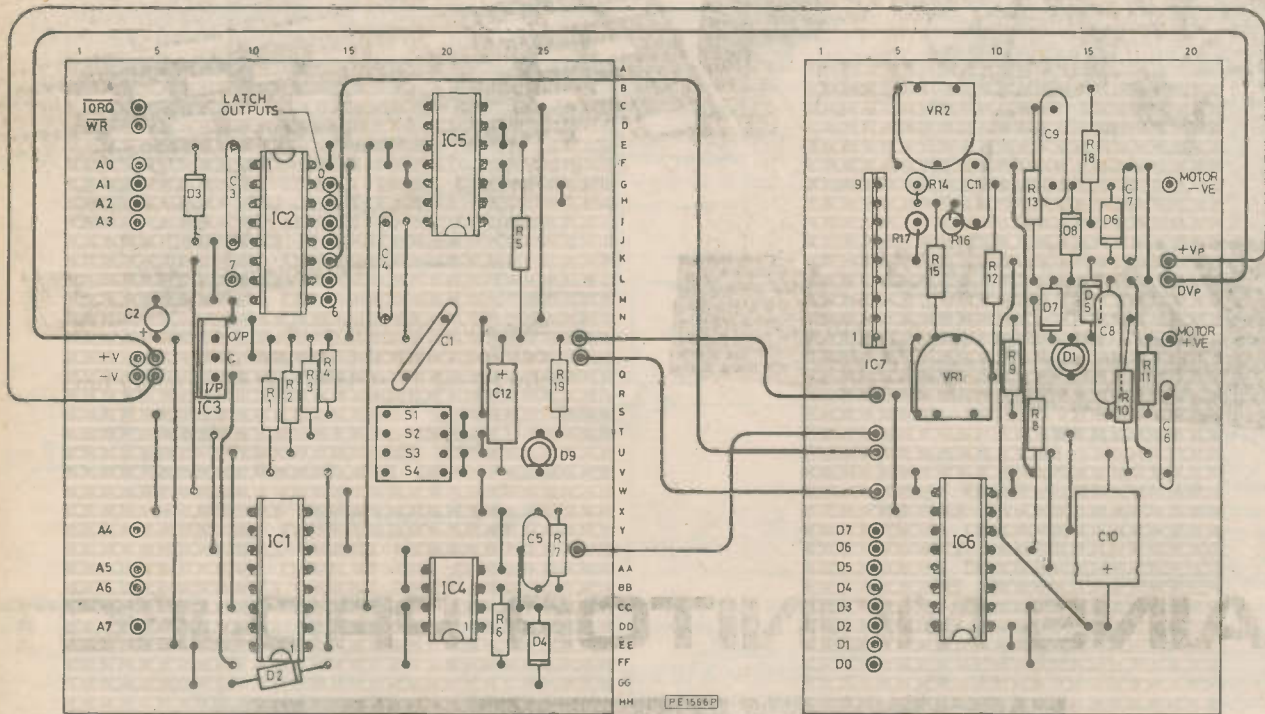


Fig. 9. Veroboard layout

could look like this:

```

3E 00 LD A,0FFH
; Put required value in Accumulator.
D3 24 OUT (24H),A
; Output the Accumulator to the port.

```

In BASIC, the simple instruction OUT 36,

255 would suffice. (36 is the decimal equivalent of 24H, the port address, and 255 the decimal equivalent of 0FFH.) For full speed reverse use the value 00H (0 decimal), for stopped use 07FH (127 decimal), and for slower speeds use values in between. Finally,

don't forget the heatsink on IC7! The i.c. has been placed at the edge of the board to allow for this. The resulting motor speed control provides a simple illustration of a typical use for power op-amps, either as two single devices or a pair as used specifically in Fig. 9.

FEBRUARY FEATURES...

**8
EXTRA
PAGES**



LOAD SIMPLIFIER



See and hear software coming down the line and get the LOAD level right first time, every time

Solid State Reverb

MAINS MONITOR PROJECT

EVERYDAY
ELECTRONICS
and computer **PROJECTS**

FEBRUARY 1985 ISSUE ON SALE FRIDAY, JANUARY 18


Signal Generator & F-V Converter

JOHN M. H. BECKER

ANY electronics enthusiast needs a signal generator and frequency meter nearly as much as a soldering iron and multimeter. The last two should be part of anyone's workshop but the degree of enthusiasm does not necessarily warrant the expense of highly accurate generators and counters. Often only an indication of approximate frequencies is required, together with a unit that makes readily controllable sounds with suitably shaped waveforms.

GENERATOR CHIP

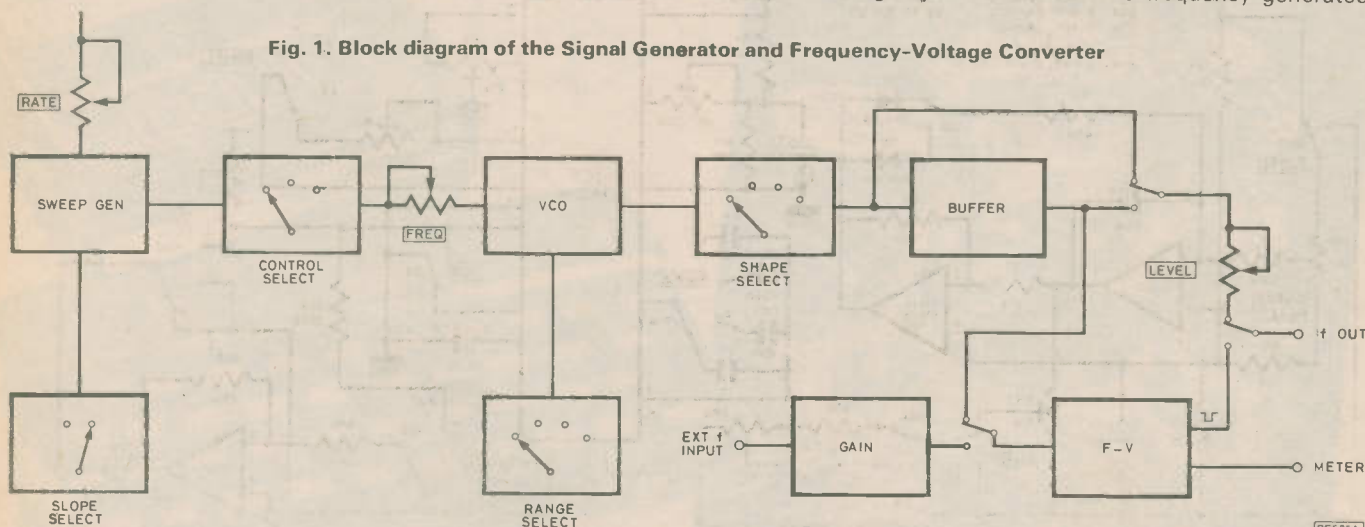An XR2206 function generator chip has been chosen in preference to the normally selected type 8038 as it has a greater variety of waveforms available, together with a wider sweep range on each selected setting. The oscillograms show the wide range of waveforms available. The basic frequency range is selected by S1, bringing in the desired frequency setting capacitor C4-C7. The frequency generated




This unit has been designed as a reasonable quality, moderate cost, dual purpose unit suitable for average and addicted constructors alike. It produces well shaped waveforms of frequencies ranging from 2Hz to 78kHz in four tunable ranges, and includes automatic ramp control of a frequency sweep, both upwards and downwards. Additionally it includes a frequency to voltage converter that can be coupled to an ordinary multimeter, or digital voltmeter to give a direct read out of the approximate frequency being generated, or fed in from an external source. It is intended for use with an existing power supply or, for short periods with batteries, from 9V up to 18V dc. Provision has also been made to mount discrete power supply components directly onto the p.c.b. so that the unit can be fully independent of other equipment.

can then be controlled by either a varying voltage or a varying current. For normal manual selection of the desired frequency, current control is used, and is relative to the resistance of the total of VR4, VR5 and R8. In this mode VR5 is taken directly to ground by S5. As the resistance of these potentiometers decreases, so the output frequency rises in relation to the formula: $f = 1/(R \times (C/1000)) \times 1000$, where C is the value of the selected capacitor C4 to C7 in microfarads, and R is the total resistance in circuit with pin 8 of IC2.

VR4 provides coarse tuning of the frequency, and VR5 fine tuning. The maximum resistance range that is permissible with IC2 is from 1K to 2M, though is limited to a maximum of about 1M in this unit. This allows a reasonable overlap between the switched ranges, without making the

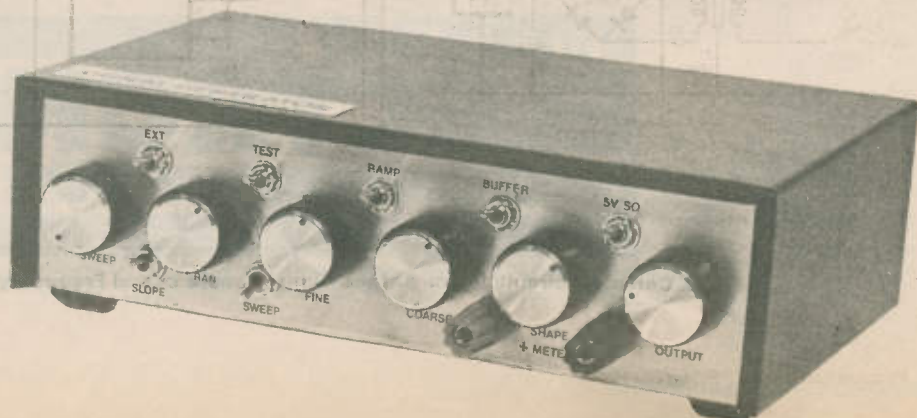Photograph illustrating the external assembly of the Signal Generator and F-V Converter



SPECIFICATION...

TOLERANCE

The figures quoted refer to those obtained on the prototype and may vary slightly in other units in accordance with normal component tolerance factors.

FREQUENCY TO VOLTAGE CONVERTER

Good linearity from 200Hz to 30kHz directly readable on a standard multimeter or digital voltmeter. Accessible internally and externally.

FREQUENCY GENERATOR

Basic switched frequency ranges = (1) 2Hz to 81Hz, (2) 20Hz to 851Hz, (3) 200Hz to 8400Hz, (4) 1970Hz to 78800Hz. Coarse and fine tuning of selected frequency range. Switch selected waveforms—sine, triangle, square, ramp, pulse, and variations (see photographs 1–6). Sweep modulator—rising and falling ramps, switch selectable, rate 6 to 40 cycles per minute. Frequency outputs—switched, buffered or unbuffered via amplitude control from nil to 5V peak to peak. Fixed 0V/+5V amplitude square wave derived from internal oscillator or external source up to about 80kHz. Four switched reference frequencies.

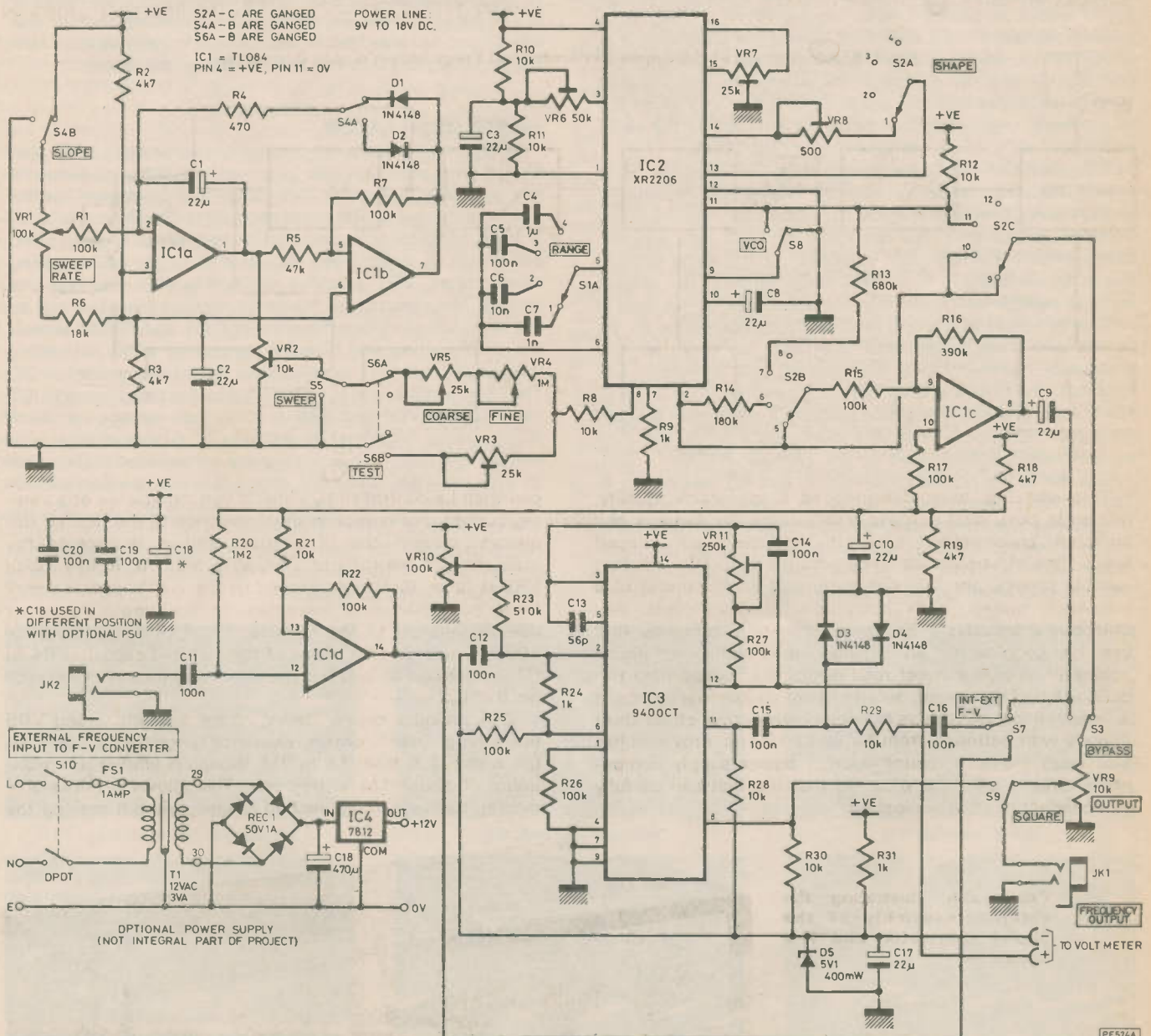


Fig. 2. Complete circuit diagram of the Signal Generator and Frequency-Voltage Converter

fine tuning too coarse. Switching in VR3 by S6 instead of VR4 and 5, a preset reference frequency can be selected. The i.c. contains its own current controlled amplifier and the amplitude of the signal generated as seen at pin 2, is pre-settable by VR6. This controls the sine, triangle, and ramp waveform maximum levels. The squarewave however is derived from a different section and is at approximately full line level amplitude as determined by the current through the load resistor R12. The shape of the triangle and ramp waveforms is predetermined within IC2 itself. For sine wave related waveforms, shaping is preset by VR8, and the symmetry trimmed by VR7.

WAVEFORM SELECTION

Three basic waveform selections can be chosen with S2. With S8 open, the choice is sine, triangle and square. In position 1 (sinewave) the output comes from pin 2 of IC2, and VR8 is in circuit, controlling the sine shape. In position 2, (triangle wave), the output again is from pin 2, but at a level approximately twice that of the sine wave and VR8 is out of circuit. In position three (squarewave), the output is taken from pin 11 IC2. With S8 closed the squarewave is directly fed to the control pin 9, and internal circuitry of the chip is automatically switched by it to produce ramp related waveforms in the first two positions of S2. In this mode the frequency of oscillation now becomes affected by the value of R9 and the formula changes to: $f = (2/C/1000) \times (1/R) \times 1000$, using the same parameters as before. Effectively this means that the frequency with S8 closed will be approximately twice that with it open. In position S2, looking at the inverted output of IC1C, the rising ramp is sine shaped, followed by the steep drop. In position 2 the rising ramp is linear, again followed by a steep drop. Study of the second formula though will show that the steepness of the drop is related to values of R9, and the controlling resistance on pin 8. As the two resistances approach equality, so the steepness lessens, and a falling ramp also develops. The best ramps are thus created with the resistance on pin 8 at the greater end of the scale. In position 3 the output is again from pin 11, but consists of a mark-space pulse, the duty cycle of which determined by the formula: $RA/(RA + RB)$, where RA is the resistance on pin 7, and RB that on pin 8. The negative going pulse length is moderately constant throughout the range for the same capacitance selection. The mark-space factor is also reflected in the shape of the ramps with a flattening of the apex, but is really only noticeable at small values of capacitance.


OUTPUT ROUTING

In most instances it is preferable for the amplitude of the different waveforms seen at the final output to be roughly equal. As previously seen there is an inherent level difference between the three main waveform ranges, IC1C is thus included to even these out. The gain of this stage is of course dependent upon the relationship of the total input resistance to the value of the feedback resistor R16. The choice of resistors R13–R15 ensures a reasonable match of the levels. The inverted phase output from IC1C is decoupled by C9, taken via S3 to the level control VR9 and then to the output via S9. However the frequency pass range of IC1C is less than that of the range available from IC2. For normal audio applications, the frequency response of IC1C is sufficiently adequate, but distortion becomes more prevalent as the frequency rises above about 30kHz, as shown in the oscillograms.


Additionally the loading of C9 causes square wave distortion at lower frequencies. S3 is thus included to bypass IC1C so that the output is unbuffered allowing the full range of IC2 to be used. Note though that the unbuffered output also contains a d.c. bias that is approximately half line level with S2 in positions 1 & 2, and that the phase is inverted.

SWEEP OSCILLATOR


When testing out some circuits it is sometimes preferable for the frequency range to be swept upward or downwards at a controlled automatic rate rather than by manual control of a potentiometer. The ramp generating circuit around IC1A & IC1B provides this control. The frequency range of ramp generation is determined by C1 with larger values giving slower rates. VR1 provides the tuning of the sweep rate setting. The direction of the ramp produced is governed by the direction of voltage flow through D1 and D2. S4 selects the diode routing, and reverses the polarity of the controlling voltage through VR1 in relation to the reference level at C2. The changing d.c. voltage produced by the ramp controls IC2 via VR2, S9, VR4 and VR5. In this mode voltage control of IC2 is being employed in addition to current control. For correct operation of IC2 the voltage sweep seen at the wiper of VR2 must lie below 3V, above this and the oscillator of IC2 will cease. VR2 thus needs adjustment to keep the sweep voltage within this range. The frequency control range provided by the varying voltage is less than that produced in the manual mode, and VR4 and VR5 are used to select the desired band width.

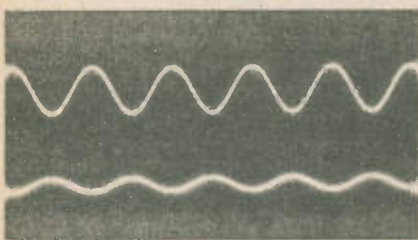


Sine (normal) S2₁

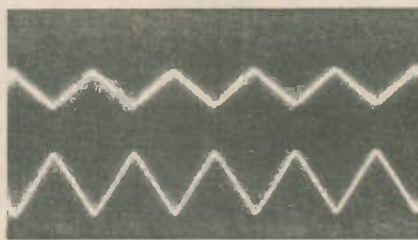


Triangle (normal) S2₂

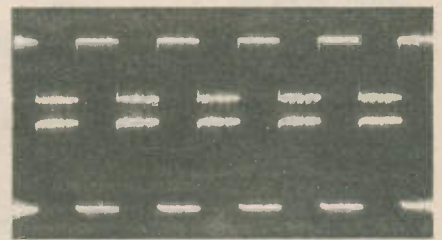


Square (normal) S2₃

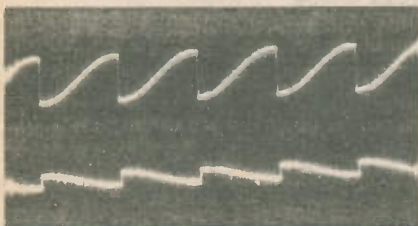


Sine (ramp) S2₁

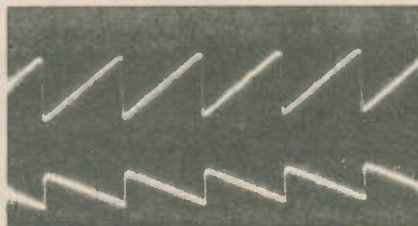


Triangle (ramp) S2₂

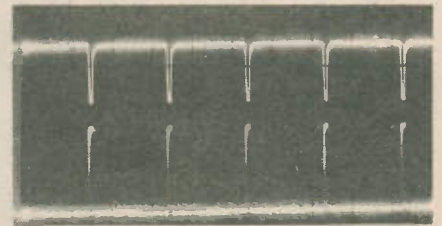


Square (pulse) S2₃

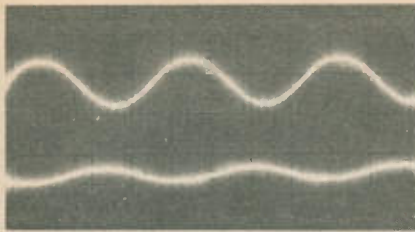

Sine (high freq) S2₁

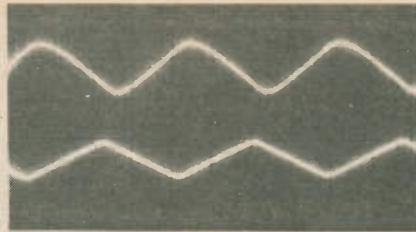

Triangle (high freq) S2₂

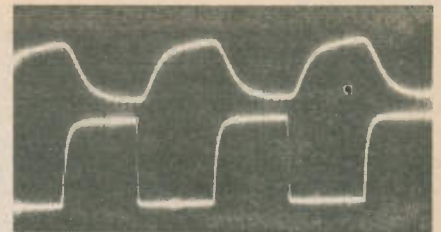

Ramp (high freq) S2₃

FREQUENCY TO VOLTAGE CONVERTER

IC3 performs the f-to-v conversion, producing an output voltage that, within the range, is related linearly to the frequency fed in. The range available is determined by the gain given to the feedback via R27 and VR11, with a slew rate and ripple reduction level set by C14. High values for C14 will give reduced ripple for lower frequency signals, but will increase the time taken for the voltage to stabilise when the frequency is changed. The relative minimum output voltage in the absence of an input frequency should be as close to zero as can be set by the bias control VR10. VR11 is used to set the maximum range. The output voltage is referenced to an intermediate level of about 5V as set by Zener diode D5. The negative lead of the meter used to monitor the voltage is taken to this level, and the positive lead to the output from pin 12, IC3. If the meter negative lead were to be taken to the normal 0V or ground line then the reading would also contain the reference voltage of 5V and inaccurate readings would result. For stable operation of the conversion, the input frequency seen at pin 11, IC3 should be at a constant level of about 1V p-p. To maintain this amplitude even for low level input signals, the signals are taken via the gain stage IC1D for external signals which gives an amplification of about, a little over 100. The signal is then attenuated to the optimum level by diodes D3 & D4. For internal frequency reading, the signal is taken direct from the output of IC1C, and similarly attenuated. S7 selects the choice of internal or external frequency monitoring. In addition to producing a frequency related voltage, IC3 also produces a square wave output of 5V amplitude. There is a slight time lag between the edges of the input frequency and of the out-

put 5V squarewave. S9 can switch in this frequency output in place of that produced directly by IC2. This means that an external frequency of indifferent level and shape can be converted for controlling circuits that require a 5 volt squarewave. The external loading permissible though is limited by the value of R30 and too great a load will reduce the voltage.

POWER SUPPLY

Most enthusiasts probably already have power supplies in their workshop capable of driving this unit, and so a separate one is not included. The minimum voltage requirement is 9V, and the maximum permissible +18V as dictated by the limits of IC3. The current drawn is about 30mA, up to 20mA of which is consumed by IC2. This current is a bit too high for the unit to be powered for long periods from a battery supply, though one could be used briefly in an emergency. Alternatively a battery eliminator might be suitable, providing it can tolerate the current without the voltage dropping below 9V and that the ripple content is negligible. The printed circuit board though includes positions for the mounting of the rectifier and voltage regulator as shown in the suggested optional 12V power supply circuit. This supply was not used in the prototype and is not regarded as an integral part of the project. The transformer should be bolted to the metal box, and normal mains electricity safety precautions observed. Note that with this suggested power supply C18 has its positive end connected to a different track position, and it may be necessary to mount it vertically rather than horizontally. The use of a heat sink with the regulator i.c. should not be necessary.

COMPONENTS . . .

RESISTORS

R1,R7,R15,R17,R22, R25-R27	100k (8 off)
R2,R3,R18,R19	4k7 (4 off)
R4	470
R5	47k
R6	18k
R8,R10,R11,R12,R21	
R28-R30	10k (8 off)
R9,R24,R31	1k (3 off)
R13	680k
R14	180k
R16	390k
R20	1M2
R23	510k

All resistors $\frac{1}{4}$ W $\pm 5\%$

CAPACITORS

C1-C3,C8-C10,C17	22 μ , 10V elect. (7 off)
C4	1 μ , 63V elect.
C5,C11,C12,C14-C16, C19,C20	100n polyester (8 off)
C6	10n polystyrene
C7	1n polystyrene

C13
C18

56p polystyrene
470 μ , 25V elect.

SEMICONDUCTORS

IC1	TL084 (quad op-amp)
IC2	XR2206
IC3	9400CT (R.S. 307 070)
D1-D4	1N4148 (4 off)
D5	5V1 Zener, 400mW

POTENTIOMETERS

VR1	100k mono rota
VR2	10k skeleton
VR3,VR7	25k skeleton (2 off)
VR4	1M mono rota
VR5	25k mono rota
VR6	50k skeleton
VR8	500 skeleton
VR9	10k mono rota
VR10	100k skeleton
VR11	250k skeleton

MISCELLANEOUS

P.c.b. and p.c.b. clips (4 off)
Round knobs (6 off)
I.c. sockets, 16 pin, 14 pin (2 off)
Jack socket, 3.5mm
Jack sockets mono (2 off)
Box and rubber feet
Meter terminals (2 off)

SWITCHES

S1,S2	3P4W (2 off)
S3,S5,S7-S9	SPDT (5 off)
S4,S6	DPDT (2 off)

Constructor's Note

A complete kit of parts is available from: **Phonosonics**, 8 Finucane Drive, Orpington, Kent BR5 4ED. Price £54.00, inclusive of VAT. Post and packing £1.00.

ASSEMBLY

After the straight forward component assembly and subsequent joint checking procedure has been carried out, wiring should be commenced in a methodical fashion, ticking off each wire on the wiring diagram as connections are made. First connect up all the panel controls between themselves. Secondly wire up to all the p.c.b. points closest to the front panel. Finally connect up the rear and remaining connection points. These latter wires should preferably be brought under or round the edges of the p.c.b. Taking them over makes the wiring untidy. Keep the wiring short, but long enough for turning the board over for examination without over straining the connections (too much flexing of taut wires can cause breaking at the joins). The prototype has the meter terminals on the front, but with hindsight, mounting them on the back would be better.

The regulator IC4, and the rectifier REC1, are part of the optional power supply, together with the transformer T1. These components may be omitted if not required as the unit will run quite efficiently from any 9V battery.

SETTING UP

A fair selection of presets has been included to enable the maximum accuracy to be obtained throughout the unit. The only really critical one is VR2, as the sweep control may not operate if this is incorrectly set. Inadequate setting of the others will only cause lack of linearity. If an oscilloscope is not available intelligent decisions will need to be made, listening to the sounds while adjusting the presets.

First, S1 position 1 (lowest freq), S2 position 1 (sine), S3 on (buffered output), S4 either way, S5 off (sweep off), S6 off (manual freq control), S7 off (internal f-v), S8 off (standard waveforms), S9 off (vco output), VR1-3 midway, VR4-5 max clockwise (highest freq), VR6-8 midway, VR9 max, VR10-11 midway. Switch on and check that pin 3 IC1A, pin 3 IC2 are at approximately half line voltage, and that the positive end of D5 is at about 5V. Plug in to normal amplifier. If no sound is heard then check the wiring, and that the switches are wired the correct way up. Assuming that sound is heard, check that VR4 and 5 vary the frequency, and that S1 changes the ranges. Switch on S6, and adjust VR3 to the desired fixed frequency on the second range of S1. In the author's unit this was set for approximately 440Hz. Check that S8 brings in the ramp associated

* DOTTED LINE SHOWS CONNECTION OF C18 IF OPTIONAL PSU IS USED
 ** IC4 AND RECTIFIER ARE PART OF OPTIONAL PSU AND NOT INTEGRAL PART OF PROJECT.


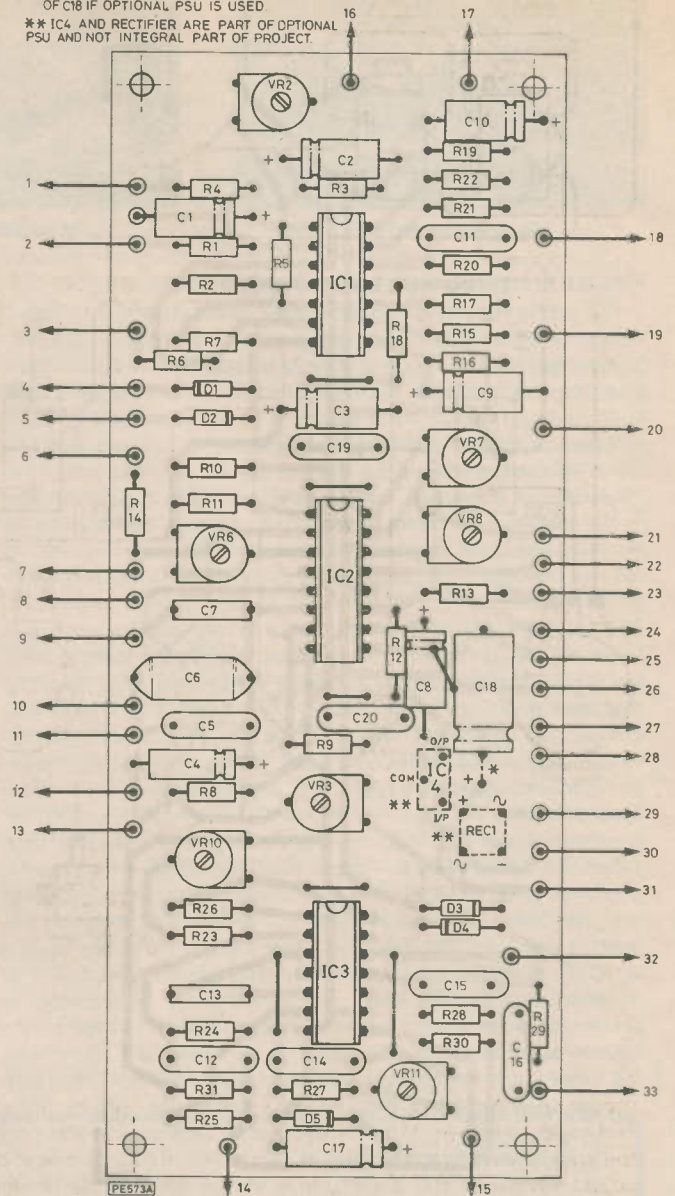


Fig. 3. (Above) Showing the p.c.b. design and component layout of the Signal Generator. (Left) Photograph illustrating the internal view of the chassis assembly showing the switch, sockets and p.c.b. layout

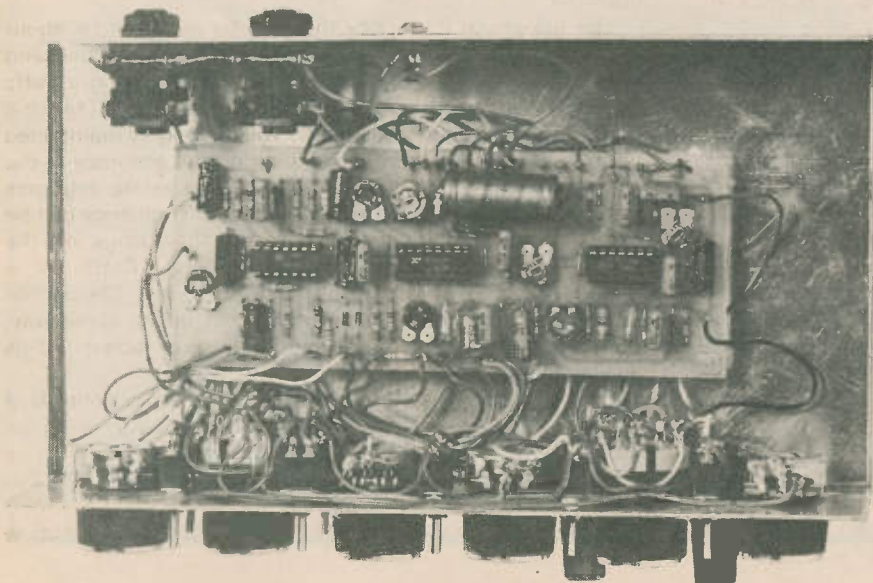

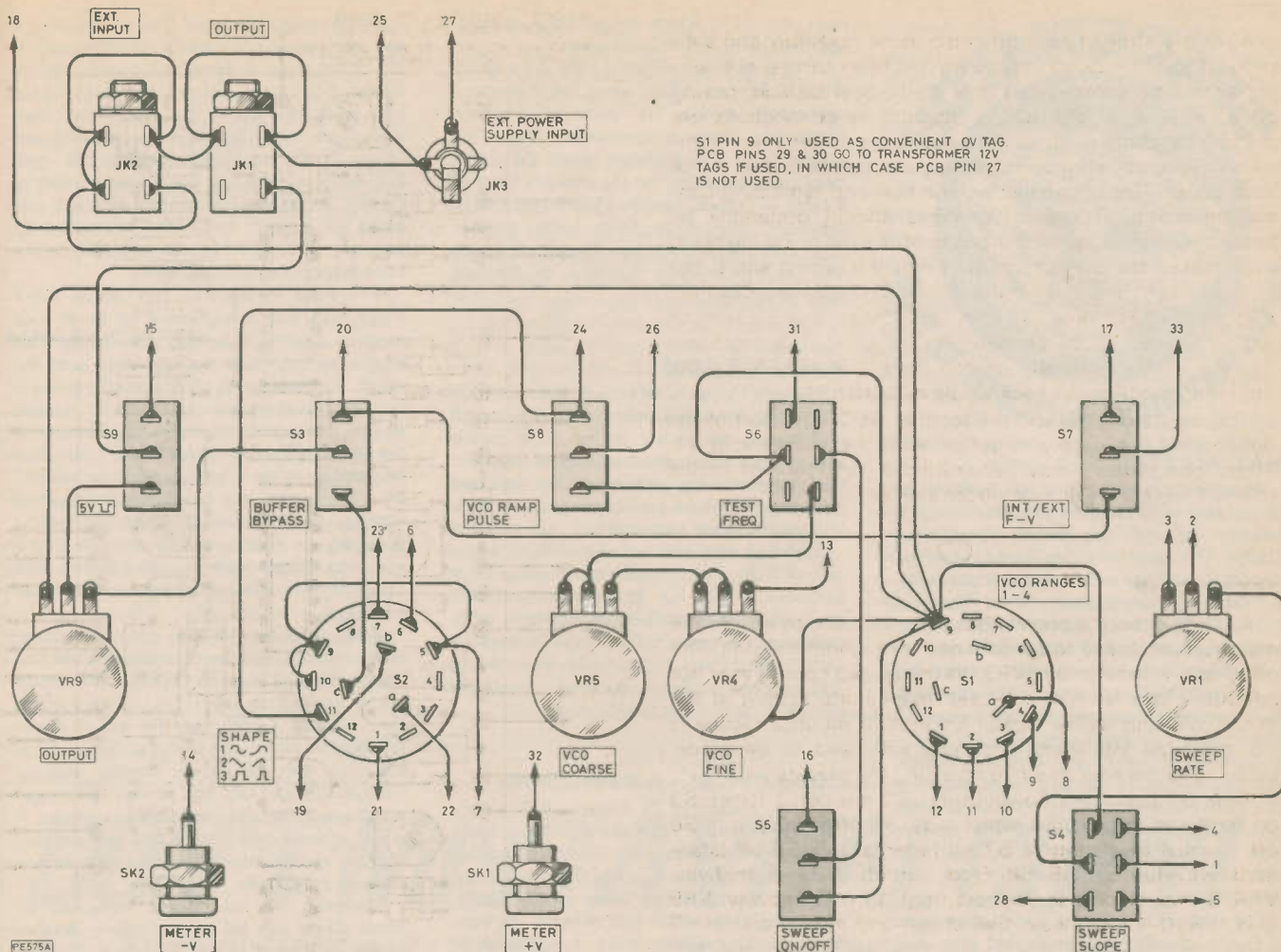


Fig. 4. Wiring diagram of the Signal Generator

ranges of waveforms, then switch back to the normal range, and to squarewave. Monitor the output jack socket and note the squarewave amplitude level. Switch to triangle wave and adjust VR6 until the amplitude is similar without flattening of the waveform peaks. Switch to sine wave and adjust VR8 for the best sine shape, then VR7 for the best symmetry. If necessary readjust VR8.

Switch S3 to bypass and check all waveforms can be switched in, though as previously stated they will be at widely varying levels. Switch S6 back to manual control, then S5 to sweep control. Check that a ramp waveform appears at pin 1 IC1A, and that switching S4 varies the direction, also that VR1 varies the rate with the ramp in both directions. Return scope probe to the output jack socket, and adjust VR2 for the smoothest sweep response. If the wiper is too far to the OV end the generator frequency will dwell at the high end, with it too far towards IC1 the generator will cut out at the low frequency end. With careful adjustment a smoothly varying rising or falling sweep range can be set. Switch off the sweep control and set a frequency output from IC2 of precisely 10kHz. Check that an attenuated version of this frequency reaches pin 11 IC3 via S7. With the external input jack socket grounded (as it will be without a jack plug in), switch S7 to external. Connect a multimeter across the meter output terminals and adjust VR10 for a reading of exactly zero volts. Start off with a meter range of

about 5 volts, then after the initial adjustment has been made the meter can be switched to its lowest range for greater precision. Set meter to a range for monitoring exactly 1V. Switch S7 back so that the 10kHz signal reaches IC3. Very carefully adjust VR11 until a precise voltage of 1 volt is obtained.

The maximum frequency that can be read will be about 30kHz to 35kHz, beyond this IC3 will fail to respond and show a constant reading of around 3.5V. Applying a 1kHz signal should produce approximately 0.1V. Tracking downwards in frequency, linearity will be roughly maintained until about 200 Hz or so, depending on the accuracy of the setting of VR10 and VR11. Once the boundary extremes have been established, a direct reading of frequency can be taken from the multimeter by converting the voltage into the readily calculable frequency. Thus if 1V = 10kHz, 3V = 30kHz, 0.5V = 5kHz, 0.05V = 500Hz, etc. Check that an external frequency can be monitored in the same way, then finally that a squarewave output of about 5V is available from pin 8 to IC2.

After setting up the f-v converter the frequency controls of the unit can be calibrated and control legends applied to the panel, using a rub down lettering like letraset or similar, then coating them with a suitable spray protector. If care has been taken in the setting up, the end result will be a marvellously versatile dual purpose new unit for the workshop. ★



RING MASTER

Perhaps the most interesting development during the past few months has been the visual detection of the ring-system surrounding Uranus. The rings were first found indirectly, because they produced a series of occultations of a faint star; subsequently, D. A. Allen and J. Crawford, at Siding Spring Observatory in Australia, photographed them in infra-red.

Studies of them have now been carried out by Richard Terrile and Bradford Smith, using the 2.5-metre reflector at the Las Campanas Observatory in Chile together with a highly sensitive CCD or Charge-Coupled Device. The ring-system is clearly shown, together with all five known satellites—Miranda, Ariel, Umbriel, Titania and Oberon. The pictures show the great power of the CCD, which is at least thirty times more sensitive than any photographic plate.

The rings of Uranus are quite unlike those of Saturn. Terrile and Smith find that their albedo or reflecting power is only about 2 per cent, so that they are blacker than coal-dust. They are also narrow; there are at least eight

rings, not all of which are perfectly circular, and their composition is unknown.

If all goes well, we should learn more about them in January 1986, when the *Voyager 2* spacecraft makes its pass of Uranus. Meanwhile, there is speculation about the possibility of a ring-system round the outermost giant, Neptune, but the presence there of a large retrograde satellite (Triton) may have prevented any rings from being formed. Again, we pin our hopes on *Voyager 2*, which will rendezvous with Neptune in the late summer of 1989.

HALLEY'S COMET

Halley's Comet is, of course, still much too faint to be detected except with very powerful instruments, but recent studies show that it may prove to be somewhat brighter than had been expected. Unfortunately, this does not mean that it will be a brilliant spectacle, as it has been on many past returns.

It should become a naked-eye object at the end of 1985, before perihelion passage on 9 February, 1986, but British observers will need clear skies. When at its best, after perihelion, the comet will be in the far south—well placed for Australians and South Africans, but not for Europeans, who will not see it at all until it has faded considerably.

NOVA CYGNI—A NEW LOOK

On the evening of 29 August, 1975, I went into my observatory to make some routine observations of variable stars. When I looked up at the familiar constellation of Cygnus, I had a surprise. There, shining down unmistakably, was a bright star which had certainly not been there on the previous night. I estimated its magnitude as 2.4, slightly fainter than Gamma Cygni, the central star of the "cross" of Cygnus.

Having satisfied myself that it really was a new star or nova, I made a telephone call to the observatory at Herstmonceux. I was, of course, fairly sure that the star had already been reported—and so it proved; it had been discovered some hours earlier by Kentaro Osada in Japan, before darkness fell over England. I imagine that I was about sixtieth in the list of independent discoverers; the star could not possibly have been overlooked by anyone with more than a rudimentary knowledge of the constellations.

The most remarkable fact about Nova Cygni was that it brightened up by at least nineteen magnitudes in only a few hours. This was a record, both for amplitude and for speed. Its decline was also unusually quick. I estimated its magnitude as 1.8 on 30 August, so that it was then much the brightest star in the constellation apart from Deneb; but it had dropped to below 3 by 1 September, below 5 by 4 September, and faded below naked-eye visibility by 7 September, when I saw it as fiery red—in fact, as red as any star I have ever seen. Within a few months it had become too faint to be observed except with powerful telescopes.

Apart from Nova Cygni, only three novae seen since 1930 have attained the first magnitude: DQ Herculis (1934), CP Lacertae (1936) and CP Puppis (1942), though others have become visible with the naked eye—notably HR Delphini, which was discovered in 1967 by the well-known English amateur George Alcock and had a very prolonged maximum of around the fourth magnitude. It is still above magnitude 13, and probably will not fade much further, as this was also its pre-outburst magnitude.

However, the exceptional behaviour of Nova Cygni has led to particularly detailed studies of it, and efforts have been made to detect a cloud of debris round it. This has now been a successful operation.

THE SKY THIS MONTH

Winter skies are always glorious, thanks to the presence of Orion, the Hunter, and his magnificent retinue, but at the moment the dearth of bright planets continues—apart from Venus, which is at its very best in the evenings. Mercury is, in theory, a morning object, and may indeed be glimpsed just before sunrise, but it is well south of the celestial equator, so that European observers are unfavourably placed.

Mars may be seen in the south-west during the early evening, and moves from Aquarius into Pisces by the end of the month, but its magnitude is now only 1.2, and no telescope will show much upon its surface. Saturn, in Libra, rises well before the Sun, but is low down and by no means prominent, while Jupiter passes through conjunction on 14 January and is therefore out of view altogether. There are no eclipses this month, and no bright comets are expected. The Moon is full on 7 January, and new on the 21st.

During winter evenings the brilliant yellow star Capella is almost overhead (a position occupied by the equally brilliant Vega during evenings in summer). Close beside Capella lie the three fainter stars making up a triangle. They have been nicknamed the Haedi or 'Kids', and two of them are very remarkable objects.

Epsilon Aurigae, at the apex of the triangle, is an extremely luminous supergiant, at least 60,000 times as powerful as the Sun. Every 27 years it fades down by almost a magnitude, not because it is intrinsically variable but because it is being eclipsed by a companion which has never been seen at all.

The nature of the invisible secondary is still a matter for debate. It was once believed to be a very young star, not yet hot enough to shine; there were also suggestions that it might be a black hole, but it now seems more likely that it is a relatively small, hot star with an associated extensive shell of material. The last eclipse ended in 1984, so that for more than two decades nothing further will be happening.

Look at the 'Kids' and you will see that Epsilon is now the brightest member of the trio. The faintest, Sadatoni or Zeta Aurigae, is also an eclipsing binary with a period of 972 days, but we know much more about it; the primary is a red supergiant, while the secondary is a much smaller and hotter star.



It is sheer coincidence that these two exceptional eclipsing binaries lie side by side in the sky. There is no true connection between them; Epsilon is much further away from us than Zeta.

Ingenuity Unlimited

A selection of readers' original circuit ideas. Why not submit *your* idea? Any idea published will be awarded payment according to its merits. Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not in the text.

THERMISTOR

THERMOMETER

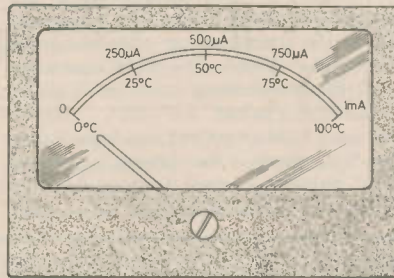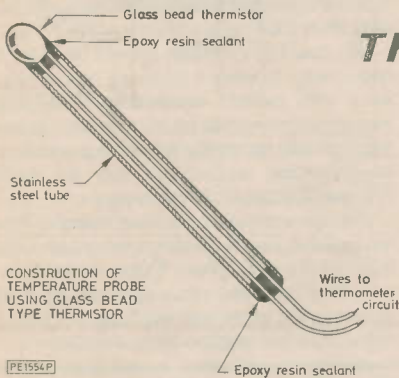

Construction and calibration of the Thermistor Thermometer

RT	R1	R2	R5	R6	R7
JA-03	7k5	5k6	22k	1k2	0 C.
VA3704	10k	6k2	10k	1k	10k

TABLE 1


°C	0	30	70	100
ERROR	+3.3	-2.0	+1.7	-2.6
AT	+4.0	-2.5	+2.2	-3.2

TABLE 2

THE conventional bridge circuit recommended for thermistors is somewhat inaccurate. Better results can be obtained using the arrangement shown here. The op. amp, IC2 acts as a voltage source, with current measured by the meter ME1. This configuration corrects for most of the thermistor's non-linearity. An offset current flows through R5 and VR1, and sensitivity is set by VR2 and R6. Assuming a full-scale current of 1mA, an output of 1mV/°C is conveniently obtained at the output and this can be used to drive a chart recorder, for example. The supply voltage is regulated by IC1, and a 3-way switch allows the battery to be checked. Resistor values for two types of NTC thermistor are given in Table 1. JA-03 is metal-sheathed (RS no. 151-120) and VA3704 (Mullard no. 2322-627-11472) is a glass-bead device. Both have a resistance at 50°C, of the order of 1k7.

Kettles and ice-buckets are unpredictable gadgets! Calibration was done at 10, 50 and 90°C, using a water-bath and laboratory-grade mercury thermometer. The error curve is cubic, with a deviation within 2 or 3 degrees centigrade over most of the range, increasing near the 0° and 100°C limits.

C. J. D. Catto,
Elsworth,
Cambridge.

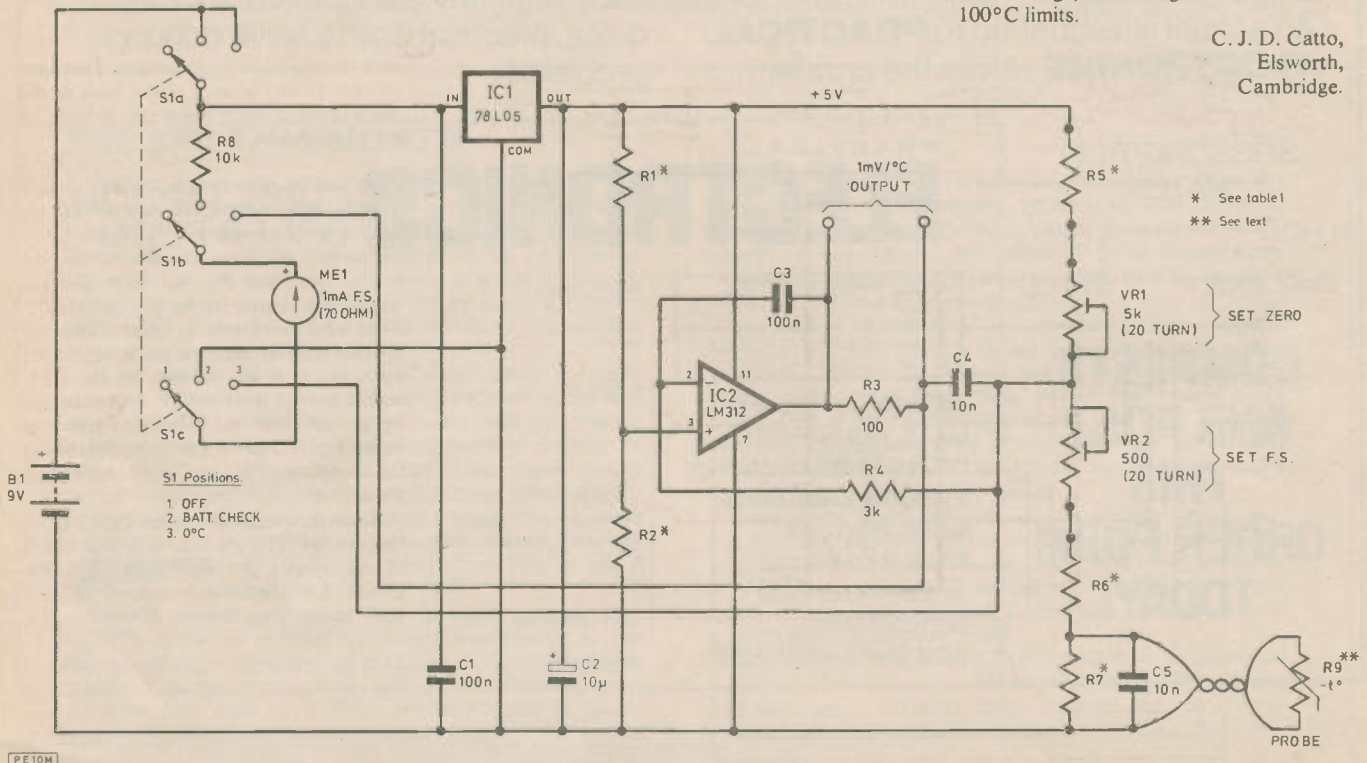

LOGIC RECORDER

THE logic recorder is designed to fill the gap between the logic probe and the logic analyser by displaying a sequence of eight data bits on a bank of i.e.d.s. Data is stored synchronously with the system clock after a trigger pulse from the circuit under test.


Data is fed into IC4, an octal D-type flip-flop wired as a shift register, though a 74LS164 shift register could be used instead. D2 represents the most recent data.

Suppose that latch IC1a/b is set so that D10 is unlit. IC1 pin 6 is high so IC3 is reset, its 'A' output is low, IC1d is disabled and IC1c is enabled via IC2b. When the ARM button is pressed the latch sets, lighting D10 and freeing IC3 to count. On the rising edge of IC2c pin 8, the single-bit counter in IC3 clocks, disabling IC1c and the ARM button and enabling IC1d to clock IC4 and, via IC2d, the 3-bit section of IC3.

After eight clock pulses from the system under test, IC3 pin 11 goes low, resetting the latch via C1. Provided that the ARM button has been released the logic recorder resets and displays the data received until it is rearmed.

IC2a and IC2c are used as programmable inverters to select the desired trigger and clock edges. D1 protects the recorder against reverse polarity on its power supply leads which are connected to the test circuit.

G. Strange,
Loughborough,
Leics.

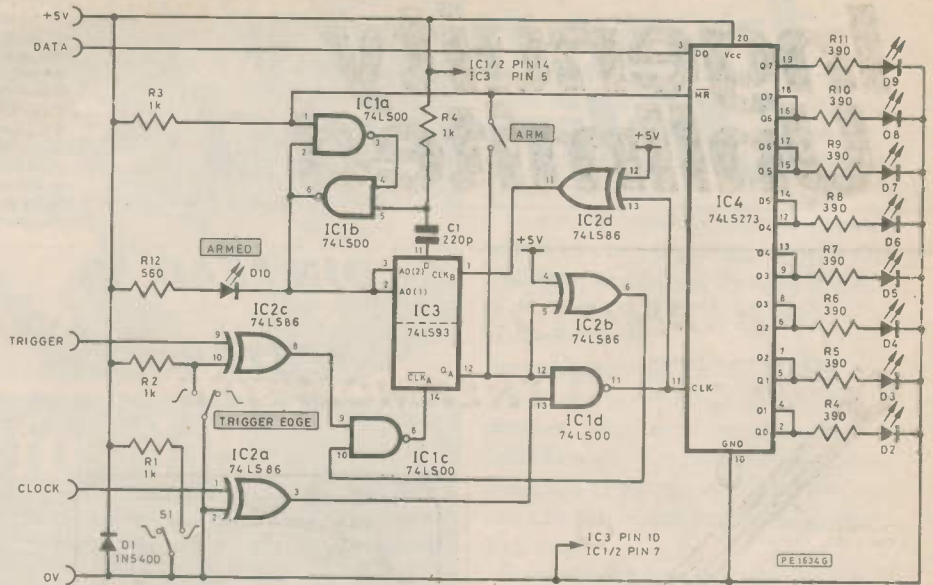

May be 1 or 0

D7	D6	D5	D4	D3	D2	D1	D0
1	1	X	X	X	X	X	X
128	64	32	16	8	4	2	1
1	1	1	0	1	0	1	1

e.g. D2 and D4 are low
 $128 + 64 + 32 + 0 + 8 + 0 + 2 + 1 = 235$

Table 1. Showing example of IN127 command

ZX SPECTRUM BUFFERED INPUT PORT (6 BIT)


MOST designs for input ports use devices such as the 74LS245 octal transceiver, but during the current chip shortages, these devices are either impossible to obtain or very expensive. There are other possible buffering chips, such as the 74LS126, but these are more difficult to design a circuit layout for.

In my design I have used the 74LS365 Hex buffer/driver with gate enable inputs—the only disadvantage is that we now have only 6 inputs.


The circuit itself is very simple: the port is I/O mapped by A7 and address decoding is performed by IC1, a 74LS02. Thus when the following control lines are low— \overline{IORQ} to indicate an input output operation and \overline{RD} to indicate the CPU wishes to read from the I/O port indicated by the address on the address bus. The outputs of IC2 are put onto the databus of the computer. C1 and C2 are decoupling capacitors.

Since the circuit is mapped by A7 being low, an IN127 command will give 255 if all inputs are high (logic 1), as will be the case if they are left unconnected. If bit 1 (D0) is low then the result will be 254. Possible results are summarised in Table 1. Thus the result of an IN127 command in this case would be 235.

A. Moran,
Reading,
Berks.

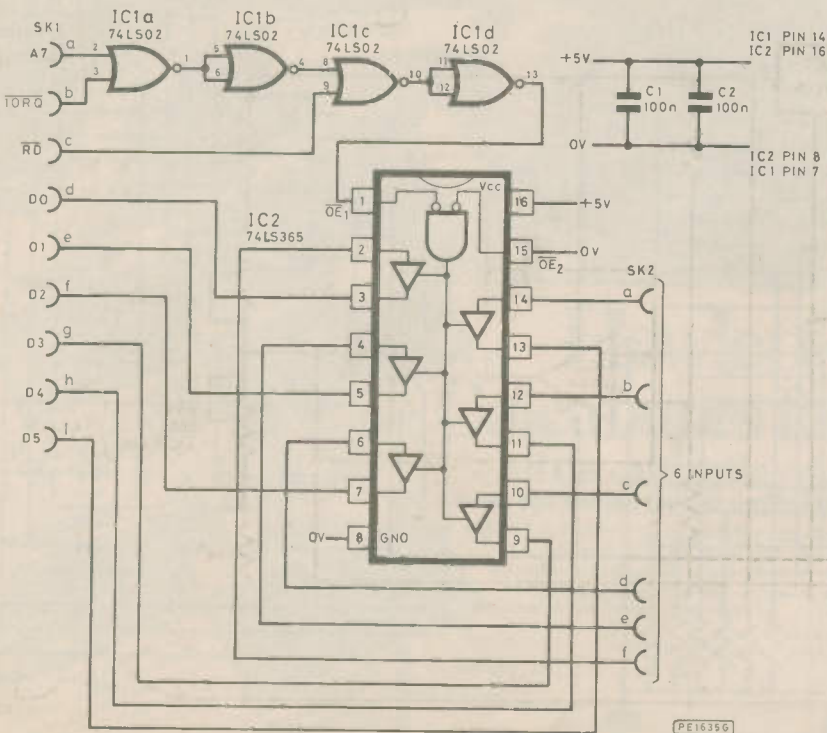

Ingenuity Unlimited

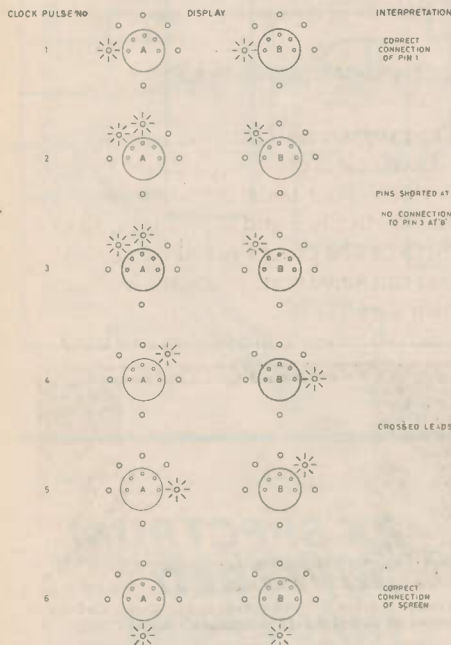

DIN LEAD TESTER

HAVE you ever wondered whether all your problems might just be due to a faulty DIN lead? If so, you'll no doubt have discovered what an awkward operation it can be to test one; but here is a simple solution.

The following design will test DIN leads for open circuit, short circuit and wrong connections all in one go. Whereas with a continuity tester you need to test each pin individually, this circuit gives an immediate indication of the connections (or lack of connections) between pins at either end.

IC1 is a 4017, which is a decade counter with decoded outputs. It sends each pin high, in sequence, moving on to the next

one every time it receives a clock pulse. For a 5 pin DIN, the sixth output is connected to reset and thus counts through 0,1,2,3,4 and 5. Six pulses are allowed to enable the screen to the tested separately (note however that this is often connected to the middle pin). The clock used to drive IC1 is produced by a standard CMOS oscillator based around IC2 (a 4011 quad NAND), the NAND inputs being shorted together as shown to act as inverters. This i.c. type was chosen merely so that fewer gates were left unused. A hex inverter would serve just as well. IC3 and IC4 are 4050 hex buffers used to drive the l.e.d.s.

The clock frequency is normally about 1kHz, providing an apparently constant display. In this mode any broken connections will immediately show up as unlit l.e.d.s at 'B'. By pressing switch S1 the 68k resistor R1, is disconnected and the clock frequency reduced so that a more detailed representation of the condition of the DIN lead is given. Two common types of 5 pin DIN lead exist; straight through and mirror image.

STRAIGHT THROUGH—L.e.d.s at 'A' and 'B' should light in the same order.

MIRROR IMAGE—L.e.d.s at 'A' and 'B' should light in opposite orders. Crossed leads can thus be detected by incorrect orders at 'B'.


Any two l.e.d.s lit simultaneously at one end in this mode indicate shorted leads at that end.

Some sample displays are given. Using CMOS logic, the unit can be readily powered by a 9V (PP3) battery.

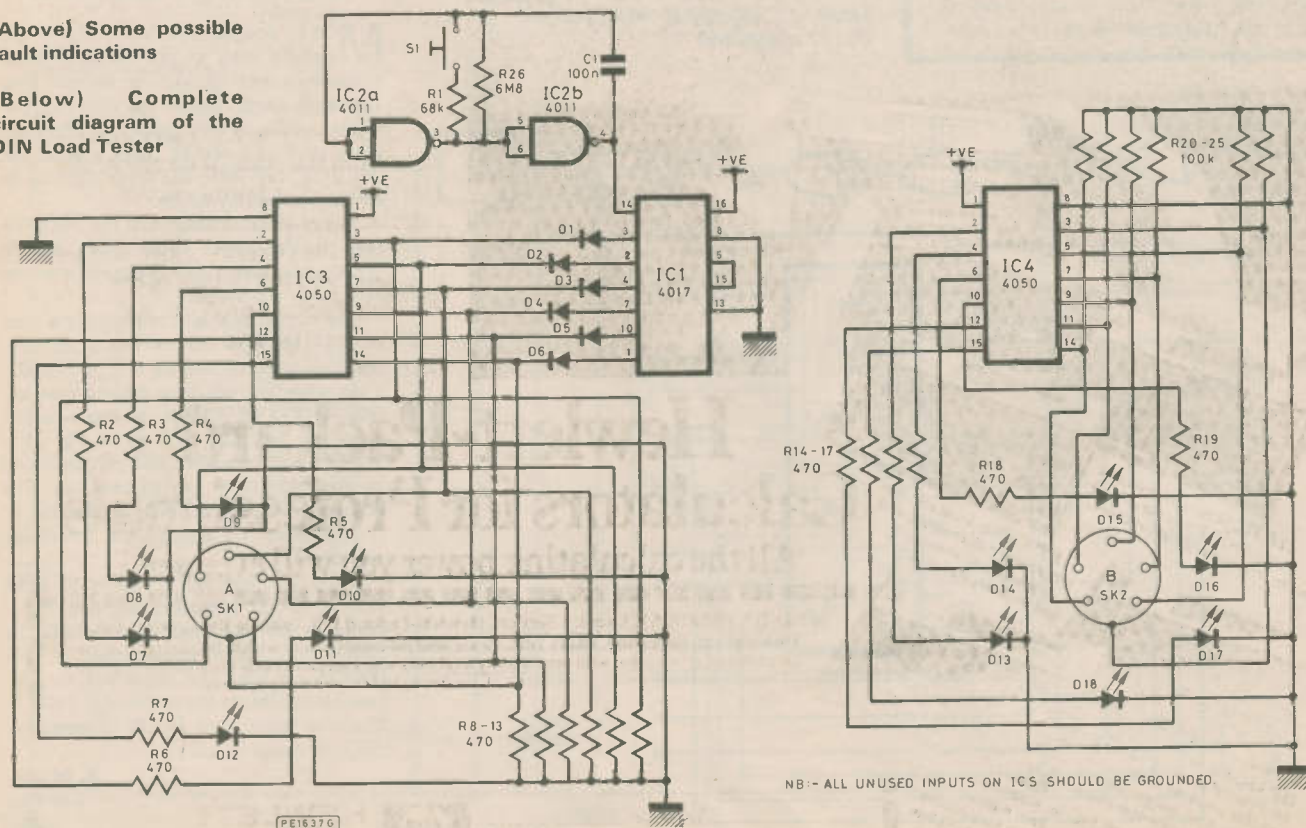
C. Walden,
Selby,
S. Yorks.

(Above) Some possible fault indications

(Below) Complete circuit diagram of the DIN Lead Tester



From your student days...

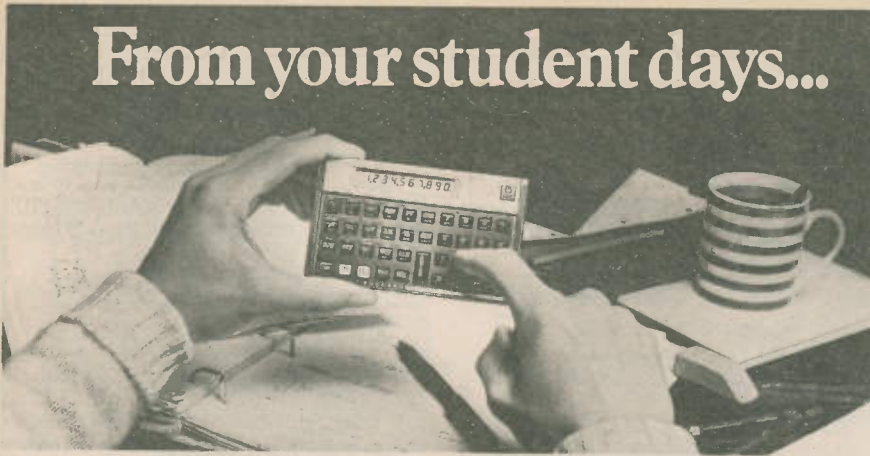

to your first job...



to your own company...




An instant answer to every calculation you will ever make? With a Hewlett-Packard Professional Calculator, the answer is yes. We introduced Calculators for Professionals—sophisticated, powerful calculating facilities—around ten years ago, and our range has a calculator built for the kind of work you do.

There is a professional calculator for scientists and engineers, for software and computer specialists, for higher mathematics activities and for business users.

Pre-programmed for your needs

Each one is pre-programmed to perform your usual calculations automatically—and in addition, all of them can be programmed by you so you can solve your problems in your own way.

So wherever you are, you can have

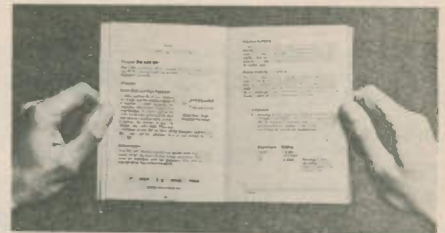

A complete manual of instructions and programs has been written for each of the HP professional calculator range.

answers you can depend on, always at your fingertips. With the minimum of effort, in the minimum of time. Each has a memory that will store information even with the power off. And will come with an owner's handbook, so you are operational right from the start. You can see the Hewlett-Packard professional calculators at your dealer. Or complete the coupon below, and we will send you full details of the Hewlett-Packard professional calculator range and how it can help you.

Hewlett-Packard Calculators for Professionals

All the calculating power you will ever need.



HP 11C is for scientists and engineers. Pre-programmed maths, trig, log and stat functions.

HP 12C for business. Pre-programmed discounting and depreciation, interest and business statistics.

HP 15C for mathematicians. 448 bytes of program capacity, complex numbers facility, root finding, integration and ten matrix operations.

HP 16C for software activities. Four number bases, versatile bit manipulation and up to 64 bits in binary.

SEND TO: FREEPOST, Enquiry Section, Hewlett-Packard Ltd, Eskdale Road, Winnersh, Wokingham, Berkshire, RG11 1BR. Please send me details of the Hewlett-Packard professional calculator range (together with details of my local stockists). I am particularly interested in

- Science and engineering applications
- Higher mathematics applications
- Software and computer applications
- Business applications

Name _____ Position _____
 Company _____
 Address _____
 _____ Postcode _____
 Tel No: _____ PREL 03



SUPER HY-LIGHT STROBE KIT

Designed for Disco, theatrical uses, etc.

Approx. 16 joules. Adjustable speed. Price £45 + £2 p&p (Total inc. VAT £54.05). Case and reflector price £15 + £2 p&p (total inc. VAT £19.55). Footcandle SAE for further details including Hy-Light and Industrial Strobe Kits.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

- 4ft 40 watt £10.44 (£12.00 inc. VAT)
- 2ft 20 watt £7.44 + £1.25 p&p (£9.99 inc. VAT)
- 1 1/2ft 15 watt £5.00 + 75p p&p (£5.61 inc. VAT)
- 13in. 10 watt £4.00 + 75p p&p (£4.46 inc. VAT)
- 12in. 8 watt £3.50 + 50p p&p (£4.71 inc. VAT)
- 9in. 6 watt £3.00 + 50p p&p (£4.02 inc. VAT)
- 6in. 4 watt £3.00 + 50p p&p (£4.02 inc. VAT)



230V AC Ballast Kit for either 6in, 9in or 12in tubes £5.50 p&p 55p (£6.96 inc. VAT).

For 13in. & 18in. Tubes £6 p&p 75p (£7.76 inc. VAT).

For 12V DC op. 12in. & 13in. tubes only £5.50 p&p 75p (£7.18 inc. VAT).

175 Watt Self-Balasted Black Light Mercury Bulbs. Available for either B.C. or E.S. fitting. price £10.80 + p&p £1.25 (total inc. VAT £13.85).

L.T. TRANSFORMERS
"Special Offer" 0-3V-0-6.3V at 10 Amp (12V 0 10 Amp or 6V at 20 Amp) Price £9.00 p&p £2.00 - inclusive of VAT £12.65 N.M.S.

ROBOT ENTHUSIASTS
The following two Motors are ideally suited for experimenters in this field:
1. ESCAP precision Swiss-made ironless rotor, 6V DC geared M.O.Tor with 70-1 gearbox. 6V DC - 16 r.p.m. 3V - 8 r.p.m. amazing power; no load current; only 10 ma approx. Size: 4 x 2 1/2 cm. Ex-equipment, tested and guaranteed. ONLY £4.50 + 50p p&p (total inc. VAT £5.75).
2. 12/24V D.C. Reversible Precision built motor manufactured by Escap - will operate from 24V down to 2V DC - Current consumption negligible. A range of speeds between 2 to 36 r.p.m. obtainable: 6 Volt DC - 9 r.p.m. N.I.L G.M.A; 12V DC - 18 r.p.m. N.I.L 10 M.A; 24V DC - 36 r.p.m. N.I.L 18 M.A. Total length of motor and gearbox 90 M.M. Max. Dia 42 M.M. Shaft length 15 M.M. Shaft Dia 6 M.M. Approx. half manufacturers price: £15.00 p&p £2.00 - total inclusive of VAT £19.55.

VBL4 CENTRIFUGAL BLOWER
240V AC powerful 1/50 h.p. .23A motor. £18.00 + £2.00 p&p (Total inc. VAT £23.00). N.M.S.
1224V DC Centrifugal Blower £7.50 + £1.00 p&p (Total inc. VAT £9.78) N.M.S.

COOLING or EXTRACTOR FAN
Quiet smooth running. Size 4 3/4 x 4 3/4 x 1 1/2. Supplied for 240V a.c. operation. Price £4.75 + £1 p&p (Total inc. VAT £6.62) N.M.S.



240V A.C. SOLENOID VALVE
Designed for Air/Gas at 0.7. Water 5 psi. Inlet-outlet 3/8. Forged brass body. Manuf. Dewarswitching Assoc. Price £5.50 + £1 p&p (£7.48 inc. VAT) N.M.S.

Ample parking space
Showroom open
Monday-Friday



SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB. Tel: 01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only. Open Saturdays
9 Little Newport Street
London WC2H 9JJ
Tel: 01-437 0576

VARIABLE VOLTAGE TRANSFORMERS

- INPUT 230, 240V a.c. 50/60 OUTPUT 0-260V
- 200W, 1A Max. £15.00
- 0.5KVVA/22A Max. £19.00
- 1KVVA 5A Max. £27.00
- 2KVVA 10A Max. £41.00
- 3KVVA 15A Max. £54.00
- 5KVVA 25A Max. £99.00
- 10KVVA 50A Max. £181.00
- 15KVVA 75A Max. £275.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS

- Dual input 200-240V or 380-415V. Star connected
- 3KVVA 5amp per phase max. £113.40
- 6KVVA 10amp per phase max. £170.10
- 10KVVA 16amp per phase max. £345.45



Comprehensive range of TRANSFORMERS L.T. ISOLATION & AUTO (110-240V). Either cased with American socket and mains lead or open frame type available for immediate delivery. Leaflet on request.

12V D.C. BILGE PUMPS

- 400 G.P.H. 15ft. head, 3amp, £8.00 + £1.00 p&p (£10.35 inc. VAT).
- 700 G.P.H. 10ft. head, 3.5amp, £11.50 + £1.50 p&p (£14.95 inc. VAT).
- 1750 G.P.H. 15ft. head, 9amp, £15.00 + £1.75 p&p (£19.26 inc. VAT).



SINGLE DIAPHRAGM COMPRESSOR NMS

Max. 20 PSI. One CFM approx. 240 volts A.C. £18 + £2 p&p (£23 inc. VAT).

EPROM ERASURE KIT
Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case to include 12, 8 watt 2537 Angstr. Tube. Ballast unit, pair of bi-pin leads, Neon indicator, safety microswitch, on/off switch and circuit.
LESS CASE: Price £13.60 + 75p p&p (Total inc. VAT £16.50).
Warning: Tube used in this circuit is highly dangerous to the eyes. Unit must be fitted in suitable case.

SOLID STATE E.H.T. UNIT

Input 230V A.C. Approx. 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec, to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, e.g. supplying neon or argon tubes etc. £6.50 + 90p p&p (Total inc. VAT £8.50) N.M.S.

FROM STOCK AT PRICES THAT DEFY COMPETITION

AC GEARED MOTORS	C.F. BLOWERS
DC MOTORS	AC CAPACITORS
MICROSWITCHES	STROBE KITS
RELAYS	FLASHTUBES
REED SWITCHES	CONTACTORS
SOLENOIDS A.C. or D.C.	SYNCHRONOUS MOTORS
PROGRAMME TIMERS	

WIDE RANGE OF XENON TUBES
WRITE/PHONE IN YOUR ENQUIRIES

Superior Quality Precision Made NEW POWER RHEOSTATS



New ceramic construction, heavy duty brush assembly, continuously rated
25 WATT 5/10/25/50/100/150/250/300/500/1K
1.5K £3.80 + 30p p&p (£4.71 inc. VAT).
100 WATT 2500 £5.50 + 50p p&p (£6.90 inc. VAT).
100 WATT 75/100/250/500/1000/2500/5000/10K/15K/20K/30K/50K
£9.50 + 75p p&p (£11.78 inc. VAT).
Black Silver Skirted Knob calibrated in Nos 1-9, 1/2in. dia brass bush. Ideal for above Rheostats 30p ea. + VAT.



INSULATED TESTERS NEW!
Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work on stand speed clutch. Size L 8in., W 4in., H 6in. weight 6lb. 500V. 300 megohms. £49 p&p £2 (£58.85 incl. VAT). 1000V 1000MQ £55 + p&p £2 (£65.55 incl. VAT) SAE for leaflet.

SPECIAL OFFER!

AUTO TRANSFORMER tapped 90-260V. 3.5KVVA 1 phase totally enclosed in metal case, mt. Woden. Price: £60.00 + carriage at cost + VAT. N.M.S.

GEARED MOTORS

5 rpm 240V AC Mf. by Carter. £6.05 £1 p&p (£8.11 inc. VAT). N.M.S
20 rpm 115V AC Synchronous. torque approx. 80lb/in. £20.00 + £4 p&p (Total inc. VAT £27.60). N.M.S.
TRANSFORMER 240V operation. £9.15 + £2.00 p&p (Total inc. VAT £12.82). 28 rpm Torque 20lb/in. reversible 1800h p. 110V AC. Price: £9.50 + p&p £1.80 (Total inc. VAT £12.99).
Suitable TRANSFORMER for 230-240V AC operation. Price: £5.20 + p&p £1.40 (Total inc. VAT £7.59). N.M.S.
38.3 rpm GEARED MOTOR. Torque 35lb/in. reversible 115V AC inc. start capacity. Price: £11.55 + p&p (Total inc. VAT £15.58). N.M.S.
Suitable TRANSFORMER 230V AC operation. Price: £4.50 + 50p p&p (Total inc. VAT £5.75).

CROWN 37 rpm 2000lb.in. approx. 110V AC, reversible geared motor. Price: £35 p&p £4.50 (£45.42 inc. VAT). N.M.S.
Suitable TRANSFORMER for above £10 p&p £1.50 (£13.22 inc. VAT).

57 rpm 240V 1/22 h.p. continuously rated REVERSIBLE 50lb.in. manul. by Winstruments New. Ideal for garage doors, curtains etc. ONLY £12.00 + £2.00 p&p (Total inc. VAT £16.00).
71 rpm Torque 10lb/in., reversible 1700h p. 110V AC motor. Price: £9.50 + £1.80 p&p (Total inc. VAT £12.99).
Suitable TRANSFORMER for 230-240V AC operation. Price: £5.20 + p&p £1.40 (Total inc. VAT £7.59). N.M.S.
24V DC 200 rpm 10lb.in. Mf. by either Parvalux or Cater. Ex-equip. tested. £8.00 + £1.50 p&p (Total inc. VAT £10.33).
230/240V AC SYNCHRONOUS. 2 rpm, 6 rpm, 6 rev per day. Any type: £4.80 + 50p p&p (Total inc. VAT £6.10).

CHECK METER
200 240V A.C. 50amp, fully reconditioned. £7.50 + £1.75 p&p (Total inc. VAT £10.64).
SANGAMO WESTON TIME SWITCH
Type S251 200/250 A.C. 2 on/2 off every 24 hours. 20 amps contacts with override switch. Dimeter 4"x3". Price £8.50 + £1.50 p&p (£12.65 inc. VAT & p&p). Also available with solar dia R&T. Other types available from stock.
N.M.S. New Manufacturers' Surplus
R&T Reconditioned and tested
Goods normally despatched within 7 days.

MARCO TRADING

TRANSISTORS		DIODES		LINEAR I.C.'s		RESISTOR KITS		74LS			
AC128	30p	BF338	0.38	IN916	0.04	AA119	0.12	CA3011	1.80	L500	28p
AC176	28p	BFX28	0.28	IN4001	0.05	AA129	0.18	CA3012	1.75	L501	28p
AF239	68p	BFX84	0.24	IN4004	0.06	AA130	0.16	CA3014	2.38	L502	28p
BC107	0.10	BFX85	0.26	IN4005	0.06	BA100	0.24	CA3018	1.10	L503	28p
BC108	0.10	BFX87	0.26	IN4007	0.07	BY126	0.12	CA3020	2.10	L503	32p
BC109	0.10	BFY50	0.21	IN4148	0.05	BY127	0.10	CA3028A	1.30	L508	28p
A.B.C.	0.12	BFY52	0.21	IN4149	0.05	BY133	0.16	CA3035	2.55	L509	28p
BC147	0.09	VFY90	0.90	IN5400	0.12	BY184	0.40	CA3080E	1.80	L510	28p
BC182	0.09	BSX20	0.38	IN5401	0.15	OA47	0.10	CA3085	1.20	L51	28p
BC182L	0.09	BU208	1.55	IN5402	0.15	OA90	0.08	CA3086	0.68	L512	25p
BC184	0.09	BU407	1.65	IN5404	0.16	OA91	0.09	CA3090A	5.00	L513	33p
BC184L	0.09	MJ2955	0.90	IN5406	0.18	OA95	0.18	CA3130E	1.40	L514	58p
BC212	0.09	OC45	0.58	IN5408	0.20	OA200	0.06	CA3140E	0.60	L515	25p
BC212L	0.09	OC71	0.50	IS44	0.06	OA202	0.15	HA1336W	3.15	L520	28p
BCY70	0.15	OC72	0.52	IS921	0.08	IN914	0.04	LM324N	0.55	L521	28p
BD131/2	0.34	TIP31A	0.44					LM339	0.65	L522	28p
BD133	0.56	TIP32A	0.42					LM348	0.90	L530	33p
BD135	0.32	TIP33C	0.88					LM380	1.65	L532	28p
BD136	0.36	TIP34A	0.72					LM381N	1.45	L533	33p
BF115	0.32	TIP2955	0.60					LM382N	1.45	L537	23p
BF184	0.32	TIP3055	0.60					LM386	0.95	L574	38p
BF185	0.32	TIS88	0.40					LM387	1.45	L5122	70p
BF194	0.10	2N3055	0.45					LM389N	1.20	L5151	75p
BF196	0.10	2SC1096	0.68					LM3914N	2.55	L5159	68p
BF197	0.10	2SC1173Y	0.82					LM3915N	2.60	L5151	75p
BF200	0.20	2SC1306	0.92					ML232B	2.10	L5155	50p
BF224	0.20	2SC1307	0.40							L5157	45p
BF244	0.26	2SC1957	0.76							L5158	58p
BF244A	0.28	2SC2028	0.73							L5160	60p
BF244B	0.30	2SC2029	2.10							L5161	70p
BF259	0.32	2SC2078	1.05							L5162	72p
BF262	0.30	2SC2166	1.20							L5163	80p
BF263	0.30	3SK89	0.65							L5166	1.95
BF337	0.38	40673	0.80							L5170	1.75
										L5244	1.00
										L5245	2.00
										L5257	73p
										L5393	1.15
MICRO											
2764250n/s	5.80	Z80ACTC	3.30								
Z80ACPU	3.70	Z80ADMA	9.00								
		Z80APO	3.40								

MARCO TRADING (DEPT PE2)
The Maltings
High Street
Wem, Shropshire SY4 5EN
Tel: 0939 32763 Telex: 35565

ORDERING: All components are brand new and to full specification. Please add 45p postage/packing (unless otherwise specified) to all orders then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges etc most welcome. (Do not forget to send for our 1984 catalogue — only 65p per copy.) All orders despatched by return of mail.
NEW RETAIL 1000 sq ft shop now open Mon-Fri 9.00-5.00. Sat 9-12.00.

1984 CATALOGUE
Our latest 123 page catalogue over 4000 items fully illustrated. Send 65p now for your copy. FREE withholders over £5.00.



all in your **MARCH** issue!

LOW COST BBC SPEECH SYNTHESISER



One of the best BBC projects yet, giving effective speech synthesis for less than fifteen pounds.

NEW BBC FORUM

This is to be a new regular item for BBC Micro enthusiasts. The page may be viewed as an I/O port configured for *bidirectional* operation because we invite *you*, the reader, to contribute *your* hints and discoveries. It promises to be an exciting page with the aim of making an important contribution to understanding the BBC machine.

You have one month to prepare for the interface. So order your copy from your Newsagent now!

HEART BEAT MONITOR

If your interest is in the sports, training or medical field then you'll always need to measure pulse/heart beats. This instrument will monitor heart beats from 40 to 200 beats per minute to an accuracy of within 1 beat per minute and display the result on an l.e.d. display.

OSCILLOSCOPE - SPECIAL OFFER!

PRACTICAL

ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING

MARCH 1985 ISSUE ON SALE FRIDAY, FEBRUARY 1

FREE! READERS' ADVERTISEMENT SERVICE

PE BAZAAR

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid "date corner"**. Ads. will not appear (or be returned) if these rules are broken.

WANTED service manual or circuit for Cossor 1049 MK4 'scope, to borrow or buy please. J. Rudrum, 2 Princes Road, Eastbourne, Sussex BN23 6HG. Tel: Eastbourne (0323) 29440.

WANTED Watford Ultimium system any condition. Phone Burntwood (05436) 6043 evenings—ask for Steve.

WANTED MCP40, Tandy or similar graphics printer and Thandar PFM200A frequency meter or similar. Cheapish please! Dr. Andrew Brown, Department of Oral Surgery, John Radcliffe Hospital, Oxford OX3 9DU. Tel: Oxford (0865) 65164.

Z80A computer system including 10MB Winchester back-up cartridge drive. Can be seen working. £170 or split. Tel: 0223 277272.

DISCS! DD/SS £1.35. DD/DS for SS drives £1.45. Disc boxes: 50 disc £8, 10 disc £1.95. Martin Harlow, 194 Old Woking Road, Woking, Surrey GU22 8HR.

FLUKE 8000A DMM £40, p.s.u. and many unused i.c.'s and components. For more information send SAE. Mr. T. Pomphrey, 347 Church Road, Redfield, Bristol BS5 8AA. Tel: 0272 558980.

PYE 'Westminster' 70cm TX/RX fitted 5 repeater channels +2 Simplex, 15W TX O/P, tone burst. £75. D. C. Chapman, 6 Pickhurst Green, Hayes, Bromley, Kent. Tel: 01-462 2178.

48K ZX Spectrum and full size keyboard now fails to output logo when switched on £40. Ralph Lovelock, 14 Knightley Road, Exeter EX2 4SR. Tel: Exeter 75892.

WANTED, loan or purchase, handbook/service sheets Waltham music centre STM 50 or photostat. Costs paid. Mr. W. Hammond-Haley, 'Holmeleigh', Sleaford Road, Dunston, Lincoln LN4 2EZ. Tel: Metheringham (0526) 20661.

PE Quasar cassette deck, not working, £15 ZX81, 16K Ram, tapes £35, two unused TDM 1010's £5. Mr. J. C. D. Darwent. Tel: Dronfield 413667.

UK101 with Cegmon and 8" disk system. Needs memory expansion. £200 or best offer. Mr. S. Morgan, 17 Willenhall Road, Bilston, West Midlands WV14 6NW. Tel: Bilston 403416.

TEXAS TI-53 17 months old, working, £7. L. Stewart, 32 Cross House, Wolverhampton WY2 3EX.

WANTED PE January, March, April 1984; July 1983, April 1980, February 1978 and all before July 1977. Kenny Robertson, 82 Willow Drive, Airdrie, Lanarkshire, Scotland ML6 8JX.

TELEPRINTERS Creed 7B, 54R and 54N. Also two C37 and J37 tape recorders. Offers invited or why? Mr. John Radley, 81 Drayton Avenue, West Ealing, London W13 0LE. Tel: 01-997 4835.

SYNTHESISER, 4600, mostly working (not completely finished). Large wooden case. Internal amps/speakers. Large patchboard £180. Mr. Gaskell. Tel: Cambridge (0223) 893593.

SAFGAN 12 MHz dual beam oscilloscope, unused, as new condition, with manual and X10 probe set £150. Peter Cunningham, 11 Berwyn Avenue, Penyffordd, Nr. Chester. Tel: Caergwrlle 760172.

FOR sale PE August 1977 to October 1983. ETI February 1978 to March 1982. Offers to: R. M. James, Yew Tree House, Preston Wynne, Hereford HR1 3PE.

WANTED high resolution graphic board for UK101 (Sprite from Premier). J. Ockier, Mgr. Christiaensstraat 16, 8880-Tielt, Belgium.

300 watt switched mode PSU. Set to 60 amps 5 volts. 6" x 5" x 14". Diagrams available. Mr. P. Kirton, 4 The Grove, Shaw Heath, Stockport, Greater Manchester SK2 6QU. Tel: 061 480 4690.

TECHTRONICS 515A 15MHz single beam oscilloscope £50. Advance SG66 audio generator £40. Eddystone 830 Receiver £95. Tel: Peterborough 235042.

TELEQUIPMENT double beam oscilloscope model D43. Full working order. Also instruction manual. £60. Buyer collects. Mr. Naylor, 26 Highfield Road, Streitford, Manchester M32 8NF. Tel: 061 865 4320.

PE November 64 to December 81 less five. Some extras. Plus most 82-83. All mint. Offers. Phil Simpson, 37 Larkholme Parade, Fleetwood FY7 8LL. Tel: 03917 6317.

WANTED PE December 1975 or copy of Minimix item from that issue. Call weekday evenings only. John Colson 01-253 3176.

PRACTICAL Electronics from 1967 to 1983. Instruction manual for Tektronics 545B oscilloscope. Offers. Buyer collects. Mr. L. T. Cowell, 69 Crew Road, Haslington, Crewe, Cheshire. Tel: 0270 581157.

RANGER P.E.C.B. two for sale working order. Offers invited. Will separate if required, 27MHz legal. Mr. G. T. McDermid, 4 Aspian Drive, Coxheath, Maidstone, Kent ME17 4JZ. Tel: 0622 46354 (evenings).

TANDON disc drive D/S D/D 80 track 640K

£99 each. Acron DFS £80. Tel: 01-892 1909.

MONO valve amplifier, 3 watt, and motor, in portable timber cabinet. Two available. £10 each if collected. Tel: Oxford (0865) 779855.

AVAILABLE BD139-140, BC146 Micro TR 7806, 09 and 12 vol. regs all new for less than half price + p&p. Write to: Saied Z. Fathy, No. 25, Alric Avenue, Neasden, London NW10.

FOUR mains PCB relays type 265/4A/G2v. D.P.C.O. £5 or £1.40 each including postage. David White. Tel: 0248 722697 (evenings).

'NIGHTRIDER' car lights sequencers, drives nine channels vari-speed. Easy wiring all negative-ground cars £40 complete. Mr. S. M. Budzinski, 16 Laburnum House, Malpas Road, London SE4 1BL.

OSCILLOSCOPE Heath 10-4555 £150 ono also other instruments P.C. bridge etc. Offers, good condition, sold separately. Mr. A. Ewing, 9 Croft Crescent, Markinch, Glenrothes, Fife KY7 6EH, Scotland.

WANTED AY-3-1270 linear i.c. or RS-3-1270. Mr. J. F. Wilso, 233 Broomlee Close, Newton Aycliffe, Co. Durham. Tel: Aycliffe 312130.

WANTED two track record head for B & O record 1800 RTOR deck. Mr. C. Bressington, 17 Station Road, Ystrad Mynach, Mid-Glamorgan. Tel: 0443 813005.

EIGHT Philips LVC 150 2½hr. video tapes. Hardly used. Offers plus postage. Mr. L. T. Hill, 14 Rothesay Terrace, Bedlington, Northumberland. Tel: Bedlington 825967.

WANTED data or specimens of early transistor types. Good prices paid. Write for full details: Mr. Andrew Wylie, 18 Rue de Lausanne, 1201 Geneva, Switzerland.

MICROSYNTH Synthesiser built and tested with speakers and homemade stand £150. 8 Stourton Road, Witham, Essex. Tel: Witham 514556.

COMPONENTS transistors mainly OC/AC/BC, capacitors, resistors, chips, pots, relays, motors and other. 16 lb. £20. Mr. Turner, 4 Mill Fields, Newtown, Powys. Tel: 0686 27862.

WANTED service circuit diagrams Sugden C51 A51 purchase hire to copy. Good price paid. Richards, Maesyffnon, Caehopkin Road, Abercrave, Swansea. Tel: 0639 730629.

10 x 8255A £70 the lot or £8 each. Also printer leads for Dragon 32, BBC £9.95 each. R. Vowles, 3 Orchard Way, Uxbridge, Middx. UB8 2BN. Tel: 0895 54720.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature.....Date.....

Please read the **RULES** then write your advertisement here—one word to each box. Add your name, address and/or phone no.

COUPON VALID FOR POSTING BEFORE 1 FEBRUARY 1985 (One month later for overseas readers.)

SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.

BLOCK CAPITALS PLEASE

Name & Address:				

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid "date corner"**

PE BAZAAR
FEBRUARY 85

ROBOTS

neptune and mentor



THE ELECTRO-MECHANICS and the electronics of both robots have now been explained in previous parts, and the p.c.b.s and parts lists have been published. The actual construction and computer control of the robots is the last thing to be considered, beginning this month with NEPTUNE.

PART SIX

CONSTRUCTION

Construction starts with axis 0 and progresses upwards from there. The hydraulic cylinders of the NEPTUNE are supplied pre-assembled. First axis 0 cylinder is fitted to its sensor potentiometer, on a bracket beneath it, and then to the base plate and front plate (Fig. 6.1). There are support brackets to ensure a rigid structure and there are triangular brackets with feet on them to prevent the robot from tipping over when under load. The top slot in the rear plate is for fitting the computer interface leads to the edge connectors on the interface board. The slot beneath it is for the cables leading to the power supply which fit onto the rear plate later.

Next the top plate is fitted. Being 3mm steel this is quite heavy but this is necessary to ensure rigidity. On top of axis 0 cylinder goes the shoulder rotating axle with axis 1 mounting plate on top of it (Fig. 6.2). The weight of the arm is carried by a large thrust ball race fitted round the axle. Through the axle passes the plumbing/wiring harness which is secured to axis 1 cylinder fitted to the mounting plate.

Onto mounting rings on axis 1 cylinder the lower arms are fitted and to the upper end of these are fitted axis 2 cylinder with the upper arms attached to it (Fig. 6.3). To the end of the upper arms is fitted axis 3 cylinder which provides the wrist raising function.

A pair of mounting plates is used to secure axis 4 cylinder to the front end of axis 3 cylinder (Fig. 6.4). This applies to NEPTUNE II only, where it provides wrist yaw, a function immensely useful when picking up objects lying flat or in other difficult positions. It also greatly assists spraying into corners. Yaw is a feature usually found on only the most expensive of robots used in industry. Axis 5, the wrist rotation cylinder fits to the axle of axis 4 cylinder by means of a short plate. On NEPTUNE I where there is no wrist yaw, axis 5 fits to the top of axis 3 cylinder. The gripper clamps onto the axle of axis 5 cylinder with a single set screw enabling it to be rapidly changed. The NEPTUNES are supplied with a choice of gripper types. The robot is now ready for plumbing and wiring.


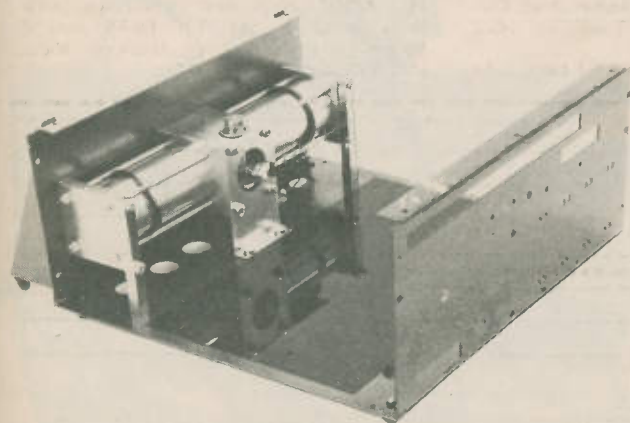


Fig. 6.1. (above): base plate and axis 0 cylinder

Fig. 6.2. (opposite): shoulder-rotating axle with axis 1 cylinder fitted to the mounting plate

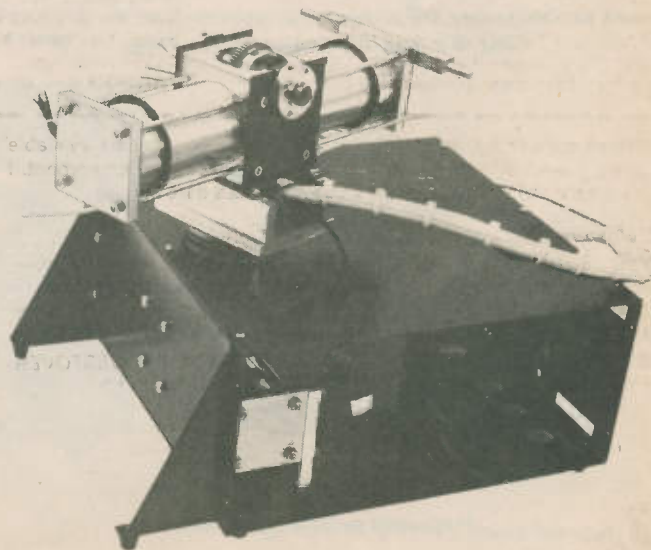

The harness is strapped onto the arms at the fixing holes with cable ties. The position for these is marked, with dabs of paint, on the harness. The pipes press into 'banjo' fittings attached to the cylinder ends with Delrin hollow bolts and the cables are trimmed and soldered to the sensor potentiometers (Fig. 6.5).

The solenoid operated valves, which control the water flow, fit with hollow bolts to a Delrin manifold (Fig. 6.6) which acts like a printed circuit board routing the water to the correct valve. The other end of the valves fit to bored Delrin bars to which the restrictors and flow rate control valves also fit (Fig. 6.7). Brackets to which the solenoid driver boards will fit are screwed to the solenoids and ensure correct alignment for the boards which clip onto the connector tags of the solenoids (Fig. 6.8). This arrangement avoids soldering to the solenoids and greatly simplifies maintenance in that the boards can be rapidly unplugged from the system. Connections to the plumbing harness

again are made with "banjo" push-on fittings and hollow bolts.

After wiring up the power supply (Fig. 6.9) and connecting to the computer interface board (no need to connect to a computer yet) the system is ready for commissioning. The sump of the hydraulic power pack is filled with water and the pump is operated with its outlet and inlet connected together with one of the plug-in pipes. This expels the air from the pipe which, after switching off the pump, is plugged into the manifold as the pressure source; the return pipe is taken from the outlet of the manifold to the sump. After pressurising the system and checking that there are no leaks the axes are tested one at a time by plugging in a solenoid driver board and the axis operated by means of a potentiometer on CN401 extend-contract connector. This will drive out most of the air. The rest of it will gradually disappear by dissolving in the water when under pressure. It then comes out of solution when returned to the sump.

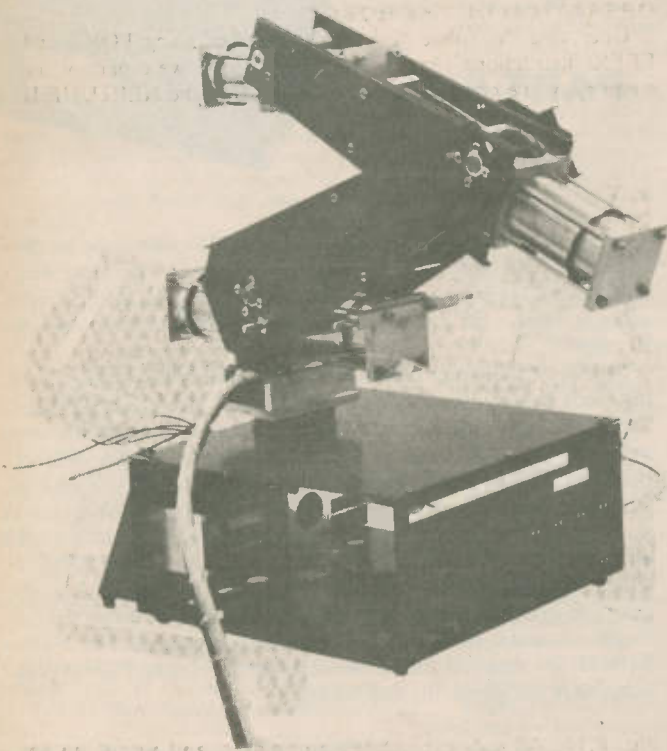


Fig. 6.3. Lower and upper arms fitted


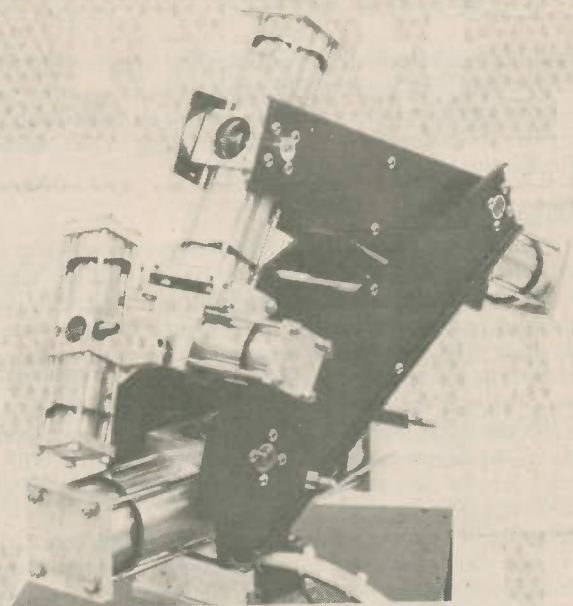


Fig. 6.4. Shoulder, upper arm and wrist assembly

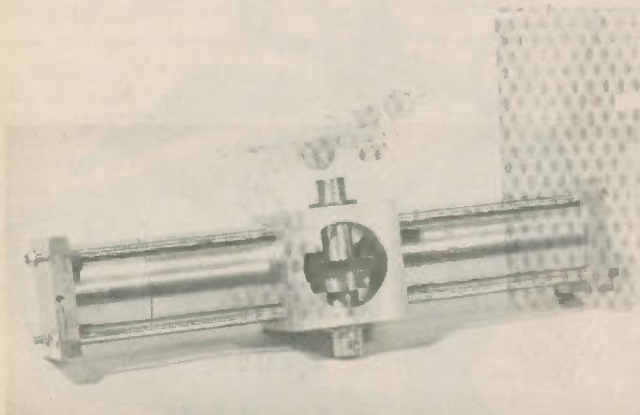

Hydraulic cylinder assembly

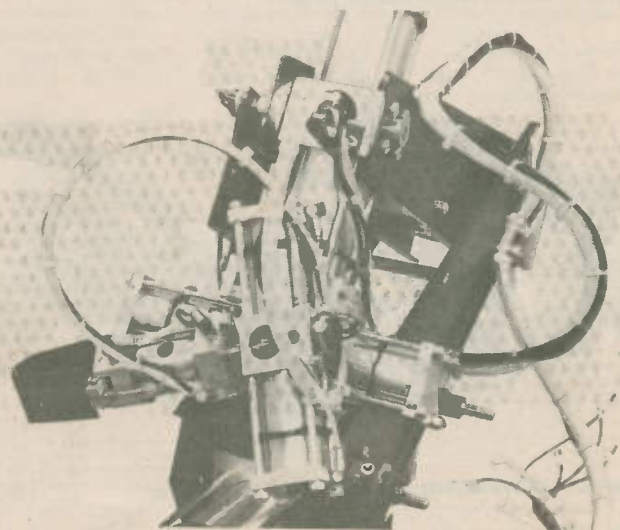


Fig. 6.5. Plumbing and wiring loom



Fig. 6.6. Hydraulic control manifold

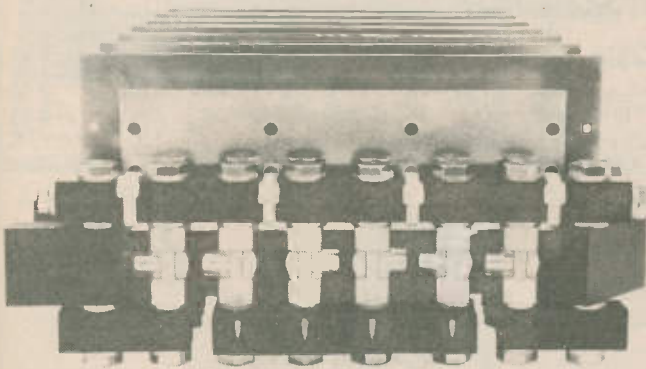


Fig. 6.7. Assembly showing restrictors and flow-rate control valves

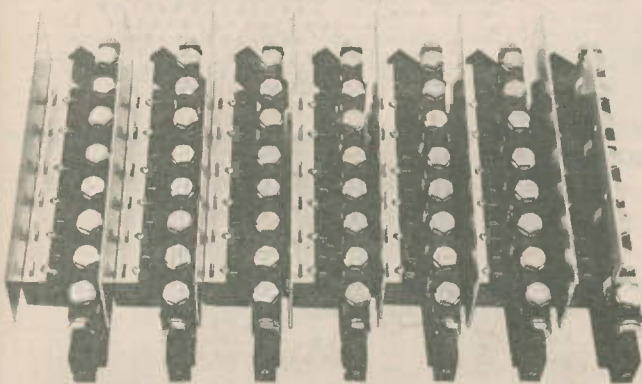


Fig. 6.8. Completed hydraulic flow-control sub-system for all seven axes

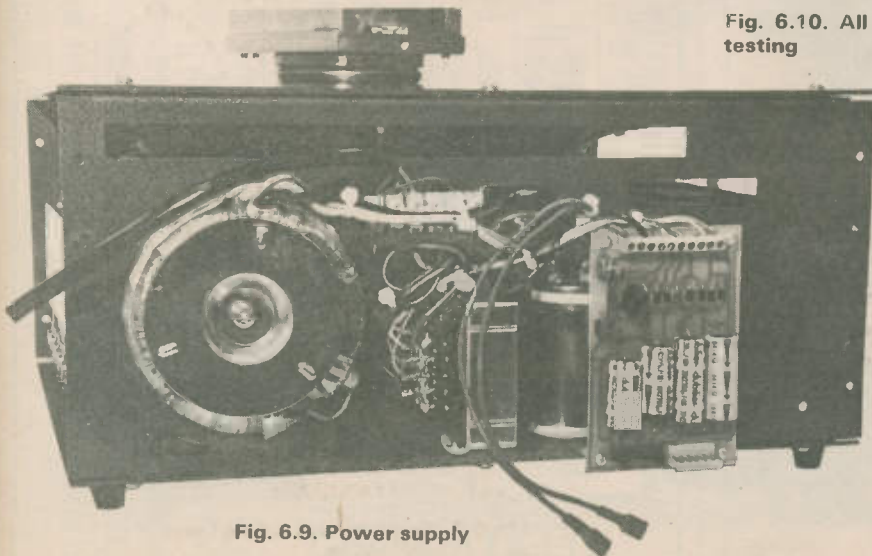


Fig. 6.9. Power supply

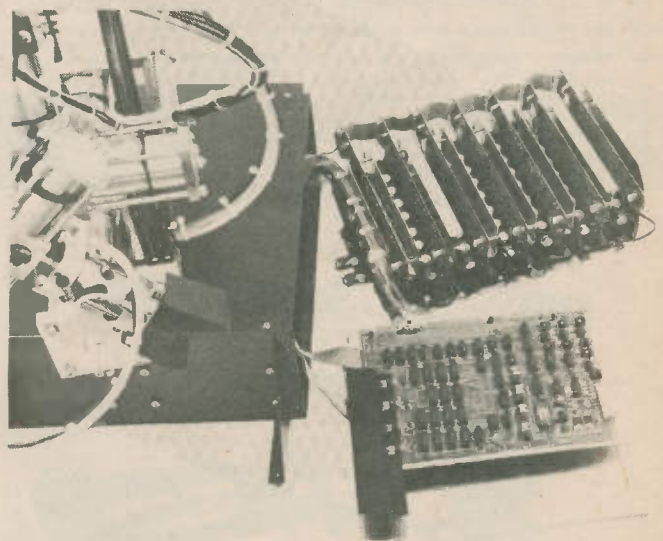


Fig. 6.10. All sub-assemblies completed and wired up for testing



Fig. 6.11. NEPTUNE simulator arm

All the solenoid driver boards may now be fitted (Fig. 6.10), the computer interface board connected to the computer and the "NEPDYN" program run. This sends and returns the chosen axis between 2 points and generates, on the monitor screen, a graph of error in the axis position against time. The error is the difference between where the axis is, as measured by the ADC, and where the axis has been told to go. With the aid of this program the restrictors are set to achieve rapid convergence of the send and return graphs without any overshooting.

After setting the restrictors of each axis, the pre-sets on the solenoid driver boards are set so that sending position 0 from the computer, by means of the "NEPTROL" program, sends each axis to just before the end of its travel. The pre-sets on the interface board are set to match the positions of the simulator (Fig. 6.11) with the positions of the robot.

The interface board is next mounted over the manifold assembly (Fig. 6.12) which is then slid into the robot base and bolted down. Following fitting of side plates and covers the robot is then ready for use.

OPERATION OF THE ROBOT

Operating the robot basically consists of using POKE and PEEK instructions sent to the robot as if it were part of the memory of the computer. To move axis 0 of the NEPTUNE II

to position DO, the start of the 'memory' is first defined. This is also the address for the most significant byte of axis 0. The least significant byte is at the next address. On the BBC, POKE and PEEK are represented by '?' and hexadecimal numbers are indicated by ''.

```
10 A=&#x0000
20 ?A=DO DIV 16
30 ?(A+1)=(DO MOD 16)*16
```

The data DO can be any integer from 0 to 4095 ($2^{12}-1$) because it is a 12-bit control system. On the NEPTUNE I it is an 8-bit system so the range is 0 to 255 (2^8-1) so only one byte is sent for each axis move. For the msb the data is divided by 16 and the remainder ignored. For the lsb this remainder is multiplied by 16 because it is the top 4 bits of the lsb that are used.

The addresses of the axes follow successively so to move axis 4 to position D4 the instructions are as below.

```
40 ?(A+8)=D4 DIV 16
50 ?(A+9)=(D4 MOD 16)*16
```


Similarly for axis 5

```
60 ?(A+10)=D5 DIV 16
70 ?(A+11)=(D5 MOD 16)*16
```

The servo system of the robot then makes the axis go to this position with no further computer intervention but with the ADC the position of the axis can be followed as it is moving. To operate the ADC it is written to at A+14. Data bit 7 is toggled and the multiplexer axis address set up. The axis address is in the bottom 4 data lines (see Table 1 October 1984). Axis 0 is at address 0000. The msb is read at A+17 and the lsb at A+16.

```
80 ?(A+14)=128
90 ?(A+14)=0
100 ?(A+14)=128
110 DAO=?(A+17)*16+?(A+16)/16
```

Fig. 6.12. Control and servo electronics ready for installation in robot base

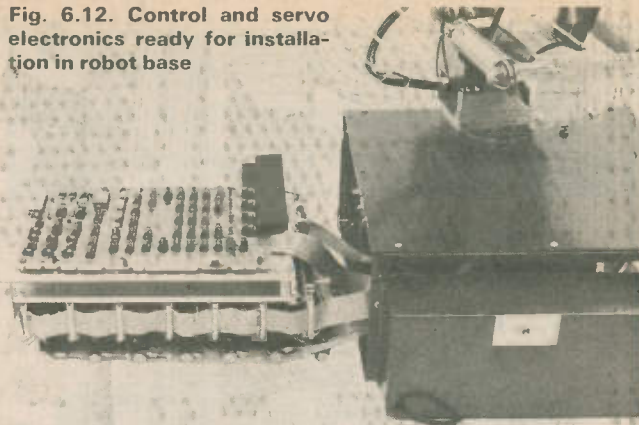

Similarly for axis 4

```
120 ?(A+14)=132
130 ?(A+14)=4
140 ?(A+14)=132
150 DA4=?(A+17)*16+?(A+16)/16
```


Reading the simulator is performed similarly but at the multiplexer axis address 8 bits higher so to read simulator axis 0:

```
160 ?(A+14)=136
170 ?(A+14)=8
180 ?(A+14)=136
190 DSO=?(A+17)*16+?(A+16)/16
```

If the simulator is constantly read and the data returned to the robot then the robot will follow the movement of the simulator.

NEXT MONTH: details of the assembly and use of MENTOR.

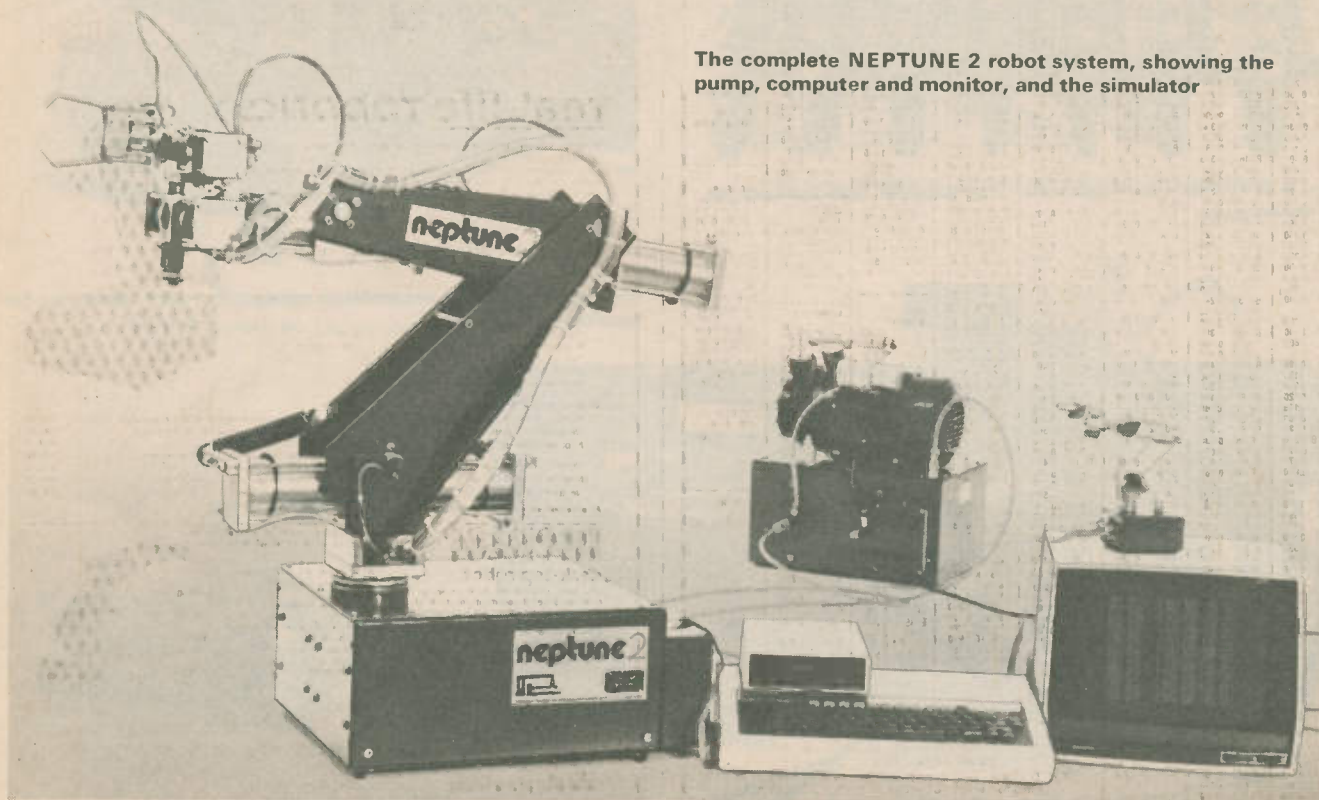The complete NEPTUNE 2 robot system, showing the pump, computer and monitor, and the simulator



Don't put it off any longer!

Protect your family and property with your know how and our security modules. Complete systems start from as little as

£39.95

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

Control Unit
Enclosure
Key Switch & 2 keys
L.E.D.'s
5 1/2" Horn Speaker
4 quality surface Magnetic Switches

CA 1250
HW 1250
KS 3901
LED 1
HS 588
MS 1025

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straight forward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today.
Order code CS 1370

CA 1250 - 2 zone alarm control unit with built in alarm & power supply **£19.95 + V.A.T.**
HW 1250 Enclosure & Hardware Kit for above **£9.50 + V.A.T.**

LED 1 - Set of 4 Led.'s in chrome bezels + Push Switch to fit HW 1250 **£2.15 + V.A.T.**
KS 3901 - 3 position Key Switch **£3.43 + V.A.T.**
HS 588 - 5 1/2" Horn Speaker, output of 11-dbs with CA 1250 or SL 157 **£6.25 + V.A.T.**
US 5063 - advanced Digital Ultrasonic Detector, high sensitivity, with false-alarm suppression **£13.95 + V.A.T.**

SC 5063 - Enclosure for US 5063 **£2.95 + V.A.T.**
IR 1470 - Infra-red system to provide 50' invisible beam, includes both transmitter and receiver **£2.61 + V.A.T.**

SL 157 - Siren Module 12V **£2.95 + V.A.T.**

Wide range of modules and accessories, etc. Send S.A.E. for details.

SELF-CONTAINED ULTRASONIC UNIT CK 5063



Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25 ft.
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1885 Key Switch 3901, 3" Speaker 3515

only **£37.00 + V.A.T.**

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 900db/s of sound, or even 130db/s with an additional speaker. All parts included and supplied with full instructions for ease of assembly.
Size 200 x 180 x 70mm. Order as CK 5063

Add 15% VAT to all prices
Add 70p post and packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday

Saturday 9.00 to 1.00 p.m.
SAE with all enquiries
Order by telephone or post
your credit card

RISCOMP LIMITED

Dept PE26,
21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT,
Princes Risborough (084 44) 6326

AA17 0.90	BCY70 0.160	BU111 1.400	TA650 0.750	2N 3771B 850	JAPANESE TRANSISTORS	PCG85 0.420	LED
AA19 0.890	BCY71 0.160	BU126 0.700	TA650 0.750	2N 3772B 900	2SA73 0.300	PCF60 0.380	LED 3mm
AA23 0.990	BCY72 0.160	BU204 0.750	TA650 0.750	2N 3773 1000	2SA74 0.300	PCF200 1.350	RED 0.850
AC126 0.230	BD105 0.260	BU208 0.700	TA650 0.750	2N 4031B 250	2SA104 0.320	PCF501 1.100	LED 3mm
AC127 0.150	BD124 1.400	BU208A 0.800	TA650 0.750	2N 4032 250	2SA106 0.220	PCF606 1.150	YELLOW 0.100
AC128 0.160	BD125 0.260	BU209 0.700	TA650 0.750	2N 4442 750	2SA473 0.370	PCG100 1.000	LED 3mm
AC128 0.230	BD131 0.250	BU326 0.850	TA650 0.750	2N 4442 750	2SB77 0.320	PC181 0.540	LED 5mm
AC176 0.180	BD136 0.250	BU405 0.850	TA650 0.750	2N 5061 200	2SB854 0.250	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	RED 0.350
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	YELLOW 0.100
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	RED 0.350
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	YELLOW 0.100
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	RED 0.350
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	YELLOW 0.100
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	RED 0.350
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	YELLOW 0.100
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	RED 0.350
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.500	LED 5mm
AC176 0.230	BD137 0.200	BU500 1.100	TA650 0.750	2N 5061 200	2SB937 1.200	PLS19 4.50	

TOOLTRONICS

MINIATURE TOOLS

PRECISION JEWELLERS' TOOLS

Rustproof Tempered Handles and Blades. Chrome Plated Handles. Swivel Heads for use on Precision work.

5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm **£1.75**

5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm **£1.75**

5T41 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Philips) screwdrivers - H0 and H1 Hex key wrenches. Sizes - 1.5, 2 and 2.5mm. **£1.75**

5T51 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm **£1.75**

SIGNAL INJECTOR

Simple push button operation. Oscillates at 700-1kHz with harmonics to 30MHz. 4.4V p/p output. Impedance 100. Ideal for trouble shooting with audio equipment. One "AA" penlight battery supplied. O/No VP96 **£2.50**

LOGIC PROBE

Automatic levelling. White LED indication. Minimum width of measuring pulse 30 milliseconds. Maximum input frequency 10MHz. Input impedance: 100kΩ. Power consumption: 40mA maximum. Power supply: 4.5-18V d.c. ORDER NO. VP97 **£10.50**

CURRENT/POL CHECKER

Heavy duty test prods with built-in indicators for testing polarity, indicates whether a.c. or d.c. 3.5V to 400V. O/No VP98 **£3.00**

TESTER

Universal tester with ceramic buzzer. Tests diodes, transistors, resistors, capacitors and continuity. One "AA" penlight battery included. Test current: Max 2µA, 1.2V. Test voltage: 1000V. Response range: 100MΩ. Max voltage: 500V. Internal resistance: 390kΩ. Length: 135mm. O/No. VP99 **£5.00**

CIRCUIT TESTER

D.C. continuity tester for circuit checking on allow voltage equipment and components. Diode checking also possible. Takes two AA batteries. 90cm lead has crocodile clip. Body length 145mm. O/No. VP100 **75p**


MINIATURE VICE

Miniature plastic and metal vice with strong suction base for portability. Single action to secure or release suction. Plastic jaws with rubber pads 20mm wide, open out to 40mm. Dims: 85 x 65 x 60mm approx. **FANTASTIC VALUE** O/No. VP95 ONLY **£1.60**

METRIC & BRITISH MEASURES

Steel tapes in sturdy ABS plastic case. Silk wrist strap. These yellow coated convex tapes have inch and metric graduations. Automatic push-button return. 2m long x 13mm wide. O/No. VP89 **£1.75**

13 PIECE TOOL KIT AND CASE

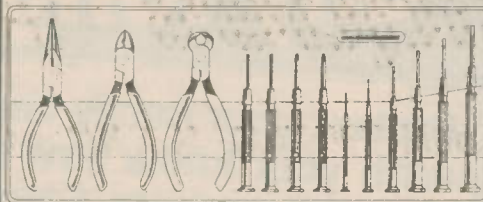

ONLY **£7.50** ORDER No. VP102

13-piece tool set housed in attractive moulded plastic case with clear sliding cover. 1 off 5" snipe nose "radio" pliers with side cutters. 1 off 4 1/2" side cutters. 1 off 4 1/2" end cutters. 2 off hex "Allen" key drivers 3.2mm and 2.5mm. 2 off cross-point "Philips" drivers No 0 and No 1 (with tommy bar). 6 off precision screwdrivers. Sizes from 1mm to 3.5mm.

LOW COST CUTTERS/PLIERS - SPECIAL DRIVERS

Miniature round nose cutters - insulated handles 4 1/2 inch length. Order No. Y043.
Miniature long nose pliers - insulated handles 5 1/2 inch length. Order No. Y044.
Miniature bend nose pliers - insulated handles 4 1/2 inch length. Order No. Y045.
Miniature end nipper - insulated handles 4 1/2 inch length. Order No. Y046.
Miniature snipe nose pliers with side cutter and serrated jaws - insulated handles 5 inch length. Order No. Y042.

FLEXI DRIVER

A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 3/4 inch. Order No. FS-J Flat blade 4mm FS-2 Cross point No. 1 **£1.75** each.

GRIP DRIVER

8 inch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No. SD-1 Flat blade 4mm SD-2 Cross point No. 1 **£1.20** each.

ALL AT **£1.55** each

ANTEX SOLDERING IRONS

MODEL	WATT	O/NO	PRICE
SX	25	1931	£5.40
CX230	17	1972	£5.30
CX250	15	1948	£5.20

ANTEX ST4 IRON STAND
Chromium plated steel spring - in plastic base insulated, with wiper pad. O/No 1939 **£1.75**

PORTABLE SOLDERING IRON
12v.t. 25 watt. Works from car battery. 2 core cable with heavy duty croc clips. D/No 1971 **£5.60**
Ideal outdoor motorist, boat, caravan owner. SK1 SOLDERING KIT - for miniature work. Kit consists of: 1-15w iron (C240) 3 bits: 3/32", 5/32", 3/16". Solder & heat shunt + Booklet "How to Solder". O/No 1938 **£8.00**

BA BOX SPANNER SET

Chrome one of each size: 0.8A, 2BA, 4BA, 6BA, 8BA. Fixed Chrome Vanadium Steel Shaft in Plastic Handle. O/No 2057 **£4.00**

DESOLDERING PUMP

High suction pump with anti-corrosive casing & Teflon nozzle. Spare nozzle. O/No 1937 **50p**

CRIMPING SET A crimping tool set consisting of a crimping tool suitable for insulated terminals. Supplied with 34 assorted terminals in a plastic tray with hinged, transparent lid. O/No 1966 **£3.75**

PICK-UP TOOL

Spring-loaded "Pearl grip" pick-up tool for small components. Four fingers extend to 14mm dia. when plunger is pressed and close up when retracted. Chrome metal. Pocket clip. O/No VP139 **£1.75**

IC EXTRACTION TOOL

IC Extraction is made relatively easy with this tool. The IC is held by specially designed teeth. O/No 2015 **50p**

MAINS NEON TESTER/DRIVER

Has strong transparent handle with insulated screwdriver blade & pen type pocket clip - rated at 500v max. Length 140mm (5 1/2"). O/No 2016 **55p**

SUB-BOX

A neat swivelling disc provides close tolerance substitution resistors of 36 preferred values from 5 ohms to 1kOhm. Simply fix clips into circuit and swivel until optimum result is achieved. O/No VP112 **£4.75**

BATTERY TESTER

Tests all types of battery including standard, NICAD, Alkaline, etc. Takes all standard sizes including 6V lantern, batteries and watch/hearing aid cells. Also tests fuses and lamps by means of internal 9V (PP3) battery. Can also be used to recharge NICAD batteries by means of external 3-12V d.c. power supply (not included). Dims: 185 x 103 x 30mm (approx.). Full instructions provided. O/No. VP101 **£7.00**

POWER SUPPLY

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug input - 240V AC 50Hz, Output - 3, 4, 5, 6, 7.5, 9 & 12V DC Rating - 300mA MW88. O/No. 137 **ONLY £3.75**

BRAND NEW LCD DISPLAY MULTITESTER

RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
3 1/2 digit. 16 ranges plus HFE test facility for PNP and NPN transistors. Auto zero, auto polarity. Single-handed, push-button operation. Over range indication. 12.5mm (1/2 inch) large LCD readout. Diode check. Fast circuit protection. Test leads, battery and instructions included.
Max. indication - 1999 or 1999
Polarity indication Negative only
Positive readings appear without a sign
Input Impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range 5 C to 50 C
Power Supply 1 - PP3 or equivalent 9V battery
Consumption 20mW
Size 155 x 88 x 31mm

RANGES
DC Voltage 0-200mV
0-20-200-1000V Acc. 0.8%
AC Voltage 0-200-1000V
Acc. 1.2% DC Current 0-200µA
0-2-20-200mA 0-10A Acc. 1.2%
Resistance 0-2-20-200k ohms
0-2 Megohms Acc. 1%
BI-PAK VERY LOWEST PRICE **£45.00** each
Leather case for 188m **£2.50** EACH

MULTITESTER

1000 ohm including test leads & Battery
AC volts - 0-15-150-500-1,000
DC volts - 0-15-150-500-1,000
DC currents - 0-1ma-150ma
Resistance - 0.25 K ohms
100 K ohms
Dims - 90 x 61 x 30mm

O/No. 1322 OUR PRICE **£6.80** ONLY

HT320 MULTITESTER

Facilities for testing transistors. Mirror Scale, leads and bats
SPEC
DC Volt: 20,000 O.P.V
AC Volt: 8,000 O.P.V
DC Volt: 0-0.1-0.5-25-10-50-250-1000V
AC Volt: 0-10-50-250-1000V
DC Current: 0.50µA-2.5mA-25mA-0.25A
Resistance: 2K-20K-2M-20M Ohms
AF Output: 10dB to +22dB for 10V AC
As a Trans Tester tests Leakage, Current (Icc), DC Current, Amplification, Factor (Hfe)
Dims: 146 x 95 x 55mm
Order No. 1323 **£15.40**

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM
12V charger, 3 collets & 3 x Twist Bits
1 Sheet PCB Transfers 210mm x 150mm
1 Etch Resist Pen
1 1/2 pack FERRIC CHLORIDE crystals
3 sheets fibreglass board
2 sheets Coppelad copper clad board
Full instructions for making your own PCB boards
Retail Value over **£15.00**
ORDER NO. VP81
OUR BI-PAK SPECIAL KIT PRICE **£9.95**

RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size 2 cross point size 4 & 6. 1 Ratchet handle 5-in-1 Kit. O/No. 329B **£1.45** each.

BI-PAK

Send your orders to Dept PW9 BI-PAK PO BOX 6 WARE, HERTS
SHOP AT 3 BALDOCK ST. WARE, HERTS
TERMS CASH WITH ORDER. SAME DAY DESPATCH. ACCESS.
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7005
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 19% to your Total order. Postage add 75p per Total order.

Sequential Logic Techniques Part 5

M. TOOLEY BA and D. WHITFIELD MA MSc CEng MIEE

LAST month we carried out a detailed investigation of the operation of a universal shift register. This month we shall turn our attention to another device which finds a wide range of applications in the digital world, the data multiplexer.

Data multiplexers, or data selectors as they are sometimes known, generally have one output and several inputs. Any one of the inputs can, by placing appropriate logic levels on its control inputs, be routed to its output. Data multiplexers thus provide us with a means of sending several different digital signals along a common signal line.

In essence the data multiplexer acts as a multi-way switch however, by virtue of its internal logic and unlike its conventional analogue counterpart, the device will only operate with digital signals.

The switch equivalent of the simplest form of data multiplexer is shown in Fig. 5.1. This two-way arrangement

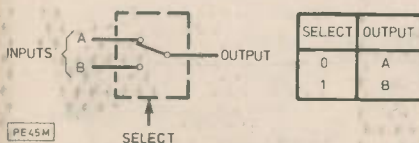


Fig. 5.1. Simplified switch equivalent of a two-way data multiplexer

is equivalent to a single-pole double throw (SPDT) logic switch. The two switch states are controlled by means of a third select input. When a logic 0 appears on the SELECT input the switch moves to position A whereas, when a logic 1 appears on the SELECT input the switch moves to position B.

The internal logic of the two-way data multiplexer is shown in Fig. 5.2.

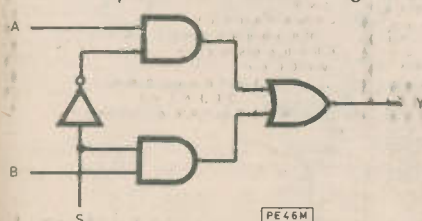


Fig. 5.2. Logic arrangement of a two-way data multiplexer

This simply consists of two two-input AND gates, a two-input OR gate and an inverter. The truth table for this arrangement is given in Table 5.1. As

A	B	S	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Table 5.1. Truth table for simple two-way data multiplexer

can be seen, whenever the SELECT input is at logic 0 the output, Y, takes the state of the A input whereas, when the SELECT input is at logic 1, the output takes the state of the B input.

By grouping together the states for which the output remains unaffected by one or other of the inputs (we shall, for obvious reasons, call these the "don't care" states!), the truth table of the two-way multiplexer can be reduced to that shown in Table 5.2.

A	B	S	Y
0	x	0	0
1	x	0	1
x	0	1	0
x	1	1	1

x = don't care

Table 5.2. Simplified version of table 5.1

DATA INPUTS				SELECT INPUTS		OUTPUT
A	B	C	D	S0	S1	Y
0	x	x	x	0	0	0
1	x	x	x	0	0	1
x	0	x	x	0	1	0
x	1	x	x	0	1	1
x	x	0	x	1	0	0
x	x	1	x	1	0	1
x	x	x	0	1	1	0
x	x	x	1	1	1	1

x = don't care

Table 5.3. Truth table for a four-way data multiplexer

This truth table shows rather more clearly than its predecessor how the SELECT input operates; the X's in the truth table being used to denote the "don't care" states.

The switch equivalent of a four-way data multiplexer is shown in Fig. 5.3.

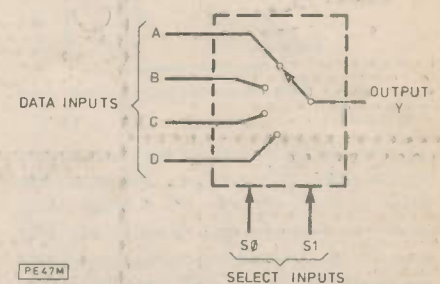


Fig. 5.3. Simplified switch equivalent of a four-way data multiplexer

Here the output, Y, can be connected to any one of the four data input lines, A to D, by means of an appropriate input on the two select lines, S0 and S1. The truth table for the four-way data multiplexer is shown in Table 5.3. The corresponding Boolean expressions are:-

Output	Select Inputs
Y = A	$\overline{S_0} \cdot \overline{S_1}$
Y = B	$\overline{S_0} \cdot S_1$
Y = C	$S_0 \cdot \overline{S_1}$
Y = D	$S_0 \cdot S_1$

We shall now investigate the operation of a practical four-way data multiplexer, the 74LS153.

THE 74LS153

The 74LS153 contains two four-way data multiplexers which have common select inputs. The pin connections of the two 74LS153 are shown in Fig. 5.4. The two halves of the device

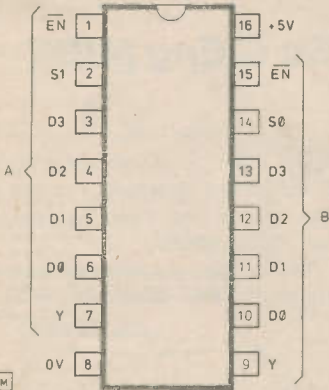


Fig. 5.4. Pin connections for the 74LS153

(referred to as A and B) are conveniently brought out to pins on opposite sides of the package; the A-side using pins 1 to 7 whilst the B-side uses pins 9 to 15. Supply connections, using the conventional pins 8 (0V) and 16 (+5V), are common to both halves of the device.

Each half of the 74LS153 has its own active low enable, \overline{EN} , input. When these inputs are taken to logic 1 the corresponding outputs immediately go to logic 0 irrespective of the state of

any of the data (D0 to D3) or select (S0 and S1) inputs.

The internal logic of the 74LS153 is shown in Fig. 5.5. This clearly shows how the \overline{EN} inputs are gated with the select, inverted select, and data inputs at each of the four four-input AND gates on both sides of the device. The outputs of each set of AND gates are then combined in a four-input OR gate. The 74LS153 is effectively nothing more complex than a two-pole four-way switch!

The complete truth table for the 74LS153 is shown in Table 5.4. This truth table is, of course, identical for each half of the device. When both select inputs (S0 and S1) are at logic 0, the output (Y) reflects the state of the D0 input. With S0 at logic 1 and S1 at logic 0, the output takes the state of the D1 input, and so on.

The circuit used for our practical investigation of the 74LS153 data multiplexer is shown in Fig. 5.6. It should

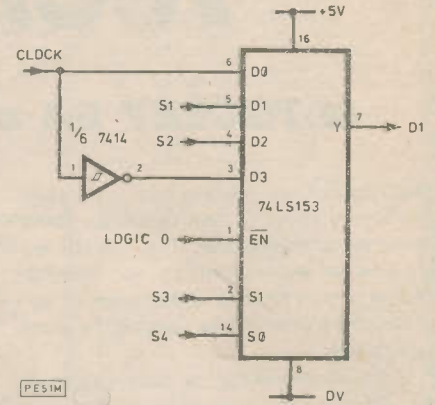


Fig. 5.6. Practical arrangement used to demonstrate the action of the 74LS153

SELECT INPUTS		DATA INPUTS				ENABLE	OUTPUT
S0	S1	D0	D1	D2	D3	\overline{EN}	Y
x	x	x	x	x	x	1	0
0	0	0	x	x	x	0	0
0	0	1	x	x	x	0	1
1	0	x	0	x	x	0	0
1	0	x	1	x	x	0	1
0	1	x	x	0	x	0	0
0	1	x	x	1	x	0	1
1	1	x	x	x	0	0	0
1	1	x	x	x	1	0	1

x = don't care

Table 5.4. Truth table for the 74LS153 data multiplexer

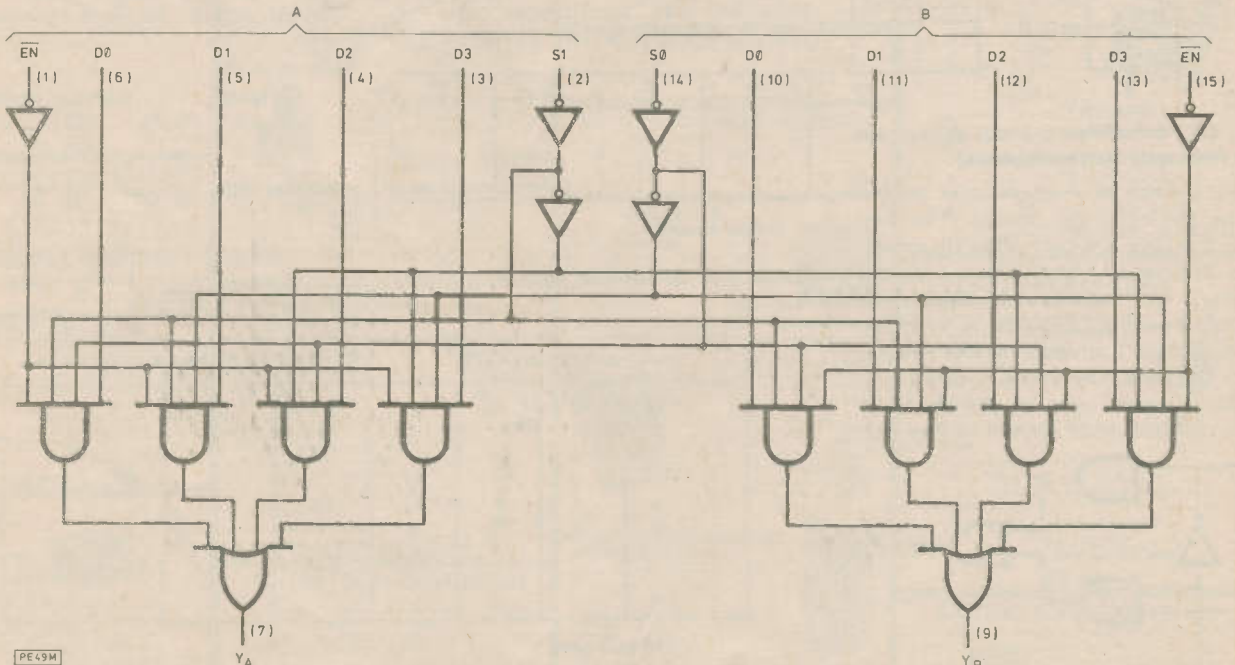


Fig. 5.5. Internal logic of the 74LS153

be noted that only one half of the device is used. In order to provide four different data inputs which may be readily distinguished from one another, D0 is fed from the clock whilst D1 and D2 are fed from the Logic Tutor's momentary push buttons, S1 and S2 respectively. The remaining data input, D3, is fed from an inverted clock signal derived from a 7414 inverter. The relevant half of the device is enabled by hard wiring the \overline{EN} input to logic 0 whilst the two latching Logic Tutor switches, S3 and S4, are used to determine the state of the select inputs, S1 and S0 respectively.

The 7414 should be inserted into socket D whilst the 74LS153 should be inserted into socket E with the usual orientation convention (pin-1 of each device to the respective connection marked on the Logic Tutor PCB) being observed. The following links are required:-

- D1 to clock
- D2 to E3 (data input D3)
- D7 to 0V (common)
- D16 to +5V (supply)
- E1 to logic 0 (active low enable)
- E2 to S3 (select input S1)
- E4 to S2 (data input D2)
- E5 to S1 (data input D1)
- E6 to clock (data input D0)
- E7 to D1 (D1 indicates the output)
- E8 to 0V (common)
- E14 to S4 (select input S0)
- E16 to +5V (supply)

(A total of 13 links)

The select inputs should initially both be set to logic 0 by appropriate adjustment of S3 and S4. The output indicator, i.e.d. D1, should then be seen to flash 'on' and 'off' in sympathy with the clock which is connected to the D0 input line.

S4 should now be adjusted to produce a logic 1 on the S0 line whilst S3 remains at logic 0. In this condition the i.e.d. will stop flashing and become extinguished. Now depress S1 to produce a logic 1 on the D1 input. The i.e.d. will become illuminated whilst S1 is held down and will become extinguished again when S1 is released.

S3 and S4 should now be adjusted to produce logic 1 and logic 0 on the S1 and S0 select inputs respectively. S2 should now be depressed to produce a logic 1 on the D2 input. The i.e.d. input will become illuminated for as long as S2 is held down.

Finally, S4 should be adjusted to produce a logic 1 input whilst S3 remains at logic 1. In this condition D1 should be seen to flash 'on' and 'off' in sympathy with the inverted clock. (i.e. when the clock i.e.d. is 'on', the output i.e.d. is 'off', and vice versa). We can summarise these observations as shown in Table 5.5.

SELECT INPUTS		OUTPUT (D1)
S1 (S4)	S0 (S3)	
0	0	D0 (CLOCK)
0	1	D1 (S1)
1	0	D2 (S2)
1	1	D3 (CLOCK)

Table 5.5. Outputs provided by the circuit of Fig. 5.7. (Note: brackets indicate Logic Tutor functions)

A PRACTICAL APPLICATION OF THE 74LS153

We shall now turn our attention to a simple practical application of the 74LS153 four-way data multiplexer. Let's assume that we wish to provide digital selection of the output frequencies of a four-stage binary counter. The four Q outputs of the binary counter can be fed to the four data inputs of the multiplexer whilst the two select inputs are fed with a two-bit control signal.

The circuit of a suitable arrangement is shown in Fig. 5.7. IC1a forms a simple relaxation oscillator in which the output frequency is determined by the time constant, $C \times R$. IC1b forms an inverting buffer, the output of which is a rectangular pulse wave having a duty cycle of approximately 1:2 and a frequency of approximately 32Hz. This signal is then fed to the CLOCK input of IC2, a 7493 four stage binary counter.

In order to enable the normal counting sequence, the two master reset inputs, MR1 and MR2, are taken to logic 0 and the four Q outputs then have frequencies of 16Hz, 8Hz, 4Hz and 2Hz approximately.

The 7414 and 74LS153 devices should be left in sockets D and E whilst the 7493 should be inserted in socket B checking, as usual, that pin-1 aligns with B1. The following links should then be made:-

- B1 to B14
 - B2 to B3
 - B3 to logic 0
 - B5 to +5V (supply)
 - B10 to E4
 - B11 to E5
 - B12 to 0V (common)
 - B13 to E3
 - B14 to E6
 - B16 to D4
 - D1 to logic 0 (via a 47 μ F 25V cap)
 - D1 to D2 (via a 470 ohm 0.25W)
 - D2 to D3
 - D7 to 0V (common)
 - D16 to +5V (supply)
 - E1 to logic 0
 - E2 to S3
 - E7 to D1 (D1 shows o/p freq.)
 - E8 to 0V
 - E14 to S4
 - E16 to +5V (supply)
- (A total of 20 links and 2 components)

The two select inputs should first be set to logic 0 using S3 and S4. The output indicator (i.e.d. D1) should then be seen to flash rapidly 'on' and 'off' with a frequency of approximately 16Hz. The three other possible settings of S3 and S4 should then be tested.

NEXT MONTH: De-multiplexers and time domain multiplexing.

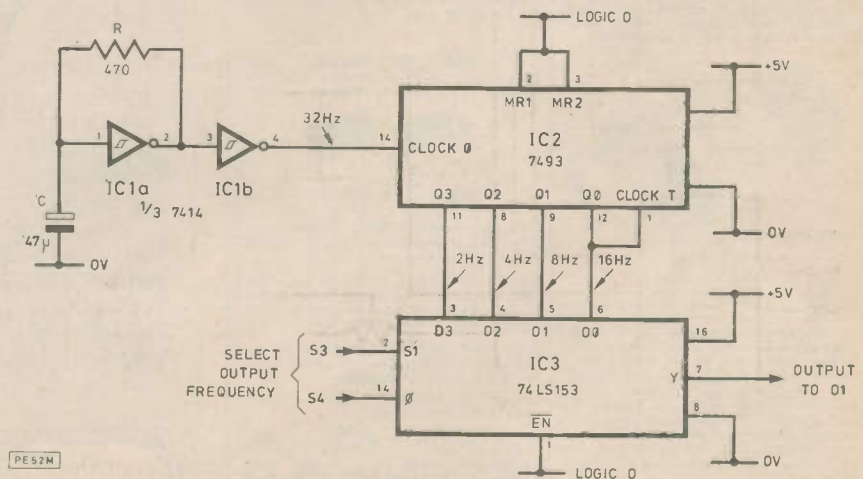


Fig. 5.7. Simple application of the 74LS153

Heathkit - IT'S A PLEASURE TO BUILD

Bring the enjoyment back into your hobby with a kit from Heathkit. The beautifully illustrated documentation and step-by-step instructions make building a Heathkit a relaxing, absorbing pleasure! Choose from their huge range of fascinating kits and self-instruction electronics and computing courses.

The Heathkit range includes the ultimate in amateur radio kits, computerised weather stations, a highly sophisticated robot, a 16-bit computer kit and a range of home (or classroom) learning courses. These state-of-the-art courses have easy-to-understand texts and illustrations, divided into sections so that you can progress at your own pace, whilst the hands-on experiments ensure long-term retention of the material covered.



*You'll be proud to say,
"I built it myself!"*

You'll find Heathkits available for Amateur Radio Gear • Car Test Equipment • Kits For The Home • Self-Instruction Courses • Computer Kits • Test Instrument Kits • Kits For Weather Measurements.

All the most popular kits and educational products are fully detailed in the 1984 Maplin catalogue (see outside back cover of this magazine for details) or for the full list of Heathkit products send 50p for the Heathkit International Catalogue complete with a UK price list of all items.

All Heathkit products available in the UK from:

Maplin Electronic Supplies Ltd.
P.O. Box 3, Rayleigh,
Essex, SS6 8LR.
Tel: (0702) 552911.

(For shop addresses see back cover.)

NEW THIS MONTH

Z917 PSU PANEL - 320x190mm with MJ802 (30A 100V 200W) on large heatsink. 7 smaller heatsinks contain 2x7805, 7812, 7905; 2xMJ2955; 2SA473. Also 555, 3 x 4A bridge rects, large smoothing caps, multway plugs and sockets etc. Ex-equip working order. Only £8.50.

DIP BOARD

Fibreglass DIP board 158x165mm double sided with 58w 0.1" edge connector gold plated. Vero. £3.50.

20 WAY RIBBON CABLE


Twisted and flat computer grade for lower crosstalk. Reformed into flat sections every 21" for IDC connectors. Only 70p/21" or £25 per 100ft reel.

3½ DIGIT LCD DPM

Type 900S self powered. Input range 4-20mA. Contained in std DIN enclosure 96x48x100mm. £15.

"TREKKER"

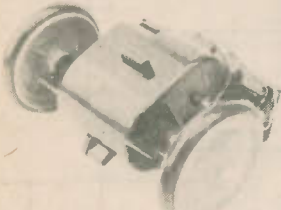Computer-controlled Robot built around the gearbox described below. Complete kit of parts inc PCB, program listings for BBC (other micros soon). £44.85. 20W ribbon cable (min 3m recommended - 5m better). £1.30/m. SAE for illustrated leaflet.



The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the back ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors etc. £5.95. Suitable. Two new types of wheels can be supplied (the aluminium discs and smaller plastic wheels are now sold out). Type A has 7 spokes with a round black tyre and is 100mm dia. Type B is a solid heavy duty wheel 107mm dia with a flat rigid tyre 17mm wide. Photo shows gearbox with one of each type of wheel on it.

PRICES: Gearbox with data sheets: £5.95 ea
Wheel type A: £0.70 ea
Wheel type B: £0.90 ea

1984/85 CATALOGUE

84 page A4 size - Bigger, Brighter, Better - more components than ever before! With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00!! Winter Supplement due out November - Send large SAE for your free copy.

1W AMPLIFIER

Z914 - Audio amp panel 95x65mm with TBA820 chip. Gives 1W output with 9V supply. Switch and vol. control. Just connect batt. and speaker. Full details supplied. Only £1.50, 10 for £12; 25 for £25.

FIBRE OPTICS


Scoop purchase of single and twin cable. For use with visible light or infra-red. Core 1mm dia, overall 2.25mm dia. Single 50p/m; 20m coil £6.30. Twin 90p/m; 20m coil £11.00.

MINIATURE RELAYS

PCB mounting, DPXD size 20x15x15mm. Available in 3, 9 or 12V. £1 each.

AM TUNER PANEL

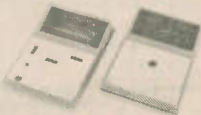Z916 - For use with mono amp above. Neat panel 60x45mm. Only £1.50; 10 for £12.00.



These digital multimeter cases are moulded in high impact black plastic and are offered at an extremely attractive price to clear stocks.

DP2010 - 110x80x20mm, this too has cut-outs for range switches and terminals with a smart aluminium fascia marked with ranges etc. Battery accessible by removable cover on back 75p.

DP100 - Same size as above, but this was for use as a digital thermometer, so there's only a single 9mm Ø hole in the front panel 75p.


Official orders welcome - minimum invoice charge £10. Np. min. on CWO.

Our store has enormous stocks of components and is open from 9.5.30 Mon-Sat. Come & see us!

GREENWELD
443C Milbrook Road Southampton
SO1 0HX Tel (0703) 772501/783740
All prices include VAT. JUST ADD 6p P&P

FOR QUALITY COMPONENTS BY MAIL ORDER

ELECTROVALUE

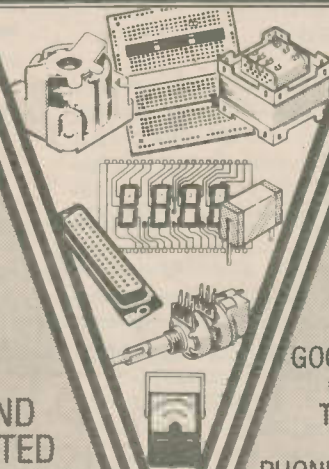

FREE 44 PAGE PRICED AND ILLUSTRATED CATALOGUE ON REQUEST

FREE POSTAGE GOOD DISCOUNTS GOOD SERVICE THOUSANDS OF STOCK ITEMS PHONE YOUR ORDER ACCESS OR BARCLAYCARD

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475
North Branch, 680 Burnage Lane, Manchester M19 1NA
Phone 061 432 4945
Please mention this publication when replying

Mono/Stereo

Chorus & Flanger

JOHN M.H.BECKER

PART TWO

THE clock signal that causes the delay chips to sample and transfer their charges from stage to stage is produced by IC9 (Fig. 6). This is a standard linear voltage controlled oscillator chip that produces a squarewave output the frequency of which is related to the value of C24, the current through VR9, and the voltage present on pin 9. The single output from IC9 needs to be split into two opposing phases as required by the delay chips. If a normal phase split were to be given then the opposing edges of the antiphase square waves would coincide. This overlap is prone to causing system noise from the delay chip outputs even though the TDA1097 is basically a low noise device, capable of a 77dB signal-to-noise ratio at a 100kHz clock frequency, though this degrades slightly with lower clock rates. The overlap on the edges of the clock is eliminated by the flip flop stage IC10 in conjunction with the NAND gates IC11a-b. C25 and R83 slow down the mutual triggering of the flip flop and gates, resulting in a twin phase output having a short delay between the respective squarewave edges. Oscillograms Fig. 7a to 7c show the 'with' and 'without' effect of the overlap elimination.

Varying the voltage applied to pin 9 of IC9 varies the clock frequency. For the automatic modulation of the clock a constantly varying voltage is produced by the low speed triangle wave oscillator around IC8a-b, and having a frequency governed by the resistance of VR7 and the value of C22. (Oscillogram Fig. 8.) Decreasing either increases the output frequency. The modulation can be switched in and out by S4, and the level varied from nil to full by the depth control VR8. C23 slightly rounds off the triangle peaks at faster modulation speeds. The modulating frequency range is controllable between about 50 milliseconds and 30 seconds, the clock frequency range is between about 12kHz and 100kHz. For a single delay chip the delay time range is thus

about 64ms to 7.68ms, cascading two delays doubles the delay times. With the modulating oscillator switched out of circuit the unit can of course be used as a standard reverb or short-echo unit, though these effects will not be so pronounced as those obtainable with the *September 1984 PE Echo-Reverb* unit.

POWER SUPPLY

The unit has been designed to operate from two 9 volt batteries producing +9V/0V/-9V, and drawing between 13mA and 20mA, depending on the clock oscillator rate. IC2 and IC3 though do not like a total voltage drop across them in excess of 16V, which also means that controlling voltages must not exceed this either. The positive voltage delivered to IC2, 3, 9, 10 and 11 is thus reduced to a more suitable level by the drop across the resistor R62 in the delay line bias divider network. The voltage at R62 is within limits with all i.c.s in circuit, but may rise if any of the said 5 are not in their sockets when power is applied. IC9-11 will not mind, but IC2 and 3 may object. The unit may be operated from a stabilised power supply if preferred. The acceptable range is from +5V/0V/-5V to +9V/0V/-9V. If it is necessary to run from a power supply greater than +9V/0V/-9V then two voltage regulator devices should be inserted between the power supply and the unit as shown in Fig. 9. The voltage drop across the regulators must be greater than 2V, and R62 may be replaced by a link wire.

CONSTRUCTION

The component layouts for both boards are shown in Figs. 10 and 11. The short link wires on the p.c.b.s can be made from resistor cut-off leads shaped to the correct spacing with thin nosed pliers. Sockets should be used with all i.c.s. The wiring diagram for the unit is shown in Fig. 13. Bring the

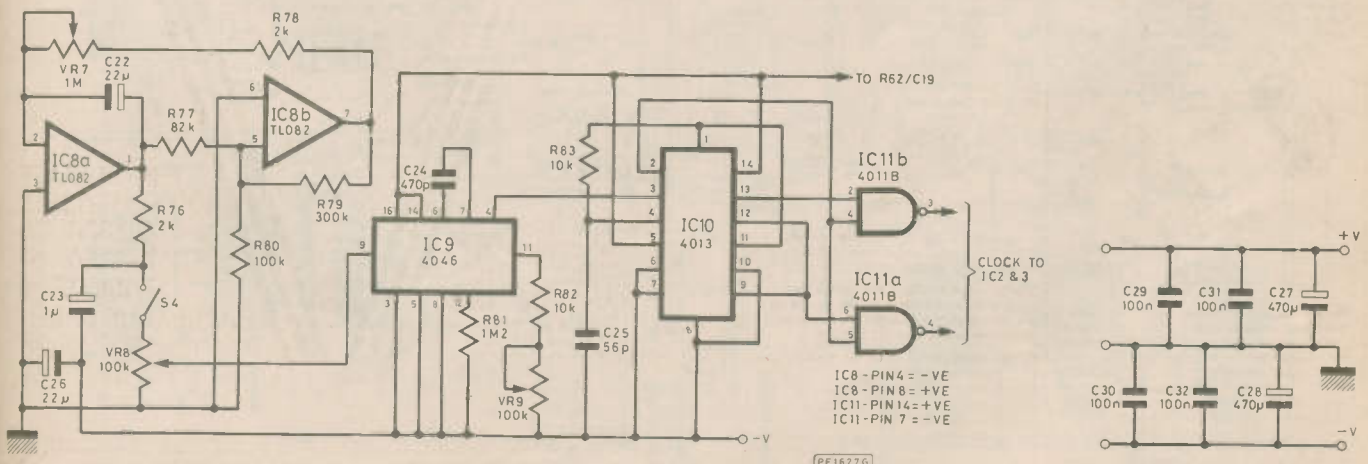


Fig. 6. Circuit diagram of the Clock Circuit

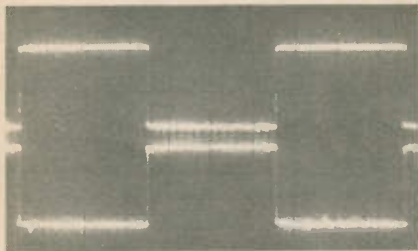


Fig. 7a. Usual appearance of two square-waves without overlap removal

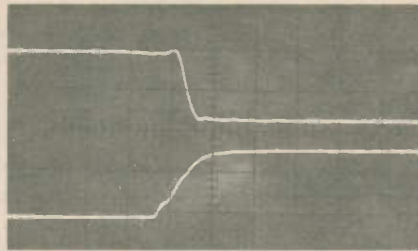


Fig. 7b. Close up of overlap

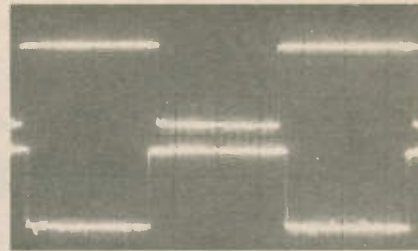


Fig. 7c. Accentuated overlap removal as used in unit

Fig. 7. Clock edge overlap of two anti-phase square-waves



Fig. 8. Modulation oscillator waveform

OPTIONAL REGULATOR FOR REDUCING VOLTAGE FROM EXISTING PSU TO LEVEL SUITABLE FOR CHORUS UNIT.

PE1633G

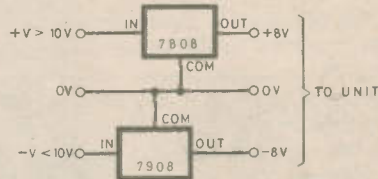


Fig. 9. Optional regulator circuit

connecting wires neatly around the edges of the p.c.b.s to the controls. The clock leads to IC2 and IC3 should be brought forward past C19, turn left at the front panel, then along to the small p.c.b., turn right and connect. Do not take them on what appears to be the shorter route across the main p.c.b. as this would direct them across some parts that might pick up any stray radiation signal. Unless you have the

eyes of an eagle, thoroughly check all the p.c.b. joins with a magnifying glass. Only after all checking has been done should the i.c.s be inserted into their sockets, remembering that IC2, 3, 7, 9, 10 and 11 are MOS devices and require the normal handling precautions. The main point being to keep yourself and equipment free of static electricity by touching a grounded source before handling them.

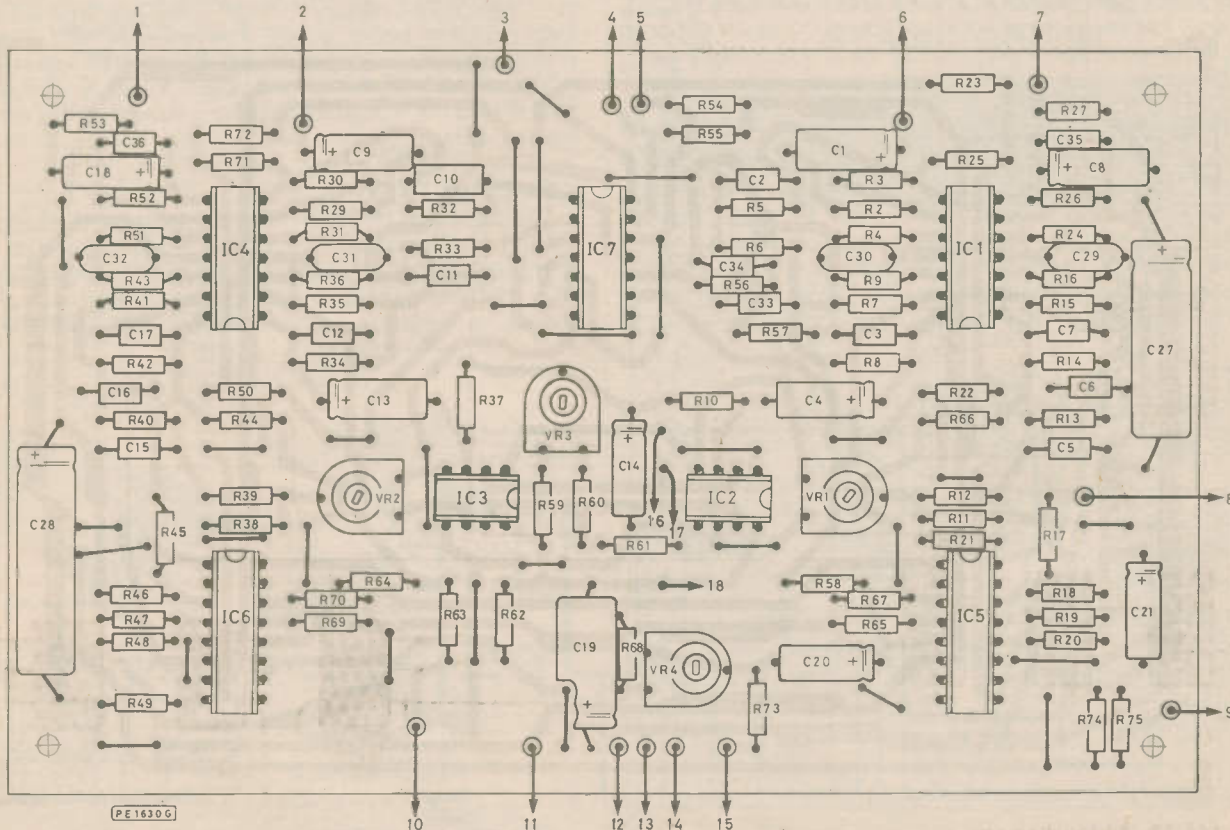


Fig. 10. Component layout of the Main Board

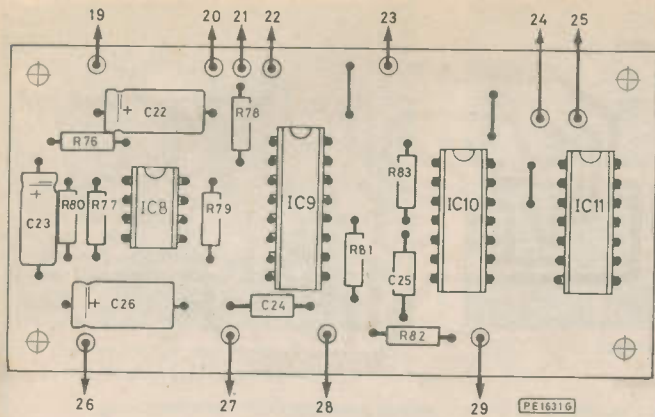


Fig. 11. Component layout for the Clock Board

SETTING UP

This is quite straightforward and specialised equipment is not needed. First, VR1 to VR3 midway, VR4 max resistance (anticlockwise), VR5 and VR6 min, VR7 to VR9 max, S1 to S4 off. Plug in a music signal from a prerecorded source into the X1 socket. Check that the output level reaching the main amplifier used is the same as the original. Switch on S3 enabling the VCA, and bringing up VR6 a change in amplitude and tonal quality should increase. Rotating the clock oscillator speed control VR9 to its maximum resistance will slow down the delay and emphasise the double tracking effect. This will be more apparent with staccato sounds rather than mellow drawn out notes. Adjust VR3 around its midway point until minimum waveform distortion is heard, which will also coincide with the best delay effect. If an oscilloscope is available, the waveform balance will be obvious when monitoring the output at VR1 and VR2 in the presence of a strong input signal. (Oscillograms Figs. 12a and 12b.)

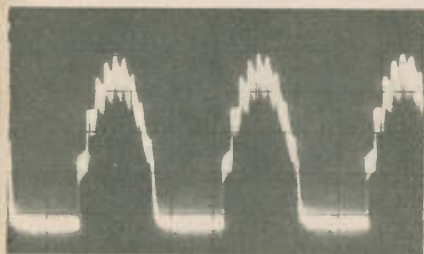


Fig. 12a. Sine-wave with VR3 unbalanced but VR1 correct


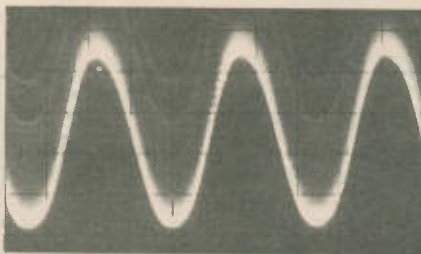


Fig. 12b. Sine-wave with both VR1 and VR3 correct

Fig. 12. Traces seen at the wiper of VR1

Switch on S4 bringing in the sweep modulator. Varying VR8 will vary the modulation depth, and VR7 will vary the modulation rate. Switch off S4, reset VR9 to slowest clock speed, VR6 to maximum level, switch on S2 for feedback enabling. Slowly bring up VR5 and a hollowness to the signal should come in. Maximise VR5 and carefully reduce the resistance of VR4 until the circuit almost goes into full feedback howl. If howl occurs, sharply

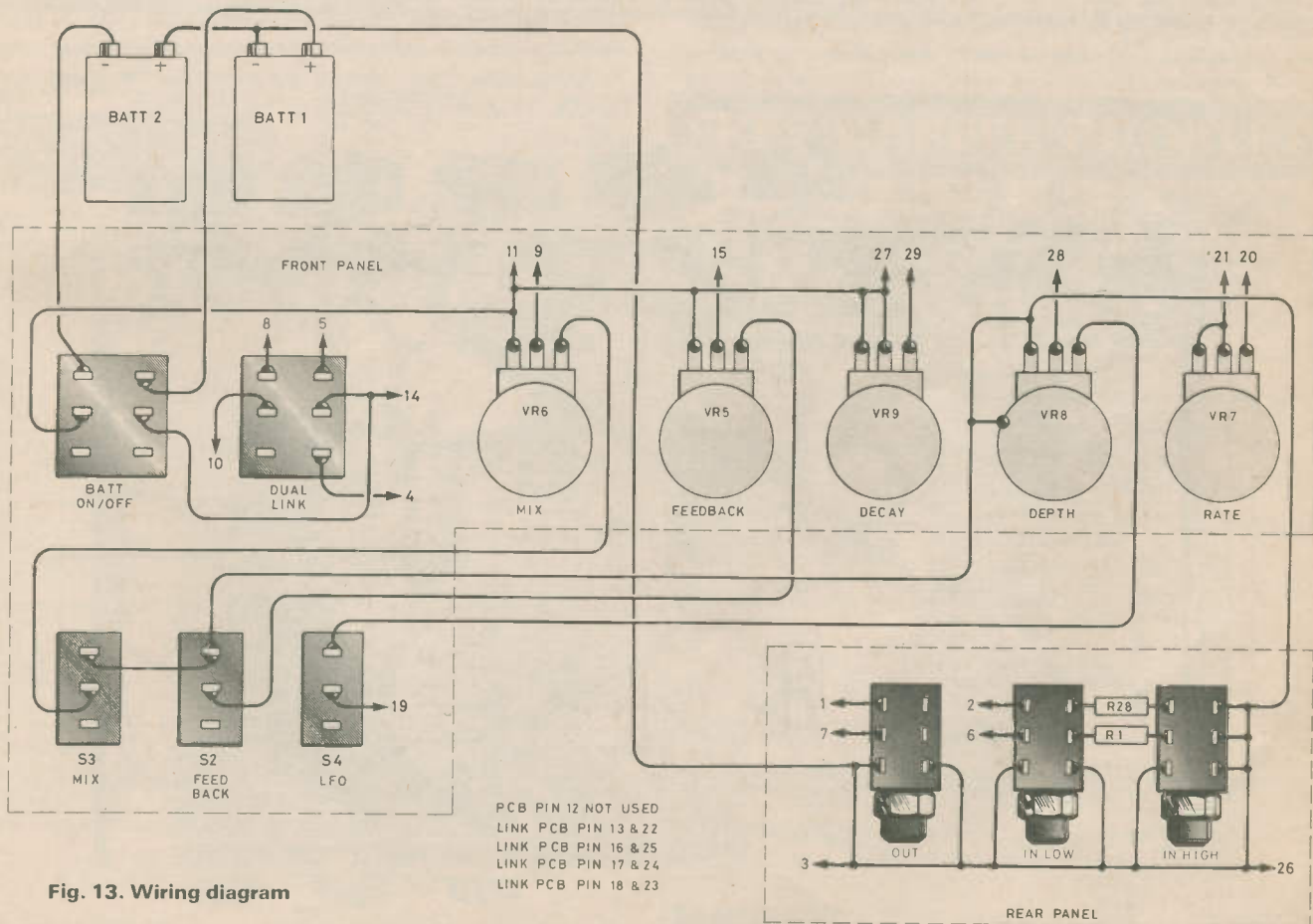

PCB PIN 12 NOT USED
LINK PCB PIN 13 & 22
LINK PCB PIN 16 & 25
LINK PCB PIN 17 & 24
LINK PCB PIN 18 & 23

NOTE R1 & R28 ON JACK SOCKETS

Fig. 13. Wiring diagram

PE1632G

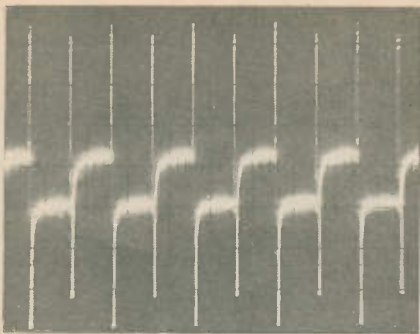


Fig. 14a. Clock residual with VR1 unbalanced (no signal)

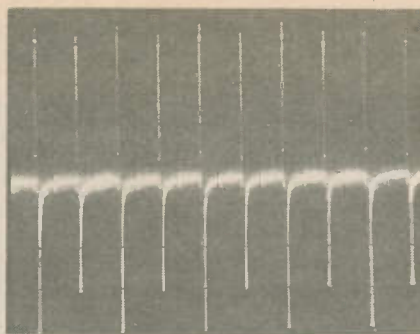


Fig. 14b. Clock residual with VR1 balanced (no signal)

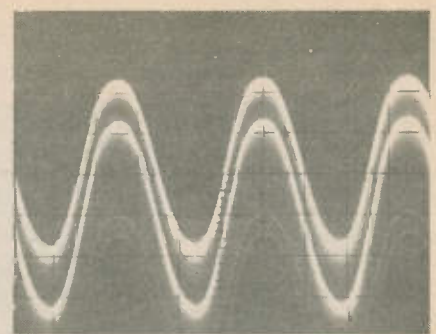


Fig. 14c. Sine-wave signal with VR1 unbalanced but VR3 correct


Fig. 14. Traces seen at the wiper of VR1

reduce VR4 and start again. Aim for the closest possible to the howl point. Howl is more likely to occur with strong bass notes. Switch on S1 to couple the two delay circuits in series and so produce the double emphasis. If necessary back off VR4 slightly as the increase in level may kick the circuit into howl again. If an oscilloscope is not available VR1 and VR2 should be left midway and ignored, otherwise adjust them for the best balance point of the residual clock frequency in the absence of an input signal. (Oscillograms Figs. 14a to 14c.) Switch on S4 and experiment with the various settings until familiar with the control options available, if necessary readjusting VR3 or VR4.

USE

There are no restrictions to the type of signal fed in provided that the amplitude is less than the distortion level, and that the type of music lends itself to enhancement within the factors discussed earlier and summarised below. It will soon become obvious which type of music requires which particular control setting for the best effect. This is a

matter of personal preference, but the author feels that as with any effects unit, moderation is the keyword. Certainly overemphasis of an effect is dramatic, but it is easier to become tired of an over dramatic effect than one which produces a discrete change. In general terms music having a high harmonic content, but otherwise of a simple nature, will benefit most. Mellow or full orchestral sounds will not show the same degree of change. In the first case there is insufficient harmonic information available in the signal for the effect to fully develop. In the second case, the sound is already so full that the effect will probably be lost amongst the tonal complexity unless the original sound is full of spiky waveforms. The harsher sounds of voice, drums, harmonically rich synthesiser and organ music produce excellent effects as the waveforms involved are complex. Pure sine tones and muted waveforms, especially in the lower octaves, will be less apparent. For the chorusing effect a slower clock oscillator speed is preferable as the delay time is greater, for flanging, faster clock speeds are better as the phase shift occurs then at a more marked rate and spacing. ★

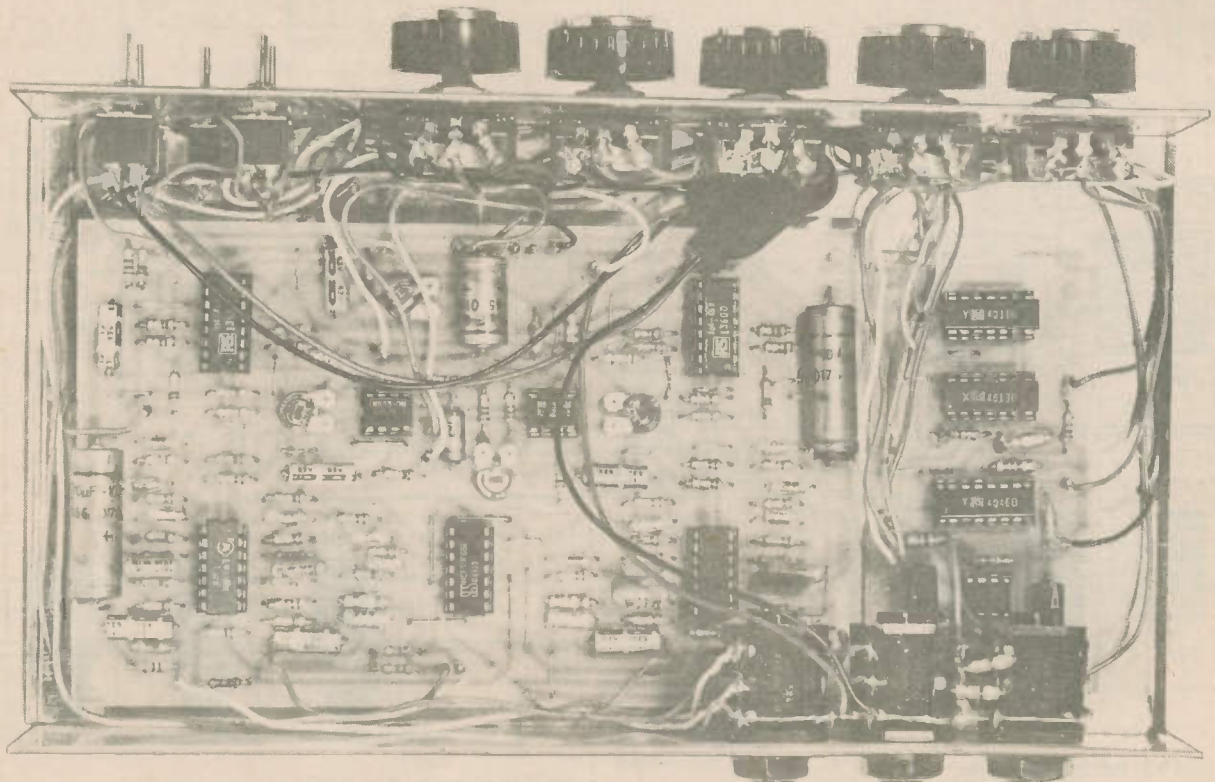

Photograph illustrating the internal details of the Chorus and Flanger Unit


P.E. AUDIO EFFECTS AND OTHER SUPER SOUND KITS!



P.E. MONO-STEREO ECHO-REVERB (SEP84) 200ms echo, lengthy reverb, multi-tracking kit as published - BLK box: SET 218 £55.66



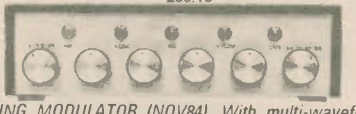P.E. FILTER-SHIFT PHASER (OCT84). Enhanced Phasing with modulated filter shifting. Kit as published - BLK box: SET 226 £39.13



P.E. RING MODULATOR (NOV84). With multi-waveform VCO, Noise Gate & Auto-level Control. Kit as published - BLK box: SET 231 £39.99



P.E. MONO-STEREO CHORUS FLANGER (JAN85). Superb dual mode music enhancement. Kit as published - BLK box: SET 235 £55.66

BLK BOX - steel & aluminium, black plastic finish. STO BOX - plain aluminium, lipped lid. SET codes include PCBs, parts, instructions, boxes, wire, solder. More details & kits in catalogue - send S.A.E. (Overseas £1 or 5 IRC's).

	CODE	STD BOX	BLK BOX
BASS BOOST: Increases volume of lower octaves	SET 138B	£8.46	£11.46
BLOW BOX: Voice operated VCF & VCA for fascinating effects	SET 214	£24.33	£28.33
CHORUS (SIMPLE): Multiplied solo enhancement	SET 162	£31.40	£34.90
COMPRESSOR: Limits & levels maximum signal strength	SET 133	£10.86	£13.86
ENVELOPE SHAPER: Note triggered AOSR unit with VCA	SET 174	£17.15	£20.65
EQUALISER: Variable combinations of Low, Mid, Top & Notch	SET 217	£22.33	£25.83
EQUALISER: 10 Channels fully variable	SET 134	£37.83	£41.83
FADER: Voice operated with 5 response controls	SET 167	£14.21	£17.21
FLANGER (SIMPLE): Fascinating phased resonance effects	SET 153	£22.74	£26.24
FREQUENCY CHANGER: Tunable note & waveform modifier	SET 172	£34.46	£37.96
FREQUENCY DOUBLER: Guitar octave raiser & tone changer	SET 98	£12.40	£15.40
FUNKY-WOBULO: Modulates a singing voice	SET 149	£9.80	£12.80
FUZZ: Smooth distortion, retains attack & decay	SET 91	£10.57	£13.57
GUITAR OVERDRIVE: Heavy fuzz with selectable qualities	SET 56	£19.73	£23.23
GUITAR SUSTAIN: Extends note decay time, with noise gate	SET 222	£22.81	£25.31
GUITAR TO SYNTH INTERFACE: With voltage & trig outputs	SET 173	£32.87	£36.37
HAND CLAPPER: Auto & manual variable clap effects	SET 197	£22.69	£25.69
HEADPHONE AMP: 2 watts into phones or speaker, variable	SET 156M	£12.03	£15.53
JABBERVOX: Voice disquiser with reverb & tremolo	SET 150	£23.84	£27.34
METRONOME: With audio output & visual beat & downbeat	SET 143	£13.81	£16.81
MIC PRE-AMP: Variable gain & switched tone response	SET 147	£7.13	£10.13
MIXERS: Several in catalogue			
MOCK STEREO: Splits mono signal into stereo simulation	SET 213	£19.87	£23.37
MULTIPROCESSOR: Flng, Rvb, Faze, Fuzz, Wah, Trem, Vib	SET 189	£57.14	£61.14
MUSIC MODULO: 8 variable tremolo & wah guitar effects	SET 196	£18.79	£21.79
MUSICAL CALL SIGN: Programmed call sign generator	SET 121	£12.91	£16.41
NOISE GATE: Reduces tape & system noise	SET 145	£9.97	£12.97
PHASER (SIMPLE): Auto & manual rate & depth controls	SET 164	£18.40	£21.90
REVERB: (SIMPLE) Mono/stereo, variable depth & delay	SET 203	£25.54	£29.54
RHYTHM GENERATOR: Computer driven, 9 drum effects	SET 185	£30.64	£34.64
RHYTHM GENERATOR: 15 pre-programmed rhythms, 9 effects	SET 170	£35.64	£39.14
ROBOVOX: Versatile robot type voice modifier	SET 165	£21.03	£24.53
SPEECH PROCESSOR: Clearer speech and level control	SET 110	£9.68	£12.68
STORMS EFFECTS: Auto & manual wind, rain & surf effects	SET 154	£15.86	£19.36
SWEEP GENERATOR: Auto sine wave 20Hz-15KHz, variable	SET 169	£16.41	£19.91
TOM-TOM SYNTH: Sound triggered, multivariable	SET 190	£15.05	£18.05
TOPE CONTROL: Bass, mid, treble, gain & cut	SET 139	£13.17	£16.67
TREBLE BOOST: Increases volume of upper octaves	SET 138T	£8.13	£11.13
TREMULO: Mono variable rate & depth modulation	SET 136	£9.71	£12.71
VOLTAGE CONTROLLED FILTER: 12dB, variable modes	SET 178	£17.02	£20.52
VOCALVOX: Modular vocoder, 7 chans, extendable	SET 152	£64.31	£68.31
VOICE OF SWITCH: Variable sensitivity & delay	SET 155	£12.44	£15.44
WAH-WAH: Auto, manual & note triggered	SET 123L	£13.41	£16.41
	SET 140	£17.26	£20.76

MAIL ORDER: Add 15% VAT & E1 P&P to all orders (overseas details in cat). Payment CWO, CHQ, PO, ACCESS, VISA. Details correct at press. E&OE. Oespach usually 10-14 days.

PHONOSONICS, DEPT PE52, 8 FINUCANE DRIVE, ORPINGTON, KENT, BR5 4ED.

Tel: Orpington 37821 (STD 0689, London 66), Mon-Fri 10-7.

ORIC AND SINCLAIR COMPUTERS



Oric 1 computer 48K £85 (£82) £92. Oric Atmos computer 48K £171 (£158) £168. Oric Colour Printer £134 (£123) £140. Sinclair flat screen TV (£113) (£105) £115. Sinclair Spectrum Plus Computer £182 (£178) £187. Sinclair QL Computer £406 (£385) £410. Sinclair Spectrum 48K £131 (£131) £143. Microdrive £51 (£50) £60. RS232 interface 1 £51 (£50) £60. Special offer:- Microdrive + Interface 1 + 4 cartridges £102 (£100) £120. Blank microdrive cartridges £5.50 (£6) £7. Standard floppy disc interface for Spectrum £102 (£92) £112. (See Cumana disc section for suitable disc drives). Fuller FDS keyboard for spectrum £52 (£52) £62. Fuller master unit £56 (£56) £62. Interface 2 £20.45 (£20) £24. 32k memory upgrade kit for 16K spectrum (issue 2 and 3 only) £31 (£28) £30. Spectrum Centronics printer interface £51 (£47) £52. ZX printer has been replaced by the Alphacom 32 £71 (£69) £82. 5 printer rolls (state whether Sinclair or Alphacom) £13 (£16) £21. ZX81 computer £45 (£44) £54. 16K ram packs for ZX81 £28 (£25) £30.

COMMODORE COMPUTERS

Commodore C16 Starter Pack £145 (£142) £162. Commodore Plus/4 £305 (£281) £301. Commodore 64 £222 (£215) £235. Converter to allow most ordinary mono cassette recorders to be used with the Vic 20 and the Commodore 64: £9.78 (£9) £11. Bargain package: cassette converter + compatible cassette recorder £37 (£38) £44. Commodore cassette recorder £43 (£44) £50. Printer interfaces for Vic 20 and the Commodore 64:- Centronics £45 (£41) £46. RS232 £45 (£41) £46. Disc drive £233 (£209) £234. 1520 printer/plotter £165 (£149) £159. MPS801 Printer £235 (£220) £245. Light pen £29 (£29) £33.

SWANLEY ELECTRONICS

The Computer Export Specialists
Dept PE, 32 Goldsel Rd., Swanley, Kent BR8 8EZ, England.
Please allow 7 days for delivery.

Tel: Swanley (0322) 64851. Official orders welcome. UK prices are shown first and include post and VAT. The second price in brackets is for export customers in Europe and includes insured air mail postage. The third price is for export customers outside Europe (including Australia etc) and includes insured airmail postage.


ACORN COMPUTERS

Electron £173 (£179) £199. BBC Model B £404 (£357) £387. Kenda double density disk interface system £149 (£131) £141. See below for suitable disc drives.

CUMANA DISC DRIVES

To suit disc interfaces of Sinclair spectrum, BBC B and Videogenic. Single:- 40 track single sided £176 (£158) £178. 40 track double sided £218 (£195) £215. 80tr ss £207 (£186) £206. 80tr ds £234 (£209) £229. Dual:- 40tr ss £299 (£280) £320. 40tr ds £395 (£353) £393. 80tr ss £372 (£334) £374. 80tr ds £437 (£390) £430.

PRINTERS

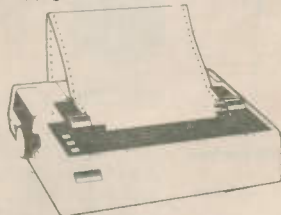

Oki Microline 80 £138 (£135) £165. Brother HR5 £162 (£146) £170. Shinwa CTI CP80 £225 (£218) £248. Cannon PW1080A £332 (£299) £329. Epson RX80 £277 (£251) £282. Epson RX80F/T £314 (£286) £316. Epson FX80 £399 (£358) £388. Combined matrix printers and electric typewriters:- Brother EP22 £173 (£166) £186. Brother EP44 £258 (£235) £260. MCP40 Oric colour printer/plotter £134 (£123) £140. Interfaces to run the above printers from Vic and the Commodore 64 £45 (£41) £46. We can supply interfaces to run the above printers from Sharp computers £58 (£52) £55. UK101, SUPERBOARD AND VIDEOGENIE

We still support these Computers. Write for our list.
COMPUTER REPAIRS
We offer a world-wide repair service. Write for a quotation.

FREE CAREER BOOKLET

Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you.

Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today — at no cost or obligation at all.

GCE

Over 40 'O' and 'A' Level subjects from which to choose. Your vital passport to career success.

COMPUTER PROGRAMMING

RADIO AMATEUR'S LICENCE

ELECTRONICS

INTERIOR DESIGN

COMMERCIAL ART

WRITING FOR PROFIT

TV, RADIO & AUDIO SERVICING

CAR MECHANICS

BOOK-KEEPING & ACCOUNTANCY

Please send FREE DETAILS for the course ticked above.

Name

Address

P.Code

ICS

ICS Dept. EDS 25
8 Elliot Place
Clydeaway Centre
Glasgow G3 8EF

041 221 2926
or 01 622 9911
(all hours)



DRA 100

DOPPLER RADAR INTRUDER ALARM



SIMPLY THE BEST

- ★ **The best** because its blanket coverage means that all doors and windows can be covered without the need for individual switches and wiring.
- ★ **The best** because its low power RF radiation pattern is unaffected by air disturbance – unlike ultrasonic or passive IR systems.
- ★ **The best** because movement can be detected through brick walls. Intruders can be deterred before they intrude!
- ★ **The best** because the system can be enlarged by the addition of passive detectors such as reed switches, heat detectors, personal attack buttons etc.
- ★ **The best** because the size of the protected area is variable. Careful adjustment of the transmitters allows "safe areas" to be created, enabling legitimate callers to avoid triggering the alarm.
- ★ **The best** because it represents top value, the DRA 100 in kit form costs less than most perimeter wiring systems – and offers so much more protection for your money.

Standard Kit (including 2 transmitters) **£119.00 + VAT**

Pair of extra transmitters **£29.00 + VAT**

Special Offer

Extended Kit (including 4 transmitters) **£139.50 + VAT**

The DRA 100 is available from

POWERTRAN cybernetics Ltd.

PORTWAY INDUSTRIAL ESTATE,
ANDOVER, HANTS. SP10 3PE.
TEL (0264) 64455



TWO FABULOUS OFFERS FROM

ALCON

The incredible 'MINI 20'

28 ranges
20k Ω /V d.c. & 4k Ω /V a.c.
(With protective fuse)

Accuracy: 2% d.c. and resistance,
3% a.c.

28 ranges: d.c. V 100mV, 3V, 10V,
30V, 100V, 300V, 600V. d.c. I 50 μ A,
600 μ A, 6mA, 600mA. a.c. V 15V,
50V, 150V, 500V, 1500V. a.c. I
30mA, 300mA, 3.0A. Ohms 0–2k Ω ,
0–2M Ω dB from –10 to +62 in 6
ranges.


Dimensions: 105 x 130 x 40mm.

The 28 ranges cover all likely requirements. Operation is straightforward, just turn the selection switch to the required range.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10.00.

THE IDEAL INSTRUMENT
FOR THE CONSTRUCTOR

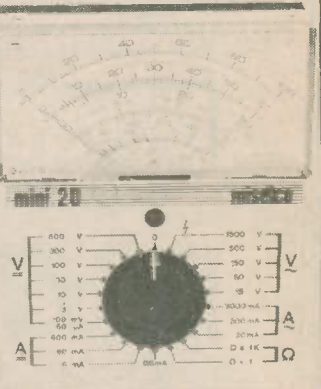
(complete with carrying case, leads and instructions)



ONLY £21.60

'SUPER 20'

A SUPER PROTECTED UNIVERSAL MULTIMETER

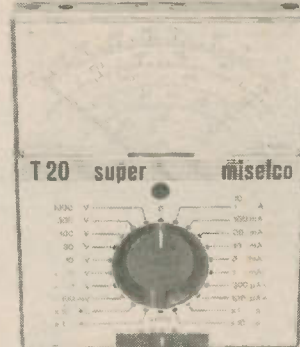

★ 20K Ω /V
AC AND DC

★ 39 RANGES

★ INDESTRUCTIBLE
(automatically protected
on all ranges but 10A)

Accuracy: d.c. ranges and Ω 2% a.c. 3% (of f.s.d.)
39 ranges: d.c. V 100mV, 1.0V, 3.0V, 10V, 30V, 100V, 300V, 1000V.
d.c. I 50 μ A, 100 μ A, 300 μ A, 1.0 μ mA, 3mA, 10mA, 30mA,
100mA, 1A, 10A
a.c. V 10, 30V, 100V, 300V, 1000V;
a.c. I 3mA, 10mA, 30mA, 100mA, 1.0A, 10A.
 Ω 0–5.0k Ω , 0–50k Ω , 0–500k Ω , 5M Ω , 50M Ω .
dB from –10 to +61 in 5 ranges.

Dimensions: 105 x 130 x 40mm.

These special offers is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £20.00.

(complete with carrying case,
leads and instructions)

ONLY £33.50

PRICES Our prices include VAT and postage and goods are normally despatched by return.

For details of these and the many other instruments in the Alcon range, including multimeters, components measuring, automotive and electronic instruments, please write or telephone:

ALCON Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

MICRO-BUS

and MICROPROMPT

ECONOMIC DIGITISER

Sir—Here is a low cost, easy to make project for use with an X/Y plotter, that can be connected to the expansion interface of the UK 101, or virtually any other micro.

The system consists of a flexible arm, equipped with two linear potentiometers and a pointer. This pointer moves over a limited surface of 20 × 20cm. The voltages, generated by the movement are a measure of the position of the pointer. Those potentials cannot be used directly for X/Y plotting, because of their non-linear output.

A solution of that problem is found, by the application of the formula, which gives the relationship between X, Y and the angles of rotation V and H.

If now the analogue values of these angles are translated to digital, the calculation with a BASIC program becomes possible.

The BASIC program can be perceived as a limited loop with continuous conversion, so that the manual movement of the pointer can be digitally stored in memory. It permits also direct writing to a high resolution display.

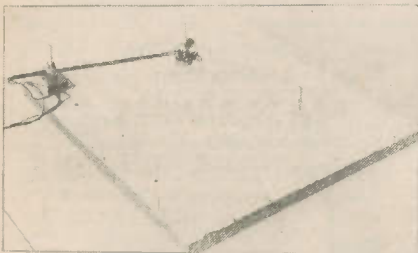


Table 1 shows a typical BASIC program for illustration, and the following notes apply:
5–30 Initialisation of the PIA (A and B) for input.

VIA (A and B) for output.

40–180 Loop for storing data in memory.

190–280 Loop for playback to X/Y recorder.

If the digitiser is used with the UK 101, it may be used with the PE—Expansion Interface published in Jan–July 1981.

I do not use the internal A/D and D/A converters, because I wanted a binary indication for the D/A output and also there is only one output in the interface. You will find the schematics joined.

The potentiometers must be of good quality and very linear. A resolution of approximately 2mm is possible on a surface of 20 × 20cm.

During storing in memory, the values of X and Y are continually displayed, and must be integer, positive and between 0 and 255.

The value of L (line 100) is a multiplication constant to certify an optimum sweep between 0 and 255.

The number 255 (line 110) is added to invert the value of Y, which is negative in this area.

Line 50 in the program is the number of points you wish to fix. The movement of the pointer shall not exceed 3cm/sec.

Line 255 defines the speed of playback, and

Prototype digitiser

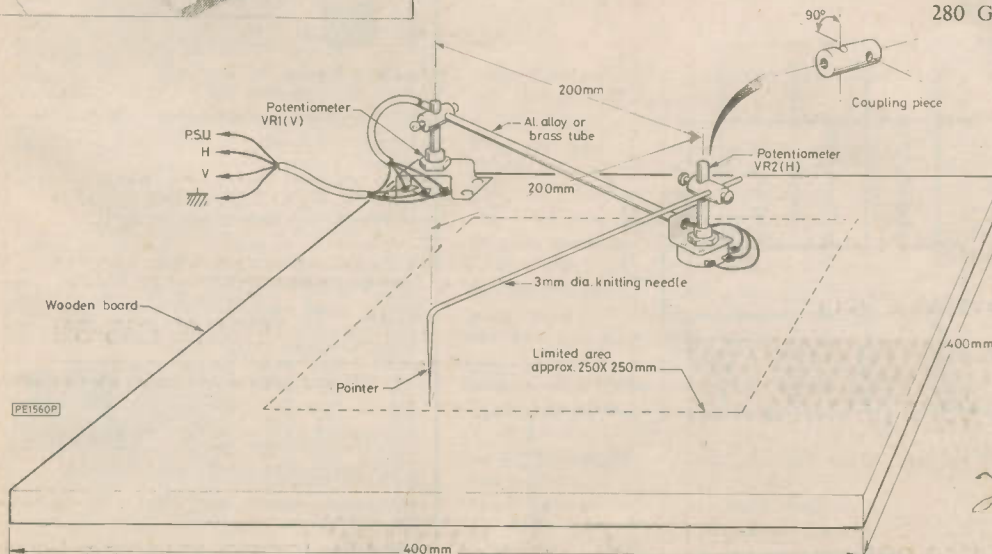


Table 1. Suggested software for calculating the angular co-ordinates

```

5 REM : X/Y PLOTTING ROUTINE
10 P=61340:Q=61342
15 U=61344:W=61345
17 POKEU+2,255:POKEW+2,255
20 POKEP+1,0:POKEP,0:POKEP+1,255
30 POKEQ+1,0:POKEQ,0:POKEQ+1,
  255
40 INPUT "READY FOR START";A$
45 R=5000:S=6000
50 FOR N=1 TO 200
60 POKEP+1,60:POKEP+1,52
70 V=PEEK(P)/100
80 POKEQ+1,60:POKEQ+1,52
90 H=PEEK(Q)/100
100 L=150
110 Y=L*COS(V)+L*COS(V+H):Y=
  INT(Y)+255
120 X=L*SIN(V)+L*SIN(H+V):X=
  INT(X)
130 PRINT X,Y
140 POKER,X:POKES,Y
145 POKEU,X:POKEW,Y
150 R=R+1:S=S+1
160 NEXT N
180 PRINT"END OF LOOP"
190 INPUT"DO YOU WANT A
  PLAYBACK";B$
195 IF B$="Y" THEN 210
200 IF B$="N" THEN 40
210 R=5000:S=6000
220 FOR N=1 TO 200
230 X=PEEK(R):Y=PEEK(S)
240 POKEU,X:POKEW,Y
250 R=R+1:S=S+1
255 FOR D=1 TO 50:NEXT
260 NEXT N
270 PRINT"END OF PLAYBACK"
280 GOTO 190
  
```

Fig. 1. Mechanical construction of the digitiser

Fig. 2. Sample of handwriting traced and stored from the digitiser

Handwriting
Handwriting

MICRO-BUS

and MICROPROMPT

depends on the type of X/Y recorder (graphic, scope, screen).

J. Ockier,
Belgium.

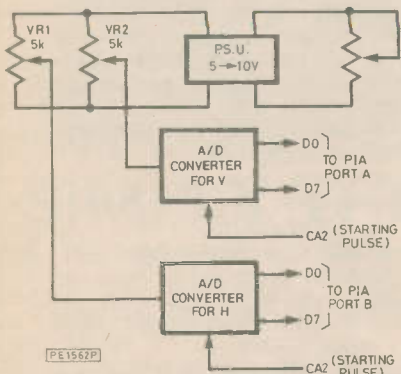


Fig. 4. Block diagram of the digitiser

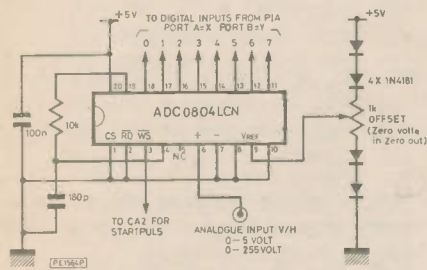


Fig. 5. The ADC channel

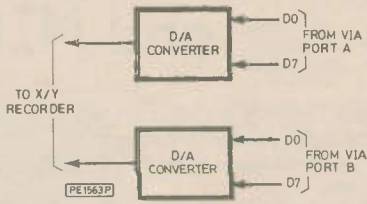


Fig. 3. Block diagram of principle

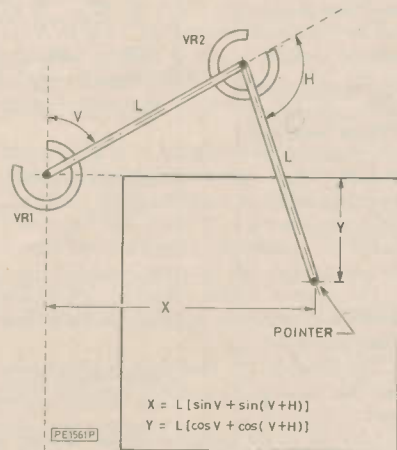


Fig. 6. A plan view showing the geometrics of the digitiser. Good quality highly linear potentiometers must be used to obtain a resolution of around 2mm

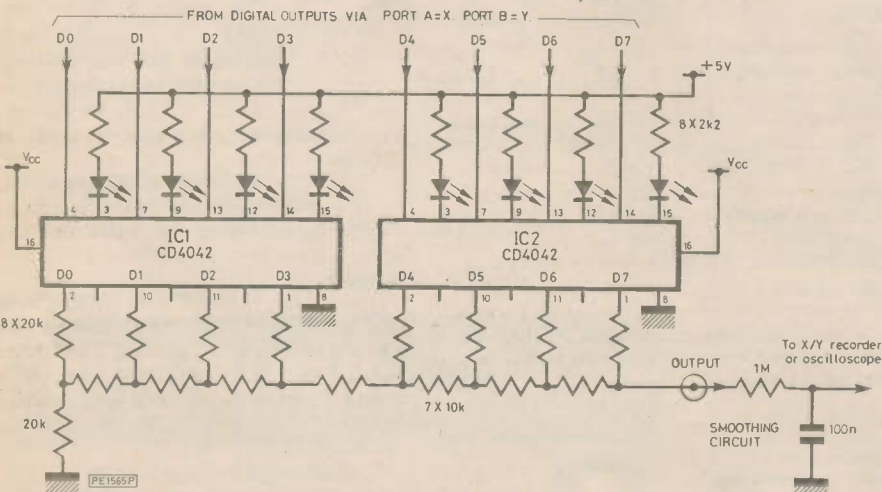


Fig. 7. Converting back to analogue for driving a plotter

baker

★ BAKER ★

GROUP P.A. DISCO
AMPLIFIERS post £2

150 watt Output, 4 input Mixer pre-amp. Illustrated £99
150 watt Output, Slave 500 mv. Input 3 Speaker Outputs £80
150+150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs £125
150 watt P.A. Vocal, 8 inputs. High/Low Mixer Echo Socket £129
100 watt Valve Model, 4 inputs, 5 Outputs. Heavy duty £125
60 watt Mobile 240v AC and 12v DC. 4-8-16 ohm+100v line £89
Reverb Unit for Microphone or Guitar £35 PP £1
Electronic Echo Machine for mic/guitar £85 PP £1. Deluxe £95.

BAKER LOUDSPEAKERS Post £2 each

Type	Model	Size	Watts	Ohms	Price
P.A./Disco/Group	DG50/10	10	50	8/16	£18.00
Midrange	Mid 100/10	10	100	8	£25.00
Hi-Fi	Major	12in	30	4/8/16	£16.00
Hi-Fi	Superb	12in	30	8/16	£26.00
P.A./Disco/Group	DG45	12in	45	4/8/16	£16.00
Hi-Fi	Wooler	12in	80	8	£25.00
Hi-Fi	Auditorium	15in	60	8/16	£37.00
P.A./Disco/Group	DG75	12in	75	4/8/16	£20.00
P.A./Disco/Group	DG100	12in	100	8/16	£26.00
P.A./Disco/Group	DG100/15	15in	100	8/16	£35.00

DISCO CONSOLE Twin Decks, mixer pre amp £145. Carr £10.
Ditto Powered 120 watt £199; or Complete Disco £300.
120 watt £300; 150 watt £360; 300 watt £410. Carr £30.

DELUXE STEREO DISCO MIXER/EQUALISER as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. Headphone Monitor, Mike Talkover Switch As above with 7 Band Graphic £138. **£124 PP £2**

P.A. CABINETS (empty) Single 12 £32; Double 12 £38. carr £10.
WITH SPEAKERS 75W £54; 90W £73; 150W £82; 200W £90.
HORNBOXES 200 Watt £32, 300 Watt £38. Post £4.

WATERPROOF HORNS 8 ohms 25 watt £22. 30 watt £25. 40 watt £33. 20W plus 100 volt line £38. Post £2.

MOTOROLA PIEZO ELECTRONIC HORN TWEETER 3 3/8" square £5
100 watts. No crossover required. 4-8-16 ohm. 7 3/8" x 3 3/8" £10

CROSSOVERS: TWO-WAY 3000 c/s 30 watt £3. 60 watt £5. 100 watt £6.
3 way 950 cps/3000 cps 40 watt £5.50. 100 watt £10.

LOUDSPEAKER BARGAINS Please enquire, many others in stock
4 ohm, 5" 7x4in. £2.50; 6 1/2in, 8x5in. £3. 8in. £2.50; 6 1/2in, 25V £7.50.
8 ohm, 2 3/8in. 3in. £2; 5x3in, 6x4in, 7x4in, 5in. £2.50; 6 1/2in, 8 x 5in £3; 8in. £4.50; 10in. £5; 12in. £6. 8in. 25W £6.50. 8in. hi-fi 60W £12.50.
15 ohm, 2 1/2in. 3 1/2in, 5x3in, 6x4in. £2.50; 6 1/2in 10W £5. 8in. £4. 10in. £7.
25 ohm, 3in. £2; 5x3in, 6x4in, 7x4in. £2.50. 12ohm, 12ohm, 3 1/4in. £4. £1.

Make	Model	Size	Watts	Ohms	Price	Post
AUDAX	WOOFER	5 1/2in, 25	8	£10.50	£1	
GOODMANS	HIFAX	7 1/2x4 1/4in	100	8	£30	£2
GOODMANS	HB WOOFER	8in	60	8	£13.50	£1
WHARFEDALE	WOOFER	8in	30	8	£9.50	£2
CELESTION	DISCO/Group	10in	50	8/16	£21	£2
AKAI	WOOFER	12in	80	8	£16	£2
GOODMANS	HPG/Group	12in	120	8/15	£30.00	£2
GOODMANS	HPD/DISCO	12in	120	8/15	£30.00	£2
HHH	DISCO/Group	15in	48/115	8	£4	£4
GOODMANS	HP/BASS	15in	250	8	£72	£4
GOODMANS	HPG/BASS	18in	230	8	£84	£4

METAL GRILLES 8in. £3.00, 10in. £3.50, 12in. £4.50, 15in. £5.50, 18in. £7.50.

RCS SOUND TO LIGHT CONTROLLER KIT
Printed circuit. Cabinet. 3 channels. 1,000 watts each. Will operate from Hi-Fi or Disco. £19. Post £1.
Ready Built Deluxe 4 Channel 4,000 watt sound chaser + speed + programme controls £69. Mk 2 16 programmes. £89. PP £2

MAINS TRANSFORMERS Price Post

250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A	£7.00	£2
350-0-350V 250mA, 6.3V 6A CT £12.00 Shrouded	£14.00	£2
250V 60mA, 6.3V 2A	£4.75	£1
220V 25mA, 6V 1 Amp £3.00 220V 45mA, 6V 2 Amp £4.00	£1	
Low voltage tapped outputs available		
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00	£2
ditto 2 amp £10.50 3 amp £12.50 5 amp £16.00	£2	
31-25-0-26-33 6amp	£14.00	£2

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid
9V, 3A, 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1 1/2A; 30V, 5A; 17-0-17V, 2A, 35V, 2A; 20-40-60V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 50V, 2A

£8.50 post 50p MINI-MULTI TESTER
Pocket size instrument. o.p.v. DC volts 0.5, 25, 250, 500. AC volts 10, 50, 500, 1000. DC 0-250µA, 0-250mA. Resistance 0 to 600K.
De-Luxe Range Double Meter, 50,000 o.p.v. 7 x 5 x 2in. Resistance 0/20 meg in 5 ranges. Current 50µA to 10A. Volts 0.25V 1000V DC, 10v/1000v AC. £25.00 post £1

PANEL METERS 50µA, 100µA, 500µA, 1mA, 5mA, 100mA, 500mA, 1amp, 2amp, 5amp, 25 volt, VU 2 1/4x2x1 1/4in. £5.50 post 50p

EQUIPMENT CASES: Black Vinyl Covered Top, Ali Base
4 x 2 1/2 x 2 1/4in. £5.50; 6 x 4 x 1 1/2in. £3.60; 8 x 5 x 2in. £4.00; 11 x 6 x 3in. £5.50; 11 3/4 x 6 x 5in. £9.00; 15 x 8 x 4in. £12.00.

ALI ANGLE BRACKET 6 x 3/4 x 3/4in. 30p
ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75; 6 x 4in. 55p; 12 x 8in. £1.30; 10 x 7in. 95p; 8 x 6in. 90p; 14 x 3in. 72p; 12 x 5in. 90p; 16 x 10in. £2.10; 16 x 6in. £1.30.
ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.
4 x 2 1/2 x 2in. £1.20; 3 x 2 x 1in. £1; 6 x 4 x 2in. £1.90; 8 x 6 x 3in. £3.00; 12 x 5 x 3in. £3.60; 6 x 4 x 3in. £2.20; 10 x 7 x 3in. £3.60.

HIGH VOLTAGE ELECTROLYTICS

20/500V	75p	8+8/500V	£1	32+32/500V	75p
32/350V	45p	8+16/450V	75p	32+32+32/450V	£1.50
32/500V	95p	16+16/350V	75p	16+32+32/500V	£2.50

SINGLE PLAY DECKS. Post £2

Make	Drive	Model	Cartridge	Price
GARRARD	Rim	6200	Ceramic	£22
BSR	Belt	12 Volt	Ceramic	£20
BSR	Belt	P232	Magnetic	£28
BSR	Rim	P207	Ceramic	£20
AUTOCHANGER	BSR		Ceramic	£20
AUTOCHANGER	GARRARD		Ceramic	£24

DECCA TEAK VENEERED PLINTH space for small amplifier Board cut for BSR or Garrard 18 3/4in. x 14 1/4in. x 4in. £5. Post £1

TINTED PLASTIC COVERS for Decks. £5 each, Post £1
17 7/8 x 13 1/2 x 3 1/4in. 18 1/4 x 12 1/2 x 3in. 21 1/2 x 14 1/4 x 2 1/2in. 17 x 12 7/8 x 3 1/2in. 14 7/8 x 13 x 3 1/4 14 1/2 x 13 1/2 x 2 3/4in. 22 5/8 x 13 7/8 x 3in. 16 5/8 x 13 x 4in. 21 x 13 3/8 x 4 1/8in.

RADIO COMPONENT SPECIALISTS

Dept 4, 337, WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 01-684 1665

ACCESS Post 85p Minimum. Callers Welcome. VISA Lists 34p. Same day despatch. Closed Wed.

VERNON TRENT *at Large!*

V.T.'s views and opinions are entirely his own and not necessarily those of PE

I'VE JUST had an idea. It doesn't happen all that often. So when it does I like to tell somebody about it.

I've been thinking that as we become more and more a button-pushing civilisation, our ability to communicate with each other, in the way we have been doing since the dawn of mankind, is going to take a nasty knock.

Here's an extreme instance. If and when we reach the stage where we wish our workmates good morning by punching up the salutation on a keyboard—even though we may be no more than an office apart—then sooner or later there can only be one consequence: total atrophy of the vocal chords. There's a lot in the old saying, if you don't use it you'll lose it.

And think what that could lead to in the years after you and I are laid in earth.

The end of live theatre as we know it. The death of opera. The finish of slanging matches in the House of Commons. The demise of spicy revelations at posh cocktail parties. Wholesale redundancy of bingo callers. No more air-cleaning rows between married couples. No more whispered exchanges of sweet nothings between young lovers. The start of mute TV and the passing of radio. The amputation of vocal links with people of other lands... Try that little lot for starters. Of course, cynics will say that out of such evil there comes much good.

No more screeching prima donnas. The end of pompous party political gas. The boon of being able to get happily stoned at social functions without having to endure a load of inconsequential chitchat. No more having to bear—though Mum might be upset—the twice-weekly yap of Coronation Street. No more having to study impossible foreign languages. Enhanced matrimonial bliss, made possible by the blessing of mutual silence. Goodbye, the saints be praised, to Russel Harty and Michael Parkinson; and a merciful deliverance from all that is worst in imported American TV.

★ ★ ★ ★

There's another aspect worth considering, now that we're diving at an ever-increasing pace into the electronic age. How is the keyboard syndrome going to affect the way we educate our children? What, for example, is to be the fate of the good old three Rs?

If you can bear a moment of near-geriatric nostalgia, let me recall Miss Richardson. She was a grey-haired lady who was totally dedicated to thumping the rudiments of good English into the skulls of her elementary school charges. She had no time for anyone unwilling to share her love of the glories of language and gems of literature. We went

through hell with the old girl. But we emerged with enriched minds.

Then there was old Bandy Andrews. I take off my hat to him as well. He firmly believed that the only worthwhile subjects in the curriculum were simple addition, division, multiplication and subtraction. These were the intellectual vitamins on which he thrived. Anyone who resisted the same diet was beyond the pale.

Finally there was Charlie Atkinson—long since departed for that great big college of calligraphy in the sky. It was he who trained us to express our callow thoughts in splendidly-rounded hands that were a joy to behold. It was his good luck to pass on before the ballpoint pen—which some people feel killed individual style stone dead—came into universal use.

"We must all accept, indeed embrace, progress as our sires did the wheel."

I agree that our education in those days was pretty elementary. But it had soul and substance. It nurtured the development of latent talents and equipped us for the years ahead. Some of us even got places on the strength of it.

★ ★ ★ ★

Leaving aside the emotional ramblings, let's look at things in perspective.

The computer, the microprocessor and all their derivatives, with us and yet to come, cannot fail to play an enormous part in our future lives. Nobody but an idiot would deny that. We must all accept, indeed embrace, progress as our sires did the wheel.

But I can't help feeling that we still need the basic support of established educational practices as a preliminary to hurling ourselves headlong into the fresh technologies. There is no substitute for a grounding in the three Rs. Nothing can replace the human larynx as a channel for human understanding.

Someone is bound to say that writing as I do for an electronics journal I ought to be more aware of which side my wafer is diffused. Point taken. As I said at the beginning, it's just an idea. But I still reckon that Miss Richardson, Bandy Andrews and Charlie Atkinson still have a job to do.

★ ★ ★ ★

We're all TV critics. Whenever we moan from our armchairs we're carrying out the function, even though it's without an audience or a reward.

I'm no exception. The other night I was watching a programme called "I'll Be Alright On The Night". Presented by that brilliant jester, Denis Norden, it purports to be a collection of rejected sequences resulting from cockups by distinguished performers while recording their programmes.

It is passable entertainment and moderately funny. And, I suppose, acceptable to the gullible. But, because I have that kind of mind, I suspect that some of these boops are specifically produced in order to provide a relatively inexpensive spin-off. Alright, such conning is perfectly legitimate if it keeps people happy and laughing.

On the other hand, if these lapses from professional standards, which betray a rather irresponsible approach to the job, are genuine, then ought we not to be just a little concerned?

Television is a voracious consumer of time, talent and, above all, money. Money, by the way, which you and I help to provide by passing our crisp oncers across the Post Office counter every year.

Thinking along those lines, it's not easy to accept as a matter of mirth—perhaps even affectionate sympathy—the banalities which such programmes offer.

Sorry Denis. I'm sure it's not your fault.

★ ★ ★ ★

According to a recent newspaper report, the robots of the future are going to be a lot more cuddly. Apparently 'not tonight darling' will not be a feature of their synthesised vocabulary. Sounds promising.

A spokesman for Cardiff University claims that whispering words of love and affectionate snuggling-up will present no problems for these romantic devices.

Moreover, he promises us, they will be endowed with limitless energy. Sounds even more promising.

But will there be anything in the circuitry to handle that well-known limitation—the headache?

★ ★ ★ ★

In the meantime, it is reported that America has added a new category to census statistics:—Robots.

The first robot count is underway this month and will be aimed at robots on factory assembly lines. The special census form also has a section to collect information about home robots.

A more frightening rumour is the news that special robots are being seriously considered for duties as "personal" and home security guards. These robots are, it is claimed, programmed to deliver varying degrees of bodily harm; from simple electric shocks to "dismemberment".

It appears that the only obstacle is the expected multi-million dollar lawsuits that could be lodged by injured parties.—A case for Robot against Robot?

PRACTICAL ELECTRONICS PRINTED CIRCUIT BOARD SERVICE

Printed circuit boards for certain PE constructional projects are now available from the PE PCB Service, see list. They are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: **PE PCB Service, Practical Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG.** Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title, order code and the quantity. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

NOTE: Please allow 28 days for delivery. We can only supply boards listed here or in the November 1984 issue.

PROJECT TITLE	Order Code	Cost
FEB '81		
Slave Light Dimmer	102-01	£1.88
MAR '81		
27/28MHz Converter	103-01	£1.79
Microphone Mixer	103-02	£1.83
Period Power Tester	103-03	£2.25
APRIL '81		
Speech Processor	104-01	£1.55
Mini Drill	104-02	£1.50
MAY '81		
Digisounder	105-01	£6.65
Thermometer	105-02	£1.49
JUNE '81		
pH Meter	106-01	£2.06
SEPT '81		
Horologium	109-01	£3.16
"	109-02	£3.11
"	109-03	£2.97
Analogue Frequency Meter	109-04	£2.87
Ignition System	109-05	£2.47
	109-06	£2.28
APRIL '82		
Med. Resolution Equaliser (UK 101)	204-01	£1.73
Enlarger Timer	204-02	£4.02
AUG '82		
Automatic Photographer	208-01	£1.94
Home Alarm	208-02	£3.21
SEPT '82		
Waveform Digitiser	209-01	£8.24
FEB '83		
Radio Booster	302-02	£1.80
MAR '83		
Into the Real World	303-01	£3.99
Accessory PSU	303-02	£1.35
4½ Digit Frequency Meter	303-03	£3.69
APRIL '83		
Phaser	304-01	£3.41
JUNE '83		
Program Conditioner	306-01	£2.30
SEPT '83		
Guitar Active Tone Control	309-01	£2.27
Ground Communication System	309-02	£2.13
	309-03	£2.31
DEC '83		
Expanding the Vic 20	312-01	£5.18

PROJECT TITLE	Order Code	Cost
MAR '84		
Spectrum Autosave	403-01	£1.83
APRIL '84		
Microstepper	404-01	£10.74
MAY '84		
Sustain Unit	405-02	£2.82
Audio Signal Generator	405-03	£4.28
"	405-04	£2.51
JUNE '84		
Cross Hatch Generator	406-01	£3.52
JULY '84		
Simple Logic Generator	407-01	£7.73
EPROM Duplicator	407-02	£3.74
Alarm System	407-03	£3.19
Oscilloscope Calibrator	407-04	£4.23
AUG '84		
Comm. 64 RS232C Interface	408-01	£3.02
Field Measurement	408-02	£3.19
"	408-03	£2.76
Digital Dice	408-04	£4.23
Simple Logic Analyser	408-05	£2.93
Alarm System	408-06	£4.24
"	408-07	£3.14
"	408-08	£3.23
SEPT '84		
Parallel to Serial Converter	409-01	£2.92
Through the Mains Controller	409-02	£2.88
"	409-03	£2.71
OCT '84		
Logic Probe	410-01	£1.90
NOV '84		
Computer DFM Adaptor	411-01	£2.76
DEC '84		
Ni-Cad Charger	412-01	£2.40
JAN '85		
Outrider Car Computer (Set of 2 boards)	501-01/2	£9.10
FEB '85		
Modular Audio Power System		
Pt-1: Power Amp Board	502-01	£4.19
Spectrum DAC/ADC Board	502-02	£3.69

PE PRINTED CIRCUIT BOARD SERVICE
Please send me the following p.c.b.s.

	Order Code	Quantity	Price
.....			
.....			
.....			
.....			
I enclose cheque /PO for £			
Name			
Address			
.....			
.....			

★★ NI-CAD BARGAINS ★★

Re-chargeable Nickel-cadmium batteries in stock. Ex-equipment but very little used condition. DEAC 10000K Button Stacks 6 cells — 7.2V. Size 2 1/4 x 2" diam. Capacity 1AH. £3 inc. VAT (p&p 25p). DEAC 60000KZ Button stacks 3 cells — 3.6V. Size 1 1/4 x 1 1/4" diam. Capacity 6AH. £1.50 inc. (p&p 20p). Also available — PCB's from which these batteries have been removed containing Transformer, Diode rectifiers, smoothing capacitors, DPDT Relay, fuses etc. ONLY £1.50 each inc. VAT (p&p 75p). Complete board & batteries £5 (p&p £1).



★★ STEPPER MOTORS ★★

Brand new stock of 'ASTROSYN' Type 20PM-A055 stepper motors. 28V DC. 24 steps per rev. 15 oz-in torque @ 100PPS. Body length 2 1/2", diameter 2", shaft 1/4" diam x 4 1/4" spirally threaded. Weight 16oz. Price each £11.50 (p&p 50p). Connections supplied. INC. VAT.

★★ STEPPER MOTORS ★★

In stock — used, but excellent condition, 4-phase steppers. 50 steps/rev motor with (removable) gearbox giving a 300:1 reduction. 6V DC operated. Complete with a driver board requiring just a single 6V rail and pulse input. Motor measures 1" x 2" diameter, gearbox 3/4" x 2 1/4" output shaft. PCB's from which these batteries have been removed containing Transformer, Diode rectifiers, smoothing capacitors, DPDT Relay, fuses etc. All for just £8 inc. VAT (p&p 50p).



OPTICAL ISOLATORS

SPERRY UNIVAC M4000 opto-isolator units providing 2KV of insulation between Modems and Terminals. 25 way 'D' connectors (RS232C Interface) in and out. Measures 9x5x7". Complete with handbook. £16.50 inc VAT & p&p.

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam). Counting up to 15 each inc VAT & p&p. Brand new with mounting instructions. Only £2.50

★★ CROSS-HATCH GENERATORS ★★


LARGEAR COLOURMATCH CM500MPG. UHF television pattern generators giving cross-hatch, dot and grey scale patterns. Fully tested and guaranteed. NOW JUST £27.50 inc VAT & p&p.

LARGEAR COLOURMATCH CM6010RG Gated Rainbow colour pattern generators. Cross-hatch/dot & gated rainbow (RGB) colour bar patterns. £65 inc

UNAOHM E0684 PAL Colour-bar & pattern gen. £275 +

KORTING 82512 PAL/NTSC Colour & pattern gen. £275 +

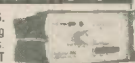Mail Order customers please add £2.50 postage each item.



RALFE ELECTRONICS

10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753




'OSCILLOSCOPES'

HEWLETT-PACKARD 141A Storage Oscilloscope. HEWLETT-PACKARD 1707A dual trace 75MHz £750. TEKTRONIX 454A dual trace 150MHz sweep delay £950. TEKTRONIX 453 dual trace 50MHz sweep delay £900. TELEQUIPMENT D75 dual trace 50MHz sweep delay £450. SONY/TEKTRONIX 335 dual trace 35MHz portable. TEKTRONIX 7704 frame and plug-in units. GOULD OS1000B dual-trace 20MHz.

All these units are sold in full operational condition and calibrated to spec. All prices are subject to additional VAT & carriage (Securicor) + £10

★★ TEST EQUIPMENT ★★

MARCONI TF1313A 0.1% Universal Bridge. WAYNE KERR 9221 Universal Bridge. SULLIVAN R4000 Inductance Bridge. MARCONI TF2604 Electronic Multi-Meter. MARCONI TF2502 RF Power Meters DC-1GHz. 10w fsd £350. UNADHM E0684 PAL Colour-bar and Pattern Generator £275. KORTING 82512 PAL/NTSC Colour Pattern Generator £275. ROHDE & SCHWARZ 5DR AM Signal Generator 0.3-15Hz. DATRON MODEL 1051 Digital Voltmeter. ROHDE & SCHWARZ Resonance Frequency Meter 470MHz-2.5GHz. ROHDE & SCHWARZ Polyscop SW08 II. BRUEL & KJAER Heterodyne Voltmeter 0.5-240MHz. AIRMED Display Oscilloscope 273, 4-trace, 14x10" CRT. £195. RIKADENKI 3-channel Chart Recorder. Model B-341.

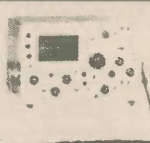

453 £500
454 £350

★★ 125W MAINS INVERTERS ★★

12V DC Battery Input to 230V AC. Output @ 125 watts crystal-controlled 50Hz time-base oscillator, fully enclosed in blue-steel cases with integral 13A socket. Dimensions approx. 4 x 6 x 10". BRAND NEW. £65 + VAT (p&p £2).

★★ MAINS STABILISERS ★★

Small quantity available of brand-new Gould ECVN250A constant voltage transformers. 190-260V AC input to 240V AC output @ 250 watts. £45 each + VAT (p&p £3).

★★ SWEEPERS ★★

TELEONIC 2003 System. 800-1500MHz £325. TELEONIC SM2000 with 500-900MHz plug-in £175. KNIGHT KG-687 3-220MHz £150.

PLEASE NOTE: All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months' guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES. EQUIPMENT WANTED!

★★ TEKTRONIX ★★

FILE MANAGER SYSTEM MODEL 4907 Option 31 (Third disc drive). 4051 Graphic System compatible. GPIB (IEEE 488-1975) compatible.

★★ STEPPER MOTORS ★★

Brand new stock of 'ASTROSYN' Type 20PM-A055 stepper motors. 28V DC. 24 steps per rev. 15 oz-in torque @ 100PPS. Body length 2 1/2", diameter 2", shaft 1/4" diam x 4 1/4" spirally threaded. Weight 16oz. Price each £11.50 (p&p 50p). Connections supplied. INC. VAT.

★★ COMPUTER PERIPHERALS ★★

1.6MB 8" FLOPPY DISC DRIVES - New Stock

After our recent sell-out of the DRE7100 FDD's, we are pleased to offer another bargain package as follows. BRAND NEW American 'MFE Corp' model M-700 DOUBLE SIDED 8" Disc Drives. Massive storage capability up to 1.6MBytes. Full IBM compatibility. External power requirements are ±5V at 1.2A and +24V at 1.1A. Full spares/back-up available U.K. (Elcomatic's). Current list is over £315.

★★ NOW LOWEST PRICE EVER £160 - INCLUDING MANUAL INC CARRIAGE & INC VAT ★★

★★ 19M BYTES WINCHESTER ★★

Now available again, UNITED PERIPHERALS 3100 Minidisc Drives (3x8" sealed patterns) capable of over 19MB. Sold in un-tested, un-guaranteed condition for just £125 inc VAT, carriage and copy of handbook.

★★ MULTI-RAIL LINEAR PSU's ★★

Recent stock of brand new COUTANT ESM-Series Power Supplies at surplus prices. Model ESM15.2 giving regulated, stabilised DC outputs 5V @ 1.5A and ±12V to ±15V @ 1.5A each and an un-stabilised 24V @ 2A. 240V AC input. Measures 5x8x11". Fully enclosed. In original cartons with handbooks. £45 each + VAT (p&p £2).

★★ SWITCH-MODE POWER SUPPLIES ★★

Fully tested and guaranteed PSU's now at LOWEST EVER PRICES. Manufactured by FARNELL, GOULD/ADVANCE.

5V @ 10 amps	£18	12V 16A (110V in)	£20
5V @ 20 amps	£20	5V @ 60 amps	£35
19V @ 15 amps	£35	12V @ 15 amps	£40

All prices now include VAT, packing and posting.

★★ CENTRIFUGAL BLOWERS ★★

'TORIN' Type U62B1. 230V Cap 'Start' (supplied), very powerful (200W, 3000 rpm) centrifugal fans for large rack cooling or enclosure extraction applications. Overall dimensions 20x12 cms, outlet 6x4 cms. BRAND NEW. Surplus stock. £15 each inc. VAT, p&p £1.50.

★★ INSTRUMENT COOLING FANS ★★


Recent stock of BRAND NEW 5 bladed axial cooling fans measuring 3 1/2 x 3 1/2 x 1" (stimline fans).

230V AC 10 watts	£7.50 + VAT
115V AC 13 watts	£6.50 + VAT

★ NB: These fans are under 1/2 RS price. Postage each 50p
★ Quantity discounts available for 10+

MASTER Electronics - Microprocessors - Now! The PRACTICAL Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic & computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagrams.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.

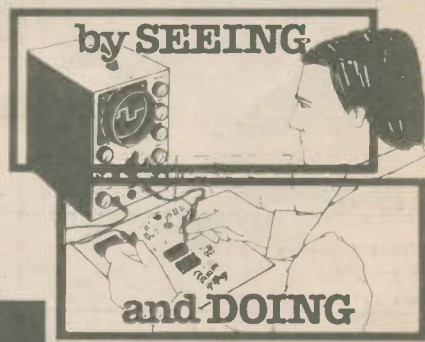

New Job? New Career? New Hobby?

Please send your brochure without any obligation to — I am interested in:

NAME _____
ADDRESS _____

- ELECTRONICS. B.N.R.E.S. PE2.
 MICROPROCESSORS
 RADIO AMATEUR LICENCE
 CITY & GUILDS EXAMS

Other Subjects _____

BLOCK CAPS PLEASE



OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)

British National Radio & Electronics School Reading, Berks. RG1 1BR



When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

RECEIVERS AND COMPONENTS

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. FORRESTERS (NATIONAL RADIO SUPPLIES), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

TURN YOUR SURPLUS capacitors, transistors, etc into cash. Contact COLES HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 584188. Immediate settlement.

RESISTORS 1,000 MIXED 1/4w, 1/2w, 1w, 2%, 5%, 10%, C. Film £3.45 inc P&P D. J. HOOKER, Romney Marsh Electronics, Pennywood, Clark Road, Greatstone, Romney Marsh, Kent TN28 8PB.

BELLS TELEVISION SERVICES for service sheets of Radio, TV, etc £1.50 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Banks Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 Mfds — 5p.
22 & 47—6p, 100—7p, (50V—8p), 220—8p, (50V—10p), 470—11p, (40V—10p), 1000/15V—15p, 1000/25V—25p, 1000/40V—35p, 4700/25V—70p.

Subminiature bead Tantulum electrolytics.
0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 63V — 14p.
2.2/35V, 4.7/25V—15p, 10/25V, 15/16V—20p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V—32p.
15/25V, 22/25V, 47/10V—35p, 47/16V—80p.

Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf.—3p, 56 pf. to 330 pf.—4p, 10% 390 pf. to 4700 pf.—5p.

Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.

Polystyrene E12 Series 63V. Horizontal Mtg.
10 pf. to 820 pf.—3p, 1000 pf. to 10,000 pf.—4p.

Miniature Polyester 250V Vert. Mtg. E6 Series
01 to 068—4p, 1—5p, 15, 22—6p, 33, 47—10p, 68 — 12p, 1.0 — 15p, 1.5 — 22p, 2.2 — 24p.

Mylar (Polyester) Film 100V. Vertical Mounting.
001, 0022, 0047—3p, 01, 022—4p, 04, 05, 0.1—5p.

High Stability Miniature Film Resistors 5%.
1W E24 Series 0.51R—10MΩ — 1p.
1W E12 Series 1R0 to 10MΩ — 1p.
1W E12 Series 10R to 10MΩ — 5p.
1W metal film E12 Series 10R-1MΩ, 5% — 2p, 1% E24 — 3p.
1N4148—2p, 1N4002—4p, 1N4006—6p, 1N4007—7p.
BC107/8/9—12p, BC147/8/9, BC157/8/9, BF195 & 7—10p.
8 Pin i.c.'s 741 Op. amp—18p, 555 Timer—24p.
Dil. Holders 8 pin—9p, 14 pin—12p, 16 pin—14p.
LED's 3 & 5mm. Red—10p, Green & Yellow—14p.
Grommets for 3mm—11p, Grommets for 5mm—2p.
20mm. Q.B. Fuses 15, 25, 5, 1, 2, 3 & 5A—5p.
20mm. Anti Surge 100mA to 50A—8p.
20mm. Fuseholders P.C. or Chassis Mtg—8p.
Battery Snaps (pairs) PP3—6p, PP9—12p.
400mW Zener diodes E24 series 2V7 to 33V—8p.
Prices VAT inclusive Post 20p. (Free over £5.00).

THE C.R. SUPPLY CO.
127, Chesterfield Rd., Sheffield S8 0RN.

HOME SECURITY CONT.

WHO CAN PUT A PRICE ON A PEACE OF MIND

PROFESSIONAL EQUIPMENT AT LOW! LOW! PRICES.
HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES

ADVANCED SECURITY PRODUCTS LTD
2 Ealing Road, Aintree,
Liverpool L9 0HU, Merseyside.

Tel: 051-525 3440

FREE CATALOGUE PHONE OR S.A.E.

HOME SECURITY

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
 - HIGHEST QUALITY EQUIPMENT
 - FREE DIY DESIGN GUIDE
 - FULLY ILLUSTRATED
 - MICROCHIP CIRCUITRY
 - QUICK DESPATCH SERVICE
 - FULL INSTRUCTIONS
- SEND SAE OR PHONE

C-TEC SECURITY, Dept PE
60 Market St, Wigan WN1 1HX.
Telephone (0942) 42444



CENTURION ALARMS

Manufacturers of Professional Alarm Equipment for DIY & the TRADE. Send now for our New 16-page Brochure. Full of Information & the Lowest prices.



Tel: (0484)

21000
or 35527 24 ht

CENTURION Dept PE
93 Wakefield Road,
Huddersfield.
HD5 9AB
W. Yorks.

® CENTURION is a Registered Trademark of Centurion Alarms

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for.....
insertions. I enclose Cheque/P.O. for £.....
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)

NAME

ADDRESS

PRACTICAL ELECTRONICS

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846

Rate:
36p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

EDUCATIONAL/TUITION

IMPROVE YOUR PROSPECTS

with skills that employers want – learn the easy way with modern home study courses from Ideal Schools.

MODERN ELECTRONICS

Train for success in the fastest ever growing industrial sector.

COMPUTER PROGRAMMING

The demand for Programmers is increasing constantly – don't miss out! For free booklet write today to



IDEAL SCHOOLS
(Ref. PE2)
60 St Enoch Sq
Glasgow G1 UK.
Tel: 041-248 5200

COURSES

FULL-TIME TRAINING COURSES

15 MONTHS
B-TEC NATIONAL CERTIFICATE
in TELEVISION & VIDEO SERVICING

15 MONTHS
B-TEC NATIONAL CERTIFICATE
in COMPUTING TECHNOLOGY

9 MONTHS
B-TEC HIGHER CERT (HNC) in
COMPUTING TECHNOLOGY & ROBOTICS

- PRINCIPLES OF ELECTRONICS
- TELEVISION (MONO/COLOUR)
- VIDEO CASSETTE RECORDERS & CCTV
- COMPUTERS & MICROPROCESSORS
- INDUSTRIAL ROBOTICS

Short courses (from 6 weeks)
with previous electronics
knowledge.

Courses commence
Jan '85, April '85, September '85.

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept: AA, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721.

SERVICES

INVENTORS
Think of something new?
Write it down! –

American industry offers potential royalties for your innovations and new products. We offer free confidential disclosure registration and initial consultation in London regarding your idea's potential value. Write without delay for your free information package.

American Inventors Corporation
82, Broad Street, Dept PT
Westfield, Massachusetts 01086
United States of America.

A fee based marketing company.

BOOKS AND PUBLICATIONS

FULL SIZE, top quality service sheets £2.50 + I.s.a.e. CTV/Music Centres £3.50 + I.s.a.e. Repair data almost any named TV-Video £10.50 inc. circuits. I.s.a.e. brings any quote free magazine/price lists. TISPE, 76 Churches, Larkhall, Lanarkshire. 0698 883334.

FOR SALE

P.E. BACK NUMBERS May '76 to February '82. Offers: Tadley 3743.

PRACTICAL ELECTRONICS MAGAZINES. Believed to be complete set. From issue one. Offers: 01-642 4029.

OSCILLOSCOPES: Tektronix 516 (dual) £140, RM17 £65, Dumont 50MHz dual £140-£260. Try-out welcome. Insured delivery + £7. PDP11/05 system £370. Teletypes £40. SINCLARE 01-316 1779.

SPECIAL OFFERS. SE250C signal injector £2.20. 15 watt amplifier board £7.65. Antex C/siron £5.95 P&P 40p. Thousands of components in stock. Phone or write for price list. SPECTRUM RADIO & ELECTRONICS LTD, 36 Slater Street, Liverpool L1 4BX. 051-709 4628.

MISCELLANEOUS

ADAPTORS – Power supplies for calculators, TV games, computers etc. Send for details. RTE ELECTRONICS, Britania Mill, Rossendale, Lancs. BB4 8BA.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showroom, opposite Odsal Stadium.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC. Faced steel. Vast range, competitive prices start at a low £1.50. Punching facilities at very competitive prices. BAZELLI, (Dept. 23), St. Wilfreds, Foundry Lane, Halton, Lancaster LA2 6LT.

THE SCIENTIFIC WIRE COMPANY				
811 Forest Road, London E17. Telephone 01-531 1568				
ENAMELLED COPPER WIRE				
SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	9.09	5.20	2.93	1.97
TINNED COPPER WIRE				
14 to 30	3.97	2.41	1.39	0.94
Fluxcore				
Solder	5.90	3.25	1.82	0.94

Prices include P&P VAT. Orders under £2 add 20p.
SAE for list of copper and resistance wire.
Dealer enquiries welcome.

COMPUTER LEADS, made to order. Please send S.A.E. with requirements to: S & A LEADS, 94 Ladies Grove, St Albans AL3 5UB

ELECTRONIC ORGAN KEYBOARDS and other parts being cleared out as special offer. ELVINS ELECTRONIC MUSICAL INSTRUMENTS, 40a Dalston Lane, London E8. Tel 01-986 8455.

CLEARING LABORATORY, scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders etc. Tel. 0403-76236.

HEATHKIT. U.K. spares and service centre. CEDAR ELECTRONICS, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. (0684) 73127.

CABINET FITTINGS

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers.

ADAM HALL SUPPLIES LTD.

Send
30p cheque/
P.O. for illustrated
catalogue: Adam Hall (PE Supplies),
Unit G, Carlton Court, Grainger Road,
Southend-on-Sea.

Leader of the Packs

AC/DC COMPONENT PACKS

Pack No.	Qty	Description	Price
TF 11	12	RED 5mm LED	£1.00
TF 12	30	500mz ZENERS 5%	£1.00
TF 15	50	1 amp Rect. Diodes in 4000 series	£1.00
TF 16	6	1 amp Bridge Rect.	£1.00
TF 17	100	Transistor pads	£1.00
TF 18	20	A/S Fuses 20mm	£1.00
TF 19	10	3A Rect. Diodes	£1.00
TF 110	2	ORP 12	£1.00
TF 111	5	BR 100 DIAC	£1.00
TF 112	10	BC109B	£1.00
TF 113	10	LC's all different	£1.00
TF 114	50	BFR 86	£1.00
TF 115	12	8 pin DIL sockets	£1.00
TF 116	20	10mm Horiz. Pre set (10 values)	£1.00
TF 117	10	Slide Pots – 3K all the same	£1.00
TF 118	10	Mixed Pots	£1.00
TF 119	10	Feed throughs	£1.00
TF 120	25	Electrolytic Caps	£1.00
TF 121	50	Polyester Caps	£1.00
TF 122	100	Mixed Resistors – incl. Wire Wound	£1.00
TF 123	100	Mixed Transistor Hardware	£1.00
TF 124	25	5mm LED clips and rings	£1.00
TF 125	10	BC 107	£1.00
TF 126	10	BC 108	£1.00
TF 127	6	Green 5mm LED	£1.00
TF 128	6	Yellow 5mm LED	£1.00
TF 129	150	Mixed nuts/bolts/washers/self tapper	£1.00
TF 130	25	Mixed Electrolytics Axial	£1.00
TF 131	25	Mixed Electrolytics Radial	£1.00
TF 132	50	Mixed Polyester Axial	£1.00
TF 133	50	Mixed Polyester Radial	£1.00
TF 134	15	BC 337	£1.00
TF 135	20	500MA A/S 20mm Fuse	£1.00
TF 136	50	Mixed Ceramic Discs	£1.00
TF 137	50	Mixed Ceramic Plates	£1.00
TF 21	200	47 pf 160V Polystorite Cap	£2.00
TF 22	10	LM 3900 N	£2.00
TF 23	10	Mixed DTL	£2.00
TF 24	5	4700 mf 25V Tag Elect 2" x 1"	£2.00
TF 25	10	1000 mf 63V Ax Elect	£2.00
TF 26	50	.022 mf 400V RAD POLY	£2.00
TF 27	10	100 mf 250V Ax	£2.00
TF 28	10	2.2 mf 160V Polyester RAD	£2.00
TF 29	10	VDR's	£2.00
TF 210	10	Mixed TTL (74 series)	£2.00
TF 211	4	2N 3055 H(RCA)	£2.00
TF 213	200	IN 4151 Diodes	£2.00
TF 214	200	IN 4148 Diodes	£2.00
TF 51	100	White/Red 5mm LED	£5.00
TF 52	50	BC 108C	£5.00
TF 54	1/2KG	Reel 22g ersin multicore	£5.00
TF 55	10	2N3055 H(RCA)	£5.00
TF 56	5	OCP71	£5.00
TF 57	3	10,000 mf 40V Comp. grade elect	£5.00
TF 58	720	1/4W Carbon film 1w-10Mw ten values	£5.00
TF 59	25	1,000 mf 25V Axial	£5.00
TF 510	25	1,000 mf 25V Radial	£5.00

ALL PRICES INCLUDE VAT – ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.
TERMS: Cash with order. POST & PACKING: Please add 75p to total order.

AC/DC ELECTRONICS COMPONENTS
DEPT P.E., 45 CHURCH STREET,
ENFIELD, MIDDLESEX.

LOOK - IT'S HIS NEW YEAR SPECIAL!

TREAT YOURSELF THIS NEW YEAR



We are the main stockists for 'BEARPARTS', the new name in electrical, electronic and audio components.

Interested? Send S.A.E. and receive your

FREE

'BEARPARTS' sample pack.

BEARPARTS

CONTENTS OF PACK:

BC 612 Transistor, Red LED, 1N4004 Diode, T1 646 Diode, 560pf 200v Capacitor, 10k, 150k Resistors, 2k Multiturn Potentiometer, 48A Crimp Eyelet, Rubber Grommet, Instrument Wire, Sleeving.

COMPLETE SOLDERING KIT

(For the Hobbyist/Electronics Engineer)


FOR LESS THAN £10!!

Comprises of:-

- Antex Miniature 15W 240v AC Soldering Iron
- Antex Iron Stand c/w Sponge
- Desolder Pump
- 2 mtr Solder
- Desolder Braid
- 13A Plug



Iron Stand c/w Sponge

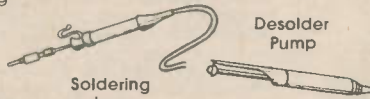

Soldering Iron

Desolder Pump

ONLY £9.85
Please add 80p P & P + 15% VAT

LIMITED OFFER WHILE STOCKS LAST!

Call in and see our new counter now open. 9.00 - 5.00 Mon-Fri & 9.00 - 12.00 Sat. Too far to call? Don't worry, export/mail order is our speciality. Why not write and find out more.



24 hr answerphone for credit card orders
Tel: 0244 536699



SYSTEMS ELECTRONIQUE

(U.K.) LTD.

26 Engineer Park, Sandycroft, Deeside, Clwyd CH5 2QD.
Tel: (0244) 536700.

CLEF ELECTRONIC THE CLEF CMS



The FULLY programmable digital synthesiser that you can AFFORD

THE NEW CLEF COMPUTER MUSIC SYSTEM is so user programmable that you need a BBC Micro to run it! 32 harmonically programmable oscillators. 32 programmable envelopes. 5 octave touch sensitive keyboard, up to 4 OSC/ENVS per note. Real time sequencing. Massive potential for future software. Complete system (without BBC Micro) £495 built. Phone or write for details. Modular systems also available.

MUSIC MASTER RHYTHM PROGRAMMABLE DRUMS



As Published in P.E.

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.

COMPLETE KIT £79

STRING ENSEMBLE ROTOR-CHORUS MICROSYNTH P.C.B. & ELECT KITS £86.90

PERCUSSION SYNTH P.C.B. & ELECT KITS £97.90

88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation on Piano Key Inertia.

COMPONENT KITS

including Keyboard

88 NOTE £266

72 NOTE £234

The above may also be purchased in four parts.

SQUARE FRONT KEYBOARDS

88 NOTE £60

49 NOTE £29

73 NOTE £50

30 NOTE £19

KEYSWITCH ITEMS ALSO AVAILABLE



ALL PRICES INC. VAT. CARR & TELEPHONE ADVICE. S.A.E. for full Specs & MANF. PRICES. VISA-ACCESS-AMERICAN EXPRESS. Competitive quotes can be given for export. Allow 3-14 days for normal despatch.

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept P.E.) 44A BRAMHALL LANE SOUTH BRAMHALL STOCKPORT CHESHIRE SK7 1AH TEL 061-439 3297

BAND-BOX PROGRAMMABLE BACKING TRIO



As Published in P.E.

THREE PIECE BACKING BAND Generates the sounds of three instrumentalists to back Soloists DRUMS + BASS + KEYBOARDS Over 3,000 chord changes (60 scores) on 132 different chords - 16 chord sounds. Master Rhythm also required.

FULL KIT £265 BUILT £370

OVERSEAS ORDERS

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only.

Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

INDEX TO ADVERTISERS


AC/DC Electronics.....	71	ICS Intertext	63
Adam Hall Supplies Ltd	71	Ideal Schools	71
A.D.E.	70	ILP Electronics	4
Alcon Instruments	64	London Electronic College	71
American Inventors ..	71		
Bensham Recordings	72	Mapplin Supplies.....	58,
Bi Pak	54	Cover IV	
B.N.R.S.	69	Marco Trading.....	46
Centurian Alarms	70		
Circuit Holdings	5	Phonosonics	63
Clef Products	72	Powertran .. Cover II,	64
Computonics	70	Ralfe Electronics	69
C.R. Supply Co.	70	R.C.S.	66
Cybernetic Applications	53	Riscomp.....	53
Electrovalue	58	Scientific Wire Co.	71
G.C.H.Q.	20	Service Trading.....	46
Grandata	53	Skybridge	20
Greenwell	58	Swanley	63
		Systems Electronique	72
Henry's Electronics.....	20	Tandy	19
Hewlett Packard	45	T.K. Electronics	6
Hi-Tech Components	26-27	Watford Electronics..	2-3

P.E. HYPERCHASER

4 CHANNEL PSEUDO INTELLIGENT LIGHT UNIT

- ★ 16 Programmes
- ★ Manual/Auto Programme
- ★ Individual Dimming
- ★ Manual Flash Buttons
- ★ Strobe Outputs
- ★ Sound To Light

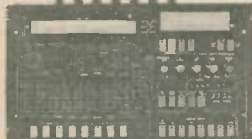Not just a light unit but a sophisticated & comprehensive effects unit. A full kit of parts including P.C.B., Facia, Case, etc. Reprint of article on request. PRICE INCLUDING P&P **£84.95**



P.E. STAR DESK

- ★ 8 Channel Twin Preset Mixer
- ★ 4 Independent Channels
- ★ 8 Programmes
- ★ 1KW Output/Channel (can be boosted to 2KW/Ch)
- ★ Timed Crossfade
- ★ Strobe Outputs
- ★ 4/8 Channel Sequences
- ★ Manual Flash Buttons
- ★ Soft/Hard Sequence

A truly magnificent unit ideal for clubs, groups, drama, etc. A full kit of parts inc. PCB, Facia, Case, etc. Reprint of article on request. PRICE INCLUDING P&P **£209**

BENSHAM RECORDING LTD

327 Whitehorse Road, Croydon, Surrey CR0 2HS
9 am-5 pm. Mon-Sat.
Please allow 14 days for delivery





From a gentle purr to a mighty roar, the tightly controlled power of the beast is yours to command!

PROFESSIONAL QUALITY HIGH POWER LOUDSPEAKERS

A new range of superb quality loudspeakers.

- ★ Virtually indestructible high temperature voice-coil reinforced with glass-fibre
- ★ 100% heat overload tolerance
- ★ Advanced technology magnet system
- ★ Rigid cast alloy chassis
- ★ Linen or Plastiflex elastomer surrounds
- ★ 5-year guarantee (in addition to statutory rights)




Available in 5, 8, 10, 12, 15 and 18 inch models with 8Ω and some 16Ω impedances and with input powers ranging from 50W to 300W e.g.

- 5in. 50W 95dB 8Ω: XG39N / 16Ω: XG40T £17.95\$
- 8in. 100W 98dB 8Ω: XG43W £29.95\$
- 10in. 100W 100dB 8Ω: XG46A £29.95\$
- 12in. 100W 101dB 8Ω: XG49D £29.95\$
- 12in. Twin Cone 100W 100dB 8Ω: XG50E / 16Ω: XG51F £31.95\$

Note - the output power doubles for each 3dB increase (ref 1W @ 1m).

PRECISION GOLD MULTIMETERS

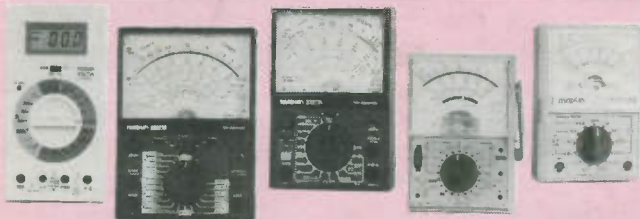

A new range of very high quality multimeters offering truly amazing quality at the price.

- Pocket Multimeter, 16 ranges, 2000Ω/V DC/AC £6.95\$ (YJ06G)
- M-102BZ with Continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95\$ (YJ07H)
- M-2020S with Transistor, Diode & LED tester and 10A DC range, 27 ranges, 20,000Ω/V DC £19.95\$ (YJ08J)
- M-5050E Electronic Multimeter with very high impedance, FET input, 53 ranges including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95\$ (YJ09K)
- M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated PCB for long-term reliability and consistent high accuracy (0.25% + 1 digit DCV) £42.50\$ (YJ10L)

N.B. All our prices include VAT and Carriage. A 50p handling charge must be added if your total order is less than £5 on mail order (except catalogue).

MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
 - LONDON 159-161 King Street, Hammersmith, W6. Tel: 01-748 0926.
 - MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
 - SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 25831.
 - SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Tel: 0702-554000
- Shops closed all day Monday.

§ Indicates that a lower price is available in our shops.

All new in the 1985 Catalogue



Our huge range of top quality electronic components at very competitive prices are all detailed in our catalogue, and with well over 600 new lines in our 1985 edition and many design improvements, it's well worth getting a copy. Here are just a few examples from the catalogue. (The items below are NOT kits).

- ★ Most phono and jack plugs now with integral strain relief sleeve - gold-plated types also available from 14p (gold from 70p)
- ★ Stereo Disco Mixer with cross-fade, talk-over, cue monitoring, aux input, slide controls. Only £58.95 (AF99H)




- ★ 10-Channel Stereo Graphic Equalisers - 3 models - basic; with peak level meter; and with spectrum analyser - from £77.95



- ★ Digital Delay Line permits Slap-back, Doubling, Flanging, Chorus and Echo. 11 controls. Only £195.00 (AF98G)
- ★ Video Enhancer improves picture quality when recording from one VTR to another, and with TV's with monitor input. Only 28.95 (XG59P)
- ★ Detailed descriptions of the exciting new 74HC range of IC's which combine the advantages of CMOS and TTL. From 46p
- ★ Keyboards: sloping keys, two-tone grey, mounted in steel frame, very smart cases (extra) available. 61 keys, only £33.95 (YJ12N) 79 keys, only £37.95 (YJ13P)
- ★ 1% Resistors now 50ppm/°C, 0.4W, only 2p each!
- ★ Auto transformers 120/240V 50VA, £10.75\$ (YJ56L). 100VA £14.95\$ (YJ57M). 150VA £16.95\$ (YJ58N). 250VA £21.95\$ (YJ59P).
- ★ Digital Clinical Thermometer. Only £13.95 (FK51F)



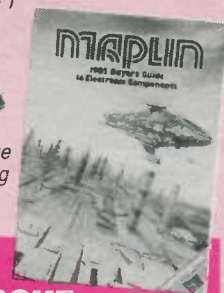Check our 1985 Catalogue for all our other fascinating new lines.



☎ Phone before 2pm for same day despatch.

1985 CATALOGUE

Pick up a copy now at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).

Post this coupon now for your copy of the 1985 catalogue. Price £1.35 + 40p post and packing. If you live outside the U.K. send £2.40 or 11 International Reply Coupons. I enclose £1.75.

Name

Address

Featured in
Electronics &
Music Maker

TAKE COMPLETE CONTROL OF YOUR MUSIC with the

MCS-1

professional quality MIDI-controlled sampling unit

Once again, Powertran and E&MM combine to bring you versatility and top quality from a product out of the realms of fantasy and within the reach of the active musician.

The MCS-1 will take *any* sound, store it and play it back from a keyboard (either MIDI or Iv/octave). Pitch bend or vibrato can be added and infinite sustain is possible thanks to a sophisticated, looping system.

All the usual delay line features (Vibrato, Phasing, Flanging, ADT, Echo) are available with delays of up to 32 secs. A special interface enables sampled sounds to be stored digitally on a floppy disc via a BBC microcomputer.

The MCS-1 gives you many of the effects created by top professional units such as the Fairlight or Emulator. But the MCS-1 doesn't come with a 5-figure price tag. And, if you're prepared to invest your time, it's almost cheap!

Specification

- Memory Size: Variable from 8 bytes to 64K bytes.
- Storage time at 32 KHz sampling rate: 2 seconds.
- Storage time at 8 KHz sampling rate: 8 seconds.
- Longest replay time (for special effects): 32 seconds.
- Converters, ADC & DAC: 8 bit companding. Dynamic range: 72 dB.
- Audio Bandwidth: Variable from 12 KHz to 300 Hz.
- Internal 4 pole tracking filters for anti-aliasing and recovery.
- Programmable wide range sinewave sweep generator.
- MIDI control range: 5 octaves.
- +1 $\frac{1}{2}$ /octave control range: 2 octaves with optional transpose of a further 5 octaves.

Digital Delay Line



Introduced in 1982, Powertran's DDL has brought digital quality effects to thousands of musicians. Still available in kit form at only £179.00 + VAT.

KIT
£499
+ VAT

BUILT
£699
+ VAT



Write or phone now to place an order.
Powertran Cybernetics Limited,
Portway Industrial Estate,
Andover, Hants, SP10 3PE.
Telephone: 0264 64455



POWERTRAN cybernetics Ltd