


JULY 1992

£1.95

TELEVISION

SERVICING · VIDEO · SATELLITE · DEVELOPMENTS

FREE 32-PAGE CATALOGUE

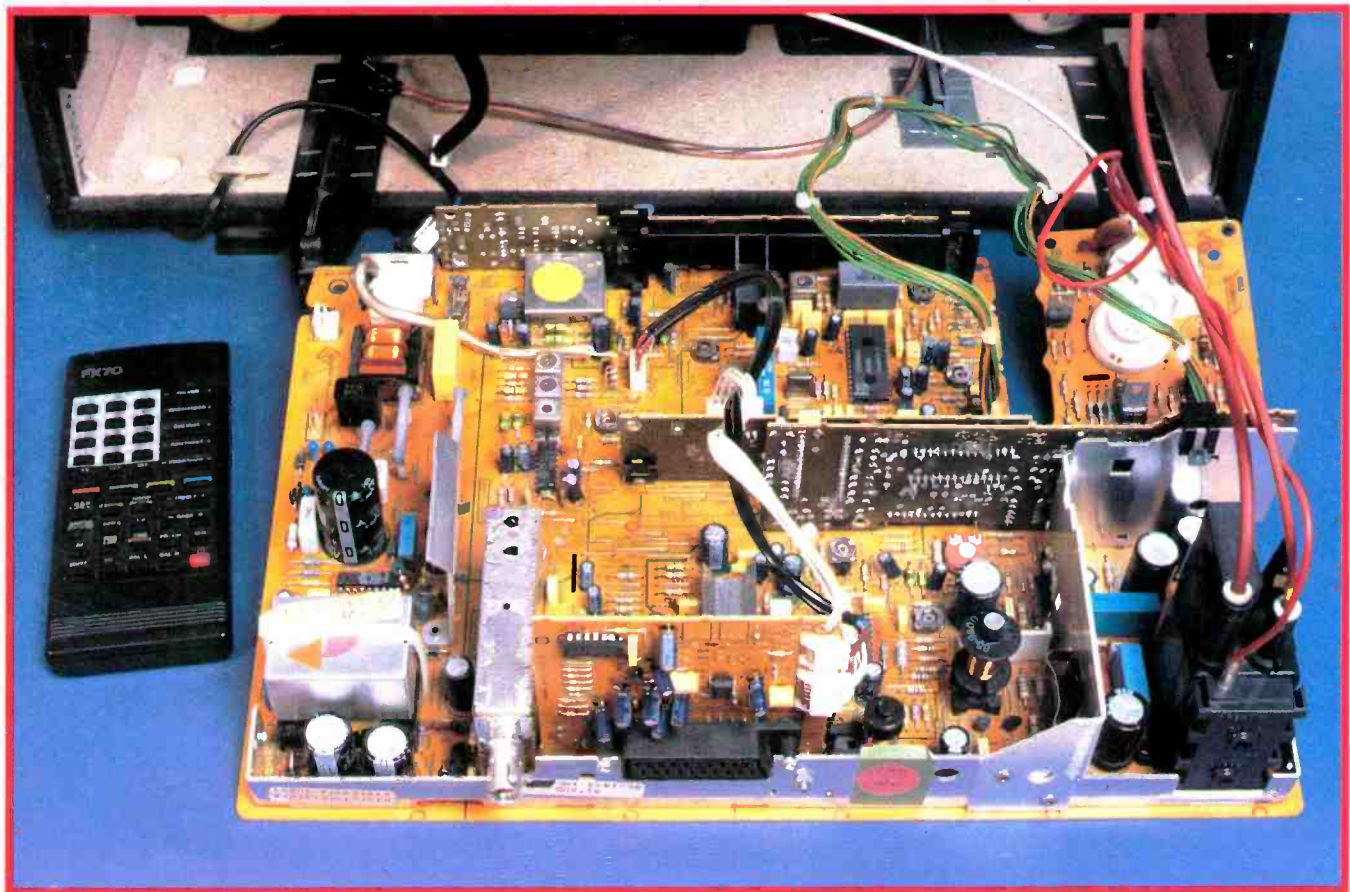


**Servicing the Tatung 160 Chassis
Scart Switching Unit • DX-TV
Channel 5 Reception Problems
Satellite Notebook • CD Casebook
VCR Clinic • TV Fault Finding**

We would like to point out that we say no

**This means
that no
matter
what
spare you
need we've got
it!**

**Our aim is to offer
you the customer
the widest range of
spares, service
aids and
equipment to
enable you to keep
abreast with
today's demanding
technology.**

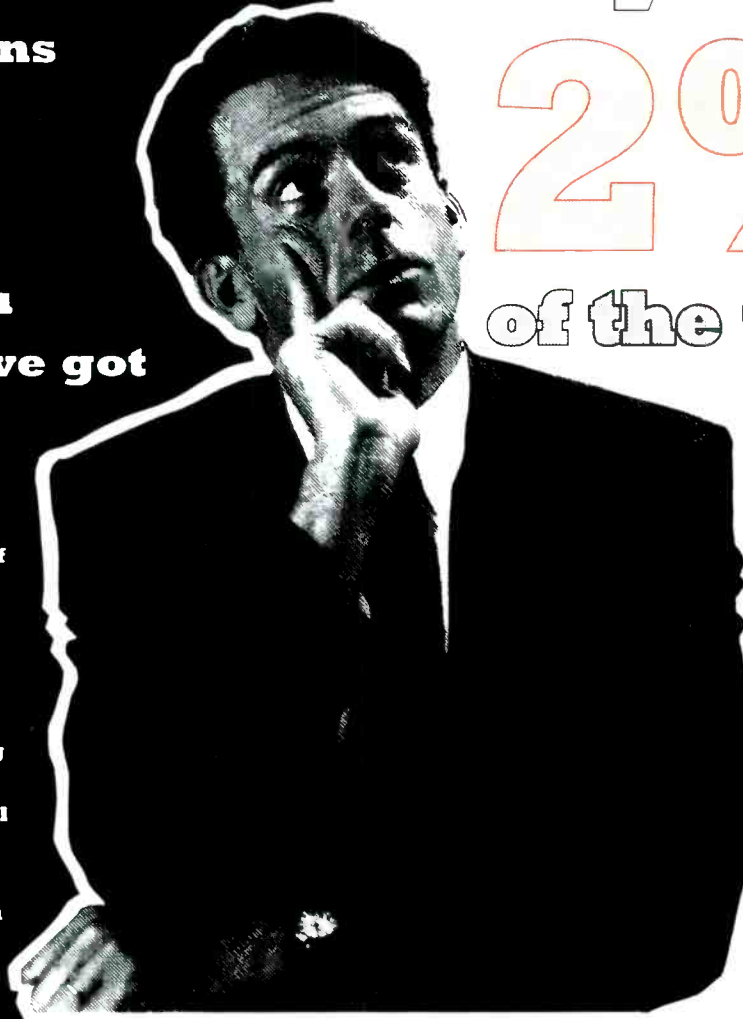**No order is to small
phone us now and
order your spares.
And remember you
don't have to use
part numbers, so
its even easier to
get what you need.**



20%
of the time.

SHARP

PHILIPS

FERGUSON

GRUNDIG

NIKKAI

SANSUI

and many others


WVAE

TEL: 0734 876444

Head Office: 11, Arkwright Road, Reading, Berks. RG2 0LU
Tel: 0734-876444 Fax: 0734-867188 COPS No: 0734-311969

Enterprise Park, Reliance Street, Manchester. M10 0AL
Tel: 061-682-1415 Fax: 061-682-9031 COPS No: 061-683-4411

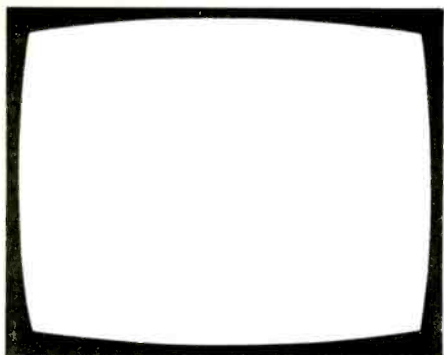11, Marhill Road, Carlton, Nottingham. NG4 3AJ
Tel: 0602-870789 Fax: 0602-878772



TELEVISION

July
1992

Vol. 42, No. 9
Issue 501

On sale June 17th

COPYRIGHT

© Reed Business Publishing Ltd., 1992. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Editorial correspondence should be addressed to "Television", Editorial Dept., Reed Business Publishing, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

INDEXES AND BINDERS

Indexes to Vols. 37 and 38 are available at £1.50 each from the Editorial office (address above). Photostats of the indexes to Vols. 31-36 can be supplied at £1 each. Make cheques etc. payable to Reed Business Publishing Ltd.

Binders that hold twelve issues of *Television* are available for £5 from Television Binders, 78 Whalley Road, Wilpshire, Blackburn BB1 9LF. Make cheques out to "Television Binders".

SUBSCRIPTIONS

An annual subscription costs £23 in the UK, £28 overseas (by surface mail - ask for airmail quote if required). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

Subscription hotline for 24-hour ordering with Credit Card number 0789 200 255.

BACK NUMBERS

Subject to availability, copies of issues published during the last 12 months are available at £2.50 each from Television Back Issues, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Make cheques/postal orders payable to Reed Business Publishing Ltd.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to published designs nor comment on alternative ways of using them.

this month

- 629 Leader**
- 630 A Scart Switcher Unit** *Keith Wevill B.Sc.*
Provides switching, manually or automatically controlled, between scart-connected VCR and satellite TV receiver inputs to a TV set, with priority for the VCR input. Also provides for recording of satellite TV programmes and the use of a second TV set independently.
- 634 Servicing the Tatung 160-180 Chassis** *Eugene Trundle*
These popular sets were also sold under the Deccacolour and other brand names and remained in production for several years. The model range caters for remote and non-remote controlled models and different screen sizes with 90° or 110° deflection. A detailed fault survey based on experience gained with large numbers of these sets.
- 639 Photostat Service**
- 640 Teletopics**
News, comment and developments.
- 641 Letters**
- 645 Next Month in Television**
- 646 VCR Clinic**
Reports from Eugene Trundle, Brian Storm, Alfred Damp, Michael Dranfield, Nick Beer, Ronnie Boag, Gerald Smith and John Edwards.
- 648 Filters for DX-TV Systems, Part 2** *Keith Hamer and Garry Smith*
Practical ways of using filtering techniques to avoid interference problems. Also the use of a second aerial to provide interference cancellation.
- 650 TV Fault Finding**
Reports from Philip Blundell, AMIEE, Mick Dutton, Steve Cannon, Chris Avis, Michael Dranfield, Roger Burchett and Stephen Leatherbarrow.
- 653 What a Life!** *Donald Bullock*
A particularly difficult customer can have unfortunate economic consequences.
- 656 Channel 5 Reception Problems** *Harold Peters*
Details of the Channel 5 transmitter allocations and coverage with an explanation of the causes of possible interference problems and the need for careful tuning.
- 660 Long-distance Television** *Roger Bunney*
DX conditions and reception and news from abroad, including satellite notes.
- 662 CD Player Casebook**
Reports from Mike Leach and P.J. Roberts, G1VUV.
- 663 Satellite Notebook** *Nick Beer*
Faults and problems experienced with satellite TV installations.
- 664 Test Case 355**

OUR NEXT ISSUE DATED AUGUST WILL
BE PUBLISHED ON JULY 15

AAY32	9p	B0332	40p	BT779	140p	TIP117	50p	DA47	10p	PCF801	110p	AN7145	195p	ICL7611	50p	LM3909	80p	STK436	490p	STK7228	800p	TA7310	100p
AC107	40p	B0361	60p	BU10A	110p	TIP120	37p	DA90	10p	PCF802	50p	AN7146	210p	ICL7612	50p	LM3910	80p	STK437	490p	STK7229	800p	TA7311	120p
AC125	30p	B0370	30p	BU105	80p	TIP121	47p	DA200	10p	PCF806	115p	AN7154	180p	ICL7660	240p	LM3914	160p	STK439	550p	STK7308	500p	TA7312	120p
AC127	30p	B0370	30p	BU108	100p	TIP125	47p	DA202	10p	PCH200	100p	AN7156	240p	ICM7555	60p	LM3915	160p	STK441	680p	STK7310	510p	TA7313	110p
AC128	36p	B0410	50p	BU109	80p	TIP126	56p	IN314	2p	PC182	80p	AN7168	260p	ICM7556	80p	LM3916	160p	STK443	740p	STK7348	410p	TA7315	200p
AC128K	36p	B0410	50p	BU109	80p	TIP127	56p	IN314	2p	PC182	80p	AN7172	270p	ICM7556	80p	LM3916	160p	STK443	740p	STK7348	410p	TA7315	200p
AC141K	45p	B0434	30p	BU111	140p	TIP130	30p	IN4002	3p	PC185	80p	AN7222	180p	KA2101	100p	M50117P	320p	STK459	560p	STK7358	500p	TA7324	200p
AC142K	45p	B0435	31p	BU124	60p	TIP131	30p	IN4003	3p	PC186	80p	AN7256	150p	KA2102	100p	M50117P	320p	STK460	720p	STK7402	600p	TA7325	90p
AC176	22p	B0436	30p	BU126	65p	TIP321	30p	IN4004	3p	PC186	80p	AN7256	150p	KA2103	100p	M50120P	650p	STK461	820p	STK7404	400p	TA7328	150p
AC176K	28p	B0436	38p	BU180	100p	TIP321	30p	IN4005	3p	PC186	80p	AN7336	200p	KA2209	125p	M50130P	650p	STK462	720p	STK7408	880p	TA7335	110p
AC187	40p	B0438	38p	BU184	100p	TIP142	90p	IN4006	3p	PL200	110p	AN7410	250p	KA2210	230p	M50130P	650p	STK465	720p	STK7410	1200p	TA7341	250p
AC187K	40p	B0439	38p	BU204	75p	TIP145	65p	IN4007	4p	PL2	60p	AY3-1015	290p	KA2212	80p	M50130P	650p	STK465	720p	STK7410	1200p	TA7341	250p
AC188	25p	B0440	40p	BU205	70p	TIP146	90p	IN4008	4p	PL3	60p	AY3-1200	800p	KA2214	150p	M51161	400p	STK465	720p	STK7410	1200p	TA7341	250p
AC188K	40p	B0441	40p	BU206	70p	TIP147	100p	IN4009	4p	PL4	60p	AY3-1350	450p	KA2216	100p	M51355P	300p	STK465	720p	STK7410	1200p	TA7341	250p
AC192	48p	B0533	50p	BU208	70p	TIP150	90p	IN5401	8p	PL5	180p	AY3-8910	360p	KA2263	100p	M51387P	200p	STK465	720p	STK7410	1200p	TA7341	250p
AD199	48p	B0534	38p	BU208A	60p	TIP151	90p	IN5402	8p	PL500	110p	AY3-8910	360p	KA2263	100p	M51387P	200p	STK465	720p	STK7410	1200p	TA7341	250p
AD199	48p	B0535	38p	BU208AT	90p	TIP2955	42p	IN5403	8p	PL504	120p	AY3-8910	360p	KA2263	100p	M51387P	200p	STK465	720p	STK7410	1200p	TA7341	250p
AF125	50p	B0536	38p	BU208D	90p	TIP3054	45p	IN5404	8p	PL508	200p	BA301	85p	KA2401	150p	M51545P	300p	STK465	720p	STK7410	1200p	TA7341	250p
AF125	50p	B0537	38p	BU209	140p	TIP3055	42p	IN5405	11p	PY81	100p	BA311	85p	KA2412	350p	M51545P	300p	STK465	720p	STK7410	1200p	TA7341	250p
AF139	30p	B0538	40p	BU225	190p	TIS44	40p	IN5406	12p	PY88	100p	BA311	85p	KA2412	350p	M51545P	300p	STK465	720p	STK7410	1200p	TA7341	250p
AF239	30p	B0643	50p	BU226	190p	TIS61	15p	IN5407	12p	PY88	100p	BA333	100p	KA2914A	300p	M51724P	300p	STK465	720p	STK7410	1200p	TA7341	250p
BA145	10p	B0647	50p	BU325	65p	TIP147	100p	IN5409	9p	PL84	80p	BA401	80p	LA1130	240p	M51742P	300p	STK465	720p	STK7410	1200p	TA7341	250p
BA148	10p	B0649	50p	BU326	75p	TIS93	20p	IN5410	9p	PL84	80p	BA401	80p	LA1130	240p	M51742P	300p	STK465	720p	STK7410	1200p	TA7341	250p
BA145	10p	B0649	50p	BU326	75p	TIS93	20p	IN5410	9p	PL84	80p	BA401	80p	LA1130	240p	M51742P	300p	STK465	720p	STK7410	1200p	TA7341	250p
BA157	12p	B0676	40p	BU406D	85p	VK1010	88p	SKE4F206	60p	3mm	250p	BA511	160p	LA1185	150p	M53206P	100p	STK465	720p	STK7410	1200p	TA7341	250p
BA157	12p	B0676	40p	BU406D	85p	VK1010	88p	SKE4F206	60p	3mm	250p	BA511	160p	LA1185	150p	M53206P	100p	STK465	720p	STK7410	1200p	TA7341	250p
BA205B	24p	B0678	40p	BU407D	80p	VN66AF	100p	SR2M	60p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC107	8p	B0679	40p	BU408	75p	VN88AF	115p			GREEN	8p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC108	8p	B0680	40p	BU408D	80p					RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC109	8p	B0681	40p	BU409	80p					RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC109C	10p	B0682	45p	BU426A	70p	ZTX107	11p	8PIN	5p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC118	11p	B0705	50p	BU500	100p	ZTX109	11p	14PIN	6p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC140	20p	B0707	50p	BU508A	70p	ZTX122	27p	16PIN	12p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC140	20p	B0708	50p	BU508AF	70p	ZTX122	27p	16PIN	12p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC142	20p	B0711	50p	BU508D	80p	ZTX301	17p	20PIN	12p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC143	20p	B0736	50p	BU508DF	75p	ZTX302	17p	22PIN	14p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC147	8p	B0826	50p	BU526	115p	ZTX303	24p	28PIN	14p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC148	8p	B0826	50p	BU526	115p	ZTX303	24p	28PIN	14p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC149	8p	B0829	50p	BU530A	100p	ZTX304	24p	30PIN	14p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC157	8p	B0899	50p	BU536	140p	ZTX320	29p	40PIN	18p	RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC159	8p	B0901	50p	BU562	150p	ZTX501	13p			RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC160	30p	B0937	60p	BU626	150p	ZTX502	13p			RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC171	10p	B0K32	100p	BU801	80p	ZTX543	25p			RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC172	10p	B0K33	60p	BU806	75p	ZTX504	25p			RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC177	14p	B0K65	80p	BU807	70p	ZTX550	24p			RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC178	14p	B0K65	80p	BU807	70p	ZTX550	24p			RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC179	14p	B0K65	80p	BU807	70p	ZTX550	24p			RED	5p	BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC182	7p	B0W93	50p	BU920	130p	2N696	26p	BZK61 RANGE	2V to 3V	9p		BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC182	7p	B0W94	50p	BU921	130p	2N698	26p	BZK61 RANGE	2V to 3V	9p		BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC183	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC184	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC184	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC184	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC184	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC184	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC184	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210	75p	M53274P	200p	STK465	720p	STK7410	1200p	TA7341	250p
BC184	7p	B0Y52	100p	BU932	130p	2N708	26p					BA516	180p	LA1210									

LINEAR IC's - Cont.	TD44503 300p	TD44504 300p	TD44505 300p	TD44506 300p	TD44507 300p	TD44508 300p	TD44509 300p	TD44510 300p	TD44511 300p	TD44512 300p	TD44513 300p	TD44514 300p	TD44515 300p	TD44516 300p	TD44517 300p	TD44518 300p	TD44519 300p	TD44520 300p	TD44521 300p	TD44522 300p	TD44523 300p	TD44524 300p	TD44525 300p	TD44526 300p	TD44527 300p	TD44528 300p	TD44529 300p	TD44530 300p	TD44531 300p	TD44532 300p	TD44533 300p	TD44534 300p	TD44535 300p	TD44536 300p	TD44537 300p	TD44538 300p	TD44539 300p	TD44540 300p	TD44541 300p	TD44542 300p	TD44543 300p	TD44544 300p	TD44545 300p	TD44546 300p	TD44547 300p	TD44548 300p	TD44549 300p	TD44550 300p	
TD44551 300p	TD44552 300p	TD44553 300p	TD44554 300p	TD44555 300p	TD44556 300p	TD44557 300p	TD44558 300p	TD44559 300p	TD44560 300p	TD44561 300p	TD44562 300p	TD44563 300p	TD44564 300p	TD44565 300p	TD44566 300p	TD44567 300p	TD44568 300p	TD44569 300p	TD44570 300p	TD44571 300p	TD44572 300p	TD44573 300p	TD44574 300p	TD44575 300p	TD44576 300p	TD44577 300p	TD44578 300p	TD44579 300p	TD44580 300p	TD44581 300p	TD44582 300p	TD44583 300p	TD44584 300p	TD44585 300p	TD44586 300p	TD44587 300p	TD44588 300p	TD44589 300p	TD44590 300p	TD44591 300p	TD44592 300p	TD44593 300p	TD44594 300p	TD44595 300p	TD44596 300p	TD44597 300p	TD44598 300p	TD44599 300p	TD44600 300p

25D121 100p	25D122 100p	25D123 100p	25D199 100p	25D200 100p
-------------	-------------	-------------	-------------	-------------

JAPANESE TRANSISTORS		25A472 35p	25A473 35p	25A474 35p	25A799 35p	25A800 35p
VIDEO HEADS		AWA 66AV77	AKAI VS 105112115116125126201220250301	AKAI VFP100V77VS500V95009800	AKAI 8808A124510V50091000	ANIRAD VCR 4600S200900TVR1	ANIRAD VCR 7000	ANIRAD VCR 6006100	ANIRAD TVR2TV330CR4600VCR4600MKIIVCR4700	AUTHENTIC 1890	AWA 1890	BAIRD 890630189028039060228028	BAIRD 89048232489254893589418933934	BAIRD 8909812	BAIRD 890883189338940	BAIRD 8942	BAIRD 89478948	BAIRD 8950	BLAUPUNKT RTV1002002211214222224RTX100RTX200	BLAUPUNKT RTV306307309131315161520	BLAUPUNKT RTV31001A312317319320	BLAUPUNKT RTV32425	BLAUPUNKT RTK238	BLAUPUNKT RT424	BLAUPUNKT RT444	BLAUPUNKT RTX260	BOSCH BUA235	BOSCH VRH50	BOSCH VRR70	BOSCH VRR25	BOSCH VRR30	BRANDT ELECT VK13435	BRANDT ELECT VK32336373839454849511231319349495	BRANDT ELECT VK42642943943945	BRANDT ELECT VK437	BRANDT ELECT VK445	BRANDT ELECT VK449	BRANDT ELECT VK489	CANON VR10	CANON VR30A30B30E40A	DAEWOO VCP 11 RFAF	DECCA 8300	DUAL EVR 101	DUAL VR7071480819091	DUAL VR 8596	DUAL VR 87	EDISON VC130213371352140263029302932934122	EDISON VK21322512	EDISON VK2362340	EDISON VK2502532263254	EDISON VK2632	EDISON VK2637	EDISON VK42645	EDISON VK4382439	FUNAI E11VFP100VP1400VCR40012SVCR4500	FUNAI 4800V175200600400600VFP3000	FUNAI VCR4600S400600	FISHER FVH510520530615622710715720721722	FISHER 910VPH82071905060809119159165000	FISHER VBS700750076009000VBS35007007600	FISHER 980VBR330	FISHER VBS7000VBS100VBS9000	FISHER FVH11718721722VFDH720	GRANDATA LTD	K.P. HOUSE, UNIT 15,	POP IN COMMERCIAL CENTRE,	SOUTHWAY, WEMBLEY,	MIDDLESEX, ENGLAND	Tel: 081-900 2329 Fax: 081-903 6126	FOR EVEN MORE BARGAINS																																																																																																																																																																																																																																																																				

IDLERS & PULLEYS REPLACEMENTS			
AMSTRAD		Reference	
VCR7000		150280	£1.50
AKAI			
VS1-2, VS4-5, VS15	FF-REW IDLER	M1327773	£4.50
VS1-2, VS4-5, VS15	T-UP IDLER	BV327815	£6.00
V9700	IDLER	BV321979	£6.00
VS125, 126, 155, VS165, 240, 244, VS245, 247, 248, VS250, 512, 515, 516	IDLER ASSY	MZ366960J2	£11.00
FERGUSON			
3V16-22	T-UP IDLER	PU47752	£4.50
3V16-22	T-UP IDLER	PU49280	£6.30
3V23, 3V29-30, 3V31-32, 3V35	REEL IDLER	PU48967	£3.00
3V23	ROLLER ASSY	PU49042A	£4.00
3V29-30, 3V31-32, 3V35-36, 3V38-39, 3V49	T-UP IDLER	51402	£1.45
3V29-30, 3V31-32	T-UP CLUTCH	PU51380	£2.60
3V35-36, 3V38-39, 3V49	REEL IDLER	PU55374	£2.85
3V35-36, 3V38-39, 3V49	T-UP CLUTCH	PU55373	£2.25
3V58-59, 3V64-65, FV10-11, FV12-13, FV14	IDLER ARM	PU58645	£2.50
3V42	CLUTCH ASSY	PU55822	£13.50
3V44	CLUTCH ASSY	PU57658	£11.50
3V42, 43, 48, 53, 56	T-UP CLUTCH	PU56043-1-4	£2.80
3V42, 43, 48, 53, 56	SUPPORT CLUTCH	PU56044-1-5	£2.80
FISHER			
FVHP520, FVHP530	FF-REW PULLEY	H1638531	£1.00
FVHP615	COMP IDLER ASSY	F11430420400300	£3.30
FVHP615	GEAR IDLER ASSY	F11430490400900	£5.50
FVHP840	REEL T-UP ASSY	F11430410400900	£6.50
FVHP905, 906, 908, FVHP910, 916	GEAR IDLER ASSY	F11430490402400	£6.20
FVHP975, 990, 999, FVHP5000, 5100	IDLER	F11430420400700	£5.20
GOLDSTAR			
	IDLER	435038A	£2.50
HITACHI			
VT11-33, VT63-64, VT14, 17, 19, 38, 57, VT86, 88	FF-REW IDLER	6886971	£1.50
	PLAY IDLER	V-6861482	£3.20
	CLUTCH ASSY	6879515	£7.50
VT120-220	CLUTCH ASSY	6886824	£7.50
VT8000-8300, VT8500-8700, VT8000-8300, VT8500-8700, VT8000-8300, VT8500-8700	FF-REW IDLER	6413663	£2.80
VT8000-8300, VT8500-8700	PLAY IDLER	6414221	£3.60
VT8000-8300, VT8500-8700	FF-REW PULLEY	6383531	£0.80
VT9300-9500, VT9300-9500, VT9300-9500	FF-REW IDLER	6861471	£3.30
	PLAY IDLER	6861482	£3.20
	IDLER	681505	£3.00
	IDLER	687043	£3.80
VT11-33, VT63-64	FF-REW IDLER	6886971	£1.50
HINARI			
VXL3, VXL20	REEL IDLER	40000009	£1.50
ITT			
VR3905, VR3906	T-UP IDLER	PU51402	£1.45
VR3906	REEL IDLER	PU55374	£2.85
VR3913, VR3943	REEL IDLER	PU48967	£3.00
JVC			
HR330, 3660, 4100, HR7200, HR7600, HR7650, HR7655, HR7200, HR7600, HR7650, HR7655, HR7700	T-UP IDLER SML	PU49280	£6.00
	T-UP CLUTCH	PU53462A	£3.00
HR7200, HR7600, HR7650, HR7655, HR7700	ROLLER ASSY	PU49042A	£4.00
HR3300, 3660, 4100, HR7200, 7600, 7650, HR7655, HRD110, HRD120-121, HRD225, HRD110, HRD120-121, HRD225	T-UP IDLER LRG	PU17752	£4.50
	T-UP IDLER	PU51402A	£1.45
HRD110, HRD120-121, HRD225	T-UP CLUTCH	PU55373	£2.25
HRD110, HRD120-121, HRD225	IDLER ARM	PU55374-3-8	£2.85
MATSUI			
VX730, 735, 750, 755, VX810, 820, 880, 990	CLUTCH	850A00005	£6.50
MITSUBISHI			
HS306, 307, 318, 319, HS410, 710	GEAR ASSY	522P00201	£6.25


IDLERS & PULLEYS REPLACEMENTS — Cont.			
NATIONAL			
NV322, NV600, NV688, NV777, NV788	IDLER UNIT	VXP0463	£3.00
NV333	IDLER ARM	VXL0997	£3.60
NV333, NV366	IDLER UNIT	VXP0401	£0.75
NV333, NV366	PLAY IDLER	VXP0433	£3.00
NV333, NV3000	ACTION GEAR	VVG0016	£0.60
NV333, NV2000, NV3000	LOADING GEAR	VXP0325	£2.00
NV7800			
NV333, NV2000, NV3000	INTERMEDIATE GEAR	VXG0017	£0.65
NV333	CAM GEAR	VXG0158	£1.00
NV366	IDLER ARM	VXL0997	£3.60
NV370, NV430, NV730, NV830, NV850, NV870, NVG7, NVG10, NVG12, NVG18	IDLER ARM	VXP0521	£1.20
NV370, NV430, NV870, NV730, NV830, NV850	CAM GEAR	VVG0200	£1.20
NV730	IDLER UNIT	VXP0581	£2.50
NV2000, NV3000	IDLER UNIT	VXP0331	£1.20
NV2000, NV3000	IDLER UNIT	VXP0329	£1.20
NV2000, NV3000	CAM GEAR	VVG0069	£1.00
NV2000, NV3000	ACTION GEAR	VVG0016	£0.60
NV7000, 7200, 7800	IDLER UNIT	VXP0344	£1.00
NV7000, 7200, 7800	CLUTCH	VXP0343	£5.50
NV8400, NV8600, NV8610, NV8620	IDLER UNIT	VXP0245	£1.20
NV8610, NV8620	PLAY IDLER	VXP0243	£1.20
NV8620	CLUTCH	VXP0343	£5.50
NV600	IDLER	VXP0488	£3.50
NVG21-25, NVG40-45	PULLEY UNIT	VXP0767	£5.80
ORION			
VH200-201	IDLER	850A200004	£3.50
VH555-700, VH844-900, VH1000-1500, VH1800, VP200, VH530, VH535-630, VH635-640, VH893-1440, VH2500-2600, VH2700-4010, VH5010	IDLER	850A200005	£6.50
PHILIPS			
DV464, VR6462, VR6463, VR6660, VR6660	IDLER	52220334	£2.50
VR6460, VR6520, 6920, DB532, VR6542, VR6843	IDLER ARM REEL IDLER	40340162	£1.70 £7.50
SANYO			
VHR110, VHR1300, VHR1500	IDLER	1430662T14730	£5.00
VTC5000, VTC5150, VTC9100, VTC9300, VTC9300	FF-REW IDLER IDLER FF ROLLER ASSY	1430741T20001 1430551T01400 1430547T00200	£3.00 £1.20 £2.20
VTCM10-20	REEL DRIVE PULLEY	1430662T10350	£5.00
VHR2100, VHR2300	IDLER	6130374899	£5.00
VTC5000, VTC5150	PULLEY	143-0-662T-01201	£5.20
VTCM10	PULLEY	143-0-662T-10350	£5.50
SHARP			
VC651, VC681, VC685, VC7300, VC7700	IDLER ASSY PLAY IDLER KIT	NPLYV0107GEZZ NPLYV0041+ NDA1V1007	£6.15 £5.00
VC381, VC383, VC386, VC8381, VC9100, VC9300, VC9500, VC9700	IDLER	NIDL0005GEZZ	£1.50
VC300, VC387, VC481, VC482, VC483, VC496, VC571, VC585	IDLER	NH0L0006GEZZ	£1.50
VC780-781, VC785-787, VC793-VC772	REEL IDLER	NPLTV0111GEZZ	£7.00
SAISHO			
VR1100, VR1200, VR1200HD, VR1600, VR2500, VR3300, VR3500, VR3600	CLUTCH	850A200000	£6.50
SAMSUNG			
VT510-511, VT520-610, VT611-616, VT620-621-626	IDLER WHEEL	65224704220	£1.50
VT510-511, VT520-610, VT611-616, VT620-621-626	IDLER COMPLETE	69000250330	£4.50
SONY			
C6, C7	IDLER KIT ASSY IDLER ASSY	A-6706391 X-36533100	£3.50 £3.80
SL-C5, SL-C7	REW PULLEY	A-6706-348-B	£4.00
SL-C6	REW PULLEY	A-6706-391-A-B	£3.00
CASSETTE DC MOTORS			
6V MOTOR			£2.00
9V MOTOR			£2.00
12V CW MOTOR			£2.00
12V CCW MOTOR			£2.00
13.2V CW MOTOR			£2.90
13.2V CCW MOTOR			£2.90
CASSETTE TAPE HEADS			
MONO HEAD			£0.90
STEREO HEAD			£1.50
MINI HEAD			£2.30
AUTO REVERSE HEAD			£2.60

VIDEO MOTORS		
AMSTRAD		
VCR 7000	REEL MOTOR	£17.00
FERGUSON & JVC		
PU 45979, 3V16, 3V22, HR3300, HR3660	CAPSTAN MOTOR	£21.00
PU 55371V, 3V35, 3V36, 3V38, 3V39	CAPSTAN MOTOR	£19.50
8943, 8944, HRD110, HRD120, HRD121, HRD225		
PU 46414, 8904, 8922, HR3300, HR3320, HR3330, HR3360, HR3660, HR3660	DRUM MOTOR	£19.50
PU 51381V, 3V39, 3V30, 8930, HR7200, HR7300	REEL MOTOR	£26.50
PU 58635V, 3V58, 3V59, 3V64, 3V65, 8950, 8951, FV10B, FV11R, FV12L, FV13H, FV20B, FV21R, FV22L, HRD170, HRD180, HRD230, HRD370, HRD430	CAPSTAN MOTOR	£29.00
PU 58636W, 3V58, 3V59, 3V64, 3V65, 8950, 8951, FV10B, FV11R, FV12L, FV13H, FV14T, FV20B, FV21R, FV22L, HRD170, HRD180, HRD230, HRD370, HRD430, HRD530	REEL MOTOR	£18.00
3V43, 3V44, 3V45, 3V48, 3V53, 3V54, 3V55, 3V56, 3V57, 8945, 8947, 8948, HRD140, HRD150, HRD455, HRD565, HRD725, HRD755, HRP50, R73AF	LOADING MOTOR	£8.00
MITSUBISHI		
288P02801, HS300, 301, 302, 310	MOTOR REEL SPOOLING	£33.50
288P02806, HS303, 304, 320, 330, 700	MOTOR REEL SPOOLING	£31.50
288P03401, HS303, 700	MOTOR REEL TAKE-UP GEN	£21.00
NATIONAL		
MYN 135V5L, NV332, NV333, NV340, NV366	REEL MOTOR	£13.50
VEM0212, NV730, NV770	MOTOR REEL GEN	£30.00
SANYO		
4-529V-10800 (RM11), VTC5000, VTC5150	REEL MOTOR	£6.30
SHARP		
RMOTV 1008GEZZ, VC200, VC381, VC384, VC385, VC386, VC483, VC3300, VC8381, VC9100, VC9300, VC9500, VC9700	REEL MOTOR	£13.50
RMOTV 1007GEZZ, VC387, VC483, VC486, VC585	REEL MOTOR	£16.50
RMOTV 1010GEZZ, VC300, VC402, VC471, VC477, VC481, VC482, VC488, VC496, VC500, VC571, VC581, VC582, VC583, VC584, VC5F3, VC8481, VC8581	REEL MOTOR	£16.00
SONY		
BHF 1100D, SLC7	CAPSTAN MOTOR	£25.00
CASSETTE HOUSING		
FERGUSON & JVC		
3V38, 3V39, 8943, 8944, 8951, 3V35, 3V36, HRD110, HRD120, HRD121, HRD225		£24.00
3V42, 3V43, 3V44, 3V45, 8945, 8947, HRD140, HRD141, HRD150, HRD455, HRD725		£24.00
8948, 8950, FV10B, FV12L, FV13H, FV14T, FV20B, FV21R, FV22L, HRD230, HRD430, HRD530		£24.00
3V58, 3V59, 3V64, 3V65, FV11R, HRD170, HRD180, HRD370		£24.00
VIDEO LAMPS		
UNIVERSAL VIDEO LAMPS 12V 60mA (300mm WIRES)		£0.30
PANASONIC VIDEO LAMPS		£0.50
SONY FLYBACK TRANSFORMERS		
Part No.	Models	Price
1-439-216-00	KV-2002E, 2010E, 2200E, 2015, 1820E, 2010SE, KV-2012ME, 2016ME, 2015ME, 2010ME	£14.00
1-439-256-11	KV-2704EC, 2704UB, 2704ET, 2704E(A), 2704E	£40.00
1-439-286-21	KV-2215UB, 2217UB, 2215E1, 2215FE, 2212EX, 2215ET	£30.50
1-439-289-21	KV-2705F, 2705FE, 2705UB, 2705E, 2706UB, 2720EC	£40.00
1-439-303-00	KV-2064EC, 20PS1, 2082ME7, 2056EC, 2060SA, KV-2062E(ESP)	£22.75
1-439-311-00	KV-1440AEC, 1440AS MK2, CPS-14CD3, CPV-14CD2, KTX-1350NF, KTX-1430UB	£22.00
1-439-332-21	KV-2756, 2730EC, 2730FE, 2764EC, 2752UB, 2752F	£30.00
1-439-333-00	KV-1882EC, 1882UB, 1882F, 1882CH, 1882AEB, 1882AM, KV-1882ME3, 1882HK, 1882AS, 16TR1, 882EC(PS), 1770R, KV-19HT1A, 19FX1MT, 18G2, 1602M7, 1602GE, ADM-166, KV-2092UB, 2096UB	£21.50
1-439-363-21		£22.00
NATIONAL LINE OUTPUT TRANSFORMER		
TLF 146-11B		£19.00
TLF 15542F		£25.00
TLF 14568F		£26.00
TLF 14567F		£26.00
TLF 14715F		£27.00
TLF 14749B		£20.00
NATIONAL TRANSFORMERS		
TLF 6609B		£23.00
HITACHI TRANSFORMERS		
2434274		£18.00

GRANDATA LTD
 K.P. HOUSE, UNIT 15,
 POP IN COMMERCIAL CENTRE,
 SOUTHWAY, WEMBLEY,
 MIDDLESEX, ENGLAND
 Tel: 081-900 2329 Fax: 081-903 6126

TRIPLERS							
UNIVERSAL	£4.50	41256-10	110p	8256	700p	75-154	65p
THORN 9000 SERIES	£8.00	41464-12	150p	8257	220p	75492	55p
PHILIPS G9	£7.50	41464-10	200p	8271	3400p		
G8 520 550	£7.50	6116	80p	8279	270p	8126	95p
K13	£4.50	6264-15	160p	8283	400p	8178	110p
DECCA 100 SERIES	£7.50	6264-12	200p	8284	440p		
120 130	£6.50	6264-10	210p	8287	260p		
ITT CVC 20 30	£7.00	62256-12	300p	8288	650p		
CVC 825	£8.00	6502	300p	8748	700p	SIMMS	
RANK 120A	£7.00	6502A	360p	8755	800p	256K x 9-80	1000p
UNIVERSAL		65022	930p	Z80ACPU	100p	256K x 9-70	1100p
To fit 20AX TUBE	£8.00	6522	280p	Z80BCPU	160p	1MB x 9-80	3000p
30AX TUBE	£8.00	6551	380p	Z80ADMA	200p	1MB x 9-70	3200p
		6800	210p	Z80AP10	150p		
		6802	220p	Z80BP10	150p	SIPS	
		6803	500p	Z80AC1C	140p	256K x 9-80	1100p
		6808	500p	Z80RC1C	200p	256K x 9-70	1200p
		6809	500p	Z80AS10	210p	1MB x 9-80	3100p
		6810	150p	Z80AS10-1	210p	1MB x 9-70	3200p
		6818	380p	Z80AS10-2	210p		
		6821	130p	Z80ADART	260p		
		6840	290p			OPTO COUPLERS	
		6845	200p			4N25	50p
		6850	90p	74S289	180p	4N26	50p
		8080A	380p	74S387	200p	4N27	50p
		8085A	300p			4N28	50p
		8088	500p	75107	65p	4N29	90p
		8088	480p	75110	75p	4N30	90p
		8156	300p	75113	100p	4N31	90p
		81LS96	130p	75122	110p	4N32	100p
		81LS97	130p	75150	95p	4N33	100p
		81LS98	130p	75154	95p	4N36	58p
		8224	240p	75162	100p	4N37	58p
		8226	240p	75182	700p	4N38	65p
		8243	250p	75183	95p		
		8250	750p	75188	95p	LED DISPLAY	
		8251	200p	75189	55p	MAN74	100p
		8253	160p	75195	55p	MAN8910	200p
		8255	160p	75451	185p	DL747	120p

VIDEO HEAD TESTER

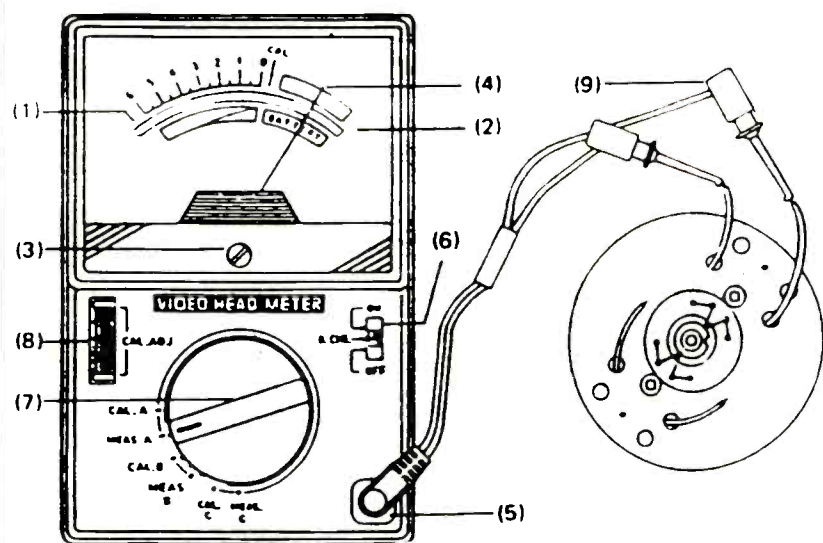

1. Mechanical Position of Pointer
2. Scale Plate
3. Pointer Adjusting Screw
4. Pointer
5. Measuring Socket
6. Power ON/OFF and Battery Check Switch
7. Range Selector Rotary Switch
8. CAL. ADJ. (calibration volume)
9. Measuring Clip

***** STOP PRESS *****

PHILIPS PRESSURE ROLLER ASSEMBLY

for the following models:
 DV186, 190, 286, 562, 761,
 VR6180, VR6185, VR6285,
 VR6382, VR6367, VR6467,
 VR6468, VR6870, VR6182.
 6290, 6291, 6293, VR6393,
 VR6468, VR6670, 6760, 6761,
 VR6970
 Part Number: PS 403-40205 Price ... 625p

SOLDERING IRONS

Wooden Handle
 30 Watt 220/100 Volts Soldering Iron..... 3.50
 40 Watt 220/100 Volts Soldering Iron..... 3.50
 60 Watt 220/100 Volts Soldering Iron..... 3.50

PRICE

YF-225 VHS £30.00 + VAT
 YF-225B BETAMAX £29.00 + VAT

GRANDATA LTD

K.P. HOUSE, UNIT 15, POP IN COMMERCIAL CENTRE,
 SOUTHWAY, WEMBLEY, MIDDLESEX, ENGLAND
 Telephone: 081-900 2329 Telex No: 932 885 (Sunmit)
 Fax: 081-903 6126
 Access & Visa Card accepted. Open Monday to Saturday.

PLEASE PHONE US FOR TYPE NOT LISTED
 HERE AS WE ARE HOLDING 5000 ITEMS
 AND QUOTATIONS ARE GIVEN FOR LARGE
 QUANTITIES.

Please send £1 P&P and VAT at 17½%. Govt,
 Colleges, etc. Orders accepted. Quotations
 given for large quantities. Please allow 7 days for
 delivery. All brand-new Components. All valves
 are new and boxed. Prices quoted are subject to
 stock availability and may be changed without
 notice.

WHATEVER YOU NEED IN **SATELLITE** TV EQUIPMENT, WE HAVE THE **SOLUTION.**



Satellite Solutions offers an unbeatable service for SMATV and all multi-viewer TV systems.

We have the best equipment at the most competitive prices. But most importantly, every item is available with our famous Installer/Contractor technical and **on-site** support. This ensures you success with TV system contracts of every size.

In fact, **Satellite Solutions** can make even the largest, most complex projects risk free for you with the following products and services:

- ★ On-Site Survey
- ★ Full Design & Installation Support
- ★ Full Range of Equipment
- ★ Leading Names in Satellite TV
- ★ Widest Range of Test Equipment
- ★ Repair & Maintenance Contracts
- ★ Regular Trade Newsletter
- ★ Pro. and Domestic LNBs
- ★ LNB Components
- ★ Wide Range of Dishes
- ★ Pro. HV Switches
- ★ Head End Equipment
- ★ UHF/VHF Products
- ★ Wide Accessory Range

So call Jo Griffiths on the **HELPLINE** for your **FREE** copy of our *Trade Only Catalogue* offering the best **Satellite Solutions** around.

HELPLINE
0604 670900

SATELLITE SOLUTIONS

35 Quarry Park Close,
Moulton Park,
Northampton NN3 1QB
Fax: (0604) 671343




HOW TO INCREASE YOUR PROFITS, IMPROVE YOUR SERVICE, WITH COST EFFECTIVE TEST EQUIPMENT.

HAMEG OSCILLOSCOPES

HAMEG are Europe's top selling DUAL TRACE OSCILLOSCOPES. Select from four superb models. All, with the exception of the HM 1005, incorporate a useful COMPONENT TESTER. Size - all models - 285mm x 145mm x 380mm. Clear display 8cm x 10cm. Mains supply: 110/220/240V AC 50/60Hz. All supplied with 2 PROBES, a COMPREHENSIVE MANUAL and a 2 YEAR WARRANTY.


HM203-7 20MHz STANDARD

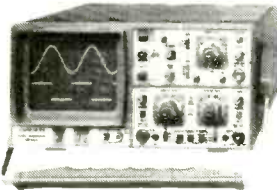

- SPECIFICATION**
- * 2 Channels
 - * Bandwidth: DC - 20MHz
 - * Sens: Ch.1, Ch.2, 1mV/cm
 - * Timebase: 0.1s - 20ns/cm
 - * Triggering: DC - 40MHz
 - * Active TV - Sync - Separator
 - * Variable hold-off
 - * Trigger LED indicator
 - * Calibrator: 1KHz Square wave
 - * Component tester
 - * Plus many features

Price £338.00 + £59.15 V.A.T. FREE Specialist Carrier Delivery

HM604 60MHz UNIVERSAL

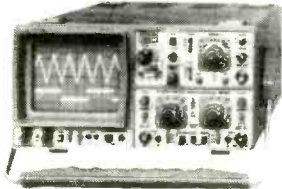

- SPECIFICATIONS**
- * 2 Channels
 - * Bandwidth: DC - 60 MHz
 - * Sens: Ch.1, Ch.2, 1mV/cm
 - * Timebase: 2.5s - 5ns/cm
 - * Triggering: DC - 80MHz
 - * Active TV - Sync - Separator
 - * After delay trigger
 - * Sweep delay
 - * Delay line
 - * Trigger LED indicator
 - * Calibrator: 1KHz & 1MHz Sq. Wave
 - * Component tester

Price £610.00 + £106.75 V.A.T. FREE Specialist Carrier Delivery


HM1005 100MHz UNIVERSAL 3 CHANNELS - UP TO 6 TRACES



- SPECIFICATION**
- * 3 Channels
 - * Bandwidth: DC - 100MHz
 - * Sens: Ch.1, Ch.2, Ch.3, 1mV/cm
 - * Timebase A: 2.5s - 5ns/cm
 - * Timebase B: 0.2s - 5ns/cm
 - * Triggering DC - 130MHz
 - * After delay trigger
 - * Delay line
 - * Trigger LED indicator
 - * Overscan LED indicator
 - * Active TV - Sync - Separator
 - * Calibrator: 1KHz & 1MHz Sq. Wave

Price £792.00 + £138.60 V.A.T. FREE Specialist Carrier Delivery

HM205-3 20MHz DIGITAL STORAGE

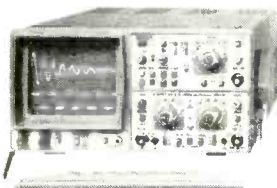

- SPECIFICATION**
- * Digital Storage
 - * Analogue real time (Same as 203-7)
 - * Bandwidth: DC - 20MHz
 - * Sens: Ch.1, Ch.2, 1mV/cm
 - * Timebase Digital: 5s - 1µs/cm
 - * Triggering DC - 40MHz
 - * Active TV - Sync - Sampling
 - * Max sampling rate: 2 x 20MHz
 - * Memory: 2 x 2048 x 8 Bit
 - * Dot joiner
 - * Printer/plotter output

Price £610.00 + £106.75 V.A.T. FREE Specialist Carrier Delivery

B.K.'s CRT TESTER REJUVENATOR

Tests and rejuvenates blue, green and red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120 x 65 x 60mm. Supply 240V AC

Price £34.00 + £5.95 V.A.T.

DIGITAL CAPACITANCE METER


* High accuracy.
* 0.1pF-2,000µF.
* LCD display.
* 8 ranges.
* Accuracy +/- 0.5%.
* Full scale +/- 1 digit.
* Inc. protective case.

Price £39.99 + £6.99 V.A.T.

LEADER FM STEREO SIGNAL GENERATOR


At last! A generator specifically designed for testing and fault finding on FM stereo and monaural VHF receivers including stereo multiplex circuits.

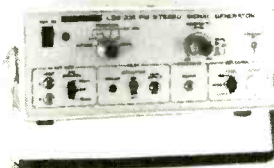- FEATURES**
- * Carrier frequency 100 - 1.1MHz (adjustable).
 - * Output level 0.1mV - 10mV.
 - * Pilot signal 19KHz +/- 2Hz.
 - * L & R separation over 50dB.
 - * External Modulation 50Hz - 15KHz.
 - * Pre-emphasis 50µs, 75µs & off.
 - * Comprehensive test lead set included.
 - * Mains powered.
 - * Size: 80 x 200 x 250mm.



Price £299.00 + £52.33 V.A.T.

LEADER HIGH VOLTAGE METERED EHT PROBE

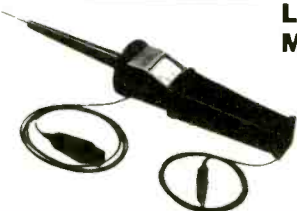


Light weight, easy-to-grip high-impact plastic handle with arc-over protection and no need of extra equipment. An indispensable item in your TV service kit. Measures up to 40kV DC with safety and the greatest of ease. Entirely self-contained. Connect the lead clip to chassis and probe tip to the check point, read the meter for voltage.

A must for the Health and Safety at Work Acts.
Price £66.00 + £11.55 V.A.T.

B & K PRECISION CRT ANALYSER-RESTORER

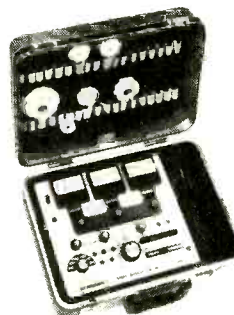The number one CRT Test Instrument. Over 5000 U.K. Television engineers wouldn't be without it.



* All CRT's checked identically, including all in-line and one gun types * Tests all three guns of colour CRT's simultaneously under actual operating conditions (model 490) * Exclusive multiplex technique (model 490) * Measure true dynamic beam current that actually passes through G1 aperture to screen * Measures all shorts and leaks - preserving more CRT's * Tests focus electrodes lead continually finding faults that other testers miss * Uses most powerful restoration method known with minimum danger to CRT * Rejuvenated CRT's guaranteed as new for two years * Obsolescence proof - perpetual set up chart updated and new adaptors developed * Tests and rejuvenates VDU's and oscilloscope tubes * A range of over 40 CRT base adaptors available * Increase profit * Pays for itself in months.

Prices


Model 490 Tri-dynamic three meter instrument inc. 6 common adaptors.....	£509.00	£89.08 V.A.T.
Without adaptors.....	£446.00	£78.05 V.A.T.
Model 480 Single meter instrument inc. 6 common adaptors.....	£375.00	£62.63 V.A.T.
Without adaptors.....	£310.00	£54.25 V.A.T.

SADELTA SIGNAL STRENGTH METERS

The Sadelta Field Strength Meters have been designed to facilitate the dish alignment of satellite TV systems and aerial alignment of VHF/UHF television and radio systems. Signal levels can be accurately measured on the TC402-C and the TC90, allowing the evaluation of signal conditions for satisfactory operation. Both models have a clear LCD direct frequency readout, coupled to a multiturn tuning control enabling precise channel identification.


TC402-C VHF & UHF

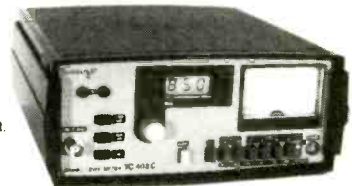- FEATURES**
- * Three bands:
Low VHF: 45-110MHz
High VHF: 110-300MHz
UHF: 470-862MHz
 - * Digital display for direct frequency readout.
 - * Built-in monitor loudspeaker AM FM.
 - * Signal measurement from 20µV to 100mV.
 - * Powered by eight 1.5 AA batteries.
 - * Fully portable with sturdy carrying case.



Price £259.00 + £45.33 V.A.T.

TC90 VHF-UHF-SAT.

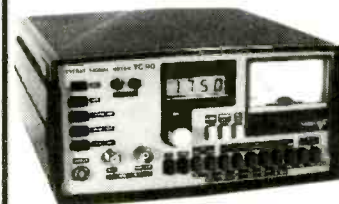

- FEATURES**
- * Five bands:
Low VHF: 45-110MHz
High VHF: 110-300MHz
Hyper VHF: 300-470MHz
VHF: 470-862MHz
Satellite: 950-1750MHz
 - * Digital display for direct frequency readout.
 - * Signal measurement VHF/UHF 20µV to 3V.
 - * Signal measurement satellite -70dBm to -10dBm.
 - * Audible indication of satellite signal level.
 - * Built-in monitor loudspeaker AM/FM (not satellite).
 - * Powered by rechargeable battery (complete with charger 220/240V AC).
 - * Fully portable with sturdy carry case.

Price £499.80 + £87.47 V.A.T.

BLACK STAR COLOUR PATTERN GENERATOR THE 'ORION' THREE-IN-ONE PAL VHF/UHF - PAL VIDEO COMPOSITE - R.G.B.

The Orion is a compact, bench instrument offering a wide range of patterns and facilities at a truly low cost.


In addition to a switchable sound carrier facility which allows use with the majority of PAL TV systems, the Orion provides highly flexible RGB outputs, ensuring compatibility with most video monitors.

More than 50 pattern combinations can be selected, including those for testing static and dynamic divergence, video amplifier linearity, colour purity, general colour performance, focus etc.

A separate video input to modulate camera signals; fully variable RF and video output levels facilitating AGC testing; trigger output allowing easy triggering of difficult oscilloscope waveforms; external sound modulation input via DIN connector for frequency response testing of TV sound systems; adjustable wide frequency coverage of VHF and UHF TV bands.

Just some of the features making the Orion Pattern Generator an indispensable tool in the manufacture, test, and servicing of televisions, and computer and video monitors.

- FEATURES**
- * Colour bars, purity, greyscale, crosshatch, dots, focus, etc.
 - * VHF/UHF Channels.
 - * 5.5MHz, 6.0MHz, 6.5MHz Sound Carriers.
 - * Internal/External Sound.
 - * External Video Output.
 - * Trigger Output.
 - * PAL B,D,G,H,I,K.
 - * Separate R, G, B and sync. O/P's.
 - * RGB @ TTL & 1V.
 - * Green - 0.3V Syncs.
 - * Composite Video Output.
 - * Variable RF/Video Output.
 - * Switchable Video Polarity.
 - * Mains powered 220/240V AC 50/60Hz.
 - * Size: 98 x 219 x 240mm.

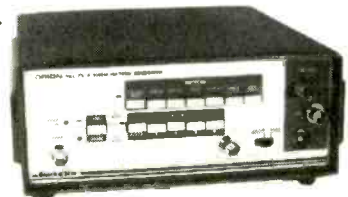


Price £229.00 + £40.08 V.A.T.

U.K. POST PAID, export enquiries welcome. Visa/Access or cheque with order, payable B. K. Electronics. Official Orders welcome from Govt. Depts., colleges, P.L.C.s etc. Large (A5) S.A.E. for technical leaflets of complete range. Credit card orders are accepted by phone, fax or post. Delivery normally within seven days.




B. K. ELECTRONICS
UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA
ESSEX S52 6TR
Tel.: 0702 - 527572 Fax: 0702 - 420243

PHILIPS STU901 D2MAC + PAL

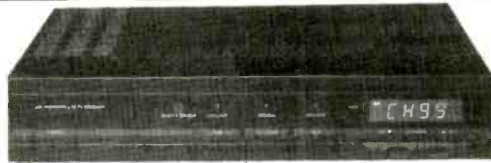

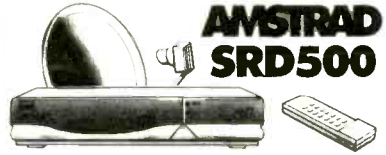★ The JSR3300 is a multi-satellite receiver which comes with a dish drive unit



AMSTRAD SRD500



E.E.C.



DISCUS SATELLITES



MONTEREY 40



ECHOSTAR 5500

THE NEW POWERMID



USE YOUR EXISTING REMOTE CONTROLS TO OPERATE YOUR

TV, VIDEO, HI-FI OR SATELLITE FROM ANYWHERE IN YOUR HOME

PACE SS 9200 IRD



90 CHANNEL * INBUILT VIDEOCRYPT * WEGENER STEREO * VCR TIMER * ON SCREEN GRAPHICS * 3 X SCART * COMPACT LNB * MESH DISH

AMSTRAD SRD 600 MAC



* 99 CHANNEL * INBUILT VIDEOCRYPT * INBUILT EUROCRYPT * DUAL LNB * PAL * MAC * MESH DISH

D² MAC DECODERS

★ NOKIA 2200 PAL D/2 MAC RECEIVER ★ 2 SCAN SOCKETS ★ EUROCRYPT CARD READER ★ SHVS SOCKET ★ EXTRA DECODER LOOP THROUGH ★ 2x PHONO/AUDIO SOCKETS



**FREE VIDEOCRYPT WITH ALL MOTORIZED SYSTEMS
FREE INSTALL KIT WITH ALL FIXED SYSTEMS**



"ALL YOU NEED TO KNOW IS US"

E.E.C. SATELLITE SERVICES



0702-471321 SALES HOTLINES 0702-480169

1426 LONDON ROAD, LEIGH-ON-SEA, ESSEX SS9 2UL



ACCESSORIES

POWERMID + PACE VIDEOCRYPT + SCART LEADS + PHONO LEADS + GLOBAL SWITCHES + DIPLEXERS + FACE PLATES + BT21 SCART SWITCH BOXES + INSTALLATION KITS + DISHES + REFURBISHED AMSTRAD RECEIVERS + REFURBISHED DECODERS + UNIVERSAL REMOTES + SINGLE BAND/DUAL BAND/TRIPLE BAND LNB'S + SWEDISH MICROWAVE LNB'S + HEMPT

SKY CARDS IN STOCK

STOP PRESS PHILIPS STU901 ONLY £549.00 INC V.A.T.

TRADE ENQUIRIES WELCOME

ELC EAST LONDON COMPONENTS		AUDIO TELEVISION VIDEO		COMPONENTS AT VERY KEEN PRICES		TEL: 081-472 4871 FAX: 081-503 5926	
REMOTE CONTROLS FROM £9.99 VIDEO BELT KITS							
IDLER TYRES 50p							
VIDEO HEADS FROM £6.99							
Over 200 models at very attractive prices:							
AKAI, AMSTRAD, FERGUSON, FISHER, GOLDSTAR, HINARI, HITACHI, LOGI, MATSUI, ORION, PANASONIC, SAISHO, SHARP AND MANY MORE							
VIDEO SPARES							
3V29 TAKE UP IDLER	£1.00	FISHER	FAH615/725	£1.00			
3V29 F.F. REW IDLER	£2.60	FISHER	FVH 905/910	£1.00			
3V59/65 FV10/14 IDLER	£1.50						
3V23 LOADING ROLLER BAR	£3.99	SANYO	VAH1300	£2.15p			
SHARP 0005 & 0006	£1.95	VHR3300		£2.05p			
SHARP V0651 ASSEMBLY	£6.99						
VT11/14/17 IDLER	£1.95	AKAI	HA1394				
VT11 CLUTCH ASSEMBLY	£6.99	VS2.5FG		£1.00p			
VT100/225/260 IDLER	£2.75p	VS105/250		£6.99p			
NFC 9013 IDLER	£4.99	GRUNDIG					
SANYO VHR3300 IDLER	£3.99	VS180		£1.45p			
AKAI VS105/250 CLUTCH ASSEMBLY	£11.99	VS300		£1.90p			
SAISHO VR380 CLUTCH	£4.99	VS380		£1.75p			
MITSUBISHI HS337 F.F. IDLER	£2.70p	HINARI	HA13108				
ALBA SENTRY PULLEY	£1.35p	HA13118		£1.25p			
MATSUI LIMITER POST	£1.25p	VXL3-20		£1.50p			
PANASONIC NV370 IDLER	£1.95p	VXL4-35					
FISHER 615 IDLER	£3.50p	MITSUBISHI	HA14400				
FISHER GEAR ASSEMBLY	£4.50p	HA4445		£2.50p			
AMSTRAD PINCH WHEEL MOO KIT	£5.99p	LA4460		£1.60p			
UNIVERSAL TRIPLER	£4.99p	LA4461		£1.60p			
UNIVERSAL TRIPPER WITH FOCUS	£7.99p	VC381		£1.00p			
HITACHI MODULE HM6251	£5.99p	VC9300		£1.50p			
TENSION BAND FOR MOST MOD. FROM	£1.99p	TV L.O.P.T.					
CIRCUIT PROTECTOR ICP	80p	TKXU White		£18.99p			
TK10 FOCUS UNIT	£7.99p	TK100 Green		£17.99p			
PHILIPS BACK-UP BATTERY	£1.50p	HINARI 4.5		£16.99p			
ALBA SWITCHER 11.5 SV	£2.50p	FIDELITY 20		£12.99p			
TV SWITCHER FOR MOST MODELS FROM	£1.00p	HITACHI		£19.99p			
SONY FUNCTION SWITCH	£1.00p	KV2704.5		£22.99p			
SCART TO SCART LEAD	£3.99p	KV2752		£22.99p			

◀ INFRA-RED DETECTOR ▶

Magic Mirror

◀ INFRA-RED DETECTOR ▶

IR 1 STANDARD SIZE MIRROR

IR 5 CREDIT CARD SIZE

IR 2 SPATULA MIRROR

IR 6 KEY FOB

ALL ONE PRICE £9.00 inclusive of VAT FREE POST & PACKING

OR ANY TWO for £16 including VAT OR ANY THREE FOR £20 including VAT

DISCOUNTS CONSIDERED ON OTHER QUANTITIES. RING FOR DETAILS.

Electronic Consultant Services

6 NETHERSOLE STREET, POLESWORTH, TAMWORTH. B78 1EE
Phone: (0827) 330392; Fax: (0827) 331041

EXPORT ENQUIRIES INVITED

104 ABBEY STREET ACCRINGTON, LANCs BB5 1EE
☎ 0254 236521/232611
FAX 0254 395361
24 Hr Answering Service

SMILE ITS SUMMER
SEND LARGE S.A.E. FOR TRADE CATALOGUE

ONE OF THE LONGEST ESTABLISHED MAIL ORDER SUPPLIERS. WE CONTINUE TO GIVE FAST, FAIR AND EFFICIENT SERVICE. WE HAVE STOCKS OF

- ★ TELEVISION COMPONENTS
- ★ VIDEO COMPONENTS
- ★ REMOTE CONTROLS
- ★ CABLES, LEADS, PLUGS etc
- ★ AERIALS AND ACCESSORIES
- ★ HOME SECURITY PRODUCTS

STOP PRESS:- NOW IN STOCK AMSTRAD FX6000AT FAX MACHINE WITH ANSWERPHONE £485 + VAT

TRUST US!!
(ASK FOR FULL BROCHURE)

BRAND NEW TV'S + VIDEOS

e.g. 14" REMOTE CONTROL TV	£125 + VAT
TWIN SPEED R/C VIDEO REC	£174 + VAT
10" MAINS/BATT CTV R/C	£140 + VAT
21" MULTISYSTEM R/C TV	£222 + VAT


AND NOW SATELLITE SYSTEMS

WE HAVE A FULL RANGE OF FIXED AND MOTORISED SYSTEMS. ASK FOR FULL LIST AT TRADE PRICES — INCLUDES LNB'S, DISHES, MOUNTS, RECEIVERS, ACTUATORS, POLARISERS etc.

e.g. AMSTRAD SRD 600 (D2 MAC)	£319 + VAT
PACE SS920 (D2 MAC)	£245 + VAT
1.2db LNB	£45 + VAT
RG6 CABLE (100M)	£24.95 + VAT

CALLERS WELCOME AT TRADE COUNTER

MON-FRI 9-5pm
SAT 9-4pm

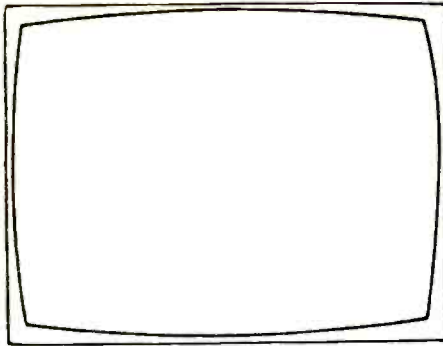

TELEVISION

EDITOR

John A. Reddihough

EDITORIAL ASSISTANT

Tessa Winford

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 617 or faxed to 081-652 8956.

ADVERTISEMENT MANAGER

Jan Thorpe
081-652 8114

SALES MANAGER

Shona Finnie
081-652 8115

CLASSIFIED SALES EXECUTIVE

Pat Bunce
081-652 8339
Fax 081-652 8931

ADVERTISING ADMINISTRATION

Kathy Lambert
081-652 8116

ADVERTISING PRODUCTION

Brian Chapman
081-652 8681
Fax 081-652 8917

PUBLISHER

Robert Marcus
081-652 3930

READER HELPLINE

For help if you have difficulty obtaining *Television* phone 081-652 8620

SUBSCRIPTION ENQUIRIES

0444 440 421

SUBSCRIPTION HOTLINE

24-hour subscription ordering with credit card number phone 0789-200 255

COVER PHOTO

This month's cover photograph shows the Tatung 160 chassis. See servicing article on pages 634-9.

First Fruit

Consumer electronics markets are doing poorly worldwide. This is partly due to recessionary economic conditions and partly due to market saturation. The latter may be cured by the introduction of innovative new products; that's the hope, anyway. Leading Japanese manufacturers have been reporting poor results. Matsushita has announced a pre-tax profit fall of 39 per cent during its last trading year while Sony, despite a 5.7 per cent increase in sales, recorded a pre-tax profit fall of 44.1 per cent and its first loss since being listed on the Tokyo Stock Exchange in 1958. JVC reported its first loss in four decades, Hitachi recorded a pre-tax profit fall of 37.4 per cent and Pioneer a pre-tax profit fall of 13.4 per cent. Many of these companies envisage no improvement in trading conditions during the present year. Matsushita says that the Japanese consumer electronics market has been flat for five years now: according to Hitachi there has been a two-year downturn in the domestic AV market. There are hopes that new products – CD-I, DCC, the Mini Disc, multimedia devices and so on – will lead to a revival. But it will take a time for consumers to respond to these new offerings.

Some years ago Japanese consumer electronics companies jumped into semiconductor device manufacture as a way of spreading their interests. All that this seems to have done is to increase competition and reduce profitability in tight markets. Possible ways forward were outlined by Toshiba in an interesting presentation on new uses for microelectronics. These include new memory technology to replace the use of hard discs, multiplex wiring arrangements for cars, "neuron" chips for networking in buildings, using mains electricity lines, processor-controlled smart cards and signal compression/expansion technology for use in multimedia devices, HDTV receivers and digital VCRs. Interesting that Toshiba sees a move to the lower operating voltage of 3V for microelectronics.

Although R and D expenditure is being cut back, progress continues to be announced by Japanese consumer electronics manufacturers. Despite disappointing sales the cost of HDTV sets for the Japanese MUSE system continues to fall. Toshiba has just introduced a 36in. model that sells for the equivalent of about £10,500. Sharp recently announced a set to sell at the remarkably low figure of about £4,500 equivalent. It's not clear whether there is a significant performance difference between these sets. But the major hope for the future of the consumer electronics market lies with multimedia devices that combine computer with other technologies. In this connection it was significant that Apple Computer was able to show a prototype of its new "digital personal assistant", the Apple Newton, at the recent Chicago Consumer Electronics Show. It's the result of collaboration between Apple and Sharp.

As with other things from Apple, operation of Newton depends on icons that are printed on the screen. You use a pen to write on the screen, using the device like a note pad – there are no buttons except for the on/off switch. The prototype measured about 7 x 4½ x 1in., the screen being 5 x 3in. You can write words or draw sketches on the screen, though you can't at present use joined-up writing – this is being worked on. Even so the handwriting recognition programme is sophisticated and has already won acclaim. It can handle rough sketches and will make them symmetrical: a rough circle for example can be automatically rounded and centred. Speech recognition will be added to later Newton products. Newton stores what you tell it, filing information in appropriate places to give easy access when required. It has for example an electronic calendar for appointments. The exact specification for the initial models has not yet been finalised and will depend on the price, which is likely to be in the £275-£400 range.

A major feature of Newton is that it can communicate via fax, telephone or a computer network. Early models will use an IR system to exchange data with a computer over short distances. At a later date Apple envisages incorporating radio facilities for communication over longer distances.

Software support will be required. An example given by Apple describes the use of Newton to help with a visit to Paris. Newton could obtain information such as a Metro map, a phrase book or a guide to well-known places by phone. Using the pen to point to a station on the Metro map would tell you how to get there while Newton could translate items written on its screen.

Newton uses a RISC microprocessor designed in the UK by Advanced Risc Machines. Flash memory cards that can store up to 20Mbytes of data are used – they are similar in size to a credit card.

There is a possibility that Newton will be available in the UK some time next year, at around £300. Competition could put in an appearance quite soon: Tandy announced at the Chicago Consumer Electronics Show that it will be developing and producing personal information devices in conjunction with Casio. There could be standards battles of the type we've seen in the computer and video fields. To get its Newton technology established, Apple is prepared to license other manufacturers – in fact Apple expects royalties to contribute a significant proportion of its Newton revenue within a few years. The company expects the multimedia device market to be around \$315 million million a year by the start of the next decade.

The concept of a product that combines computer and communications technology to provide information services and entertainment is attractive and it seems that getting such products to the market at reasonable prices will be no great problem. Maybe by the time that consumers have got over their present debt burden and reluctance to spend they will be ready for it.



A Scart Switcher Unit

Keith Wevill, B. Sc.

My brother recently moved house. To celebrate he bought a new all-singing, all-dancing Nicam stereo TV set and VCR with remote control units that would not look out of place on the flight deck of Concorde. The previous owners of the house had left a complete satellite TV receiver, which must say something about the quality of the programmes, so he had the problem of connecting these three units together. He also wanted to be able to watch the output from the satellite TV receiver or the VCR in another room without interfering with the use of the main TV receiver.

The initial arrangement he adopted is shown in Fig. 1. It's probably the most common arrangement for a TV set, a VCR and a satellite TV tuner. The input from the u.h.f. aerial is passed to the TV receiver via the satellite TV tuner and the VCR. The VCR is tuned to the satellite receiver's u.h.f. output so that satellite TV programmes can be recorded, the TV set being tuned to the satellite receiver and the VCR on separate channels.


This worked but didn't allow the outputs from the VCR and the satellite tuner to be heard in stereo or the satellite tuner's output to be recorded in stereo. There was also some interference due to interaction between the two u.h.f. modulators and it was difficult to tune the TV set. These modern tuning systems have a lot to answer for – and complex instructions.

A splitter in the u.h.f. feed to the main TV set enables a second TV receiver to be connected. This will give only mono sound from the VCR and the satellite TV tuner, which was considered to be perfectly acceptable.

The interference was minimised by retuning the VCR's modulator to about ch. 31, but this still didn't permit the output from the VCR or the satellite TV tuner to be heard in stereo.

All the units have scart connectors however, so the obvious thing to do was to connect them all together using scart cables. This brought a new problem: the TV set has only one scart connector. Initially we connected the VCR to the TV set via a scart cable, leaving the satellite TV signal at u.h.f. The result was an instant and dramatic improvement in the picture quality from the VCR, with stereo sound. But there was only mono sound from the satellite TV tuner and, as before, the VCR recorded only mono sound from the satellite tuner. The simple answer to this was to move the scart cable between the TV set, VCR and satellite tuner as required. But scart connectors aren't designed for repeated plugging in and unplugging, especially by my brother. A more elegant solution was thus required and the scart switch was born.

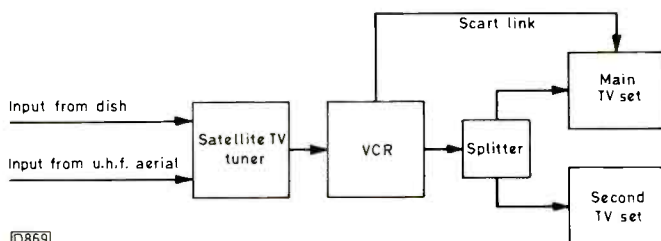The basic requirements of the switch unit were to provide switching between the outputs from the VCR and the satellite



D859

Fig. 1: Usual method of connecting a satellite TV receiver, VCR and TV set, with optional scart link and splitter to add a second TV set.

TV tuner, with the VCR having priority, and to enable the VCR to record the satellite tuner's output. The requirement to be able to watch the output from the VCR or satellite tuner on a second TV set without affecting the use of the main TV set made the control logic more complex, but the final solution permits either automatic or manual control of the source switching for the main TV set.

Fig. 2 shows a block diagram of the switch. The video signals from the VCR and the satellite TV tuner are buffered before being fed into the video switch, whose output is buffered before being fed to the TV set. The satellite TV

Components list

Resistors:

R1	75Ω	R17	75Ω	R33	47k
R2	4.7k	R18	3.3k	R34	47k
R3	4.7k	R19	1k	R35	470k
R4	3.3k	R20	5.6k	R36	47k
R5	1k	R21	10k	R37	47k
R6	5.6k	R22	1k	R38	470k
R7	10k	R23	3.3k	R39	10k
R8	1k	R24	100Ω	R40	10k
R9	3.3k	R25	1k	R41	10k
R10	100Ω	R26	1.2k	R42	10k
R11	1k	R27	100Ω	R43	10k
R12	1.2k	R28	270Ω	R44	100k
R13	100Ω	R29	75Ω	R45	100k
R14	270Ω	R30	10k	R46	100k
R15	75Ω	R31	47k	R47	2.2k
R16	10k	R32	47k	R48	10k

Capacitors:

C1	33μF, 16V	C10	220nF
C2	47μF, 16V	C11	220nF
C3	47μF, 16V	C12	2.2μF, 16V
C4	10μF, 16V	C13	2.2μF, 16V
C5	100nF	C14	220nF
C6	220μF, 16V	C15	220nF
C7	33μF, 16V	C16	2.2μF, 16V
C8	47μF, 16V	C17	2.2μF, 16V
C9	220μF, 16V		

Semiconductor devices:

D1-6	N4148	Tr5	BC337
IC1	4053	Tr6-8	BC548
IC2	TL084	Tr9	BC558
IC3	4081	Tr10	BC337
Tr1-3	BC548	Tr11	BC548
Tr4	BC558		

Hardware:

S1	One-pole, four-way switch
SK1-3	Scart sockets

HENRY'S
EXCITING
SPECIAL OFFERS!!

BIG, BIG SAVINGS
HURRY LIMITED STOCKS

DM301
19 range
3 1/2 digit mm

FEATURES: Pocket Dmm with 12mm display AC/DC volts 6 ranges DC current to 10 amps 5 resistance ranges Diode test With leads, battery & instructions

ONLY £10.95
UK post etc £2.00
Post free when you Buy Two!

TL3400
31 range 3 1/2 digit mm with 25mm Large Display
FEATURES: 2 Capacitance ranges AC/DC volts AC/DC current to 20 amps 6 resistance ranges to 40M ohm Diode test Continuity test Logic checker with buzzer Auto range frequency counter Peak hold button Temperature test

ONLY £39.95
(Temp probe option extra)
UK post etc £2.00
Post free when you Buy Two!

TL34
33 Range 3 1/2 digit mm
24mm Large Display
FEATURES: 5 Capacitance ranges 6 resistance ranges to 20M ohm Diode and transistor test AC/DC volts ranges 5 ranges AC/DC current to 20 amps With leads, battery and instructions

£25.95
UK post etc £2.00
Post free when you Buy Two!

Instrument stockists for: ■ Hameg Scopes
■ Black Star ■ Thurlby ■ Thandar ■ Test Lab
Always special offers for callers.

Brand new ASTEC SW mode power supply
Three pin mains socket input, on/off switch
Output: +5 volt 3.75 amp, +12 volt 1.5 amp
-12 volt 0.4 amp 115-230 VAC Input Size
7.0 x 5.3 x 2.5 ins with circuit

ONLY £12.95 (UK Corr etc £2.05)
Carr paid when you Buy Two!

COLOUR CATALOGUE
WITH SUPPLEMENTS
SEND SAE FOR CHQ
Callers £2.00
FREE to
Trade/Education
(Write for Fax)

OPEN 6 DAYS A WEEK FOR CALLERS OR TELEPHONE ORDERS

ALL PRICES INCLUDE UK VAT

SPEAKERS FOR PA, DISCO AND HIGH POWER CAR SYSTEMS

All models available 4 ohms or 8 ohms
10" 150 watt (250w Max) H/D Boss. Huge £29.95
Magnet £15.95
8" 75 watt Boss/mid vented coil £22.95
12" 90/120 watt Boss/mid vented coil £22.95
12" 400 watt (800w max) H/D Boss Huge £89.95
12" Magnet £82.95
15" 250 watt (400w max) H/D Boss Huge £82.95
Carr/pack/ins extra

LARGE RANGE OF AMPLIFIERS, GRAPHICS, SPEAKERS AND SYSTEMS IN STOCK FOR PUBLIC ADDRESS - DISCO AND IN-CAR

HENRY'S AUDIO ELECTRONICS
404 EDGWARE ROAD, LONDON W2 1ED
Tel: 071-724 3564/071-258 1831 Fax: 071-724 0322
DISCOUNTS FOR QUANTITY AND EDUCATIONAL

SONY TUBES RE-PROCESSED WITH ORIGINAL SONY GUNS

HIGH TEMPERATURE RE-PROCESSING of Sony, Mullard 45AX, 30AX, in-line, PiL, Mini (22.5) Neck and FST Tubes.

3702B22 £48.00	A51-231X ITT £46.00	A51EAL00X Philips £58.00
370KRB22 Toshiba £48.00	A51-570X Mullard £46.00	A51EBS00X £58.00
370LHB22 Hitachi £48.00	A51-580X Mullard £46.00	A51JAR00X Toshiba £64.00
400FB22 Sony £58.00	A51-590X Mullard £46.00	A51JK00X Sony £74.00
510YB22 £58.00	A56-540X Mullard £48.00	A51JH10X Sony £74.00
520S822 Sony £64.00	A56-701X ITT £48.00	A53JBW00X Sony £64.00
560EB22 Hitachi £54.00	A66-540X Mullard £56.00	A59EAK00X Philips £64.00
560YB22 £54.00	A67-701X ITT £56.00	A64JK10X Sony £95.00
570HB22 Sony £64.00	A34EAC00X Philips £48.00	A68JMT10X Sony £95.00
680DB22 Sony £85.00	A34JBU10X Sony £64.00	A68JYK10X Sony £95.00
680EB22 Sony £85.00	A44JEX10X Sony £78.00	AXM37-001 £48.00
	A44JF210X Sony £78.00	AXT37-001 £44.00
	A49JHT00X Sony £64.00	AXM51-001 £46.00
	A49JLV10X Sony £74.00	AXT56-001 £52.00

For tube types not listed please enquire
All Tubes Guaranteed 12 Months

All prices quoted are excluding VAT.
Exchange CRT is required.

Callers welcome.
Please phone first.
Nationwide Delivery Available.

Very low Delivery Charge for Deliveries within M25 Area

BRAND NEW TUBES AT COMPETITIVE PRICES WHILE STOCKS LAST

AXM37-001 A34EAC00X 3702B22 510SKB22 510UB22 510XC22 510YT22 510ZCB22
370LHB22 370KRB22 5108V22 510SLB22 510VHB22 510XTB22 510YUB22 A56-540X

D.I.Y. Television Tube Polishing Kit

Contains everything you need to Polish scratches and small chips on your CRT screens
All you require is an electric drill. Written instructions are provided. Guaranteed to work.
Worldwide Delivery Total Price £63.00 includes P&P and VAT Available from Luton only

Your local stockist are:

WEST ONE
Distributors Ltd.
Chesham, Bucks.
Tel. 0494 778197

WELL VIEW
114-134 Midland Road,
Luton, Beds, U.K. LU2 0BL.
Tel. 0582 402499

WELL VIEW
Southampton, Hants.
Tel. 0703 449783

EURAS SYSTEM

The largest Database of CD, TV and Video Repair Tips information in Europe
Available On-Line or in Books and now...

NEW STAND-ALONE PC VERSION

- Purchase the whole system or just one manufacturer
- It's fast and easy to use
- There are no hidden costs
- Updates available
- Suitable for any IBM compatible PC
- You can even enter all your own repair tips

"No more bits of paper"

STILL AVAILABLE:

The Books
or
The On-Line System

- 73,000 Repair Tips
- 5,300 Models
- 180 Manufacturers

Tel:
0272 724475
Fax:
0272 723374

Euras International Limited
Heston House, 79 Emery Rd,
Brislington, Bristol BS4 5PF,
England

AIWA
AKAI
ALBA
AMSTRAD
ARISTON
ARISTONA
B & O
BAUER
BOSCH
BRANDT
BLAUPUNKT
BUSH
CANON
CHINON
DECCA
DUAL
FERGUSON
FIDELITY
FISHER
FUNAI
GEC
GRAFTZ
GRUNDIG
HANSEATIC
HITACHI
INTERFUNK
ITT
JVC
KENDO
KENWOOD
LOEWE
MARANTZ
MATSUI
METZ
MITSUBISHI
NEC
NECKERMAN
NOVA
NORDMENDE
ORION
PANASONIC
PHILIPS
PIONEER
PYE
QUELLA
QUELLE
SABA
SAMSUNG
SANYO
SCHNEIDER
SHARP
SIEMENS
SONY
TATUNG
TELEFUNKEN
THOMSON
THORN
TENSAI
TOSHIBA
TELERENT
UHER
UNIVERSUM

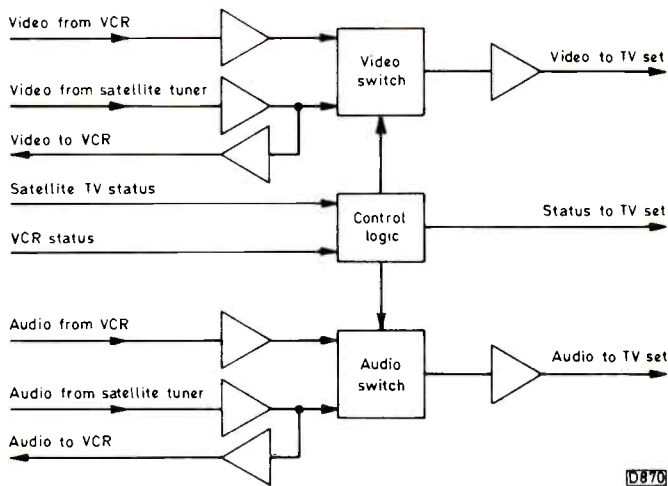


Fig. 2: Block diagram of the scart switcher unit. The audio inputs and outputs are in practice in L/R form.

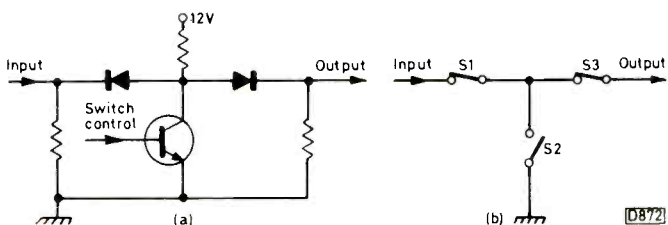


Fig. 3: Operation of the discrete component video switches. (a) Circuit arrangement; (b) equivalent mechanical switch system.

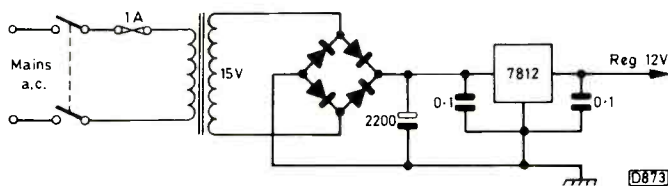


Fig. 4: Suitable power supply. Transformer rating 10VA.

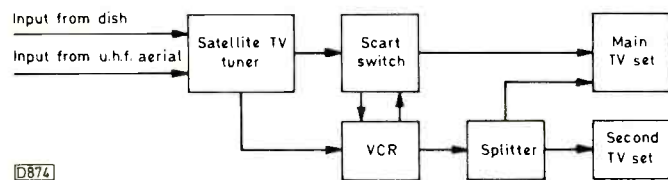


Fig. 5: Block diagram showing the connections to the scart switcher unit.

tuner's output is also buffered and fed to the VCR to enable it to be recorded (always assuming that this is worthwhile!). The control logic uses the source switching signal at pin 8 of the scart sockets or the mode switch to determine which input is passed to the TV set.

Switching Circuitry

Fig. 6 shows the circuit diagram of the scart switcher unit. Each video input is terminated by a 75Ω resistor and fed to an emitter-follower (Tr1 and Tr6) whose output is fed to a switch that consists of two series diodes (D1/2 and D3/4) and a parallel transistor (Tr2 and Tr7). Fig. 3 shows how the diodes and transistor are arranged and the equivalent circuit. When the transistor is off the two diodes are forward biased, which is equivalent to S1 and S3 being closed and S2 being open. Thus the video signal passes through to the TV output

buffer amplifier (Tr3-5). When the transistor is switched on however the diodes are reverse biased, which is equivalent to S1 and S3 being open and S2 closed, and no signals can pass through. This form of switch, with both series and parallel elements, provides excellent isolation in the off state with virtually no breakthrough of the unwanted signal.

The outputs from the switches are buffered before being fed to the TV CVBS output socket SK3. The output buffer amplifier has a gain of two which, with the 75Ω output resistor, gives an output of 1V into 75Ω for an input of 1V. An identical output buffer amplifier (Tr8-10) is used to feed the satellite TV signal to the VCR socket SK1.

Two sections of a 4053 triple analogue switch (IC1) are used to select the VCR or satellite TV left and right channels. The third switch in this i.c. is used to control the switch transistors Tr2/7 by earthing the base of one of them. The outputs from the switch are buffered by two sections of IC2 and fed to the audio outputs of TV socket SK3. The satellite TV audio signals are also buffered before being fed to the VCR socket SK1.

Control System

The control circuit uses three gates of a 4081 CMOS and gate (IC3) and has four modes of operation, automatic, TV, VCR and satellite, which control the state of SK3's status pin. In the automatic mode, if either the satellite or VCR status input is high the output status is high, switching the TV set over to its scart input, and the video and audio outputs from the switches come from whichever input, satellite or VCR, has its status pin high. In the event of both status inputs being high the VCR has priority, as the video and audio switches are both controlled by the VCR status signal. In the TV mode the output status pin is held low irrespective of the state of the satellite or VCR input status, enabling the satellite receiver and VCR to operate independently of the TV set.

When the VCR or satellite mode is selected only the VCR or satellite receiver respectively can switch the status pin. These modes permit remote viewing of the VCR or satellite TV receiver via the u.h.f. cable without affecting the off-air viewing via the main TV set. They also allow the VCR's output to be viewed via the main TV set while the satellite receiver's output is being viewed via the second TV set by switching S1 to VCR and vice versa by switching to satellite. This facility can be removed if not required. In this case delete IC3 and link together pins 4 and 5, 1 and 3 and 8 and 10.

The audio and video switches are controlled by the VCR status input signal via one of the and gates: when the signal is high, the VCR input is selected. Controlling the switch in this way ensures that the VCR has priority over the satellite receiver and that when the mode switch is set to satellite the audio and video switches are set to select the satellite inputs irrespective of the state of the VCR status input.

Miscellaneous Points

Construction is not unduly critical. The circuit can be built on Veroboard or a similar universal PCB. Keep all lead lengths short, especially around the video amplifiers, and use sockets for the two CMOS i.c.s. These i.c.s should be inserted after all the other components have been fitted.

The circuit requires a 12V supply. Fig. 4 shows a suitable circuit using a 7812 regulator which should be mounted on a heatsink.

No details of the case are given. Individual constructors can choose a case to suit their own requirements, bearing in mind that three scart connectors need to be fitted.

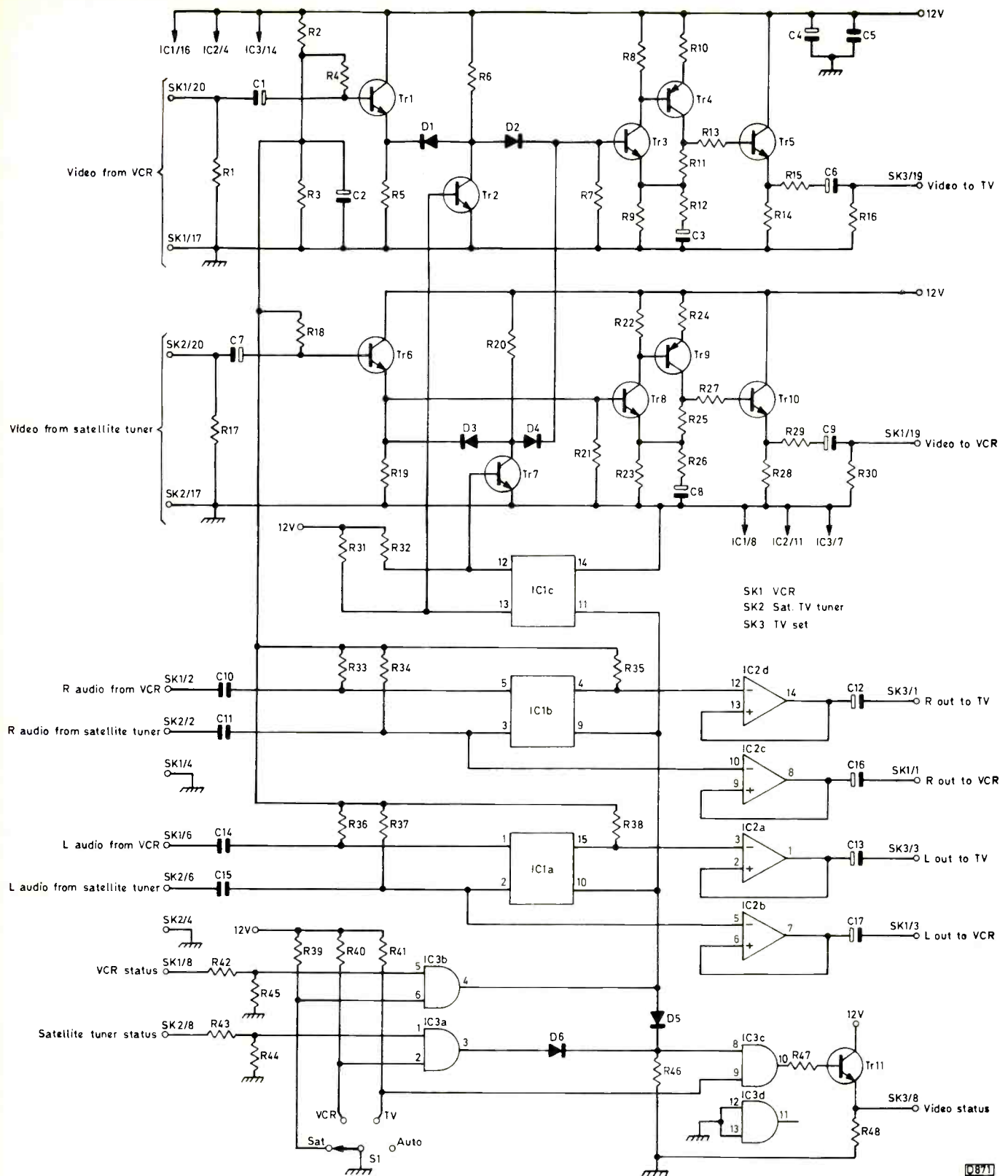


Fig. 6: Circuit diagram of the scart switcher unit.

The final arrangement of the TV sets, the VCR, the satellite TV tuner and the scart switch is shown in Fig.5. If the u.f.f. signal strength is low or noise is evident on the picture it may be necessary to add an amplifier to boost the signal level before splitting it to feed the second or even a third TV receiver. When recording from the satellite TV tuner remember to select the line input from the VCR.

The scart switch could be used to connect two scart equipped VCRs to a TV set instead of a satellite receiver and a VCR. Alternatively a camera or computer could be connected. These arrangements would enable the TV set to mon-

itor the input while the input is being recorded by the VCR.

As it stands the circuit doesn't cater for RGB inputs. I hope to add this facility at a later date.

Finally some errors were introduced during the editorial preparation of my previous article (October 1991) that described a scart interface circuit. D6 and D9 were shown the wrong way round in Fig. 3: their cathodes go to the collector of Tr1. Tr5, type BC337, was omitted from the components list. With the Ferguson TX10 chassis the point at which to connect the i.f. disable input is at pin 5 of plug 4 (pin 9, as printed, is correct for the TX9 chassis).

Servicing the Tatung 160-180 Chassis

Eugene Trundle

Tatung has been manufacturing TV sets in the UK for over a decade now, having taken over the Decca operation in 1981. The first UK-produced Tatung sets used the very good Decca 120/130 series chassis, which had been designed in Bradford. They were followed by the 140 series chassis then the 160 series, the subject of the present article. The Research and Development Department moved to Telford in 1985 and went on to produce the 165/170/180 series chassis, which are also covered here. These chassis are only now being superseded by a new type. Throughout the development of the chassis mentioned above there has been continuous evolution. This is quite a contrast with the sudden and radical changes in TV design adopted by some manufacturers.

The 160 is a basic "live" chassis with manual operation (no remote control) designed to drive 90° picture tubes with screen sizes from 14 to 22in. Apart from that on the tube base panel all the circuitry is on a single PCB which carries the user controls at the front. Fig. 1 shows the basic arrangement in block diagram form. Potentiometers are used for channel selection, there's manual grey-scale setting and a simple audio channel. The main innovation at the time was the use of the TDA4503 chip which took the place of three or four earlier generation chips.

The 165 chassis is similar but incorporates remote control (RC60 system) and a more comprehensive control system based on an M491 chip. Features include voltage-synthesis tuning, digital channel readout and remote control of channel changing, volume and standby.

The 170 series chassis, introduced in early 1988, is again similar in construction and design but has an isolated power supply to enable a scart connector to be incorporated. It also has the more advanced RC70 remote-control system, with a 30-programme frequency-synthesis tuning system and search and memory facilities. With minor circuit variations it drives

90° tubes with screen sizes from 14 to 21in. Stereo sound and teletext can be fitted, the latter in CCU or Fastext form.

The 180 is a development from the 170 for use with 25 and 28in. tubes with 110° deflection. It differs mainly in the line scan drive section and the tube base panel circuitry.

The model number gives a great deal of information about the set. Brand is indicated by the first letter - T for Tatung, D for Deccacolour. The second letter indicates the screen size in inches as follows: N 14; O 15; P 16; T 20; U 21; V 22; Y 25; Z 26; B 28. Next comes the first digit: 1 indicates non-remote control, 8 remote control and 9 teletext. The second digit is used for chassis designation: 6 for 160 series, 7 170 series, 8 180 series. The remaining digits are styling numbers, giving no useful engineering information. The later 170/180 series chassis sets have a third prefix letter to denote the following features: Q FS tube; S pseudo or playback stereo and scart socket; T Secam and scart; U Secam only; V scart only; X German broadcast stereo, scart and Secam. Before home entertainment gear all went charcoal grey the suffix letter gave information on cabinet colour: R rosewood; T teak; W walnut; A alternative. As an example of all this, Model TBS9816 is a 28in. Tatung set with teletext and stereo, using the 180 chassis.

Fault History

Most of our experience has been gained with the 160/165 series chassis. In general therefore our comments relate to them, though many are relevant to the 170/180 series chassis. In the latter case you'll have to bear in mind that component reference numbers may differ from those given here. Where a common fault relates to a specific chassis this will be stated.

We'll start with the construction and physical characteristics. The controls at the front of manual sets (160 chassis)

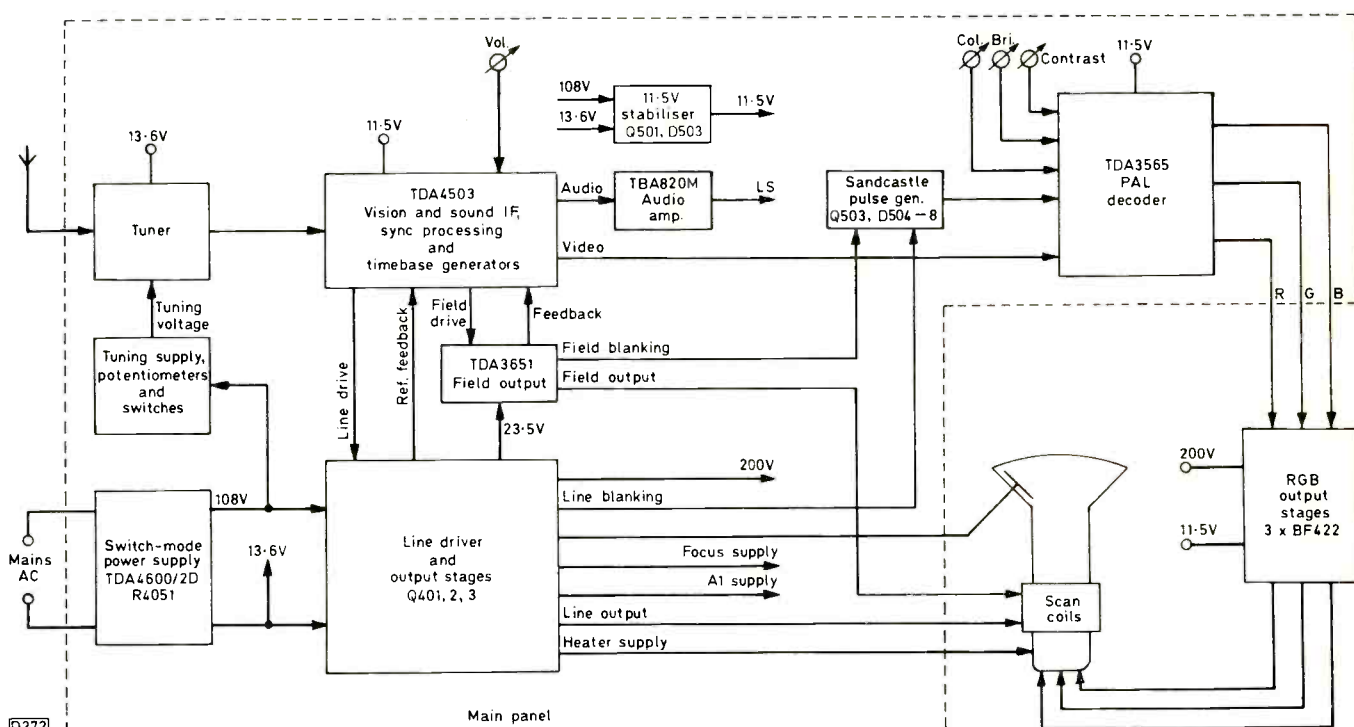


Fig. 1: Block diagram of the 160 series chassis. The 165 is similar, with the addition of remote control.

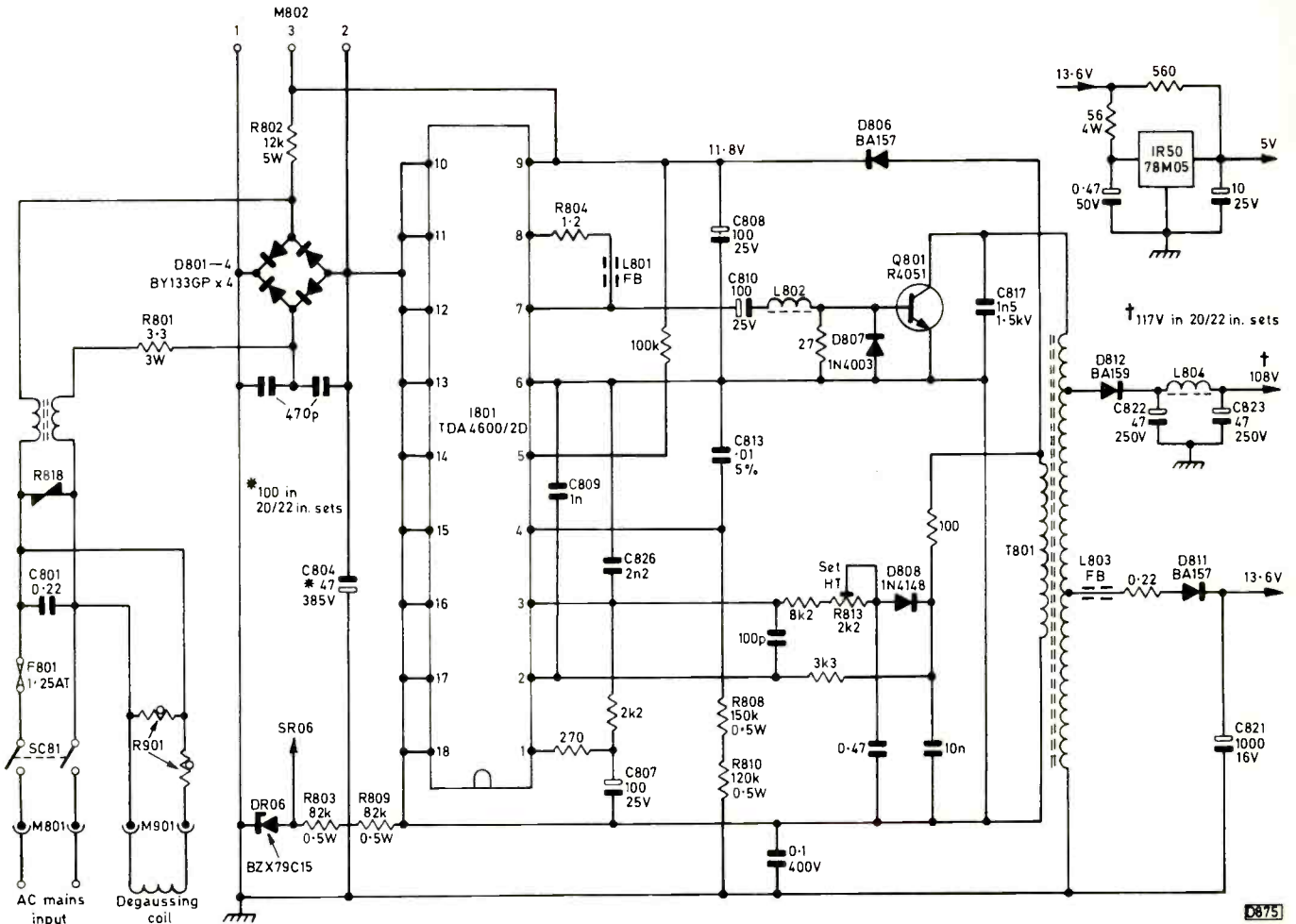


Fig. 2: The switch-mode power supply circuit used in the 160/165 series chassis. DR06, R803 and R809 are omitted in the 160 chassis sets. I801 pin functions are as follows: 1 4V reference output; 2 waveform crossover point sensing; 3 feedback voltage input; 4 chopper transistor collector current simulation; 5 undervoltage sensing; 6 0V; 7 Q801 switch off; 8 Q801 switch on; 9 11.8V supply; 10-18 0V.

break off very easily, necessitating replacement of the potentiometer and knob, which is usually lost. With these sets the station-selector buttons tend to become noisy and intermittent. If the tuner buttons are all pushed in simultaneously (this usually occurs when the set is being carried) they can be released by pushing the flat-blade end of the tuning tool or a small screwdriver into the little hole at the right of the switch-bank and rotating it. This trips the latching bar, releasing the buttons.

In later, large-screen models the front cabinet feet often break off, leaving the set dangerously unstable if it's not stand-mounted. Front flaps and doors tend to be shed easily due to the flimsy plastic fixings. Replacements come without labels and badges. Order these separately if you can't transfer the old one(s). The front glass retaining strip on early monitor-style sets can become statically charged: a resistive earthing lead, part number 05-3312-2, was added during production and can be fitted in older sets if necessary.

When refitting the 165 chassis ensure that the lens on the IR receiver doesn't foul the cabinet - if force is used, something will be broken! The IR filter can be removed by releasing the clips inside the cabinet to enable the lens to be "steered" through the cabinet front. Refit the filter after doing this. Leaving the filter out reduces the sensitivity in remote-controlled sets. Some early 170/180 chassis panels tended to slide backwards in use to the point where the mains on/off switch wouldn't latch: this was due to inaccuracy in drilling the securing-clip fixing hole at the rear.

In the 160/165 chassis there's a tendency for dry-joints to develop on all the electrical components heatsinked on the

rear metal wall: this is a rife source of trouble in the power supply and timebase departments. The 170/180 chassis don't suffer in this way but bad joints between mother and daughter boards are very common, giving rise to all sorts of intermittent symptoms. The most common sufferers are the text board and the panel that carries the scart connector. To ensure good contact it's necessary to clean inside the sockets of the connectors. In chassis where the customer controls are on a front daughter board user pressure generally leads to dry-joints with the mother board. The main panel becomes very discoloured at half a dozen different points beneath hot-running components in the 170/180 chassis. No carbonisation has set in so far but we've had to replace at least two 180 panels with holes burnt in them due to arcing at a dry-jointed capacitor, C433, alongside the line output transformer. It's worth checking the connections to this capacitor on every 180 chassis you come across.

When servicing Tatung sets it's a good idea to have a spare mains lead complete with flying-socket PCB termination. This saves straining or breaking the cable retaining strap in the cabinet and ensures that you don't forget to replace it after carrying out the repair.

The Chopper Circuit

These models all have a switch-mode power supply fed from a full-wave mains rectifier. The 160/165 chassis use a TDA4600/2D chopper control chip with an R4051 chopper transistor and non-isolating transformer. The circuit is shown in Fig. 2. A basically similar arrangement is used in the

170/180 chassis, but the chip is type TDA4601, the transistor is type S2000AF and the transformer provides mains isolation.

The failings and foibles of power supplies that use the TDA4600 family of control chips have been covered in previous articles in these pages. J. LeJeune's article in the November 1991 issue is particularly well worthwhile reading.

For blowing the chopper transistor, failure to start or shut-down after a few minutes' operation, check the ramp generator resistors R808 and R810 (R813/814) – component reference numbers in brackets apply to the 170/180 chassis. A shorted chopper transistor generally takes the control chip with it. In this event the following items should also be replaced: C810 (C807), D807/8 (D806/7) and R804 (R805). Get the replacement from Tatung when you have to replace the chopper transistor Q801 in the 170/180 chassis: beefy and reliable transistors of Toshiba manufacture are supplied. This also applies with the line output transistor Q403.

A shattered mains input fuse F801 doesn't necessarily mean a disaster story in the chopper department – it's very common for the degaussing resistor R901 to go short-circuit. Replace it with the correct type obtained from Tatung. The mains filter capacitor C801 rarely fails. Some very early production sets were fitted with a fast 1A or 1AT mains fuse: replace it with a 1.25AT type and fit a label (part no. 83-2536-7) to show the new rating. Another cause of a blown mains fuse, with possibly damage to Q801 and its friends, is C817 (C813). This capacitor, which is in parallel with the chopper transistor, sometimes has a bulge in its plastic shell.

If the set is quiet and dead with the mains fuse intact the mains switch SC81 (SC801) may well be open-circuit internally. The surge limiter resistor R801 (R802) can do the same thing – sometimes there's a visible crack in its body. In this case check the rectifier diodes D801-4 as well. It's an odd fact that when lightning gets into the set, presumably via the mains lead, the chopper control chip I801 can be destroyed without any damage to other components.

You may come across a set that will come on after a remote-control command but not from the action of the mains on-off switch. Check the auxiliary (momentary) contact in the mains switch then, in the 165 chassis, R803 and R809. A disconcerting hiss during standby operation with the 165 chassis can be cured by replacing C826 with a series combination consisting of an 0.1 μ F capacitor and a 330 Ω resistor.

Incorrect power supply output voltage is not unknown! If the voltage is low the symptom may be no worse than foldover at the top of the picture. Check whether the track of the control potentiometer R813 (R808) has fallen in value, then check the resistors that lead back to pin 3 of I801. High output voltage, with the line output stage throbbing and bristling, can be the result of D808 (D807) going short-circuit or low-resistance.

Failure of the mains rectifier's reservoir capacitor C804 (C805) will put a raucous 100Hz ripple on the h.t. line, with the picture torn in three and a rasping buzz from the speaker.

The power supply is amenable to checks with a light-bulb load and being supplied via a variac.

The metal plate on the 170/180 chassis chopper transformer sometimes buzzes or squawks in operation. Reclamping it generally provides a cure. Another odd fault with early-production 170 chassis sets is interference to VCR-derived pictures from the power supply. It shows as bright white dots that move across the screen. The cure is to fit a mains filter, part no. 15-7636-2, in location Z801 on the main PCB after removing links J851 and J853.

Finally a fault whose cause may seem to be in the power supply but isn't! Sets fitted with the 160/165 chassis will go dead if the 12V supply fails due to breakdown of the little

stabiliser. Check Q501, D503, R507 and R508. The job is done by a three-legged chip, I802, in the 170-180 chassis. It also implements the standby function. Before condemning this item check for dry-joints at its legs and that the standby switch circuit consisting of Q802 etc. is in order.

Timebase Generator Section

The sync separator and timebase generators in these sets are very reliable. In early versions of the 160 chassis the value of R114 should be changed to 2.7k Ω to reduce flutter at the top of the picture, and for improved VCR operation R117 should be changed to 1.2k Ω and C111 to 0.22 μ F. The value of R106 can be increased to 150k Ω or 180k Ω to improve picture stability in the VCR search modes and, surprisingly, to reduce sound buzz with some VCR/TV combinations. Early 160 chassis that suffer from instability in the VCR trick modes benefit from the value of the tuner a.g.c. decoupling capacitor C004 being increased to 22 μ F.

In the 170/180 chassis I401 (TDA2759) can fail due to c.r.t. flashover. This generally removes the line drive.

Apart from the feed resistor R401 going open-circuit the line driver stage has never given us any problems. As with all sets however there are several things to talk about in the line output stage.

The Line Output Stage

Very common indeed is a short-circuit efficiency diode. It's D401, type BY133GP. Replace it with the more reliable BY228 or BY299. The line output transformer T402 can fail in either of two ways. It can develop internal shorted turns/leakage, putting a heavy load on the power supply which shuts down with a low purr or squeal. Alternatively, typically in the large-screen 180 chassis, it can fail spectacularly, with vivid blue sparks flying from its casing to the adjacent chassis bar. In the latter case check the tuning capacitor C405 (C421) for dry-joints or internal failure: dry-joints on this capacitor will sometimes make themselves known before any other failure occurs. Other dry-joint favourites in the 170/180 chassis are at D401 and C423, the symptom with the latter being a vertical white line down the centre of the screen. Dry-joints at C433 in the 180 chassis can cause severe burning of the PCB. Also confined to the 180 chassis is failure of D405, affecting picture width and EW pincushion correction. Apart from the line output transistor Q403 dry-joints are not so prevalent in the 160/165 chassis.

The thick-film focus and first anode potentiometers are mounted on a plastic moulding that's fixed to the back of the diode-split line output transformer. The first anode section sometimes fails, the result being fluctuating brightness. The potentiometer assembly is not available separately from Tatung. We have however successfully transplanted the controls from transformers that have failed in other ways, so don't throw away dead LOPTs! Because of the different chassis and tube type variations several different types of line output transformer are used: make sure that you order and fit the correct type for the set being repaired.

Occasionally one or other scan collapses intermittently to a line. In this event check for dry-joints at the soldered connections to the deflection coils.

Field Scanning

The field generator and output stages are in different chips. In the 160/165 chassis the drive is generated by the TDA4503 chip and then applied to the TDA3651 output chip which is on the rear panel. The 170/180 chassis have a

TDA2579 sync/timebase generator chip, the field output chip being a TDA3651 in the 170 chassis and a TDA3654 in the 180 chassis. In general the field timebase reliability is good. Bear in mind that most cases of field collapse result in the black-screen symptom, a protective measure to prevent tube damage – the action depends on the sandcastle pulse feed to the colour decoder chip. Turn up the first anode control to confirm that there's no field scan.

The most common cause of field collapse in the 160/165 chassis is dry-joints at the pins of the TDA3651 output chip I301. This can sometimes destroy the chip and take out the power supply surge limiter resistor R411. The value of this resistor varies in different models: replace like with like and for BEAB's sake get it from Tatung.

Also confined to the 160/165 chassis is a fault that results in picture roll as the set warms up. The three resistors R301/2/3 in the field hold network are usually responsible. Replace them all.

The field timebase is more reliable in the 170/180 chassis because the output chip's mounting position avoids dry-joints. All we've had with these sets is the odd failure of the output chip I301 and, apparently for internal reasons, of the fusible safety resistor R433, again resulting in picture tube cut-off.

Receiver Section

The tuner and i.f. sections of the 160/165 and 170/180 chassis are quite different, but neither of them give much trouble. For tuning drift or zero tuning voltage (stuck on ch. 21) check the 33V stabiliser I001 (I002) then if necessary its feed resistors R007/011 (R005/6). Failure of I001 in the 170/180 chassis can also stop the TDA/SAB3035 CITAC chip working. Replace the TAA550 stabiliser in the 160/165 chassis with the more reliable ZTK33B type.

The tuner itself is occasionally responsible for tuning drift or low gain. Ensure that the replacement is of the correct type: you may stock or buy types that look similar and will fit but give low gain or no results due to incompatibility. We seem to have more trouble with water coming down our customers' aerial leads. This can write off the "direct entry" tuners used in the 170/180 chassis or the rear-mounted isolator socket used in the 160/165 chassis.

We've had one or two failures of the a.g.c. decoupling capacitor C105 in the 170/180 chassis. This upsets tuner gain. Otherwise the i.f. department is very well behaved.

Video and RGB Departments

The 160/165 chassis, unsullied by text or auto grey-scale correction, has a very simple video section consisting of a TDA3565 chip and its peripheral components. These items give virtually no trouble. Failure of R518 in the line blanking circuit can give rise to strange colour and brightness effects by upsetting the sandcastle pulses. The TDA3562A chip used in the 170/180 chassis is not as reliable as the TDA3565: it can fail, typical symptoms being a blank white raster or no colour. Check the sandcastle pulse at pin 7 however before replacing it. If the picture brightness "pumps", check R523 at pin 18.

Low contrast faults can occur in all chassis, generally due to a defect in the beam-limiting department. Check zener diode D501, diode D502 and bleed resistor R408 in the 160/165 chassis. Their equivalents in the 170/180 chassis are D503 and R430. To replace the latter you have to remove the line output transformer! A very bright raster with flyback lines indicates that the supply to the RGB output stages has failed: check R201 and, in the 160/165 chassis, R410 which

is just behind the line output transformer.

R201 brings us to the tube base panel and a very common source of trouble with these sets, the multiway connector which links it to the main panel. If you get spasmodic fluctuations of either the brightness or individual colours check the contacts to the wire conductors, at both ends if necessary. In the later chassis types (mainly the 170/180 series) the set-background potentiometers sometimes become noisy: all that's required is a squirt of switch cleaner and movement to and fro.

In all except the 180 chassis the RGB output transistors' collector loads consist of three 47k Ω , 0.5W resistors connected in parallel. If one of these resistors goes open-circuit or changes value correct grey-scale cannot be achieved and suspicion may well fall on the tube... Check each resistor in the afflicted stage out-of-circuit. The little BF422 transistors never seem to fail, and apart from a couple of cases of flashover at the focus spark gap we've had no other problems on the tube base panel.

Tubes

The tubes fitted in Tatung TV sets are generally reliable and perform well: all we have to report here are a couple of cases of internal flashover/arcing in 14in. Toshiba tubes and a tendency, shared by many other makes and models, to "hot bulge" in the large, wide-angle tubes used in 180 chassis sets. The effect of this is local impurity in bright picture highlights, typically text displays. The cure is in the hands of the user: turn down the contrast or select another picture!

If you replace a picture tube minor modifications to the circuitry may be required to accommodate differences in tube base and scan yoke characteristics.

Teletext

Apart from occasional chip failure, which is not difficult to diagnose, the only problem we've encountered in the text section has been drop-out of one or other of the primary colours from the display. The cause has been poor contact between the text panel and the main board.

It's possible to convert a CCU text system to Fastext by replacing the text board, swapping IR01 (MAB8441P) over with one that has a 123 suffix, removing link JR03, adding link JR01 and fitting a new fascia panel to the remote control handset – but this is not recommended as a routine service job!

Audio Section

The sound quality is not good in the small-screen sets with very small loudspeakers, but this is common with little TV receivers. Some of our hard-of-hearing customers have dislocated the cones of these small speakers by running them at high volume continuously – the result is severe rattling and distortion.

Early production 160 chassis sets suffered from noisy and fierce volume control operation. This was cured by adding a 10 μ F capacitor across the track (negative side to chassis), changing R606 to 5.6k Ω and R607 to 560 Ω . An occasionally encountered fault is weak or non-existent sound with a vision buzz: check ceramic filter Z601, type SFE6.0. The audio output chip in mono-sound sets gives little trouble: to date we've had to replace only one.

The stereo-sound models in the 170/180 range have a separate a.f. PCB in the top right-hand corner of the cabinet, viewed from the rear. There are two versions, 5 + 5W and 15 + 15W, the latter working at full power only when external

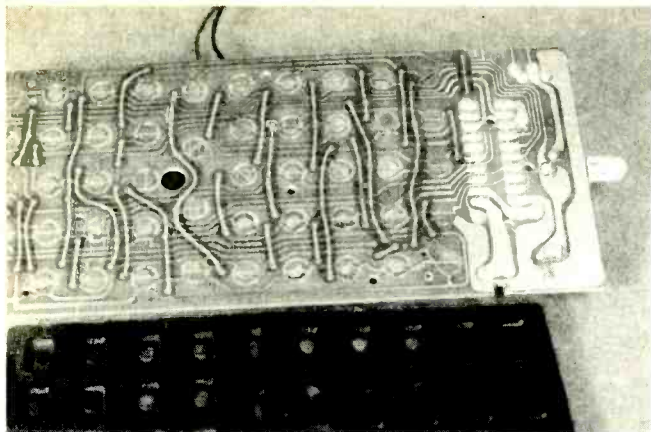


Fig. 3: Inside the remote-control handset. The PCB with IR emitter and the troublesome membrane.

4Ω speakers are connected. We've had several failures of the TDA1521A and TDA2030 audio power output chips, with various symptoms – crackles, distortion and internal short-circuits. For distortion in or loss of one channel without any sign of an electrical overload check the TDA1524A stereo preamplifier chip IA03 first: it's easy to do with an oscilloscope.

Remote Control

The remote-control handset is the Achilles' heel of these sets! The contact membranes wear rapidly or become polluted: we order ten or twenty of them at a time. The ceramic resonator (XT01) breaks away from the PCB, usually at one leg: after repair we glue it down on to the board. The solder pads break or become dry-jointed at the i.c. or at the transmitter LED. When it's roughly handled the PCB cracks and is better replaced than repaired. Finally the battery contacts are fragile and become latched. Again it's wiser to replace them than carry out repair or retensioning.

Loss of on-screen graphics is usually due to "pilot error", with the user having inadvertently cancelled them via the remote-control handset.

Control Systems

The IR receiving photodiode sometimes becomes noisy, the result being insensitivity or complete lack of remote control. Ensure that the IR handset is working before suspecting this however, and don't forget to refit the optical filter as absence of this makes the system insensitive.

Occasional loss of the channel 1 memory data in the 165 chassis can be caused by a mains-borne transient that coincides with switch on. The cure is to fit a 10μF, 35V electrolytic capacitor across RR34 (base of QR06), negative side to chassis. Intermittent failure to come out of the standby mode with early 165 chassis sets can be cured by changing RR60 (IR01, pin 26) to 3.3kΩ.

The microcomputer chip used in the system employed by 170/180 chassis sets can fail, giving rise to faults on the I2C bus. A quite common fault is failure of the 4MHz crystal X001: the symptoms are inability to tune in stations and the display digits incrementing at about five-second intervals. Breakdown of the PCD8572 memory chip gives rise to various troubles, the most common being failure to store channel tuning data.

If you have to replace the MAB8441 microcomputer chip IR01 make sure that you fit one with the correct suffix: several types of internal software (indicated by the suffix) are in

use to give various feature options, and the MAB8441 chips you have in stock may well be for different TV makes altogether!

In Conclusion

The long list of faults given above shouldn't be taken as indicating that these sets are less reliable than those from other manufacturers. It arises because we deal with these sets in large numbers. With the exception of the remote-control handset these receivers are as good as most other designs. Spares are easy to obtain from Tatung and their prices are reasonable.

Finally I'd like to acknowledge the help of my colleagues Ted Callow and Dion Watson in the preparation of this article.

PHOTOSTATS SERVICE

Newer readers may have missed important servicing features that have appeared in *Television* over the past few years. We have therefore in operation a photostat service to make this information readily available. Photostats of the following servicing features, listed in alphabetical order, can be supplied at the prices shown. Please send requests to: Television Editorial Department, Room L323, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Cheques/POs should be made payable to Reed Business Publishing Ltd. There are two standard prices, see below.

Feature	Price
B and O L/LX2500/2800 chassis	A
Decca 80/100 chassis	A
Decca 120/130 chassis	A
Ferguson FV31R VCR	A
Ferguson TX10 chassis	A
Ferguson TX100 chassis	A
Finlux 1000 series chassis	A
Fisher FVH-P520 VCR	A
Mitsubishi CT2227	A
Mitsubishi Euro-4 chassis	A
Mitsubishi HS304 VCR	A
Panasonic D1 VCR deck	A
Panasonic G VCR deck	B
Panasonic NV333/366 VCRs	A
Panasonic NV370/830/850 VCRs	A
Panasonic NV730 VCR	A
Panasonic NV777/780 VCRs	A
Panasonic NV2000/2010/3000 VCRs	A
Panasonic U3 chassis	A
Panasonic U4 chassis	A
Panasonic U5 chassis	A
Salora F chassis	A
Salora G and H chassis	B
Salora J chassis	A
Salora K and L chassis	B
Sanyo CTP7130/1/2	A
Sony KV2252/2256/2752/2762	B

Prices, A = £2.50, B = £3.50
Please allow 28 days for delivery.

Teletopics

BBC SELECT

The launch of BBC Select is taking the BBC into subscription TV. BBC Select is a commercial company whose main role is to sell airtime to programme makers wishing to use the service, which operates during the night-time hours, between 2 a.m. and 6 a.m., when BBC-1 and BBC-2 are normally off the air. The service will be aimed at specialist audiences, particularly in the professional and business spheres. As we write this at the end of May some initial programmes, for example a nursing news service, are being transmitted in the clear and tests are being carried out for scrambled transmissions which are expected to start in late June or early July. The service will be built up gradually.

Over £10 million has been invested by the BBC in BBC Select, which is now selling the service to production companies, investors and other interested parties. Programme makers will earn revenue via a variety of methods including subscription, sponsorship and advertising. A decoder, called a Selector, will be required for the reception of scrambled programmes. The scrambling system is VideoCrypt S, which is a version of the VideoCrypt T system used by BSkyB.

The Selector is a small box that's connected to a VCR. It uses a smart card system: in addition to unscrambling the VideoCrypt signal it automatically switches the VCR on and sets it to record. The Selector is compatible with VCRs that have an IR receiving window. Users simply have to remember to insert a blank tape and leave the VCR on in the standby mode. Selectors will be sold direct by the BBC's Subscriber Management Centre in Bristol, the price being £275 which includes VAT and installation. Initial enquiries should be sent to BBC Select, Woodlands, 80 Wood Lane, London W12 0TT (081 576 2000). Rental or leasing are a possibility being considered.

The Subscriber Management Centre is to be run by SSL, a subsidiary of the Post Office. It will collect subscriptions, handle customer enquiries and manage the smart cards.

BBC Select services will include Executive Business Club (management training), Business Education Club (for business studies students), Accountancy Television Service (training and news), Legal Network Television (training and updating), Farming Now (weather, news and information), Computer Look, a medical programme for hospital staff and GPs and various language teaching services. Clear programmes include Nursing Update and The Way Ahead, a series from the DSS made by Thames TV. Advertising and sponsorship will be allowed only with scrambled services. Sport, film and music services may be added at a later date.

BROADCASTING NEWS

The ITC has awarded the licence for the Channel 3 (ITV) public teletext service to Teletext UK Ltd. BBC engineers are leading an international project that will develop optical routing systems for studio centres. The EC sponsored project is part of the RACE (it stands for R and D in Advanced Communications technologies in Europe) programme that is expected to lead to a Europe-wide wideband digital optical-fibre communications network using WDM (wavelength and time division multiplexing).

Videodat, a new data broadcasting service that transmits digital data to users via satellite, is now available in the UK. Following a test launch at the Cable and Satellite 92 exhibi-

tion, Cambridge Computer has been appointed exclusive UK distributor of the decoders and software required to receive the German-developed service. Over 25,000 decoders have already been sold in Germany, where the service was introduced fifteen months ago. It's said to be cheaper than the use of dial-up modem line systems while providing higher standards of graphics presentation than teletext, viewdata etc. Cambridge will be selling the new decoder and related software for £120 plus VAT. The service transmits text or graphics data during the field flyback blanking part of a video signal. You fit the decoder between a satellite receiver's video output and a PC.

The EC has formally adopted a directive requiring all HDTV transmissions to use the HD-MAC standard. All other widescreen broadcasts must use the D2-MAC standard. At the NAB Technology Exhibition in Las Vegas last April Vision 1250, a consortium whose object is to promote the HD-MAC system, showed a 1,250/1,050-line converter developed by Thomson. A system for 35mm film to 1,250-line HDTV conversion and vice versa was also on show. The BBC is to screen an HD-MAC OB of a Welsh National Opera production later this year, also to selected audiences HD-MAC pictures from this year's Wimbledon.

According to the *Financial Times* Satellite Monitor some 71,000 dish installations were carried out in April, a decline compared with March and with April 1991. A Euromonitor report suggests that by 1996 satellite TV will account for twenty per cent of all UK viewing. This compares with five per cent at present.

SPARES NEWS

The Amstrad spares operation at Newcastle Under Lyme (see last month's spares guide) has been closed. Spares are now available from Amstrad Spares and Service, Fleet House, River Way, Harlow, Essex CM20 2EE. The spares ordering line is 0277 209 508, the spares enquiry line 0277 209 509. Fax no. is 0277 209 559.

SEME has been appointed official supplier of Pioneer spares to dealers and service engineers who are not authorised Pioneer distributors.

Wizard Distributors has been awarded BS5750 Quality Assurance Certification. It's understood that Wizard is the first company in the component distribution field to be given this certification, which is now required by many local authority and educational customers.

LAUNCHES

Matsushita is to launch the Panasonic RSDC10 digital compact cassette player in Japan on September 21st. Features will include a twelve-letter LC display that shows playing time, tape title, artist's name and track number and title, Dolby B and C for analogue cassettes and optical digital input and output sockets. Production will initially be 1,000 units a month and the price around £575. No UK launch details have been released. The Technics brand name is expected to be used in Europe for the players while Panasonic will be used for the tapes. Philips and Polygram have announced that the prices of prerecorded DCC tapes will be similar to those of current compact discs. BASF expects to sell blank DCC90 cassettes at about £5 when they become available in September. BASF's DCC-Maxima range will employ chromium-dioxide tape and provide playing times of 60, 75 and 90 minutes. Cassettes with 105- and 120-minute playing times are expected to be introduced early next year.

Sony plans to launch its Mini Disc system in Japan by November 1st, with launches in the main overseas markets

by Christmas. Record/playback machines are expected to sell for around £340 with playback only models selling for some £255. The 64mm discs have a playing time of 74 minutes. Sony's ATRAC (Adaptive Transform Acoustic Coding) signal compression system uses only about a fifth of the data required by the CD and DAT formats.

TECHNOLOGY

Matsushita has demonstrated a 26in. (diagonal) flat-panel display that uses plasma technology. The company considers that about 15in. diagonal is the limit for thin-film transistor

LC displays. Mass production of the 26in. plasma displays could start within two years, offering HDTV quality. Within the last two years Matsushita has succeeded in increasing the brightness produced by its plasma displays from 30 to 100 candelas/sq.m. About 64 high-voltage driver chips are required, which is a disadvantage compared with LC displays that can be driven by low-voltage driver chips.

Texas Instruments has developed a new type of solid-state image sensor for consumer electronic products. Instead of using charge coupling to provide the scanning action the new sensor is a bulk charge modulated device (BCMD), employing an active CMOS array that works like a memory.

Letters

CHANNEL 5 PROBLEMS

Bill Wright's letter (May) is the most sensible thing I've read on the subject of Channel 5. I wholly agree that it will be clumsy and unfair to meddle with channels 35-38 which were long ago set aside for home entertainment use by items such as VCRs, camcorders, computer games, satellite TV receivers and other equipment that uses an r.f. modulator. Not only will VCRs need to be retuned to avoid the local Channel 5 frequency, other r.f. modulators will also require off-setting, especially those used with VHS-C camcorders when playing back tape from the camera to a TV set. Another problem is posed by the "non-licensable in the UK" video-sender: will these illegal (to use but not to buy!) transmitters be officially adjusted as well?

The ITC has allocated channel 37 to Croydon for Channel 5 reception in the London area. Reception of the existing four channels in North London is patchy. That's why a 70W relay station was installed at Alexandra Palace, to provide a fill-in service for adjacent areas like Wood Green. Unusually, this relay service uses horizontal polarisation. More recently the erection of new high-rise buildings in various parts of North London has caused problems with reception of all four channels transmitted from Crystal Palace. Reception of a Channel 5 u.h.f. signal transmitted from even farther away (Croydon) and at a higher frequency will present even greater difficulty.

Our local newspapers here have for some weeks reported reception problems in the Enfield/Lea Valley areas caused by reflection of Crystal Palace signals from the new steel-cladded, 800ft Canary Wharf tower, the result being severe ghosting. Poplar, which was also affected, was given four alternative frequencies from a local fill-in, but some 100,000 viewers in Enfield and the Lea Valley, who still have to pay the full licence fee, have been told that they cannot be helped because no frequencies are available there. A cable company operates in the area, but not everyone can afford the extra expense.

In the main the ITC has allocated channels 35 and 37 for Channel 5 use. Channel 34, only one channel space away at one end, is already used in several areas by low-power relays and for BBC-2 from the high-power (500kW) Caldbeck station in Scotland. At the other end of the slot channel 39 is used by about a hundred transmitters. These are mostly low-powered ones but there are a few high-power, horizontally polarised transmissions including those from Hannington (Southern region) at 250kW and Rosemarkie (Scotland) at 100kW. I regularly receive BBC-1 Chatton (100kW) sound and vision using a loft-mounted aerial. Thus existing high-power transmitters could interfere with new low-power adjacent channel transmissions and existing low-power relays

could suffer interference from new low-power adjacent channel stations. To expect a revised channel 34-39 spectrum to be able to accommodate so many signals satisfactorily seems to be asking rather a lot.

Wouldn't it be better to transmit Channel 5 using frequencies away from the existing u.h.f. channels, with either up or down conversion to channels 35-38 at the viewer's end? An active aerial with a built-in converter could be used, either weatherproofed outdoors or, where the signal strength is high, as a set-top unit. The present ITC proposals require the use of a new aerial and possibly a booster, so a system using up or down conversion should involve little extra expense. Before anyone says that there are no spare channels outside 35-38, why not consider reclaiming part of Band III for TV use? With today's digital technology it should be possible to accommodate colour information and stereo sound at v.h.f. and the service area would be greater. Incidentally if the proposed Channel 5 eventually includes a teletext service would the average installation correctly display all the information transmitted?

*Ivor Nathan,
Southgate, N. London.*

I was impressed with Bill Wright's arguments (letters, May) for not transmitting on channels 35-38 the proposed Channel 5 service. With the termination of the BSkyB transmissions via the Marco Polo satellite at the end of the year, couldn't the ITC allow a fifth channel plus the present four terrestrial ones to be transmitted via this satellite? This would solve all the interference problems mentioned by Bill Wright. In addition the BBC and the Channel 3 franchisees would have a proven, copyright secure system to expand into widescreen and HDTV, while use of one of the excellent MAC systems would give a boost to the UK's TV industry. BBC-2 and Channel 4 could be phased out from the terrestrial transmitters over a time scale of say two-three years, leaving space for local/regional TV. I feel that local TV is something the public would like but has been neglected.

I rather like the phrase "sub PAL" which fits the standard of BSkyB transmissions from the Astra satellite very nicely. It seems odd that France, Germany, Norway and Sweden can afford D2-MAC satellite TV transmissions while the UK can't go forward in this way. So I ask the ITC to think carefully before losing the use of this system: let's resurrect Marco Polo.

*Brian Webb,
Havant, Hants.*

I can appreciate Bill Wright (Letters, May) regretting the change that Channel 5 will bring to the outstandingly well engineered four-channel u.h.f. system. But I do think that he overlooks what will be a transformation in the aerial industry, not just for manufacturers but for installers as well. At present the market is dominated by the "one small aerial" that

requires very little skill to install. Channel 5 will call for all those unique skills that Mr. Wright and other quality installers possess. A typical installation will require the measurement of the current four channel and the new fifth channel signal levels then selecting the right combination of aerials and combiner. At the same time the customer may need help with retuning of his/her VCR and satellite TV system.

It's up to the franchisee of course to provide the really attractive programmes that the consumer will see as value for money. The one-off cost of the new aerial installation and the VCR retune will be followed by twenty plus years of free viewing since the fifth channel will be advertisement funded.
*Alan Pedersen, Sales and Marketing Director,
Antiference Ltd., TV Division,
Aylesbury, Bucks.*

UNECONOMIC JOBS

Over recent months a number of jobs have proved to be more than a little troublesome, i.e. taking longer to repair than the item's current value. Here are a couple of examples.

The first was a Bush 2114 colour portable. It arrived with a report which said that there was slight picture jitter and some interference after a few minutes' viewing. Several hours were spent trying to trace the cause of the trouble – a dry-joint was suspected. To cut a long story short, the cause turned out to be the line output transformer: a pinhole in the plastic casing provided a shorting path to chassis via the mounting bracket. A new transformer cured the fault but cost the customer some £55!

A more recent job concerned an electronic clock-radio which required a new mains transformer with one 12V and two 5V tapplings, each rated at 0.5A. Including labour the repair would have cost £12. So the customer decided not to bother. But this was after I'd spent over half an hour on a job that didn't warrant a charge.

Isn't it strange how one profitable job is usually followed by two that aren't?!

*M.J. Austin,
Yelverton, Devon.*

COLOUR CHIP VARIATIONS

In his May column Donald Bullock mentioned a problem with the Telefunken and Philips versions of the TDA3562A colour decoder chip. I'd like to draw attention to a similar problem with the TDA3561A colour decoder chip. Our difficulties started when we had a Philips K35 set with teletext in for repair. The fault was no luminance, and we concluded that the colour decoder chip was responsible. The set uses a TDA3560 chip, but we'd none in stock. We did have a couple of TDA3561As and had fitted these in the past with no problems (some data books list this i.c. as a suitable equivalent). After fitting one the luminance fault had been cured but when the remote text button was pressed there was a blank screen. Selecting the text mixed mode (picture with teletext superimposed) gave us a picture with teletext luminance only (or monochrome teletext), i.e. no RGB signals. When we fitted the other TDA3561A chip we had beautiful text and pictures – but didn't know how lucky we were!

A few weeks later a K30 came in with the same no-luminance fault. We again fitted a TDA3561A chip, having restocked, and guess what? Perfect luminance but exactly the same teletext fault. To cut a long story short we didn't at the time know that there are two versions of this chip, one of Philips and the other of Telefunken (TFK) origin, and that they are not always interchangeable in teletext sets. I never

did get the chance to find out the technical differences between the two chips. Does anyone know?

And why has this anomaly only recently come to light? We now fit the Philips version in Philips equipment and the Telefunken chip elsewhere. This policy has worked – so far!

In the same article Donald mentioned having to replace a TDA4600/4601 chopper control chip in a Bush 2020T receiver. When a TDA4600/4601 chip fails you should always replace the high-value resistors connected to pins 4 and 5, also the surge limiter resistor, before switching on – not the other way round as described. These resistors often go open-circuit intermittently.

*Graham Richards,
Rochdale, Lancs.*

TELEPHONE TEST SET

There was an error in the presentation of my telephone test set article in the May issue. In Fig. 2 (page 503) relay RLA was shown switched to the negative supply in its rest position: this would result in no switching action with S2 closed.

Here are a couple of modifications that may be helpful to others. I used a sluggish relay in a unit I recently built for another engineer and found that its action could be improved by adding a 1N4148 diode between R3 and S2, with its cathode to S2. The switching point was improved by using a 7815 regulator in the IC1 position.

*Ian Rees,
King's Lynn.*

MARCO POLO RECEPTION

Having read Colin McCormick's letter (April) I too purchased a brand new BSB receiver, aerial and remote control unit, for just £40. I already have an Amstrad SRD400 that gives excellent results with Astra but couldn't resist the opportunity to gain hands-on experience with a BSB unit despite the fact that transmissions will cease in December.

My upstairs workshop faces almost south. After connecting the units and adjusting the TV set to receive the built-in test signal I pointed the aerial at the window and brought it slowly around to a south-westerly direction. The signal-strength bargraph displayed on the screen enabled me to optimise the direction for maximum signal strength with nil noise – this with the aerial peering through double-glazing. I asked the BSB people to authorise the receiver but unfortunately its number couldn't be authenticated. A return visit to the supplier produced an exchange unit and this time on completion of my telephone call to BSB I was able to receive a first-class picture and sound.

I'm delighted at being able to receive the signals without having to mount the Squarial outdoors: it's a beautifully manufactured unit – too good to bolt to a wall and expose to the elements. Its bracket is now clamped to my workbench, adjacent to the window, and it's providing superb sound and vision.

*Harry Hughes,
Rhondda, Mid-Glamorgan.*

THORN 1590 POWER SUPPLY

I feel that J. LeJeune's suggested power supply modification for the Thorn 1590 series chassis (May issue) is unnecessarily complicated while as a routine repair it would be uneconomic. For some years I've been using a TIP42C as a replacement for VT21 and have never had one burn out. It takes five minutes to fit. Where there's been a burn up in the original circuit an LM7812 regulator chip can be used, see

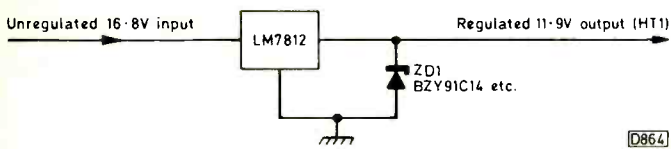


Fig. 1: Use of a regulator chip in the 1590 chassis.

Fig. 1, and is very effective. I include zener diode ZD1 across the output as a crowbar in case the regulator chip should go short-circuit. This will prevent damage to the set such as the c.r.t.'s heater burning out.

L. Mackenzie, T.Eng., Stellar TV and Video, Edinburgh.

PANASONIC G DECK

I would like to comment on M.P. Prakash R. Lewis's short article on the Panasonic G deck in the December 1991 issue. My earlier article on the G mechanism didn't include extensive reference to the power supply in VCRs that use the G mechanism simply because we've had few failures - in our experience Panasonic switch-mode power supplies are amongst the most reliable we've come across. From the model numbers he quotes I assume that Mr. Prakash R. Lewis is an overseas reader. This could explain our different experiences. Where the mains supply is lower than in the UK the power supply will have to work harder, which could increase its likelihood to failure.

One other small point that may be correct for these non-UK models but isn't for some early UK ones is that there are more than the two brass screws to secure the cage over the cassette carrier: the points made in my article regarding the

correct screws in these other positions is most important (specifically Models NVG21/5).

Incidentally I wonder whether Donald Bullock tried replacing the loading belt in the 3V35 with intermittent timer operation? This symptom is common to most VCRs: the belt becomes slack but the fault shows up initially only with timer operation when the machine has been dormant for some time and/or is in a cold room, e.g. at night.

Nick Beer,
Bideford, N. Devon.

PATTERN PARTS

I read with interest Nick Beer's letter (April) on the pros and cons of VCR mechanical pattern parts. As an "authorised nationwide distributor of spares for Ferguson, Hitachi and Philips and the "sole non-account distributor" for Sanyo, we have a policy of supplying genuine parts wherever possible. On the rare occasion when an alternative part has to be offered for these four major manufacturers we state that the part is an alternative and do not show the manufacturer's part number on it. For example replacement type video head part numbers are prefixed with either VH or VID and the abbreviation ALT is included alongside the description to indicate that an alternative part is being offered. Should we experience a quality problem with a pattern part that product is quickly withdrawn. Those items that have a manufacturer's part number alongside the CHS part code are specifically of that manufacturer's origin, supplied by the manufacturer concerned.

In the case of manufacturers for whom we don't have the facility to supply their genuine spares and components we offer a limited range of popular spares of either genuine or

RECESSION - RECESSION - TIRES - TIRES

HEY LOOK, recession is still on and why not increase your profit margin by using J.J. COMPONENTS Idler tires?

EXAMPLE: 10x Sharp tires cost £1.80 + P&P + VAT. That repairs 10 videos each at £20 - Totals to £200.

1x Sharp original idler cost £2.85 + P&P + VAT. That repairs 1 video at £30 - Totals to £30

THIS PROVES THAT
"£" GETS BIGGEST BY
USING J.J.'S TIRES



TIRES



TIRES

+

=



TIRES

IN MOST IDLERS IT'S
TIRES THAT GETS
WORN OUT AND NOT
THE PLASTIC

MOST POPULAR TIRES AVAILABLE: PACK OF 10 EACH: MINIMUM 3 PACKS ORDER

AKAI	PT. NO.
VS1-5	32773: FF/REW
WS1-5	327815: TAKEUP

FERGUSON/JVC	PT. NO.
3V29/HR7200	PU 48961: REEL
3V29/HR7200	PU 51402: PLAY
3V35/HRD110	PU 55374: REEL
FV11/HRD170	PU 58645: PLAY
8902/HR3660	PU 49282: REWIND

FISHER	PT. NO.
725/840	1430420400400: FF/REW
975	1430420400700: FF/REW

HITACHI	PT. NO.
VT11/17	6886971: FF/REW
VT5000	6413144: REWIND
VT8000	6414221: PLAY
VT9300	6861471: FF/REW
VT9300	6861482: PLAY

MITSUBISHI	PT. NO.
HS318	TIRE

NEC	PT. NO.
19013/9033	1618081: PLAY

PANASONIC	PT. NO.
NV300	VXP 0433: PLAY
NV300	VXP 0401: FF/REW
NV370	VXP 0521: PLAY
NV600	VXP 0515: FF/REW
NV600	VXP 0488: PLAY
NV730	VXP 0581: FF/REW
NV2000	VXP 0331: PLAY
NV2000	VXP 0329: FF/REW
NV7000	VXP 0344: FF/REW
NV7000	VXP 0343: PLAY
NV8600	VXP 0245: REWIND
NV8600	VXP 0243: PLAY

SANYO	PT. NO.
VHR1500	143-0-662T14730: PLAY

SHARP	PT. NO.
VC481	NIDL0006GE22: TIRE
VC9300	NIDL0005GE22: TIRE
VC699	NPLYV0107GE22: TIRE
VCA100	NPLYV0111GE22: TIRE

SONY	PT. NO.
SLC7	6706342B: TIRE

UK'S NUMBER ONE
MAIL ORDER COMPANY

Please phone us for the types not listed. Please add 60p post & packing and then add 17.5% VAT TO THE TOTAL

ALL items subject to availability, and prices can change without notice. Government, Colleges, Schools & Institutes orders accepted. All components are brand new. Best quotations given in large quantities.

STOP PRESS: ALSO HITACHI & JVC SPOOL TIRE AVAILABLE AT 50p EACH

Stock subject to time of ordering, but don't get disappointed as delivery arrives every month.

J.J. COMPONENTS

63 THE CHASE, EDGWARE,
MIDD. HA8 5DN, ENGLAND
Tel: 081-952 4641 Fax: 081-952 4641

Callers by appointment only. Hold for telephone line to connect due to Faxlink.

alternative description from a variety of sources, the pattern types being of predominantly Konig origin whose quality we've found to be of an excellent standard with almost no complaint from our customers.

*Freddie Whipp, Sales Manager,
Charles Hyde and Son Ltd.,
Prospect House, Barmby Road,
Pocklington, York YO4 2DP.*

USE OF DECIBELS

I must thank C.J. Boyce for his comments on my letter about VCR to TV receiver interfacing using the scart system. I had hoped that my simplified approach, quoting the instance pertinent to the case in point, would have been adequate: I didn't want to cloud the issue with a dissertation on dBs. Since Mr. Boyce has opened this Pandora's box however I feel obliged to reply.

I agree that dBm can be referred to any impedance; many instruments, e.g. spectrum analysers, quote a reference level of 0dBm into 50Ω. However dBm has its roots in the audio communications business, where the use of 600Ω lines is common. So does dBV, but I don't agree with Mr. Boyce when he states that dBV figures are also meaningless unless related to the system impedance. The term dBV was introduced in 1951 and originally applied to high-impedance microphones which could be used to drive valve amplifiers of typically 5MΩ input impedance. Sensitivity for such microphones is expressed as dBV (0dBV = 1V) for a sound pressure of 1 dyne/sq. cm. If the microphone is loaded, a correction factor is applied to determine its output, or perhaps it's expressed in other terms, e.g. dBm. So although dBV relates to energy, i.e. the sound received by the microphone, no power is provided by the microphone in its unloaded condition and the decibel level is referred to voltage alone, developed across the terminals.

The next historical step allowed dBV to refer to the open-load voltage developed across the terminals of any signal source. (The impedance need not be known at this stage but can be measured by loading the source with a resistor that halves the voltage output. The value of the load resistor is then equal to the source impedance.) Logically, we can now apply the reciprocity principle: for example, when connecting a communications recorder across telephone lines (recording telephone conversations is permitted in many applications, including banks, financial dealing rooms and air traffic control). The recorder must be invisible to the system, and is designed to present a high impedance that absorbs negligible power when bridged across the signal line. It's appropriate therefore to refer to the recorder's input sensitivity in dBV, which can be simply cross-referred to dBm by invoking the appropriate voltage relationship, e.g. 0dBV = +2.2dBm ref. 600Ω. Mr. Boyce may raise his eyebrows at this but dBV appears in this context in both regulatory documentation and equipment specifications. Now you can see why I dropped so naturally into the use of dBV for specifying the audio output of a VCR. This brings me to my next point.

Mr. Boyce appears to chide me gently over my "6dB attenuator" (a pity about the negative sign in the caption to Fig. 1 of my original letter – fortunately the text was o.k.: I referred to -6dB networks, not attenuators!). As a communications man I think in dBs. The output from my VCR has a source impedance of 1kΩ, the maximum allowed by the scart standard, while the TV set has an input impedance of 100kΩ.

Rule of thumb says that since there's a two orders of magnitude difference between these impedances an attenuator will yield a result close to a 6dB loss if its two elements are of equal value and each are an order different from the source

and terminating impedances, that is 10kΩ. As I'd run out of 10kΩ resistors I used 15kΩ instead. If you do the full calculation the precise attenuation works out at 6.95dB. The 0.95dB makes no perceptible difference in this instance of course, but experience is needed when applying rules of thumb: I sometimes work with equipment where errors in excess of 0.1dB are unacceptable, and then there's no substitute for accurate calculations and precise measurement techniques.

Finally, getting back to my Hitachi VCR, like Mr. Boyce I believe that its audio carrier modulation level is low compared with that of prerecorded tapes. The machine gives excellent results however, and since the work that prompted my first letter I have had no further problems.

*Keith Cummins,
Holbury, Hants.*

DIFFERENT DECIBELS

I feel that I should add a few words to C.J. Boyce's discussion on the decibel (May). It's far more important to understand the various definitions of the decibel in practice than to get bogged down in the exact science behind such measurements.

The dBm is an abbreviation for dB(mW), which is the ratio of a power level to 1mW. It's important to appreciate that it is the wattage portion of this that's the reference. A signal can be of 0dBm (i.e. 1mW) in any impedance, but to avoid confusion this is usually specified, e.g. 0dBm (50Ω) which equals approximately 220mV and not 4.472mV as C.J. Boyce states. In practice the dBm is rarely used, and is often erroneously used when it is.

The dBu refers to a ratio of voltages without any reference to impedance. 0dBu is taken to be 0.775V in an "unspecified" impedance, hence the little "u". This is what is loosely referred to as "dB", a measurement of voltage ratios rather than a power ratio. It's therefore perfectly correct to specify a measurement in dBu without stating an impedance, as it's the comparison of one voltage to a reference. What load impedance you choose to put across the circuit is your decision, it's nothing to do with the way in which the measurement is specified.

dBV is where 0dB equals 1.000V – note the upper case V. This is commonly used in Japanese Home Studio equipment, where the standard level is -10dBV, i.e. 100mV. It should not be confused with dBv, with lower case v, which is used by some British manufacturers and means 0.775V into a high-impedance load. For practical purposes it can be considered as being equal to dBu.

While on the subject of dB, a word is needed on the "Vu meter". A Standard Volume Indicator consists of a Vu meter and a calibrated attenuator in series, both connected across an audio circuit. Levels are measured by adding the meter reading and the attenuator value. The most common setting is with 0dBu equal to a reading of -4 on the meter. What this means in practice is that 0Vu = +4dBu. This setting is commonly found on sound mixing desks and some "home studio" gear. With most cassette recorders however a setting of 0Vu is equal to 0.775V at the output terminals, i.e. 0dBu. Sometimes "0Vu" equals 1.000V (0dBV). All these ways are equally valid in the Vu specification. Care should be taken however to ensure that you know how the meter is set before attempting to align equipment. It's not uncommon to find equipment where "0Vu = 1.000V (0dBV)" has been wrongly aligned to read 0Vu = 0.775V (0dBu). The best idea is to get a millivoltmeter that's scaled in both dBV and dBu and make sure that you read the correct scale!

Finally a plea. If you write specifications in dBs, stick to

dBu unless you have a really good reason not to. It's also a good idea to write them in the form of say +6dBu (0.775V), with the "0dB" reference in brackets. Please also include a specification chart at the front of manuals, detailing the exact specification of the measurements within. It can save much guesswork.

Ron McCaskill,
Aberdeen.

HELP WANTED

Wanted: Service manuals for the Bush/Murphy A823B CTV chassis and the Philips G11 chassis with teletext. H.E. Chamberlain, 70 Cromwell Road, St. Judes, Plymouth PL4 9QP.

Satellite TV enthusiast requires remote controls, polariser and actuator arm for the Sky Scan K1. Holmes, 14 Anthony Close, St. John's, Colchester, Essex CO4 4LD. 0206 841 561.

Can anyone provide or indicate a source for: (1) spares and information on the IRTE 1.5m dish; (2) similarly for the Ferguson 1.5m dish; (3) repair service for the Sinclair flat-screen TV set. K. Dulay, 5 Llewellyn Road, Leamington Spa, CV31 2BJ.

Keen DXer requires help in sorting out a fault with the Teleton TA12DU v.h.f./u.h.f. receiver. Signals seem to be weak at the lower end of the v.h.f. band. S. Mildoon, 2 Sandringham Avenue, Broadway Estate, Willenhall, W. Midlands WV12 5SX.

Can anyone help with spares for a Grundig Super Colour Model 4632, or a complete set and remote control? T. Milverton, 121 Borrowdale Road, Northfield, Birmingham B31 5QL (021 477 2044).

Can anyone supply a circuit diagram and/or service manual for an Ultravision 2000 projection TV set? It was made in Mexico by the Zenith Corporation. K.C.H. Catlett, 119 Dormington Road, Kingstanding, Birmingham B44 9LE (021 360 8773).

Can anyone supply or suggest a source for the following? A LOPT (part no. TLF6024C) for the Panasonic Model TC481. A two-stick e.h.t. tray for the Thorn 1580 series chassis (10kV, BRC part no. 00D4-034). Roy Burchett, 12 Ormonde Road, Hythe. Kent (0303 267 969).

Can anyone supply any service information on a Kyoto Model TC21PS? It's a 21in. PAL/SECAM FST set sold in France but made in the UK. Mark Adams, 64 Maple Drive, Portinfer, Guernsey (0481 52417).

Can anyone supply a small quantity of new Thorn 1500 main smoothing blocks (150/150/100µF, 300V)? I can supply Thorn 1400 mains smoothing blocks new. R.E. Bailey, 51 Robin Gardens, Waterlooville, Hants PO8 9XF.

Can anyone supply two flaps for the Philips 17CT2619/05S? Sarah Burton, Circuit Services (Lincs), 31A High Street North, Ruskington, Sleaford, Lincs NG34 9DY (0526 833 023).

Can anyone supply a used, second-hand or redundant remote control handset for a JVC HR7700EK VCR? B.G. King, 25 Mere Oak Road, Perton, Wolverhampton WV6 7NB (0902 741 956).

Can anyone supply a TDA8150 chip for an Osaki CTV20T (circuit reference IC101)? Vic Rummery, Tele-Service, 28 Lower Bore Street, Bodmin, Cornwall PL31 2JY (0208 72011).

Does anyone have a scrap Sony TC-K96R or TC-K77R cassette deck? We require the right-hand cassette guide that attaches to the metal door frame. Sony part no. is 3-551-091-00. Contact Nigel J. Burton, Mays Hi-Fi, 27 Churchgate, Leicester LE1 3AL (0533 514 444).

next month in

TELEVISION

FREE CATALOGUE

The latest components/equipment catalogue from East Cornwall Components is included free with the August issue of *Television*.

● SERVICING THE FINLUX 3000 SERIES CHASSIS

This is an all-singing, all-dancing TV chassis with a digital data bus (I2C) to control operations – programme memory, tuning, signal and deflection waveform processing. Thus to carry out any setting up the service mode has to be entered. Despite all this many faults are the standard ones you get, with the power supply, in this case a fairly straightforward TDA4601 type chopper circuit, etc. Steve Cannon lists common problems and provides guidance on checking the digital control system.

● AD CONVERTER OPERATION

Analogue-to-digital signal converters (DACs) are now widely used in TV sets, video equipment, computers and test equipment. Little information on their operation has been published however, though an understanding of this can be helpful when fault finding. David Botto decided to investigate and found that he had to breadboard some circuitry in order to check and analyse its operation.

● SERVICING THE MICROVITEC CUB

The Microvitec Cub is one of the most commonly encountered computer monitors. It's UK built and caters for RGB or TTL inputs. Arthur Rumbelow, G3KKC, provides a guide to specific faults and their cures based on considerable workshop experience. The notes apply to Models 1431, 1441, 1442, 2031 and 2032.

● TEST REPORT: TESTLAB LOGIC PROBE

A logic probe is the digital equivalent of the old-style signal tracer and is almost essential for fault tracing in digital circuitry. Eugene Trundle tests the TestLab TL07, a typical example of a modern logic probe.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW

TO
(Name of Newsagent)

Please reserve/deliver the August issue of TELEVISION (£1.95), on sale July 15th, and continue every month until further notice.

NAME

ADDRESS

VCR Clinic

Reports from Eugene Trundle, Brian Storm, Alfred Damp, Michael Dranfield, Nick Beer, Ronnie Boag, Gerald Smith and John Edwards

Sanyo VHR3300

We've had three of these machines with the same evil intermittent fault which snaps a tape completely in two – sometimes! This model apart, it's rare for any VCR to break a tape though it often occurs when efforts are made to remove a tangled tape. With the VHR3300 the disaster occurs at the beginning of tape threading, due to a reel brake problem. Look at the feed spool's hard brake arm. On its left there's a metal pin which is, or should be, pushed by an underdeck lever. The pin can work upwards in the plastic arm to the point where it rides over the lever. Its correct position is where it just clears the topmost surface of the underdeck plastic cam. Fix it in position with Superglue or, better, replace the arm assembly. **E.T.**

Tatung TVR6111

This model is similar to those in the Amstrad range of three or so years ago. A symptom that's becoming common is intermittent ejection of cassettes, either when one is inserted or at random during play. The cause is dry-joints at the tags of the three microswitches (start, in, out) on the horizontal PCB fixed to the right of the front-loading gantry. **E.T.**

Philips VR6462/Finlux 1010 etc

These machines use the early Philips VHS deck with conventional M loading of the tape. Many of them now suffer from insufficient reel torque in the fast transport modes – fast forward, rewind, cue and review. Typical symptoms are spillage with E180 or E240 tapes in the forward search mode and long rewind times. Some models benefit from the official modification – fit a 22Ω resistor across R3101/3103 in the reel motor drive circuit. Whether or not you do this, check for excessive friction between the reel idler wheel and the guide plate below it, and for gummy shafts on the spool turntables. To cure the latter problem, remove the turntables and thoroughly clean the holes in them, then clean and polish the shafts. Apply a tiny drop of light oil when reassembling. **E.T.**

JVC GRC11

This record-only camcorder promptly ejected a tape whenever one was inserted. With no cassette present the lid would open only when the power was removed and then restored. A check showed that pin 30 (eject) of the microcomputer chip was permanently low at about 1.1V. This was caused by an electrically leaky eject slide switch. A replacement had to be fitted. **E.T.**

Panasonic NVL25

A curious set of symptoms greeted me with this machine: no "power on" and the timer flashed zeros, but above these were the words "write" and "erase" – it was not something I'd ever seen before. The machine would accept a tape, but as the controls were inoperative it wouldn't return the tape. This suggested to me that the systems and servo chip IC2001 was probably all right. I'd also no good reason to suspect the timer chip IC7501. Voltage checks between these two chips showed that the serial data and serial clock lines were the source of the trouble. The serial data line was sitting at about

1V while the serial clock line, at around 4V, was closer to the normal condition for these lines.

Disconnecting IC7501's serial data pin removed the "write erase" from the display, but the line's voltage remained low. Disconnecting the other two chips connected to the serial data line, IC2001 and IC6801, also had no effect – the voltage remained low. The only other possibility was the 270pF capacitor C6012 which is connected between the line and chassis. When I eventually found it (it's a small, surface-mounted capacitor tucked away at the edge of the main board) it turned out to be leaky. A normal-sized replacement restored correct operation. **B.S.**

Panasonic NVG21

The playback sound gave a fair impression of a washing machine and a tumble drier working in unison, drowning the recorded sound with buzzing and spurious oscillation. Voltage checks around IC4001 in the sound section produced no clues except that the noises were reduced when the meter's probe touched the input pin. So attention was turned to the input circuitry, where R4021 (47Ω), a surface-mounted resistor connected to a filter network, was found to be open-circuit. **B.S.**

National NVG33

A dead power supply was the trouble with this foreign machine. Checks in the switch-mode power supply failed to reveal any shorts in either the primary or the secondary side, so attention was turned to the start-up circuit. We found that C1003 (1μF, 250V) was open-circuit. **B.S.**

Ferguson 3V44

For once the symptoms displayed agreed with the fault description on the job ticket. This said dirty heads. Cleaning them didn't help however and the reason for this was soon apparent: the drum motor was running backwards at full speed. D408, a 5.1V zener diode, was short-circuit. **A.D.**

Sony SL615

While this machine was still apart after being serviced we found that no functions could be obtained via the operation board though remote control operation was correct. The "fault" was eventually traced to the fact that there was no earth link to the operation board because the bottom case was open-circuit: normal operation was restored when the bottom case was refitted. **A.D.**

Amstrad VCR6000/6100

There was neither forward wind nor rewind as the reel brakes were on. They would come off if the brake plate, reference 261, or the brake actuator, reference 262, was operated manually before selecting a wind mode, but when a wind mode

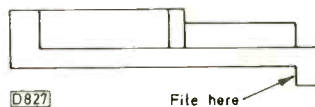


Fig. 1: Cure for Amstrad VCR6000/6100 fault.

was stopped then selected again the reel brakes once more remained on. The cause of the problem was that the brake actuator plate moved but the brake plate didn't. Careful observation showed that the lever trigger, reference 260, didn't return to its correct resting place, thus inhibiting movement of the brake plate. Filing at the point shown in Fig. 1 cured the fault. **A.D.**

Panasonic NV333

The capstan servo wasn't locked, the symptom being a noise bar that floated through the playback picture. This is typical of a no CTL pulse fault, but checks on the CTL section of the circuit showed that it was working correctly. Further checks revealed the fact that the 9V supply to the tracking control was missing. This is the "except Rec 9V" supply. It comes from the syscon panel where Q6003 was found to be open-circuit. **A.D.**

Panasonic NVG40

Fast forward and rewind were o.k. but the machine didn't play. When we checked the operation of the mechanism we found that the P5 unit arm didn't come across fully in the stop mode. This was because the "pull-out sector gear" was broken. We replaced the gear and also the mode switch as it's the most likely thing to have caused the gear to break. **R.B.**

Panasonic NVG12

There was a rather unusual symptom – no sound in any mode, including E-E. A sound signal was going from the TV demodulator PCB to the audio pack, where all the audio goes. It wasn't being switched out of the BA7752LS chip IC410 however. The supplies and the d.c. switching conditions were all correct so it seemed that the i.c. was faulty. A replacement restored the sound. **N.B.**

Panasonic NVG12

This machine would enter the record mode and proceed as if everything was o.k., but when you rewound the tape and replayed it the previous recording was still present. Although the machine entered the record mode it didn't produce the delayed record 12V supply. There was no 12V at the emitter of Q6005 as Q6006 was switched off because its base voltage was high. Q6006's base voltage should be pulled down by the record prevent switch line from the microcomputer chip IC6001. The voltage was correct at IC6001, the cause of the fault being a break in the print between the cathode of D6005 and R6041 as the print winds its way through the pins of the audio pack. **N.B.**

Ferguson FV52L

This machine had been installed only two days previously, yet here I was looking into why it lost about twenty minutes an hour. The cause was fairly simple – reference crystal 01 was dry-jointed on both legs. This was probably due to the fact that the PCB holes are much too large for the legs of this device. **N.B.**

Panasonic NVG45

Steve Beeching mentioned the sync separator modification for this model in his Camcorner feature last January. I reported on the problem a couple of years ago and pointed out that the modification could be improved by adding an

extra 47k Ω resistor across the components that Panasonic supply. I'd found this to be necessary because users complained about severe drum twitch and HSP running through the picture when recording from early Bush/Alba satellite TV receivers (the ones that used to drift off tune). I had heard that the video output from these units was suspect and that there was a modification for them. But customers who rented G40s and G45s from us preferred us to take action. **N.B.**

Samsung VI710

Playback was fine but there was no E-E sound or vision. Inputs from the line or tuner were missing. There was vision at pin 4 of the TA8605N chip IC303, but only hash at pin 10. The amplifier inside the chip had to be all right as it fed both the playback and E-E video through to pin 10. So the cause of the problem had to be in the switching. The chip was stuck in the playback mode as pin 13 remained high. But the PB 5V was switching correctly – so where was the 5V coming from? Not via the white-clip network but from within the chip itself. We proved this by disconnecting the pin and finding that the 5V was still present here. A new chip restored normal operation. **N.B.**

Panasonic NVM7

A common problem with these and other full-size camcorders is that the unit powers up and then, within a few seconds, shuts down again. The clue is that the mechanism doesn't shuffle as it should, the cause being a faulty M54543L loading motor driver chip. It's easy to check the i.c. If its supply is present and there are correct commands at its logic pins but no output is provided the chip is defective. Another clue is that the chip's supply falls when the load should be on. **N.B.**

Panasonic NVJ40

This machine drifted off tune on any channel above 59. The cause was a faulty tuner. **N.B.**

Salora SV6910

There were no functions and no clock display. FR2 in the power supply was open-circuit. **G.S.**

Akai VS33

This machine kept going to standby. The drum speed was found to be erratic and a check on the drum PG waveform showed that noise was present. Replacement of C6, which was leaky, on the drum motor PCB provided a complete cure. **G.S.**

Akai VS35

The playback picture was marred by numerous white dashes which were similar to the spots produced by e.h.t. arcing in a TV set. The cause of this interference was traced to the fact that the head preamplifier screening plate's chassis earthing screw was loose. Retightening it solved the problem. **J.E.**

Ferguson 3V55

The loading motor continued to run after the cassette had been ejected. As a result the loading belt squealed loudly. We found that the cause of the fault was the mode opto-switch assembly. It's available from CPC at a very reasonable price under part no. TNPU35632A3. **M.Dr.**

Filters for DX-TV Systems

Part 2

Keith Hamer and Gary Smith

In this concluding part we'll provide guidance on dealing with the various types of interference that can affect DX reception.

Interference from FM Radio

For Band II reception (the TV channels are just below the f.m. radio broadcast band) it's desirable to incorporate some form of filtering since in many areas the f.m. radio transmissions are very prone to penetrate this part of the band. F.M. radio transmissions also occasionally find their way into Bands I and III, with the result that "blank" or fuzzy-looking carriers appear at certain points. In Band III for example channels E5/6/7, i.e. at twice the f.m. carrier frequency, can be affected. You can use a scanner to confirm that the interference is caused by f.m. transmissions. Alternatively a D100 DX receiver can be used for the purpose simply by setting the sound spacing to zero and listening to the signal.

A length of coaxial cable approximately 75cm long can be connected in circuit to remove f.m. interference in Bands I/II, acting as a stub filter (see last month). Shorten the cable one centimetre at a time, using wire cutters, while observing the interference or listening to the carrier with a scanner or D100 receiver as described above. Find the cable length at which the interference falls to a minimum level. If you keep snipping, the interference will increase as the optimum stub length has been passed. The higher the frequency of the offending signal the shorter the coaxial stub will need to be. Don't short-circuit the free end of the stub as it will then have the opposite effect and the interference will rise to a maximum level.

A two-way aerial switch can be used, see Fig. 1, when a quarter-wave stub is employed to remove f.m. radio interference in Bands I/II. This enables the stub to be switched in or out of circuit quickly depending on whether a limited (for TV reception) or full (for f.m. listening) response is required. The switch also enables a variety of quarter-wave stubs to be connected quickly when experimenting. Modify the switch by

linking two of the switch connections as shown, thus providing a permanent path for the signal from the aerial.

Alternatively a variable acceptor circuit, see Fig. 2, can be used. Where f.m. radio interference is particularly bad it may be an advantage to use this circuit in addition to a stub. Connect it at the amplifier's input. Use a small trimmer to provide adjustment to reduce the f.m. signal level.

A coaxial stub filter can't be used to remove f.m. interference in Band III because it will also remove signals at multiples of the frequency to which it's cut, e.g. a stub cut to 100MHz will also have an effect at 200MHz. Instead, the Band III (high-pass) leg of a diplexer or triplexer can be used to remove the f.m. radio interference.

UHF Breakthrough at VHF

Where strong local u.h.f. signals cause interference by overloading a Band I or III mast-head amplifier additional filtering can be added at its input. For u.h.f. breakthrough in Band I try the low-pass (Band I) section of a diplexer. For breakthrough in Band III use a low-pass v.h.f. type which has a cut-off above Band III. Alternatively a simple u.h.f. acceptor circuit can be used, see Fig. 3. Operation is simple: adjust the trimmer just enough to remove the interference from the wanted channel.

UHF breakthrough at UHF

Where a high-level u.h.f. signal overloads a distribution amplifier the acceptor circuit can be added prior to its input and adjusted to reduce the level of the offending u.h.f. group while DX signals present in the other two groups are passed through. The filter can be inserted in-line where the mast-head amplifier is powered from the distribution amplifier since it passes d.c.

If a mast-head amplifier is being overloaded remove it from the mast and install it indoors with the variable filter connected to its input. In extreme cases the cross-modulation will affect the entire u.h.f. band: by adjusting the trimmer's screw to attenuate the local u.h.f. group the interference will be removed from the other groups.

The local group of u.h.f. channel signals can be attenuated simply by using the leg of a u.h.f. diplexer that doesn't allow for this group. U.H.F. diplexers are normally used to combine the outputs from two u.h.f. aerials of different groups. They are available in group A + BCD (sometimes known as A + E) or group AB + CD versions. There are variations with the latter type, with different response cut-off points between the upper and lower groups of channels. If a u.h.f. group diplexer is used to remove the local transmissions for the purposes of DX-TV reception it must be stressed that the method is suitable only for attenuating group A or CD transmissions: the group B channels cannot be attenuated without sacrificing one of the other two groups as well.

Band I Signals in Band III

During an intense Sporadic E opening you may occasionally find Band I channel signals in Band III. Before claiming exotic reception, disconnect the Band I aerial to ensure that the picture is not being produced as the result of some form



Broadcast weather chart showing an intense area of high pressure and an associated occluded front. The photograph, taken in 1974, also shows the line-pairing effect produced by interference.

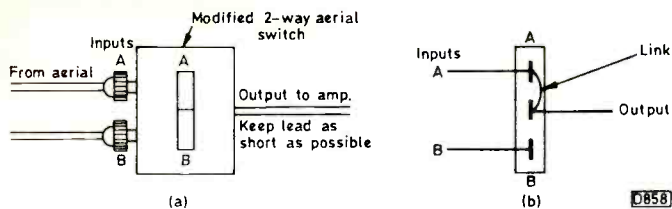


Fig. 1: Incorporating a switchable stub. (a) Basic arrangement; (b) slide switch modification.

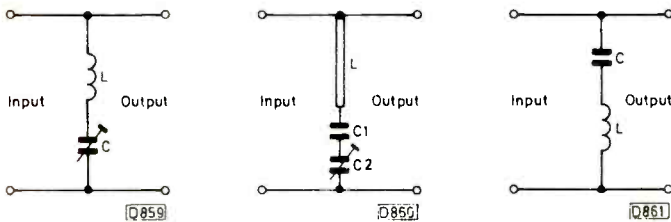


Fig. 2 (left): Variable acceptor circuit for f.m. band signals. Coil L consists of 4-5 turns of 0.25in. diameter 20 s.w.g. wire air-spaced over 3/8in.; C is 5-60pF.

Fig. 3 (centre): Acceptor circuit for u.h.f. signals. L is a 2.5 cm length of 20 s.w.g. wire; C1 is 6.8 pF; C2 2-10pF.

Fig. 4 (right): Simple acceptor circuit for 27MHz signals. C is 100pF; coil L consists of 15 turns of 24 s.w.g. enamelled wire, diameter 3/16in.

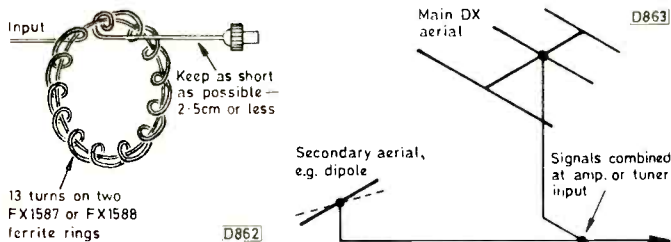


Fig. 5 (left): Ferrite ring filter.

Fig. 6 (right): Signal cancellation with a second aerial.

of cross-modulation – this is particularly likely where a distribution amplifier is used. When more than one receiver is in use a combination of tuner settings can sometimes produce an up-conversion effect. This has led to red faces and disappointment on more than one occasion in the past.

CB Breakthrough

CB interference usually occurs around channels IA/E3 in Band I, at twice the CB transmission frequency. If the cause is an overloaded mast-head amplifier a high-pass filter at its input should provide a remedy or at least a worthwhile reduction. As an alternative the simple acceptor circuit shown in Fig. 4 can be tried, connected across the amplifier's input.

In many cases unfortunately the CB installation will not be tuned correctly and will thus radiate harmonics at Band I frequencies. The use of a 27MHz filter at the input of an amplifier will not in this case provide a cure because the interference is at approximately 54-55MHz. CB harmonics at this frequency have been received at distances of over 500m.

Sometimes the 27MHz (or other h.f.) signals are picked up on the outer braid of the coaxial downlead and transferred to the tuner which can then be overloaded, especially if it uses bipolar transistors. In this case the use of a ferrite ring filter (see Fig. 5) will sometimes provide a cure.

Removing In-band Interference

Simple filtering usually won't help with in-band interference because it will also remove or seriously attenuate the wanted

signal. In the 405-line era however notch filters were commonly used by UK DXers to remove interfering BBC-1 vision or sound carriers. These are most effective when the interfering signal is at least 250kHz away from the wanted signal.

In recent years there has been a great growth in the use of cordless telephones and baby alarms operating at around 49.6MHz, which is uncomfortably close to the 49.75MHz channel R1 vision carrier frequency. It's unlikely that a notch filter would provide an effective remedy because of the closeness of the two frequencies. Use of the 6-metre band (around 50MHz) by radio amateurs also causes problems for DXers, particularly those who live close to a repeater or beacon.

Use of a reduced i.f. bandwidth helps a great deal provided the interference is not at exactly the same frequency as the wanted signal. Directional aerials may also help in reducing the interference, provided in this case that it doesn't come from the same direction as the wanted signal.

Interference at the same frequency as the wanted signal can be removed by using a process known as phase cancellation. In this case a second aerial picks up as much as possible of the offending interference, which is then mixed with the wanted DX signal. One hundred per cent cancellation can sometimes be achieved. The signal from the extra aerial must be 180° out of phase and of equal amplitude to the interference picked up by the main aerial when the two signals are combined. This may sound rather complicated, but bear with us.

When the 405-line system was in use in the UK the channel B2 and E2 vision carriers coincided at 48.25MHz. This meant that DXers within range of a channel B2 transmitter had great problems in resolving channel E2 vision successfully. Several enthusiasts tried a simple phasing system to provide a remedy. It's technically primitive but works. The output from a channel B2 dipole was connected to the amplifier's input in parallel with the channel E2 signal and was rotated, experimentally, through various angles. A position occurs where the channel B2 interference drops to virtually nil. In one case a position where cancellation occurred was found in the garden, at ground level, and the dipole was then carefully fixed in this position. Despite the mismatch that was present when the cables were joined the end results were startling. Thanks to the system weak signals from the channel E2 Kissi transmitter in Ghana were seen for the first time.

Rotating the main aerial alters the phase difference of course. So other fixed dipoles had to be used for different directions. One DXer discovered that his portable TV set's telescopic aerial was in circuit when the main DXing array was connected and that this enabled a similar cancellation effect to be achieved.

This approach also works at other frequencies, though much patience and experimentation are required. If this is of any consolation, the stronger the interference the easier it is to remove it. Phase cancellation doesn't work where more than one interfering carrier is present at a particular frequency.

A Band I electronic phaser unit was described by Roger Bunnay in the January 1981 issue of *Television*. It uses a fixed aerial with rotary controls for amplitude and phase adjustment. The D100 converter system can be supplied with a dual aerial-input socket for connecting a coaxial stub filter or a second aerial for phase cancellation purposes.

Fig. 6 shows the principle of phase cancellation using a second aerial.

HS Publications, 7 Epping Close, Derby DE3 4HR (0332 381 699) can supply the F1013 triplexer mentioned last month at £5.95 including UK postage and packing. The D100 converter system is also available from this source.

TV Fault Finding

*Reports from Philip Blundell, AMIEE,
Mick Dutton, Steve Cannon, Chris Avis,
Michael Dranfield, Roger Burchett and
Stephen Leatherbarrow*

Philips CP90 Chassis

This set was dead with a whistling noise coming from the power supply – the over-voltage crowbar thyristor was firing. By running the set with reduced mains input (via a variac) we discovered that the 95V from the power supply was rising to over 100V, pointing to a fault in the error amplifier stage. Checks here showed that transistor 7701 (BC548) was short-circuit base-to-emitter. **P.B.**

Philips K40 Chassis

There was no sound output from this set. Checks showed that the volume control voltage from the SAB3035 chip was being held down. To cut a very long story short, the cause of this was the on-off switch! Its momentary-make contacts were stuck together. One to watch out for. **P.B.**

Philips GR1-AX Chassis

I've had this fault a couple of times now. The symptoms are no colour and a vertical black bar across the screen. The cause is a crack in the print by the line output transformer, where the PCB fits into the back cover. Check the track that runs from pin 10 of the transformer. **P.B.**

Philips CP110 Chassis

For a "flashing" picture check whether R3415 (470k Ω) or R3412 (180 Ω) on the tube base panel is open-circuit. **P.B.**

Philips CP90 Chassis

This set came from another dealer because it kept blowing its BUT11AF line output transistor. A new transistor would last only a couple of days. The e.h.t. was normal, no dry-joints were visible and the transistor's base drive waveform was o.k. I then noticed that the set was a late model fitted with the A51AEL30X05 tube. This called for a few component changes, including the use of a BUT12A line output transistor. The correct transistor lasted long enough for line tearing to be seen before I managed to switch the set off. The line output transformer was faulty. **P.B.**

Philips GR2-1AX Chassis

This set would intermittently blank out the picture and mute the sound for a few seconds. Channel changing seemed to instigate the fault. We found that the /VD pulse to pin 27 of IC7708 disappeared in the fault condition. The source of the pulse was traced back to the TDA2579B/N1 timebase generator chip IC7470 where the field-rate part of the sandcastle pulse disappeared though the line-rate part was o.k. When the chip was tried in another set it took the fault with it. A replacement was ordered and when fitted provided a complete cure. **P.B.**

Sony KV2752 (PE3 Chassis)

This set led us a merry dance. It had recently had a new TDA3562 field output chip fitted but the complaint now was that the picture and sound would go off when the set had warmed up, leaving a horizontal white line across two-thirds

of the centre of the screen. We saw this happen in the customer's house and were able to establish that the 12V supply disappeared because rectifier diodes D659 and D653 both went open-circuit when warm. These were replaced and the set worked well for a couple of days.

The customer then said that the set had started to drift off tune. A new tuner seemed to put that right but two days later we were back again. This time the symptoms were tuning drift and the colour saturation in the top half of the picture being less than that in the bottom half. We took the set back to the workshop and put it on soak test. It ran for days without the fault showing. Then one day while cricket was on the grass became less green towards the top of the picture.

The most likely cause of the fault seemed to be some kind of hum modulation on one of the supplies. Scope checks showed that there was a 6V ripple on the 40V supply that feeds the 30V tuning voltage stabiliser. The 33 μ F reservoir capacitor C653 was o.k., but adding a 10 μ F capacitor across the 40V line removed the ripple and restored correct colour saturation. The cause of the problem was the 1.2 Ω surge limiter resistor R651 which had risen in value to 15 Ω . The excessive ripple was being developed here. **M.D.**

Hitachi G8Q Chassis

The complaint with this set was no tuning. It employs pulse-width modulated tuning, the relevant output from the SAA1293 chip being integrated to provide the tuning voltage. As there was no tuning voltage at the tuner we checked back to the source. The pulse-width modulated output from the chip was present at the base of Q1506 and its mark-space ratio altered as the tuning was varied. This transistor's collector voltage also varied, but only slightly – not enough to span the required tuning range. The path from the collector of this transistor to the tuner is via several resistors, first on the tuning panel, then on the control panel and finally on the main board. We eventually found that one of these resistors, R1534, had gone high in value, a replacement (39k Ω) restoring normal operation. **M.D.**

Sharp C1420

A point worth noting with these sets and models that use a similar chassis is that if R623 (1.2M Ω) goes high in value the result will be intermittent tripping, usually on bright scenes. Unfortunately the line output transformer is also a common cause of intermittent or permanent tripping. **M.D.**

Ferguson ICC5 Chassis

This set was in the shutdown state. When switched on it would trip three times then become lifeless. That's the usual trip sequence with this chassis. It can sometimes be a nightmarish situation as the fault can be almost anywhere – the protection circuits are very sensitive. As a start we disconnected pins 8 and 10 of the line output transformer, but the set still tripped. Next various secondary supplies from the chopper transformer were disconnected including, inadvertently, pins 17 and 18. A note was then made in the service manual warning never to do this or else the power supply will suffer impending doom. As a result of my miscalculation a new BU508 chopper transistor was next fitted. Back, ahem, to the original fault.

new BU508 chopper transistor was next fitted. Back, ahem, to the original fault.

A glimmer of light appeared at the end of the tunnel when pin 22 of the chopper transformer was disconnected – the set powered up with a raster. There was no sound though as pin 22 is the 36V supply to the stereo audio board. When the audio output chips IS40 and IS41 were checked the left-hand channel one was found to be low-resistance from its supply input to chassis. A new TDA2030A42 chip put matters right. S.C.

Salora J Chassis

The sound was o.k. but there was no picture – the screen was completely dark. A check on the drive waveforms from the colour decoder chip, at pins 13, 15 and 17, showed that they were missing. In addition the d.c. content was low. The brightness and contrast control voltages were present at the chip and altered appropriately depending on the function selected. The luminance input was also fine. Time to check the sandcastle pulses. These also looked fine. But wait a minute, something doesn't seem right. When the scope was set to the line frequency a perfect line blanking sandcastle waveform was seen, but at field frequency there was no blanking waveform present. We traced the pulses back to the point where the separate components are added together to give the distinctive waveform shape. The field component comes from the field output chip ICB400 via DB402 and TB400. ICB400 was delivering pulses but they were going AWOL at the base of TB400. The cause of this was that TB209 was short-circuit collector-to-emitter. When a new BC307 was fitted up came the picture. S.C.

Sony KV211XMTU

There was an intermittent fault on this set – the screen would light up bright green. The fault was heat related, so it was time for the hairdryer. We found that the cause of the fault was definitely on the video panel, which was a bit of a surprise as we've had a few faulty transistors on the tube base PCB in these sets. The fault could be made to appear by heating around the colour decoder chip. C302, the green sample-and-hold capacitor, was suspect but proved its innocence on being replaced. It didn't take long though to trace the source of the fault to the green on-screen display buffer transistor Q311. The original type is JC501, but the 2SC2785 is a direct, Sony official replacement. A new one cleared the trouble. S.C.

Osume CTV1484R

Amazing aliases abound with colour portables: this remote-controlled cash'n'carry weirdo turned out to be an Alba set in disguise. The trouble was loss of channel selection and uncontrollable, maximum sound when the set had been in operation for a few minutes. Heat and freeze probing suggested that a 455kHz crystal on the front remote control/tuning board was faulty. A suitable transplant was obtained from a defunct Sharp remote control panel. Fitting it restored normal operation. C.A.

Tatung 160 Chassis

A type of fault that's becoming more common is the dreaded "demolition syndrome", when one small failure starts a chain of destructive events. Our first discovery with this dead set was that the line output transistor was short-circuit. We removed it and temporarily connected a 60W bulb across its

emitter-collector connections. The power supply then worked but there was no line drive from the TDA4503 chip because its 11.5V supply was missing. Regulator transistor Q501 was non-conductive because one of its two 12kΩ base bias resistors was open-circuit. We replaced both resistors (R507/8) and fitted a new R4050 line output transistor. When we switched the set on it sprang to life – with a bright raster. The 10Ω filter resistor R201 in the feed to the RGB output transistors was open-circuit. Did a falling 11.5V supply distort the line drive, turn the RGB output transistors hard on, blow R201 then destroy the line output transistor? Send your answers to anyone but me! C.A.

Ferguson TX90 Chassis (20in version)

The field scan was stretched across the top and bottom but cramped across the middle. After a few minutes the fault would clear, but a squirt of freezer on the 68V zener diode D137 would bring it back. The diode had a 200kΩ leak when cold. C.A.

Ferguson TX90 Chassis

A rolling picture with horizontal ripples across the screen is a common fault with these sets. The usual cause is that R236 or R241 in the pulse feed to the TDA4500/S1 chip IC102 is high in value or open-circuit. This time however the identical symptoms were accompanied by a clatter when the set was turned over, caused by the ferrite core that had fallen out of the line driver transformer T103. Memories of the 3000 chassis! C.A.

Luxor B2 Chassis

The trouble with this portable was low output from the power supply at only some 90V instead of 129V. The set-h.t. control PN01 had no effect. As a first step we changed the BRY55 thyristor TN02, using an MCR101 as we didn't have the BRY type in stock. This produced some improvement. The set-h.t. control now worked, but we couldn't get an output above 110V. Assuming that the set would work correctly only with the correct thyristor we obtained and fitted one. All this did was to restore the original fault! Further checks showed that the 5.1V zener diode DN18 had only 1V at its cathode, and we then discovered that RN28 (560kΩ) was open-circuit. Replacing this resistor along with RN29 (330kΩ) for good measure restored the set to working order. All that was now needed was to reset the set-h.t. control for 129V at the cathode of DN13. M.Dr.

Amstrad TVR1

This machine came in dead. The mains supply was present up to the relay in the TV section but the relay didn't operate when the monitor button was pressed. In this model the standby power supply comes from the VCR section, so we started our investigation here. Fuse F604 (630mA) in the power supply had blown and a replacement blew at switch on. We disconnected plugs and found that the short-circuit was across the all 5V line. The output from the 5V regulator transistor Q603 goes to the syscon PCB, but extensive checks here failed to reveal the cause of the short-circuit. We then discovered that the fault disappeared when one of the inter-connecting plugs between the VCR and the TV sections was disconnected. This enabled us to establish that the short was on the tuning preset PCB. Desoldering various suspect components brought us to C1109 (100μF, 10V) which decouples pin 1 of IC1102. When this had been replaced the fuse held

and the TV and VCR were back in working order.

If you get one of these in with the complaint that the TV section won't switch on when the monitor button is pressed though the monitor on LED lights up, check whether the timer record button is pressed in. It will save you having to strip down the VCR. **M.Dr.**

Matsui 1455

There was no luminance and the on-screen display characters flared badly to the right, extending to the edge of the screen. A check on the luminance waveform at pin 23 of IC202 showed that all was well here, but the signal was missing at the emitter of the 2SA562 luminance amplifier transistor Q202 which turned out to be leaky. A replacement restored full luminance but the on-screen display fault was still present. The on-screen display signal is fed to the base of Q202 via a 1N4148 diode which also turned out to be leaky, but the fault was still present when a replacement had been fitted. Further checks brought us to the collector of the 2SC1815 buffer transistor Q408 where the voltage was 7V. The correct figure is 0.13V. The transistor tested o.k. when removed but a replacement cured the fault. **M.Dr.**

Philips K35 Chassis

The reported complaint was of picture flicker but when we switched the set on there was a small picture – about two inches was missing all round. As the h.t. was correct at 140V attention was turned to the line output stage where the tuning capacitor C567 was found to be badly dry-jointed. This was presumably the cause of the flickering mentioned on the fault ticket. The fault was still present when we resoldered the joints so C567 was removed. It was then obvious that severe heating had occurred, caused by the dry-joint, and the capacitor was visibly deformed. On test we found that its value had fallen from 8.2nF to 2nF. A replacement capacitor cured the fault but with the lower e.h.t. the picture was very disappointing. Amazingly the line output transistor had suffered no damage. **M.Dr.**

Matsui 2160

Sound but no picture was the complaint. There was h.t. at the collector of the line output transistor but no e.h.t. because the transistor's base drive was missing. R428 and R427 which provide the supply to the driver transistor Q401 were red hot but the transistor was o.k. A check at Q401's base showed that there was no input, only a d.c. voltage of 1V which turned the transistor on. The μ PC1420CA chip IC401 had the correct 12V at pin 38 and the voltage at the X-ray shutdown pin was correct at 0V. A d.c. reading of 3V was obtained at the line drive output pin 26 however. After disconnecting this pin the voltage rose to 12V. Clearly the chip was defective, a replacement curing the fault. **M.Dr.**

Fidelity CTV140R (ZX4010 Chassis)

The chopper and line output transistors were both short-circuit. The cause was not hard to see – the on-off switch had obviously been arcing for some considerable time and was now visibly burnt. **R.B.**

Network NWC1401

A new customer, obviously shopping around, asked if I would like to repair a dead Network colour portable. Being one of the more helpful types she said that it was actually a

Grundig set, or so the salesperson had claimed. Now some Network sets did have Grundig innards, but this was not one of them. On removing the back shell I was confronted with a suspiciously Toshiba-looking chassis. The 2SC2068 line driver transistor proved to be lazy, starting when warm but not when cold. The manual for the Bush BC7000/7100 (Rank T24 chassis) proved to be useful (Toshiba X53 chassis for those more used to the maker of the original chassis). **R.B.**

Crown 14CX25

This 14in. portable is fitted with a Sanyo chassis. Failure of the line output transistor can be caused by the 0.0022 μ F, 2kV line output stage tuning capacitors C709/710 being dry-jointed. I traced the cause of no colour to the 2SC65Y burst amplifier transistor Q311 being open-circuit base-to-emitter. A BF259 worked all right in this position. **R.B.**

Rediffusion Mk 3 Chassis

We get a lot of these sets ex-rental. No sound is usually caused by OR71 (820 Ω , 0.5W) overheating and going open-circuit. This is now a very common fault. Fit a 1W replacement. In the dual-standard versions (aerial/cable compatible i.f./s.f. boards) the component reference number is OR55.

If the set tries to start up but the blowing of 6FS1 (1.6AT) on the power panel puts a stop to the proceedings you need spare boards, a variac and patience. If a substitution check proves that the power supply panel is not responsible check the thyristors in the line output stage. On one occasion 5C4 (0.1 μ F, 1kV) was visibly bulged – a replacement restored normal operation. On two occasions recently the line output transformer has been the cause of the problem. If a variac is not available a neon tester held near the transformer will usually show "pulsing" if the transformer is o.k. and the cause of the fault lies elsewhere. Even with a heavy leak in the line scan thyristor the neon lit. **R.B.**

Fidelity ZX3000 Chassis

There was severe line tearing and stressful noises came from within the set. The cause of this situation was the 33 μ F, 250V h.t. reservoir capacitor C100 which was open-circuit. Interesting that the fault condition varied with different brightness levels. **S.L.**

Hinari CT5

An open-circuit resistor was the cause of field collapse. The offending item was R422, 10 Ω , off pin 5 of the line output transformer. It seems to supply Q310 with collector voltage/bias, though from our photocopied circuit it's sure hard to tell! **S.L.**

Binatone 01/9014 Colortron

These nice little sets are very common in our area. A recurrent problem we have is with the start-up circuit. There are two 180k Ω , 0.5W resistors here, R622 and R633, and one invariably succumbs. We fit more manly replacements. **S.L.**

Ferguson TX100 Chassis

The picture would occasionally turn a distinct shade of green. This usually showed up after a quarter of an hour or so. It was noticed that from switch on the green output took a shade longer to appear than did either red or blue. The culprit was C51 (0.47 μ F). **S.L.**

What a Life!

Donald Bullock

A bit of sun is always cheering. So I got up early the other day and raced Greeneyes to the bathroom. "Lets have my Healthybran and fruit" I cried, "and my sugar-free coffee. Let me get to the workshop. I want to get on and work."

The JVC HRD230

With breakfast over I strode to the workshop and put the first job on the bench. It was a JVC VCR – an HRD230. Rewind and fast forward were o.k. but it wouldn't record or play. The tape laced then unlaced and that was that. The head drum was still.

After checking the power circuits I decided to replace the STK5481 just to be sure. As I'd feared, this made no difference. So I carried out some voltage checks around IC601, the 64-leg M50965-628 chip in the mechacon circuit. As some of the voltages were wrong I replaced the chip then switched the machine on and tried it with a cassette. The drum now revolved and the tape loaded satisfactorily, but the take-up spool kept faltering to a stop and the tape spewed into the mechanism. Progress, but there was still something wrong.

Checks in the associated circuitry showed that the voltages around the M54644BL chip IC604 were haywire. Fitting a new one restored the machine to full working order.

Well, I'd had to work for results that time, but I'd won. Perhaps, for a change, I was going to have a good day.

Mrs Libber's Sanyo CBP2145

My next caller put an end to this hope. I wish Mrs. Libber had gone to Snoddies. They can take strident, mouthy women in their stride. She asked for a house call, which wasn't on, even though her set had only a "slight fault". So she sent her husband along with it. The set turned out to be a 22in. Sanyo CBP2145, which is fitted with the E2 chassis. Later that evening she phoned to ask whether it had been done. It hadn't.

Next day I put the set on the bench. There are two channel selector buttons, for up and down, at the front. The trouble was that they didn't work until the set had been on for about five minutes. After a spell with the freezer and hairdryer I decided to take out the front panel to apply a little contact cleaner and resolder the joints, which is faster to say than do. Operation of the set seemed to be better after doing this but it was still not good enough. So I set about obtaining a manual and meanwhile had a word with Sanyo. I was advised to change C398, a 100µF 16V electrolytic across one of the 5V lines. It made no difference, so I decided to wait for the manual.

Then the phone rang again and Mrs. Libber said she was getting impatient. She'd bought the set, at enormous expense, so that they could watch television. They couldn't because I had it. Why was it taking so long to fix such a slight fault? And she hoped it wouldn't cost much.

I should have given the set back to her then and there, but since I'd got involved I decided to press ahead. For the time being I had to work as well as I could without the manual. I changed one or two items in the supply, including the L78M05-RA 5V regulator IC395 and D395 which supplies it. Next day Mrs. Libber came on again and I suggested that she had the set back until I'd received the manual, studied it and

ordered any bits I suspected. In that way she'd have the use of the set until I was ready, hopefully, to have it back and cure the fault quickly.

Her husband, a rather sheepish fellow, came, shook my hand and offered to pay for my trouble so far. I told him that I wouldn't charge until the job was finished. Off he went with the set, smiling away, leaving me to reflect on why such shrews always seem to marry such decent chaps.

Then Greeneyes went to Spain for three weeks, with our eldest offspring, leaving me to look after the three youngest ones. I assured her that I could cope. In no time at all we were all down with flu and I was too ill to work. By the time I'd recovered the house was full of TVs and videos brought in for repair. I hardly knew which way to turn.

My first caller was Mrs. Libber. The set now changed channels perfectly she said. It must have been a bit of dust on the controls, so I needn't attend to that. But I'd obviously done something to the set because there was now sometimes a noise on the sound, accompanied by a faint chirp from within.

"I can't take it anywhere else" she said, perhaps sensing that I was a little less than fond of her, "because since you caused it you'll know at once how to put it right." Her husband brought the set, all apologetically, into the workshop and when he'd gone I put it on test. Within a couple of hours Mrs. Libber was on. "Have you got it right? I miss my television set."

The set behaved itself for hours, then I heard a slight "ccrr-ing" noise that seemed to come from the line output transformer. I placed a blanket over the set and it was soon chirping enough for me to be able to investigate. The noise definitely came from within the line output transformer, and now the brightness was affected as well.

I had an identical Fisher set awaiting a line output transformer. It arrived as I was working on the Sanyo set. The part numbers matched, so I fitted the new transformer, all £30 worth of it, in Mrs. Libber's set. As a cross-check I installed the chirping transformer in the Fisher set. After a while the Fisher began to chirp, and a few hours later the transformer suddenly warmed up and died. Meanwhile Mrs. Libber's set was behaving perfectly with the new transformer. Then suddenly she was back, with her husband.

"I'm not happy with the time you've taken on our set" she said. "You're still running your little advert, so you can't blame pressure of work. I know that you've been ill, but we can't help that. I came to you because I wanted service. We've been to the Weights and Measures about you."

I glanced at Mr. Libber. "Are you better, Mr. Bullock?" he began, smiling nervously. She glanced at him and his smile went.

The set seemed to be working all right with the new transformer, but I wanted to be sure. I ignored Mrs. Libber and addressed her husband. "If you telephone tomorrow I may have good news about your set." Off she strode, with her husband in tow.

The set continued to work well after being boxed up. So next day I asked him to collect it. While waiting for him I pondered on what to do about charging. I'd spent a lot of time on the set and fitted an expensive line output transformer that I now had to re-order. If I made a charge I'd be stuck with Mrs. Libber in the event of a further fault occurring. Or, come to that, if a passing aeroplane fluttered her picture or the programme went off the air.

When Mr. Libber called I told him that I wasn't happy about my dealings with his wife and didn't want to see or hear from her again, that fitting a new line output transformer had cured the latest trouble and that there wouldn't be a charge.

DECLARATION OF QUALITY

AS DISTRIBUTORS OF QUALITY VIDEO SPARES FOR THE LAST TEN YEARS, WE FULLY UNDERSTAND THE REQUIREMENTS OF THE REPAIR TRADE. THERE IS A CERTAIN QUALITY WHICH MUST BE MAINTAINED IN ORDER TO EXECUTE HONEST, RELIABLE REPAIRS. THEREFORE, WE GUARANTEE THAT ALL VIDEO SPARES SUPPLIED BY US ARE OF THE FINEST QUALITY AND WE CAN ASSURE YOU THAT ALL STOCKED ITEMS WILL BE DISPATCHED THE SAME DAY.

Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price
AIWA		AV-66		AV-77		AKAI		ALBA		ALCRA		AMSTRAD	
Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2511 £9.81	Video Head	VID 2713 £23.74	Video Head	VID 2713 £23.74	Video Head	VID 2676 £20.94
Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1756 £3.63	Pinch Roller	VID 1787 £3.63	Pinch Roller	VID 1787 £3.63	Pinch Roller	VID 2078 £3.05
Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 1049 £3.05	Belt Kit	VID 1049 £3.05	Belt Kit	VID 1049 £3.05	Belt Kit	VID 2578 £3.12
Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1002 £3.71	Idler Replacement Set	VID 1002 £3.71	Idler Replacement Set	VID 1002 £3.71	Idler Replacement Set	VID 1002 £3.71
Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81
Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27
Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54
CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75
AV-77		AV-77		AV-77		AV-77		AV-77		AV-77		AV-77	
Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29
Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87
Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32
Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54
Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81
Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27
Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54
CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75
AV-77		AV-77		AV-77		AV-77		AV-77		AV-77		AV-77	
Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29	Video Head	VID 2546 £15.29
Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87	Pinch Roller	VID 1755 £3.87
Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32	Belt Kit	VID 7519 £1.32
Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54	Idler Replacement Set	VID 1001 £3.54
Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81	Capstan Motor	VID 1005 £1.81
Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27	Capstan Motor	VID 1260 £24.27
Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54	Real Table Rubber Tyre	VID 1423 £3.54
CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75	CTL Unit	VID 2637 £59.75

NEW IN STOCK, A LARGE RANGE OF SLIMLINE REMOTES. JUST SUPPLY MAKE, MODEL & PART No. FOR AN IMMEDIATE QUOTE.

NEW FAX NUMBER 0902-29052

10,000 Line Catalogue available with order, or by request. SAE please (9" x 4") Telephone 0902-712083 773122 (24hr answering machines for Access & Barclaycard users.)

Prices quoted are subject to stock availability and may be changed without notice.

For quantities of 100+ per line - Please ask for special quote.

Orders from Govt. Institutions, Schools, National etc. accepted with official order.

All goods should be delivered within 4 working days

TRADE COUNTER OPEN DAILY 9am-5pm

Channel 5 Reception Problems

Harold Peters

By this autumn we should know to whom the licence for the fifth, and last, terrestrial UK TV channel has been awarded. Whoever it is looks to be in for a tough time. The franchise holder must undertake to retune or modify any equipment with which the Channel 5 transmissions interfere. This is a job that's easier said than done. There are likely to be other problems, as outlined in various recent letters in the correspondence pages. The purpose of the present article is to pull together as much information as is currently available to help prepare readers for what lies ahead. After looking at coverage we'll go over the theory behind possible causes of interference for the benefit of those who are a bit rusty on this side of things or who, for a quarter of a century, have been able to take the current channel allocations for granted.

The Broadcasting Act

The Broadcasting Act, 1990 didn't help. It merely made provision for a fifth TV service using mainly channels 35-37. Apart from the retuning proviso, the rest of its text was devoted to specifying the programme requirements. The Independent Television Commission asked National Transcommunications Ltd. and others to assist it in working out how the extra service can be fitted into the gap between Bands IV and V and the extent of the obligation for the licensee to retune users' equipment. Potential bidders can see what they are in for by getting the ITC report - a snip at £587.50 a copy.

Some Comments

Last December's Teletopics column mentioned that the licensee will not be responsible for retuning VCRs etc. if the interference is caused after the viewer has installed equipment (aerials etc.) for Channel 5 reception: it will be down to the viewer to get this done when the installation is carried out. A letter from Gareth Foster in the same issue pointed out that the intention is to cross-polarise the Channel 5 signal with respect to the other four at many transmitting sites, i.e. use vertical instead of horizontal polarisation. He reported that one reason for this is to avoid interference to Irish and French stations that already use the relevant channel. Bill Wright, in the January issue, put the point of view of the signal provider dealing with more programmes than the basic four plus VCR and satellite TV, experiencing difficulty in

finding room for them all let alone any newcomers. There must be many more of you who are equally worried but didn't write about it. So let's start by looking at the current channel allocations to see how Channel 5 fits in, see Fig. 1.

Channel Allocations

Up to now TV networking has been in Bands IV (channels 21-34) and V (channels 39-68). The space in between, channels 35-38, was left as a no-man's land occupied by signals other than TV, some of which have only recently been cleared. For the last decade or so almost all the extra equipment connected to TV sets, i.e. VCRs, video games, computers and more recently satellite TV tuners, has used this gap to add its signal(s) to the incoming networked four. VCRs usually leave the factory tuned to channel 36, which is a great help to installers.

Channel 5 is to use this gap (channels 35-38), with the majority of the stations using channel 35 or 37 as these two channels have been the easiest to clear of other services. About half a dozen or so mostly low- or medium-power stations will use a channel outside the 35-38 group. Table 1 lists the carrier frequencies for channels 34 to 39.

Coverage

The coverage plan grew from a combined survey for a possible "city TV" provision carried out in 1987. It was found that by concentrating on the areas of greatest population density a fifth service could reach 60 per cent of the population. Further work improved this to 70 per cent, using twenty five transmitters. This scheme was in the process of getting international approval by the time that the Broadcasting act was passed. By using some channels outside 35-38 the coverage has been further increased to 75 per cent and, at the time of writing, the extra eight transmitters are hopefully getting international clearance, bringing the total up to 33.

The "city TV" idea was included in the network plan to enable the licensee to arrange for local "opt-outs". It shows up particularly in some of the "extra eight" stations. Initially Winter Hill would have served both Liverpool and Manchester: now Storeton gives Liverpool its own station, with Winter Hill providing Manchester's "city TV". Likewise the Nottingham station leaves Sutton Coldfield to serve Birmingham, Craigkelly serves Edinburgh so that Glasgow can

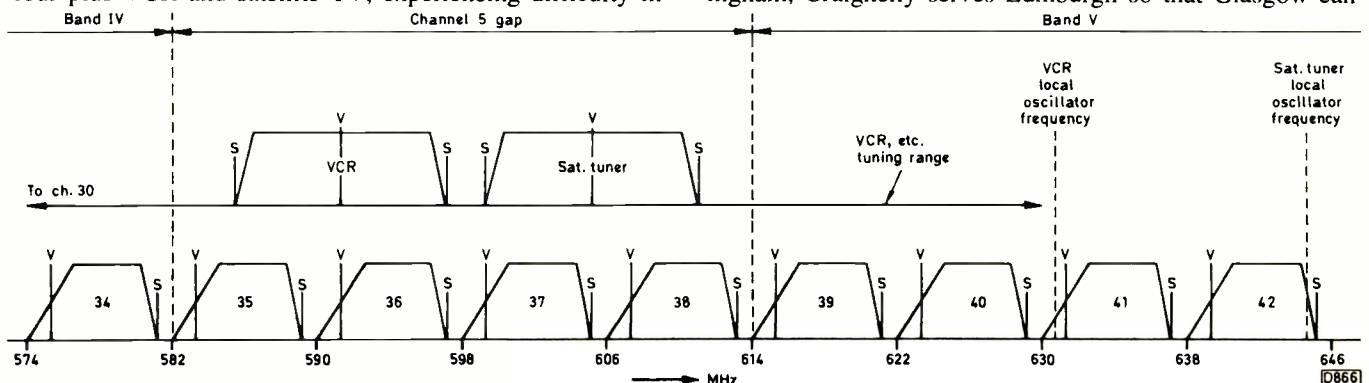


Fig. 1: The gap between Bands IV and V where most of the Channel 5 transmitters will operate. There are four broadcast channels but only two VCR/satellite tuner/video game etc. outputs can be accommodated as their modulators produce a double-sideband output that takes up to 12MHz.

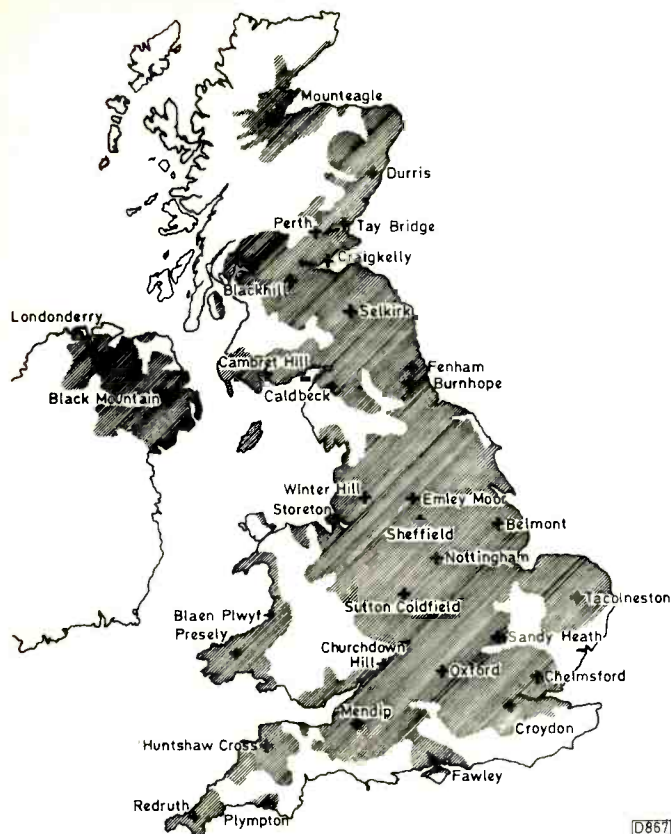


Fig. 2: Approximate predicted coverage of the Channel 5 service, using 33 transmitters.

have Black Hill, and Fenham serves Tyneside leaving Burnhope to cater for Teeside. Sheffield also has its own station so that Emley Moor can serve Leeds. The only area where a second station couldn't be arranged was the Bristol Channel, so Bristol shares Mendip with Cardiff. Other gaps in the frequency spectrum made it possible to have extra stations for Carlisle (Caldbeck), Cheltenham and Gloucester (Churchdown Hill) and Bedford (Sandy Heath). You've probably been checking this against the map (Fig. 2) and Table 2 and have already noticed that not all the transmitters are co-sited with existing main stations and that where they are the polarisation is usually different.

Co-channel Interference

The use of only channels 35 and 37 to cover the UK is asking for co-channel interference – we get enough of it with the present networks. Because of this, many of the present stations are offset from the nominal channel carrier frequency by plus or minus five-thirds of the line frequency (26.0416rec.kHz), which has been found to give the least

Table 1: Ch. 34-39 carrier frequencies.

Channel	Vision, MHz	Sound, MHz
34	575.25	581.25
35	583.25	589.25
36	591.25	597.25
37	599.25	605.25
38	607.25	613.25
39	615.25	621.25

Plus or minus offsets for co-channel operation. For Nicam sound add 5.52kHz to the sound carrier.

objectionable patterning. Even so with a transmitter stability of plus or minus 200Hz the degree of impairment can vary from downright annoying to being barely perceptible. To permit Channel 5 powers as high as they are planned, a precision of plus or minus 1Hz is required. This calls for reference via satellite to an atomic clock or something similar. In many cases the e.r.p. is similar to that of the existing four main-station channels. This would result in interference without the previously mentioned use of cross-polarisation. Seven of the proposed Channel 5 transmitters use horizontal polarisation, the rest being vertically polarised. Only at ten locations will the new service be co-polarised with the existing transmissions, Emley Moor being the best example. An extra aerial will almost certainly be required for Channel 5 anywhere else.

To keep Europe happy there's not a single main Channel 5 station along the entire south coast while the power at Tacolneston, Croydon and Redruth is substantially less than that for the present services.

Just to be helpful, a Home Office ruling barred the BBC from providing transmission services for Channel 5. This is the reason for most of the stations being on NTL landlord sites, including old 405-line masts like Croydon, Burnhope, Black Mountain etc. The exception here is Sutton Coldfield. Birmingham's Channel 5 station could have used the Lichfield mast, but BBC-1 from Sutton Coldfield would be on the "second channel" (channel 46) and a lot nearer to the city. The problem is solved by co-siting Channel 5 at Sutton Coldfield, cross-polarised. This is a typical n + 9 interference problem (see later).

West London has a problem of its own. Heathrow uses channel 36 for aircraft, Channel 5 is on ch. 37 and BBC-2 has been on ch. 33 for some thirty years. So viewers with a VCR and a satellite TV receiver won't have a lot of room in which to manoeuvre.

Aerials

Just to recap, the present receiving aerial groups are as follows:

A	chs. 21-34	colour code red
B	chs. 39-53	colour code yellow
C/D	chs. 48-68	colour code green
E	chs. 39-68	colour code brown
W	chs. 21-68	colour code black

The majority of existing aerials will not be suitable for Channel 5 reception. The areas where it might be possible, because the signals are co-polarised, are Perth, Caldbeck (Carlisle), Londonderry, Belfast, Newcastle, Leeds, Liverpool, Sheffield, Nottingham and Bedford. In these areas group A or B aerials are required for the present services: they should be able to pick up chs. 35-37 reasonably well.

Receiving aerials are tuned to have a flat response over most of their intended bandwidth. The elements are cut to a length that corresponds with half a wavelength of the wanted frequency. The folded dipole, which is the signal collector, is cut to the nominal centre frequency dimension. To achieve a wide bandwidth response the directors are cut shorter and the reflector elements are longer. It follows from this that if a high-band aerial (i.e. group C) is asked to pick up a lower channel there comes a point where the reflector is less than a quarter wavelength and acts as a director, effectively turning the array round to point the other way. Similarly if a low-band array is asked to pick up a higher channel there comes a point where its directors act as reflectors and it, too, points the other way. As a rule of thumb, the more ele-

Table 2: Channel 5 transmitters.

Transmitter	Ch.	E.R.P.	PO	Co-sited services	
		kW		E.R.P., kW	Aerials
Belmont	35V	500	-	500	A H
Black Hill	37V	500	0	500	B H
Black Mountain	35V	500	-	0.025	B V
Blaen Plwyf	35V	100	-	100	A H
Burnhope	35V	500	-	Radio	
Caldbeck	56H	10	0	500	A H
Cambret Hill	37V	20	-	16	B H
Chelmsford	35H	1	-	None	
Churchdown Hill	48H	1		Radio	
Craigkelly	48V	4		100	A H
Croydon	37V	250	+	LBC radio	
Durris	35V	500	+	500	A H
Emley Moor	37H	870	+	1000	B H
Fawley	35V	2	0	None	
Fenham	37V	2		2	A V
Huntshaw Cross	35V	100	0	100	C/D H
Londonderry	37V	10	0	10	B V
Mendip	37V	126	-	500	C/D H
Mounteagle	35V	100	0	Radio	
Nottingham	34V	2	+	2	A V
Oxford	35V	200	+	500	C/D H
Perth	35V	2	-	2	B V
Plympton	35H	2.5	-	2	C/D V
Presely	37V	100	+	100	B H
Redruth	37V	3	-	100	B H
Sandy Heath	39H	10	-	1000	A H
Selkirk	35V	50	0	50	C/D H
Sheffield	67V	2.5		5	A V
Storeton	39V	2.8	0	2.8	A V
Sutton Coldfield	37V	1000	0	1000	B H
Tacolneston	37V	30	-	250	C/D H
Tay Bridge	37H	2	-	0.5	B V
Winter Hill	35V	500	+	500	C/D H

V = vertical polarisation, H = horizontal polarisation, PO = precision offset.

ments an array has the more abrupt is the transition. So in general it looks like installing another array where Channel 5 is required.

Vestigial Sideband Transmission

As with the present services, Channel 5 will use vestigial sideband transmission. This is something you've probably taken for granted for the last thirty or so years, so a recap won't be amiss.

To save spectrum space the vision modulation, in the form of a.m. sidebands, is radiated at only frequencies higher than the carrier - or at least they would be were it not necessary to attenuate the carrier itself to keep the signal proportions right. As you can see from Fig. 3, this is done by a slow roll-off of the sidebands below +1.25MHz, reaching zero at -1.25MHz (with respect to the carrier). The f.m. sound is 6MHz above the vision carrier while the Nicam sound is at +6.552MHz. The vision carriers are spaced 8MHz apart, so between the end of Band IV (ch. 34) and the beginning of Band V (ch. 39) there is 32MHz of space into which four more vestigial sideband channels can be fitted.

This is fine for broadcasters. But your VCR, satellite

receiver etc. has a simple modulator without sideband shaping, also a sound carrier that pops up at each side of the double-sideband signal (refer back to Fig. 1). This incidentally explains why you can so often get two tuning peaks when tuning a TV set to a VCR that's playing a tape or in the E-E mode. It's better by far to bring up the "bars" using the switch at the back. In this mode there's no sound carrier to fox the TV set's a.f.c. system, but we digress.

Thus the output from a VCR/satellite etc. modulator occupies a full 12MHz, so you can get only two "channels" into the no-man's land between Bands IV and V. Because such modulators are tunable five channels either side of ch. 36 they can be shifted well away from any potential Channel 5 signal, but this is where the fun starts, because it's not only the frequencies between chs. 34 and 39 that can produce patterning interference.

Patterning

All VCRs, TV sets etc. use the superhet principle, with the local oscillator on the high side. The vision i.f., which is the difference between the local oscillator frequency and the frequency of the carrier being received, is 39.5MHz (or maybe

the Euro 38.9MHz). One result of the frequency conversion process is that the sound and vision carriers change place. Thus the sound i.f. is low at 33.5MHz (Euro 32.9MHz). It's normally suppressed in favour of the intercarrier sound (6MHz) and gives no problems, which is as well since the vision carrier gives us plenty to contend with.

Consider ch. 36, whose vision carrier frequency is 591.25MHz. The local oscillator frequency of a VCR with an i.f. of 39.5MHz will be 630.75MHz, pushing into ch. 41 with which it will interfere. Another source of patterning occurs at twice the i.f. (79MHz), in this case 670.25MHz, the equipment's "second channel". This comes around chs. 45 and 46.

We thus have the likelihood of herringbone patterning in channels 41 and 45/6 caused by a working VCR or satellite TV tuner. Because of the channel spacing from the original carrier this is known as $n + 5$ and $n + 9$ interference. These are the most common and most difficult to shift forms of interference. Vision i.f. harmonics continue to appear at intervals of 39.5MHz right up the band as far as the region of ch. 60 and can cause trouble especially when the incoming u.h.f. signal is weak in comparison.

An interfering signal at -26dB (voltage) is still perceptible enough to be irritating, which means that with a wanted signal at just below the threshold of comfort, say 500 μ V, a mere 25 μ V of interference can irk mightily. It's viewers whose main station uses Band V frequencies that will be most likely to suffer from the start up of Channel 5. It's a simple enough matter to detune the VCR etc. away from the new Channel 5 station, but you must ensure that in doing so you are free from interference on the higher in the band stations required. If you have more than one item of auxiliary gear (VCR, satellite TV tuner etc.) have them all up and running while you, or your friendly local Channel 5 representative, is doing the retuning.

If Band IV signals are being received, tuning the VCR etc. to a channel higher than the Channel 5 one should be all that's needed, but with more than one item the modulators may run out of range before you can clear the channel. Most in-built modulators will tune five channels either side of ch. 35 but, as mentioned earlier in the case of West London, this leaves little room in which to move about when Channel 5 has been allocated ch. 37, Heathrow is still using ch. 36 and BBC-2 has been using ch. 33 since u.h.f. broadcasting began.

Cross-modulation

Cross-modulation is most likely to be a problem with non-co-sited transmitters where reception of a weaker Channel 5 signal from some distance away is required close to a strong local station. The TV set will display both the wanted and unwanted pictures - amongst other things.

Cross-modulation occurs when the r.f. amplifier transistor in the tuner is overloaded. It then behaves as a non-linear

amplifier (call it a detector if you prefer). As a result, mixing takes place between the incoming signals. If all the incoming signals are of equal strength, cross-modulation can be overcome by applying a.g.c. to the r.f. amplifier transistor to reduce its gain so that it behaves as a simple linear amplifier.

To avoid mixer noise putting snow on the picture, the start of the r.f. a.g.c. action is normally delayed until the input rises above 3mV: the a.g.c. crossover control sets this delay. With an input of less than 3mV a.g.c. is applied to the i.f. amplifier. If the wanted signal is say 1mV and an unwanted one 10mV, the a.g.c. output from the detector, being based on the wanted signal, will not be large enough to switch control to the r.f. amplifier, which as a result will overload. As long as the difference in signal level is not too great, careful adjustment of the a.g.c. crossover potentiometer to start r.f. control earlier will help. Economics assist here: if the signals are strong a simple aerial is used, keeping the input levels down. Unfortunately, being flatly tuned the r.f. amplifier tends to act on the sum of all the signals it receives. Thus with 10mV each of VCR and satellite TV receiver output on top of all the other inputs it's driven towards the overload point.

Retuning

Whilst on economics, let's end the theory part by looking at how Channel 5 will be expected to tackle the retuning. Retuning is the collective word used by the ITC to cover all forms of interference removal, including the fitting of filters etc. Potential Channel 5 licencees expressed so much concern about this that the ITC issued additional guidance last January in question and answer form. This goes as follows.

Who will do the retuning? This is up to the licencee: whoever he recruits or trains must satisfy the ITC's definition of competence to do the job in a "proper manner".

Can viewers do their own tuning? Certainly. But help can still be obtained if this is unsuccessful.

Will there be delays? It's hoped that much of the retuning will be done before the start of transmissions, using test transmissions which will be kept as short as possible to avoid troubling unconverted equipment. Requests for retuning should be honoured within 21 days, or seven days once the service begins.

What if the trouble recurs? If a second Channel 5 transmitter comes into operation nearby for example and further help is required this remains the broadcaster's responsibility and expense.

How will viewers know what's causing the interference? The licencee is expected to publicise the start-up date for the Channel 5 service in each area and to encourage requests for retuning.

What about fiddles and malpractice? This one is still being worked on.

In Conclusion

It looks as if we're in for an interesting time. A lot could change before the start of the service, but it would be a pity if the "city TV" concept was watered down. That's my view anyway, and while being personal I must thank the ITC's Engineering Information staff for keeping me up to date and for permission to reprint their coverage map.

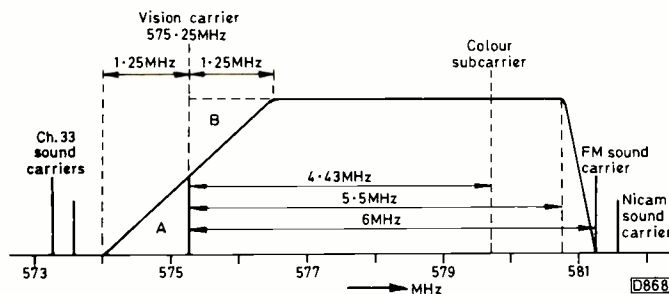


Fig. 3: The frequency spectrum of ch.34 showing the vestigial sideband arrangement. The roll-off begins at +1.25 MHz with respect to the vision carrier: sideband area A compensates for the missing area B.

Long-distance Television

Roger Bunney

Now that the summer is here F2 layer propagation has lessened considerably and we can hope for a dramatic increase in Sporadic E (SpE) propagation. We are however still high up on the descending slope of Solar Cycle 22: my experience gained over the past thirty years suggests that as a result the 1992 SpE season will be little better than last year's indifferent one. Hopefully I'll be proved wrong!

There were in fact a couple of good days for SpE reception during April. Tropospheric enhancement also occurred on several days, with widespread reception on the 6-10th across much of the UK. The 6-8th were the best days. On the 6-7th there was extensive reception of v.h.f./u.h.f. signals from Scandinavia and also reception from Germany and Luxembourg. Of particular note were certain of the new Swedish TV4 transmitters (chs. E46 and 50). There were fewer Scandinavian signals on the 8th, but the "usual" Benelux Band III/u.h.f. stations were present instead. A German relay station was noted transmitting the SAT 1 service - check ch. E52 during the next opening. The 9th was similar to the 8th: on the 10th reception was more from the south, with Spanish u.h.f. transmitters being received in the south west - Canal Plus Espagne was seen using the PM5544 test pattern.

The only F2 reception during April consisted of midday sightings of Iran and Dubai ch. E2 on the 12th.

The SpE log is as follows:

11/4/92	TVE (Spain) chs. E2, 3.
17/4/92	TVE E3; DR (Denmark) E3; TVR (Rumania) R2.
20/4/92	DR E3; HTV (Yugoslavia) E3.
21/4/92	+PTT (Switzerland) E2, 3; DR E3.
22/4/92	+PTT E2; TVE E2, 3; SVT (Sweden) E3; NRK (Norway) E4; CST (Czechoslovakia) R1, 2.
23/4/92	+PTT E2; NRK E2; SVT E2.
24/4/92	+PTT E3; DR E4; JRT/HTV E3; RTP (Portugal) E2; DR E4; ARD (Germany) E2; MTV-1 (Hungary) R1; TVE-2 E2.
26/4/92	NRK E2; TVE E2, 3.
3/5/92	RAI (Italy) IA; DR E3; ARD E2; NRK E2, 3.

Our thanks to Brian Williams (Penarth), Roger Fussell (Torpoint), Simon Hamer (Powys), David Glenday (Arbroath) and Peter Schubert (Rainham) for sending in reception reports.

Exiting news from Garry Smith (Derby). Comparison of Gulf War pictures in a BBC-2 documentary and his own shots of F2 layer reception has confirmed that he received the Egyptian ch. E2 second network transmitter at Dumyat - power is only 900W e.r.p. Other photographs of clocks and logos confirm Egyptian reception. The signal strength was very high and, by F2 standards, the single signal hop was short. Our congratulations to Garry on this excellent reception. In view of the number of other mystery F2 loggings on ch. E2 we need perhaps to reconsider the transmitters in Egypt and the Lebanon.

Aerial Techniques has just published its latest (and larger) catalogue, which is packed with TV reception and satellite TV goodies for both conventional and DX reception. It's

available at just £1 including UK postage from Aerial Techniques, 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH (0202 738 3232).

News Items

Sri Lanka: Various new services have either started or are due on-air shortly. The Teleshan company is to start a service using chs. E3, 4 and 21 (some reports suggest E2 and 3). Maharaja Television is now in operation, run by Singapore interests. Sunflower Systems Ltd. is setting up a local service based in Colombo, with the transmitter at Nuwara Eliya.

Cyprus: A pay-TV service called Lumiere Television (LTV) has started in Nicosia and is to be extended to Limassol and Larnaca. The Irdeto system, similar to M Net, is used for scrambling. Transmissions are from 1700-2400.

France: The La Sept channel operators are discussing with Arte Deutschland TV GmbH, a subsidiary of ARD and ZDF, a new service that will take over the La Cinq transmission facilities and channels.

Malaysia: Kuala Lumpur is likely to have two new services by next January, SNS (Subscriber News Service) and TV4.

Singapore: There are plans to start three Pay-TV services using u.h.f. channels.

Portugal: SIC (Independent Media Co.) and TVI (Independent Television) are to set up services. SIC hopes to be in operation this winter, using RTP transmitter facilities; TVI will establish its own transmitter network.

Andorra: The ORTA service has been suspended following the cessation of funding by the government.

Zimbabwe: A second TV network is to be established.

Czechoslovakia: The OK3 network in Bohemia and Moravia is to continue until the end of the year. Czech TV is now operating from a new ch. R41, 100kW e.r.p. transmitter at Domazlice/Vrani. Zlin-TV is carrying out tests from the old OK3 Zlin ch. R51 transmitter.

The 50MHz Amateur Band: Amateurs are now active in this band in Lithuania, Estonia and Latvia: there are also two amateur transmitters in Greenland. Transmissions are prohibited in Monaco, where Tele Monte Carlo holds the rights to the old 819-line ch. F2 that covers the 50MHz spectrum. Though it hasn't used the channel for many years TMC refuses to relinquish the allocation. This is also preventing French amateurs in the Alpes-Maritime region from using the band.

New DX Tuner

HS Publications, 7 Epping Close, Mackworth Estate, Derby DE3 4HR has introduced a new DX tuner, Model D400, that covers Bands I/II/III and part of the u.h.f. spectrum. The i.f. bandwidth can be varied and the output is at u.h.f. for feeding to a domestic TV set. Price is around £50. We propose to include a review of this simple to use tuner next month. Meanwhile further details can be obtained by sending an s.a.e. to the above address.

New TV Networks

The BDXC has supplied details of the Norwegian TV2 network that's due to come into operation in early September. The u.h.f. channels will be as follows: Odderoya/Kristiansand E30; Mandal E24; Kvinesdal E40; Arendal E25; Lillesand E22; Fevik E30 and E54; Mandvikheia E47; Vennesla (Krist. N) E53; Sogne (Krist. W) E32; Grimstad E42; Tvedestraand E27. Oslo and Bergen will probably use ch. E12.

The Finnish government has granted nine licences to operate experimental local TV services in thirteen regions. They

last until June 1997. Transmitter locations are: Savolinna, Rauma, Kouvola, Lammi, Narpio, Savitaipale, Ylivieska, Kristiinankaupunki and Korppoo. These are all small towns: applications to run services in Helsinki were rejected. Our thanks to Perti Salonen (Vaajakoski) for this information.

Satellite News

We paid a visit to the Cable and Satellite 92 Show at Olympia during the month. To us it was less interesting than last year as there were fewer small traders offering "bits and pieces" and essential components at bargain prices. This is partly due to the demise of the black-box industry that kept many small dealers in business offering low-price Filmnet decoders. Many new receivers were on display. Echo-sphere's manual SR50 receiver continues to be popular despite it being "all knobs". The company launched its new ultra-low threshold weak-signal LT530 receiver which is intended for the African/Middle East market. It looks like a promising development and we hope to review it shortly.

Several companies had long Yagi aerials in stacked formation for either S Band Arabsat or C Band (4GHz) reception. Space and Scientific (Reading) showed a massive C Band quad-stack Yagi with a claimed gain approaching that of a 2.4m dish – around 36dBi. The boom length is over 2m. This company has had considerable success with an S band version and produced the C band array as a high-gain, low-profile system that avoids the visual impact of a large dish. The Bentley Walker Group (Hayling Island) also showed various S Band Yagi systems along with specialised equipment intended for use in the Middle East.

CNN International is now using transponder 28 (11.62GHz vertical) at the 19°E Astra slot in addition to the feed via Intelsat VI F1 at 27.5°W – the latter feed is to be transferred to Band C. Unfortunately the Astra feed is to be scrambled at a later date. Astra is apparently being used because of the greater coverage, extending to Spain and the Canaries. Incidentally CNN International is also to provide a 24-hour DTH service via the Japanese Superbird B satellite.

September is likely to see the start of a BBC/Thames Television channel via Astra, initially clear but with Videocrypt encryption starting next spring.

Television New Zealand is seeking funds for a satellite channel with a footprint covering Asia via the Palapa craft. ABC Australia is also considering a satellite channel with Asian coverage.

German broadcaster Deutsche Welle is to start an equivalent of BBC World Service TV from Eutelsat II F1 at 13°E, initially starting with four hours of transmissions a day. The satellite already carries DW's external radio service. It also carries a daily news exchange between Capital Studios in Israel and Visnews, London.

Intelsat has signed an agreement with China Great Wall Industry Co. to use a Long March rocket to launch a future Intelsat bird. Discount terms have been introduced by Intelsat for broadcasters seeking to use transponders with digital sound carriers that give CD quality audio with only 25 per cent of the bandwidth required for traditional modulation.

The TV Plus 11.67GHz (horizontal) channel via Eutelsat II F3 at 16° E has been carrying 16:9 format transmissions from time to time since last February, with Matsushita Satbox encryption on occasions. Der Kabelkanal (11.09GHz hor.) via Eutelsat II F1 at 13°E is to adopt scrambling shortly.

Finally some decisions from WARC '92 relating to satellite transmissions. The Broadcast Satellite Service – Sound (BSSS) band has been agreed as follows. Worldwide 1.452-1.492GHz using Digital Audio Broadcasting (DAB) only, but on a secondary user basis in Europe until the year 2007. An

What you've all been waiting for...!

- ✓ Multi-standard TVs & VCRs
- ✓ Satellite Equipment
- ✓ Signal Strength Meters
- ✓ TV DXing Equipment
- ✓ Rotators
- ✓ Masthead Amplifiers
- ✓ Filters
- ✓ Accessories

It's now available!

Write in for your copy today!

Building on our success story over the past decade, we are proud to present our latest catalogue, now regarded as a reference work in its own right for both the trade and enthusiast markets.

We've got it all listed, from satellite equipment to TV-DXing, from SECAM/PAL transcoders to Canal Plus decoders, from an F-plug to a multi-standard video recorder, from a VHF/UHF signal strength meter to an NTSC/PAL/SECAM teletext TV.

We've even developed a full facility manually tuned enthusiasts satellite DXing receiver to find those weak transponders. And we've stocked all those little bits and pieces that no-one else keeps.

Send £1 for our glossy brand new 34 page catalogue, which you will receive back by return of post.



11 Kent Road, Parkstone, Poole Dorset BH12 2EH
Tel: 0202 738232 Fax: 0202 716951

Aerial Techniques

additional BSSS band for exclusive US use is 2.310-2.360GHz, and a secondary band 2.400-2.450GHz. A further BSSS band, 2.535-2.655GHz, will be used in parts of Asia. A new worldwide primary band has been allocated from 2007 for HD-TV: in the Americas this will be 17.3-17.8GHz, elsewhere 21.4-22.0GHz.

Cable Losses

The feeder is often overlooked when the merits of an aerial system are being considered. Yet the cable is perhaps more important than the aerial itself, since the few precious microvolts of a rare DX signal can easily be lost when inferior cable is used. Unfortunately the quality of coaxial cable has deteriorated over the past decade, due in part to the rising price of copper. The conductive braid often resembles fragile tinsel wire, the result being inferior screening. When you are considering the purchase of cable, pay attention to its electrical and physical construction as well as the claimed attenuation figures. If in doubt, the now readily available satellite

Table 1: Cable attenuation figures (Volaxial range) in dB/100m.

Frequency	RF60	RF75	RF100	RF125
50MHz	7.86	6.81	5.10	4.59
100MHz	11.22	9.72	7.29	6.57
200MHz	16.05	13.89	10.45	9.42
500MHz	25.85	22.36	16.93	15.30
650MHz	29.65	25.67	19.47	17.61
850MHz	34.15	29.57	22.48	20.36

TV coaxial cable can be used: this has the conventional 75Ω impedance and in addition has a plaited screen and an over-laying copper tape.

Attenuation figures are revealing. If a considerable run is required the best quality cable available within your overall budget should be used. As an example, Table 1 gives the attenuation figures in dB per 100 metres for the Volaxial range, which consists of four types. The RF60 is mainly intended for short runs with low v.h.f. applications while the top of the range RF125 is primarily for u.h.f. use. Remember that a 6dB voltage drop represents a fifty per cent fall. The overall thickness of RF60 cable is 4.7mm, which compares with 7.61mm for the RF125 type.

When installing cable avoid tight bends, do not hammer staples on to the cable tightly and beware of braid whiskers

that can short to the inner conductor at the aerial terminals or coaxial plug.

A remarkable new type of feeder, called Cavo-flex, was recently reported in *Six News*. It actually provides gain! Because of its design, which features a 3/8in. diameter internal vacuum cavity, the 0.75in. solid feeder increases signal power by up to 3dB per 100ft. The vacuum cavity has nil signal resistance, resembling the characteristics of free-space propagation. Before you all rush out to Maplins however Cavo-flex is not available in the UK. Its price would be very high, and because of its method of construction it's far less flexible than conventional coaxial cable. It cannot be bent and will be unhappy being wound around an aerial rotor. An aerial feeder with gain does sound rather like an April 1st press release!

CD Player Casebook

Reports from Mike Leach
and P.J. Roberts

Denon DCD910

This player suffered from the all too common fault of skipping and jumping. In the past I've had one or two problems with the worm gear sticking in these machines, but in this case the laser assembly was the cause of the fault. It's the Sony KSS150A type, which was replaced by the KSS210A. The laser unit in these machines is nice and easy to change, not requiring a complete strip down. Just take off the bottom cover and move the plastic bar that holds the gear in place to one side: the laser unit will then come out from the top. Reverse this procedure when fitting the replacement. M.L.

JVC XLE3

This machine was fitted with a new laser unit as it wouldn't read the TOC. The manual said it was fitted with an Optima 2 but the ticket inside the machine said Optima 3. Anyway we fitted an Optima 2 and all seemed to be o.k. Then the trouble started.

First the machine came back with the complaint of skipping and jumping. As we couldn't find anything wrong we set it up and it seemed to be o.k. Three weeks later it came back again because of no sound, but no one told me that this was the same machine that had had the new laser unit fitted and was still under guarantee. We found that the cause of this new fault was the YM3815 digital decoder chip, so the machine was sent back to the customer as an uneconomical repair. Suffice it to say that the machine reappeared along with its rather unhappy owner. Apologies were made and a new YM3815 chip was fitted.

Hopefully the customer is now happy, but the story does highlight one of the problems we face in this trade. If your garage fits a new clutch and three weeks later the battery goes flat you buy a new one and have done with it. It's not as straightforward in the consumer electronics field: how do you try to explain to a customer who has just spent a lot of money on an item such as a laser unit that the player now wants say another forty pounds being spent on it within the repair guarantee period? It's not an easy one. I think it's best just to put such things down to experience. M.L.

Philips CD371

This player wouldn't spin the disc or read the TOC. On further investigation I found that in addition the laser didn't light. A quick check on the supply lines established that all

was in order here. I didn't suspect the laser at this stage and decided to look around the a.p.c. circuit. If you look at the circuit diagram you'll see that the laser is supplied from the 9V rail via R3532, transistor 6527 and R3533. Time for the meter again. A check around this circuit showed that transistor 6527 had 9V at its collector, so R3532 was o.k. Its base was at 0V however, so either R3530 was open-circuit or C2546 was short-circuit. Cold checks with the power disconnected showed that C2546 was indeed short-circuit. With a new 10μF capacitor installed the player found focus, read the TOC and played the test disc without difficulty. P.J.R.

Jamo DS50

This CD multiplayer/tuner/amplifier certainly gave me a run for my money. It all started with a simple CD player fault. The unit wouldn't read the TOC or play, nor would the disc spin up. On dismantling the unit I found that, due to hard grease on the sled worm gear, the pick-up was stuck half way along the slide rails. The worm gear was cleaned but the pick-up still refused to move. The trouble was that the sled motor driver transistors Q104 (2SB892S) and Q105 (2SD1207S) both had collector-emitter leakage and had destroyed their 2.2Ω feed resistors R147/8. They had probably been damaged by the jammed pick-up.

With new transistors and resistors installed the pick-up returned to its rest position, the lens moved and the laser lit. But focus wasn't found when a disc was loaded, so the disc wouldn't spin up. This time the cause of the trouble was the CXA1081M r.f. preamplifier chip. This was replaced and the focus offset adjustment was carried out. A disc was then loaded and play was selected. Focus was found and the disc spun up, but the tracking servo didn't lock.

At this point I noticed a couple of other burnt 2.2Ω resistors, R142/3. These are the feed resistors for the tracking driver transistors Q108 (2SB892S) and Q109 (2SD1207S) which were also leaky. The pick-up's tracking coil was checked and found to be o.k., so replacement transistors and resistors were installed. The E-F balance was adjusted and the focus offset and PLL adjustments were checked.

After all this I wondered whether anything else would be wrong. Taking my heart in my hand I loaded a disc and pressed play. Focus was found, the disc spun up, the tracking servo locked and sound came from the speakers. Also the test disc played all right. I reassembled the player and gave it a short soak test before returning to the customer. P.J.R.

Satellite Notebook

Nick Beer

A mixed bag of technical tales from the satellite department this month.

Interfaces

Last month I mentioned the Global interface which enables receivers designed for use with Marconi-type head units to be used with an electromagnetic polariser (there's also one that works the other way round). I found that it wouldn't work with a FUBA/Nokia polariser but had heard that it was o.k. with Racal units. I used it successfully with a Panasonic kit.

Having heard of my tests our sales department arranged to rent a Pace 9200 IRD to a customer who had purchased a top-of-the-range Panasonic TV set. The customer had said that he already had a dish and required only the receiver, so our salesman said we'd connect the two together.

The customer was some distance away in west Somerset and I went to do the job with little information on the installation. On arrival I found that the set was to be installed on the top floor of a large hotel, with access via a real warren of passages and tight stairways. The owner had installed the dish himself – the story as to how he came by a dish but no receiver was confused but seemed to relate to a house that had burnt down... He had fitted the dish right outside a fire exit, in a position where anyone intending to make a quick departure via the fire escape would have knocked himself silly immediately after going through the door.

The head unit was a Tatung Early Bird type with an electromagnetic polariser. A check with the meter showed that the dish had been aligned surprisingly well – it wasn't inclined quite enough. I set up the new TV set and tuner (lifting out a G11!) and found that use of one of the Global interfaces gave perfect results – alignment was far easier than with any other polariser I've tried.

The hotel owner's wife was rather on the friendly side and, judging by the collection of video tapes proudly displayed on shelves behind the set, she was an avid watcher of certain late-night German channels. The hotel's distribution system was arranged so that the output from a VCR or a satellite TV receiver could be fed to all rooms from the owner's flat. Mrs. hotel owner insisted that I showed her how to disconnect this should she want to watch something "privately"...

Tandy Receiver

I was recently asked to connect a Videocrypt decoder to a Tandy satellite TV receiver. It was a tiny affair, about six inches wide, that worked with a Marconi-type LNB. I'd not come across one before. Unfortunately there's no video output, so a decoder can't be connected. The customer didn't seem too surprised when he was told about this and willingly bought a new IRD from us. Thanks Tandy!

Local Interference

We've been getting a lot of calls recently to see satellite receivers and VCRs in the local, town area because of complaints of no vision or patterning. The cause of the trouble is that we have a new relay TV transmitter that uses channels

30, 40, 43 and 46. For customers who have a satellite TV receiver and possibly two VCRs the ch. 30-40 spectrum is getting busy and some careful tuning is required (can't wait for Channel 5, which in this area will be on ch. 35 from Huntshaw Cross!).

Despite being a local relay it's quite high powered – the BBC and NTL have been playing with the power since the station opened but there's still an imbalance between Channel 4 and the others (it's much higher). Good reception from the mast is possible many miles outside the intended service area, which means that its transmissions are being picked up on Huntshaw Cross aerials even though these are oppositely polarised and facing the wrong way. It's for this reason that the number of calls because of interference is far greater than might have been expected. When we explain to under-guaranteee satellite receiver owners that the problem is due to a new terrestrial transmitter some miles away they either think we're taking the Mick or say "I read about that trouble in *What Satellite?*", referring to the Eutelsat II F3/Astra 1B problem.

Beosat LM at 12GHz

We decided that it might be worth experimenting to see what we could get with our motorised system allied to the B and O LM in the 12/12.5GHz bands. So I fitted a Sharp multiband LNB with a noise figure of 1.3dB nominal in place of the 0.9dB, 11GHz LNB. This Sharp LNB is switched between the 11GHz and 12GHz bands by altering the LNB supply voltage from 12V to 18V. The Beosat LM has provision for this (LNB and LNB+ in the SETUP menu). You also have to type in the local oscillator frequency for the upper band, in this case 11.470GHz. We could get nothing at all however.

I checked that the switching worked and confirmed the local-oscillator frequency with Eurosat then phoned B and O who confirmed that the system wouldn't work unless the LM was equipped with version 3.0 or higher of the software. This did indeed get us some signals – more on this another time.

SMATV

There is, understandably, a lot of interest at present in SMATV systems: with higher than ever interest in the Astra transmissions there's a large potential market for communal systems. In terms of distribution frequency there's more than one way of going about an installation. I've recently encountered a couple of communal systems where the i.f. signal from the LNB is converted to a lower part of the u.h.f. spectrum and fed to viewers via the terrestrial u.h.f. distribution system. In one case each house has a single coaxial outlet plate whose output is split and fed to the TV set and a translator for the satellite i.f. The way these items were configured gave little thought to the likely life of the outlets!

One resident came to our shop and rented a TV set, a VCR and a satellite receiver, saying only that he was connected to a communal system and therefore didn't need a dish. When our installer arrived and found no satellite feed he concluded that a translator was required and asked the customer whether he had one or had arranged to have one provided via the Housing Association. The customer told him not to be so silly – the satellite receiver simply plugged into the TV outlet, into which he had, incidentally, already plugged a Y splitter to facilitate feeding a set in the kitchen. He wouldn't believe our installer until the two of them visited a neighbour who confirmed that he had "a box which cost £40". Our customer then complained about it all being a con. I became involved and suggested to him that £40 plus 22p a week was far cheaper than the £8 or so a month rental plus

£79.50 installation for a dish he probably wouldn't be allowed to erect anyway, but he didn't seem to want to see it this way – he then suggested that he would go to Radio Rentals for a dish!

Remote Control Interaction

We've discovered that the remote control unit used with the Finlux SR5100 IRD, a Cambridge made unit, interacts with the Ferguson Model 51P7 CTV receiver (TX98 chassis). Selection of certain functions will result in the TV set entering the AV or tuning mode, which is most inconvenient. This is something to bear in mind before concluding a sale or rental.

Corrections

Reference was made in the May Notebook to "the Bang and Olufsen product development manager". This was due to an editorial misunderstanding. The reference should have been to my own firm's Bang and Olufsen business development manager. The editor apologises for any embarrassment caused. Bang and Olufsen markets its own motorised satellite TV system, which is quite different from the system we devised and have been supplying.

While on the subject of corrections, the AV expander unit in the B and O Link article (January) is Model AVX-1, not aux-1.

TEST CASE 355

Time was when we collected AV equipment from schools and colleges for service and repair and took it back afterwards. In these hard times, with educational budgets as tight as everyone else's, to save money the equipment is brought to us – if the geography master or the caretaker can't fix it! Neither of them could fix this Hitachi VT410, so the headmaster dropped it in on his way home and asked us to ring him with an estimate before doing any work.

The pupils at Easthurst School for young gentlemen hadn't been very gentle with this machine! The loading cradle was bent and the cassette flap had been wrecked. Apart from these two items, a deck service and head clean were required. As always in this trade we had to do most of the work before an estimate could be made: unless the machine is operational, how do you know what problems there are? Our final check before giving a quote for the cost of the repair was to carry out a recording test. And here we ran into a snag. Although playback of a good tape was fine, when the machine's own recording was played back there was a flickering picture that was overlaid with spots and blobs – the classic symptoms of a blocked head.

We cleaned the heads and made another recording, but the results were exactly the same. When one of the machine's recordings was played back via another machine the same spotty, flickering pictures appeared. We hooked up an oscilloscope to check the off-tape f.m. signal waveform: the shape of the envelope clearly showed that one head wasn't recording anything on the tape while the other head was working

normally. The heads were cleaned once more and were this time examined closely with a watchmaker's eyeglass magnifier. They appeared to be perfectly all right, as did the connections to the head drum at the plug and socket on the bottom of the preamplifier PCB.

This machine doesn't have a luminance recording current preset, but we reasoned that if there was anything wrong with the writing current both heads would be affected equally. Nevertheless we made a check at pin 2 of the head connector – this is the common record feed to both heads. The waveform here was good. Could one of the heads be faulty? If so, what sort of fault would completely remove the head's ability to record while leaving its reading ability intact? Could something strange have happened to the rotary transformer? The preamplifiers and heads were disconnected, at accessible points, and the continuity of all the windings was checked. Both transformers were o.k.

The REC 9V supply switches the heads into the record mode. It enters the head preamplifier PCB at pin 9 of CN6. A check showed that 9.2V was present here in the record mode. At this point we decided to change the head drum. Another VT410 that had been refurbished for rental provided a drum for the purpose. For a test like this there's no need to go through the complete alignment procedure. We soon had the substitute head installed and spinning. Once again playback of the workshop test tape was entirely satisfactory but only alternate fields could be recorded: the same spotty, flickering playback picture greeted our disappointed gaze.

The cause of the trouble was eventually found. It was a tiny component which we didn't even have to draw from the stores – there was a spare unused one in the machine itself! What was it? For the answer and another diagnostic puzzle, see next month's issue.

ANSWER TO TEST CASE 354 – page 588 last month –

The Tatung TRX1801 satellite TV tuner that was the subject of last month's test case had to be fitted with three new 12V regulator chips before it was truly repaired. The replacements would go open-circuit within a few days of being fitted, to the exasperation of the tuner's user, Mr. Tate, and the chagrin of the service department – especially poor Philbert who had to do the fetching and carrying.

During our tests in the workshop the tuner worked perfectly signalwise and the output from the regulator chip IC802 remained steady at 12V, monitored by a meter hooked up for the purpose. In fact without its case the tuner might have gone on working indefinitely, for the basic cause of the problem was overheating in the little regulator chip despite its heatsink. It got very warm indeed, too hot to touch for long. A check with another tuner of the same type showed that the current being drawn from the regulator was correct: but the other tuner's regulator didn't run nearly so warmly – and neither did its mains transformer!

This was the key to the diagnosis. In the faulty set the voltage applied to the 12V regulator (and indeed to the others, but they were not so distressed by it) was excessive because the mains transformer was defective – perhaps with a few shorting turns, or perhaps just out of specification. A replacement transformer solved the problem by reducing the dissipation of the third regulator we had to fit in the IC802 position. It's still in there and working.


BOOK HERE FOR DISNEY WORLD!

YES!
Your



catalogue can book you into.....

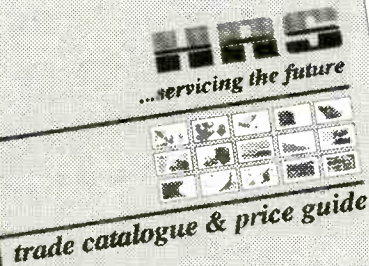Need a catalogue? phone our
SALES DESK on 021 789 7575
(recognised trade only)



1991/1992

DISNEY WORLD, FLORIDA

A fabulous family holiday for four at *DISNEY WORLD, FLORIDA*.



Plus

4 EURO DISNEY WEEKENDS

One of four
EURO DISNEY WEEKENDS

for two

Plus

MYSTERY PRIZES

Up to four
MYSTERY PRIZES
and there are hundreds to be won!



FOR ALL YOUR SPARES-AND MOST OF YOUR OVER THE COUNTER LINES INTO THE BARGAIN! OVER 25,000 LINES!

WHEN YOU CAN GET SO MUCH FROM HRS, WHY GO ANYWHERE ELSE?

GET INTO THE HRS CATALOGUE-AND BOOK YOURSELF A BONANZA!

SALES DESK

☎ **021 789 7575**

FREE FAX

0800 212179

ORDER NOW!

The choice is yours. And here's how to get it:

1. Make sure your next order to
2. Answer the four skilful fun questions on the
3. Send your entry back



is for

£50

OR MORE.

FREE ENTRY FORM

which will come with your invoice.

(Hint: many of the answers are already in your HRS catalogue).

FREEPOST

NO STAMP NEEDED

BY THE CLOSING DATE.



FIRST COMPETITION STARTS JUNE 1st, followed by three more - one after another - ending August 29th.

EURO DISNEY WEEKEND
for the first correct solution opened on each of the four closing dates.

MYSTERY PRIZE
Plus FOR EVERY Plus
CORRECT ENTRY

FABULOUS FAMILY HOLIDAY AT DISNEY WORLD FLORIDA*

* (or if preferred, 1-YEAR HIRE of a new 7cwt diesel van)

To the first all correct entry drawn from all four competitions.

FREE, SAME DAY DESPATCH ON ALL ORDERS, LARGE OR SMALL

HRS ELECTRONICS A Division of Ring Lamp Co. Ltd., Garrets Green Lane, Birmingham B33 0UE

TRANSISTORS Cont.

Table of transistor part numbers and prices, including models like 2SD1391, SDC1397, etc.

TD8180 ORIGINAL

Table of transistor part numbers and prices under the TD8180 ORIGINAL heading.

DIODES AND THYRISTORS

Table of diode and thyristor part numbers and prices, including models like BA157, BR100, etc.

ASK FOR SEMICONDUCTORS NOT LISTED

VIDEO HEADS

Table of video head part numbers and prices, including brands like AMSTRAD, FERGUSON, HITACHI, and PANASONIC.

VIDEO HEADS Continued

Table of video head part numbers and prices, including models like 3HSSU3N-NV430, 3HSS3N-NV777, etc.

ASK FOR VIDEO HEADS NOT LISTED

The above heads are new.

BELT KITS

A range of belt kits in stock from 60p to £2.40. Makes for most models available including: Alba, Akai, Amstrad, Ferguson/JVC, Fisher, Funai, GEC, Goldstar, Granada, Grundig, Hinari, Hitachi, Mitsubishi, NEC, Orion, Panasonic, Philips, Saisho, Samsung, Sanyo, Schneider, Sharp, Sony, Tensai, etc.



LINE OUTPUT TRANSFORMERS

Table of line output transformer part numbers and prices, including models like LOPT Hitachi CPT1476, LOPT Hitachi CPT2276, etc.

Other ITT transformers available

Table of ITT transformer part numbers and prices, including models like Fidelity all models up to 20" ZX3000, Fidelity Panel for ZX2000, etc.

Hitachi and Matsui LOPTs in stock

VIDEO MOTORS

A range of Reel Motors made by Ferguson, Hitachi, Sanyo, Sharp & Panasonic are available, please state model and make. We stock capston motors makes include Ferguson/JVC, Hitachi and Sharp.

Sharp Reel Motor Pulley only £1.20

Replacement of plastic pulley on a number of Sharp Reel Motors with the above metal pulley gives better rewind/FF performance.

IDLER ASSEMBLIES

Table of idler assembly part numbers and prices, including brands like FERGUSON, FISHER, HITACHI, PHILIPS, PANASONIC, SONY, and AMSTRAD.

PHILIPS

Table of Philips part numbers and prices, including models like VR6460 6920 Idler Arm (Original), DV464, 6462, 6463, 650 etc. Idler Kit, etc.

PANASONIC (All Original)

Table of Panasonic part numbers and prices, including models like NV370 Idler Arm Unit VXP0521 Gen, NV8600 8610 Play Idler VXP0243, etc.

SANYO

Table of Sanyo part numbers and prices, including models like Idler VHR1100, 1300, 1500, Idler VHR1200, 2300, 2500, 2700, etc.

AMSTRAD

Table of Amstrad part numbers and prices, including models like 4500, 4600 MOD KIT INCLUDES PINCH ROLLER AND IDLER CLUTCH, Limiter Post Assembly, etc.

REMOTE CONTROLS

Ferguson, Grundig, ITT, Philips, Pye, Sony, Hitachi, Matsui, Logik, Panasonic, Saisho, Salaria, Samsung, Tashiko, Tatung, Toshiba. Various models TV & Video From £10.00

MANY HITACHI TV REMOTE CONTROLS NOW IN STOCK

SONY REMOTE CONTROL RUBBER PAOS. STATE MODEL FOR PRICE

New Additions

Table of remote control part numbers and prices, including models like Universal Remote Control, Sony type RC670, RM670, RM673, etc.

TV ON/OFF SWITCHES

ITT, Philips, Decca, Thorn, Fidelity, Grundig, Sony and Hitachi. State model for price.

PINCH ROLLERS

A range of Pinch Rollers is in stock, most of them £2.80. Makes include Akai, Amstrad, Ferguson, Fisher, Funai, GEC, Goldstar, Grundig, Hinari, Hitachi, ITT, JVC, Marantz, Mitsubishi, NEC, Nordmende, Orion, Panasonic, Philips, Samsung, Sanyo, Schneider, Sharp, Sony, Tensai, Thomson, Toshiba etc. Please state model and make.

BACK-UP BATTERIES

Philips 1.2V Back up Battery £1.75, Philips 2.4V Back up Battery £2.80

Wider Range Available

OTHER SPARES

Table of various electronic spares and their prices, including Universal Video Copying Kit, Universal Copying Kit (Scart), Universal Camcorder Kit, Video Cassette Lamps from, CRT Anode Caps, Video Tape Splicing Kit, Hitachi TV Frame Module HM6251, Hitachi TV Frame Module HM6232, Cassette Housing Assembly by Ferguson, Cassette Loading Roller Assembly 3V23, 3V31, 3V32, 5.5V Back Up Cap, Degaussing Positor Blue, Degaussing Positor White, Cassette Housing Assembly Hitachi VT11, End Sensor for Hitachi VT63, 64, 65 (Pair), Cassette LED Sensor for Panasonic etc, I.C. Circuit Protectors, Clear Service Cassette, Push Button Unit Thorn TX90, Matsui/Saisho Limer Post, Cassette Housing Modification Kit for Sharp VCA113HM Series, Includes cassette switch and star sensor PCB Fault symptom No eject & intermittent load/unload, Video Idlers Spring Kit, Video Washer & E Chip Kit, Universal Video head Puller.

MODE SELECT SWITCHES MANY OTHER VIDEO AND TV SPARES IN STOCK

Back Tension Bands in Stock for Akai, Fisher, Hitachi, Ferguson, JVC, Mitsubishi, Panasonic, Sanyo and Sharp. Maintenance Kits available for Alba, Amstrad, Ferguson, Fisher, Goldstar, Goodmans, Granada, Hinari, Hitachi, JVC, Matsui, Mitsubishi, Nikkai, Panasonic, Philips, Saisho, Salaria, Schneider, Sentra, Sharp, Sony, Tashiko, Toshiba.

SEND FOR PRICE LIST.

Trade Counter now open Monday-Friday 9.00-5.30. Saturday 9.00-1.00. Nearest Underground Station - Southfields District Line.





OMEGA SATELLITE LTD.

INSTALLATION THROUGHOUT UK MAINLAND

SHOWROOM NOW OPEN

VIDEO PLUS
VIDEOING MADE
EASY)
INTRODUCTORY OFFER
£49.99

PACE SS9200 IRD
COMPLETE SATELLITE
SYSTEM (inc receiver
+ Dish)
£249.00

FIVE SKY CHANNELS
VIA THE MARCO POLO
SATELLITE
only
£35.00

FERGUSON INTEGRATED
DECODER COMPLETE
SATELLITE SYSTEM
(inc receiver + Dish)
£229.00

ASTRA
SYSTEMS
FROM
£99.99

NIMBUS IRD
COMPLETE SATELLITE
SYSTEM (inc receiver
+ Dish)
£299.00

SEE WHAT YOU'RE MISSING FROM SKY T.V.

INSTALLATION KIT – inc. Cable,
Clips, F. Connectors, Plugs, Fixing
Bolts, etc.

£11.99



SKY MOVIE CARDS
AVAILABLE

L.N.B.s from £49.99

Full range of accessories available

SPECIAL
LIMITED OFFER
MIDI HI-FI SYSTEM
only
£65

PHONE NOW:

0273 845066

SPECIAL
LIMITED OFFER
MIDI HI-FI SYSTEM
WITH C.D. only
£149.99



44 KEYMER RD, HASSOCKS, WEST SUSSEX

Trade Enquiries: 0273 842924

FAX: 0273 843140



PROFESSIONAL TRAINING IN SATELLITE INSTALLATION

Demand for Satellite Television both in the UK and Europe is increasing at an astonishing rate. In just two years over a million dishes have been installed in the UK alone. By 1996 over six million homes are expected to have a satellite system. **THIS MEANS OVER THE NEXT THREE YEARS SOME FIVE MILLION SATELLITE TV INSTALLATIONS ARE EXPECTED IN THE UK.**

These installations are now likely to come sooner, rather than later, given the recent coup by BSkyB in obtaining exclusive rights to broadcast live football coverage.

If you have a technical background and are interested in becoming a part of the satellite revolution then why not become a qualified satellite television engineer?

NETWORK TRAINING has trained over 200 engineers to date and can offer the following courses:

- Two day fixed and motorised systems installation and maintenance programme. Practical hands on training and useful business advice to enable you to set up as an independent operator. Recognised qualification on completion.

- Four day City & Guilds approved training programme covering installation of communal satellite systems for blocks of flats and hotels, known as SMA'TV. There are close to four million of these installations in the UK. City & Guilds qualification awarded to successful candidates.

All courses held at the University of London.



*For further information
and a free information pack
please contact us on*
071 837 3388.

**NETWORK
TRAINING**

RADIO CODE READER/RE-PROGRAMMER

Here is an opportunity to turn your IBM or compatible PC into a highly profitable tool. Our code-reader, connected to your PC, will read the security codes on leading makes of car stereo's. You can also re-program new codes or restore corrupted data. There is no need to spend thousands of pounds on a decoder that will decode everything. With our system, you only pay for ONE decoder and whatever software modules you require, currently PHILIPS, FORD, GRUNDIG, BLAUPUNKT, with more on the way. You will have access to our lifetime telephone support service and we will keep you fully informed of all developments.

The cost of the code-reader is £200.00 + vat and the software is £195.00 per module + vat, with discounts available if you purchase more than one module.

All enquires to:

ELECTRONIC SOUND SYSTEMS
62 High Northgate, Darlington, Co. Durham.
Tel: 0325 484089 or Fax: 0325 465921
Mobile: 0860 221099.

TUBES TUBES TUBES

14" Portable Tubes	from only £19
20" GEC/Hitachi	only £29
22" 20AX	only £25
20" KT3	only £39
14" narrow-neck portable tubes	only £39

12", 14", 20" mono	only £5
18", 19", 20" Delta	only £5
20", 22", 26" Redif. Mk III	only £5
22", 26" Thorn 9.6	only £5
26" Finlandia (670ALB22)	£5

Offers on quantities

Carriage and VAT extra

**Ring Irene or Jane,
giving tube number;
for price and availability**

**TRADE TV and VIDEO
SERVICE AVAILABLE
IN THE
MIDLANDS
AREA**



EXPRESS TV
The Mill, Mill Lane,
RUGELEY, Staffs WS15 2JW
Tel: 0889-577600
Fax: 0889-575600

VINASONIC DISTRIBUTORS

UNIT 4A ABBERLEY STREET
SMETHWICK
BIRMINGHAM
B66 2QU
ENGLAND
Tel: 021-565 1727
Fax: 021-555 5367

TRADE ANNOUNCEMENT

SONIC TV DISTRIBUTOR'S BUSINESS IS TAKEN
OVER BY US. NEW STOCK ARRIVING EVERY DAY

B-GRADE STOCK

+

EX-RENTAL STOCK

WE ARE VERY KEEN TO ESTABLISH NEW BUSINESS
RELATIONS WITH OUR UNIQUE IDEAS TO WORK
TOGETHER WITH SMALL OR BIG DEALERS

DIRECT LOAD DELIVERED TO YOUR DOORSTEP

F.S.T.
FROM £65

BASIC T.V.
FROM £15

TEXT
FROM £35

SLIMLINE VIDEOS
FROM £75

TOP LOADER
FROM £45

FRONT LOADER
FROM £55

QUANTITY
DISCOUNTS
AVAILABLE

BRAND NEW
VIDEOS
FROM £120

GENUINE UN-
TESTED STOCK
AVAILABLE

ALL PRICES ARE SUBJECT TO V.A.T.

EUROPE'S

LARGEST EXPORTER
OF EX-RENTAL TV & VIDEOS

AVAILABLE
FROM ALL
GOOD NEWSAGENTS

A new menu for Windows Users


Windows User is the new practical magazine to help you get the most out of your Windows environment.

Every month you'll enjoy a varied menu of news updates, features and reviews, making Windows User the essential reference for the computing environment of the 90's.

Make sure of your copy by ordering from your local newsagent **NOW**.

To subscribe call our **Credit Card Hotline** on **0789 200 255**

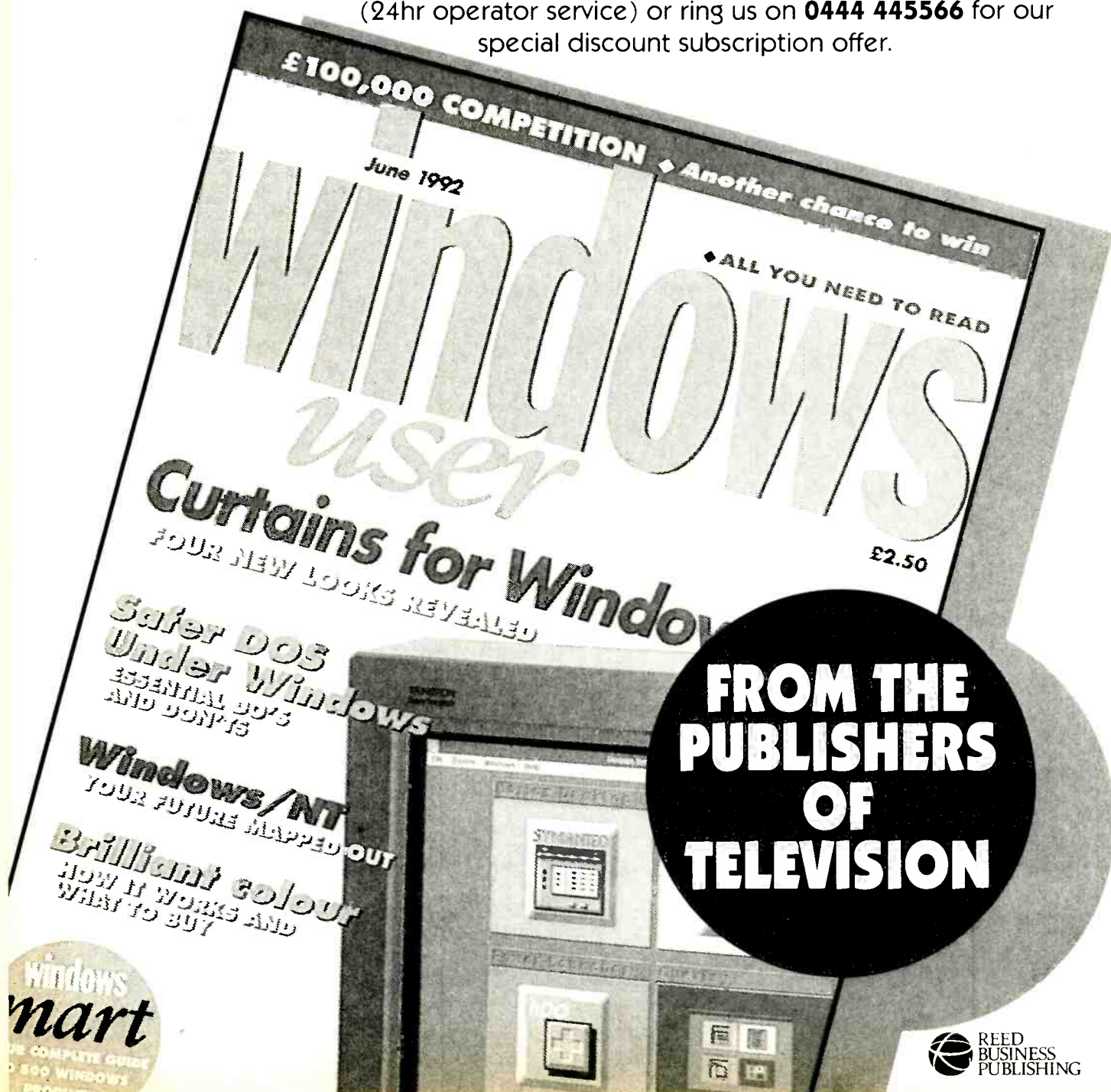(24hr operator service) or ring us on **0444 445566** for our special discount subscription offer.



VIDEO HEADS



Table listing various video heads from brands like AKAI, JVC, Matsui, and others, including model numbers and prices.

Table listing cassette tapes from brands like JVC, Matsui, Philips, and others, including model numbers and prices.

Table listing various motor components from brands like JVC, Matsui, Philips, and others, including model numbers and prices.

Table listing various belt kits from brands like NEC, Nikkai, and others, including model numbers and prices.

Table listing various rediffusion components from brands like Samsung, Sharp, and others, including model numbers and prices.

Table listing various idler components from brands like Hinari, JVC, Matsui, and others, including model numbers and prices.

Table listing various idler components from brands like Philips, Grundig, and others, including model numbers and prices.

REEL MOTORS



Table listing various reel motor components from brands like Amstrad, Ferguson, and others, including model numbers and prices.

CAPSTAN MOTORS



Table listing various capstan motor components from brands like Amstrad, Ferguson, and others, including model numbers and prices.

PLUS MANY MORE CASSETTE HOUSING



Table listing various cassette housing components from brands like Amstrad, Ferguson, and others, including model numbers and prices.

BELT KITS



Table listing various belt kit components from brands like Akai, Matsui, and others, including model numbers and prices.

IDLERS/ Take Up Wheel



Table listing various idler and take-up wheel components from brands like Amstrad, Philips, and others, including model numbers and prices.

IDLERS Cont.

Continuation of idler components from brands like Hinari, JVC, Matsui, and others, including model numbers and prices.

How to design your own satellite TV system and get it right ...



... with the **SATMASTER** program by *D J Stephenson, you can!*

requires
IBM PC compatible with
MS DOS 3.0 or higher
and 1Mb of hard disc

- Design your own system and test its performance *before* you install it!
- Quickly find essential dish setup angles: elevation, azimuth, polarisation offset for any satellite from any location in the World!
- Easy-to-use pop-up menu interface makes tedious tasks simple for everyone!
- Complete with User Manual!
- 20,000 word on-screen technical guide and context-sensitive help!
- Calculates full link budget including dish size optimisation ensures the best quality picture!
- Plot beamwidths and lobe patterns and judge potential interference from neighbouring satellites!
- Results and graphs can be output to screen or printer!

Includes satellite footprint and magnetic variation maps for Europe.

*Take out the guesswork ... order **SATMASTER** today.*

Swift Television Publications

17 Pittsfield, Cricklade, Swindon SN6 6AN Tel or Fax 0793 750620

ORDER FORM

Please send me _____ **SATMASTER** program(s) (3.5" disk) @ £35 each, postage FREE in UK, Europe add £2, Other add £4.

I enclose cheque/PO for £ _____ made payable to Swift Television Publications, or please debit my Access/Visa credit card,

No. _____

Expires: _____



Name: _____

Address: _____

Postcode: _____



C.T.V.

UNIT 5, THE PHOENIX BUILDING, RUSHOCK TRADING ESTATE,
DROITWICH ROAD, NEAR KIDDERMINSTER

TELEPHONE: 0299-251522 0836-585829/0860-809673 (24 HR)

**SUPPLIERS OF HIGH QUALITY EX-RENTAL
TELEVISIONS AND VIDEOS
LARGE STOCKS ALWAYS AVAILABLE
ALL AT COMPETITIVE PRICES**

Also available: 'B' Grade Products, Audio, Microwaves
and Complete Range of Televisions and Videos

OPEN: MON-FRI - 9.30-5.30

TEL: 0299-251522
0836-585829 / 0860-809673 (24 HR)
Fax: 0299-251543 **EXPORT ENQUIRIES WELCOME**

HOCKLEY DISCOUNT TELEVISIONS

14" MONO
PORTABLES
MAINS &
BATTERY
IN STOCK

V.H.S. VIDEO HEADS

FROM £6.25 → AND LOTS MORE!

**£180 VIDEO TAPES
ONLY 79p**

KARAOKE
TWIN TAPE
MIDI-SYSTEMS
From £48.50

13A
PLUG TOPS
ONLY 28p

UNIVERSAL REMOTE CONTROL MEMOREX AV⁴

Pre-Programmed only £15.95

BU508A
TRANSISTORS
ONLY 69p

50 WATTS
HI-FI
SPEAKERS
ONLY £30.00

TWIN-SPEED 'B' GRADE

VIDEO'S AT LOW, LOW PRICES

★ PLUS MANY MORE: OFFERS

100M ROLL
CO-AXIAL
CABLE £8.75

VIDEO SENDERS Only £4.75
(NON-CERTIFIED FOR U.K.)

OPENING HOURS
MON-SAT 9-7pm
SUN 10-2pm

**BEST PRICES ON FANS
IN TOWN**

ALL PRICES SUBJECT
TO VAT PLUS
CARRIAGE

i.e. 12" 3-speed Oscillating ONLY £10.95

P.I.R. FLOODLIGHT £18.50

**ALSO → ARRIVING DAILY - FRASH 'B' GRADE
TELEVISIONS, VIDEOS, WALKMANS, TELEPHONES,
ANSWERING MACHINES, MIDI-SYSTEMS,
CAR RADIO'S, ETC.**

**100's of TV/VIDEO COMPONENTS AND
ACCESSORIES IN STOCK**

GIVE JAZZ A BUZZ

140 Hockley Hill, Hockley,
Birmingham B18 5AN
Tel: 021-515 2003
Fax: 021-515 2004

WE HAVE MOVED TO
A NEW ADDRESS
ON THE SAME
ROAD

CAR PARKING ON
SITE. TRY US
- YOU'LL
LIKE US

CALLING SCOTLAND

WE CAN NOW SUPPLY GOOD CLEAN
WORKING BOXED B GRADE STOCK IN
YOUR AREA. PLEASE CONTACT US
FOR PRICE LIST AND FURTHER
INFORMATION.

CALLING IRELAND

NOW AVAILABLE DUAL STANDARD
BRAND NEW 21" REMOTE CONTROL
CTVs FROM £130.
ALSO DUAL STANDARD 14" REMOTE
CONTROL CTVs.

B GRADE STOCK RETURNED GOODS

14" Portables from	£70	14" Portables from	£25
20" Remote CTV from ..	£105	Front load VHS from	£50
20" Fasttext from	£140	Midi Hi-Fi's from	£20
L/P VHS from	£120	21" CTVs from	£40
10" Mains/bat from	£90	Radio Cassettes from	£15

GOGGLEBOX
DISCOUNT ELECTRICAL WAREHOUSE

TEL: LEEDS
0532-310359
ASK FOR ROBERT

ALL ABOVE PRICES PLUS VAT AT 17.5%

**BRAND NEW TV & VCR STOCK
IN STOCK NOW**

VCR SP/LP From £155.00
 25", 28" FST Nicam Fast Text £POA
 14" Portable, Remote £POA
 10" Colour Main/Battery, Remote £130.00

NIKKAI MULTISYSTEM TV IN STOCK

14", 20", 21" FST (VHF/UHF) PAL, SECAM, NTSC

AMSTRAD DD8900 Double Deck £279.00
 AMSTRAD STV20 CTV with Stereo Satellite Receiver
 and Decoder £279.00

NEW (B) GRADED FERGUSON STOCK

NEW 59P7 FAST TEXT £POA
 41P3 FAST TEXT £POA
 68K4BQ FAST TEXT WITH NICAM... £POA
 59L5Q Nicam Fast Text £POA
 FV37 (Nicam), FV41, FV42..... £POA

**EXCELLENT RANGE OF
EX-RENTAL TVs & VCRs THORN**

THORN TX9 Basic From £25.00	THORN FST Stereo/Text £POA
THORN TX9 R/C £POA	THORN 8940 (3V9) (Stereo)... £48.00
THORN TX9 Text £48.00	THORN 8941 (3V31) £65.00
THORN TX10 Basic £POA	THORN 8942 (3V32) £70.00
THORN TX10 R/C £POA	THORN 8943 (3V36) £115.00
THORN TX10 Text £POA	THORN 8944 (3V35) £POA
THORN TX10 Stereo/Text £POA	THORN 8945 £POA
THORN FST Basic R/C £75.00	THORN 8947 £POA
THORN FST Text £85.00	

MIDI SYSTEMS FROM £45.00.

CD HI-FI SYSTEMS FROM £110.00

NON-THORN VCRs FROM £35.00.



Fresh Stock arriving daily — ring for update on stock



**PORTABLES ★ LATE FST
TOP BRANDS ALL BOXED
IN STOCK — TOO MANY TO LIST**



LARGE STOCKS ALWAYS AVAILABLE

**REPAIR TAKEN ON SATELLITE RECEIVERS —
ANY MAKE — TRADE OR RETAIL WELCOME**

Brand New Handsets for TVs & Videos from only £7.50

★ ALL PRICES ARE SUBJECT TO VAT ★ (OFFERS APPLY WHILE STOCKS LAST) ★

OPEN MON.-FRI. 9 a.m. — 5.30 p.m. SAT. 9 a.m. — 1.00 p.m.

WHY TRAVEL THE WHOLE COUNTRY?

**RING OFF OR AMIN NOW ON DIRECT LINE TO
TV WAREHOUSE**

LEEDS (0532) 444200 FAX: (0532) 425777

MOBILE PHONE — 0850 326866 — 24HRS


EXPORT ENQUIRIES WELCOME

SUPERVISION

UNIT 16, TOWER WORKS, 2 GLOBE ROAD, LEEDS LS11 5QG
 OFF WATER LANE, NEAR HILTON HOTEL. EASY ACCESS FROM M1 & M62 (2 Mins)

W. TREE TRADE TVs

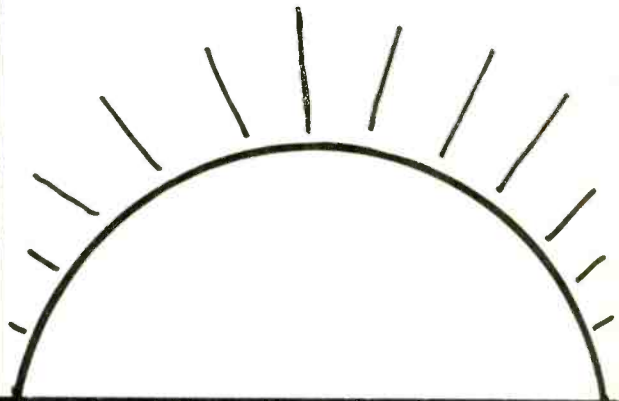**Suppliers of ex-rental
TVs & Satellite systems.
New & B stock available.
Please ring us for details.**



UNIT ONE, SUNSHINE MILLS, WORTLEY ROAD, LEEDS 12.

Telephone: 0532 638804 Fax: 0532 310275

**ELECTRONICS
WORLD**

+ WIRELESS WORLD

**SIX PAGES
OF ELECTRONIC
CIRCUIT DESIGN
EVERY MONTH**

Subscribe today and save £10

Simply phone our credit card
 hotline on 0789 200 255 for a
 special subscription price of £20
 for 12 issues*.

BRITAIN'S LARGEST INDEPENDENT

PRESTON

439 Oakshott Place,
Walton Summit Ind. Estate
Preston (M6 Junc. 29)
Tel: 0772-312101



BIRMINGHAM

208 BROMFORD LANE
ERDINGTON,
BIRMINGHAM B24 8DL
Tel: 021-327 3273
Fax: 021-322 2011

TV & VIDEO WHOLESALERS

CARDIFF

Unit J7,
Colchester Trading Estate
Colchester Avenue
Cardiff CF3 7AP
Tel: 0222-471485



THIS MONTH'S SPECIAL

UNIVERSAL ORIGINAL HANDSET FOR
TOSHIBA TV & VIDEO (Model remote,
text & fast text) **£8.00 + VAT**

(ALL PRICES SUBJECT TO VAT)

LONDON

The Royal London Estate,
Unit 2, 29-35 North Acton Rd
London NW10
Tel: 081-961 5005



**'B' GRADE
AVAILABLE
(BOXED)**



TELEVISIONS

A51F
59M5
68M5
78M5

VIDEOS

FV42L
FV41R
FV32L
FV31R



**CALL IN AT YOUR LOCAL BRANCH TODAY AND SEE OUR RANGE
OF EX-RENTAL AND B GRADE STOCK**

EXPORT ENQUIRIES WELCOME

West Midlands T.V. & Video Wholesale

Summer Sale Now On



This Month's Special

WORKING 3V35
VCR only
£55

Colour TVs working from £15
Teletext working from £39
Top Loader Videos..... from £35

WORKING 21" F-S-T
SANYO TVs only
£69

B-GRADE L CD REMOTE
LONG PLAY VCR only
£129

B-GRADE 20" OSD
TELETEXT TVs from
£139

Large Selection
Portable TVs from only
£39



1/2 mile of Junction 10 M6 — Easy Parking facilities.

UNIT 3, BENTLEY LANE INDUSTRIAL PARK
BENTLEY LANE, WALSALL WS2 8TL


Tel: 0922 724542 Fax: 0922 722208 Mobile: 0860 499495 24 HR

OPEN: Monday to Friday, 9-6pm
Saturday, 9-2pm. Sunday by appointment

Delivery service throughout the country

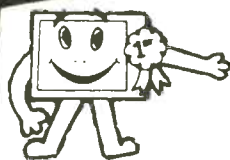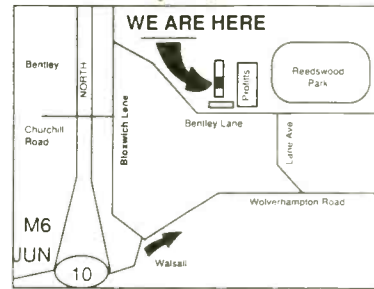

CentreVision

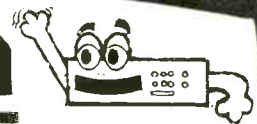

Suppliers of Surplus TVs & Videos to the Trade
CENTREVISION HOUSE · SLOPER ROAD · LECKWITH · CARDIFF · CF1 8AB

ALL SIZES, ALL MAKES
TELETEXT INCLUDED — NON FST £38


Above prices based on quantity purchases

Phone: 0222 344754

WE WON'T BE BEATEN ON TV AND VIDEO ...
CALL IN PERSON FOR THE BEST DEAL AROUND.



**THE LARGEST
WHOLESALE
IN WALES**

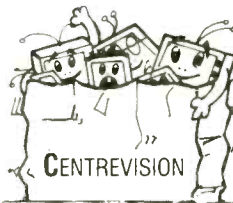

**SPECIAL
ONE-DAY
OFFERS**

**STOCK
ARRIVING
DAILY**

EXPORT ENQUIRIES WELCOME — ALL PRICES + VAT

TELEPRICE

LIMITED

STOP PRESS
FARNBOROUGH
moving end of JUNE
- phone for details
0252 540814

SWITCH ON!
TO QUALITY
EX-RENTAL TV
& VCR. PLEASE
RING FOR DETAILS

AINTREE

UNIT 2, RACECOURSE IND. EST.
ORMSKIRK ROAD, AINTREE
LIVERPOOL L9 5AL. TEL:
051 530 1285 IAN MAC

LEEDS

UNIT F2, COPLEY HILL
TRADING EST., WHITEHALL
RD, LEEDS LS12 1HS. TEL:
0532 422774 LES CORKE

AVONMOUTH

5 PORTVIEW ROAD
AVONMOUTH, BRISTOL
BS11 7LQ. TEL:
0272 235093 KARLA REALE

GLASGOW

9 COLQUHOUN AVENUE
HILLINGTON IND. EST.
GLASGOW G52 4BN. TEL:
041 883 2610 IAN DORAN

NOTTINGHAM

UNIT 8, ASCOT PARK
INDUSTRIAL ESTATE
SANDIACRE, NOTTINGHAM. TEL:
0602 491385 JOHN JEYS

SUNDERLAND

9A/B, 94 CARRMERE RD
LEECHMERE IND. EST.
SUNDERLAND SR2 9TE. TEL:
091 523 5554 BRIAN CADE

SOUTH LONDON

22 FRANTHORNE WAY,
OFF RANDESDOWN ROAD, BELLINGHAM,
LONDON SE6 3BS. TEL:
081-695 0877 JAMES MAYE

FARNBOROUGH

40 INVINCIBLE ROAD
FARNBOROUGH
HANTS GU14 7QU. TEL:
0252 540814 COLIN GORDON

ANGLIAN T.V. WHOLESALE

**EX-RENTAL TV's & VCRs
THORN AND GRANADA**

**NEW 'B' GRADE-MAJOR BRANDS
*STOCK CHANGING DAILY***

**Secondhand Guaranteed TV, Video,
spares now available**

**BEST POSSIBLE PRICES
RING FOR DETAILS**

***NOW IN LARGER PREMISES AT:*
20 RASH'S GREEN IND ESTATE
DEREHAM, NORFOLK
TELEPHONE (0362) 691611**

CREWE WHOLESALE TV LTD.

WE HAVE SLASHED OUR PRICES.

WORKING TV'S FROM £15.00.
WORKING TEXT TV'S FROM £45.00
TAKE 5 £45.00 — TEXT ONLY £200.00.

LARGE SELECTION OF WORKING
AND UNTESTED STOCK.

WORKING TOP LOADING VIDEOS
FROM £40.00.
WORKING FRONT LOADING VIDEOS
FROM £50.00

WORKING LONG PLAYING STEREO
VIDEOS ONLY £70.00

AT LEAST 1 DELIVERY, TO EACH
UNIT, PER WEEK.

CALL NOW FOR NEW PRICE LIST.

CREWE — OPEN 9.30 TO 5.30
MONDAY-FRIDAY

TEL: 0270 582924.

★ UNTESTED STOCK ONLY ★

BLACKBURN — OPEN 10.00 TO 4.00
WEDNESDAY-FRIDAY

TEL: 0254 264489

**CAMPION
WHOLESALE LTD.**

**QUALITY USED T.V.
& VIDEO
COMPLETE RANGE OF
T.V.'s AND VIDEOS
MOST MAKES AND
MODELS AVAILABLE**

**STOCK ARRIVING DAILY
T.V.'s from £3.00
Videos from £30.00
Prices Ex-VAT**

**Free Delivery Service
to most areas of the U.K.**

UNIT 80, BARRACKS ROAD,
SANDY LANE INDUSTRIAL ESTATE,
STOURPORT-ON-SEVERN,
WORCESTERSHIRE DY13 9QB

Just 10 Mins from
M5 Junct. 6 Worc's North

For your export
requirements contact us.

**0299-879642 or 879643
FAX: 0299 827984**

CENTRAL TV



EX-RENTAL

● SUPERB RANGE OF TV'S & VCR'S
● THORN & GRANADA

● DIRECT LOADS
AVAILABLE FROM SOURCE

EXPORT ENQUIRIES WELCOME

'B' GRADE

SWITCH ON TO TOP
QUALITY
BRANDS
OF

PHONE TODAY FOR BEST RESULTS

ALL SIZES OF SCREEN TV AVAILABLE,
BOTH IN FAST TEXT &
DIGITAL NICAM STEREO

VIDEOS: CURRENT MODEL

Single, Twin Speed, Nicam S-VHS

CAMCORDER

C FORMAT, FULL SIZE, 8mm

MICROWAVES ● PORTABLE ● HIFI

● SATELLITE ● VIDEOCRYPT ●

PORTABLE £90

FULL REMOTE, BOXED

CTV LONDON
Eley Estate, Nobel Road
Edmonton N18
TEL: 081-807 4090
FAX: 081-884 1314

**CENTRAL TV WHOLESALE
DISTRIBUTION LTD**
369 Stratford Road, Sparkhill
Birmingham B11
TEL: 021-772 1591
FAX: 021-766 6383



TVS FROM ONLY £15 **VCR FROM ONLY £25**

**JMG
ELECTRONICS
T.V.
AND
VIDEO
WHOLESALE**

UNIT 13A, GORTRUSH IND. ESTATE
DERRY ROAD, OMAGH,
CO. TYRONE.

**PHONE
(0662) 247911**

**N. Ireland
T.V. trade**

AERIALS

FOR TV & FM RADIO, PLUS
1000's OF MASTS,
BRACKETS, LASHING KITS,
CLAMPS, PLUGS, CABLES,
OUTLETS, DIPLEXERS ETC.

AMPLIFIERS

FOR DISTRIBUTION
SYSTEMS AND DOMESTIC,
MAST HEAD OR SET BACK.
WE HAVE ONE OF THE
LARGEST RANGES,
AVAILABLE FROM STOCK

MAIN DISTRIBUTORS

FOR ANTIFERRENCE,
LABGEAR, WOLSEY
FRINGE, TRIAX, TELEVES,
VOLEX-RAYDEX, KUBLER
+ MANY MORE

**COASTAL
AERIAL
SUPPLIES**

UNIT X2 Rudford Industrial Estate
Ford, Arundel

0903 723726

NO MINIMUM ORDER VALUE
NEXT DAY DELIVERY ACROSS UK
CARRIAGE FREE ON ORDERS £100+



**FAX: 0274
722229**

**BESCO LTD
EX-RENTAL TV'S
& VIDEOS**

**NEW 'B' GRADE
MAJOR BRANDS
TV - VIDEO - HI-FI**

PORTABLES ● FST's ● NICAM ● FASTEXT
SONY ● HITACHI ● PANASONIC ● ETC

Huge selections. Complete range.

All makes and models available.

★ New Stocks Every Day ★

VHS Video from £30
Television from £3

PICK YOUR OWN VHS VIDEOS
Lots of 10 £20.00 each (*mostly complete*)

Working Ex-Equipment Panels

IF	Converger	Decoder	Line Scan	Power	Frame
T20/22X	5	14	18	17	14
T26 X	5	16	20	17	X
Philips G11 14.50	5	12	20	20	11.50

All prices include Postage & Packing. But + VAT

★ IF THE PANEL YOU REQUIRE IS NOT LISTED PLEASE ASK ★

BRADFORD

Springmill St
Manchester Rd, BD5 7RL
Ring Tony (0274) 308186

MANCHESTER

Unit 3, Mersey Rd.
North Ind Est., Failsworth
Ring David (061) 683 4612

Visa/Access welcome
Prices are Plus VAT & Based on Quantity
OPEN 6 DAYS 9-5

**TOP CLASS PANASONIC
WORKING TV & VIDEO
+
GOOD CHEAP STOCK**

"OFF THE VAN"

Good Selection of Makes

Tom Poole or Brian Ricketts
061-273 2854/274 3409

REPO
DAISY WORKS,
345 STOCKPORT ROAD,
LONGSIGHT,
MANCHESTER

(A6 Between Stockport & Manchester almost opposite
police headquarters 3/4 mile from Apollo Theatre)

WESTERN
TRADE
SERVICES

**TV & VIDEO
WHOLESALE
FOR
DEVON & CORNWALL**


EST 14 YEARS

SUPPLIERS OF EX-RENTAL TV & VIDEO'S
THORN & NON THORN
REMOTE TEXT & VIDEO HAND UNITS
SUPPLIED WHERE NECESSARY
ALL PRICES SUBJECT TO VAT

**DELIVERIES THROUGHOUT DEVON
CORNWALL TWICE WEEKLY**

GIVE US A RING OR CALL IN
**2A BARTON HILL ROAD,
TORQUAY, DEVON**
TEL: 0803 312222 FAX: 326767

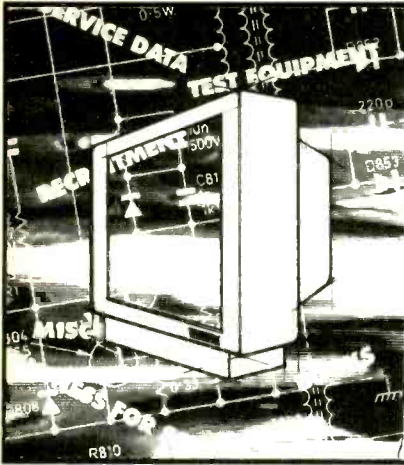CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED



TELEVISION CLASSIFIED

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting is £12.00 per single column centimetre (minimum 3 cm). Classified advertisements £1.20 per word (minimum £12), box number £4.00 extra. All prices plus 17½% VAT. All cheques, postal orders etc., to be made payable to Reed Business Publishing. Advertisements, together with remittance, should be sent to the Television Classified Room L327, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.



PHONE 081-652 8339 FAX 081-652 8931



SPARES & COMPONENTS

INTEGRATED CIRCUITS		
PRICES INCLUDE VAT, Add £1 18 POSTAGE		
TV & VIDEO I.C.s		
AN262	1.12	LA7033 3.29
AN304	2.96	LA7210 1.47
AN5015K	2.94	LA7505 2.06
AN5612	1.81	LA7910 1.23
AN5620X	3.11	LU11417A 4.23
AN6306	6.46	LU52511A 4.23
AN6320N	2.47	LVA508 1.65
AN6326N	2.88	LM1889N 3.29
AN6328	2.88	M51393AP 2.94
AN6346N	3.08	MC1408P8 1.18
AN6347	2.47	MN15823FVG 12.69
AN6350	5.02	OEC0001B 5.23
AN6360	2.14	OEC0005 5.23
AN6362	3.47	OEC2001 3.35
AN6881	2.70	SONY CX134A 4.99
BA618	1.35	TD62105P 1.18
BA6301	1.65	ULA1H035E2 1.82
BA7001	1.23	UPA53C 4.05
BA7004	1.65	UPC1382C 90
BA8500	11.69	UPC1397C 3.70
HA17458PS	82	14DN156 5.29
LA7031	2.06	14DN157 5.29
LA7032	2.42	14DN244C 5.70

HANDSETS		
VCR4600/4600MkII		£11.75
VCR4700		£17.63
VCR5200		£11.75
VCR6100 Barcode		£29.38
TS90/99 Tower System		£11.75
VCR9000 (Old Type) Handset		£11.75
L.O.P.T.		
CTV1000	FB182K	£11.75
CTV1400	FB165KA	£11.75
CTV2000	FB171	£9.40
CTV2000	FB171K	£9.40
TVR2	1810951	£13.51
TVR3	181297	£13.51
PC12-HRCD/D	MSH1FCT31	£14.10

CONVERTERS		
4700 RF CONVERTER		£5.88
5200 RF CONVERTER		£7.05

SATELLITE EQUIPMENT
DISHES, FEEDS, LNB'S ETC.
AVAILABLE. PHONE FOR LIST.

Harrison Electronics

CENTURY WAY, MARCH, CAMBS PE15 8QW.
FAX: (0354) 51416. TEL: (0354) 51289

AMSTRAD		
PRICES INCLUDE VAT, POST AND PACKING EXTRA.		
P.C.B's		
4600 Video and Audio PCB		£17.63
4600 Systems Control/Servo PCB, Display and Control PCBs		£29.38
4600 MkII Video and Audio/Timer/Control PCB Assy.		£40.82
4700 Video and Audio/Timer/Control PCB Assy.		£40.82
VCR100 Video and Audio/Timer/Control PCB Assy.		£40.82
5200 Timer and Channel Display PCB Assy.		£17.63
5200 Audio Tuner PCB		£15.28
5200 Video PCB		£14.10
5200 Syscon. Servo Power PCB		£23.50
4600 Mk II/4700 Power Supply		£4.70
CTV1400 Main PCB		£29.38
CTV2200 PCB No:3 (Part 270087)		£3.53
CTV2200 PCB No:4 (Part 270088)		£4.70
TVR1 Control Panel/Presel PCB		£7.05
TVR2 Main TV PCB		£37.60
TVR3 Main TV PCB		£43.48

MECHANISMS		
4600 Video Cassette complete mechanism (no drum or video heads)		£29.38
4600 Video Cassette complete mechanism (with drum no video heads)		£35.25
9000 Cassette Housing Assy.		£15.28

MOTORS		
4600/4700 Capstan Motor		£11.75
7000 Loading Motor MCB2B01		£3.53
9000 Loading Motor MCB9B02		£3.53

TUNERS		
5200 Varicap Tuner Type 1810829		£7.05
7000 Tuner ENV87358C2		£7.05
CTV1400 Tuner ENV87509F2		£5.88
CTV2200 Tuner UE2-B31F		£5.88

PARTS OFF PCB'S AND MECHANISM.
PHONE FOR PRICING

ALL ITEMS ARE BRAND NEW AND GUARANTEED
**** SAME DAY DESPATCH ****
Write or Phone for FULL catalogue.



ADMIN TELEVISION

PHILIPS KT3/K30, ITT, MK4, GEC, TX 9/10, TOSHIBA, HITACHI, PANASONIC BASICS £15 + VAT (IN TENS)

MK3, GEC 21/10, DECCA 80/100 BASICS £10 + VAT (IN TENS)

GII BASIC £12 TEXT £20 + VAT

ALL REMOTES £25 + VAT

ALL TEXT £35 + VAT

VIDEOS £20 AND £25 + VAT

ALL REMOTES WORKING £35
ALL TEXT WORKING £45
ALL BASICS WORKING £25

PHONE: 051-548 4414
UNIT 'J', ADMIN BUILDINGS,
KIRKBY, LIVERPOOL L33 7JX

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY
1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps D.C. Fully stabilised. Twin panel meters for instant voltage and current reading. Overload protection fully variable. Operates from 240V A.C. Compact Unit. **£45 inc. VAT** Post & Ins. £4 size 9x5 1/2x3ins.
NEW MODEL. Up to 38 volts DC at 6 amp. 10 amps peak. Fully variable. Two panel meters. Size 14 1/2" x 11" x 4 1/2". **£96 inc. VAT.** Carr £6

RADIO COMPONENT SPECIALISTS
337 WHITEHOUSE ROAD, CROYDON SURREY, U.K. Tel: 081 684 1665
List. Large SAE. Delivery 7 days. Callers Welcome Closed Wed.

ALLPARTS DISTRIBUTORS
TV & VIDEO SPARES FOR THE TRADE AND PUBLIC
BELT KITS, TRANSISTORS, ICs, REMOTES, FERGUSON, PANASONIC, SHARP, GRUNDIG, SONY, KONIG, PHILEX, AMSTRAD
ALLPARTS DISTRIBUTORS
101 ROCKY LANE, TUEBROOK, LIVERPOOL 6 4BB
051-260 4825

SURPLUS/REDUNDANT ELECTRONIC COMPONENTS WANTED
I/Cs - Tuners - Transistors - Valves - Diodes etc. any quantity considered - immediate payment.
ADM Electronic Supplies
Tel. 0827 873311. Fax 0827 874835

WIZARD DISTRIBUTORS MANCHESTER

TV, VIDEO & SATELLITE SPARES
LOEWE, SCHNEIDER, FERGUSON, HITACHI

and many other always in stock—
Video Heads for over 500 models
Service Manuals for over 200 models
Handsets for over 200 models
Spares for over 20 manufacturers
Plus huge range of IC's, Semiconductors and Service Aids, etc. etc.

WIZARD OFFER A GREAT DEAL
Counter open Monday-Friday 9am-4.45pm
Mail Order Access-Visa
TRADE ONLY
EMPRESS STREET WORKS,
EMPRESS STREET,
MANCHESTER M16 9EN.
Tel: 061-872 5438; 061-848 0060.

REPAIRS

LOEWE OPTA TV REPAIRS
FAST EFFICIENT SERVICE
Factory Trained Engineers
Competitive Rates
MARWETECH,
Unit A7B, Aladdin Workspace,
426 Longdrive, Greenford,
Middlesex UB6 8UH.
Tel: 081-575 0434 Fax: 081-575 0468

FOR SALE

MICRO-LAB
PORTABLE INSTRUMENTS
Don't waste time hunting down shorts. Our **SHORT LOCATOR** will lead you right to it in seconds! Easy to use with meter display and tone to guide you. Send just £99.95 + £3 p&p + VAT: Total £120.96 each, quoting P28, to
COLEBOURN ELECTRONICS
Dept TV, 20 Folly Lane, Telephone
St Albans, AL3 5JT 0727 44785

THRIFTY SPARES (WALES)

Centrevision House, Sloper Road, Leckwith, Cardiff CF1 8AB
INCREASE YOUR PROFITS WITH USED SPARES

MANY MAKES OF USED VIDEO AND TV PANELS - GUARANTEED WORKING HUNDREDS NOT LISTED - PHONE OUR HOTLINE **0222 344218**

VIDEO THORN, HITACHI, TOSHIBA, ITT, SHARP, AMSTRAD, PANASONIC ETC.		
USED WORKING VIDEO SPARES	From	WORKING DORIC MK3, MK4, MK4A BOARDS
MIXED BOOSTER	£12.80	MK3A LINE SCAN (STATE TUBE)
SERVO PANEL	£15.50	MK3A POWER PANEL
LOADING MOTOR ASS	£10.50	MK3A IF VIDEO ETC
BOTTOM BOARD	£20.50	MK4 LINE SCAN
MODULATOR	£15.50	MK4 POWER PANEL 90 OR 110
MECHAON	£15.50	MK4 IF PANEL
DRUM ASS	£12.80	MK4 VIDEO
CAPSTAN MOTOR	£15.50	MK4 MANUAL TUNER HEAD ASS
POWER PANEL	£15.50	MK4 REMOTE BOARD
TUNING BOARD	£18.00	MK4 TEXT BOARDS
IR100 PROGRAMMABLE REMOTE CONTROL	£20.50	MK4 FRONT ASSEMBLY
RC5301 KT330	£10.50	MK4 TRIPLERS
RC306 ITT	£10.50	MK4 CRT TUBE CALLERS ONLY
MANY MORE AVAILABLE - ALL HANDSETS + VAT ALSO SPECIAL RATES FOR P&P		MK4 TEXT HANDSET
ALL ABOVE PRICES VAT INC. MANY MAKES OF TV USED - SPARES ALSO IN STOCK		MK4A TEXT HANDSET
OPENING HOURS 9am-1pm - 2pm-5.30pm		
POSTAGE & PACKING FROM £2.50. ORDERS OVER £50 P&P FREE		
DON'T DELAY PHONE 0222 344218 TODAY		

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

TRANSFORMERS

TV LINE OUTPUT TRANSFORMERS

PHONE 081-948 3702 FAX: 081-332 0583

ALBA . AMSTRAD . BUSH . DECCA . DORIC . BLAUPUNKT .
FERGUSON . FIDELITY . GEC . GRUNDIG . GRANADA .
HITACHI . HINARI . INDESIT . ITT . KIMARA . NIKKAI .
MATSUI . MURPHY . OSAKI . NORDMENDE . LOEWE-OPTA .
REDIFFUSION PYE . PHILIPS . SANYO . SAISHO . SHARP .
SONY . SOLOVOX . SUSUMU . TANDBURG . TELEFUNKEN .
THORN . TRIUMPH . HUANYU . GOLDSTAR . BINATONE .

**FULL RANGE OF KONIG: VIDEO HEADS, BELT KITS,
IDLERS, PINCH ROLLERS, TENSION BANDS.
LARGE RANGE OF REMOTE CONTROLS IN STOCK**

TIDMAN MAIL ORDER LTD . 236 SANDYCOMBE ROAD .
RICHMOND . SURREY . TW9 2EQ. Mon-Fri 9 am to 12.30 pm &
1.30-4.30 pm
Approx. 1 mile from Kew Bridge. Sat 10 am to 12 noon

SERVICE MANUALS

For most U.K. European, Far East & USA types of CTV - MTV -
VCR - CAM - SAT - M/WAVE - AUDIO including "Unusuals" -
and all at reasonable prices.

VCR circuits also available separately for most models

Some examples from thousands of VCR manuals available.

These are all complete at £10 each

PANASONIC NV-FS100, L20, NV-MC10, MC20, MC30, MS50,
ORION D500, D1000/1100, D1200, D1500, D2000,
FERGUSON FV11R, FV12L, FV13H, FV14T, FV20B, FV30B.

+ MANY OTHER BARGAINS

Write or telephone with your requirements.

All U.K. orders subject to £1 P&P. No VAT

D-TEC

PO BOX 1171, FERNDOWN, DORSET BH22 9YG.

Telephone: 0202 870656

SERVICE MANUALS

Available for most equipment. TV.
Video, Audio, Test, Amateur Radio,
Military Surplus, Kitchen, Vintage Valve,
Computers etc.

Over 100,000 manuals available for
equipment from 1920's to the present.
Originals or photostats supplied as
available.

FREE Repair and Data Guide
Catalogue with all orders or send SAE
for your copy today.



MAURITRON (TV)



8 Cherry Tree Road, Chinnor,
Oxfordshire, OX9 4QY.

Tel: (0844) 51694 Fax: (0844) 52554

Technical Information Services



76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML9 1HE

Tel. (0698) 884585 Mon-Fri 8.30am - 5.00pm or (0698) 883334 Outwith business hours

FAX facility available all day on both lines



Write now with an SAE for your FREE QUOTE, FREE CATALOGUE & FREE NEWSLETTERS

ALL TRADE ADDRESSES GIVEN !FREE! JUST PHONE TO FIND THE NUMBER/ADDRESS YOU NEED

All orders under £25.00 please add £1.50 p&p.

All orders over £25.00 post free.

Some selected titles (Taken from over 150)

Practical TV Repairs 2nd Ed.	£16.95	S. Beeching's VCR Servicing	£30.00	Refrigeration Pocket Book	£14.95
CTV Servicing by G.King	£16.95	Servicing Mono TVs	£17.95	Spectrum Repair Guide	£5.00
The PAL System	£8.50	VHS Common Faults	£3.50	Spectrum Complete (+, 128k, etc)	£35.00
TV & Video Technology	£14.95	Microwave Servicing	£9.95	European Scrambling Sys's *New Sections	£29.00
TV & Video Engineers P/Book	£14.95	Hi-Fi Servicing Guide	£9.95	Data Reference Manual	£5.95
Practical Radio Service & Repair	£12.95	Servicing Audio & Hi-Fi	£25.00	Set of 6 Thorn's own Guides	£9.50

Order by phone
with Access/Visa

NOW, not only do we have EVERY service sheet ever produced, and

Fast
Delivery



THE WORLD'S LARGEST COLLECTION OF SERVICE MANUALS

but, we will supply circuits for any VCR we have for only £8.50 inc. p&p

& WE ARE SOLE SUPPLIERS OF VARIOUS FAULT-FINDING GUIDES, REPAIR MANUALS & TECHNICAL MANUALS



INTEGRATED SYSTEMS from TIS

10 Giant binders of CTV Circuits, Schematics, PCB's, Waveforms, etc.	£265.00
7 Giant binders of VCR Circuits, Schematics, PCB's, Waveforms, etc. (Vol. 7 New)	£190.00
All 7 VCR binders PLUS 35 Fault-Finding Guides for ALL models covered (5 New F.F. Guides)	£230.00
The 10 CTV Binders PLUS over 20 CTV Repair Guides & lots, lots more	£399.00
All the CTV & Repair Guides PLUS VCR binders PLUS fault-finding, etc.	£599.00
TVAR complete, Two books & two binders of Giant diagrams (up to A2)	£89.45

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

INFOTECH

76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML9 1HE
Tel. (0698) 884585 Mon-Fri 8.30am-5.00pm
Tel. (0698) 883334 Outwith business hours
FAX available all day, Mon-Sat, on either line

Send a large SAE for your FREE catalogue of our other publications
Please add £1.50 on all orders under £25.00. Post FREE on all orders over 25.00

Now the sole MO distributors for the complete PCP range of inexpensive books, GUARANTEED - More than Value for Money

ELECTRONIC TEST EQUIPMENT HANDBOOK

by Steve Money £8.95

Inc. analog/digital meters, bridges, scopes, sig'l gen's, counters, timers, freq meas.

ELECTRONIC POWER SUPPLY HANDBOOK

by Ian R Sinclair £7.95

Very modern, covers switch mode, DC-DC and all invert/convert

INTRODUCING DIGITAL AUDIO, 2nd edition

by Ian R Sinclair £6.95

Fabulous cover, with DCC, Mini-Disc, CD, DAT, Bitstream, oversampling, etc.

PRACTICAL DIGITAL ELECTRONICS HANDBOOK

by Mike Tooley £6.95

Over 200pp of ref data and pract instruction - Brilliant on chips, logic gates, etc.

DIGITAL ELECTRONIC PROJECTS FOR BEGINNERS

by O Bishop £5.95

12 battery, 1 power, plus variations; from instrumentation to home security

DIGITAL LOGIC GATES AND FLIP-FLOPS

by Ian R Sinclair £8.95

What they do, How they work, Simplified Troubleshooting, Full theory and practice

ELECTRONIC PROJECTS FOR HOME SECURITY

by O Bishop £6.95

Full instructions - 25 projects; simple alarm to various multi-channel systems

ELECTRONICS BUILD AND LEARN, 2nd edition

by R A Penfold £5.95

Essential practical construction for oscillators, multivibrators, bistables, logic circuits

PC MUSIC HANDBOOK

by Heywood & Evan £8.95

IBM & Compatibles: From basics through sequencing, sampling and notation

ADVANCED MIDI - USER'S GUIDE

by R A Penfold £9.95

Explains messages, timecodes, non-MIDI sync, Signal routing, Troubleshooting

J.W. HARDY

CHECK OUT OUR NEW PRICE LIST

(SEE MAY ADVERTISEMENT FOR MAIN ACCESSORIES LIST)

Networking Components		Global Sat I.F.	
75 ohm		VLC=1317 Volt Line Control DTI= Diplexed Terrestrial Input Splitters to 2GHz	
THE DOMESTIC RANGE OF SPLITTERS		2-Way 004-2GHz 5.45	
Standard coax type		2-Way 9-2GHz 6.76	
2-Way Splitter "Y" each 0.65		4-Way 9-2GHz Active 15.11	
2-Way Splitter "Y" per 50 0.48		8-Way 9-2GHz Active 27.32	
2-Way Splitter "Y" per 100 0.42		8-Way 9-2GHz 21.94	
5-Way Splitter 1in 5out 1.82		Taps to 2GHz	
6-Way Splitter 1in 6out 2.72		1-Way Tap: 004-2GHz 12 or 15dB 5.45	
		Switches to 2GHz	
		2m1 out DC +- Pulse/DC/SC 20.45	
		2m1 out DC +- Pulse 20.45	
		2m1 out VIL +- 2.5V/17 5mA 14.90	
		2m1 out VBI Variable 14.90	
		2m1 out with VLC 14.90	
		2m1 out 15-18V Line Control 14.90	
		Matrix (Magic) Switches to 2GHz 19.95	
		2x2 with VLC Active 29.95	
		2x4 with VLC Active 29.95	
		2x4 with VLC Passive POA	
		2x4 with VLC Active and DTI Passive POA	
		2x4 with VLC Active and DTI Active POA	
		2x4 + 2 VLC 004-2GHz TAP 14.26dB 175.00	
		3x4 the Original Magic Sw. 5 Types	
		Increases to 2GHz for	
		Polarity/Barb Switching	
		INT 1F Ra 1317V to LNB 1 19.32	
		INT 2F Ra 1 to LNB 1317V 24.15	
		Frequency Converters	
		K5 (Telecom) Frequency Converter 69.00	
		TE 1F Pulse Controlled 69.00	
		TE 2F V1 Controlled 69.00	
		Power Supply	
		18 Volt Power Supply 19.04	
		DC Block & Power inserter 8.21	
		DC Block & Power Inserter Dual Line Amplifiers POA	
		Flat 9-2GHz 10.35	
		Slop 004-2GHz 15.87	
		Slop 9-2GHz 15.87	
		2dB Launch Amp. 9-2GHz DTI Passive POA	
		2dB Launch Amp. 9-2GHz DTI Passive POA	
		Duplexers - For Satellite & Terrestrial POA	
		TV Sat Iso. 15dB Splitter POA	
		TV Sat Iso. 35dB Splitter/Combiner POA	
		At above with DC Pass on TV POA	
		Coaxial Wall Sockets: 004-2GHz POA	
		FM TV SAT. Diplexed Wall Socket POA	
		4-Way Tap MTU/20 25.30. 35dB 8.70	
		Single Socket Iso. to BS5613/6 V.L. Pass POA	
		4-Way Tap MTU/4/16db Terminated 9.00	
		TRADE ONLY	
		Minimum trade order £60.00	
		All prices quoted are plus	
		carriage plus VAT	
		J. W. HARDY	
		231 Station Rd, Stechford,	
		Birmingham B33 8BB.	

MAURITRON TECHNICAL PUBLICATIONS

The following is a selection from our vast range of Technical Manuals for the TV and Video Servicing Trade. Order some today.

Order Code	Title	Price
MTP-5	Video Recorder Faults - Repair Guide	£1.95
MTP-58	VHS Video Recorder Principles	£1.95
MTP-7	Transistor Radio Repair Guide	£1.00
MTP-34	TTL Integrated Circuits Databook	£4.95
MTP-10	CMOS Integrated Circuits Databook	£4.50
VHCK	Video Head Cleaning Kit	£3.50
MTP-9	Power Supplies & Voltage Regulators	£2.95
MTP-24	Transistor Equivalents and Testing Manual	£4.50
MTP-8	Record Player Speed Disc	£0.95
MTP-19	Telephone STD Code Location Guide	£3.95

SPECIAL OFFER: Order the full set of the above for only £25.00, a saving of £5.20 over the individual price of £30.20. Use Order code MTP-189.

Phone your order today using Access or Visa for immediate despatch.

All orders plus £2.35 post and packing.

Hundreds of other Repair and Data Guides available from our Catalogue available FREE upon receipt of a stamped envelope and sent with all orders.

MAURITRON PUBLICATIONS (TV3)

8 Cherry Tree Road,
Chinnor, Oxfordshire
OX9 4QY



Tel: (0844) 51694 Fax: (0844) 52554

Service Manuals available: See our other advert for details

E.C.S. INDEXES!

THOUSANDS SOLD WORLDWIDE

Edition 8 of the complete indexes now published containing approx 7,500 Faults listed in 12 Years of Television magazine.

Indexes are alphabetically listed by Make, Model, Fault, Ref and are now available for just:

£8.00 For Television & Satellite Faults

£8.00 For Video, Camcorder & CD Faults

Or **£15.00** for both sets complete with chassis & similar model guides. **Please add £1.50 (UK), £3.00 (Overseas) to total order to cover post & packing.**

A LOW COST UPDATE SERVICE IS ALSO AVAILABLE. FULL DETAILS DESPATCHED WITH ORDER.

To secure your copy/s please make Cheques/Postal Orders payable to:

E.C.S.

31 Prenton Road West,
Prenton, Birkenhead,
Merseyside L42 9PY

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

TV & VIDEO

TRADE REFERENCE MANUALS

UNIQUE REFERENCE DATA FOR THE TV AND VIDEO SERVICING TRADE.

● TELEVISION CHASSIS GUIDE

Listing thousands of Models (Colour & Mono) and their Chassis Designations. Enables you to identify any chassis for any TV from the model number. Order Code MTP-18.

● VIDEO RECORDER EQUIVALENTS

Lists all known models and their alternatives. Fully cross referenced for fast and easy use. Order Code MTP-143.

● TRADE ADDRESSES

Hundreds listed including TV, Video, Test and Computers. Includes all the obscure and hard to find suppliers of the unusual brand names. Order Code MTP-23.

THESE 3 BOOKS CONTAIN THE MOST COMPREHENSIVE REFERENCE DATA AVAILABLE ANYWHERE FOR THE TV AND VIDEO TRADE.

ONLY £5.00 EACH BOOK
PLUS £2.35 POST/PACKING PER ORDER.

Phone your order with Access or Visa for immediate despatch.

Hundreds of other Repair and Data Guides available from our Catalogue available FREE upon receipt of a stamped envelope.

MAURITRON TECHNICAL SERVICES

8 CHERRY TREE ROAD
CHINNOR
OXFORDSHIRE
OX9 4QY



Tel:- (0844) 51694. Fax:- (0844) 52554

Service manuals available - See our other advert elsewhere in the magazine.

GERMAN SERVICE SHEET SPECIALISTS

Our connections are world-wide. We furnish any kind of German, European and Japanese service sheet or manual. Thousands of different sheets and manuals in stock. For any enquiries:

DÖNBERG ELECTRONICS
Schoolmasters House, Rannafast,
Co. Donegal, Republic of Ireland.
Phone: 075 48275

WANTED

Regular Supply of Ex-Rental
Colour TVs and Videos

Cash on Collection - Quick Service

Tel. 0742 312832

TEST EQUIPMENT

P & E SERVICES

SUPPLIERS OF ALL MUTER
REPAIR AND TEST EQUIPMENT.

BMR 95 TUBE REGENERATOR
£446 + VAT

(INC SIX ADAPTORS)
BMR 700 TUBE REGENERATOR
£367 + VAT

(INC SIX ADAPTORS)
AT2 AUDIO SERVICING UNIT
£447 + VAT


ASK FOR FREE BROCHURE

34 GLAN-Y-MOR ROAD, PENRHYN BAY,
LLANDUDNO, GWYNEDD LL30 3PF.

TEL: 0492 549246 FAX: 0492 547880

MUTER · AT2 · BMR 95 · BMR 700

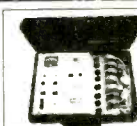AT 2, Audi-Multi-Tester, 16 test-circuits for loudspeakers, tuners, amplifiers, headphones, tape recorders, mikes, boosters.



BMR
95
BMR
700



Regenerating Computers & Measurers for CRT's with cathode protection, gas clean-up aid, short repair; exhausted CRT's becomes bright and sharp again even if all other machines do not succeed.

United Kingdom: P & E Services, Llandudno, Tel. (0492) 549246, Fax 547880.

Ireland: Dönberg Electronics, Rannafast, Co. Donegal, Tel./Fax (075) 48275.

New Zealand: TDON Ltd., Onehunga, Auckland, Tel. 6 68-907, Fax 668-499.

Germany: Ulrich Müter, Oer-Erkenschwick, Fax (0 23 68) 5 70 17.

car radios, CD-players; measurement of millivolt, drift, watt, performance; with generator, radio, signal tracer/injector, 13 volt supply etc.

TUBES

TV TUBE REBUILDER

What ever make or type. Give us a call. Polish service available.

M. B. ELECTRONICS
Unit 6, Guild Hall Ind. Estate,
Kirksandall Ind. Estate,
Doncaster DN3 1QR.
Tel. 0302 891208

REBUILT CRTs

VDU - MONITOR - TV

Image Burn-In Removed From Screen Phosphors

B.S.I. Certification

N.G.T. ELECTRONICS LTD.
120, Selhurst Road, London SE25 6LL

PHONE: 081-771 3535

Britain's Oldest Established Tube Rebuilder

BARCLAYCARD VISA INFOTECH Access

76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML9 1HE

Tel. (0698) 884585 Mon-Fri 8.30am-5.00pm

Tel. (0698) 883334 Outwith business hours

FAX available all day, Mon-Sat, on either line

Send a large SAE for your FREE catalogue of our other publications

HOW WOULD YOU LIKE TO GET ANY
SERVICE MANUAL YOU WANTED



FOR ONLY £7.50?

WELL, NOW YOU CAN!

We are running a very special offer of any 20 manuals for only £150. No catches! Order as you need them (no time limit), or as one lot of all those expensive manuals you couldn't previously afford. No hidden expenses like post & packing (that's included in the price).

And if that isn't enough!

We are giving away our Data Reference Manual FREE with every subscription to this 20 manuals for £150 offer!

PRACTICAL GUIDE TO BUYING, SELLING,
REPAIRING & SERVICING USED VCRs

Everything from choosing good ex-rentals to containing more stock faults for common ex-rentals than elsewhere at many times the cost.

Brilliant practical repair and service system.



PRACTICAL GUIDE TO
BUYING, SELLING,
REPAIRING &
SERVICING USED TVs



More stock faults and servicing advice on TVs. Again containing more data than books at twice the price.

Only £9.95 each or £16.95 for both

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

MICROWAVES

HOW THEY WORK! HOW TO TEST! HOW TO REPLACE!

Designed specifically for Domestic Appliance Engineers who want to enter the fast growing microwave industry. Packed full of useful information, presented in a simple yet informative style with comprehensive diagrams and illustrations. Fault finding procedures are included at the end of each section. The book contains easy to follow electronic control systems.

£14.95

+ £1.25 p&p

ORDER YOUR COPY TODAY!



We also supply microwave oven components

SWIFTPARK LIMITED

113 LONDON ROAD, HORNDEN, WATERLOOVILLE, HANTS. PO8 0BJ

TRADE ONLY

MICROWAVE OVEN PARTS

MAGNETRONS · DIODES · TRANSFORMERS
LAMPS · FUSES · MICROSWITCHES

PHONE NOW FOR PRICE LIST

A.W.I. MICROWAVE OVEN COMPONENTS

Samuel Whites Estate, Medina Road,
Coves, Isle of Wight PO31 7LP

Telephone: 0983 296121

Fax: 0983 296122

SERVICE DATA

User Friendly

SOFTWARE

FOR IBM COMPATIBLE PC'S RUNNING ON MSDOS
FOR THE BUSY TV/VCR SHOP/SERVICE DEPT
RECEIPT/INVOICE PROGRAM £89 + VAT + P&P

**OUR TV/VCR RENTAL PROGRAMME
IS NOW AVAILABLE**

Phone or write for details:

TBR Software 369 Chepstow Road
Newport, Gwent. NP9 8HJ
Tel. 0633 282556

SATELLITE

SATELLITE TV RECEPTION



DRAKE Receiver/Positioners from £299
Wideband Magnetic Polarizers from £29
60cm to 3m Antennas, polar mounts
11/12/14GHz LNBs - leads, accessories
SAE for Leaflets

KESH ELECTRICS LTD
Main Street, Kesh, Co Fermanagh BT93 1TF
Tel. 03656 31449 Fax. 39250 Tlx 747412

TRAINING

Looking for a home study course, in the fundamentals of electronics? Whether you are a beginner, or an old hand requiring a refresher, the

DIRECT PERSONAL LEARNING

course, could be right for you. Contact: K. Sparrow etc... 11 Claydon Green Whitchurch BRISTOL Avon BS14 0NG
Telephone: (0275) 835669

MISCELLANEOUS

CAR RADIO CASSETTES

Do you turn away work on car radio cassettes because they have security codes.

Most radio cassettes can be decoded just by replacing the eeprom (memory IC) with that of a known code, or sending the original for re-coding.

All popular makes including Philips, Ford, Pioneer, Clarion, Grundig, Blaupunkt, Fisher, JVC, Alpine, Volvo, etc.

Send now for introductory offer, one of each of most popular eeproms + comprehensive eeprom/radio decoding list. Offer includes Philips X2402P: Ford MN010: Blaupunkt Boston CC20 9346: **£17.63**

Original eeprom re-coding service **£10.00**

Inc. of VAT and P&P

Radio's sent for decoding from **£20.00**

Inc. of VAT and p&p

RADIO DECODING EQUIPMENT

We will beat any genuine written quotation for supplying a computer or software to decode radio cassettes, ring us first.

For technical or general information phone 0543 572 523 or 0831 806 574.

C.D.H. ELECTRONICS
3 Common Walk,
Huntington, Cannock, Staffs
WS12 4NB

C.D.H. ELECTRONICS

WHY BUY

SECONDHAND GOODS

Double your profits with brand new goods.


Please state your requirements. Bulk buyer only

Write to:

M.E., PO Box 2739

West Bromwich,

West Midlands B70 6EU

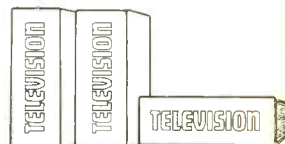

BINDERS

Binders that hold twelve issues of *Television* are available for £5 from

Television Binders,
78 Whalley Road,
Wilpshire, Blackburn
BB1 9LF.

Make cheques out to "Television Binders".

SERVICING · VIDEO · SATELLITE · DEVELOPMENTS

WORKING TVs

FROM £12

NON-WORKING TVs

FROM £5

VIDEOS NON-WORKING

FROM £15

VIDEOS WORKING

FROM £40

**ALL WORKING STOCK
SOAK TESTED**

DIRECT LOADS AVAILABLE

**TEL 0302 323834
GENERAL FACTORS**

UNIT 28, CARR GRANGE WORKS,
HYDE PARK, DONCASTER, SOUTH YORKSHIRE

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

LINEAGE

WANTED: KT66, KT88, PX4, PX25, transistors etc. If possible send a written list. Prompt reply and payment. Billington Export, Unit F2, Oakdene Industrial Estate, near Horsham, West Sussex RH13 8AZ. Callers strictly by appointment only. Phone: 0403 865105, Fax: 0403 856106, Telex: 923492 TRAG.

OCHRE MILL Technical Services. Grundig TV spares for most models to 1985, fast, friendly, helpful, sensible prices. Gr Lype Farm, Charlton, Nr. Malmesbury, Wilts SN16 9DR. Tel. 0666 823228.

WANTED PETRO-SCOTT 1416T or 1716T television (1955). Preferably complete but anything considered. Will collect. Mr Catt 081-686 2389 evenings.

SKY VIDEOCRYPT decoder service sheets with colour decoding tracks £15. Amstrad satellite tuneable audio £18. E.M.O., Ramsbottom, Lancashire BL0 9AG. 0706-823036.

STUDY ELECTRONICS on the BBC Micro. An interactive approach to learning. Three program titles now available. 'Introduction to Electronics Principles' Electronics Mathematics and 'Digital Techniques' Programs include theory, examples, self test questions, formulae, charts and circuit diagrams, user inputs and calculated outputs £29.95 each + £2.00 pp. Cheque or postal order to E.P.T. Educational Software, Pump House, Lockram Lane, Witham, Essex CM8 2BJ. Please state BBC B/Master Series and disc size.

C.R.T. FOR oscilloscopes, monitors, etc. Regret no domestic TV types. Possibly biggest stock of scope types in England! Big stocks of DG7-5/6/32, M31-184W etc. Billington Export, Unit F2, Oakdene Industrial Estate, near Horsham, West Sussex RH13 8AZ. Callers strictly by appointment only. Phone: 0403 865105, Fax: 0403 856106, Telex: 923492 TRAG.

METERS RECONDITIONED. £1.00 slot meters for TV rental £4.95. 50p slot £2.95. AUDIOTECH Tel: 07903 245.

PRIVATE RETAILER has excellent part exchange colour televisions and videos to clear. Tel: 0494 814317.

WANTED: OLD IMI Polar II U.H.F. tuners in good working order. Telephone 081-646 0002.

VALVES, HUGE STOCKS, credit cards accepted. Full 45 page valve catalogue now available. £2.00 post paid. VVC, 20a Cosham Street, Mangotsfield, Bristol BS17 3EN. Telephone: 0272 565472 (24 hours). Fax: 0272 575442 (24 hours).

TELEVISION AND radio technical books and magazines. 1936 to 1976. S.A.E. for lists. 80 Johnston Road, Oakdale, Poole, Dorset BH15 3HT.

COLOUR BAR GENERATOR cost £150, as new, hardly used. £99 ono. U-View, Doncaster O302 855017.

AVO MULTIMETER Model 8, £45.00. 500 volt megers £30.00. Prices plus VAT and p&p. Send SAE for lists of Surplus Instruments & Scopes etc. A.C. Electronics, 17 Apleton Grove, Leeds LS9 9EN. Tel: 0532 496048.

TELEVISION CLASSIFIED LINEAGE

advertisements can be submitted on this coupon with a cheque made payable to Reed Business Publishing, Television Classified Room L327, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. The charge per word is £1.20 plus 17½% (minimum £12.00 + VAT.)

TV7/92

For Issue Dated or next available. Total insertions Total of Cheque £
 Name Address
 Post Code Tel Num Signature



Debit my Access/
 Visa Card (delete)



Expiry Date

VAT Reg. No. 238 8937 10

ADVERT INDEX

Aerial Techniques	653
Anglian T.V. Wholesale	682
Audio Electronics	631
AZ Electric	666-667
Besco Ltd	684
BK Electronics	624
Bull Electrical	669
Campion	683
Central TV Wholesale Distribution Ltd	683
Centrevision	680
Coastal	683
Crewe Wholesale	683
C.T.V.	677
East Cornwall Components	628
East London Components	627
Economic Devices	654-655
EEC Satellite Services	625
Electronic Computer Workshop	627
Electronic Sound Systems	671
Electronics World	678
Euras International Ltd	631
Express TV Supplies	671
GGL Components	626
Gogglebox	677
Grandata Ltd	618-622
Hockley Discount Televisions	677
HRS Electronics plc	665
Hussain Central TV Ltd	679
ICS-Intertext Group Ltd	666
JJ Components	659
JMG	683
KSA Wholesale Components	674-675
Manor Supplies	635
Marapet	668
Network Satellite Systems	671
Omega	670
Pays-UTV	691
PV Tubes	627
Repo TV	684
Satellite Solutions (UK) Ltd	623
Senz Components	692, IBC, OBC
Stewart of Reading	666
Supervision	678
Swift Television Publications	676
T Powell	668
Teleprice Ltd	681
Vina Sonic Electronics	672
Vista Electronics	668
W. Tree Trade Warehouse	678
Well-View	631
Western Trade Services	684
West Midlands TV & Video Wholesale	680
Willow Vale Electronics	IFC
Windows User	673

PAYS-UT.V.

**SUPPLIERS OF WORKING
 NEW + USED
 TV'S, VIDEOS,
 MICROWAVES +
 FRIDGE FREEZERS.**

**TEL: NOTTINGHAM 0602-500002
 LONDON 081-568 8182**

WE DELIVER ALL AREAS!



**PHONE
 FOR DETAILS**



TX90 REMOTE PANEL IC TMS1000 AND M293 £12 LNB's WITH FEED HORN AND POLARIZER 10GHz to 12.75GHz 1.5 db s.n. £35. SEND FOR DATA.		SATELLITE RECEIVERS 19 C.H. with Hand Set £40 32 C.H. Postage £5.00		SEND FOR DATA D2 MAC SATELLITE RECEIVER, LNB AND DISH. £50 (£10 Post) PHILIPS STEREO HEADPHONE £4.00 PHILIPS C.D. MECH. 691-30212 £19.00	
JUST SPRAY AND IT IS CLEAN. PHILIPS' NEW VIDEO HEAD SPRAY CLEANER: £2.10 OR 10 FOR £1.50 EACH		60cm SATELLITE DISH £35 Postage £5.00		REPLACES 90% of Philips Handsets Philips Video R1/V Handset AV5661 with LCD AV5659 display £6	
SMALL SATELLITE TUNERS (950 to 1750 MHz). L.F. frequency 400MHz.....£9.00 each VHF/UHF S.BAND TUNER.....£3.00 NEW PLASTIC CASE 32 C.H. SAT-RECEIVER (no hand set).....£35 (Post £5) NEW METAL CASE SAT-RECEIVER, 32 C.H. WITH DOLBY B & CHANNEL C (no hand set).....£35 (Post £5) DAM MAINS CHASSIS AMSTRAD MONITOR C.....£10 UNIVERSAL TRIPLER, NEW TYPE.....£4.00 VIDEO LEADS.....80p AMSTRAD Line O.P. Transistors with Diode 2SD/453.....£1.00 BU208A.....£1.00 VIDEO LAMPS, Long Lead.....24p HITCHHIK & GEC FRAME, Thick Film.....£6.00 FIDELITY SPLIT DIODE FCC2215AE.....£20 FCC2015BE.....£10 FCC2215BE.....£10 K30 FRONT PANEL TEL. TEX TYPE.....£5.00 NEW G11 LINE OP PANEL.....£8.00		CAMCORDER SANYO NP22 6v 1300mah Rechargeable Battery Pack £6.00		PH500 Panic and Button Transmitter 180MHz.....£1.00 G11 CAP 250V, 470M.....£1.35 NEW PROFESSIONAL SATELLITE RECEIVER WITH HAND SET, METAL CASE WITH METER, DOLBY CHANNEL C WITH POLARIZER SUPPLY £50 £5 post SEND FOR DATA AND PHOTO	
PHILIPS YEARS AHEAD THE CREDIT CARD CALCULATOR Solar Powered.....£3.75 NEW PHILIPS SBC 1833 Solar & Battery Powered Calculator.....£8.00 THORN PANEL TX9 REC & REMOTE PANELS with Mains Trans.....£5.00 TX10 REC & REMOTE PANELS with Mains Trans.....£5.00 TX100 FRONT PANEL.....£5.00 TX100 TUBE BASE ON PANEL.....£3.00 TX9IF.....£2.00 THORN PANEL NoS15-35A, 548,02, 564,01, 509/102, 515/173, 508/161.....£5.00 THORN TX STEREO SOUND O.P. PANEL (I.C. TA7277P).....£1.00 THORN VIDEO AERIAL AMP 01 M4-597401.....£6.00 ULTRASONIC TRANSDUCER.....15p IN LINE 12-35 VOLT SUPPRESSOR 4.000 MRD.....20p		COMPUFILTER £12 13 Amp Sockets on distribution box with filters, plug and lead (3 Amp per socket)		Gas Soldering Irons Variety Nickel Cadmium Batteries from Telephone Type to Sub-C.50p per cell. Mainly in packs of 6 to 8. SPECIAL PRICE £8.00 AUTO RANGE DC and AC and Resistance Pocket 3000 Philips.....£12.00 G11 8 Touch Button with Lamps, Non-remote Philips New Hand Set Digital RC5991 fit all Text Sets after G11.....£18.00 £12.50	
KT3-K30-K4-K40 CTA ET C Mains Switch.....75p each G11 LOPTS.....£3.00 PHILIPS DESK TYPE Dual Power Calculator SHC1704.....£7.00 K40 FOCUS POT.....£1.00 4.7µ KT3 W/V.....5p FOCUS POT HDK TPA1000.....£2.00 KT3 Triplers.....£5.00 K3 Text Front Panels with I.C.s (SAA 3027P/SAB3013/ HO448328).....£5.00 G8 100K Pots on Panel & Lead for 6 Push Button Unit K30 Mains Switch remote.....£2.00 K35 Mains Switch remote.....75p K35 Aerial Socket and Plug in Lead to Tuner KT3-K30 Slider Pots 4.7µ.....20p each LARGE Focus Pots, Fits Pvc, GEC, I.T.T., Decca.....75p		Philips Stereo Headphones No. SBC 3140.....£4.00 144MHz Changed Over Relay Aerial.....50p 10mm THICKNESS SOLAR POWER RADIO WITH EARPHONES.....£2.00 TX9-TX100 FRONT PANEL £5 WITH REMOTE £10 NON REMOTE 8 push button £10		PHILIPS Desk Calculator.....£7.00 PHILIPS UNIVERSAL BATTERY TESTER SBC 1695.....£5.00 GEC 20AX POWER SUPPLY Mark 1 and 2.....£10.00 ONE I.C. K35 Decoder.....£10.00 REGULATED PWR. SUP. 500MA 1.5V-12V DC switched + & -.....£5.00 ITT Tuner & IF. Can HF-module 2 UK.....£20.00 KT3-K30 IF.....£5.00 STR5481.....£5.00 TX100 Push Button Unit 16 CH.....£10.00 WIRE PIPE stud detector.....£4.00 MICROWAVE leak detector.....£4.00 WIRE & PIPE detector.....£4.00 FERGUSON HAND SETS 10 for £5.00	
L.C.D DISPLAY LANGUAGE TRANSLATOR — ENGLISH, FRANÇAIS, DEUTSCH, ESPAÑOL, ITALIANO — £15 GLASS HEADS Diodes 200/1.2A.....50 for £1.00		MIXED TOSHIBA HAND SETS FIVE FOR £12		SECURITY FLASHING LIGHT WITH RED & AMBER LENSES & MAGNETIC FACILITIES £10.00 EACH DAMAGED AMSTRAD (640 Colour Monitor Chassis.....£6 + Post £3.	
G11 OPT Panel.....£4.00 G11 Tip Switch.....£20.00 G11 Decoder Panel.....£5.00 G8 Push Button Unit.....£2.00 G8 Conv/Panel New Back Type.....£4.00 Have you got Acid Rain in your garden? PH METER Video Power Supply for Amstrad. Last year model. Mains Transformer for Amstrad Video.....£5.00 £1.50 25p (£1.995) LATEST VIDEO For Latest Philips, GEC, Pye and Hitachi. Front panel with memory chip and bush button and pots and LEDs.....£6.00 NEW		TX100 FRONT PANEL £5 8 Button 100 OHM 20p Each S.W. Filters 1 OHM 50p Each SW 153.....SW 334 SW 154.....SW 179 SW 154.....SW 514 SW 508A.....SW 179 SW 153.....SW 153 SW 270.....SW 178 SW 303.....SW 701 SW 303.....SW 177 SW 203.....SW 453 SW 185A.....SW 630 SW 505.....SW 1453 SW 146.....SW 260 SW 453.....SW 2153 SW 174A.....		DECODER C-CAM PHILIP MADE for K40 CHASSIS IC No. TDA 3590 £8.00 EACH FIDELITY NON TEXT HAND SET for 3000 chassis. 8 button £5.00 56420A 20A/600V THYRISTOR.....£1.75 LCD VIDEO AMSTRAD HANDSET for models 1990 £8 each ITT BG2032-642A TRIPLER £5.00 ITTENOKIA RF IF MODULE £20 A M S T R A D 8600 VIDEO MAIN PANEL MODULATOR IF TUNER and ICs Damaged Panels £5.00 Model A1 to A33 SALORA & LUXOR 32 CH SATELLITE RECEIVERS No hand set £30.00 post £5	
MAINS TRANSFORMER 240v in/230v/8v.....£1.00 GREEN HIAT, NEC, LED's.....3p each 100 for 12 15V015V 1 Amp Print Type 12+12V 2.8VA Print 1X17 8+8V 1 Amp Print.....£1.00 £1.00 75p 75p ET596 UHF V/CAP Tuner, small FIDELITY Panels with I.C. FIDELITY LOPT Split Diode AT2076/80 AT 2076/280.....£2.50 £5.00 £5.00 SATELLITE TUNER UNIT 2427611.....£15.00 TX10 8 way button unit THORN TX90 Remote chassis 14" Complete.....£8.00 £12.00 MSHIFCP709.....£7.77		TX90 TO TX100 8 BUTTON UNIT £4.00		TELEPHONE EXT. LEAD 3 Metre.....30p LEAD SCART TO D PLUG.....£1 BRIDGES RECTIFIER Mixed BR.31 to 34 2 Amp to 5 Amp..... 8 for £1.00 TX90 MOD 3714B The Sweep Tuning System TX9139001.....£12.00 T6070V TX9 Transistor.....£1.00 VIDEO SCART TO SCART ALL PIN, LONG LEAD £3.00 ALL PINS TX90 TX925 TX100 Mains Switch with Stand-by and Lead.....50p each UNIVERSAL VIDEO-RECORD KIT STEREO This kit may also be used to connect a mono to stereo. £10.	
2433752 £20 2432984 2432971 2432301 2435016 2433952 2434393 2432211 T9048A 18T185B243 T90309D K4 L.O.P.T. K35 L.O.P.T. K40 2433452 2432984		SPLIT-DIODE 2433752 £20 TX100 Green Spot £15.00 TX100 Yellow Spot L.O.P.T. £10.00 TX91 White Spot L.O.P.T. £15.00 Split Diode 110P £12.50 Orion 65-3M G11 C85-9793-6 DST 81N243 TFB4023AD £10.00 MSHIFPT131 £12.00 MSHIFB27 £10.00 DST186N243 £10.00 36362 36482 36761 36831 36832 36833 3692179 3692279 L.O.P.T. SPLIT-DIODE PHILIPS £10 EACH		TRANSFORMERS 2435701 £10 2435012 £10 FERGUSON 47003481 £10 AT206600 AT2048/11 AT2095 AT2076/35 AT2076/38 AT2076/51 CVC 820 CVC 800 AT2076/55 AT2076/71T AT2084/15 RCU51 £13325 OT2041 FR165KA Orion 2076/51 2432401 2433451 SHARP MSHIFCP709 £10 EACH FTT MOST SETS New Thorn Hand Set Type u/v (£10) BRIDGE RECTIFIERS 10 FOR £1.00 4 Amp for Video Power Supply VIDEO MOTOR for V185 type VCO/D28.....£8.00 AMP TUNER IF for V1568 Hitachi & GEC.....£9.00	
SATELLITE TUNER 950MHz-1750MHz £5.00 TIT PANEL CMC 301 CMC 113 CMC 302 CMC 115 CMC 303 CMC 964 £5.00 VIDEO LEADS 4 for £1 SEL ITT IFB254F2 Front Panel £15.00 DECCA — GEC — ITT 6 push button £5.00		BURGLAR ALARM £2.00 with siren 9 VOLT RELAYS 35p 5V 12V-24V-48V Large and Small BUZZER 6 VOLT. Small 10P EACH		KIKUSYI 20 MHz OSCILLOSCOPE (5020) £200 40 MHz OSCILLOSCOPE (5042) £250 60 MHz OSCILLOSCOPE (7060A) £1000 ODELAY PROGRAMMABLE 12V/1 AMP POWER SUPPLY WITH MAINS PLUG £4 PHILIPS HALOGEN LIGHT. NEW. NO ON/OFF SWITCH. NO HANDLE WITH CORD. BLACK IN COLOUR £5 PHILIPS HAND SET G11 TEXT IN RED G11 HAND SET PHILIPS RC5 G11 TEXT ULTRASONIC £10 HAND SET £12.50 ULTRASONIC £10 EASY CONTROL £70 TRV3 Amstrad Cassette Mechanisms. New with 2 motors and sound head. £15. TVR3 Power Supply. £5. Amstrad Television Tuner UHF. Small. Fits most Amstrads. £6. SENDZ SEE BACK PAGE PHILIPS SBC 522 RGB1 GENERATOR £90 PHILIPS SBC 850 ANALOG MULTIMETER £11.50 PHILIPS SBC 520 L.F. FUNCTION £75.00 THORN TX 85 AND TX 96 CHASSIS £20.00 EACH FERGUSON ICC5 STEREO O.P. PANEL ICs TDA8405 TDA8421 THA1204 £10 Burglar Alarm Has time delay to set.....£2 Mains Transformer 240v In 110v to 120v out 1 amp post £3	
NEW 12" 90% MONO TUBES £10 4600 TO 8600 AMSTRAD VIDEO HAND SET WITH LCD £10 NICAM MKII KIT MODULE £20.00 with data					

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

LA11440 £1.00	K35 Decoder £8.00 K35 Sound OP £4.00 Thick Film Daughter Kit 33122-127-43891 £3.00	12 C11, K30 Tex Rec Front Panel with I.C. £5.00	K4 Focus Pot Plug in £1.00	Fidelity Tube Base with transistor & focus pot £1.50	Bush Tube Base on panel £1.00	TX10 Tube Base on Panel £3.00	1100 L.O.P.T., Green Spot TX100 Thorn £7.00	Universal Tripler with small focus pot, Green type £7.00	Black Triplers K13 Triplers £6.00 S.T.C. Universal Tripler ITT CVC 5-8-9 £3.50 Rank 125L-E Tripler Rank 11TCP A-823 £3.50 TU125 30K Rank £3.00 11 TEZ Rank £3.00 C9 Philips £4.80 GEC 2110 £4.00 3500 Thorn £3.00 8500 Thorn £4.00 9000 Thorn £7.00 9500 Thorn £4.50 9600 Thorn £4.00 2040 GEC £3.50 GEC TVM25 Tripler £2.00 Universal Tripler £5.00 G8 Tripler £5.00 CVC 20-32 £5.00 Decca 80100 £4.50 Grundig TVK 52 £2.50 ITTBO 19c 731 £3.00 ITTJY £4.00 D22 for Pyc 18" colour portable £4.00 LP 119363 £4.00 BG 10041 £3.25 ERO Tripler print type with foams P07 £5.00 BG2087 £5.00 T/Ext ultrasonic rec'r panel £14.00 12/14V 200 for £25.00 20 for £5.00	Thorn Spares 9000 Frame panel £8.00 9000 C neck panel £1.50 3 Way regulated adaptor 240V 6V/7.5V/30mA £3.50 Rank/Toshiba prech unit 0354 £9.50 4 Push button unit prech £1.00 6 Push button VHF/UHF for V/sep, GEC + Decu type £7.00 7 Push button for CVC's ITT £8.00 K13 12 Push button unit £2.00 K13 (Export) 12 P.B.U. £2.00 6 Push button Unit Thorn £1.00 6 Push button GRC £6.00 6 Push button PVE 731 £6.00 Hearing aid unit £3.00 Rank Z718-4 P/B Unit MECH £4.00 7 Button Unit GEC with Lamps £7.00 697 Push Button Unit £6.00 Z916B panel £5.00 T513AP panel £5.00	TT14 GEC TEX-DECODER 13 IC Panel with cable form £9.50	PHILIPS Decoder SAA IC 5020-5030 5040B-5050 £8.00	K40 Test Panel £8.00	FERGUSON TX85 CHASSIS £20.00 TX86 CHASSIS £20.00 TX96 CHASSIS £20.00	DIODES Bridge KBI-408 40p BY 126 10p BY 127 10p BY 133 10p BY 134 10p BY 176 25p BY 179 25p BY 184 25p BY 187 10p BY 190 40p BY 196 30p BY 198 10p BY 2044 8p BY 206 - BY 407 Eqy. 8p BY 208/80 8p BY 210/40 5p BY 210/80 10p BY 223 60p BY 224/60R 4.8A/600V bridge 60p BY 226 15p BY 227 15p BY 228 1500V 20p Flat BY 229 black 15p BY 229 Red 20p BY 229/40 30p BY 229/60p Tag 30p BY 229/80 30p BY 237 5p BY 254 10p BY 255 10p BY 298 10p BY 299 10p BY 406 8p BY 527 20p BY 407a 10p BY 448 10p HY 500/200 - 5 amp 8p BY 527 10p BY 602 10p BYW 26C 10p E247 10p GP20G 5p GR198KG (TX10) 30p XK 3102 20p BYW 26/200 50p Bridge TX10 800/5 amps 30p K13R 35-02 Bridge £1.50 Bridge Rec. D35B10 40p BY171800 12p	International Rectifier EHT Diodes G770/HV34 6KV 3 for 8p 6A/600V Stud Diodes 20p BTW 92/80/R £3.00 6A/1000V Stud Diodes 20p 25A473 PNP CP 10p	Voltage Regulators +5V/UA78POSSC 30p -8V/78M8c £30p +6V/78M06c 30p LM317T 30p LM337 30p LM342/18 30p LM340T 5.1 50p +12V/LM340T12 50p +18V/MC78M18 20p +24V/78M24 £30p MC 7724cp 40p MC 7824 40p	Power Supply for Sinclair Spectrum +2 £5.00	U 19885 40p U 3832 15p U 3845 15p MR 508 10p MR 501 10p MR 502 10p BCW 71R 30p BYF 1202 10p BYF 1204 10p BYF 3126 40p BYF 3214 40p BYX 10 10p BYX 36600 35p BYX 38300 25p BYX 49/600R 75p BYX 55/350 10p BYX 55/600 (Bead) 50p BYX 36600 10p BYV 95B 10p BYV 95C 12p BYV 96D 10p BYZ 106 10p BPW 41 15p BYW 56 2A/1000V G11 15p BYW 29/50 15p BYW 95C 10p BZU 15/24 54p BZY 93c75 50p BZW 15/18 30p BZW 15/30 10p BZW 70c6v2 10p BZW 79.3v 10p	Bush Thyristor RCA 76122 £1.00 Chassis type Transformer 240V/20v-500Ma 75p 240v/12V 500mA 75p CVC 20 tube base £2.00 Tube Base Rank & G11 £1.20	BRIDGES KBL005 30p KBL02 30p KBP04 30p WIK4 15p WIK5 20p 800V Bridges 2/2 Amp 30p	G11 Drawer ASS 3 pots Mans Switch and Lead £2.00	K30 Drawer Ass with pots cable forme £1.00	TX10 Drawer with 8 way pots ass £2.50	Hills 9 piece tool kit in case £5.00	Philips Coaxial Cable Stripper SBC325 £7.50	Self adjusting cutter stripper £5.00	10 mixed tube bars £4.00	5000 Diodes-Resistors £3.00 pack	*D/P push mains switch 20p each	Mains lead & two pin socket for radio cassette 35p	TV loop aerial 75p	Radio Telescopic Aerial £1.00	Philips Silicon Grease £1.50 each	Freeze Philips £1.50 each	Foam Cleaner Philips £1.50 each	Contact Cleaner Philips £1.50 each	100 Coax Plugs EACH 14p	Desolder pump + 2 nozzles Philips £4.00	Flat Red LED and Green 5p	50kgm 60/40 Solder reel £6.00	Dual vu meter -20 - +10db £1.00	K30 Thermistor 23226629800R 75p	Desolder Pump £2.50	Portasal Flameless Gas Soldering Iron £16.00	100 Mixed 20mm Fuses £2.50	Hill Meter Leads, S/Rubber and Probes £4.00	CV R617 10p Y 716 10p Y 729 30p Y 730 10p Y 827: 6A/1KV 20p Y 860 30p Y 933 5p Y 969 50p Y 997 30p Min 12 volt Relays R 1038 40p R 1039 40p R 2049 80p R 20106 £1.00 R 2029 50p R 2210 60p R 2257 60p R 2265 50p R 2305 50p R 2306 30p R 2322/2323 pair 15p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2433=BD124 50p R 2540 £2.00 R 2737 40p R 2738=TIP41 30p R 2775=TIP41c 40p R 3129=TIP47 40p T 6068V 50p R 4050 £1.00 S 2008b 80p 25DR98B £1.00 25C1942 £1.00	Hitachi sets etc. STR454 £2.00 STR620 Kit £6.00 S 200AF line o.p. £1.00 25C940 £1.00 BU 105/04 80p BU 108 10p BU 124 50p BU 126 80p BU 180A 60p BU 204 75p BU 205 75p BU 206 10p BU 207 £1.00 BU 208 10p BU 208A 75p BU 208D 90p BU 222 10p BU 326 £1.00 BU 407 60p BU 426A 45p BU 540 £1.00 BU 500D 10p BU 508A 90p BU 508AF £1.00 BU 508D 80p BU 508V £1.00 BU 705 £1.00 BU M66A £1.00 BU M07 £1.00 BU K24 50p BUT 11 50p BUT 13 600V-28A £1.00 BUW 11 50p BYW 20/8-9 60p BYW 95 10p BUX 39 25A-150V £1.00 BUX 84 50p BUX 85 50p BUX 49 20p TIC 106a 30p TIC 116m 30p TIC 116n/Y 1003 30p TIC 126N 30p TIC 225S 30p TIC 226E 30p TIC 226m 30p TIC 238m 30p TAG 226/600 30p TICV 106D 30p (TWO case 2A/400V) 10p TIP 29 25p TIP 30 25p TIP 30A 25p TIP 30B 25p TIP 30C 25p TIP 31 25p TIP 32 50p TIP 33B 50p TIP 33C 70p TIP 34A 50p TIP 34B 70p TIP 35B 70p TIP 35C 70p TIP 35D 80p TIP 36 50p TIP 36C 70p TIP 41 15p TIP 41B 40p TIP 41D 10p TIP 42 10p TIP 42/BRC 6109 10p TIP 48 40p TIP 49 30p TIP 57 30p TIP 101 30p TIP 102 30p TIP 110 20p TIP 115 50p TIP 117 50p TIP 125 35p TIP 126 30p TIP 127 30p TIP 130 40p TIP 131 60p TIP 136 50p TIP 140 50p TIP 142 80p TIP 640 35p TIP 645 75p TIP 761A-1000V/4Amp T6132 40p T6136 40p T6140 40p T6147 40p T6149 40p T6151 40p	Philips Handset IC £3.00 SAA301P £3.00 MAB8461/WO63 £3.00	MAB 8420P-C031 £3.00 MAB 8400B-6 £3.00 MAB 8440P-D070 £3.00 MAB 8440P-D033 £3.00 MAB 8440P-D056 £3.00 MAB 8441P-T001 £3.00 MAB 8441P-T132 £2.00	M58484F £2.00	Hand Sets - Fidelity £15.00 to £35.00	ITT 8 and 6 Push Button Pyc 725 L.O.P.T.s £1.00 Pyc 731 L.O.P.T.s £6.00 Thorn 8500-8800 L.O.P.T.s £5.00	CMC 301 front panel £5.00 CMC 303 front panel £5.00	CMC 302 Panel with TC mains switch etc £5.00	Tunable Satellite Modulator 5.5MHz MPPI 1000T 6.0MHz MPPI 1140 £4.00 each	Safe Block £5.00	6 Sub C/Nical Batteries £1.80	Ferguson TX85 TX86 Switch Mod Transformer £4.00	ICCS Ferguson Switch Mod Trans 3112-338-32642 £4.00	ICCS L.O.P.T. DST 884243 £10.00 each DST 884243	ICCS Remote I.C. CCUF RG07 £3.00 CCUF RG09 £5.00	Ferguson L.A.T.R Hand Set ICCS Mod £8.00	K13/K30 ITT Text £12.50 K13/K30 Full remote £15.00 K13 Power supply £4.00 GEC Infrared 2236-2026 £4.00 GEC 8 button full remote £14.00 GEC push pad handset button blips 10p each	Pyc & Philips handset K13-K30 chassis No. RC (5150-RC5176-RC5071-RC5177) Special Price £13.00 RC 4001 K13 and Teletex £14.00 IT CVC 32 handset repaired £15.00 CVC 32 Hand Set £15.00 CVC 45 3 and 2 Pin £12.50 TX10 Hand Set Text £12.50 TX9 with Text £2.00 TX10 Focus Pots £5.50	ITT TV & Video Processor, 1200 Type C10.00	PHILIPS UNIVERSAL HANDSET £12.00 RC5 K13 - K45 We have all parts for Philips Handsets	RC5353 £15.00 RC5301 £12.00 Philips RC5 £15.00	TEXT-TYPE Replace Hand Set for Philips K13-K30, K4 etc £12.50	THORN HANDSETS 9000 - 9600 - TX9 - TX10 - TX100 Text and Non-Text £10.00	PHILIPS RC5171 £12.00	K35-K4 HAND SET Repaired for £5.00
---------------	--	---	----------------------------	--	-------------------------------	-------------------------------	---	--	--	--	--	---	----------------------	--	---	--	--	---	---	---	---	--	--	---------------------------------------	--------------------------------------	---	--------------------------------------	--------------------------	----------------------------------	---------------------------------	--	--------------------	-------------------------------	-----------------------------------	---------------------------	---------------------------------	------------------------------------	-------------------------	---	---------------------------	-------------------------------	---------------------------------	---------------------------------	---------------------	--	----------------------------	---	--	--	---	---	---------------	---------------------------------------	---	--	--	---	------------------	-------------------------------	---	---	--	---	--	--	--	--	--	--	---	--	-----------------------	------------------------------------

